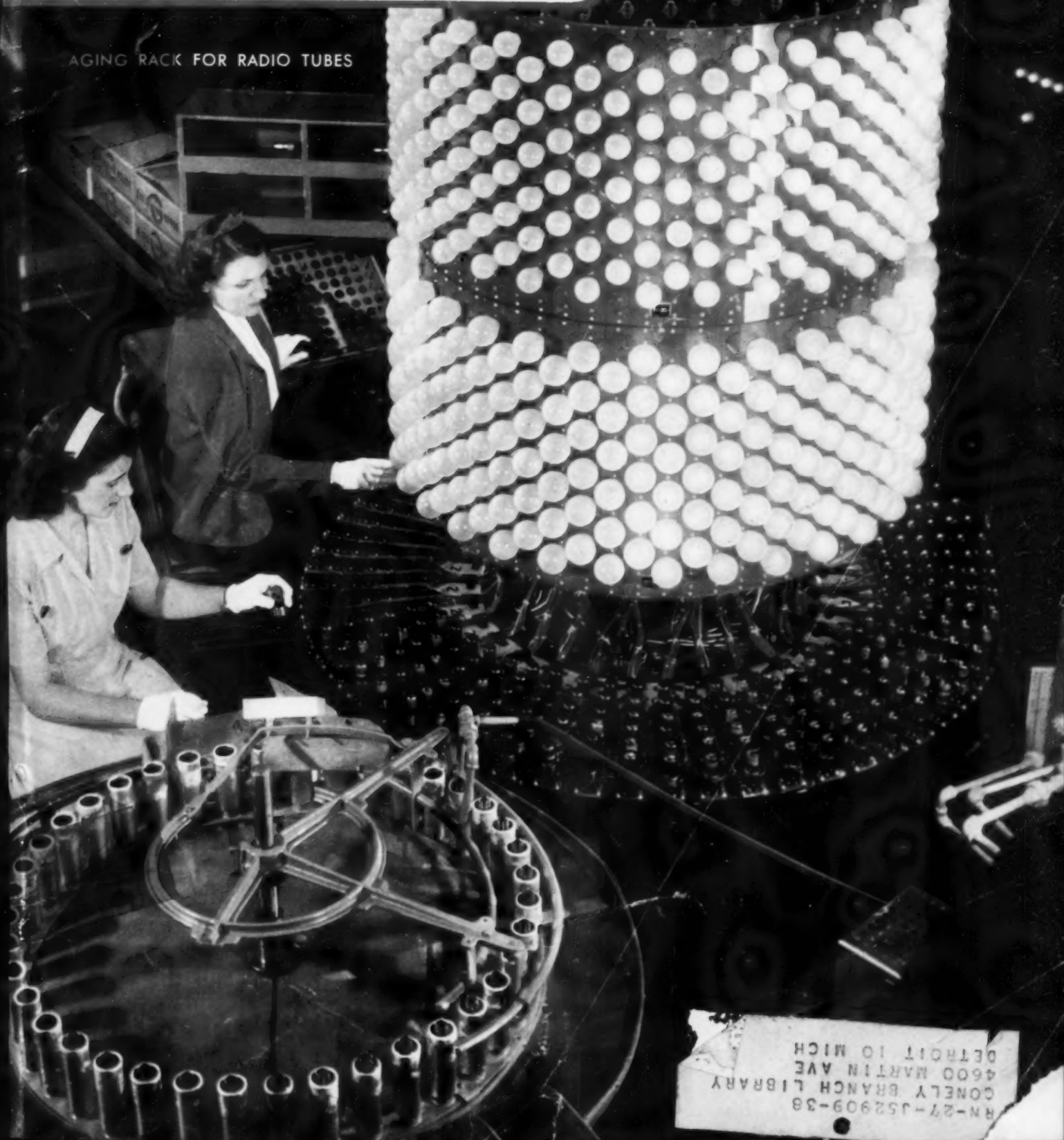


RADIO NEWS

DWIGHT F. CONELY BRANCH

DECEMBER
1947
35¢

AGING RACK FOR RADIO TUBES



RM-27-J52909-38
CONELY BRANCH LIBRARY
4600 MARTIN AVE
DETROIT 10 MICH

When you're glad
you have a
Snap-on

Snap-on
Octo-Grip
TRADE MARK
SCREW DRIVERS

● What a difference a good screw driver makes! But what makes a *good* screw driver . . . a Snap-on OCTO-GRIP screw driver? Nickel-molybdenum alloy steel blades, electrically heat treated to give the correct combination of toughness and hardness . . . tested hard-tempered tips, precision ground and shaped to prevent "chewing" and breakage . . . easily grasped, OCTO-GRIP plastic handles, non-rolling and shock-proof . . . balanced design that insures deftness, sureness and speed under all working conditions. These are the "musts" in a really good screw driver . . . and they are in every Snap-on OCTO-GRIP driver you buy.

Snap-on also makes other fine screw drivers . . . more than 75 different models, including Phillips screw drivers in both one piece and detachable head models, Reed & Prince drivers, offset and hammer head and spark testing drivers . . . in fact, every type of screw driver required for

radio maintenance and service. Snap-on screw drivers, like Snap-on's 4,000 other tools, are available

through nationwide direct-to-user tool service. "Ask your Snap-on man", or write for information.


SNAP-ON TOOLS CORPORATION
8120-L 28th AVENUE • KENOSHA, WISCONSIN
International Division: Kenosha, Wisconsin, U. S. A.





I BROKE INTO RADIO BY PRACTICING IN SPARE TIME WITH THE BIG KITS FROM N.R.I.

HOBERT HEAD

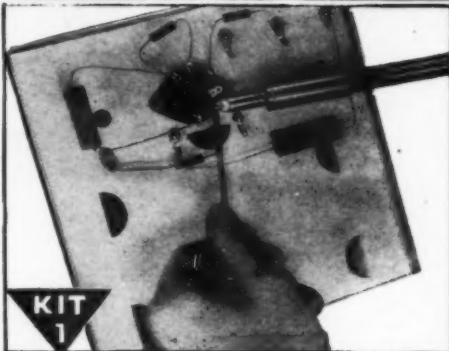


KIT 1

N.R.I. sends you Soldering Equipment and Radio parts; shows you how to do Radio soldering; how to mount and connect Radio parts; gives you practical experience.




KIT 2

Early in the course you build this Tester with parts N.R.I. sends. It soon helps you fix neighborhood Radios and earn EXTRA money in spare time.

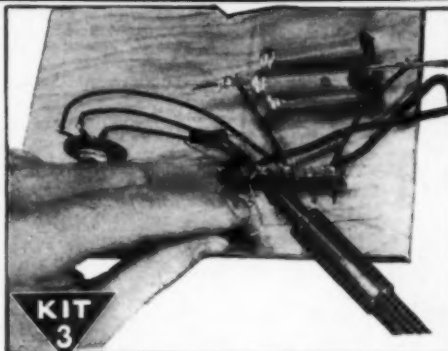


KIT 3

You get parts to build Radio Circuits; then test them; see how they work, learn how to design special circuits; how to locate and repair circuit defects.

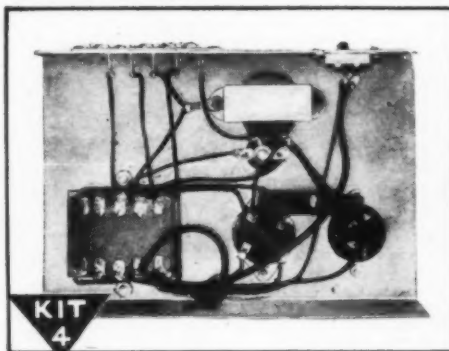


KIT 4

You get parts to build this Vacuum Tube Power Pack; make changes which give you experience with packs of many kinds; learn to correct power pack troubles.

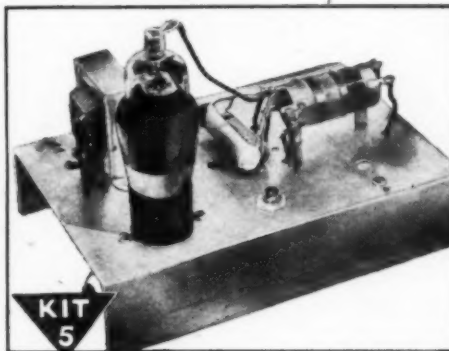

KIT 5

Building this A.M. Signal Generator gives you more valuable experience. It provides amplitude-modulated signals for many tests and experiments.

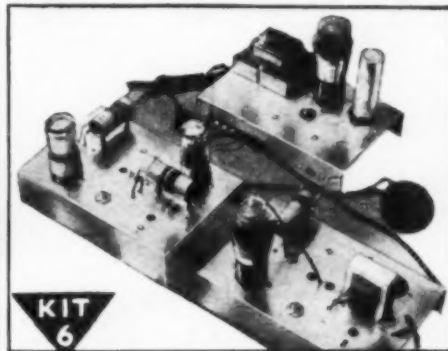

KIT 6

You build this Superheterodyne Receiver which brings in local and distant stations—and gives you more experience to help you win success in Radio.

LEARN RADIO by Practicing in Spare Time

Do you want a good-pay job in Radio—or your own money-making Radio Shop? Mail Coupon for a FREE Sample Lesson and my FREE 64-page book, "How to Be a Success in RADIO—Television, Electronics." See how N.R.I. gives you practical Radio experience at home—building, testing, repairing Radios with BIG KITS OF PARTS I send!

Many Beginners Soon Make Good Extra Money in Spare Time While Learning

The day you enroll I start sending EXTRA MONEY manuals. You LEARN Radio principles from my easy-to-grasp, illustrated lessons—PRACTICE what you learn with parts I send—USE your knowledge to make EXTRA money fixing neighbors' Radios in spare time while still learning! From here it's a short step to your own full-time Radio Shop or a good Radio job!

VETERANS

You can get this training right in your own home under G. I. Bill. Mail coupon for full details.

Future for Trained Men Is Bright in Radio, Television, Electronics

It's probably easier to get started in Radio now than ever before because the Radio Repair business is booming. Trained Radio Technicians also find profitable opportunities in Police, Aviation, Marine Radio, Broadcasting, Radio Manufacturing, Public Address work. Think of even greater opportunities as Television and Electronics become available to the public! Send for free books now!

Our 33rd Year of Training Men for Success in Radio

My training includes TELEVISION • ELECTRONICS • F M

Good for Both—FREE

Mr. J. E. SMITH, President, Dept. 7NR National Radio Institute, Washington 9, D. C.

Mail me FREE, without obligation, Sample Lesson and 64-page book about how to win success in Radio—Television, Electronics. (No salesman will call. Please write plainly.)

Age.....

Name.....

Address.....

City..... State.....


(Please include Post Office zone number)



APPROVED FOR TRAINING UNDER GI BILL

Editor
OLIVER READ, WSETI
Managing Editor
WM. A. STOCKLIN
Technical Editor
H. S. RENNE, EX-WOPTS
Associate Editors
RAY FRANK, W9JU
FRED HAMLIN
NORMAN L. CHALFIN
GAYTHE LITTELL
P. B. HOEFER
C. M. SULLIVAN
Staff Photographer
ARTHUR E. HAUG
Staff Artist
R. S. KUPJACK

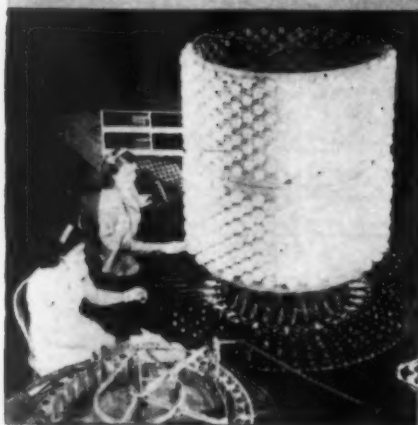Advertising Manager
L. L. OSTEN
Midwestern Advertising Manager
JOHN A. RONAN, JR.
Art Director
HERMAN R. BOLLIN



COVER PHOTO: Tube aging rack at Hytron's Newburyport plant. An incandescent lamp, acting as a current limiting resistor, is in series with each tube element. This final seasoning and degassification operation results in the processing of more uniform radio tubes. (Photo by Steinhard)

Chairman of the Board and Publisher
WILLIAM B. ZIFF
President
B. G. DAVIS
Secretary-Treasurer
ARTHUR T. PULLEN
Vice-Presidents
GEORGE BERNER
Advertising and Sales Director
MICHAEL H. FROELICH
Editorial Director
H. J. MORGANROTH
Production Director
H. G. STRONG
Circulation Director
BRANCH OFFICES
NEW YORK (1)
 Empire State Bldg., W17-0400
Manager, Eastern Division
CHARLES R. TIGHE
LOS ANGELES (14)
 815 S. Hill St., Ucker 9213
Manager, Western Division
WILLIAM L. PINNEY
TORONTO
 21 King Street, East
ASSOCIATED COMPANIES
 Ziff Davis, Ltd., Grafton Bldg.
 Western Gate, London, England
 Ziff-Davis-Patel, Ltd.
 190 Hornby Road, Bombay, India

RADIO NEWS

First in radio-electronics

Average Paid Circulation over 148,000

Reg. U. S. Pat. Off.

DECEMBER, 1947

FOR THE SERVICEMAN-DEALER

Publicity Means Sales.....	Philip Lesly	43
Television Installation (Part 4).....	W. W. Waye	52
10.7 mc. I.F. Transformers.....	J. C. Michalowicz	55
New AM-FM Signal Generator.....	Guy Dexter	58
Practical Radio Course.....	Alfred A. Ghirardi	68
Don't Be a Dagwood.....		100

FOR THE AMATEUR

Beginners' Traffic Transmitter.....	A. E. Hayes, Jr., W3LVY	46
Build Your Own Automatic Key.....	G. W. Gunkel, W6NMS	51
Miniature Ten Meter Phone Transmitter.....	Donald R. Rhodes, W6UVY/8	60
A Compact E.C.O. Controlled Transmitter.....	Harry R. Hyder, W2LIW	62

OF GENERAL INTEREST

Television Tubes by the Thousands.....	Frank E. Butler	39
Electronic Photoflash Unit.....	W. G. Many	44
The Recording and Reproduction of Sound (Part 10).....	Oliver Read	48
An Experiment in Voice Controlled Relays.....	Leon A. Wortman	56
Hands That See.....		66

DEPARTMENTS

For the Record.....	The Editor	8	What's New in Radio.....	86
Spot Radio News.....	Fred Hamlin	18	Technical Books.....	164
Within the Industry.....		28	Manufacturer's Literature.....	166
Short-Wave.....	K. R. Boord	65	New Receivers.....	180
RN Circuit Page.....		82	Letters from Our Readers.....	184



COPYRIGHT 1947
 ZIFF-DAVIS PUBLISHING COMPANY
 185 North Wabash Ave., Chicago 1, Ill.
 VOLUME 38 • NUMBER 6



Member
 Audit Bureau of
 Circulations

RADIO NEWS is published monthly by the Ziff-Davis Publishing Company, 185 N. Wabash Ave., Chicago 1, Ill. Subscription Rates: in U. S. and Canada \$4.00 (12 issues), single copies 35 cents; in Mexico, South and Central America, and U.S. Possessions, \$4.00 (12 issues); in British Empire, \$5.00 (12 issues)—all other foreign countries \$5.00 (12 issues). Subscribers should allow at least 2 weeks for change of address. All communications about subscriptions should be addressed to: Director of Circulation, 185 N. Wabash Ave., Chicago 1, Ill. Entered as second class matter March 9, 1938, at the Post Office, Chicago, Illinois, under the Act of March 3, 1879. Entered as second class matter at the Post Office Dept., Ottawa, Canada. Contributors should retain a copy of contributions and include return postage. Contributions will be handled with reasonable care but this magazine assumes no responsibility for their safety. Accepted material is subject to whatever revisions and by-line changes that are necessary. Payment made at our current rates, covers all authors', contributors', or contestants' rights, title, and interest in and to accepted material, including photographs and drawings.

RADIO NEWS

"THE hottest ham performance ever at this price . . ." That's the verdict of amateurs who have had a chance to try Hallicrafters new Model SX-43.

This new member of the Hallicrafters line offers continuous coverage from 540 kilocycles to 55 megacycles and has an additional band from 88 to 108 megacycles. AM reception is provided on all bands, except band 6, CW on the four lower bands and FM on frequencies above 44 megacycles. In the band of 44 to 55 Mc., wide band FM or narrow band AM just right for narrow band FM reception is provided.

One stage of high gain tuned RF and a type 7F8 dual triode converter assure an exceptionally good signal-to-noise ratio. Image ratio on the AM channel on band 5 (44 to 55 Mc.) is excellent as the receiver is used as a double superheterodyne. The new Hallicrafters dual IF transformers provide a 455 kilocycle IF channel for operating frequencies below 44 megacycles and a 10.7 megacycle IF channel for the VHF bands. Two IF stages are used on the four lower bands and a third stage is added above 44 megacycles. Switching of IF frequencies is automatic. The separate electrical bandspread dial is calibrated for the amateur 3.5, 7, 14, and 28 megacycle bands.

Every important feature for excellent communications receiver performance is included.

Model **SX-43**



\$169⁵⁰


FEATURES FOUND IN NO OTHER RECEIVER AT THIS PRICE

- ALL ESSENTIAL AMATEUR FREQUENCIES FROM 540 kc to 108 MC
- AM - FM - CW RECEPTION
- IN BAND OF 44 TO 55 MC: WIDE BAND FM OR NARROW BAND AM . . . JUST RIGHT FOR NARROW BAND FM RECEPTION
- CRYSTAL FILTER AND EXPANDING IF CHANNEL PROVIDE 4 VARIATIONS OF SELECTIVITY ON LOWER BANDS
- SERIES TYPE NOISE LIMITER
- TEMPERATURE COMPENSATION FOR FREEDOM FROM DRIFT
- PERMEABILITY ADJUSTED "MICROSET" INDUCTANCES IN THE RF CIRCUITS
- SEPARATE RF AND AF GAIN CONTROLS
- EXCEPTIONALLY GOOD SIGNAL-TO-NOISE RATIO
- SEPARATE ELECTRICAL BANDSPREAD CALIBRATED FOR THE AMATEUR 3.5, 7, 14 AND 28 Mc BANDS

BUILDERS OF

Skyfone

AVIATION RADIOTELEPHONE

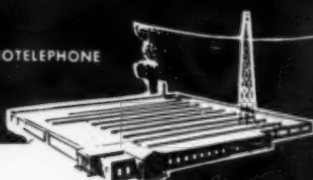

hallicrafters RADIO

THE HALLICTRAFTERS CO., MANUFACTURERS OF RADIO AND ELECTRONIC EQUIPMENT, CHICAGO 16, U. S. A.
Sole Hallicrafters Representatives in Canada: Rogers Majestic Limited, Toronto-Montreal



AUDIO TRANSFORMERS for [UNIFORM RESPONSE LOW DISTORTION

IN 3 FREQUENCY RANGES

*Write for Catalog
showing complete
new stock line*


Full Frequency Range

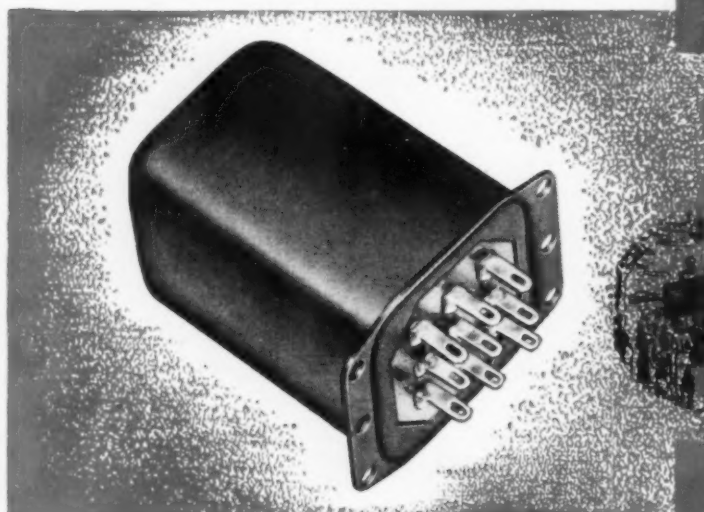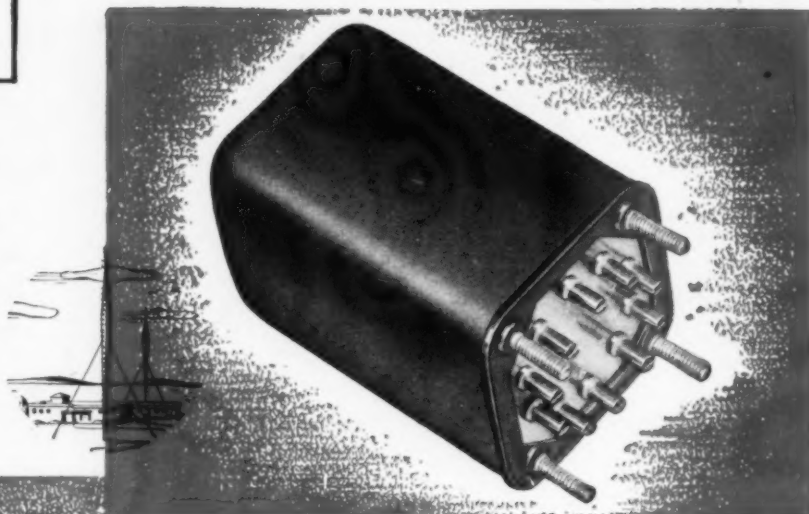30 to 15,000 Cycles, provides uniform response over this entire band with $\pm 1/2$ db up to 10 watts of audio power, within ± 1 db over 10 watts. Standard RMA impedances. Hum balancing coil structures and nickel alloy shielding. Included are Input, Output, Driver, and Modulation Transformers; Modulation Reactors. *Sealed in Steel* construction, stud mounting, with pin-type terminals.




Public Address Range

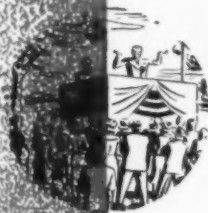50 to 10,000 Cycles, frequency response within $\pm 1/2$ db up to 10 watts of power, within ± 1 db over 10 watts, throughout this range. Secondary impedances match 600 and 150-ohm lines, 16, 8 and 4-ohm reproducing systems. Listed are Driver and Output Transformers. *Sealed in Steel* construction, flange mounting, with solder lugs or wire leads.



Communications Range

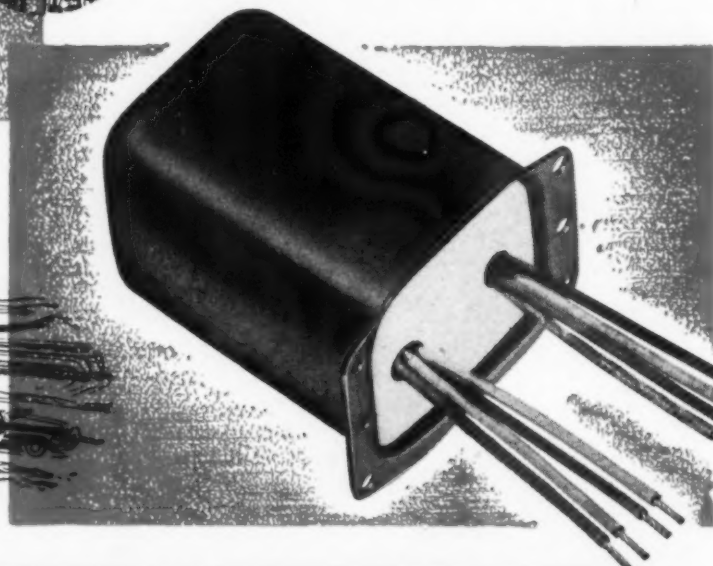200 to 3,500 Cycles, affords response with variations not exceeding ± 1 db over the range of voice frequencies. For use with 600 or 150-ohm lines. Input, Output, Driver and Modulation Transformers offered. *Sealed in Steel* construction, flange mounting, with wire leads or solder lugs.



CHICAGO TRANSFORMER

DIVISION OF ESSEX WIRE CORPORATION


3501 ADDISON STREET • CHICAGO 18, ILLINOIS



**I Put You to Work with Your Hands to LEARN RADIO!
You Build Receivers! You Make Typical Defects Occur
and Make Tests to Prove the Theory!**

**YOU GET
8 BIG KITS OF RADIO
PARTS & EQUIPMENT
including
2-BAND SUPER
RECEIVER!
and 16 RANGE METER
FOR TESTING**

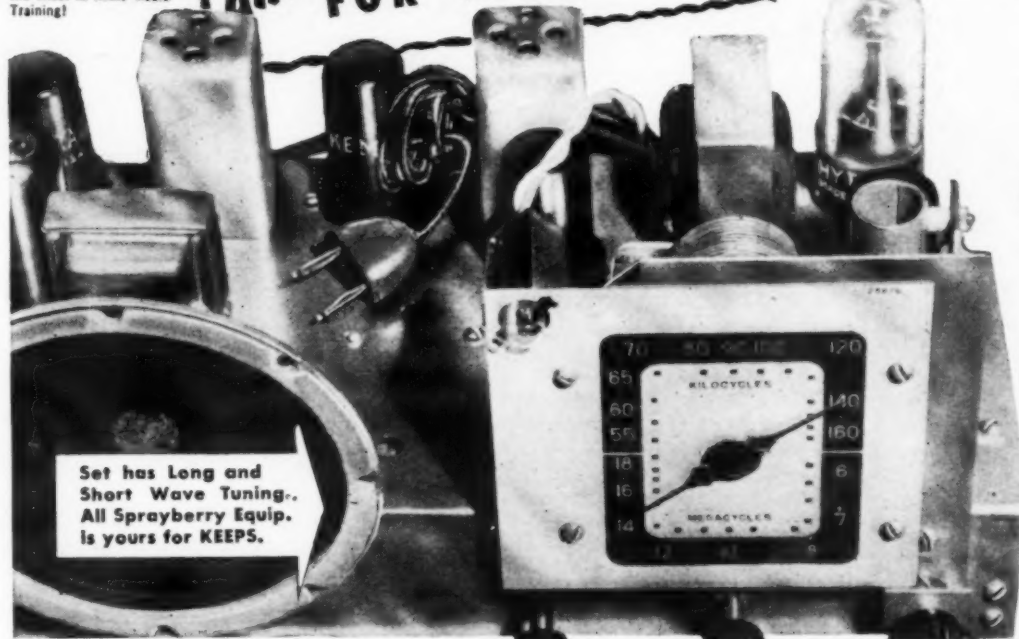F. L. SPRAYBERRY, PRES-
IDENT of the SPRAYBERRY
ACADEMY OF RADIO. This
is the man who directs
your study. His years of
experience and Radio
"know-how" assure you of
the finest in home Radio
Training!



Set has Long and
Short Wave Tuning..
All Sprayberry Equip.
is yours for KEEPS.

**LEARN RADIO
to MAKE MONEY!**


LOW COST TRAINING — EASY PAYMENT PLAN!

**You Learn at Home How to
Build and Test Dozens and
Dozens of Circuits — Simple
and Complex!**

**YOU DO
OVER 175
INSTRUCTIVE
EXPERIMENTS**




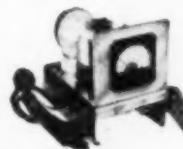
**YOU BUILD
ALL THESE TESTERS
..... AND MORE!**



I give you a fine,
moving-coil type
Meter Instrument
on Jewel Bearings
— with parts for a
complete Analyzer
Circuit Continuity
Tester. You learn
how to check and
correct Receiver
accuracy.

defects with professional speed and accuracy.

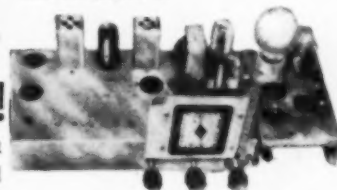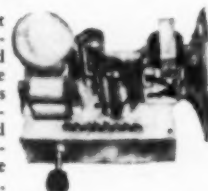You'll get
valuable ex-
perience and
practice
building this
Signal Gen-
erator and
multi-
purpose
Tester. Makes
a breeze out of fixing Radios and you
don't have to spend money on ready-
made Equipment.




Soldering, wiring, connecting Radio
parts . . . building circuits with your
own hands — you can't beat this
method of learning. When you con-
struct this Rectifier and Filter, Re-
sistor and Condenser Tester, etc., you
get a really practical slant on Radio
that leads to a money-making future.

SPRAYBERRY HOME TRAINING is PLANNED to MAKE MONEY for you FAST!

I train you with regular professional Radio Equip-
ment. I tell you exactly what to do . . . how to do
it. You handle Radio Parts, see them operate,
learn what they're for. With the fine Kits I supply,
you learn how to build Radio Circuits, construct
your own Test Equipment. I'll show you how to
cause typical Radio defects so you can watch and
see how they act. You learn the latest methods for
trouble-shooting and repair. All this adds up to

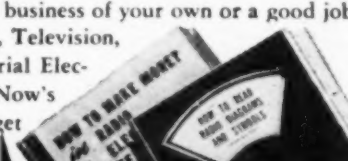the finest kind of "bench" experience. And you get
it right in your own home. In no time at all, you'll
be ready for a business of your own or a good job
in Radio, FM, Television,
Radar, Industrial Elec-
tronics, etc. Now's
the time to get
started!



VETERANS!

Approved for
G.I. Training
Under Public
Law 346.
Mail Coupon
for Full
Details.

**SEND FOR MY
VALUABLE
FREE BOOKS!**

"How To Read Radio Diagrams and Symbols"

A wonderfully complete new book, which explains
in simple English how to read and understand any
Radio Set Diagram. Includes translation of all
Radio symbols. Send for this volume at once! It's
free! With it I'll send you another Big Free Book,
describing in detail my Radio Electronic Training!

SPRAYBERRY ACADEMY OF RADIO. F. L. Sprayberry, President
Room 25127, Pueblo, Colorado

Please rush my FREE copies of "How to MAKE MONEY in RADIO, ELEC-
TRONICS and TELEVISION" and "How to READ RADIO DIAGRAMS and
SYMBOLS."

☐ Check here if a veteran.

Name _____ Age _____

Address _____


City _____ State _____

(Mail in envelope or paste on penny postcard)

December, 1947

TRANSVISION

7" TELEVISION KIT with COMPLETE FM RADIO

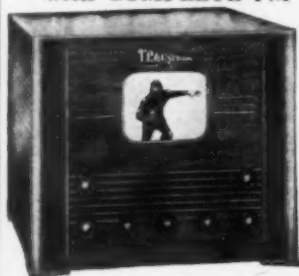

COVERS
ENTIRE
FM BAND

(87.5 TO
108.5 MC)

TRANSVISION 7" De Luxe Television Kit with FM Radio Receiver. Easy to assemble; no technical knowledge required. 18 tubes and picture tube. Folded Dipole Antenna and 60 ft. low-loss lead in cable. List \$199.00
7" Standard Television Kit. List \$169.00
Table Model Cabinets for above. List \$ 32.50
10" CONVERSION KIT with 10" Electrostatic Tube and Directions. Converts any 7" Television Kit to 10" size. List 69.00
Also 10" STANDARD TELEVISION KIT. List \$239.00
Table model cabinet. List \$35.00

Transvision Picture Blow-Up Lens

Brilliantly enlarges any 7" television picture to equivalent picture of 10" television set.


Has adapter arrangement for Transvision Panels and cabinets. Optically ground and polished to high accuracy. Plastic gives 50% greater light transmission than equivalent glass lens



. List \$19.95

Transvision 8-Tube FM Radio Receiver

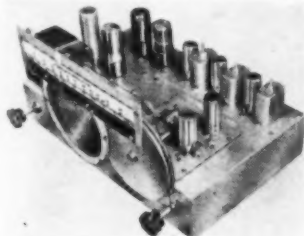Covers entire FM Band (87.5 to 108.5 mc).



No technical knowledge required for assembly. Makes an FM Radio Receiver worth 2 to 3 times cost of kit. **Model FM-1 8-tube FM Radio Receiver Kit** with 10" Speaker and Tubes. List \$64.95
FM CONVERSION KIT enables you to incorporate a complete FM Radio into your present television receiver. List \$29.95

HIGH-FIDELITY FM TUNERS

Model FMF-2 . . . 2-tube Tuner Front End (less tubes). List \$21.65
Model FMF-3 . . . 3-tube Tuner Front End (less tubes). List \$30.75
Model FM-107R . . . 3-tube IF Amplifier Kit (less tubes). List \$21.65
Model FM-107 . . . 6-tube IF Amplifier Kit (less tubes). List \$41.20

All prices fair traded. . . . All prices 5% higher west of the Mississippi River.

See your local distributor, or for further information write to:

TRANSVISION, INC. DEPT. R. N.
 385 North Ave. New Rochelle, N. Y.

For the RECORD.

• BY THE EDITOR

IT SEEMS that every once in a while some newspaper or national magazine is sold a bill of goods on something which will radically affect the techniques employed in modern radio and electronic equipment servicing.

The latest is the "cure-all" receiver described and illustrated in the September, 8th issue of *LIFE Magazine*. The article bears the title "Repair-It-Yourself Radio." The main reason for publishing the article seems to be the following: "It will also be watched with dismay by those radio repairmen who have relied on the customer's ignorance of electronics to foist huge repair bills on him."

The above seems to imply that many radio repairmen are, and have been, charging excessive prices for their work and that the average service technician is being driven around by a chauffeur as he collects exorbitant fees for his "know how." After reading the article, Mr. Set Owner thinks that at long last there is a streamlined solution to his radio repair problems. All he has to do is to take this new receiver to his local serviceman, reach for a spare replacement stage, plug it in with ease and come away with the deep satisfaction that comes with a newly discovered knowledge of having outsmarted a long established technician.

So much for the picture as it is painted. What about the reality involved? First of all Mr. Radio Serviceman is too busy to stand around while Mr. Joe Doakes goes about the task of substituting components until he finds one that will once again give him good performance. During this juggling process Mr. Technician must keep his eye on the customer in order that he does not tear the pins off the connectors or otherwise damage new parts for which he has invested a considerable sum. Suppose that the customer does finally hit the jackpot in finding a workable combination. That brings us to the matter of correct alignment of circuits. Is the customer going to do that? As he gloats in his success at being able to get the set operating, he will of course muster up a lot of courage and accordingly request the use of the technician's equipment (under proper instructions, of course,) for free.

As the clock ticks on, Mr. Technician mentally adds up the comparative time costs involved in servicing a conventional or equivalent receiver. He finds it a fact that not only has the customer wasted his own time, as well as the technician's, but he is still not assured of a satisfactory repair job.

Next comes the possibility, or should we say probability, that one of the

tubes has gone west. If it has, it would be a bit embarrassing to the customer to discover this. Chances are he would blame the serviceman for not "briefing" him when first he came into the shop with his "cure-all." He might even expect that a new tube was part of the package inasmuch as it was associated with the particular unit that he had discovered was on the fritz.

If the "cure-all" customer failed to locate the defective unit, he would be the first to put the blame squarely on the shoulders of the dealer simply because he's the guy that sold him the stuff in the first place and, therefore, it is up to him to keep him as a satisfied customer. We just can't see where the profit on a \$1.85 item can offset the time that might well be involved in re-checking the receiver and advising and explaining the procedures involved to the customer in an attempt to maintain his good will. It doesn't make sense.

The article does not reveal that changing tubes usually requires a bit of realignment on a receiver for proper reception. In fact, the article does little, if anything, to give a realistic viewpoint on the subject. Radio servicing involves a great amount of skill. Without skill it is impossible to correctly maintain a modern radio.

In the case of FM and television sets which are far more difficult to handle than prewar sets, we fail to see where the customer would even be willing to haul such equipment to a repair shop, even though he had an urge to do the repair job himself.

Have you ever seen an owner haul his washing machine down to the dealer so that he could try out various replacement wringers until he found one that would work like the original? Have you ever seen Mrs. Smith bring in a burned out toaster and proceed to try out different heater elements? Have you ever seen an owner of a vacuum cleaner take it down to a repair shop to try out a new motor? Of course not. And isn't it ridiculous to expect an American set owner to do likewise? We personally don't feel that the public at large will accept this "cure-all" service technique for their radios. And how many radiomen would support such nonsense, especially after being tagged as a scoundrel.

We have long been pioneering for improvements in radio servicing techniques and it is not our intention to pull in on the reins of progress in this field. What we do object to is the publication of a so-called "workable" plan that scoops the experts—but is full of loopholes. O. R.

There's Only One Complete Radio Buying Guide!


It's **ALLIED'S 164-PAGE**
RADIO CATALOG — *Get It!*

FREE



Everything in Radio At Lowest Prices!

Get your copy of this big **COMPLETE** book **NOW!** It's the preferred Buying Guide to everything in radio and electronic equipment for the serviceman, engineer, ham, short-wave listener, builder and experimenter. Keeps you up-to-date on the latest equipment. Saves you money on every order. Make **ALLIED** your Radio Headquarters—it's the established, dependable supply source for America's radio men. Write for the 164-page **ALLIED** Catalog today!

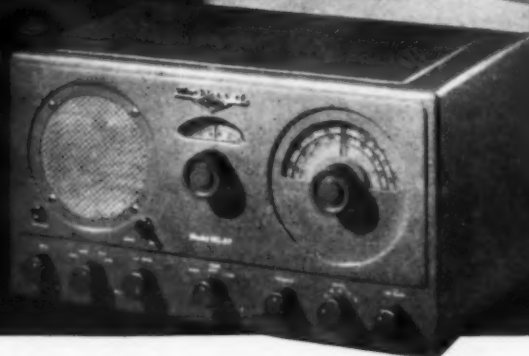

HALLICRAFTERS SX-43

The new SX-43 gives you more value—greater performance, broader frequency coverage (550 Kc. to 55 Mc. and 88-108 Mc.)—a fine investment in the medium price range. AM-FM-CW reception, Crystal filter, calibrated main and bandspread dials, variable tone control, precision-engineered for custom-built performance! Tops for the Ham or Short Wave Listener.

NET.....**\$169.50**



NATIONAL HRO-7

Newest model in the world-famous, dependable HRO line—a remarkable performer under any receiving conditions. Features modern styling, voltage-regulated 6C4 oscillator, double-action type variable noise limiter, tone control, accessory power take-off, separate power supply for 110-220 v. AC operation. Complete with tubes and power supply. Less speaker.

NET.....**\$299.36**

ORDER YOUR NEW COMMUNICATIONS RECEIVER FROM ALLIED TODAY!... The New **NATIONAL NC-57**—We Have It!

Here is the new, completely modern receiver Hams and SWL's have been waiting for—designed for maximum performance at a moderate price. The National NC-57 features extended frequency range, tuning 550 Kc. to 56 Mc., continuous in 5 bands. Has electrical bandspread for pinpoint tuning on SW and Amateur bands. Features include: Accurate calibration on all bands; automatic noise limiter; antenna trimmer; voltage-regulated RF, Oscillator and BFO; Loktal tubes in RF circuits for maximum efficiency at high frequencies; universal antenna input; emergency battery-power socket; built-in 6" dynamic speaker; 3-position tone control; BFO pitch control; 1 RF and 2 IF stages. 7 tubes plus VR tube and rectifier. An outstanding receiver guaranteeing fine performance at an amazingly low price.

NET, Complete.....**\$89.50**

Other Communications Receivers

National NC-173 & Spkr.....	\$189.50	Hammarlund SPC-400X	
National NC-2-40D.....	225.00	& Speaker.....	\$398.25
National NC-46 & Spkr....	107.40	Hammarlund HQ-129X	
Hallicrafters SX-42.....	275.00	& Speaker.....	189.15
Hallicrafters S-38.....	47.50	RME-84.....	98.70
Hallicrafters S-40A.....	89.50	RME-45 & Speaker.....	198.70
Hallicrafters S-47		RMEVHF-152A Converter	86.60
in cabinet.....	200.00	RME DB-22A Preselector	66.00

Prices are Net, F.O.B. Chicago

TIME PAYMENTS

Trade-Ins Accepted

ALLIED RADIO

Everything in Radio and Electronics

December, 1947

GET YOUR COPY OF RADIO'S LEADING BUYING GUIDE

FREE

ALLIED RADIO CORP.

833 W. Jackson Blvd., Dept. 1-MM-7
Chicago 7, Illinois

- ☐ Send **FREE** 164-Page **ALLIED** CATALOG
- ☐ Enter order for.....
- ☐ Enclosed \$..... ☐ Full Payment
☐ Part Payment (Balance C.O.D.)
- ☐ Send full information on Communications Receivers and Time Payment Plan, without obligation.

Name.....

Address.....

City.....Zone.....State.....





DAVEGA

**America's Largest Hallicrafters Dealer
68 YEARS OF DEPENDABLE SERVICE**

presenting . . .

The Ideal Christmas Gifts




hallicrafters

The Radio Man's Radio MODEL SX 43

The SX-43 offers continuous coverage from 540 Kc. to 55 Mc. and has an additional band from 88 to 108 Mc. AM reception all bands. CW on four lower bands and FM on frequencies above 44 Mc. Speaker \$19.50 additional.

**ONLY
169⁵⁰**

DAVEGA CHRISTMAS SPECIALS

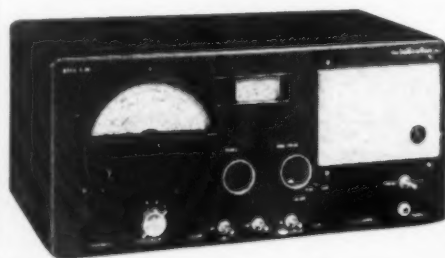

MODEL S-40A

Overall frequency range from 540 Kc. to 43 Mc. in four bands. Nine tubes, built-in dynamic speaker.

ONLY 89⁵⁰



MODEL S-38

Overall frequency range from 540 Kc. to 32 Mc. in four bands. Compact and rugged. AC-DC. Built-in speaker.

ONLY 47⁵⁰

MODEL SX-42



Greatest continuous frequency coverage of any communication receiver—from 540 Kc. to 110 Mc. in six bands. FM-AM-CW. 15 tubes. Speaker \$29.50

**ONLY
275⁰⁰**

MODEL S-47



15-tube AM-FM high fidelity receiver. Response—30 to 15,000 CPS. 12-watt audio-amplifier. Unbelievably pure tone. Speaker from . . . \$29.50

**ONLY
200⁰⁰**

Use These DAVEGA Addresses
Downtown . . . 63 Cortlandt St.
Near 13th St. . . 200 Broadway
Herald Square . . . 831 Broadway
Times Square . . . 111 E. 42nd St.
Empire State . . . 152 W. 42nd St.
Madison Sq. Garden . . . 825 Eighth Ave.

96th St. . . 2369 Broadway
Harlem . . . 125 W. 125th St.
Bronx . . . 31 E. Fordham Rd.
149th St. . . 2860 Third Ave.
Brooklyn . . . 360 Fulton St.
Brooklyn . . . 924 Flatbush Ave.
Brooklyn . . . 1304 Kings Highway
Bay Ridge . . . 5108 Fifth Ave.

Jamaica . . . 163-24 Jamaica Ave.
Astoria . . . 31-55 Steinway St.
Flushing . . . 39-11 Main Street
Hempstead . . . 45 Main St.
White Plains . . . 175 Main St.
Newark . . . 60 Park Place
Jersey City . . . 30 Journal Sq.
Paterson . . . 185 Main St.

DAVEGA

MAIL COUPON FOR DESCRIPTIVE LITERATURE

DAVEGA COMMUNICATIONS DIVISION
63 Cortlandt Street, New York 7, N. Y.
Please send full information on Communications Receivers, without obligation.

NAME
ADDRESS
CITY STATE
RN 8

SNC

transformers are

"TOPS" in Quality

Skillful engineering, highest quality materials, latest production techniques, and careful workmanship are combined in SNC transformers to give you perfect installations . . . a minimum of rejects . . . *outstanding* performance!



We invite your inquiry on custom made units for industrial application.



Get this easy-to-read catalog from your distributor —or write to factory direct.

SNC MANUFACTURING CO., INC.

Quality Transformers

WEST LAKE AVE. NEAR LEHIGH

GLENVIEW, ILLINOIS

December, 1947



The greatest RADIO HANDBOOK

WE'VE EVER PUBLISHED. Our 11th edition contains the greatest array of practical radio equipment ever shown between the covers of one book—all brand-new. All newly-designed, and newly-built by practical men, for practical men; all tested in our own shop in actual use. Larger-sized, more detailed photographs, on new larger page size (same size as this magazine).

FEATURED IN THIS EDITION ARE:

- Dozens of transmitters for all bands, and all powers up to 1 kw.
- Six chapters on Antennas, Transmission Lines, and Propagation
- One chapter devoted entirely to rotary array construction and feed methods
- One large chapter on the conversion of widely-distributed military surplus equipment to amateur and other practical use
- New constructional data on beam-tetrode amplifiers
- One chapter on determining the operational characteristics of all types of amplifiers
- New, simple FM exciter designs
- New data on transmitter control by improved methods
- New V-F-O design
- Simplified antenna tuning device and sending-wave meter
- The most extensive tube tables of any book not devoted entirely to such data

MORE MATERIAL THAN EVER BEFORE. DURABLY CLOTHBOUND, GOLD-STAMPED, FOR ONLY

\$3.00

per copy at your favorite dealer's in U.S.A. Mail orders, \$3.25 postpaid in U.S.A.; foreign, \$3.50 postpaid.



GET IT AT YOUR FAVORITE DEALER'S. If he cannot supply you, you may order direct from us by mail.

DEALERS: "Technical" discounts allowed on this book when purchased by the radio, book, and news trades in quantities for resale.

Editors and Engineers
LIMITED

1302 KENWOOD ROAD

Santa Barbara CALIFORNIA

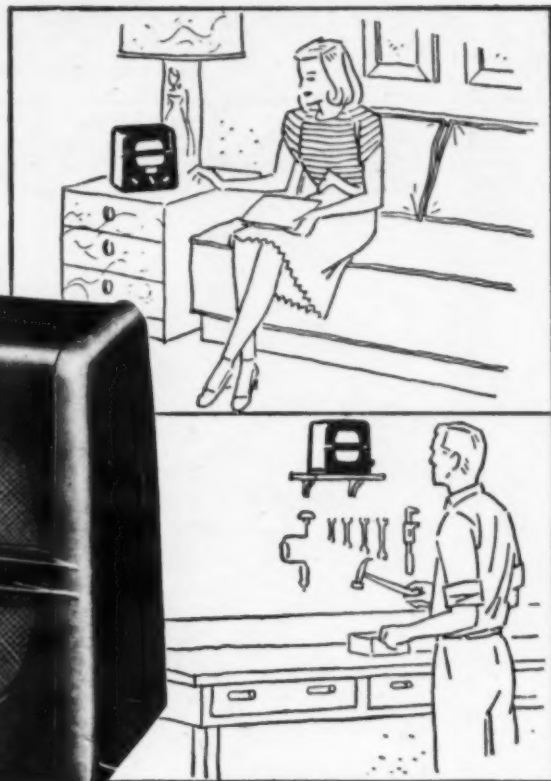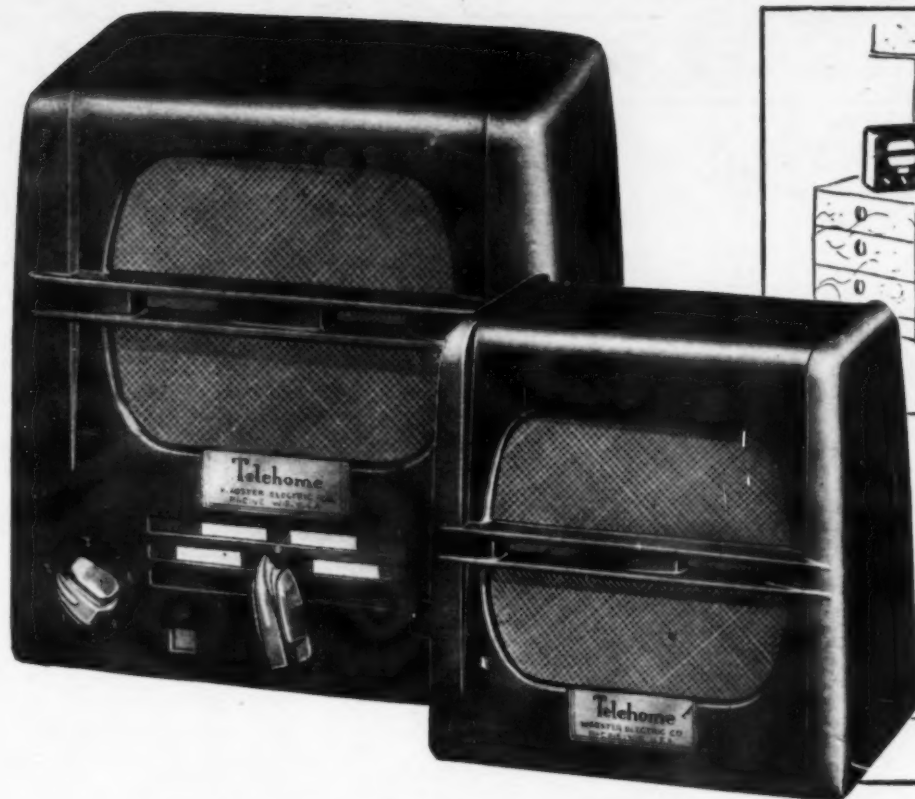

Here's what customers want! ... **New low-cost**
Intercommunication for the home
ONLY \$49⁵⁰
for Master Station, Speaker Unit and 100 feet of wire.

Prices slightly higher west of the Rockies

If you are not pushing the sale of "TELEHOME" it is not too late to do so! The Saturday Evening Post advertising promoting the sale of "Telehome" is telling millions of consumers about this new household necessity.

Housewives and home owners interested in the last word in modern convenience are now buying "Telehome" intercommunication for their homes.

Many additional prospective customers in your trade area will want to see and have you demonstrate this new item. Therefore, if you are not stocking and selling "Telehome," now is the time to do so.

This new convenience comes as a package consisting of one master station, one speaker unit and 100 feet of wire. Anyone can install it by following simple instructions. The master station has capacity for two additional speaker units which are available and can be sold separately.

In addition, a door speaker and wall-type master station for permanent and fixed installation in kitchen wall or cabinet are available. They are described and illustrated in the box at the right.

Prepare now to be the source of supply in your community.

Licensed under U. S. Patents of Western Electric Company, Incorporated, and American Telephone and Telegraph Company

WEBSTER
RACINE



ELECTRIC
WISCONSIN

Established 1909

Export Dept. 13 E. 40th Street, New York (16), N. Y. Cable Address "ARLAB" New York City

"Where Quality is a Responsibility and Fair Dealing an Obligation"


December, 1947



BY THE MAKERS OF
Teletalk



Door Speaker with bell push button

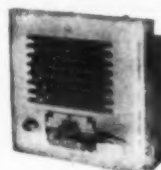

Wall-Type Master Station

Besides being the convenience that has caught the eye of the average housewife, the door speaker illustrated above offers another outstanding feature as you can answer your door without opening it . . . a safety feature that gives added protection to the home.

The wall master unit is excellent for new homes and for kitchen modernization. It has a capacity for five speaker stations.

OUR DECEMBER SPECIALS TO YOU



Walnut — \$12.95;
List, \$9.71 Net,
Ivory, Blue, Red,
\$14.95; List, \$10.57
Net. All 4 Tube
Superhets.

MODEL G-418



5 Tube Super-
het, in Walnut
Plastic Case,
\$19.95. List—
\$15.45 Net;
Ivory Plastic,
\$22.95; List,
\$17.35 Net;
Mahogany
Wood Case,
\$26.95 List,
\$18.95 Net.

MODEL G-513




6 Tube Superhet—
Special Net While
They Last, \$23.85.



5 Tubes Plus Selenium
Rectifier, Broadcast
Band and S.W. from
5.5 to 18.5 MC,
\$64.95 List, \$43.99
Net.



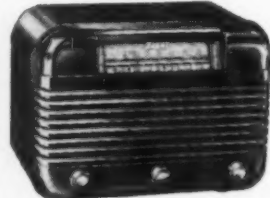
Regal Model 208—6 Tube
Superhet—List \$24.95
Net \$18.75



6 Tube Superhet 2 Band,
Broadcast and S.W. from 16
to 49 Meters, List \$34.95,
Net \$24.87



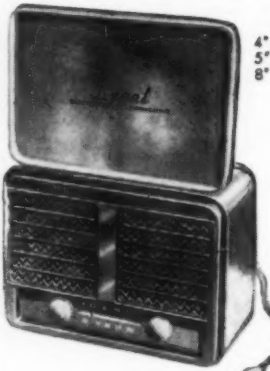Regal Model 205 — 5 Tube
Superhet in Plastic Walnut
Case, \$19.95 List — \$15.45
Net, in Pure Ivory Case (not
sprayed) \$23.95 List—\$16.95
Net



Size:
4" wide
5" high
8" long

\$29.50—List, \$22.22 Net,
Batteries \$2.03 per set

MODEL 208

Engineered by specialists in the development of broad-
cast receivers, built in our own modern laboratory.
Four times the power of pre-war radio sets. Hand-
somer in appearance and more efficient in operation.
Visual slide rule tuning dial with built-in Regalloop,
and super Alnico No. 5 permanent magnetic speaker,
with automatic volume control.

FEATURES

- Six Tubes—including Rectifier
- Single Band Super-Heterodyne
- Broadcast Band 550 to 1650 K.C.
- Automatic Volume Control
- Wave Trap Rejector
- Super Sensitive Iron Core Transformers
- 5" Alnico Wonder Speaker
- Illuminated Slide Rule Dial
- Built in Regalloop
- Works on 117 Volt A.C. or D.C.
- R.C.A. & Hazeltine License
- SIZE—Length 11½", Depth 7½", Height 8¼"
- Cabinet overall size
- WEIGHT—In shipping carton 10 lbs. 6 oz. Overall
size in shipping carton: Length 14½", Depth 10¼",
Height 11½"

MODEL 1049

Engineered by specialists in the development of broad-
cast and short wave receivers, built in our own modern
laboratory. Four times the power of pre-war radio
sets. Handsomer in appearance and more efficient in
operation. Visual slide rule tuning dial with built-in
Regalloop, and super Alnico No. 5 permanent magnetic
speaker with automatic volume control in the hand-
somest modern plastic cabinet.

FEATURES

- Six Tubes—including Rectifier
- Two Band Super-Heterodyne
- Broadcast Band 550 to 1650 K.C.
- Short Wave 16 to 49 Meters
- Automatic Volume Control
- Wave Trap Rejector
- Super Sensitive Iron Core Transformers
- 5" Alnico Wonder Speaker
- Illuminated Slide Rule Dial
- Built in Regalloop
- Works on 117 Volt A.C. or D.C.
- R.C.A. & Hazeltine License
- SIZE—Length 11½", Depth 7½", Height 8¼"
- Cabinet overall size
- WEIGHT—In shipping carton 10 lbs. 6 oz. Overall
size in shipping carton: Length 14½", Depth 10¼",
Height 11½"

MODEL 205

Engineered by specialists in the development of broad-
cast receivers, built in our own modern laboratory.
Four times the power of pre-war radio sets. Handsomer
in appearance and more efficient in operation. Visual
slide rule tuning dial with built-in Regalloop, and
super Alnico No. 5 permanent magnetic speaker, with
automatic volume control.

FEATURES

- Five Tubes—including Rectifier
- Single Band Super-Heterodyne
- Broadcast Band 540 to 1650 K.C.
- Automatic Volume Control
- Super Sensitive Iron Core Transformers
- 5" Alnico Wonder Speaker
- Illuminated Slide Rule Dial
- Built in Regalloop
- Works on 117 Volt A.C. or D.C.
- Licensed by R.C.A. & Hazeltine
- Size 6½"x7"x10"
- Weight in Carton 9 lbs.
- Also Available in Ivory

MODEL 747

The REGAL Super-Mittel! A.C. DC or BATTERY.
Small enough to be packed in a suitcase, yet uses
standard full size components! Parts interchange-
able anywhere! The only set of its size with 5 "A"
batteries and 1 "B" battery. Average life—100 hours!

FEATURES

- 4½" Alnico No. 5 speaker with a heavy duty slug
weighing 1.47 oz.
- Selenium rectifier (no rectifier tube necessary)
- Uses following tubes: 1—1R5, 1—1T4, 1—1S5,
1—3S4
- Licensed by R.C.A. and Hazeltine
- Super-Heterodyne
- Available in six different colors
- Full size 2-gang variable condenser

PARTS SPECIALS FOR DECEMBER ONLY

4 Inch Permoflux Speakers, Heavy Alnico 5 Magnet	88c
¼ Meg, ½ Meg, 1 Meg Standard Brand Volume Controls, Tapped, with Switch, 2½ Inch Shaft	44c each
Solar 20-30 MFD at 150 Volts	52c each
Solar 30-50 MFD Condenser at 150 Volts	56c each
Solar 40-40 MFD at 150 Volts	56c each
Solar 50-50 at 150 Volts Plus 20 at 25 Volts	72c each
Sprague or Cornell .01, .02, .05 at 600WV	\$4.80/100
Male AC Plugs, UL Approved, Bakelite Cap	4.25/100
Male AC Plugs, UL Approved, Live Rubber, Long Shank	6.75/100
Toggle Switches, Rotary or Throw Type	14c each

TUBE SPECIALS—SEALED CARTONS—STANDARD 90 DAY GUARANTEE

5Y3GT	33c each
35W4	40c each
5Y4G	44c each
6X5GT, 27, 25Z5	47c each
1C6, 1H4G, 32, 34, 6F6GT, 6H6GT, 12A76, 12J7GT, 12S7GT, 26, 36L6GT, 43, 45, 77, 84/6Z4, 6K7GT, 12Q7, 6S7GT, 12S7GT, 50L6GT	53c each
1A7GT, 1R5, 1U4, 354, 6A8GT, 1T4, 1S5, 6J7G, 7A7, 7B6, 7C6, 7C7, 7Q7, 12A8GT, 12BA6, 12BE6, 50B5, 71A, XXL, IV, 6A7, 6C6	63c each
1U5, 6G6G, 35Y4, 117Z6	77c each
6L6G, 7X7, 14X7	92c each

Late Scoop—Sonata "Little Maestro," World's Smallest Portable Amplified Phonograph, Alligator Leather Case with \$1578 NET
Cover, Size 9"x10"x5½", Plays Any 10 or 12 Inch Record Perfectly. \$21.95 List.

WARREN DISTRIBUTORS

3145 Washington St., Jamaica Plain 30, Mass.

Compare "Hi-Kaps"

See why Centralab's ceramic by-pass and coupling capacitors are your best buy for **QUALITY!**

"HI-KAP" FEATURES	DESCRIPTION	ADVANTAGES															
1. Impervious to moisture	Ceramic-X is non-hygroscopic. Moisture absorption is .007% or less.	No deterioration, no shorting. Longer life even under the most adverse conditions.															
2. Low mass weight	<table><tr><th>Av. Wt.</th><th>Dimensions</th><th>Values</th></tr><tr><td>.029 oz.</td><td>D—.315" L—.540"</td><td>.00005— .00025 mfd.</td></tr><tr><td>.044 oz.</td><td>D—.315" L—.830"</td><td>.0005 mfd.</td></tr><tr><td>.050 oz.</td><td>D—.340" L—1"</td><td>.000750— .005 mfd.</td></tr><tr><td>.082 oz.</td><td>D—.400" L—1.305"</td><td>.01 mfd.</td></tr></table> <p>Rating: 600 WVDC — 1000 VDC flash test.</p>	Av. Wt.	Dimensions	Values	.029 oz.	D—.315" L—.540"	.00005— .00025 mfd.	.044 oz.	D—.315" L—.830"	.0005 mfd.	.050 oz.	D—.340" L—1"	.000750— .005 mfd.	.082 oz.	D—.400" L—1.305"	.01 mfd.	For unit size and weight, Centralab BC "Hi-Kaps", made with Ceramic-X, are the only capacitors on the market which provide these voltage ratings.
Av. Wt.		Dimensions	Values														
.029 oz.		D—.315" L—.540"	.00005— .00025 mfd.														
.044 oz.		D—.315" L—.830"	.0005 mfd.														
.050 oz.		D—.340" L—1"	.000750— .005 mfd.														
.082 oz.	D—.400" L—1.305"	.01 mfd.															
3. Small size																	
4. High capacity																	
5. Special insulation	Wax impregnated, lacquered, dipped in special phenolic resin, cured and wax impregnated.	Prevents any possibility of shorting to adjacent leads, chassis or components.															
6. Convenient side leads	Heavy #22 gauge tinned copper.	Permit rapid, close-coupled connections. No tricky bending or fitting required.															
7. Low power factor	Initial — .6%. After 100 hours, 95% humidity test — 3.0%.	More efficient circuit operation, fewer failures.															
8. High leakage resistance	Initial — 5000 megohms. After humidity — 500 megohms.	Long life, more efficient performance.															
9. Maximum dependability	One-piece construction. Leads soldered directly to electrodes.	Will not short or become intermittent.															
10. Factory tested	For your protection, all units 100% factory tested before packaging and shipping.	Your guarantee to your customers of reliable service and performance.															



See why Centralab's ceramic by-pass and coupling capacitors are your best buy for **PRICE!**

NEVER BEFORE has the dependability, permanence and convenience of ceramic by-pass and coupling capacitors been offered to Radio Service Dealers at a favorable price! As more and more manufacturers turn to BC "Hi-Kaps" for longer life and better set performance, Centralab now offers you this opportunity to give yourself and your service customers the newest and finest in capacitor components! Made with high dielectric constant Ceramic-X, BC "Hi-Kaps" are rated at 600 WVDC — 1000 V. flash tested. Values from .000050 to .010000 mfd., list priced from \$1.25 to \$1.50 per envelope of five.

Look for large counter display at your Centralab Distributor. Write today for new free booklet, "Why Ceramic Capacitors", containing complete history of origin and development of ceramic capacitors!

Centralab
Division of GLOBE-UNION INC., Milwaukee

NEW RIDER BOOKS OPEN UP NEW OPPORTUNITIES FOR YOU!

JUST OUT! FM

by John F. Rider & Seymour D. Usan
CHAPTER HEADS

- Fundamental Considerations
- Frequency Modulation
- Essentials of F-M Transmitters
- Transmitters of Today (Wide Band and Narrow Band)
- The Transmission of F-M Signals
- F-M Receiving Antennas
- The F-M Receiver
- Alignment of F-M Receivers
- Servicing of F-M Receivers

Over 300 Fact-Packed Pages

TWO EDITIONS:

(Same but for covers) **\$1.80**
Paper Cover Stock.....**\$2.70**
Hard Back Cloth.....

TRANSMISSION AND RECEPTION

A thorough explanation of all manufacturers' products—transmitting and receiving: regular broadcasting, railroad, police, and "ham" equipment. Wide medium and narrow band is considered.

For radio servicemen, who can look to F-M as a big part of their future profits, for the "ham" who is considering narrow band F-M—for the student who is grooming himself for activity in the electronic field, this new book explains both the theory and servicing of F-M receivers. Its text provides an equally valuable hand-book for engineers.

BROADCAST OPERATORS HANDBOOK by HAROLD E. ENNES

A practical book written by a well known broadcast station operator for others who seek to attain high positions in that branch of electronics. 280 pages—**\$3.30.**

OUT IN
JANUARY!

INSIDE THE VACUUM TUBE



By John F. Rider. A new approach and technique that makes its message easy to understand. A solid, elementary concept of the theory and operation of the basic types of vacuum tubes based on the electro static field theory. The book, which covers diodes, triodes, tetrodes, and pentodes, presents a clear physical picture of exactly what is happening in a vacuum tube.

A goldmine for the student; a must for servicemen, amateurs and engineers. 425 Pages—\$4.50.

SERVICING BY SIGNAL TRACING



Explains approved system of diagnosing faults in radio receivers and all kinds of communication systems. The method was introduced by the author of the book, John F. Rider. The system has won endorsement by individuals and associations the world over as well as technical branches of our government. 360 Pages—188 Illustrations—\$4.00. Spanish edition—\$4.00.

A-C CALCULATION CHARTS

By R. LORENZEN. Students and engineers will find this book invaluable. Simplifies and speeds work involving AC calculations. Contains 146 charts. Covers AC calculations from 10 cycles to 1000 megacycles. —\$7.50

THE METER AT WORK



How each type of meter works and how each is used in the field to best advantage. Covers whichever phase of the subject the reader is interested in. 152 Pages—138 Illustrations—\$2.00.

AN HOUR A DAY WITH RIDER SERIES—96 PAGES.....(each) **\$1.25**

D.C. VOLTAGE DISTRIBUTION IN RADIO RECEIVERS—The applications of Ohm's law, practically interpreted in terms of how circuits are employed in radio receivers.
"ALTERNATING-CURRENTS IN RADIO RECEIVERS"—This book familiarizes you with the different forms of alternating currents in receivers. Basic facts.
RESONANCE AND ALIGNMENT—The importance of the subject in relation to all communication systems, and the clarity of this text, have sold over 60,000 of this title.
AUTOMATIC VOLUME CONTROL—An easy to understand explanation of how avc is utilized in radio receivers.

Here is technical know-how that will enable you to benefit from the fast growing manpower needs of the electronic industries. Rider Radio Books have proved their practical value in servicing shops, "ham" shacks, engineering labs., public libraries, government and private schools and colleges. They are authoritative, and easily understood. Check the listing below. Order today—and begin to "Learn RIGHT with Rider."

JUST OUT! TWO NEW RIDER 99's

PA INSTALLATION AND SERVICING

Here is a book that provides the answers to characteristic problems met in low power public address installations. In short it tells what to do and what how to service such PA systems.

UNDERSTANDING VECTORS AND PHASE

Considering the importance and wide use of vector presentations as a short-hand method of conveying the latest technical information in the radio field, it behooves every man in the technical branch of the industry to possess an appreciation of the significance of vectors. This book is a must for every student and serviceman if he is to keep pace with and understand advances in the radio art.

Each Over 130 Pages.....

Each **ONLY 99¢**

WATCH FOR EARLY RELEASE OF ADDITIONAL RIDER 99'S

VACUUM TUBE VOLTMETERS



Explains the theory upon which the functioning of the different types of v-t voltmeters is based, and also the practical applications of these instruments. Includes a bibliography consisting of 145 international references. 180 Pages—111 Illustrations—\$2.50.

THE CATHODE-RAY TUBE AT WORK



By JOHN F. RIDER. Presents a complete explanation of the various types of cathode-ray tubes and what role each element within the device plays in making voltages and currents visible. The only book of its kind! 338 Pages, 450 Illustrations—\$4.00.

SERVICING RECEIVERS BY RESISTANCE MEASUREMENT

Discusses series and parallel combinations of resistances and the distribution of currents and voltages, providing the basis underlying the circuit arrangements used in various types of radio receivers. 203 Pages—94 Illustrations—\$2.00.

ALIGNING PHILCO RECEIVERS



Complete and detailed information for aligning every Philco model from 1929 to 1941.

VOL. I—1929 to 1936—176 Pages.....\$2.00

VOL. II—1937 to 1941—200 Pages.....\$2.00

UNDERSTANDING MICROWAVES

By VICTOR J YOUNG Foundation for understanding microwave radio and radar Explained simply. Design and Operation of waveguides, magnetrons, klystrons, antennas, etc. Section I covers theory; Section II, terms, ideas, and theorems. 385 Pages. Liberally Illustrated. \$6.00.

RADAR

The complications have been removed in this entertaining book explaining Radar. Non-technical, but authentic. 80 pages, profusely illustrated, only \$1.00.

THE OSCILLATOR AT WORK



Shows how various oscillator circuits function and methods to improve their performance. Also describes the r-f and a-f oscillators used as signal sources. Covers laboratory test methods, and other related tests. 256 Pages—167 Illustrations—\$2.50.

AUTOMATIC FREQUENCY CONTROL SYSTEMS

Basic operation of discriminator and Automatic Frequency control circuits is detailed in first part of book. Descriptions of systems used in commercial receivers are fully described in second part. 144 Pages—102 Illustrations—\$1.75.

**JOHN F. RIDER
PUBLISHER, Inc.**

404 FOURTH AVENUE,
NEW YORK 16, N. Y.

(Dept. R)

Export Agent: Rocke International
Corp., 13 E. 40th Street, N. Y. C.
Cable ARLAB

*Publishers of
RIDER MANUALS*


LEARN RIGHT WITH RIDER!

FOR 17 YEARS PUBLISHERS EXCLUSIVELY FOR THE RADIO AND ELECTRONIC INDUSTRIES

CHECK
THE BOOKS
YOU NEED
AND GET
THEM
TODAY!

**"the Old Order Changeth,
Yielding Place to New"**

FTR

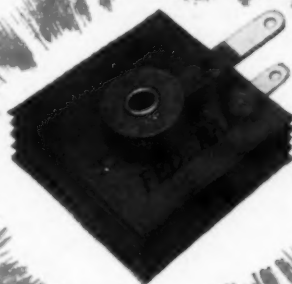

**...and this new component
CAN MEAN
NEW BUSINESS FOR YOU**

"Lots of water has gone over the dam" since the early radio fan tickled a crystal with a "cat's whisker." And every major advance in radio design has meant more and better business for the radio industry—from manufacture to servicing.

So it is with Federal's new Miniature Selenium Rectifier, which replaces the rectifier tube in AC-DC radio receivers. Already more and

more radio manufacturers are including it as original equipment — and more and more progressive service men are getting new business by installing it to *modernize* the sets they service. Here's what it can do for you:

- INCREASE YOUR BUSINESS
- ASSURE SATISFIED CUSTOMERS
- REDUCE YOUR INVENTORY

Federal's profit-making Miniature Selenium Rectifier can be obtained from major jobbers all over the country—complete with detailed instructions for installation.



KEEPING FEDERAL YEARS AHEAD... is IT&T's world-wide research and engineering organization, of which the Federal Telecommunication Laboratories, Nutley, N. J., is a unit.

Federal Telephone and Radio Corporation

SELENIUM and INTELIN DIVISION, 1000 Passaic Ave., East Newark, New Jersey

In Canada:—Federal Electric Manufacturing Company, Ltd., Montreal, P. Q.
Export Distributors:—International Standard Electric Corp. 67 Broad St., N. Y.

HARVEY

has everything
in radio

Here are a few samples of
our wide diversification



BC-314 RECEIVER

Used but in perfect condition. Two stages RF, separate local and beat oscillators. For 12-volt DC operation but easily converted to 110-volt AC. Frequency range 150-1500 KC, continuous in 6 bands. This unit is ideal as an airport or marine low frequency receiver, also a very excellent BC receiver. Complete with tubes, specially priced at\$29.50

MOTOR GENERATOR

DC to AC motor generator, manufactured by Allis Chalmers for the Navy. Rated 1250 VA output at 80% power factor. Input: 115 V., 14 amps DC. Output: 120 V., 10.4 amps AC. This unit is very conservatively rated and will easily supply 2 KW in constant duty without overheating. It has built-in voltage and frequency control to maintain constant 60-cycle output. Centrifugal governor. These units are brand new and built to Navy's usual high standards and shipboard water-resistant specs.

Harvey Special\$125

ELECTRONIC SWITCH

GE Type YE-9... designed for special studies of waveform, phase frequency relationship, etc. Will show for simultaneous comparison, on screen of single CRO, two or more independent signals. Requires no adjustment or calibration when in use.

\$59.50

STAND MIKE

Single button carbon mike in telephone type stand, with tiltable head, press-to-talk switch, 6 ft. of 3-wire cable and PL-6B plug.....\$4.95

UTC S-38 Choke. Brand new in original carton. Rated 5/25 henries, 550 mhs, 60 ohms DC res.....\$6.95

Cornell-Dubilier TJ-20040 oil-filled capacitor. Rated 4 mfd at 2000 V DC working \$3.75

Telephone:  Longacre 3-1800

HARVEY

RADIO COMPANY INC.

103 West 43rd St., New York 18, N. Y.

Spot Radio News

★ Presenting latest information on the Radio Industry.

By FRED HAMLIN

Washington Editor, RADIO NEWS

THE HARD-WON prosperity that came to the radio industry this year promises to continue over into 1948, best authorities in the field seem agreed. With all returns not yet in, '47 will undoubtedly turn out to be the greatest year in the industry's history. The coming year, while fraught with dangers and discouragements, should also hang up a number of new records.

CHIEF AUTHORITY for these statements is one of the best-informed men in radio, Bond Geddes, executive vice-president of the Radio Manufacturers Association, who is not only one to speak with caution, but who also always speaks on the basis of the vast store of statistics at RMA's command. As for this year, says Mr. Geddes, it's bound to hit history-making highs. "Despite the aches and pains always prevalent to a degree in our industry," he said recently, "present indications are that all previous production records will be broken. As the final quarter of the year customarily brings 60 per-cent of our annual sales, we can confidently look forward to a new all-time record in 1947 of about 15 million sets and a probable total dollar volume of close to three quarters of a billion."

BREAKING DOWN the production figures, Mr. Geddes has uncovered some interesting sidelights on radio trends during the current year. Believe it or not, on one type of receiver, production fell off almost to the vanishing point. This was in the manufacture of straight consoles, without phonograph apparatus, which have almost vanished from production and the market. Present production ratios are only eight-tenths of 1 per-cent in number and 5 per-cent in dollar volume, as contrasted with matching ratios in 1941 of 5.16 per-cent and 10.77 per-cent.

OFFSETTING THIS, the percentage of radio-phonograph combination receivers is about double the 1941 ratio, Mr. Geddes estimates. This includes both table and console types. Production ratios to total sets produced of table combination sets is running about 8.7 per-cent. Console combinations are up to about 10.2 per-cent of total volume. Table sets were only 4.61 per-

cent in 1941, console combinations only 5.08. The present dollar value ratio of table combination sets is 12.5 per-cent, compared to 5.51 in 1941. Console dollar value is 28 per-cent. In 1941 it was only 20.75. In production of straight table models, without phonographs, the present unit percentage is still high at 53.5 per-cent of the total volume. Auto radios are now running about 14.5 per-cent, portables 12.2 per-cent. Indications at last count were that receiving tube production would run as high as the last year peak of 205 million. Mebbe higher.

LOOKING TO 1948, Mr. Geddes sees the usual quota of "aches and pains"—and another banner year. The "temporary indigestion due to overproduction of table models," which was a headache during part of 1947, has now practically disappeared. Production has become more balanced and many of the troubles owing to obtaining wood for cabinets are gone. FM should make giant strides forward, since "1947 was only the starting point of FM." But Mr. Geddes adds a word of caution: "In my opinion, AM receivers will continue for many years to be the bread and butter of the industry, with FM and television sales as dessert." As for television, total sales for receivers in 1947 will reach some 100,000 and "with increasing commercial sponsorship by local as well as prominent national interests, television should be raised to new heights in 1948." The RMA spokesman is not pessimistic about the fact that less than one-tenth of 1 per-cent of American radio homes now have television receivers, 15 to 20 per-cent of current sales going to public places. He believes that these sales to group-consumer spots will result in stimulated home consumer demand.

BUT 1948 isn't going to be a bed of roses, and competition is going to be tough. In contrast with the industry prior to the war, when it was comparatively stable, now it is still changing over from the war years and is over-crowded. "For instance," Mr. Geddes reports, "in 1941 there were 55 receiver manufacturers. On the rolls today, both active and passive, there are 155, although many of these who



E. B. De Vry, President
DeForest's Training, Inc.

HERE'S *YOUR*
Big Chance

Profit Through Training in RADIO-ELECTRONICS

Prepare at HOME or in our CHICAGO LABORATORY to get REAL MONEY, a BETTER JOB, or a BUSINESS OF YOUR OWN

Our business is helping men . . . and young men . . . get into a well-paying future in the highly profitable fields of RADIO-ELECTRONICS. During the past sixteen years we have trained many men who desired better jobs or businesses of their own. We can effectively provide you with this same opportunity either in our new, modern Chicago laboratories or in the privacy of your own home.

If you choose to come to Chicago, we shall find comfortable living quarters for you. If you train at home, we shall send you modern, practical equipment. In either of these two methods, you will have the supervision of some of the finest instructors in the country. Fill in coupon below and we shall send you, absolutely FREE, full information about our program of building men for better opportunities in RADIO-ELECTRONICS. DeForest's Training, Inc. also includes instruction in FM Radio, Television and Industrial Electronics.

If you prefer to remain at home, you receive eight (8) big kits of radio parts and assemblies from which you can work out dozens of fascinating radio circuits to gain practical experience in your own home. In addition, you receive a 16 mm. motion picture projector and 12 information-packed reels of film which help you learn faster . . . easier. You also get modern looseleaf lessons with handy fold-out diagrams.

DEFOREST'S

TRAINING, INC.

Affiliated with the De Vry Corporation
CHICAGO • ILLINOIS

December, 1947

VETERANS

Both our (1) Chicago Laboratory and (2) Home Study training are accepted under the "G. I. Law." If you qualify, the Government will pay cost of either training you select.

EMPLOYMENT SERVICE

When you complete your training our effective Employment Service helps you get started toward a real future. Mail coupon below today . . . do not delay.

MAIL THIS OPPORTUNITY COUPON NOW!

Mr. E. B. De Vry, President
DeForest's Training, Inc.
2533 N. Ashland Ave., Dept. RN-D12
Chicago 14, Illinois

Please show me how I may get started toward a good job or a business of my own in Radio-Electronics.

Name.....Age.....

Address.....Apt.....

City.....Zone.....State.....

☐ If under 16, check here for special information.

☐ If a discharged Veteran of World War II check here.



Whatever the variety of transformers you need—whatever the number, small or large—you make sure of the same distinguishing characteristic: Merit Quality.

EXPORT DEPARTMENT:

1607 Howard Street, CHICAGO 26, U. S. A.

Cable Address: MERIT



MERIT COIL & TRANSFORMER CORP.

4427 North Clark St.

TELEPHONE

Long Beach 6311

CHICAGO 40, ILL.

SPOT RADIO NEWS

received OPA price permits and patent licenses never made a set. The ranks of manufacturers, however, include many newcomers, a few of whom are climbing up the ladder." It follows that '48 will "unquestionably be a period of extreme competition, in the American fashion" and "already there are indications of some casualties ahead." But despite this, Mr. Geddes is, on the whole, very optimistic. Summing up: "Prospects for 1948 can be regarded as sure to receive the impetus of a continued high level of general business activity, with high national and individual income, and with the assurance of wide and new markets through FM, television, and other electronic appliances."

AS WAS PREDICTED here last month, a new treaty regulating world radio operations, was signed at the Atlantic City convention in due order by the 78 nations concerned. And to give you an idea of how tough the summer-long job was, the final set of regulations, each of which had to be debated almost a word at a time during the meetings, filled 391 pages of fine print. It covered all phases of international radio communications, including operating practices, technical standards, and safety and distress signals. As an example of the work that went into this masterpiece of world amity, consider the toil of only one of its committees, concerned with frequency allocation. The group held no less than eight meetings beginning May 15 and continuing through the summer. They came up with agreements that were approved without change by the entire assembly of diplomats. And not once during their eighty sessions did any of them use invectives or throw a punch.

THE SPIRIT OF THE SESSION was made official toward the end by Leon C. Boussard, editor of "The Morning Electron," mimeographed newspaper for delegates at Atlantic City, and outstanding in its crusade to keep goodwill alive during the meetings. "I have been sitting here for five solid months," declared Mr. Boussard, "and it is a great experience to acknowledge the common sense and goodwill of the specialists and experts who here assembled. They have proved themselves real peacemongers. Never in the whole field of telecommunications have so many owed so much to so few. It was obvious—at least in Atlantic City—that there is always a solution or a compromise proposal at hand to solve the most difficult problems." Mr. Boussard recommended that "when the delegates are scattered and estranged all over this distraught world, they be requested to give five minutes thought every week to the pleasant memory of the time when they used to collaborate with other human beings who were separated by nationality, creed, (Continued on page 186)

RADIO NEWS

DESIGNED FOR THE BETTER SERVICE SHOP...



RCA's NEW FM SWEEP GENERATOR
... third unit of a
revolutionary new line

**Provides every signal you need
for fast, accurate FM alignment**

THE WR-53A removes the last element of doubt from FM receiver alignment... regardless of band-width requirements. You bring the recognized advantages of the sweep method of alignment to every FM job—speed, accuracy, and reliability that add up to a perfect job every time, in less time.


It's packed with features to make your work easier. Here's a quick check list:

- ... i-f center frequency, 8.3 to 10.7 mc
- ... adjustable i-f sweep width ... internal and external frequency modulation ...
- r-f range continuously variable from 85 to 110 mc ... provides AM or c-w signals ...
- includes step and fine attenuators ...
- a scope phase control permits centering of sweep patterns.

With the i-f sweep section, you can align i-f stages by the variable-frequency or visual method. When used with an oscilloscope or VoltOhmyst, you can quickly adjust an FM discriminator circuit by either the visual or single-frequency method. Alignment of r-f, local-oscillator, ratio-detector, and mixer circuits all become simple, routine jobs.

Here's an instrument that's comparable in performance yet half the price of similar laboratory-type equipment. It's a "natural" for the receiver manufacturer's laboratory as well as the radio service shop.

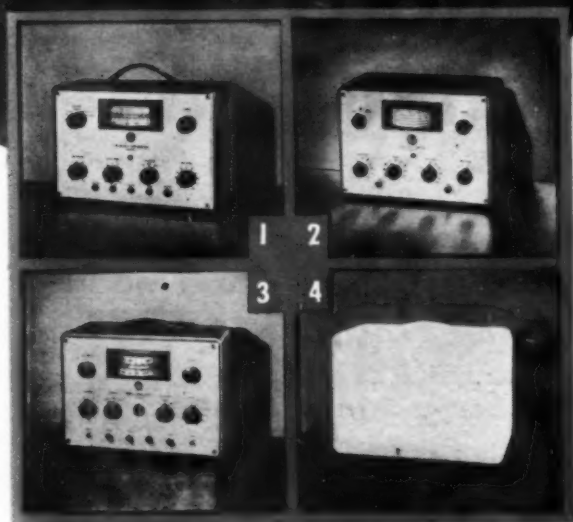A new bulletin is yours for the asking. Keep in touch with your RCA Test Equipment Distributor.



ON THE WAY—a superior line of test equipment that puts time-consuming service jobs on a profitable, production-line basis ... that anticipates all FM and television needs. Matched styling of all instruments permits attractive, convenient grouping. Watch for announcements of the other units in this new line.



TEST AND MEASURING EQUIPMENT
RADIO CORPORATION of AMERICA
ENGINEERING PRODUCTS DEPARTMENT, CAMDEN, N.J.

In Canada: RCA VICTOR Company Limited, Montreal

COMPARE Before You Buy Your Service Data

The speed with which you can complete radio repairs usually depends on the quality of your technical information service. That's why you owe it to yourself to choose the best. But don't guess. Don't take anyone's word for it. Be your own judge and jury.

Ask yourself: "Does the technical information service I use provide these features:

1. Is it *complete*—does it give me all the data I need to do the job?
2. Is the information *concise*, or is it padded with useless sales talk that makes needed data harder to find?
3. Is the data *uniform*—the same for all makes and models—or do I have to "dope out" a different layout for each model?


4. Does the data service give me *accurate* replacement listings—or do I have to guess what I should order from my parts distributor's stock?"

Don't guess about these important points. Compare PHOTOFACT Folders with any other service—point by point, set by set. Check specific models. See what PHOTOFACTS offer you—from complete disassembly instructions to exclusive Standard Notation schematics; from completely detailed drawings to exclusive exploded views. Then see what you find in others.

Be critical. Analyze carefully. Judge for yourself. Then you will know that *only* PHOTOFACT Folders will meet your actual needs.

Howard W. Sams

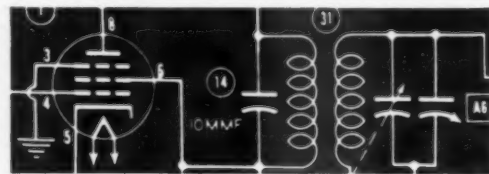Don't Miss PHOTOFACT Sets Nos. 23-28 with exclusive "Standard Notation" Schematics



Howard W. Sams 1947 Automatic Record Changer Manual

Nothing like it! COVERS MORE THAN 40 DIFFERENT POST-WAR MODELS. Absolutely accurate, complete, authoritative—based on actual study of the equipment. Shows exclusive "exploded" views, photos from all angles. Gives full change cycle data, information on adjustments, service hints and kinks, complete parts lists. Shows you how to overcome any kind of changer trouble. PLUS—for the first time—complete, accurate data on leading WIRE, RIBBON, TAPE, and PAPER DISC RECORDERS! 400 pages; hard cover; opens flat. Don't be without this manual. **ONLY \$4.95**

Howard W. Sams Dial Cord Stringing Guide

There's only one *right* way to string a dial cord. And there's only one book that shows you how. It's the Howard W. Sams DIAL CORD STRINGING GUIDE. Here, for the first time, in one handy pocket-sized book, are all available dial cord diagrams and data covering 1938 through 1946 receivers. Licks the knottiest dial cord problem in a matter of minutes. This low-cost book is a "must" for servicing. You'll want one for your tool kit and one for your shop bench. Order today. **ONLY 75c**

PHOTOFACT Sets now feature the exclusive new uniform "Standard Notation" schematics—the greatest service data development in 20 years! Every diagram is drawn to the same basic set of clear, uniform, easy-to-understand standards. Here's what the new "Standard Notation" Schematics mean to you: Makes circuit analysis simpler, quicker, fool-proof, more accurate! No more time wasted puzzling over odd-looking diagrams! No more trouble with varying symbols and confusing styles! Just ONE CLEAR STANDARDIZED STYLE FOR ALL CIRCUITS—SAVES YOU TIME—HELPS YOU EARN MORE. Subscribe to PHOTOFACT at your parts jobber now. At only \$1.50 per Set, it's the easy pay-as-you-earn way to build the world's finest service data library.

BOOST YOUR EARNING POWER!

Mail This Order Form to Your Parts Jobber Today or send directly to HOWARD W. SAMS & CO., INC., 2924 E. Washington St., Indianapolis 6, Ind.

- My (check) (money order) for \$.....enclosed.
- ☐ Send PHOTOFACT Sets ☐ No. 23. ☐ No. 24. ☐ No. 25. ☐ No. 26. ☐ No. 27. ☐ No. 28 (at \$1.50 per Set).
 - ☐ Send SAMS' 1947 AUTOMATIC RECORD CHANGER MANUAL(S) at \$4.95 each.
 - ☐ Send SAMS' DIAL CORD STRINGING GUIDE(S) at \$0.75 per copy.
 - ☐ Send PHOTOFACT Volume 1 (including Sets Nos. 1 through 10) in Deluxe Binder, \$18.39.
 - ☐ Send PHOTOFACT Volume 2 (including Sets Nos. 11 through 20) in Deluxe Binder, \$18.39.
 - ☐ Send FREE PHOTOFACT Cumulative Index.

Name.....
Address.....
City.....State.....

HOWARD W. SAMS & CO., INC.
INDIANAPOLIS 6, INDIANA

Export—Ad. Aurisma—89 Broad St., New York 4, N. Y.—U. S. of America
Canada—A. C. Simmonds & Sons, 301 King St. East—Toronto, Ontario

PHOTOFACT SERVICE

"The Service that pays for itself over and over again"

RADIO MAINTENANCE Subscribers AVERAGE

\$7800 income
per year

Successful Radio Service Technicians read RADIO MAINTENANCE regularly. It is the magazine of ideas and information for profitable service shops. It helps maintain secure, high quality operation. Where you find RADIO MAINTENANCE, you'll find successful servicing!

Each month RADIO MAINTENANCE brings you the latest developments in television, radio and electronics by top experts in the field. Each article, each department is carefully edited and presented to help you in your daily work. All these articles are invaluable as reference material; and all the articles together will form a complete reference library on everything in the Radio Servicing business. In the coming year, RADIO MAINTENANCE will bring you a complete series on each of the following: AM—FM—Television—Signal Tracing and all Test Equipment—Low Cost Business Promotion Methods—Sales Techniques for Servicemen—How to Make Huge Profits in the Sound Installation Business. Each article in a series will be a compact unit in itself—combined with the others of its series, they form a complete education—a complete service library—to bring you prestige, profit and security in your own Radio Service establishment.

AM SERIES

There are still 70,000,000 AM sets to service

Our principal source of income is servicing AM. The more sets we can get to service, the faster we can service each set, the more money we can make each week. RADIO MAINTENANCE rapid, trouble-free servicing techniques will enable you to triple your income. You will have more time to promote and build your business—for greater profit and security—present and future. Currently scheduled are 36 articles including suggestions for service shop design—portable racks for rapid movement of receivers without damage—ten-minute trouble location through simplified, modern signal tracing, circuit analysis and many other features. These RADIO MAINTENANCE articles will present a complete educational library on high profit AM radio service techniques.

SOUND EQUIPMENT SERIES

Are you prepared to get your share of the huge profits in Sound? Sound installation brings thousands of dollars every year to the service technicians with the knowledge of how to handle sound. In every community, more and better PA systems are increasing in number, and you can get contracts immediately to equip auditoriums, dance-halls, restaurants, factories, and many other establishments. RADIO MAINTENANCE in the new, forthcoming series on sound will tell you how to sell PA, plan the installation, and pick the right equipment for the job. It will cover actual installation of all types of PA components, how to instruct the owners in operation and finally how to derive additional income from PA maintenance.

Every issue of RADIO MAINTENANCE contains the information you want. . . .
Every day is RADIO MAINTENANCE day in your shop. . . . Send in the coupon today—your first issue will be mailed to you immediately!

RADIO MAINTENANCE MAGAZINE
460 Bloomfield Ave.
Montclair 3, N. J.

Please send me RADIO MAINTENANCE for

- ☐ 1 year at \$3.00
- ☐ 2 years at \$5.00

☐ Check enclosed ☐ Bill me later

Name.....
Address.....
City and State.....
*Occupation.....
Title (Service Mgr., etc.).....
Employed by.....
*Business or professional classifications are required to serve you better. Each subscriber will profit by writing one of the following classifications in space indicated.
☐ INDEPENDENT SERVICEMAN ☐ SERVICE MANAGER ☐ DISTRIBUTOR
☐ DEALER SERVICEMAN ☐ DEALER ☐ JOBBER
State your trade or occupation if not listed

BOLAND & BOYCE INC., PUBLISHERS

Same
day
Service

OHMITE 5-watt

Wire-Wound
Vitreous-Enamelled
Type

...utmost dependability
in new small size

Now you can get an Ohmite wire-wound, vitreous-enamelled resistor . . . of proved reliability . . . in the new compact 5-watt size. This new resistor has the same rugged construction . . . the same unfailing dependability . . . as the well known line of 10 and 20-watt Brown Devil resistors. Stocked in a wide range of resistance values from 1 to 10,000 ohms, with a tolerance of $\pm 10\%$.

The new 5-watt Brown Devil can be easily mounted by its $1\frac{1}{2}$ " copper wire leads. Its small size— $\frac{1}{16}$ " x $1\frac{1}{2}$ "—and rugged all-welded construction make it ideal for general industrial uses and for original and replacement purposes in radio and electronic equipment.

Investigate this new line of Ohmite resistors.

Write for Catalog 19

Contains information on
Ohmite stock items

OHMITE MANUFACTURING COMPANY
4885 Flournoy St., Chicago 44, Ill.



Be Right with

OHMITE

RHEOSTATS • RESISTORS • TAP SWITCHES • CHOKES • ATTENUATORS

RADIO NEWS

Other... new OHMITE items

TYPE AB, 2-WATT POTENTIOMETER

A new, extremely high quality molded composition unit—with a good safety factor.



Sold only thru Ohmite Distributors

$\pm 5\%$ LITTLE DEVIL COMPOSITION RESISTORS

The $\frac{1}{4}$ and 1-watt sizes of this popular resistor now in $\pm 5\%$ tolerance. Also $\frac{1}{2}$, 1, and 2-watt units in $\pm 10\%$ tolerance.



Sold only thru Ohmite Distributors

RB-2 DIRECTION INDICATOR POTENTIOMETER

A compact, low-cost unit used with a 6-volt battery and 0-1 milliammeter to indicate remotely the position of a rotary-beam antenna.



RADIO FREQUENCY PLATE CHOKES

Tiny, single-layer wound, high-frequency chokes. Six new stock sizes from 7 mc to 520 mc. Two rated 600 ma, four rated 1000 ma.



WE BRING NATIONAL SCHOOLS TO YOU FOR HOME TRAINING IN RADIO TELEVISION & ELECTRONICS

NATIONAL SCHOOLS SHOP METHOD HOME TRAINING WILL START YOU RIGHT

We will train you today to get started tomorrow in one of the thousands of opportunities opening in the field of Radio, Television and Electronics. The Home Radio Service Field continues to grow. **Television is here . . .** Television Broadcasting facilities are being rapidly expanded. Television sales, service, installation and maintenance requirements are more and more important from day to day. **Electronics is an important factor** in many applications for utility, safety, accuracy and convenience. Airlines are finding new uses for Radio bringing new benefits to air transportation. **Ships at sea** are employing Radar together with other conventional Radio apparatus for ship-to-shore communications and safety. **Frequency Modulation** is modernizing Radio Broadcasting, offering static-and-interference-free reception in the home. The list of Radio applications is almost endless, and every one represents increasing opportunities in our modern world for the **RADIO, TELEVISION AND ELECTRONICS TECHNICIAN WITH A SOLID TECHNICAL BACKGROUND.**

YOU CAN BE A NATIONAL SCHOOLS MAN

It is not a question of opportunity but rather how to take advantage of existing opportunity. Only proper training can make these opportunities a **reality**. National Schools of Los Angeles, one of the oldest and largest technical trade schools in the United States, offers you **Shop Method Home Training**, a proved method that builds qualified technicians. Here is Home Training that **BRINGS RESULTS.**

Behind all training from National Schools stands a permanent faculty of experienced instructors and engineers. These men are daily teaching resident students right in our own Shops and Laboratories. From first hand experience with students here at school, our instructors understand the needs and ambitions of men like you. All of our instructors, both Home Study and Resident, have ideal facilities to make your training practical, up-to-the-minute, interesting. It takes years of experience to know how to train men, especially in the practical technical trades. Established almost 50 years ago, National Schools has a rich background of experience to help you to take full advantage of the opportunities in the Radio, Television and Electronics Industry.

VETERANS

During the war, National trained enlisted men under contract with the War Department. Both the Armed Forces Institute and Marine Corps Institute used our lesson texts on a wide scale. Now, we are training veterans, both resident and home study, through the Veterans Administration. If you are a veteran of World War II—and qualified for training under the G.I. Bill of Rights, check the coupon for special information.



December, 1947



RADIO SHOP AT NATIONAL

BROADCAST STUDIO AT NATIONAL

Partial View of the
Facilities that Stand
Behind Your National
Schools Home Training



Since 1905

TELEVISION STUDIO
AT NATIONAL

For Over 42 Years
One of America's
Leading Trade Schools



Begin Training at Home
Later Come to Our Shops and
Laboratories in Los Angeles

—If You Prefer

National's Master Shop Method Home Training in Radio, Electronics and Television is **COMPLETE** in itself. No other training is necessary; but, some men do prefer to take a short experience course here in our resident shops and laboratories, at the end of their Home Study training. They find it helpful to spend a short period of time in our modern Broadcasting Station, or our New Television Laboratories and Studios, or our Extensive Radio Servicing Shops—as well as our departments covering every specialized phase of the Radio Industry.

You are welcome to take advantage of this additional instruction if you wish. If you are interested, check the coupon below. Full details will be sent you by return mail. National Schools' **OUTSTANDING FACILITIES MAKE IT POSSIBLE TO OFFER THE FINEST POSSIBLE TECHNICAL TRADE TRAINING IN RADIO, TELEVISION AND ELECTRONICS.**

You Get All This Radio
Experimental Equipment to
Use and Keep at Home!

LEARN BY DOING is the basic principle of National's Shop Method Home Training. We send you standard Radio parts for an interesting series of experiments which demonstrate the fundamentals of Radio, Television and Electronics. The very essence of this training is **EXPERIENCE**—you get actual experience by building many different types of circuits. You build a fine, long distance **MODERN SUPERHETERODYNE RECEIVER**, signal generator, low-power Radio transmitter, audio oscillator, etc. This **practical work** develops your knowledge of Radio step by step, makes you a **practical** Radio Technician.

G. I. APPROVED

NATIONAL SCHOOLS

LOS ANGELES 37, CALIFORNIA EST. 1905

MAIL OPPORTUNITY COUPON FOR QUICK ACTION

NATIONAL SCHOOLS, Dept. 12-RN
4000 South Figueroa Street, Los Angeles 37, California
Mail me **FREE** the two books mentioned in your ad, including a sample lesson of your course. I understand no salesman will call on me. I have checked below the plan which interests me.

NAME AGE

ADDRESS

CITY STATE

(Include your home number)

- ☐ I am interested in home study only.
- ☐ Send information on your Combined Home-Study and Modern Resident Shop Training.
- ☐ Veteran of World War II.



A telephone listens to a loud speaker in the new "free field" acoustic test room at Bell Telephone Laboratories. The sound-transparent "floor" is built of steel cables.

Test-tube for Sound

This giant "test-tube" is actually an echoless sound room at Bell Telephone Laboratories. Here engineers seek new facts about sound which will help them make telephone service still better and more dependable.

Bell scientists know a great deal about what happens to sound in electrical systems. This new room will give them a powerful tool to find out more about what happens to sound in the air.

In an ordinary living room, most of the sound addressed to you comes by way of reflections. At 10 feet less than 10% reaches you directly.

Sound that bounces at you from walls, ceilings, furniture, and your body is all right for hearing—but it poses questions for scientists who would study it uncontaminated by reflections.

The Bell Laboratories "test-tube" gives telephone people the chance to produce pure sound and analyze it reliably with respect to intensity, pitch, and direction. The entire room is lined with glass wool, contained in wire-mesh cases, wedge-shaped to give maximum absorbing area. Sound bounces along the sloping surfaces, sifts into the soft glass wool, and is gradually stifled.

This is one more example of Bell Laboratories' constant work to learn more about everything which can extend and improve telephone service.

BELL TELEPHONE LABORATORIES

Exploring and inventing, devising and perfecting for continued improvements and economies in telephone service.



RADIO NEWS

PHILCO LEADS IN BATTERY-POWERED RADIOS



SELL **PORTABLE OWNERS**

Philco provides approved types of batteries for *all* makes of portable radios—plus sales-building promotional plans to bring this profitable business to your store.



SELL **FARM RADIO OWNERS**

Philco helps you carry on consistent year 'round promotions for *all* makes of farm radios. Use these plans to increase your sales and profits.

... and gives you your biggest battery replacement market! Sell the easy way with

GENUINE **PHILCO** **BATTERIES**

Yes, owners of Philco Portables and Farm sets in your area, are the backbone of the radio battery replacement business. Sell them the batteries they *know*—the batteries that are engineered for their radios—genuine Philco Batteries. Don't work harder selling substitutes when you can sell the *real thing*. Feature Philco Dry Batteries—preferred by Philco owners—accepted by *all* for dependable quality and long life.

USE PHILCO **Local Promotions**

TO INCREASE YOUR BATTERY SALES

Famous Philco "Share-the-Cost" cooperative advertising plans are now available to help you get more of the profitable dry battery business of your community.

FOR FASTER SOLDERING 2 NEW WELLER SOLDERING GUNS with

Solderlite



The new Weller Soldering Guns with Solderlite plus the fast 5 second heating help make service work more profitable for radio, television and appliance service men, electrical maintenance men, electric motor rewinding and repair shops automotive electrical service.

A useful and time-saving tool for laboratory workers, experimenters, hobbyists, telephone installation and maintenance men. S107 100 watts single heat, D207 100/135 watts dual heat.

See your radio parts distributor or write for bulletin direct.

WELLER MANUFACTURING CO.

810 Packer St., Easton, Pa.

In Canada: Atlas Radio Corp., Ltd., 560 King St., N. W., Toronto, Ont.

Export Dept.: 25 Warren St., New York 7, N. Y.

Within the INDUSTRY

F. M. SLOAN has been appointed manager of the *Westinghouse Home Radio Division* at Sunbury, Pa., succeeding **Harold B. Donley** who has resigned.

Mr. Sloan, formerly assistant general manager of *Westinghouse Radio Stations, Inc.*, has been associated with *Westinghouse* radio activities for more than 15 years in technical and administrative positions. In addition to laying the ground work for the nationwide service organization of the Division which he now manages, Mr. Sloan served during the latter part of the war as manager of the Field Engineering Service Department for the *Industrial Electronics Division* at Baltimore.

THOMAS E. STEWART, JR., is the new chief of the *Applied Electronics Branch* of the U.S. Army Engineer Research and Development Laboratories at Fort Belvoir, Va.



He succeeds **Major E. G. Radcliff**, who has been assigned to *Purdue University* to obtain his Master's degree in electrical engineering.

Mr. Stewart, who has been employed by the Army since 1942, was recently presented the *Exceptional Civilian Service Award* for his development of metallic, non-metallic, and underwater mine detectors, a radio explosives detonator, and a barrage balloon flight analyzer.

Prior to his association with the Army, Mr. Stewart was employed by the *Sylvania Industrial Corporation* of *Fredericksburg, Va.* He is an associate member of the *IRE* and a graduate of *Pratt Institute*.

RODOLFO M. SORIA has joined the *American Phenolic Corporation* of *Chicago* as *Project Engineer* in charge of special development work on antennas and radio frequency transmission lines.

Mr. Soria obtained his Bachelor and Master degrees in communication engineering from the *Massachusetts Institute of Technology*. He was formerly an instructor in electrical engineering at the *Illinois Institute of Technology* where he received his doctorate in June of this year.

HAYDON MANUFACTURING COMPANY, producers of timing motors and apparatus, have recently moved all operations of the company into new quarters in *Torrington, Conn.*

The completion of a three-story addition to the plant has allowed the

company to consolidate operations from the *Forestville* plant under a single roof.

DAVID H. ROSS of *San Francisco* has been named northern California representative for *Bud Radio, Inc.*, of *Cleveland, Ohio*.



Long associated with the radio industry, Mr. Ross became the youngest amateur radio operator in the 7th radio district in 1926. He is a graduate of the *University of Washington* where he received his B.S. in *Industrial Engineering*. He has been associated with *Globe Wireless, Ltd.*, and *Dalmo Victor, Inc.*, in various capacities.

The company also announced that **H. J. Nelson** of *Denver* will serve as a representative for the company's products in the *Colorado, Wyoming, Montana, eastern Idaho, Utah, New Mexico* and *South Dakota* territory. He served four years in the Army as an *Engineering Officer* with the *Signal Corps*.

PETER N. TSOKRES has been named chief engineer for the *Colonial Television Corp.* of *New York*.

In his new position, Mr. Tsokres will supervise the engineering of the company's line of bar and home receivers. He succeeds **Robert Saron** who recently joined the staff of the *UNO*.

E. H. DREIFKE has recently been promoted to the post of assistant manager of the *Radio Division* of *Stewart-Warner Corporation* of *Chicago*.




Mr. Dreifke has been associated with the company for 12 years and joined the radio division in January of this year. From 1944 through 1946 he was on special assignment in charge of the firm's war contract settlements.

He was formerly employed by *Grigsby-Grunow Co.* and the *Temple Corp.*


EMPIRIA CORPORATION has recently been incorporated as a *New York* corporation serving in collaboration with their *London* colleagues, *Empiria Products Limited*.

This new concern which will maintain offices at 149 *Broadway, New York*, will specialize in the exporting

RADIO NEWS

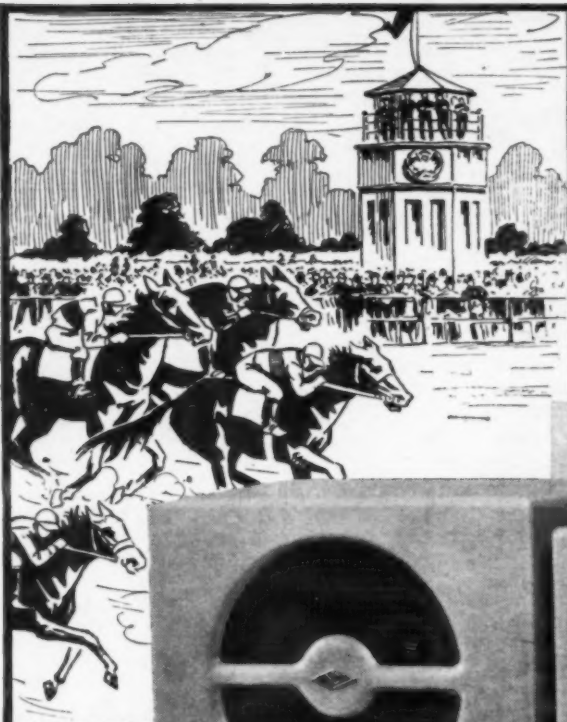

ANOTHER NATIONAL *FIRST* THE NC-183

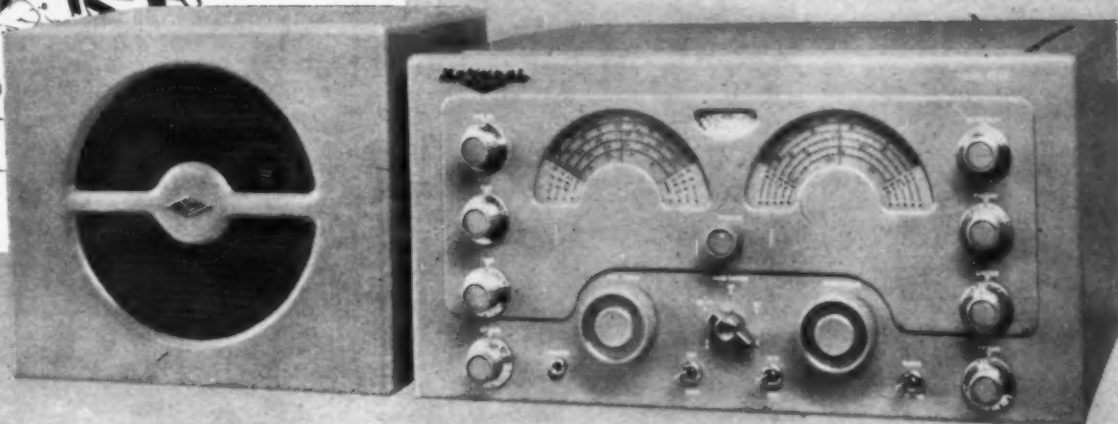

FEATURES:

- Frequency coverage from 0.54 to 31 Mc Plus 6 meter band. Band-switching on all frequencies.
- Adjustable sensitivity control for S-meter operation on either c.w. or phone.
- Automatic adjustable threshold double-diode noise limiter.
- 115 volts 50/60 cycle AC operation. Easily adapted to 230 volts.
- Amateur Net (Complete with 10" speaker)\$269.00

For the first time, a ham receiver incorporating all the latest innovations demanded by amateurs is now available at a reasonable price.

The NC-183, latest in National's great new line of communications receivers, is a band-switching set covering frequencies from 0.54 to 31 MC plus the 6 meter band. Two r.f. amplifier stages provide remarkable image rejection and the latest crystal filter aids in maintaining the highest degree of selectivity.

In addition, a stabilized voltage regulated circuit makes the NC-183 a truly top-flight performer on the highest frequencies. A push-pull audio output stage with separate 10" speaker affords excellent fidelity of output.

These, plus many other features, combine to make the NC-183 a really "hot" receiver. It will certainly become a strong favorite with those stations that specialize in digging DX out of the background.

See and hear the NC-183 at your nearest National distributor this week.

**National
Company, Inc.**
Dept. No. 15
Malden, Mass.
U. S. A.

MAKERS OF LIFETIME RADIO EQUIPMENT



**Make YOUR SHOP a
modern, profitable**

SERVICE LABORATORY

Two things — and only two things — spell success or failure in radio servicing today. One is knowledge and skill. The second is instruments. McMURDO SILVER brings you the *Laboratory Caliber Electronic Test Instruments* which turn your shop into a modern service laboratory. Simple instructions make them easy to use. They are proved by thousands upon thousands of users. Compare value and prices and LCETI will be your selection, too.

MODEL 906 FM/AM SIGNAL GENERATOR: The basic need for AM, FM, and television servicing. 8 ranges calibrated $\pm 1\%$ accurate, 90 kc. thru 210 mc. 0-100% variable 400 AM; 0-500 kc. variable FM sweep built-in. Metered microvolts; variable 0-1 volt. Strays lower than \$500 laboratory generators. Only \$99.50 net.

"VOMAX" UNIVERSAL V.T.V.M.: The overwhelming choice of experts. 51 ranges, d.c., a.c., a.f., i.f., r.f., current, db., and resistance. Visual signal tracing to 500 mc. New 5" pencil-thin flexible r.f. probe. Only \$59.85 net.

MODEL 904 CONDENSER/RESISTANCE TESTER: Measures accurately $\frac{1}{4}$ mmfd. thru 1,000 mfd.; $\frac{1}{4}$ thru 1,000 megohms. Internal 0-500 V. variable d.c. polarizing voltage. Measures condensers with rated d.c. volts applied. Only \$49.90 net.

MODEL 905 "SPARX" SIGNAL TRACER: Time-saving visual and audible signal tracing; also tests phono pickups, microphones, speakers, PA amplifiers. Is your shop test-speaker, too. 20~ thru 200 mc.; PM speaker; mains-insulated transformer power supply. Only \$39.90 net.

SEND FOR COMPLETE CATALOG. See these and Silver communication transmitters, receivers, "Micromatch," Xtal-controlled VFO, pretuned frequency multiplier at your jobber.

OVER 36 YEARS OF RADIO ENGINEERING ACHIEVEMENT

McMurdo Silver Co., Inc.

EXECUTIVE OFFICES: 1240 MAIN ST., HARTFORD 3, CONN.
FACTORY OFFICE: 1249 MAIN ST., HARTFORD 3, CONN.

of electrical, engineering electronic, and radio equipment as well as component parts and accessories.

Like the parent company, the New York concern will handle exports principally to India, the Middle East, and South Africa.

DAVE R. CHENAULT, formerly assistant advertising manager of *Sparks-Withington Company*, has been promoted to the post of sales promotion and advertising manager for the Radio and Appliance Division of the company.



Mr. Chenault was in sales work before joining the U. S. Air Force in 1943. He joined the *Sparton* organization soon after being discharged from the service and has been active in the preparation and execution of many of the company's sales promotions since that time.

E. E. FERREY has been upped to the post of Director of Public Relations for the *Farnsworth Television & Radio Corporation*.

Mr. Ferrey has served as assistant director of the Public Relations Division since joining the company in August of 1946. In his new post he succeeds Paul J. Boxell who has joined *Hill and Knowlton*, Public Relations Counsel, New York.

The new Public Relations Director was formerly news editor of Radio Station WHAS in Louisville and served as correspondent for the United Press and as extension lecturer in journalism for Indiana University.

GRENVILLE R. HOLDEN, vice-president of *Sylvania Electric Products, Inc.*, has been elected to the Board of Directors of *Electronic Tubes Ltd.* of London, a British radio tube manufacturing affiliate of *Sylvania*.



Mr. Holden was named a vice-president of *Sylvania* in April of this year after joining the company in 1943 as secretary to the Management Committee. In 1946 he was promoted to the post of Assistant to the President.

He is a graduate of Harvard University where he also served as an Economics instructor. He was formerly associated with *Eastman Kodak Co.* and during the war served the government in various capacities.

OWEN NANGLE has been appointed a district sales manager for *Zenith Radio Corporation* serving the lower Michigan and most of Indiana territories.

Mr. Nangle succeeds William H. Boyne who has been promoted to the post of general manager of the *Zenith* (Continued on page 146)

RADIO NEWS



For true to life recording there has never been
anything better than Presto Green Label Discs.



RECORDING CORPORATION • 242 WEST 55TH STREET • NEW YORK 19, N. Y.
Walter P. Downs, Ltd., in Canada

World's Largest Manufacturer of Instantaneous Sound Recording Equipment & Discs



For a better job in radio
**Modernize Your
"plant"!***

*Your 'Plant' is your technical ability Keep it up-to-date. It's a key to success!

Every manufacturing plant must maintain a program of modernization. Equipment, methods, building—all must be kept up-to-date to meet the swift-moving demands of today and tomorrow. For the same reason it is important that you invest in your own "plant" modernization program.

• If you are wise, you will match strides with radio developments. You must improve your technical knowledge not only to *bold* the job you now occupy, but to qualify for the better job you want. CREI offers you a proved program of technical self-improvement for home study in your spare time. Courses are constantly revised and kept up-to-date. CREI shows you the way to good pay and security by providing the "tools" you need to build a secure foundation for your "plant".

You can "go all the way with CREI"—from introductory basic principles to advanced training, on to specialized engineering subjects. No matter what your needs—no matter what your experience—there's a CREI course for you. These courses offer you more today than ever before—and are still at pre-inflation prices! How can you afford not to invest in "plant modernization" at this low cost?

Right now is the time to decide what the next five years will mean to your future. It costs you nothing but your time to read the facts in our 24-page booklet and to *see* and *read* the sample lesson. You can't afford not to investigate. Mail the coupon now!

VETERANS! CREI TRAINING AVAILABLE UNDER THE "G. I." BILL!

Capitol Radio Engineering Institute *An Accredited Technical Institute*

DEPT. RN-12

16TH AND PARK ROAD, N. W., WASHINGTON 10, D. C.

Branch Offices: New York (7): 170 Broadway • San Francisco (2): 760 Market St.

SAMPLE LESSON FREE

Now, see for yourself! Read one of these interesting lessons from the CREI course. You will see, in advance, how practical it is to improve your ability the CREI way.

From Practical Radio-Electronics Course:

"ELECTRON PHYSICS AND ELECTRON THEORY"—Discusses modern theories of the composition of matter, including atomic energy, and their relation to present-day radio-electronics.

From Practical Television Course:

"PICK-UP TUBES—ICONOSCOPE AND IMAGE DISSECTOR TUBES"—Discusses fundamental pick-up tubes of the television camera. It precedes the study of the Orthicon and the Image Orthicon.

MAIL COUPON FOR FREE 24-PG. BOOKLET & SAMPLE LESSON



CAPITOL RADIO ENGINEERING INSTITUTE

16th & Park Rd., N.W. Dept. RN-12, Washington 10, D. C.

Mail me ONE FREE sample lesson and your 24-page booklet, "CREI Training for Your Better Job in Radio Electronics". I am attaching a brief resume of my radio experience, education and present position.

Check One ☐ PRACTICAL RADIO-ELECTRONICS
Course: ☐ PRACTICAL TELEVISION


NAME

STREET


CITY.....ZONE.....STATE.....

☐ I am entitled to training under the "G. I." Bill.

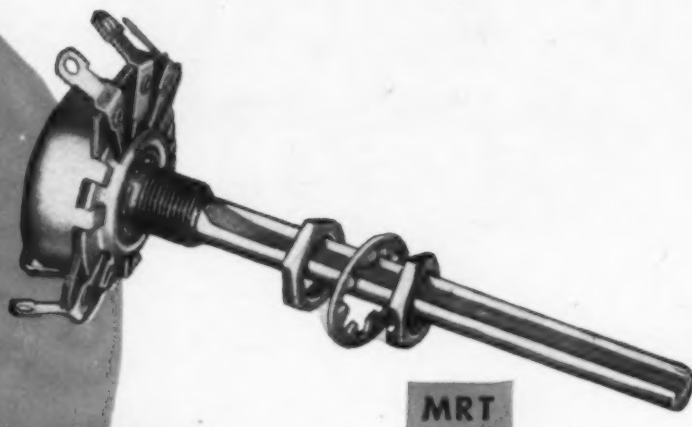
More Tapped Control Values For Your "Every Need"



MRT

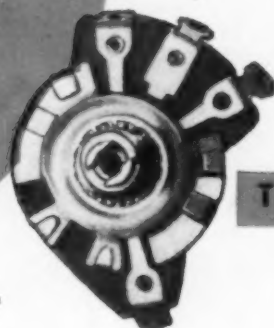

TM

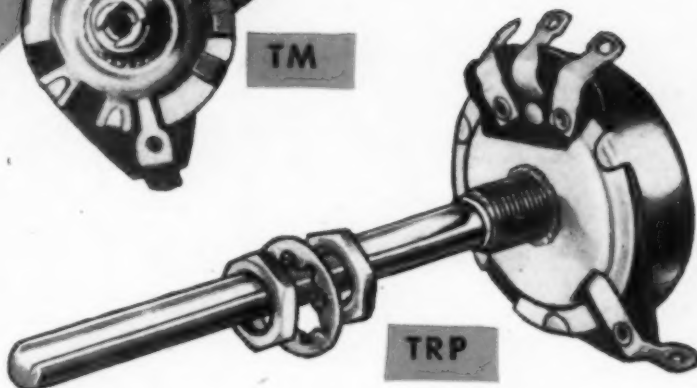

TRP

MALLORY provides every needed resistance value in its single tapped replacement controls—31 combinations of overall and tap resistances in all.

Mallory MRT Controls are available in most of the popular values, and feature an easy-to-cut channel shaft that fits all types of knobs. Mallory TMs are made in an even wider range of resistance values than the MRTs, and are used in conjunction with 30 non-wobbling, non-loosening Plug-In Shafts. They have practically universal application because they provide "special" shafts of nearly every required type.

Where shaft lengths of 3 inches or less are required, Mallory TRPs (fixed shafts)

replace large originals using set screw or spring type knobs. See your Mallory distributor.

Insist on MALLORY—the Complete Control Line

Mallory offers 33 Tapered Wire-Wound Controls ... 31 Values in Single Tapped Controls ... 10 Values in Double Tapped Controls ... 12 Clutch Type Controls ... 10 Universal Dual Controls ... and 92 Popular Special Controls.

The MALLORY "Good Service for Good Business" Plan includes ideas that will help your business grow.

Ask Your Distributor about it.

P. R. MALLORY & CO. Inc.
MALLORY


VIBRATORS ... VIBRAPACKS* ... CAPACITORS ... VOLUME
CONTROLS ... SWITCHES ... RESISTORS ... FILTERS
... RECTIFIERS ... POWER SUPPLIES.

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

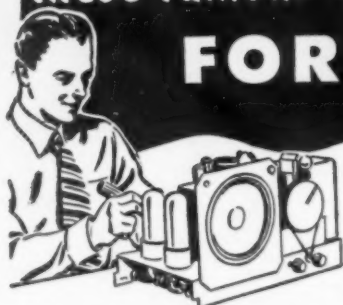
HOW'D YOU LIKE TO GET these famous Ghirardi Training Course Books FOR CHRISTMAS?



Friends or relatives are probably wondering what to give YOU this Christmas. Then why not drop a hint that nothing would please you more than Ghirardi Radio-Electronic training course books? They'll appreciate the suggestion—and you'll appreciate the books every day of your life. What finer gift could you ever hope to receive than these giant training books that make it easy as A-B-C to learn basic Radio-Electronics and to trouble-shoot and repair all kinds of radio and electronic equipment? And why not give these big books for Christmas to your own friends who are interested in radio?



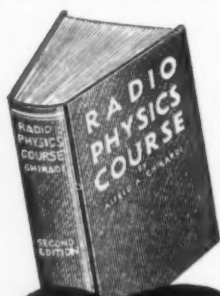BEGINNERS! LEARN BASIC RADIO-ELECTRONICS . . . as fast as you can read!



The most widely used radio training book in the world

Only \$5 for the entire course.

LEARN FAST!
LEARN RIGHT!

No matter what phase of Radio or Electronic work you'd like to specialize in, you'll need the **basic** training that Ghirardi's 3½-lb., 972-page **Radio Physics Course** book gives. More people have gotten their start from this giant book than any other book or course! On a survey among hundreds of radio service experts, engineers, instructors, etc., 9 out of 10 said that Ghirardi's **Radio Physics Course** is the finest, easiest-to-understand Radio-Electronic Training Course on the market. And you buy it for only \$5 for the complete course—on a money-back guarantee basis!

36 COURSES IN ONE!

Radio Physics Course is especially written for home study without an instructor. Nothing is omitted or condensed. Starting with a thorough, easily-understood foundation course in Basic Electricity, the book takes you step by step through the entire field of basic Radio-Electronics. Actually, **Radio Physics Course** gives you the scope of 36 complete courses in one big book. If broken into sections and sold as a series of lessons, you'd regard it as a bargain at \$50 or more. But you get it all at once! You learn as fast as you can read. Subjects that seem highly complicated in other courses are made crystal-clear both in text and by over 508 clear pictures and diagrams. Mail coupon today. Remember, you don't actually risk a cent. Our **5-Day Money-Back Guarantee** is Your Absolute Protection.

LEARN TO REPAIR RADIOS THIS FAST, EASY WAY!

You don't have to be an expert to make ordinary repairs in 4 radios out of 5! You don't need a lot of high-priced test equipment! Every receiver has its "weak" spots that give trouble first. Ghirardi has compiled case histories of these common troubles into a big 744-page **Radio Troubleshooter's Handbook**. When you want to repair a set, just look up its make and model number. 4 times out of 5 the book tells you what the trouble is—and exactly how to fix it with a few simple tools. It's a service short cut that really works. The book pays for itself in time saved the first time you use it. Smart servicemen use it on every job. Helps you repair cheap sets profitably because you don't need to waste a lot of time on them. Ideal for training new helpers.



DO TWO JOBS . . . IN THE TIME NORMALLY REQUIRED FOR ONE!

Radio Troubleshooter's Handbook tells you what to do and exactly how to do it in repairing practically every radio model in use today. And that is just the beginning. It also contains the most complete, genuinely helpful Tube Chart you've ever seen. Dozens of pages contain I-F alignment peaks for 20,000 superhets and data on I-F Transformer troubles. Hundreds of additional pages contain tables, graphs, charts and service information to help you repair any radio ever made easier, and twice as fast! You get the complete, 744-page, manual-size book for only \$5. See money-saving offer below!

Let this "AUTO-MATIC TEACHER" show you exactly how to repair OVER 4800 RADIO MODELS

Fix radios without costly test equipment!

GET COMPLETE PROFESSIONAL RADIO SERVICE TRAINING . . . At Home Without an Instructor



Makes the hard jobs easy to do!

Trains you scientifically for all phases of Radio-Electronic Service

Ghirardi's famous 1300-page **Modern Radio Servicing** is a complete, 1-volume course in **PROFESSIONAL** service methods of the kind that open doors to big-money opportunities which only scientifically trained men can grasp. It shows how to avoid guesswork by analyzing radio and other electronic circuits by professional methods. Explains how all basic types of radio test instruments work. Tells when, why, where and exactly how to use them. Shows how to troubleshoot both circuits and complete equipment; how to make repairs and replacements; how to analyze components—even how to run a successful radio service business of your own.

COMPLETE DATA ON TROUBLE-SHOOTING, INSTRUMENTS AND REPAIR

Modern Radio Servicing is invaluable as a "refresher" course for men already in the radio service business—and it's worth its weight in gold to service beginners! Everything is explained so clearly it can easily be understood at home without an instructor. 706 clear illustrations and 720 Self-Test Review Questions speed up learning. Only \$5 for the big 4-lb. book—on our **5-Day Money-Back Guarantee**. See money-saving offer in coupon.

MONEY-SAVING SPECIAL OFFER

Let Ghirardi's **Radio Troubleshooter's Handbook** save you time and money on common service jobs. Let his **Modern Radio Servicing** train you for professional service work of all kinds! Get BOTH big books for only \$9.50 (\$10.50 foreign). See Money-Saving Offer in coupon



5-DAY MONEY-BACK GUARANTEE

Dept. RN-127, Murray Hill Books, Inc.
232 Madison Ave., New York 16, N. Y.

☐ Enclosed find \$..... for which send me the Ghirardi Book(s) indicated below; or ☐ send C.O.D. (no foreign C.O.D.'s) and I will pay postman this amount plus a small postal charge when he delivers my package. If the books are not entirely satisfactory, I'll return them within 5 days and you guarantee to refund my money.

- ☐ RADIO PHYSICS COURSE \$5 (\$5.50 foreign)
- ☐ MODERN RADIO SERVICING \$5 (\$5.50 foreign)
- ☐ RADIO TROUBLESHOOTER'S HANDBOOK \$5 (\$5.50 foreign)
- ☐ MONEY-SAVING COMBINATION OFFER! Both **Modern Radio Servicing** and **Radio Troubleshooter's Handbook**, only \$9.50 for the two (\$10.50 foreign).

Name.....

Address.....

City and Zone..... State.....

Watch these three score!



Portable That's "Going Places"—Model R-1409—three-way portable, AC-DC and battery. Smart alligator-grain fabric with plastic front. 550-1700 kc. Self-contained charger increases battery life. Real beauty, exceptional performance.



Winning "Combination"—Model R-1242—combination radio and record player; 110-volt, AC-DC. Sleek, modern design in rolled-top walnut cabinet. Eye-catching grille panel. Built-in loop antenna. Single record player accommodates 10" or 12" records. Four tubes plus rectifier tube. 550-1700 kc. Compact, dependable.



Tops on Any Table—Model R-1238—table model; 110-volt, AC-DC. Handsomely designed in walnut veneer and silver-gray plastic. Striking lucite-and-chrome carrying handle, convenient and durable. Four tubes plus rectifier tube. 550-1700 kc. Built-in loop antenna. A real value.

They're fast movers *in the great line of* **DELCO RADIOS**




DELCO RADIO **A GENERAL MOTORS PRODUCT**

Delco radios are distributed nationally by United Motors Service. See your United Motors distributor about the Delco radioline.

THESE three modern-as-tomorrow Delco radios really appeal to American tastes and needs. They're a sure-fire cinch to set sales and profit records for dealers.

Each one of these smart Delco models gives you plenty to talk about in features, appearance, performance and value. Each one carries an *assurance of dependability* because it is built and backed by General Motors.

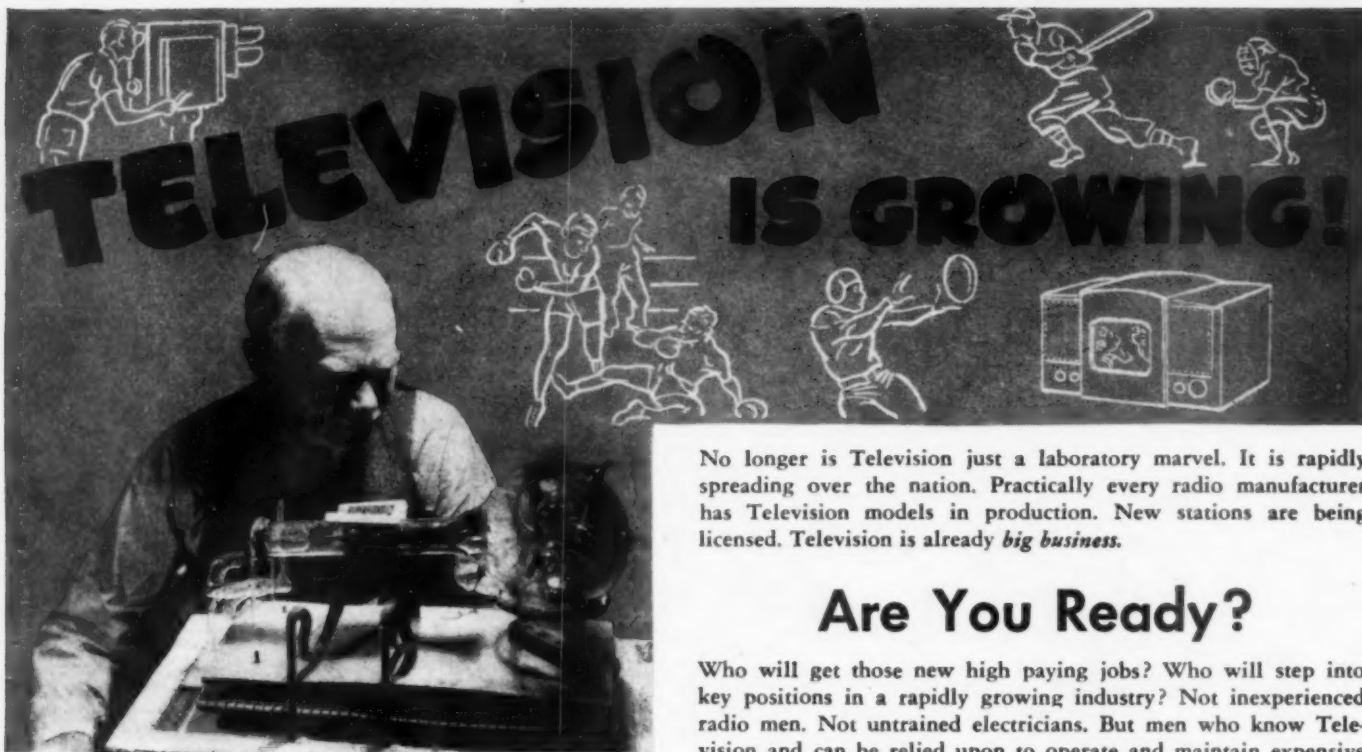You can count on Delco Radio for "the best of all that's new in radio"—and that goes for the complete line of table models, consoles and combinations. Like the original-equipment auto radios built by Delco Radio for America's leading cars, Delco home radios are a great General Motors value.



Dr. Lee de Forest

American Television—A Great Training Institution!

American Television has pioneered in Television research. Its directors have made fundamental contributions to the industry. Dr. Lee de Forest, our Director of Research and Training, is known throughout the civilized world as the "Father of Radio" through his invention of the radio tube. U. A. Sanabria, President and founder of American Television, Inc. invented the Interlace Scanning System which is now the standard of all Television. Most recently, a revolutionary new circuit which corrects a common television defect known as "ghost images" has been developed by J. M. Sanabria, head of American Television's Manufacturing Division.

Most Elaborate Training Laboratories

Every modern type of equipment obtainable has been installed for instruction purposes in what we believe to be the most extensive and elaborate Television training facilities in the world. You will find complete operating studios with the new sensitive cameras and their associated equipment. A corps of highly qualified instructors will guide your study.



No longer is Television just a laboratory marvel. It is rapidly spreading over the nation. Practically every radio manufacturer has Television models in production. New stations are being licensed. Television is already *big business*.

Are You Ready?

Who will get those new high paying jobs? Who will step into key positions in a rapidly growing industry? Not inexperienced radio men. Not untrained electricians. But men who know Television and can be relied upon to operate and maintain expensive equipment!

Start Learning TELEVISION at Home—FREE!

Prepare yourself for the endless opportunities in Television the new "American" way. Now, for the first time, you may discover in advance of entering school, just how your abilities fit into Television. If you qualify under the simple rules, you will be given a complete preliminary home study Television course absolutely free and without obligation.

Your success with the course will not only help you to decide for yourself what phase of Television you like best but will also aid us in qualifying you for residence training.

We prefer that all new resident students take this free course as it provides excellent preparation for residence study. However, there is no obligation on your part to enroll for residence training when you complete the home study course.

We urge you to take advantage of this splendid opportunity at once. Just write your name and address on a penny postcard and say: "I am interested in your free Television Course". Do it today! This offer is necessarily limited.


Approved for Veteran Training



American Television, Inc.

5050 BROADWAY

CHICAGO 40, ILLINOIS

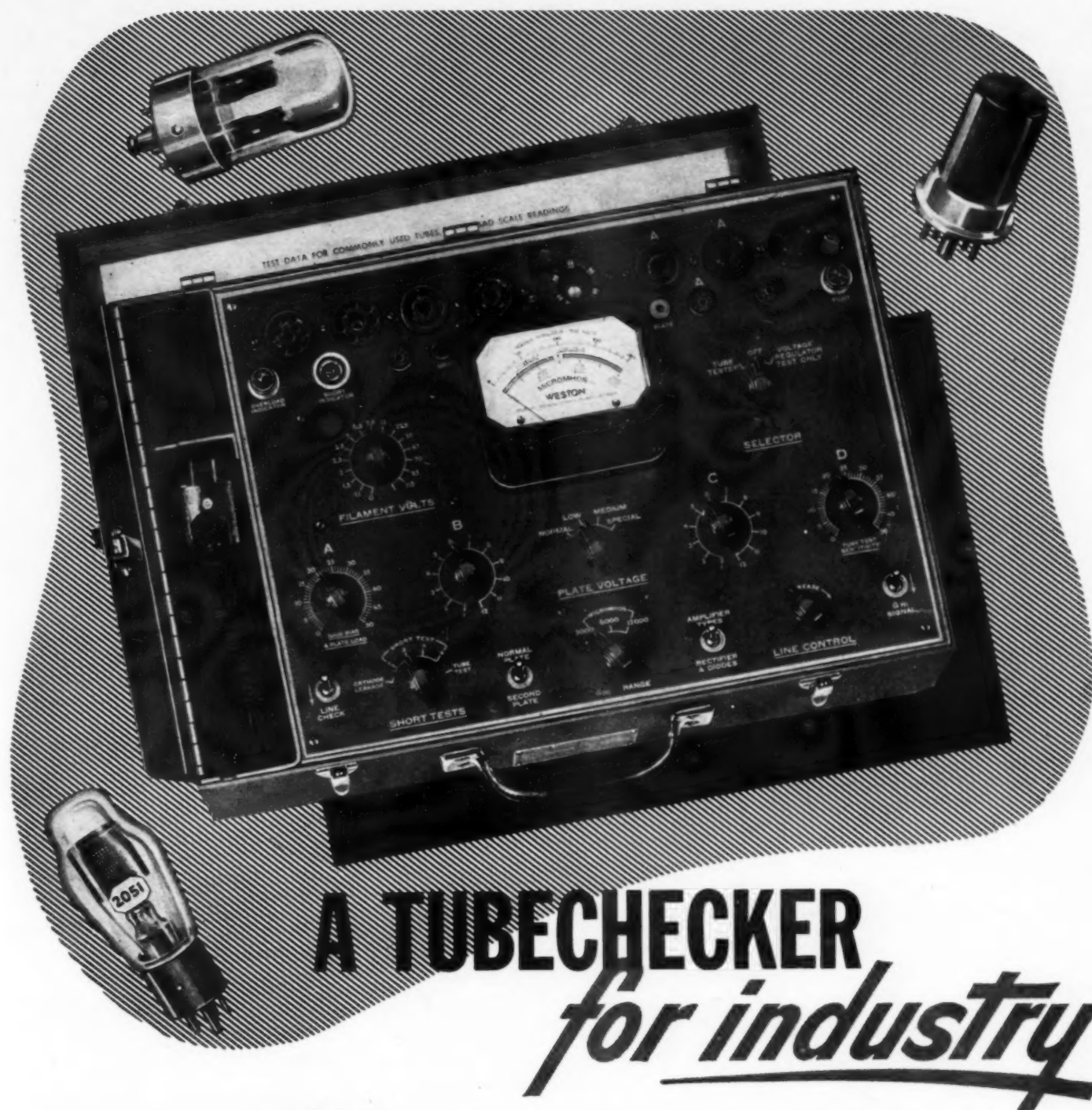

TESTS: Receiving Tubes, Voltage Regulator Tubes, low power Thyratrons

The WESTON Model 798 Mutual Conductance Tubechecker provides, for the first time, adequate tests on voltage regulator tubes, light-duty Thyratrons such as the 884, 885, OA4, 6D4, 2A4, 2050, 2051 in addition to tests on regular receiving tubes. Ranges of 12,000, 6,000, 3,000 micromhos as well as "Good-Bad" indications cover

the tube checking requirements of electronic control and radio circuits. Housed in rugged aluminum case to withstand rough usage in shop or field.

For full details consult your local WESTON representative, or write . . . WESTON Electrical Instrument Corp., 617 Frelinghuysen Ave., Newark 5, N. J.

WESTON *Instruments*

ALBANY • ATLANTA • BOSTON • BUFFALO • CHARLOTTE • CHICAGO • CINCINNATI • CLEVELAND • DALLAS • DENVER • DETROIT • JACKSONVILLE • KNOXVILLE • LITTLE ROCK • LOS ANGELES • MERIDEN • MINNEAPOLIS • NEWARK
NEW ORLEANS • NEW YORK • PHILADELPHIA • PHOENIX • PITTSBURGH • ROCHESTER • SAN FRANCISCO • SEATTLE • ST. LOUIS • SYRACUSE • IN CANADA, NORTHERN ELECTRIC CO., LTD., POWERLITE DEVICES, LTD.

December, 1947

HQ-129-X




Full range .54 to 31 mc in six accurately calibrated bands • Band spread with four calibrated ham bands and all-purpose scale • Variable selectivity crystal filter for phone or cw. • Antenna compensator for maximum image rejection and high sensitivity • Voltage regulation. Noise limiter that really kills noise • Adjustable S meter • *Three* IF stages . . . The HQ-129-X has every up-to-the-minute improvement that radio science has so far developed for amateur radio receivers.



FOUR • 20
↓ **TRANSMITTER**



FOUR • 11
↓ **MODULATOR**

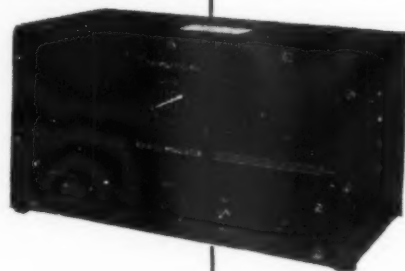

The Four-20 makes an efficient exciter for any final amplifier from a hundred watts up to a tetrode kilowatt. The Four-11 will drive a high power modulator. Why not build the big rig yourself? Use the Four-20 to drive the final and the Four-11 to push the modulator.




WRITE FOR TECHNICAL BOOKLET

HAMMARLUND

THE HAMMARLUND MFG. CO., INC., 460 W. 34TH ST., NEW YORK 1, N.Y.
MANUFACTURERS OF PRECISION COMMUNICATIONS EQUIPMENT

Television TUBES By The Thousands

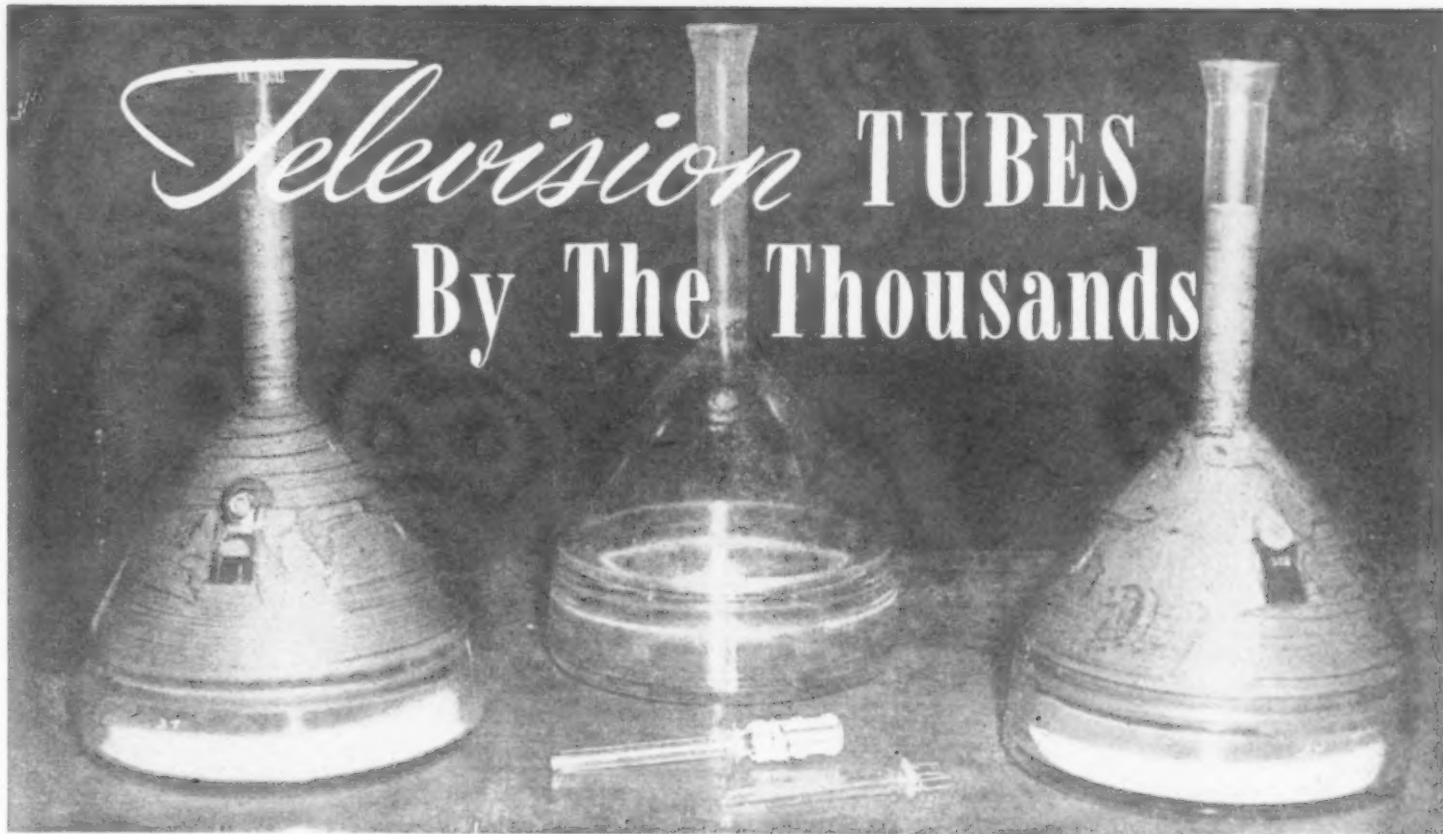

1 Completed 10" kinescope at left. Center unit is bulb blank in which the "button" has been sealed. In front of tube are the stem and completed tube element assembly. Right hand bulb shows fluorescent coating and colloidal graphite lining.

By FRANK E. BUTLER

A modern miracle of mass production is typified by the ingenious wedding of automatic machinery, technical skills, and quality-controlled materials.

THE Age of television is at hand and to speed its progress toward perfection, groups of technical experts in widely divergent professions such as electronics, optics, and the glass industries are contributing their share of scientific knowledge and experience to this end.

The technological advance is so rapid, both in monochrome and color television transmission and receiving equipment, that pictures by both systems are now being shown with surprising realism and clarity. Only very little of this advanced development remains in the laboratory stage and this is sufficiently developed to insure its appearance in homes much sooner than most of us had expected.

The rapidity and skill with which this progress has been made by television laboratories and their confidence in the future of television is evidenced by the building of new plants and the designing of special machinery for the manufacture of equipment. Therefore a peep behind the scenes of television activity should prove of unusual interest at this time.

The heart of television is the *iconoscope*—the electronic device capable of detecting the image or scene of ac-


tion that is to be televised through space, then subsequently translating the reflected light into electric impulses.


The *kinescope* is a similar electronic tube which reverses the above action whereby the televised impres-

sions are transformed back into light to form a reproduced image or "picture" on the sensitive face of the tube. To create these two companion tubes, which must combine delicateness, ruggedness, and utmost sensitivity, requires the use of nimble fingers, keen eyes, highly developed skills, modern automatic machinery and the best techniques that can be devised by the several different industries involved in the manufacture of tubes.

The factory where these tubes are produced must be fully air condi-

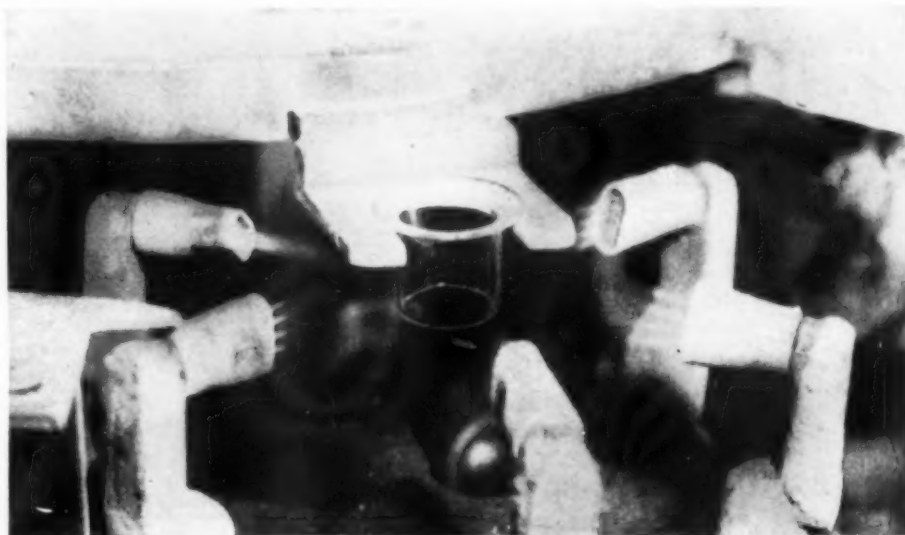2 Flare machine in which G12 glass tubing is cut off and pre-formed to provide a flat pressed stem for the tube. Glass parts are heated at various stages from 600-900° C.



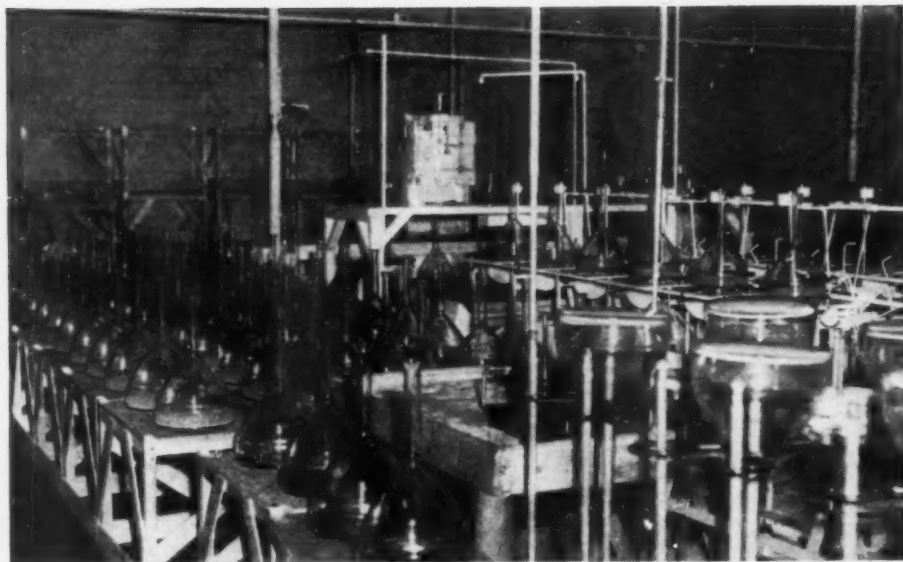

3 Hundreds of 10-inch kinescope bulbs lined up ready for the application of the fluorescent coating to the inside. Each tube receives a measured amount of solution.




4 Operators prepare the fluorescent solution which is used in the kinescopes to form the picture screen of the video tube. Quality control of the solution is vitally important here.

5 Fluorescent coating, in solution, is carefully poured into a prepared kinescope bulb.



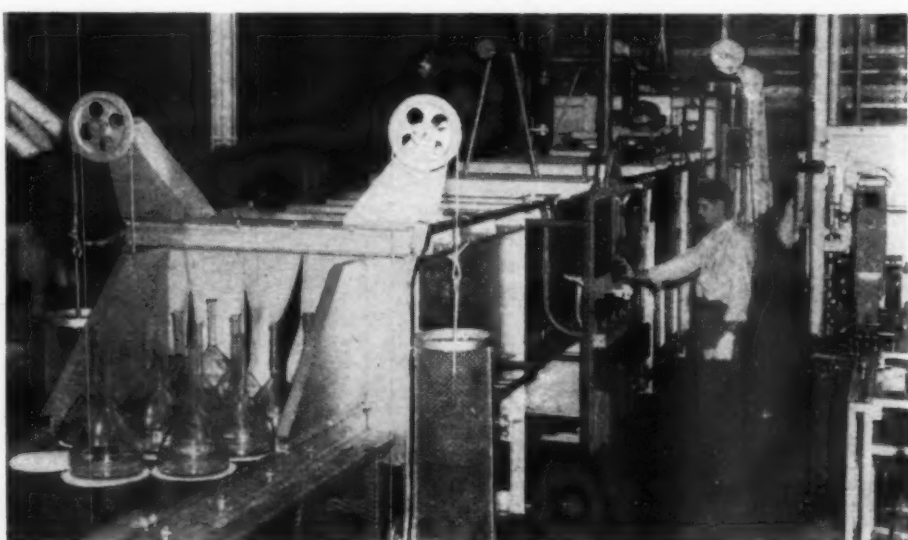6 Next step is the insertion of the "button" in the side of the bulb by means of a gas-fired torch. Operator softens the glass, punctures a hole, and inserts button.



tioned and the humidity level must be maintained at a predetermined level. In addition, the factory must also be equipped with dust filters in order to eliminate impurities which might affect the sensitive tube elements.

There are two kinds of kinescopes produced—one known as the electronic *direct view* type, and the other as the *projection* type. From the small kinescope which produces exceptionally brilliant images which are subsequently enlarged *optically* for projection on a viewing screen of a 7½ x 10 or 18 x 24 foot theater size, to the largest kinescopes which have a 10 or 12 inch face from which the image is viewed directly (without enlargement), there are many precise and intricate operations which must be performed on both the tube elements and the glass bulb.

One of the first glass operations in the production of kinescopes or iconoscopes is to make the flare of the stem which holds the elements. This is done on the flare machine shown in Fig. 2. Here gas fuel is used to heat the glass parts as they index around the automatic machine, in various stages, to temperatures ranging from 600° C. to 900° C. After a small section has been cut off and the end flared, the bottom portion is heated by a special gas flame pattern which places the heat exactly where it is wanted at the proper temperature for flat pressing. Heating time is controlled by the speed at which the machine indexes from station to station.

A battery of automatic flare machines is used in making the glass stems in which the tube element supporting the lead-in wires are sealed. Specially designed gas burners, emitting predetermined flame patterns heat the glass tubing to various stages of viscosity in order that it may be flat pressed into a stem. All of the equipment that utilizes heat in any form for processing is effi-

ciently hooded and ventilated to carry off excess heat and the products of combustion.

When this part has been formed, the lead-in wires to the tube elements are inserted and the assembled element units are placed on another automatic gas-fired machine where special flame patterns heat those parts of the stem to just the proper temperature and for just the correct time to effectively seal the wires into the glass stem. Annealing takes place immediately after the part has reached the last position on the machine. The unit is then ready for mounting the tube electrodes, after which it is prepared to be sealed into a bulb-blank, which resembles a large glass funnel with a long stem.

The bulb or kinescope blanks are subjected to many processes and operations; the first being a thorough washing, inside and out, after which they are placed in specially



7 Baking on the colloidal graphite coating requires approximately one and a half hours at 400° C in a gas-fired oven. A specially designed oven is used in this operation.



8 A non-reflecting carbon coating, designed to keep stray electrons from the picture screen, is next applied with a long-handled brush.

9 The operator is shown installing the cathode-ray gun in a modern type image orthicon camera tube which is used for video pickups.

constructed racks in the "settling-room" Fig. 3. This room is constructed on its own foundation and the floor is composed of a heavy concrete slab floating on a layer of cork. There is no physical connection to any other part of the building, thus eliminating any transmission of vibration. A measured quantity of liquid containing a fluorescent substance is then placed in each tube. The preparation of this fluorescent solution requires a high degree of skill and accuracy. The operation is shown in Fig. 4.

Next, the coating, in suspension, is carefully and accurately poured into the kinescope bulb. See Fig. 5. Slowly, the solid, active fluorescent material settles on that part of the tube face on which the electrons react to produce the image. When the settling process is complete, the re-

maining liquid is carefully decanted.


The next step in the manufacture of the tube is the insertion of a "button" in the side of the bulb. This operation, which is illustrated in Fig. 6, is performed by means of a gas-fired torch. The operator softens the glass, punctures a small hole and inserts the "button" or electrical contact which is then hermetically sealed in the tapered section of the bulb. The tube is then annealed at 450° C. by means of a continuous gas-fired radiant tube glasslehr where the cycle of passing through the heated air ranges from four to six hours, depending on the size of the tube.

The inside of the bulb is next coated with a colloidal graphite mixture which serves to carry off the electron charges after they bounce back from the screen. The grounded electrical


circuit is through the "button" previously described. Next, this inner graphite coating is subjected to a baking cycle which is performed at temperatures of 400° C. for approximately one and a half hours. This operation is shown in Fig. 7.

The operator now applies a coating of non-reflecting carbon to the interior of the tube by means of a long handled brush (See Fig. 8). This coating keeps stray electrons from the picture screen.

Fig. 9 shows the operator adjusting the delicate electrical components that are to be inserted in the tube. At this stage of production, the prepared bulb is ready to be sealed to the glass stem which supports the internal elements, or electron gun. This operation takes place on a completely automatic gas-fired sealing

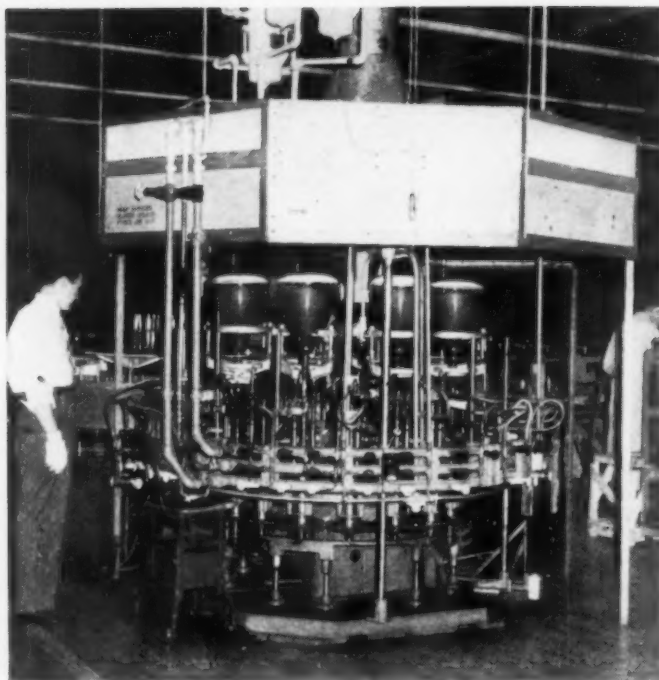

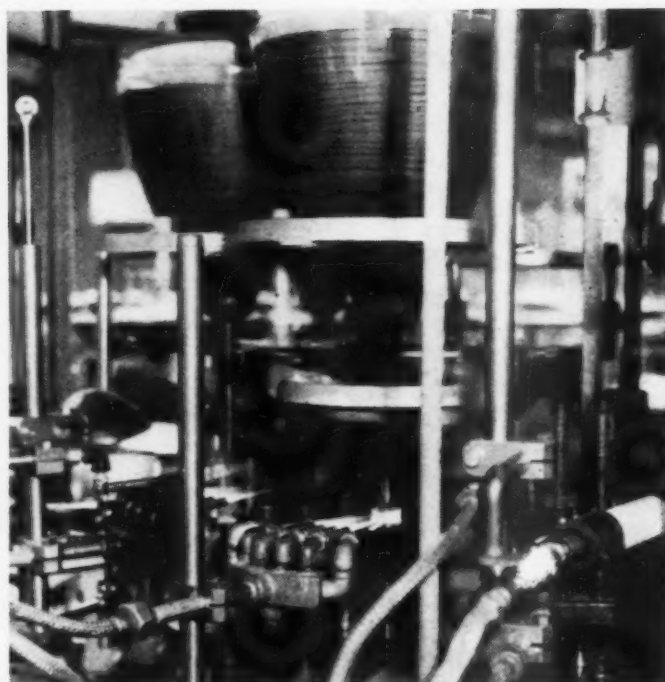10 Automatic sealing machine where elements are set in tube, the flare and bulb are sealed and the collet is cut off.



11 Close-up view of operation in which collet is cut off. The gas burner shown at right performs the annealing operation.

machine (Fig. 10) where the elements are set in the tube, the flare and bulb are sealed, and the collet cut off. These operations take place as the tubes index around the machine to their respective stations where varying patterns of gas flames perform the successive operations on the glass. At the final station the excess neck of the bulb, or collet, is cut off when the No. 6 lime glass of which the kinescope blanks are made is heated to 1050° C. by a needle flame which produces a clean, sharp cut.

After sealing, the tube progresses to an exhaust machine where an extremely high vacuum is developed. While on this machine, the glass bulb is heated by radiant heaters to its

softening point to assist the vacuum pump in removing occluded moisture and gases. The electron gun and other internal elements are heated by high frequency induction methods and, at another stage in the process, working voltages are applied to the tube elements themselves.

Fig. 11 shows a close-up view of the six needle gas flames which concentrate on the bulb neck where the collet is cut off as the tube revolves in the flame. The large gas burner, shown at the right of the photograph, performs the annealing operation. When the vacuum process has reached its final position, the tube is "tipped off"—an operation which seals the tube permanently and sev-

ers its connection to the vacuum pump.

After the tube has been evacuated and severed from the exhaust machine, the operator threads the lead-in wires into the socket base of the kinescope. This operation is shown in Fig. 12.

Final tests are then run on the complete kinescopes. The operator (Fig. 14) uses a special chart as a reference standard. Following this testing, the tubes undergo a 500-hour operational test (Fig. 13).

Larger television pictures obtainable in the projection system are the result of an optical development which is an outgrowth of a discovery (Continued on page 170)

12 Operator threads lead-in wires into socket base of a kinescope after the air has been exhausted from the tube envelope.



13 Technician checking kinescope picture tubes during a 500-hour continuous performance test run at the home plant.



14 One of the test procedures used in checking the performance of kinescopes used in home television receiving sets.



PUBLICITY MEANS *Sales!*



By **PHILIP LESLY**
Vice-Pres., Harry Coleman & Co.

A carefully planned publicity campaign can pay off for the dealer. Follow these basic rules!

MODERN merchandising involves many factors—getting salable merchandise, proper pricing, attractive store fronts, effective display, good salesmanship, advertising—and the reputation of the dealer. This one point, the most intangible of all, can make all the others ineffective if it is neglected, or can bring surprising returns if it is developed expertly.

Your reputation among your prospective customers depends on two things—the way you do business, and how much the public knows about you and your business. They go together and cannot be separated. If your business methods are basically unsound, no amount of publicity will set them right. If you don't let the public know about you, it will take a long time for your sound policies to pay off in sales.

Almost all dealers today know the basic requirements of a good business reputation:

1. Be fair to all customers. Play no favorites. Set a price on every item and offer that same price to everyone.
2. Be scrupulously honest. Be sure every customer knows exactly what he's paying for and gets a receipt for every purchase.
3. Provide liberal guarantees. Ex-

change merchandise without question if the customer is dissatisfied.

4. Offer as much service as you can afford—pickup and delivery, installations, free check-ups and estimates.

5. Remember the little extra things that please the customer—prompt delivery, etc.

What very few dealers understand is the effectiveness of publicity in letting their prospects know what they have to offer, and in building up the name of the store to the point where it attracts customers.

This familiarity of a name influences everybody's daily purchases of products: *Coca Cola*, *Ivory soap*, *Pepsodent* toothpaste and hundreds of other items. It also frequently determines the choice of store where these items and others are bought. Such places as *Macy's* and *Marshall Field's* sell more of the standard-priced, nationally advertised items than their competitors because their very names attract customers for everything they sell.

You as a dealer have two ways of attracting prospects. One is by offering "X" brand of product, which has been advertised and publicized so that many buyers will seek it out or react favorably when they find it. You, by carrying this brand, automatically gain the benefits of the manufacturer's publicity. The other

way is by making your own store the attraction, so that the prospect will say, "Let's get our radio at Milligan's" and then come to you to see what you have to offer. The ideal combination of the well-publicized product and the well-publicized store is what makes the cash register jingle.

With this in mind, and once you have firmly established the requirements of a good reputation, it will pay to begin a systematic campaign to make your store's name familiar and well-regarded.

Here are the basic principles of a good publicity program for the radio and appliance dealer:

1. Make the familiarizing of your store's name your primary objective. Before you do anything along the publicity line, be sure it will help reach this goal.

2. Simplify the path to the objective. Many of your opportunities for newspaper stories, radio mentions, and word-of-mouth comments will come from your personal activities. These won't help build up your store very much unless your name immediately brings to mind the name of the store. For this reason, it is wise to have your name a part of the store's name; "Milligan's Appliance Center" is better than "Ideal Appliance Center." It

(Continued on page 128)

ELECTRONIC PHOTOFLASH UNIT

By

W. G. MANY


Cornell-Dubilier Electric Corp.



Fig. 1. Close-up of the flash gun showing the camera mounting bracket, reflector, and synchronizer assembly. The push-button on handle is the manual trip switch, while the cable release synchronizer operates both shutter and flash.

Several new types of flash tubes make possible a photoflash suitable for high speed indoor work.

Fig. 2. The two 25 μ d. storage condensers are mounted in the lower compartment.

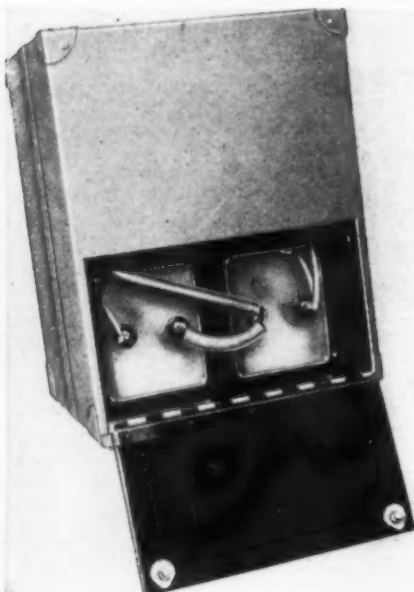

THE growing enthusiasm for electronic photoflash units on the part of both radio and photo amateurs and professionals has brought forth many new and interesting circuit and component part developments.

This semi-portable flash unit is designed to be used for any general indoor work and may be constructed of readily available parts. The unit is housed in a professional-looking war surplus cabinet which was originally designed for the SCR-211 frequency meter set.

The circuit is comprised of two principal units, a power supply and two photoflash storage condensers housed in the carrying case, and the triggering circuit and flash bulb which are housed in the flash gun handle. Fig. 5 shows the correct mounting of the simple power supply chassis in the cabinet, while Fig. 2 is a rear view of the unit showing the two condensers mounted in place in the lower section of the case.

The bakelite front panel measures

7 $\frac{1}{4}$ " x 9 $\frac{1}{4}$ " with a sub-base panel attached with brackets to provide mounting facilities for the various controls. The panel carries an a.c. on-off switch, a pilot light for the a.c. line, the 117 volt power line receptacle, a neon pilot light for the high voltage, and a coaxial connector for the lead to the flash gun. In the center of the panel is a heavy duty push-button switch for discharging the condenser bank through the 100 ohm, 100 watt resistor. It is strongly recommended, as a safety factor, that the button be pushed immediately after the power line switch is thrown to the "off" position. A slight snap of the discharge and the neon pilot being extinguished indicates that the condensers are properly discharged.

There is one point that must always be borne in mind in both the construction and operation of this photoflash unit—**DANGER—HIGH VOLTAGE**. Constructors might find it advisable to paint this warning in red letters on both sides of the cabinet as a constant reminder and as a caution to those who might be tempted to inspect the unit while it is in operation.

The over 2000 volts from the UTC Type PFI photoflash transformer is rectified through a 2X2 tube to charge the storage condensers. A tap on the transformer supplies the 2.75 volts a.c. for the rectifier tube filament. These components, along with the 100 ohm safety resistor and the series of six carbon resistors which are used as a power supply bleeder, complete the cased part of the circuit. The two rectangular can type 25 μ d., 2000 volt condensers are mounted in the lower compartment of the cabinet.

The handle of the flash gun houses a miniature series trigger tube, a model aircraft spark coil, the triggering switch, and the flash tube. A small GE flex switch or micro-switch actuates the gun manually and a socket is paralleled across this switch to provide shutter synchronization.

The new 0A5 trigger tube proved ideal for mounting in the handle of the gun as the system provides little

RADIO NEWS

delay and rapid ionization yet allows the unit to be used with almost any type of external or built-in camera flash control. The size of this tube lends itself nicely to mounting directly in the handle of the flash unit, as can be seen in Fig. 4. The switch on the gun is a manual trip for those who use the "open-flash-shut" method of taking pictures.

The handle of the gun is made from a length of heavy bakelite tubing, 13" long by 1 1/8" i.d. A piece of bakelite tubing, 1 1/8" o.d. and 1/16" thick, was cut in half lengthwise to fit inside of the tube handle. On this half-tube were mounted the seven 1/2 watt molded bakelite insulated carbon resistors, spark coil, tubular paper condensers, miniature socket, and the OA5 trigger tube. Wiring was done with light polystyrene covered stranded copper wire, with care being taken to keep the high voltage leads well separated from ground and other leads. A seven foot length of single conductor and copper braid coaxial cable, with polystyrene insulation capable of withstanding over 2000 volts, is brought out through a hole made at one side of the bakelite disc cover which is used at the bottom of the handle.

The socket for the Sylvania Type R4330 flash tube was made from an Amphenol octal base, voltage-safety socket with the upper molded shell cut off and the unused pins removed. This socket is mounted by means of two small flathead screws. The entire assembly, mounted on the half-tube, can now be inserted into the handle. An Amphenol 93-series single conductor coaxial connector is finally connected at the end of the coaxial lead ready to be inserted into the companion connector on the panel of the power supply unit.

In operation, the storage condensers will charge quickly but it is advisable

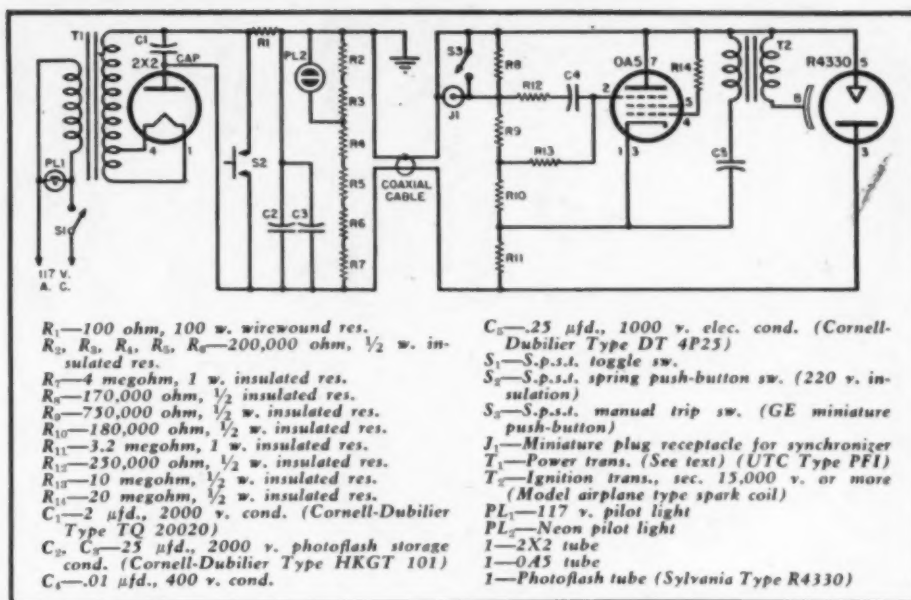


Fig. 3. Wiring diagram of the power supply unit and trigger circuit of photoflash. Power supply assembly is shown at left and gun handle assembly is shown at right.

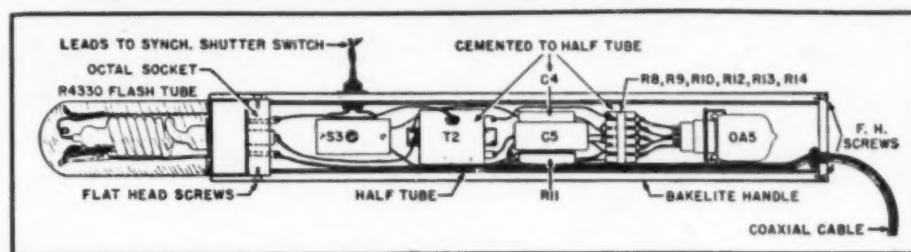


Fig. 4. Sketch showing the flash gun construction and layout of parts in bakelite tube handle. By removing the two screws in the octal socket and connections to the manual trip switch the entire assembly mounted in the half tube can be readily removed for inspection. Care must be taken to have high voltage leads well insulated and separated from ground and spark coil leads to prevent flashovers.

to allow about 15 seconds between flashes to assure time for the condensers to recharge. A weak flash or none at all will result in a poorly exposed negative.

The manufacturer's rated light output of the flash tube is approximately 12,000,000 lumens, and with internal synchronization, may be used at any shutter speed.

Fig. 5. Complete photoflash consisting of power supply in the cabinet and auxiliary triggering circuit in flash gun handle.



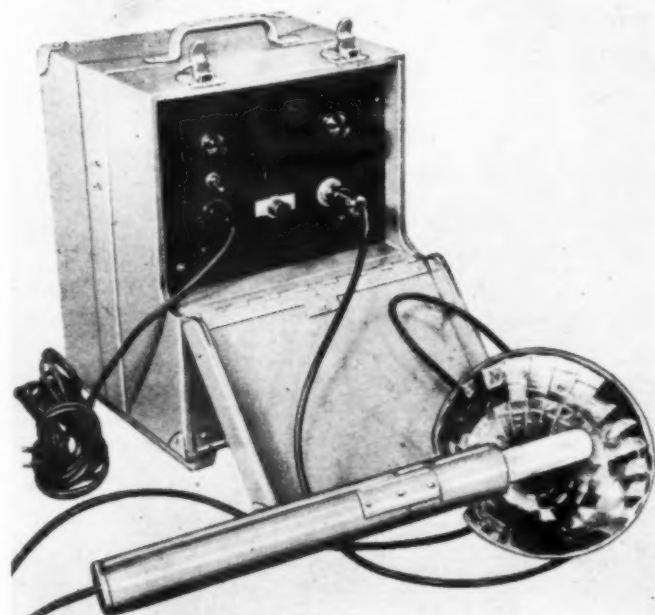


Fig. 6. Power unit with front panel removed to show arrangement of parts. Two leads connect unit to storage condensers.

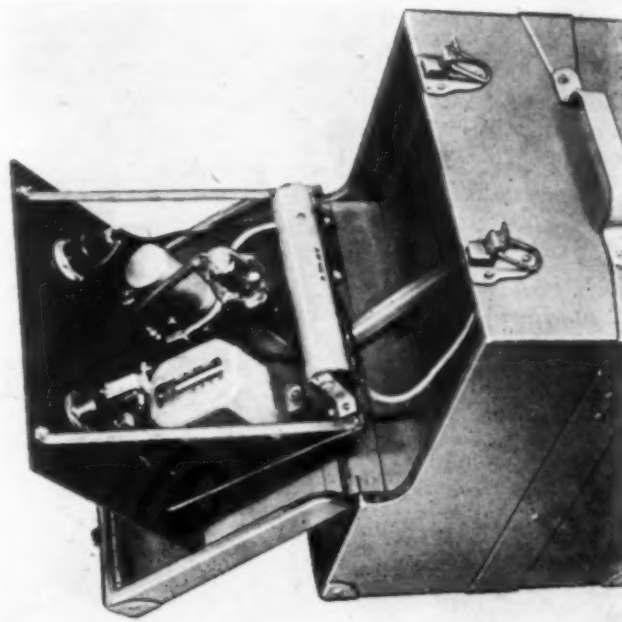

Beginners' TRAFFIC TRANSMITTER

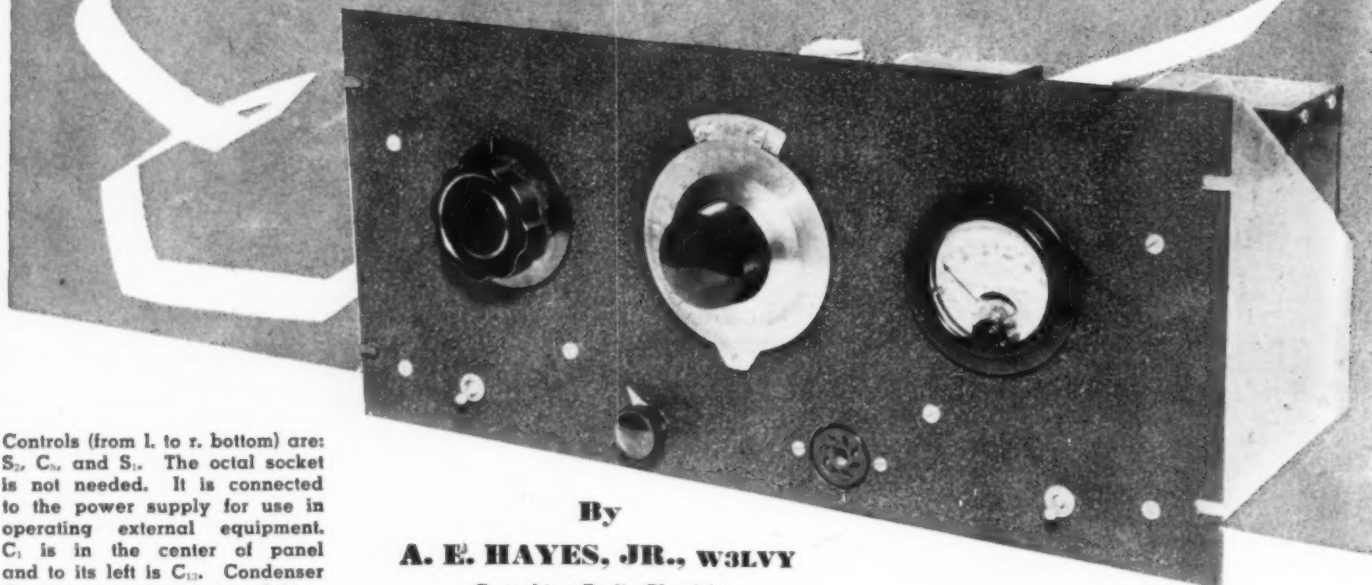

Controls (from l. to r. bottom) are: S_2 , C_1 , and S_1 . The octal socket is not needed. It is connected to the power supply for use in operating external equipment. C_1 is in the center of panel and to its left is C_{12} . Condenser C_{14} is mounted on rear flange.

By

A. E. HAYES, JR., W3LVY

Consulting Radio Physicist

Covers 80 and 40 meter bands without coil change and incorporates a v.f.o. with cathode keying.

WHEN the newcomer breaks into the traffic handling game he soon finds that his "Beginners' Transmitter" lacks several features which are essential to the traffic man and which are concerned with the oscillator circuit. The average beginner has a crystal controlled transmitter having an output of between twenty-five and fifty watts, and, more often than not, the unit is keyed in the amplifier circuit. Thus, break-in operation is impossible, and it is break-in that has contributed most during the past several years to the speed and efficiency of our major nets.

Keying the crystal oscillator is not much of a problem, as any reasonably good crystal will key quite satisfactorily up to 25 or 30 words per minute providing the principles of good design are incorporated in the circuit. In virtually any of the amateur handbooks there is a variety of crystal oscillators designed for oscillator keying.

Due to the relatively new procedure of operating most of the major traffic nets on a number of frequencies simultaneously, that is, having stations swapping messages on a number of different frequencies above and below the nominal net frequency, the crystal oscillator has become almost a "dead pigeon" due to the expense of procuring the necessary number of crystals.

Another procedure that multiplies this "cost factor" of crystals is the fact that an individual station may often be called upon by the Net Control Station to QSY to the frequency of another net to see if they have any traffic. A good variable frequency oscillator, or v.f.o., is, therefore, almost a necessity.

The above-listed requirements would seem to pose a difficult problem, a v.f.o. that keys well. In most instances the newcomer, examining a possible v.f.o. transmitter diagram, is presented with a circuit including at least an electron-coupled oscillator, one or two "Class A" buffers to isolate the oscillator from the remainder of the circuit, and a driver; all this before the final stage is considered. It is small wonder, then, that the beginner usually sticks to his simple crystal controlled transmitter, and thus is effectively prevented from getting into the traffic game.

It is the object of this article to describe a transmitter having a v.f.o. that is beyond reproach, both from the standpoint of frequency stability, and of "keyability." The transmitter to be described was built by the writer after a careful consideration of the design problems involved, and has been used nightly on one of the largest and fastest nets in the country (The Traffic Outlet), and on the very formal ARRL Trunk Line C. Reports are uniformly

all that any operator could desire.

The following specifications were decided upon, before proceeding, as the framework into which the transmitter must fit:

1. Power input to the final tube of about 50 watts.
2. Unit construction—that is, the entire unit including power supply and antenna tuning network must fit into a single 8 $\frac{3}{4}$ inch relay rack cabinet.
3. An antenna tuning network which effectively couples power into an antenna having any length from 25 feet to 500 feet or more.
4. A v.f.o. having no measurable drift after a 15 minute warmup period, and having a keying characteristic with no perceptible "chirp."
5. Eighty meter or forty meter operation without coil changes.

It was decided to first attempt a simple two-stage transmitter, a simple oscillator-amplifier arrangement. Reference to all of the established texts indicated that such an arrangement could not possibly be satisfactory, due to the lack of isolation between the frequency determining circuits and the power circuits, etc., but we proceeded, and evolved the circuit shown in Fig. 1.

In the circuit, the 6V6 oscillator is connected in a conventional electron-coupled Hartley oscillator arrangement, the frequency of which is determined by the tank circuit formed by the paralleled group comprising the condensers C_1 , C_2 , C_3 , and the inductor L_1 . Two things of top impor-

tance must be observed in the construction of the oscillator—the .001 μ fd. padding condenser C_5 must be of the type (as for example, *Aerovox* Type 1570-257L) capable of carrying a large radio frequency current and the inductor must be wound of large diameter wire on an extremely rigid, low-loss form. The coil form used in the transmitter illustrated was one of the ribbed ceramic forms available in many of the government surplus units on the market. The entire tank circuit must be wired with heavy wire, preferably silver-plated if such is available, and must be arranged in such a fashion that circuit losses are kept at a minimum. The screen and plate voltages of the oscillator are stabilized between very narrow limits by the regulator tubes V_1 and V_2 . The sliding tap on the resistor R_1 is adjusted so that the current through the regulators is about 30 ma. in the "key up" condition.

The oscillator is coupled through a condenser C_6 to the grid of the 807 amplifier, and the screen of the 807 is tied to the regulated 255 volts across the series-connected regulators. This latter precaution, though unconventional, serves to eliminate the last traces of chirp on the keyed signal. The cathodes of both the 6V6 and the 807 are effectively tied together and connected to ground through the resistor R_2 , across which the key is connected through the open-circuit jack J_1 . The use of the resistor R_2 in shunt with the key serves to greatly reduce any key clicks which might be produced by conventional cathode keying arrangements.

The amplifier is connected to the antenna-ground system through a modified pi-section tuning network, and the switch S_2 serves to permit the amplifier to supply power to the antenna in either the 80 or 40 meter bands. It will be found that this output arrangement allows the operator to use an antenna of almost any conceivable length, a feature of importance for those of us who must live in apartments and must be satisfied with a simple wire leading out the window to the nearest tree.

By way of explanation, it must be pointed out that the condenser C_5 is of such large physical size in order to minimize the heating effect due to r.f. losses through it. The less the heating of the components of a v.f.o. tank circuit the better, and in this case it is impossible to detect any rise in temperature over the ambient of any component except the 6V6 after several hours of operation. The constants of the grid tank circuit of the oscillator are selected to provide substantially 100 per-cent bandspread of the eighty meter c.w. band. The actual calibration curve, as measured, is illustrated in Fig. 2. It will be seen that the calibration is essentially linear except for a slight curvature at the low frequency end of the band. This is to be expected in the type of bandspreading circuit used. The small trimmer C_2 adjusted originally to make the band edges

December, 1947

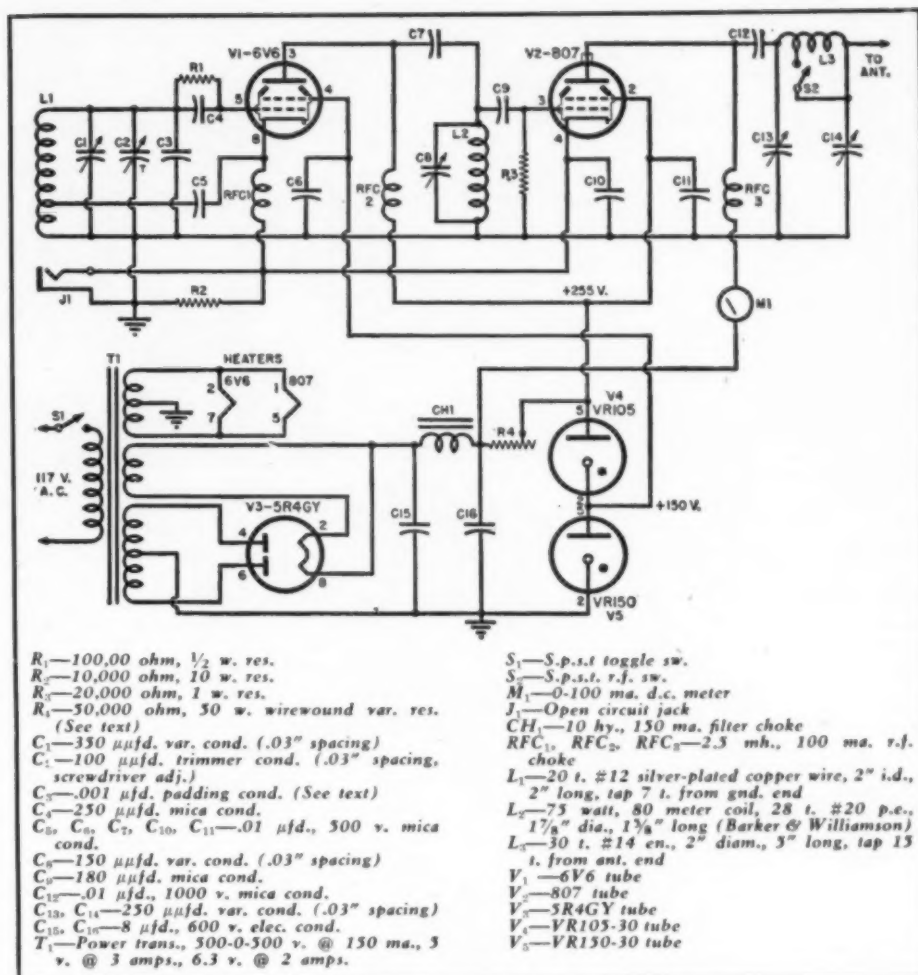


Fig. 1. Circuit diagram—a conventional Hartley oscillator is used.

"center up" on the tuning dial, may be used to correct the calibration providing any long term drift due to tube aging or the like is found. No such effect has been observed by the writer after several hours of operation.

In operation the grid circuit of the oscillator covers the range 1750 to 2000 kc. and the plate tank circuit C_5L_2 is tuned to the second harmonic



range which is the eighty meter band. The plate circuit of the 807 is tuned to 80 meters when the switch S_2 is in the "open" position, and to the 40 meter band when the switch is closed. The 807 thus functions as a doubler on 40, but it has been found that with the amount of drive available from the oscillator the output on 40 may be

(Continued on page 171)

Rear view shows placement of various above-chassis components.



Fig. 1. The Browning RJ-14 (top) and the RJ-12 (bottom) tuners represent two of the many different makes of commercially built, high quality tuners that may be used for recording off-the-air programs.

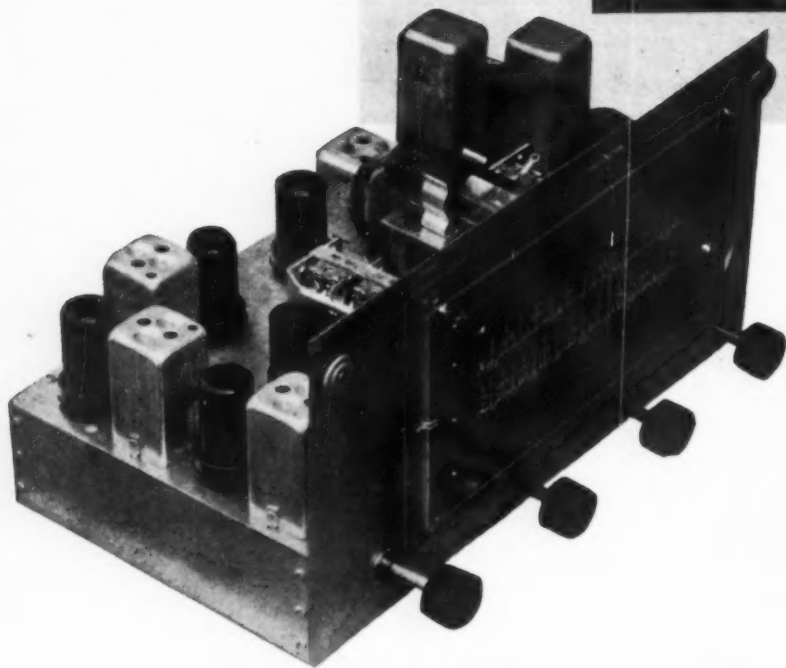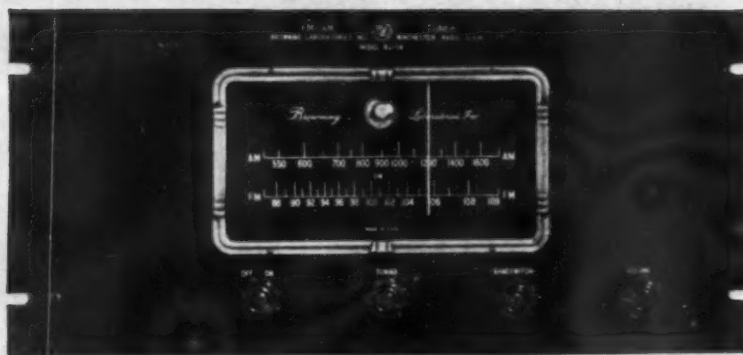

Part 10. Covering a discussion of two representative tuners, well suited to recording radio programs directly off-the-air.

By OLIVER READ
Editor, RADIO NEWS

The Recording and Reproduction of Sound

ONE of the major requirements for the recordist is a good high quality tuner for picking up signals from local transmitters and, in particular, for purposes of recording high quality music or other entertainment on his discs, etc. The requirements permit latitude in the selection of a tuner as we may begin with a simple two or three tube job employing tuned r.f. circuits, and later procure one of the universal FM-AM tuners, such as the one to be described, when we wish the ultimate in FM-AM reception for recording purposes or public address installations.

Such tuners include the *Browning RJ-12* and *RJ-14*, Fig. 1, which are designed for high fidelity reception in the 88-108 mc. FM band as well as the standard AM broadcast band. This tuner is designed for maximum performance when used with a 300-ohm FM antenna. Almost any commercial FM antenna having this impedance should work satisfactorily. It is im-

portant that no part of the antenna system be grounded because of the balanced feed required on FM operation. On AM operation, the entire antenna and feeder act as the antenna. The antenna system should, therefore, be located as high as possible. For those who wish to build their own antenna, a drawing has been provided to furnish the necessary information. See Fig. 3.

Shielded leads from the tuner to the recording amplifier are essential. When making up the cables, the center conductor should be stripped, tinned and inserted in the center sleeve of the male connector and heated until the solder flows, making a good joint. It is well to bring the braid up on the outside shell of the plug and solder all the way around. There are some cases where the shield on the lead between the audio output of the tuner and the amplifier employed may not be a sufficient ground bond between the two. In cases where

there is any hum, not present in the amplifier itself, bonding of the amplifier and tuner with copper braid of No. 16 or larger wire, should be used.

The power requirements for the tuner are 250 volts d.c. at 65 milliamperes and 6.3 volts a.c. or d.c. at 4 amperes. Occasionally the voltages are available from the recording amplifier. If these voltages are not available, a separate power supply should be used. A schematic diagram of such a unit is incorporated in the diagram Fig. 5.

The FM section of the tuner employs the famous Armstrong circuit. In the r.f. portion we find several new miniature type tubes (Fig. 5), a 6BA6 r.f. amplifier, a 6BE6 mixer, and a 6C4 triode oscillator. Following the mixer are two i.f. amplifier stages that operate at a center frequency of 8.25 mc. Excellent gain is realized in the r.f. stage and in its conversion to the intermediate frequency amplifier. In order to obtain the most effective

quieting, two limiters are used in cascade. Assuming that proper limiting is used, then the major source of distortion in FM circuits lies in the non-linearity of the discriminator characteristic. When this curve of frequency versus output voltage is linear over the range of modulation, there can be no distortion in detection. This tuner has an excellent linear characteristic. High frequency pre-emphasis, purposely introduced at the transmitter, must be compensated for in the tuner if we are to obtain a linear output voltage. A suitable high frequency attenuator compensates for the standard degree of pre-emphasis which is inserted at the transmitter.

The superheterodyne circuit employed in the AM section has one r.f. stage and one i.f. stage. It further employs a diode detector to provide audio and a.v.c. voltage. A sensitivity of one microvolt or better over the entire band is made possible by employing recently developed tubes. The bandpass of the i.f. amplifier provides a high selectivity much desired for average interference-free reception. Noise reduction benefits are realized due to this selectivity and yet the quality of reproduction remains excellent.

One of the features of this commercially built tuner is the insertion of a wave trap that is tuned to 450 kc. to provide a low impedance path to ground for any signal that might otherwise cause interference. This is to eliminate local high power, low frequency code stations in particular.

Especially designed recording amplifiers will be described in later chapters. They are well suited for use in conjunction with the *Browning* tuner as well as the simple home-made tuner to be described in the following paragraphs.

T.R.F. Tuner

A high fidelity radio frequency tuner suitable for use with a recording amplifier or public address system may be constructed from parts readily available in the average junk box. The tuner to be described was designed by *E. Bruce Pray, Engineer, Electronics Division, Sylvania Electric Products, Inc.*

In addition to its being useful for recording or in conjunction with large permanent p.a. and paging systems (such as are installed in factories, clubs and parks), the radio tuner may be coupled to all types of portable amplifiers such as small truck amplifiers and record players.

The tuned r.f. circuit is well suited to recording applications because of its inherent low distortion. The latter is obtained at somewhat of a sacrifice of tuning—the tuning ordinarily tending to be broader than in a standard superheterodyne. However, the tuned r.f. section may be engineered to have good selectivity, as well as fidelity. Another outstanding advantage is the fact that the tuned r.f. "front end" picks up less noise interference than

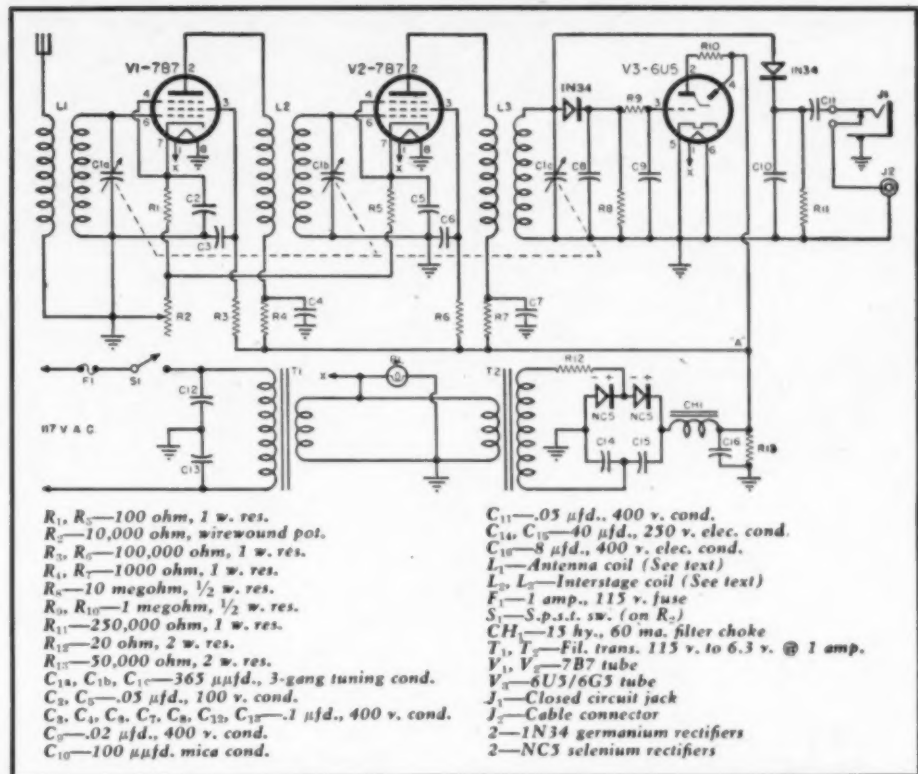


Fig. 2. Schematic diagram of a home-built, three-tube, t.r.f. tuner. The unit covers the AM broadcast band and is suitable for recording purposes.

many of the low-priced sharper tuning superhets.

This tuner has been designed for maximum selectivity rather than maximum amplification, and consists of two transformer-coupled pentode tubes, feeding into a germanium diode rectifier acting as the detector.

It is often of great importance that an r.f. tuner introduce as few additional tubes as possible. Here, we have handled this situation by employing a germanium crystal diode as the detector, and a selenium unit as the separate power supply rectifier. The rectified audio signal is delivered to an output jack located on the rear of the chassis, and to a headphone jack located on the front panel. This arrangement enables the operator to monitor the tuner ahead of the amplifier into which it feeds. This is a convenience, especially during tuning-in periods. The final radio frequency signal is also fed to another germanium

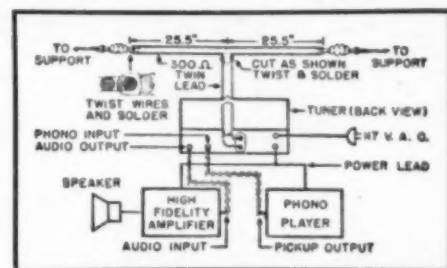



Fig. 3. Diagram shows installation wiring of an FM-AM tuner. Details for antenna construction are also given.

rectifier, the output of which is filtered and fed to the grid of an electron ray indicator tube.

This second crystal unit serves to clear up the eye image, giving a sharper pattern than ordinarily would be obtained.

The power supply operates from a 115 volt, 60 cycle source and consists of two 6.3 volt, 1 ampere filament

Fig. 4. Rear view of t.r.f. tuner. Location of parts should be followed closely.

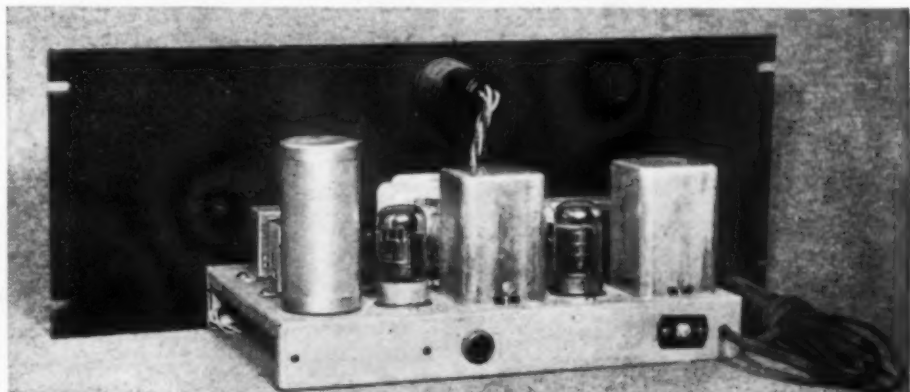

transformers with their secondaries connected together. The junction of the two secondaries is used to supply the filaments of the amplifiers, while the output of the combination, approximately equal to the line voltage, is fed to two selenium rectifiers connected as a voltage doubler. This back-to-back transformer arrangement per-

mits use of the line voltage without the dangerous ground-return common to a.c.-d.c. line power supplies. At the same time, tube heater voltage is supplied without having to incorporate line-cord resistors.

The additional plate voltage supplied by the voltage doubler results in higher output and greater sensitivity

than would be obtained with only 115 volts on the plates of the tubes.

The output ripple of the voltage doubler combination is reduced to a minimum by the addition of a 15 henry filter choke and an 8 μ fd. condenser. The 50,000-ohm bleeder resistor completes the power supply which will be more hum-free than either a series-filament arrangement or an a.c.-d.c. transformerless supply.

Layout is an extremely important factor. The first decision that must be reached in constructing electronic equipment is that of proper location of parts, and selection of a suitable chassis. This, at first sight, might appear to be wasted effort, but after rebuilding a unit several times, one then fully realizes the importance of proper parts location.

The amplifier employs a 7"x11"x1½" chassis and a standard 7"x19" panel. Above the chassis (Fig. 4) are located the tuning condenser, the two filament transformers, the three shielded r.f. transformers, the two tubes, the filter choke, and the magic eye.

The transformers and choke are mounted together and in such a way that their fields do not interfere with the tuning condenser (C_1). The tubes and coils are arranged across the rear of the chassis, with the antenna coil at the extreme left hand corner, followed by the first r.f. amplifier, the first r.f. coil, the second r.f. amplifier and the second r.f. coil. Locate the magic eye on the front panel directly over the dial.

In mounting the tube sockets (Fig. 6), arrange each one so that its grid contact is nearest to the coil connecting to the preceding stage. The plate contact then automatically will be opposite the coil of the following stage. The antenna and ground binding posts should be located at the rear of the chassis, just under the antenna coil.

Locate the two selenium rectifiers on the front of the chassis by means of two machine screws inserted through the mounting eyelets which are insulated from the discs. Caution should be exercised to avoid grounding the discs of the rectifier. These discs carry the a.c. potential, and a short circuit at this point might damage the filter condensers, the rectifiers, or the transformers. The chassis position of these rectifiers should always be such that they are not mounted adjacent to any heat-dissipating components, such as power tubes, high-wattage resistors, etc.

The two germanium crystals are mounted on a terminal strip which is placed along the left hand edge of the chassis. All grid and plate leads should be as short and direct as possible, and the plate leads kept close to the chassis.

(Continued on page 106)

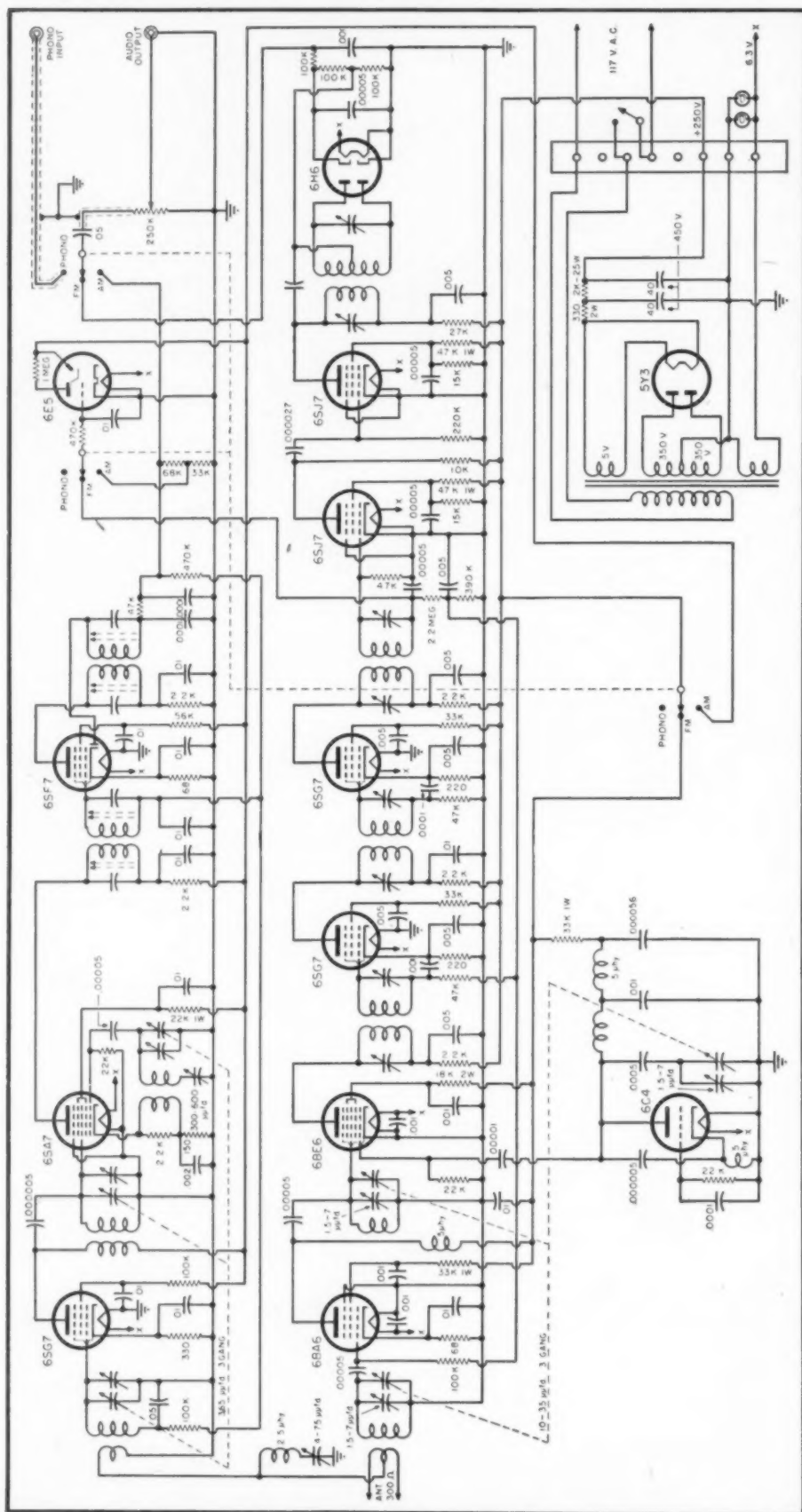


Fig. 5. Complete schematic diagram of Brownie Models RJ-12 and RJ-14 FM-AM tuners. The power supply which is incorporated in this schematic diagram is actually built as a separate unit and connected via cables.

Build Your Own AUTOMATIC KEY

Two views of the completed, home built automatic key. Over-all size is 3"x4"x5". No external power supply is required. Knob on side of case is speed control, R_1 . Note position of the micro-switch.

By
G. W. GUNKEL, W6NMS

Code key that provides automatic dots and dashes is low in cost and extremely simple to construct.

A NUMBER of articles have been published in recent years on the subject of automatic keys. Such a key should meet the following specifications: It should make perfect dots, dashes and spaces; be a single unit of the same size or smaller than a standard mechanical key; it should not be necessary to resort to purchasing a standard key in order to adapt it to an electronic key; the power supply should be included in the unit; it should be ready for instant operation without tube heater lag or consuming power in the standby period; be low cost. The key herein described is the only one, to the author's knowledge, that meets all of the above specifications.

The theory of operation is extremely simple and can best be compared with that of an ordinary buzzer or doorbell. The make and break system is the same; however, a sensitive relay connected as a buzzer is used and condensers switched across it. The time necessary for the condensers to discharge into the relay provides the necessary time lag.

Fig. 1 shows the circuit diagram for automatic dots and manual dashes. Switch X consists of a spring keying arm (a piece of hacksaw blade works well) that pivots between contacts A and B . When the keying arm is in the dot position, touching contact A , the alternating current flows through the selenium cell rectifier (a Federal 100

ma. type) where it emerges as direct current; it then flows from the keying arm X to the top contact of one side of the double-pole, double-throw relay; thence, across the contacts to the relay coil and condenser C_1 . The relay closes, opening the top contacts and the condenser C_1 starts to discharge. The relay stays closed until C_1 is completely discharged, at which time, the relay arm springs back and again makes connection with the top contact. This process repeats itself as long as the keying arm is held in the dot position. The time necessary to discharge C_1 and hence the speed of the dots is regulated by R_1 , the 10,000 ohm linear taper potentiometer connected across the relay. The spacing between dots can be adequately adjusted by varying the spring tension on the relay armature and the spacing between the relay contacts. These relay adjustments are the same for all speeds and need be

made only once. The two lower contacts on the other pole of the relay are connected to the circuit to be keyed. These contacts are connected when the relay is in the down position.

Manual dashes are made by moving the keying arm against contact B . This throws the direct current directly across the relay. The relay will open and close in conjunction with the movement of the keying arm from neutral position to contact B and return.

Fig. 2 shows the schematic for automatic dots and manual dashes.


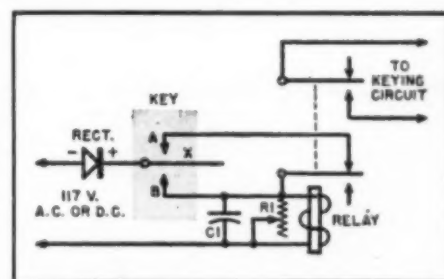


Fig. 1. Circuit that may be used to obtain automatic dots and manual dashes.

Fig. 2. Circuit diagram used by the author to obtain automatic dots and dashes.


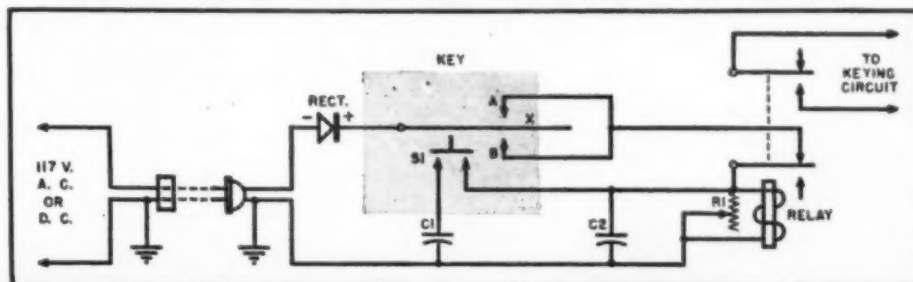


TELEVISION INSTALLATION

By W. W. WAYE

Part 4. City and urban locations usually require specialized techniques and highly directional antennas for ghost-free reception.

Fig. 1. The conventional dipole-and-director antenna is adequate for most installations, but a more highly directional antenna may be required in city or urban locations to overcome ghosts.

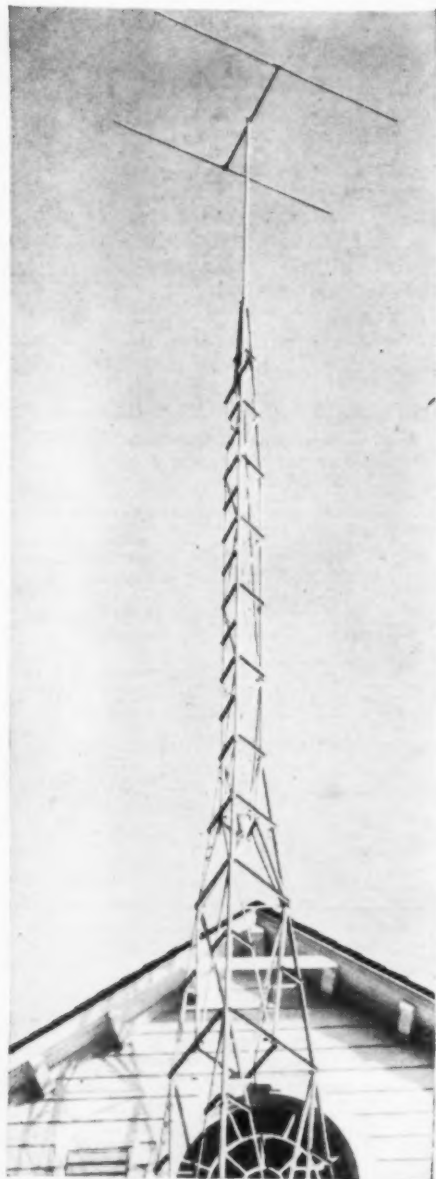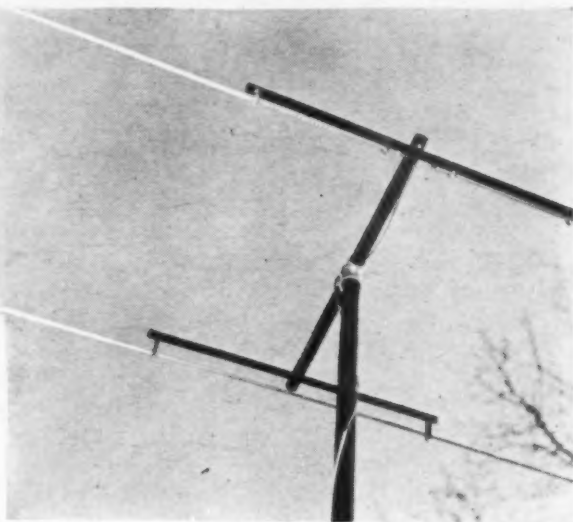

A CRITICAL requirement of every modern television set is an efficient installation capable of providing adequate reception—free from ghosts and other interference—on the TV channels desired by the customer. Properly installing a television antenna and lead-in system is no simple matter, however, because every installation is different.

The work is influenced by the type and size of the customer's house or dwelling or business establishment, and by its location with respect to local television transmitters as well as any nearby, large buildings. The work is complicated by any of several installation problems, which invariably are of more serious nature when the location is in the vicinity of urban, industrial, or commercial districts.

For a few urban locations, a single dipole may sometimes provide satisfactory reception. Usually, however, either a director or reflector is used with the dipole for greater directivity. With such a two-element arrangement (Fig. 1), there is very little pickup from the rear, and much sharper directivity with an increase in "gain" or signal strength in the forward direction. These basic antennas, previously discussed, prove entirely adequate for most suburban installations and for many urban installations.

However, in many city or metropolitan locations, it may be difficult—sometimes impossible—to site and orient such antennas for adequate, ghost-free reception, following the *Basic Procedure of Installation* (Table 1). The resulting poor reception, obtained at such locations with the set operating normally, is visible directly

Fig. 2. An increase in height of the directional antenna provides better signal reception with less electrical interference.

on the receiver picture tube, and may be analyzed in terms of these symptoms:

1. *Weak pictures* on one or the other, or both, of the *Primary* and *Secondary Channels* preferred by the customer. These pictures are often speckled with a "snowy" effect, and the image may not hold steady on the screen.

2. *Ghost images* of the direct picture signal, or, blurry or diffused reception which does not move or change. The effect is always characteristic of only one channel; it is decidedly different or even non-existent when other channels are received.

These are two common symptoms of a poor antenna installation. They are regularly encountered in urban locations, and are important indications of "what to do next."

In some cases, only a further adjustment or better siting of the existing antenna is required. In many cases, however, a more highly directional antenna is necessary for good reception, according to the degree and nature of the symptom of poor reception.

Importance of Height

With the set using a directional antenna (a dipole-and-director) and operating normally, reception of weak or "snowy" pictures on one or more television channels (Symptom 1) indicates that insufficient signal power is being received by the existing antenna. A building or other large obstruction may be blocking the direct or line-of-sight path between the receiving antenna and the transmitter, or the receiving site may be located a considerable distance from the transmitter. In either case, the best solution to this problem is to increase the height of the receiving antenna.

If a higher location is available, the



Fig. 3. Normal picture signal of test pattern as received on primary television channel.

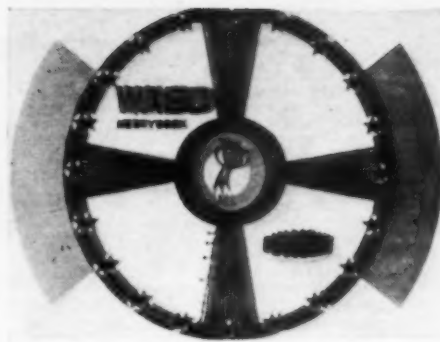


Fig. 4. Hazy effect caused by a ghost image, slightly displaced from the direct image.

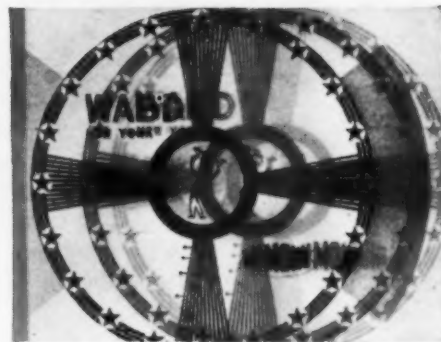


Fig. 5. Multi-image reception caused by several reflected signals appearing at antenna.

antenna should be resited. Even an elevation increase of a few feet may be sufficient for greatly improved signal reception.

However, when it is physically impossible or impractical to find a fixed location of sufficient height, the antenna should be mounted on a suitable mast above the house or building (Fig. 2). Despite the resulting increase in the cost of installation, the customer will usually approve such construction when the reception problem is properly explained.

Suitable towers can be obtained from manufacturers or structural steel companies. Proper guying and other mechanical factors of safety and sturdiness must be considered in erecting such a tower.

Siting and orienting of the antenna at high elevations follow the usual procedures (Table 1). Since long transmission lines are required for such installations, impedance matching between receiver and lead-in and between lead-in and antenna is of extreme importance.

Fig. 6. Photograph shows a typical urban installation where a conventional dipole and reflector antenna is used to provide adequate reception on the two preferred TV channels as selected by the customer.



December, 1947

A good general rule for all television installations is to erect the antenna in the clear and as high as possible.

Increased height is of particular importance when the receiving site is more than 30 miles from a television transmitter, and often may provide adequate reception of signals at particularly remote receiving locations which would not otherwise be possible.

Additional height also provides greater security from ignition and motor "noise" and other types of electrical interference.

Reception of Ghosts

The appearance of multiple images or ghosts (Symptom 2) is an indication of the reception of more than one signal from the same transmitter. Ghost images are caused by reflected signals arriving from various directions different from the direct or line-of-sight path, and their appearance on the television screen is due to the insufficient directivity of the receiving antenna.


This is one of the most important

problems of television installation. It is a common source of poor reception, encountered in all urban installations, and is a perpetual challenge to the ingenuity and ability of the technician or serviceman.

Picture signals radiated by a transmitter travel outward (in straight lines) in all directions, until the waves reach a resonant antenna, or until they strike a surface or large object and are reflected in various new directions. Since a receiving antenna is usually located as high as possible, within so-called "optical sight" of a transmitter, a direct wave (following a line-of-sight path) is the first signal to reach a receiver tuned to that channel, and this appears on the picture screen as a direct image (Fig. 3). Other radiated picture signals are reflected by various surfaces in such a way that some of these waves also arrive at the receiving antenna—but a few microseconds later than the direct wave.

When a receiving antenna is not properly sited and oriented, or is not

Fig. 7. An urban installation providing reception of three images from single station, with reflected "ghost" via path "A" stronger than direct image or ghost via path "B" (see inset). The dipole is directed toward source of reflected "A" signals for best reception, and addition of director (or reflector) removes two unwanted images from picture screen. Pattern "C" (inset) is obtained from "direct path" signal.

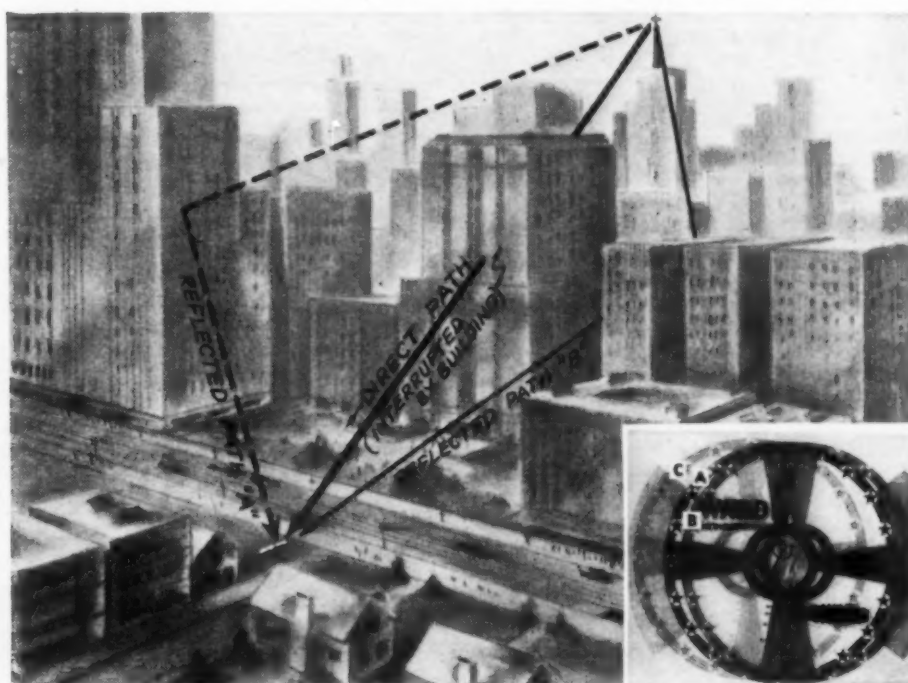

LOCATING THE RECEIVER

Best position must be satisfactory to customer, free from sunlight and electrical interference; with adequate space for viewing screen.

1. Install receiver carefully.
2. Check operation with makeshift dipole.
3. Determine customer's choice of 2 stations, for Primary Channel and Secondary Channel.

PREPARING THE LEAD-IN

Best lead-in for "probing" is "twin-lead ribbon." Match impedances. If set input is marked 300, use lead-in with 300-ohm rating. For 75-ohm input, use 75-ohm lead-in.

1. Cut extra-sufficient length of lead-in to reach from set to any point on roof.
2. If 300-ohm lead-in is used, connect short Matching Section (a 36-inch piece of 150-ohm "twin-lead ribbon") to end of lead-in on roof.

PREPARING THE "PROBE"

Installation "probe" consists of typical commercial dipole, mounted on pole, and connected to set by lead-in. Dipole is portable.

1. Assemble dipole of 2 metal rods. Use over-all dipole length of 78 inches to receive ALL channels. To favor certain channels.

Channel	Over-all Dipole Length
1	108 in.
2	90 in.
3	81 in.
4	73 in.
5	64 in.
6	60 in.

2. Connect lead-in (and Matching Section) to dipole.

3. Run wires and install simple two-way telephone or intercom between roof and set.

SITING THE ANTENNA

Best site is determined experimentally, using two-man coordination system. While man on roof uses "probing" dipole to test various locations, man at set observes merit of locations in terms of signal strength and picture quality, and absence of ghosts and noise interference.

1. Site is selected for best reception of Primary and Secondary Channels, with least effect of ghost images.
2. Attach metal mounting bracket to roof.
3. If ghost interference is not too serious and picture signals are strong, assemble a directional antenna—either a dipole-director or a dipole-reflector antenna with a mounting pole of suitable height—and erect antenna in roof mounting bracket, leaving it free to rotate.
4. If ghost images predominate and/or if desired signals are weak, first "probe" for new site, then attempt much greater height. Assemble any type of highly directive commercial antenna and erect at best site, leaving it free to rotate in roof bracket.

ORIENTING THE ANTENNA

Previous two-man coordination system is used. Antenna is oriented and tuned, based on best results observed by man at receiver.

1. Rotate antenna to best position for ghost-free reception of Primary and Secondary Channels.

2. Tune antenna by adjusting all tunable factors for best signal strength and picture quality WITHOUT ghost reflections. Install in fixed position.

3. If noise interference persists throughout siting and orienting, substitute (properly matched) coaxial cable for lead-in between antenna and set.

4. Install lead-in permanently, without slack. Recheck operation of set.

Table 1. Basic procedure for all television antenna installations.

sufficiently directional, it accepts these reflected signals and they appear on the television screen as fixed (but usually weak) images, which are identical to the direct image but are displaced horizontally and to the right of the direct image.

The amount of displacement is really an indication of the additional distance the ghost signals traveled to reach the receiving antenna. When this additional distance is short, the displacement on the screen may be so small that the result is a blurry or indistinct merger with the direct signal (Fig. 4). Greater displacements on the screen, however, produce more distinct multiple images (Fig. 5).

In all instances of ghost reception, the first image (to the left on the television screen) is the direct image. It is usually brighter than the "ghost" images, because the reflected signals lose part of their energy (or intensity) during reflection.

These unwanted signals are reflected by large buildings, apartment houses, skyscrapers, factory buildings, steel storage tanks, and other large objects or surfaces, which may be located at any distance and in any direction from either the transmitter or the receiving site. For this reason, ghost interference is particularly troublesome in metropolitan or city locations, where there are many large buildings acting as almost-perfect mirrors of television signals.

However, the procedure of eliminating ghosts is the same for either urban or suburban installations, because the key to the problem lies in the directional characteristics of these reflected signals. Ghost images arrive at the receiving site at different

angles with respect to the direct wave. For this reason, the receiving antenna must be sufficiently directional so that it accepts only the strongest signal from the transmitter—usually, but not always, the direct signal. This requires the introduction of some new techniques, within the scope of the Basic Procedure of Installation.

Ghost Elimination

After initial "probing" operations with a single dipole (Table 1) and temporary installation of a directional antenna—either a dipole-and-director or a dipole-and-reflector—it will be found, in most city or urban locations, that some degree of ghost reception is present regardless of the orientation of the directional antenna. This condition is very typical, and indicates that the directional antenna is inadequate in its particular location. A new site must be found, and the purpose of further roof activities is the reception of ghost-free signals.

Although a general procedure can be followed, each installation must be treated individually because of the specific problems posed by each location. Many hours, perhaps a day or two, may sometimes be necessary to find a ghost-free site in crowded metropolitan or industrial districts. For the two-man installation team, patience is an absolute requirement!

The importance of antenna height should first be considered as probably the simplest means of eliminating some ghosts. The usual 4- or 5-foot mast of the directional antenna can be replaced with a mast of much greater height. Or, the higher elevation of an adjacent building may be considered a better site.

Frequently, however, ghost-free reception with a conventional dipole-and-reflector antenna requires a thorough exploration of every conceivable site in the vicinity of the location most desired. This requires further, careful, patient "probing" over extended roof areas, and may even include amateur rigging and steeple-jack work atop some types of large buildings. In many instances a satisfactory site can be located, however, and then the antenna must again be oriented for reception of both Primary and Secondary Channels—and without ghost effects!

In one typical, metropolitan area, long and patient exploration revealed only one roof location that was free of ghosts (Fig. 6), where a conventional director-and-reflector Philco antenna could be used, without the additional expense of erecting a mast and without recourse to a more complicated, highly directional antenna.

Since the displacement of a ghost image (on the television screen) is a ratio measure of the additional distance required for the ghost signal to travel, it is sometimes possible to estimate distances to actual reflecting objects or surfaces by such displacement on the television screen. In this way, certain large buildings, water tanks, or other exposed objects can be identified optically. Knowledge of the location of such objects or surfaces can be used to good advantage in improving an existing antenna so that it is capable of rejecting signals arriving from the direction of such known reflecting surfaces.

As one example, a large, reinforced section of sheet metal or screening can be erected upright near the antenna, on a line with the distant source of reflected signals, so that the antenna is effectively shielded in that direction. The screen must be rigid with low wind resistance, and must be erected no closer than 8 feet from the antenna.

Ghost Utilization

In rare instances, a reflected signal may be desired in preference to the direct signal.

A condition is sometimes encountered in urban locations, where a reflected or ghost image may prove brighter and stronger than the direct signal, and the television antenna is oriented with respect to the source of signal reflections instead of to the transmitter.

In a typical case (Fig. 7), the path of the direct wave is almost entirely blocked by a tall building between the transmitter and receiving antenna. However, two reflected paths "A" and "B" are of significance. The latter wave is reflected by a small building. Wave "A" is reflected by a large, steel-and-concrete building, however, resulting in a reflected signal of considerable power reaching the antenna site. For this reason, the single dipole is turned broadside to the large building, the "source" of the strongest sig-

(Continued on page 124)

10.7 mc. I.F. TRANSFORMERS

By
J. C. MICHALOWICZ

Dept. of Elec. Eng.
Catholic Univ. of America

**Build your own i.f. transformers.
10.7 mc. is now standard for a
new band FM home receiver.**

THE re-allocation of the frequency-modulation broadcasting designation to the 88-108 megacycle band has necessitated the reconstruction of 42-50 megacycle receivers to intercept this new frequency. The most important changeover required is, of course, that of the high-frequency or input section of the receiver, but probably of equal importance, is the renovation of the intermediate frequency amplifier system, in particular, the i.f. transformers.

In choosing a proper intermediate frequency, it must be borne in mind that the image frequency must necessarily fall outside of the high-frequency band. With the old allocation of 42-50 megacycles, a 4.3 megacycle i.f. frequency was employed, its image being produced at 8.6 megacycles, which is well outside of the 8 megacycle band. So also with the new allocation of a 20 megacycle bandwidth (88 to 108 megacycles), an i.f. frequency must be used whose image falls outside of the FM band. Consequently, a frequency of 10.7 megacycles for intermediate frequency amplification has been adopted.

Although commercially-built 10.7 megacycle i.f. transformers of good bandwidth are available, they are fairly expensive. However, with the increasing availability of coil-forms and shield cans, one can construct his

own with satisfactory results. The materials used by the author are shown in Fig. 1. This type (an RCA product) is not absolutely essential; any adaptation of discarded i.f. transformer forms may be employed as long as the coil diameter and spacings as shown in Fig. 3 are followed closely. Also, the metallic shield should be of such a size as to permit at least the width of one coil diameter between the windings and the shield, both at the sides and at the ends of the coils. Inductively-tuned transformers are chosen in preference to capacitively-tuned ones, since they are more stable

and present a more compact finished product.

The winding data is shown in Fig. 3. Both secondary and primary windings consist of 17 turns of No. 28 plain en-

(Continued on page 140)


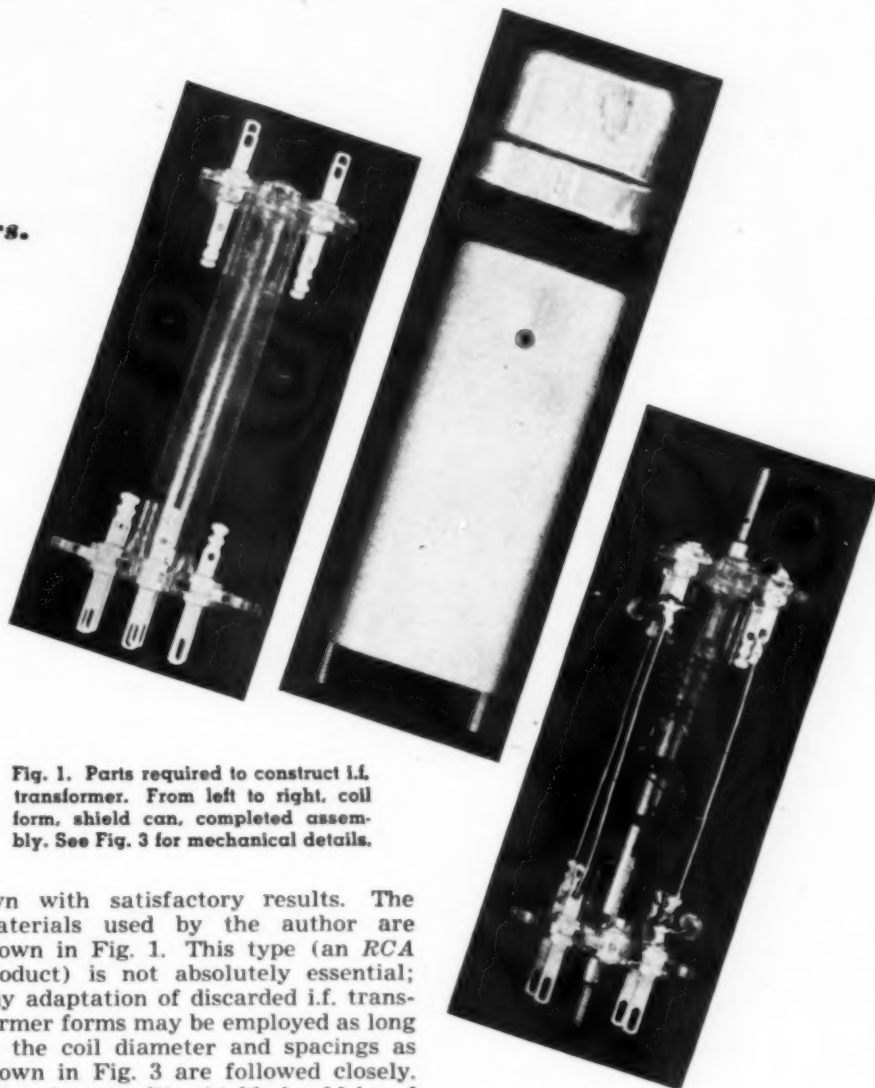


Fig. 1. Parts required to construct i.f. transformer. From left to right, coil form, shield can, completed assembly. See Fig. 3 for mechanical details.

Fig. 2. Schematic diagram of two-stage i.f. amplifier. All transformers are identical in design and construction.

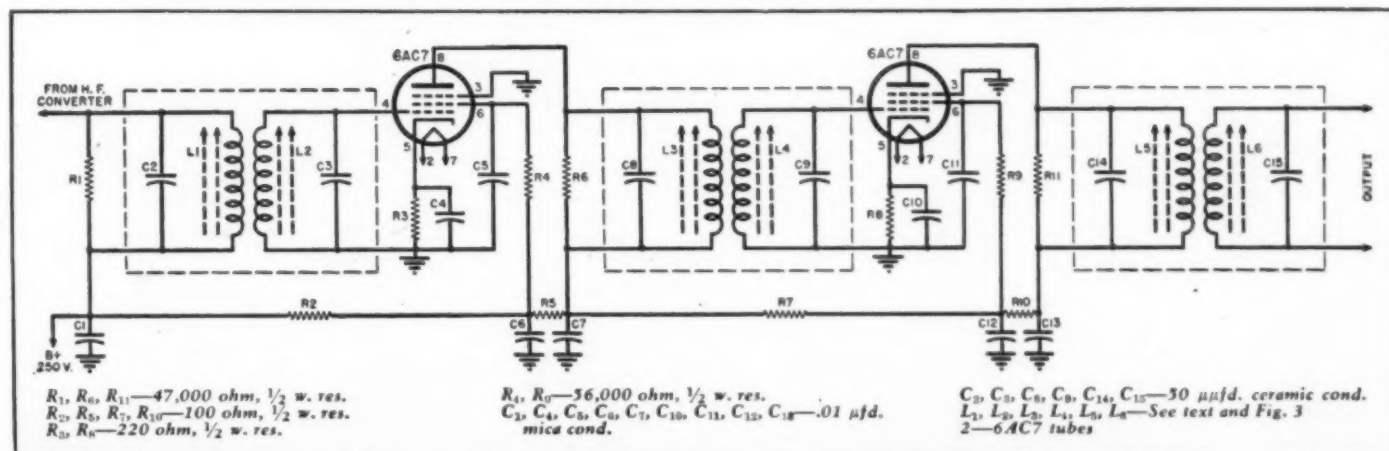

An Experiment in Voice Controlled Relays



Unit designed and built by the author. It is being used to control the operation of a paging system.

By **LEON A. WORTMAN**
Radio Station WSYR

Just "say the word" and this electronic device will control the "on-off" operation of other equipment.

THERE are countless devices that are used to carry voice frequency modulations. Most of these devices, be they intercoms, public address systems, paging systems, radio-telephone transmitters, dictating machines or recording devices, must be operated manually before they will function. If the device can be operated automatically as soon as the voice or other modulating signal is


impressed on its input, and if the device can maintain operation during the period of desired modulation, and if the device can automatically stop itself at a predetermined time after the signal has ceased, such a device speaks for itself and no pun is intended. The idea was suggested by a friend who operates a large laboratory. There is a paging system throughout the lab and its associated offices

with the microphone placed at the switchboard for the telephone operator. This was designed to save that poor overworked switchboard operator all the abuse that is heaped on her head for having forgotten to switch the microphone on when she paged "Mister Smith on two three wun!" Or she would forget to turn the microphone off after use and the whole plant became an audience for her personal conversations. The unit to be described, when added to the existing paging amplifier, eliminated the "switch throwing" operation entirely. The amplifier began feeding immediately as she started talking into the microphone and the amplifier stopped when the talk stopped.

Fig. 1 diagrams the basic circuit for the unit that was installed to perform these functions. A signal voltage impressed on the input terminals of the unit is amplified by V_1 and V_2 . C_B , acting as a blocking condenser for the d.c. plate potential of V_2 , permits the amplified signal voltages to be impressed on the anode of V_3 , which is connected as a diode rectifier. V_3 rectifying the signal voltage causes a positive potential to appear across its load, which is R_o in parallel with the grid and cathode of V_4 . The triode, V_4 , is biased almost to cut-off by the voltage drop across R_o as a result of the cathode current flow. As the signal voltage increases from zero, the voltage developed across R_o increases, making the grid less negative with respect to the cathode. As a result, the plate current flow increases instantaneously. It can then be seen that by placing a sensitive type relay in series with R_{c_k} in effect making the relay an integral part of the biasing circuit, and adjusting the bias of V_4 to the point where the relay is in normal position, an audio voltage impressed upon the input terminals of V_1 , will, in a fraction of a second, actuate the relay.

However, the relay will alternately "release and hold" as the voice or other modulation is impressed. It will "chatter" and try to follow every word. Therefore some time delay must be introduced to maintain the relay in a "hold" condition. If a condenser, C_T , is placed across R_o , in Fig. 1, a time delay to the release operation is introduced. C_T is charged instantaneously by the peak rectified voltage output of diode V_3 , and it will maintain a sufficiently high potential on the grid of V_4 to keep the relay locked in a

Fig. 1. Simplified diagram of relay unit. Complete schematic is shown in Fig. 2.

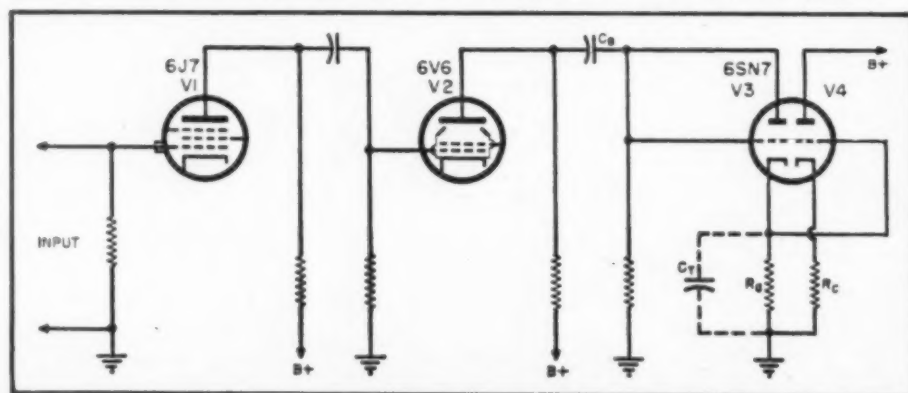

"hold" position until the charge leaks off through R_0 . The "leakage" time can be predetermined.

The combination of R_0 and C_T in parallel will preset the "release" time delay of the sensitive relay. Varying either the value of C_T or of R_0 will permit a wide variation in time. The time can be made to vary from the inherent mechanical lag of the relay armature up to several seconds or even minutes. Larger time delays are possible but the constants then become quite large electrically and physically, and the charging potentials may become inordinately high. A series of practical experiments showed that a time delay of up to four seconds from start was sufficient for most purposes. Of course it is far more practical to make R_0 the variable element while C_T remains at a fixed value. An ordinary potentiometer with smooth action as in the ordinary, well-built gain control (carbon type), connected as R_0 with the potentiometer arm going to one end of C_T and the other terminal of C_T going to the grid of V_1 , will serve ideally as the fully variable time delay control.

R_0 , in practice is a 20,000 ohm wirewound rheostat or potentiometer. Both the controls R_0 and R_1 are mounted on the back of the chassis, as seen in the photograph. A screwdriver slot adjustment is cut into the shortened shafts. These two controls, once set, seldom need be readjusted unless the type of service changes or possible bias adjustment of R_0 may be necessary when V_1 is aging or is replaced.

Fig. 2 diagrams the practical and completed circuit of a typical voice control relay unit. It is the unit shown in the photographs. This unit was used to drive the paging system. The output line is placed in series with the voice controlled relay so that talking closes the audio output line, and when the relay "releases" the audio output line is opened or broken. The output line was connected to the input terminals of a standard public address system which was used for paging. No changes or alterations of any kind are required in the paging unit. The gain controls are adjusted so that close talking is required to operate the relay unit. This is necessary so that extraneous office noises and conversations will not actuate the relay. In order that the operator can be certain she has operated the relay and that she is being heard, a small pilot light is placed within easy view to indicate that the unit is functioning. In order to utilize the set of s.p.d.t. contacts of the standard model sensitive relay, the pilot light going off rather than on indicates "in operation." The switchboard operator did not find it at all confusing. And as she said, "Just as long as something changes when I start talking."

Fig. 3 shows a model that can be used to operate a radio-telephone transmitter, act as a microphone pre-amplifier, be used to key a transmitter carrier, and generally be operated as

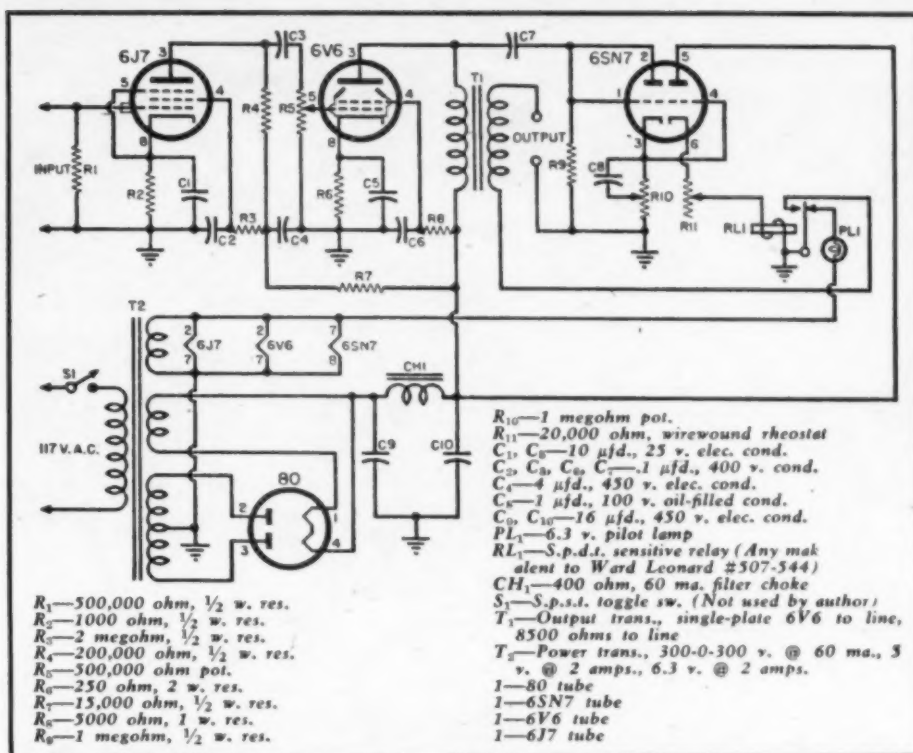



Fig. 2. Schematic diagram of a voice controlled relay unit designed to operate a paging system. Potentiometer R_{10} is time delay adjustment.

a "master control" unit for the transmitter. V_1 is a 6J7, V_2 is a 6V6, V_3 is one section of a 6SN7 connected as a diode with the grid and plate tied together, and V_4 is the second section of

the 6SN7 operated as a triode with the plate going directly to the high voltage "B" supply. With R_{10} set to approximately one second delay time, rapid

(Continued on page 161)

Fig. 3. Suggested circuit diagram of a unit that may be used as a "master control" for operating a conventional radio-telephone transmitter.

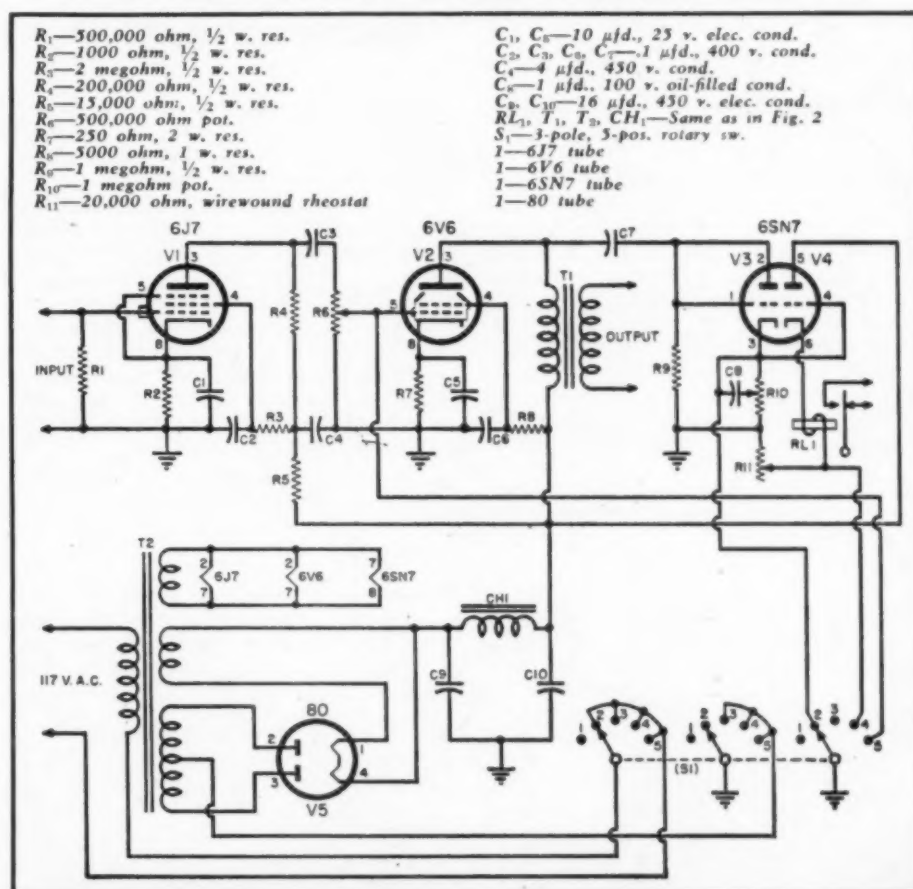

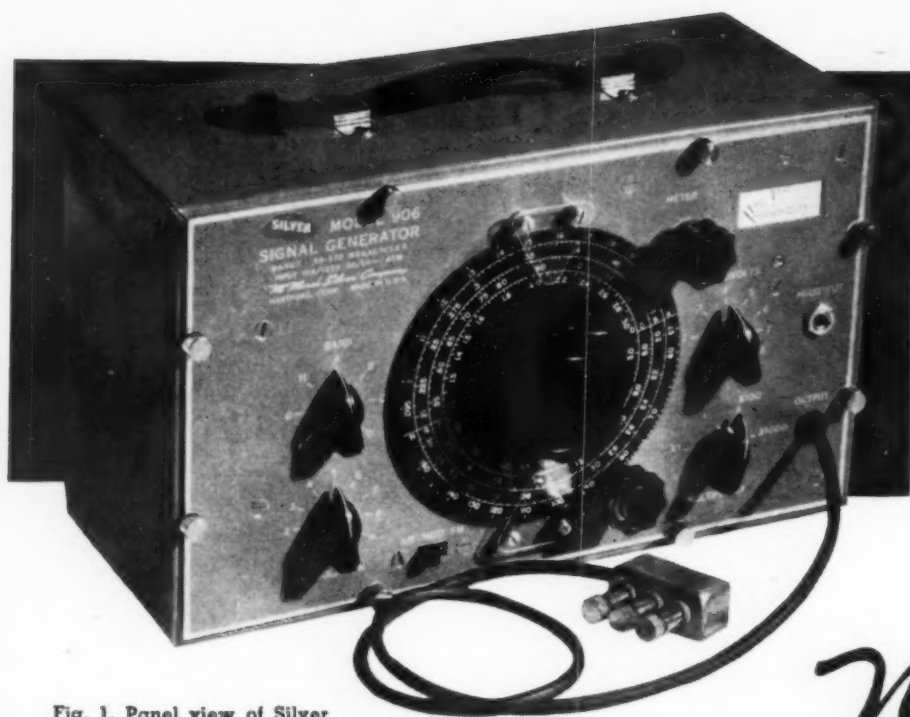


Fig. 1. Panel view of Silver Model 906 signal generator.

By
GUY DEXTER

A relatively low-priced test instrument covering 90 kc. to 210 mc. Features AM, FM, and 400 cycle audio.

New Compact **Signal GENERATOR Has Laboratory Features**

NO LONGER is a good signal generator a luxury instrument. The increasing complexity of modern radio receivers, together with the need for precise measurements and adjustments, now makes this instrument *essential* in the radio shop, as well as in the technical laboratory. The day of haphazard measurements with leaky test oscillators is past.

A signal generator is a distinct instrument having many imitations but no real counterpart. It is more than just a tunable r.f. signal source. Not every test oscillator can qualify as a signal generator. In addition to delivering accurate radio frequencies, selectable over a wide range, the modern signal generator has the following features: (1) Its output attenuator permits smooth adjustment of the signal strength to levels which may be duplicated. (2) At zero setting of the attenuator, no signal is delivered by the instrument except at very high frequencies where *total* reduction of signal strength to zero is impossible in the present state of the art. But even in the latter case, the transmitted signal is of known, negligible value. (3) The actual signal level is accurately indicated in microvolts by means of the attenuator and a self-contained output v.t. voltmeter. (4) In addition to standard 400-cycle modulation with continuously variable modulation percentage, continuously variable-width frequency modulation is also provided, in order that the signal generator may be employed in FM and television receiver measurements and in visual (oscilloscopic) adjustment of AM receivers. (5) Signal leakage (that is, the radiation of r.f. energy over any path except through the controlling attenuator) is zero,

except at very high frequencies where stray coupling reactances are very small and shielding less efficient. Even this leakage, however, is small in the laboratory-caliber signal generator.

These important features formerly were obtainable only in laboratory type signal generators costing many hundreds to even thousands of dollars. The high cost of such instruments precluded their wide use in service shops and in small laboratories. The costliness of such instruments can be attributed, at least in part, to the special manufacturing procedures, almost amounting to custom building, which have been required in the past. Using war-learned techniques, one electronic instrument manufacturer has solved the problem of building an efficient signal generator in volume production, thereby reducing the cost of this instrument to a figure within the budgets of service shops and small laboratories.

Features of the Instrument

Frequency Range. The Model 906 Signal Generator is single-dial tuned from 90 kc. to 170 mc. (amplitude modulated) and from 90 kc. to 210 mc. (frequency modulated). Calibration accuracy is ± 1 per-cent. The eight frequency bands are selected by means

of a single control knob. Band changing is accomplished efficiently by means of a coil-changing turret.

In the first seven frequency bands, fundamental frequencies are generated, and these are read directly on the main dial of the instrument. In the eighth band, the r.f. oscillator operates at frequencies equal to one-half the dial values, output being on the second harmonics of the actual oscillator frequencies. This type of operation is desirable in the 57 to 170 mc. range, since the stability of the oscillator is greater when operating between 28.5 and 85 mc. The second harmonic amplitude is substantially equal to that of the fundamental frequency because of the short excitation cycle of the oscillator.

R. F. Oscillators. Two radio-frequency oscillators are employed in the Model 906 Signal Generator. One of these is a variable-frequency unit, expressly for unmodulated and AM output; the other is a fixed frequency oscillator, used in conjunction with the v.f. oscillator for FM output.

The variable-frequency r.f. oscillator is designed around a type 6C4 miniature button-base tube, V_1 . The first models of the signal generator employed one-half of a type 6J6 as the r.f. oscillator; the other half being

RADIO NEWS

used as the 400-cycle AM modulator. Later in-production tests, however, established the superiority of the 6C4 as regards better output, increased frequency stability, and longer life.

The variable-frequency oscillator circuit is seen in the upper left-hand corner of Fig. 2. Variable condenser C_2 is the main tuning unit. C_1 is an individual trimmer paralleling each of the eight turret-mounted coils, L_1 .

In the v.f. oscillator portion of the instrument circuit, RFC_2 is a heater-isolating r.f. choke. This component, together with plate r.f. choke RFC_1 , contributes to the stability and freedom from "strays" of the oscillator.

Each coil is individually air-trimmed by means of a concentric 3-30 μ fd. air condenser, C_1 , mounted directly on the coil to which it is connected. Each

coil, L_1 , is wound on a separate ceramic form. These forms are held between two disc-type aluminum heads which form the rotary turret. As the turret is rotated into position for each of the eight frequency bands, the 3-coil contact studs are brought into contact with low-inductance, flat bronze contact springs which lead directly to tuning condenser C_2 and to tube V_1 . This arrangement insures short, direct leads. The turret method gives the convenience of switching, while actually eliminating the selector switch and its attendant losses, and providing the efficiency of plug-in coils.

Each of the coil assemblies are aligned at four to seven points in each frequency range, against precision crystal standards. Both the capaci-


tance of the trimmer C_1 and the coil inductance are adjusted in this operation. A frequency accuracy of $\pm 1\%$ or better is maintained.

The fixed-frequency oscillator (for FM) operates at 40 megacycles and is designed around the 6C4 tube, V_2 . Operating into this oscillator is a reactance modulator, comprised of the 6AU6 tube, V_3 .

The fixed-frequency oscillator and reactance modulator are placed in operation by means of the "Modulation" switch, S_2 . When this ganged 3-section switch is thrown to its FM position, the 400-cycle AM modulator is silenced and the reactance modulator sweeps the 40 mc. fixed oscillator frequency over a continuously variable width of 0 to 500 kilocycles, depending

(Continued on page 115)

Fig. 2. Schematic diagram of signal generator. A turret-type bandswitching assembly permits 90 kc. to 210 mc. coverage in 8 bands.

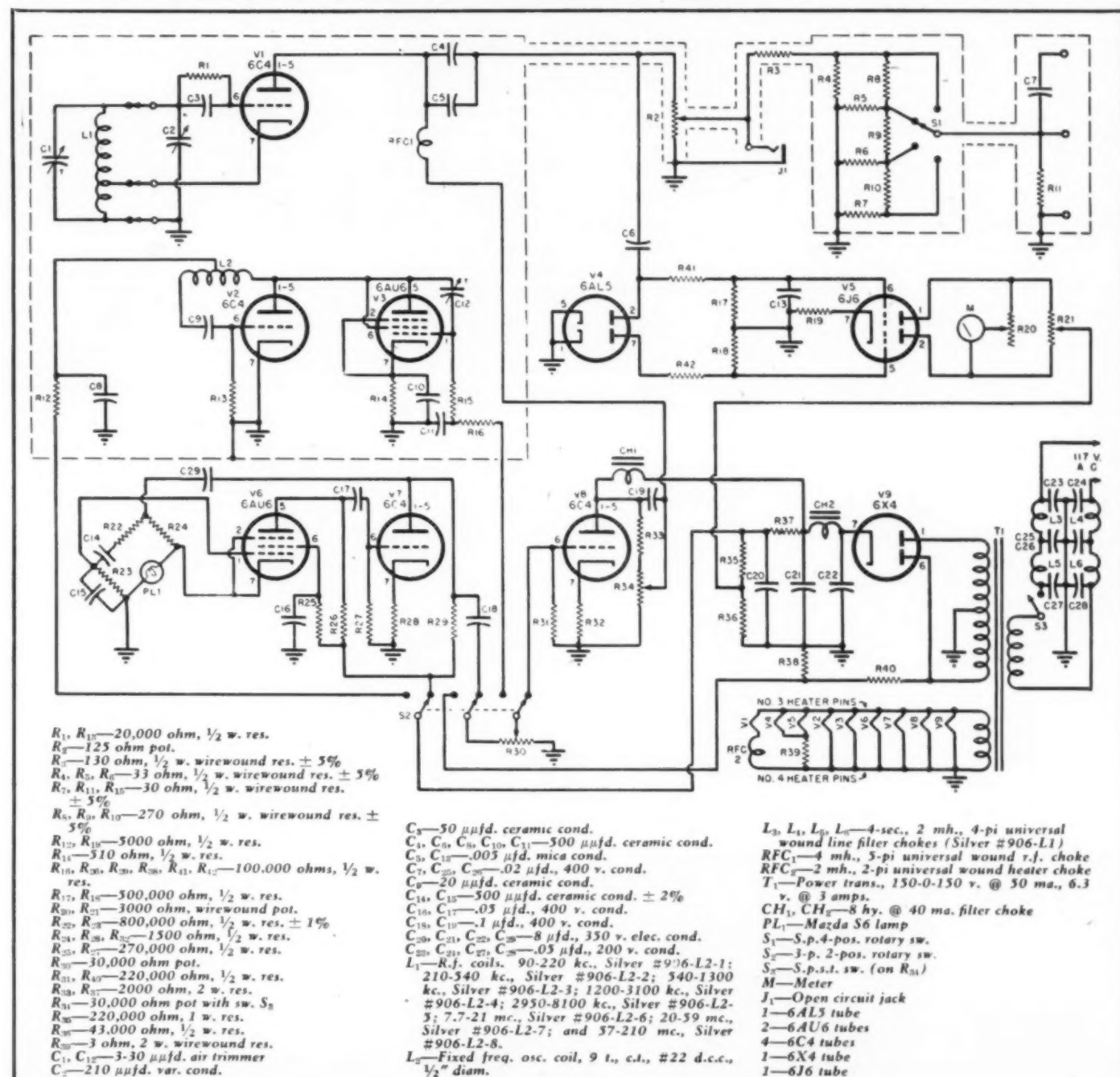

Miniature Ten Meter PHONE TRANSMITTER

By DONALD R. RHODES, W6UVY/8

Antenna Lab., Ohio State University

With only 2-watts input to final, this compact, home-built transmitter has worked out to 3000 miles with good results.

IT IS well-known to radio amateurs that the ten meter band has the unique characteristic of providing fairly consistent two-way communication over long distances with low power. It has also been observed that a low power station will often be heard as well as one using high power when conditions are right for communication with a certain part of the world, and when these conditions are not right even the high power station will not be heard. The transmitter described in this article is, to the author's knowledge, the smallest complete phone transmitter ever designed specifically for amateur operation. Very good readability and signal strength have been reported over distances of three thousand miles with an input power to the final amplifier of only two watts.

The entire transmitter, consisting of two stages of r.f. and three stages of a.f., is completely self-contained in a standard 3" x 4" x 5" metal box. This was made possible by the release of miniature type tubes on the surplus market at a price comparable to their standard metal equivalents. It was necessary to select the remaining component parts with great care due to the necessarily limited amount of space available in the box. All of the parts used were standard and are available at any amateur radio store.

A conventional circuit employing a


crystal oscillator, amplifier, and plate modulator, together with two audio stages for crystal microphone input is shown in Fig. 5. The crystal oscillator is the well-known tri-tet, used extensively among amateurs to obtain output on even harmonics of the crystal frequency. With a 40 meter crystal, sufficient output can be obtained on 10 meters (the fourth harmonic of the crystal) to drive the final amplifier. Capacity coupling between the oscillator and final amplifier is employed because of space limitations. The final amplifier is a plate-neutralized triode which is self-biased by means of a grid resistor; link coupling between the amplifier tank coil and the antenna provides a low impedance r.f. output. A 6AK6 pentode modulator operating "Class A," provides enough audio power to Heising modulate the final amplifier. This type of modulator does not require a modulation transformer, since the modulation voltage can be developed across a small a.c.-d.c. filter choke; good power regulation is also obtained since the plate current of a "Class A" amplifier remains constant at all times. For 100% modulation the peak audio voltage must equal the d.c. voltage on the final, which means that the final plate voltage must be less than the modulator plate voltage. It has been found however, that when the d.c. voltages are the same the carrier can be modu-

lated satisfactorily between 80 and 90 per-cent.

The crystal socket is mounted externally so that the transmitter frequency can be quickly changed by merely changing crystals; mounting the crystal in this position also tends to prevent the crystal frequency from changing due to crystal heating. Controls and connectors are shown in the photographs; the oscillator and final amplifier plate tank condensers, microphone jack, audio gain control, and antenna terminals are mounted on the front panel, with the meter switch and connector plugs for power, meter, and "on-off" switch mounted on the back. Screwdriver-adjustment tank condensers are used to prevent accidental change of capacity. Since the meter switch is used only during tuning of the transmitter, it also is screwdriver adjusted. The antenna terminals are National type TPB threaded polystyrene bushings with a center conductor which is molded in. Thus, by putting alligator clips on the transmitter end of the transmission line the antenna can be quickly attached or removed. Power for heaters and plates is supplied through a four-prong male Amphenol miniature connector, with a four-prong female miniature connector for meter and send-receive switch connections mounted next to it. These connectors mount in a plain round hole $\frac{5}{8}$ " in diameter and are held in place by a tempered steel retainer ring. A single-contact Amphenol coaxial plug-in connector is used for microphone input and must be thoroughly grounded to the chassis to prevent stray pickup. Also, the resistor from microphone to ground and the grid lead to the preamplifier audio stage should be as short and isolated as possible.

An old aluminum recording disc was obtained from a local broadcast station and after being cleaned up was cut, formed, and drilled as shown in Fig. 6 to provide a T-shaped skeleton chassis within the box. The chassis is mounted in the box with screws at

Fig. 1. Midget home-built transmitter—compare it for size with the Hallicrafters S-27.

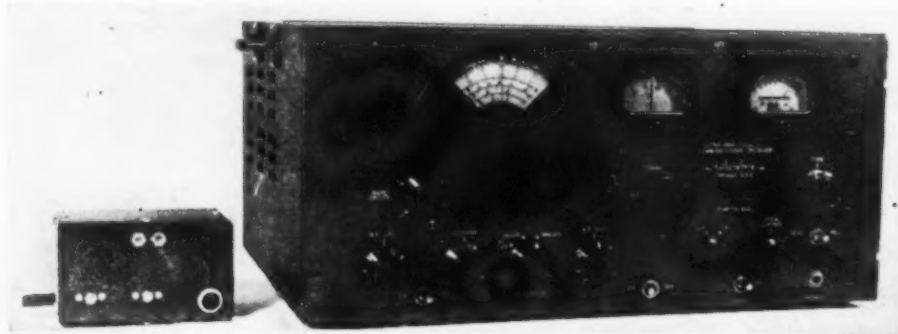

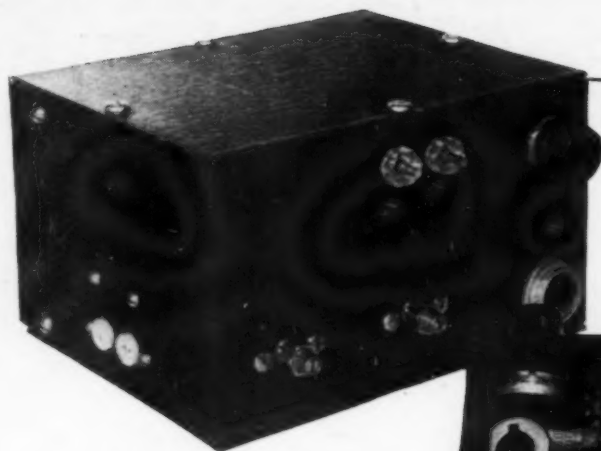


Fig. 2. Front panel view of home-built transmitter. Over-all size is 3"x4"x5".

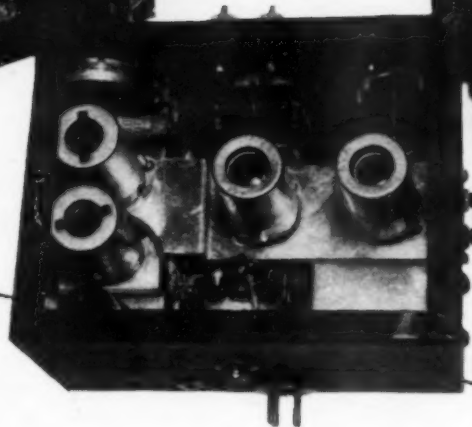


Fig. 3. Top view with cover removed. All tubes must be well shielded to prevent oscillation.

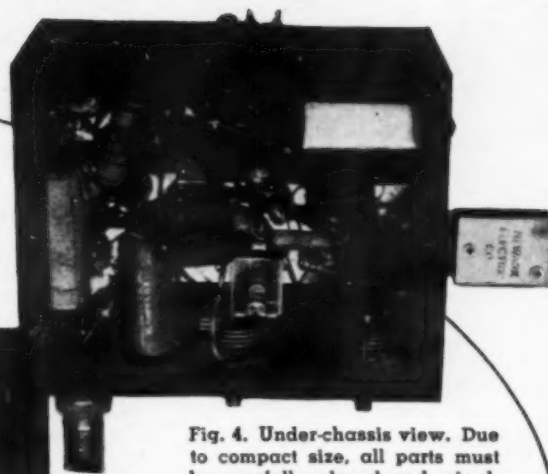


Fig. 4. Under-chassis view. Due to compact size, all parts must be carefully placed and wired.


two points of the T and by the audio gain control at the other point. Miniature type tube sockets with shields are available at surplus at a reasonable price, and help considerably in isolating the various stages. The shield on the modulator tube was omitted since it was not needed.

All wires and leads from condensers and resistors connect directly to terminals provided by tube sockets, plugs, switch, etc., which eliminates the need for terminal strips. To obtain a proper size r.f. choke (RFC₁) in the final grid lead it was necessary to remove two pi's from a standard 2.5 mh. r.f. choke and use the remaining two pi's with just enough of the ceramic core to hold them together.

The neutralizing capacity is a small 3-30 μ fd. trimmer condenser. It is screwdriver adjusted and need only be adjusted once for any amplifier tube. Out-of-phase voltage for neutralization is obtained by placing the center of the final tank coil at ground r.f. potential with the amplifier plate at one end of the coil and the neutralizing condenser between the other end and grid. The final tank condenser is a single-section padding condenser which was designed to have the rotor grounded through the mounting stubs. The connection between the rotor and grounded stub can be broken with a small, sharp chisel and then part of the metal strip connecting the two may be removed. However, being a single section condenser there will be an unbalance between the rotor capacity to ground. This unbalance will change the required neutralizing capacity slightly

(Continued on page 134)

Fig. 5. Complete schematic diagram of 10-meter phone transmitter. Crystal oscillator is the well-known tri-tet circuit.

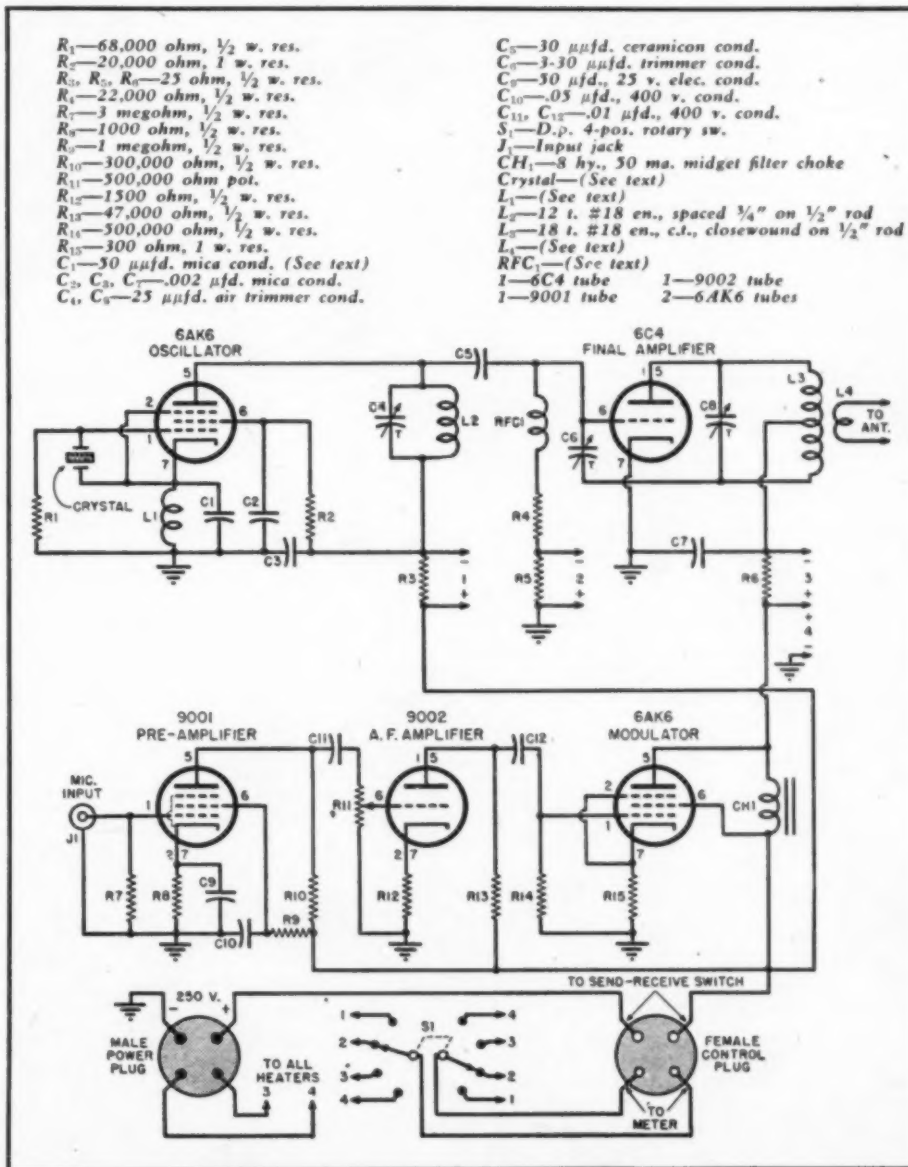

A Compact E.C.O. Controlled TRANSMITTER

This unit serves as a complete transmitter or as an exciter with either v.f.o. or crystal control.

By

HARRY R. HYDER, W2LIW

MOST amateurs build their v.f.o.'s as a separate unit, to be placed on the operating table alongside the station receiver. The v.f.o. usually feeds a string of doublers in the transmitter proper. The unit itself delivers but a watt or two of power. There is a lot to be said for isolating the v.f.o. from the transmitter as much as possible, but several transmitter manufacturers have demonstrated that it is entirely feasible to make the v.f.o. an integral part of the transmitter. This naturally requires some care in design and construction.


At this station, it was planned to make the v.f.o. as versatile as possible. Compactness was sought so that the unit could serve as a complete portable transmitter. A reasonable amount of power output was desired in order that the unit could serve as a transmitter alone, or, be used to excite a high-power final. It should operate on all bands with a minimum of coils and tuning adjustments. Provision should be included for crystal control on any band. Finally, but most important, it should put out a clean signal of high stability.

All the above requirements are met in the unit pictured above. Its outside dimensions are 7" x 14" x 8". It delivers a measured output of 20 watts on the 28 mc. band and 35 to 40 watts on all other bands (without exceeding CCS ratings!). There are only three tuning controls, changeover to crystal control is automatic, and the quality of the signal is all that could be desired.

Circuit Details

As is evident from the diagram (Fig. 2) an 802 is used as the electron-coupled oscillator, followed by a 6L6 buffer-doubler (which also serves as a crystal oscillator). The final amplifier is an 807.

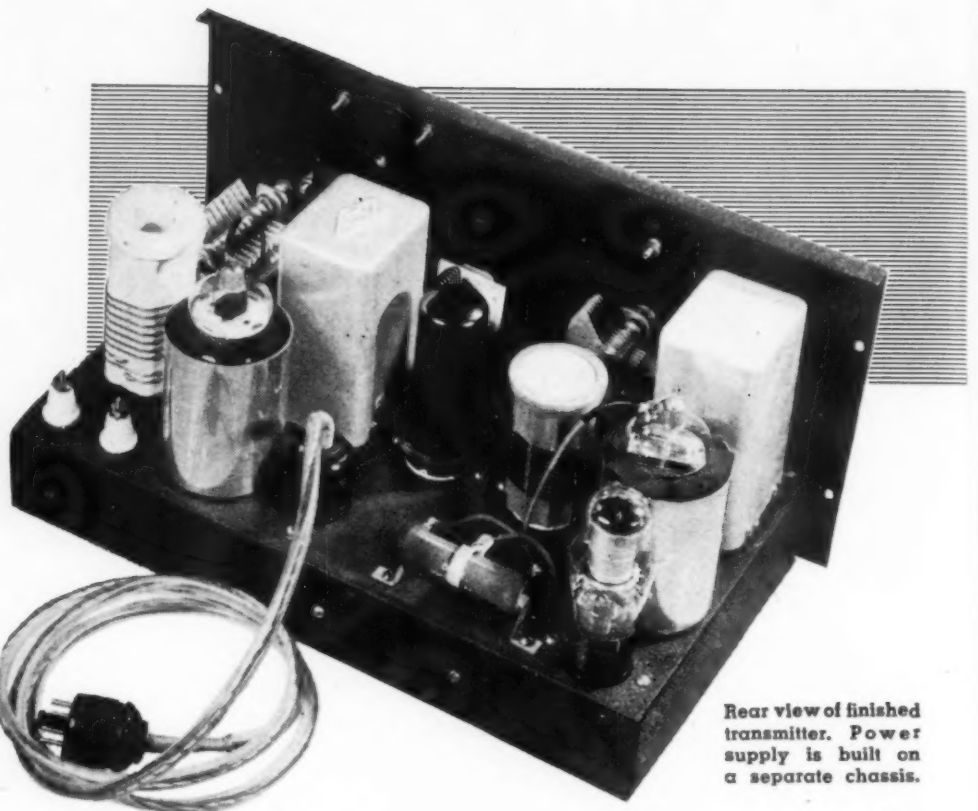The 802 was chosen because of its excellent shielding and rugged construction, so important in any self-excited circuit. Care was taken to make the oscillator stable and free of hum modulation. A tank capacity of 500 μ fd. is used, together with a 50 μ fd. "band setter" and a 100 μ fd. tun-




Rear view of finished transmitter. Power supply is built on a separate chassis.

ing condenser. The fundamental frequency range is 3500 to 3650 kc.; output is secured on that portion of the 3.5 mc. band and on all of the 7, 14, and 28 mc. bands. The filament of the 802 is at the same r.f. potential as the cathode. This removes all traces of hum modulation. The screen and suppressor are tied together. A VR-105 voltage regulator controls the screen voltage. The plate circuit of the 802 is rather interesting. On the 3.5 and 7 mc. bands, the plate impedance is a 2.5 mh. r.f. choke, mounted in a blank 5-prong coil form. On the 14 and 28 mc. bands, the plate load is a 7 mc. coil, wound on a similar form. This coil is resonated to about 7200 kc. by a mica trimmer mounted inside the coil form. Once set, the trimmer needs no further adjustment, as the tuning is sufficiently broad to cover the entire band. Enough excitation is supplied to drive the 6L6 as a doubler to 14 mc. These coils also have jumpers across some of the prongs (see Fig. 2) which make the power supply connections to the 802 plate and screen. Thus, when no coil is in the 5-prong oscillator plate coil socket, there are no voltages

(except filament, of course) on the 802. When crystal control is to be used, a crystal is plugged into this 5-prong socket. The 6L6 then operates as a straight-forward crystal oscillator. All of the crystals used were of the pre-war variety, which fit a 5-prong tube socket. For the newer type crystals an adapter may be used, or an octal socket and octal-based coil forms may be adapted.

The 6L6 buffer-doubler-crystal oscillator has sufficient cathode bias to keep the idling plate current within the dissipation rating, therefore, no provision is made for metering this circuit. The plate circuit is resonated with the aid of a $\frac{1}{4}$ watt neon bulb, which is pushed through a rubber grommet on the front panel. A wire is soldered to the center contact of the bulb and wound several times around the 6L6 plate lead, making a good, cheap, resonance indicator. In addition to cathode bias, the 6L6 has a 100,000 ohm grid leak, which increases its harmonic output. The 6L6 plate coils are found on National XR-2 1" diameter forms, and mounted inside National PB-10-5 plug-in shields.

RADIO NEWS

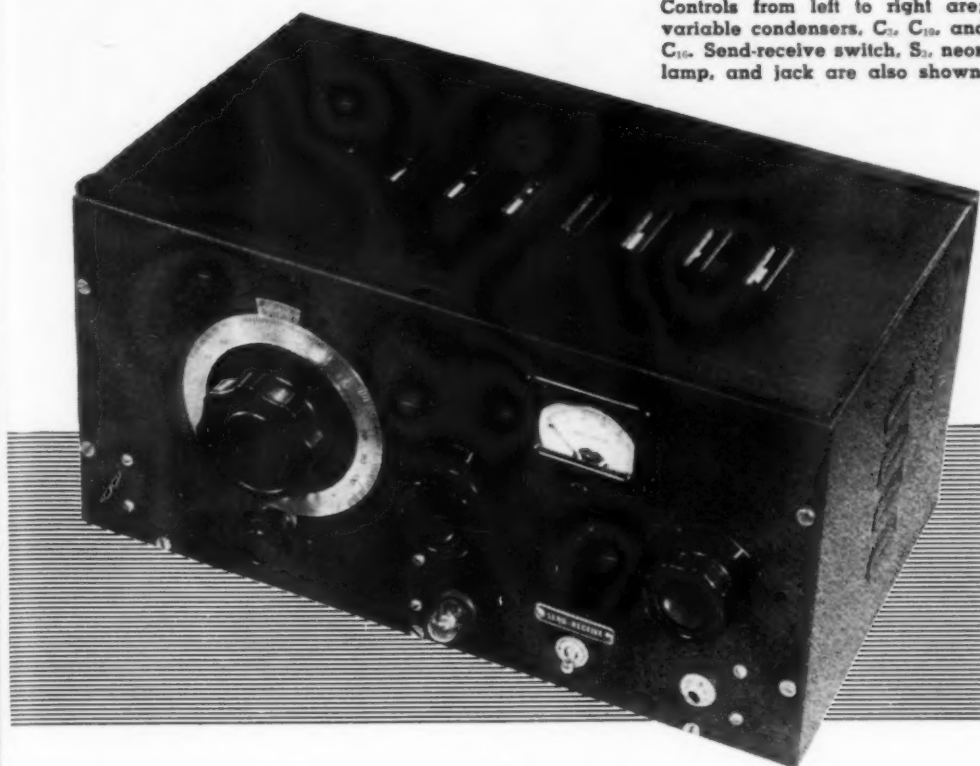

Controls from left to right are: variable condensers, C_{12} , C_{13} , and C_{14} . Send-receive switch, S_1 , neon lamp, and jack are also shown.

in diameter, has a reduction drive, and a vernier permitting it to be read to one-tenth of a division. The buffer and amplifier tuning controls are fitted with 2" diameter skirted knobs.

Most of the components are mounted underneath the chassis. A ground bus is run from one end of the chassis to the other, and all r.f. grounds and bypass returns are made to this. In addition, even though all tuning condenser rotors are grounded to the chassis, wire leads are brought from their terminals to the ground bus. This idea could well be incorporated in all high frequency gear, since it insures minimum r.f. currents in the chassis proper, thus preventing unwanted coupling between circuits.

The 802 and 807 sockets are sub-mounted 1", to increase the clearance between their plate caps and the cabinet lid. Sleeve shields are used on both the 802 and 807. The 6L6, being metal, requires no shielding. Several small pieces of sponge rubber were jammed into the 802 shield, to prevent vibration of the tube.

The 6.3 volt filament transformer is mounted on the back drop of the chassis. All power leads are brought to a male octal socket. The power cable has a female plug at one end, which plugs into the transmitter, and a male plug at the other, which plugs into the power supply. The cable is made by running insulated wires through transparent plastic sleeving.

Shielding of these coils is necessary, because of their proximity to the 807 plate circuit.

The 807 is operated as a straight amplifier on the 3.5, 7, and 14 mc. bands, and as a doubler to 28 mc. 47 ohm, 1 watt parasitic suppressors were placed in the grid and screen leads, right at the socket, before the bypass condenser. As a result, the 807 shows no traces of instability at any frequency. Bias for the 807 is obtained partly from a 200 ohm cathode resistor, and partly from a 22,000 ohm grid leak. In addition to supplying bias, the 200 ohm resistor acts as a key-click filter. The 807 screen is fed from a dropping resistor, suitably bypassed for r.f. and audio. A note of warning—the amplifier tank r.f. current flows through both the plate and screen bypass condensers. They should be placed close to the final tank coil socket, have short, heavy leads, and be of the high-voltage mica types. The 807 tank coils are standard items, manufactured by E. F. Johnson Co. Similar coils of other manufacturers may be used, of course. The 3.5 mc. coil has a 25 μ fd. double-spaced trimmer mounted internally, since it was not possible to resonate it with the 50 μ fd. tuning condenser. A 0-150 d.c. milliammeter is wired in the plate circuit. It is not a bad idea in this case, to shunt the meter with a condenser, since the r.f. field is rather strong. Output is taken from the coil links, connected to a pair of feed-throughs on the rear of the chassis.

Construction

The unit is built on a 7" x 13" x 2" steel chassis, and mounted in a 7" x 14" x 8" hinged-lid cabinet. The chassis must be spaced back from the panel about $\frac{1}{8}$ " in order to clear the front

lip of the cabinet. All tuning condenser frames are at ground potential, so no insulation problems or shock hazards exist. A good, accurate dial is a "must" in any v.f.o.; this one is 4"

Table 1. Winding data for coils required to cover 3.5, 7, 14, and 28 mc. bands.

COILS REQUIRED			
Band	Osc. Plate	Buffer Plate (L_1)	Amp. Plate (L_2)
3.5 mc.	A	C	F
7 mc.	A	D	G
14 mc.	B	E	H
28 mc.	B	E	J

If crystal control is desired on any band, an appropriate crystal may be plugged into the oscillator plate coil socket. (For socket wiring see Fig. 1.) This automatically removes plate and screen voltages from the e.c.o. The buffer then operates as a straight crystal oscillator. For 3.5 mc. crystals, use coil C for L_1 ; for 7 mc. crystals use coil D; for 14 mc. crystals use coil E. The final amplifier may be used either as an amplifier or a doubler, in order to obtain a plurality of crystal frequencies.

COIL WINDING DATA

Osc. Grid Coil (L_1)
14 t. No. 22 d.s.c., 1" long, tapped 4 t. from gnd. end. Fil. winding 4 t. interwound at gnd. end. (See diagram below.)


Osc. Plate Coils
Coil A: 2.5 mh. r.f. choke, mounted inside blank 5-prong form. (See inset Fig. 1 for wiring.)
Coil B: 12 t. No. 20 en., 1½" diam., spaced to 1½" length. 25-125 μ fd. mica trimmer mounted inside 5-prong form. (See inset Fig. 1 for wiring.)

Buffer-Doubler Plate Coils (L_2)
Coil C*: 45 t., No. 24 d.c.c., close-wound.

Coil D*: 20 t., No. 20 d.c.c., close-wound.
Coil E*: 12 t., No. 18 d.c.c., spaced to 1".
*Coils wound on 1" diam. forms mounted inside National PB-10-5 plug-in shields.

Final Amp. Plate Coils (L_2)
Coil F*: 3.5 mc., 50 w. plug-in coil. 25 μ fd., double-spaced air trimmer set to full capacity mounted inside. 32 t., No. 16 en., link 6 t. No. 16 en. (See text.)
Coil G*: 7 mc., 16 t., No. 16 en., link 4 t. No. 16 en. (See text.)
Coil H*: 14 mc., 9 t. No. 14 en., link 3 t., No. 14 en. (See text.)
Coil J*: 28 mc., 6 t. No. 12 en., link 2 t. No. 12 en. (See text.)
**Coils wound 1¼" diam. forms, 2" winding length. All link coils wound at cold end.

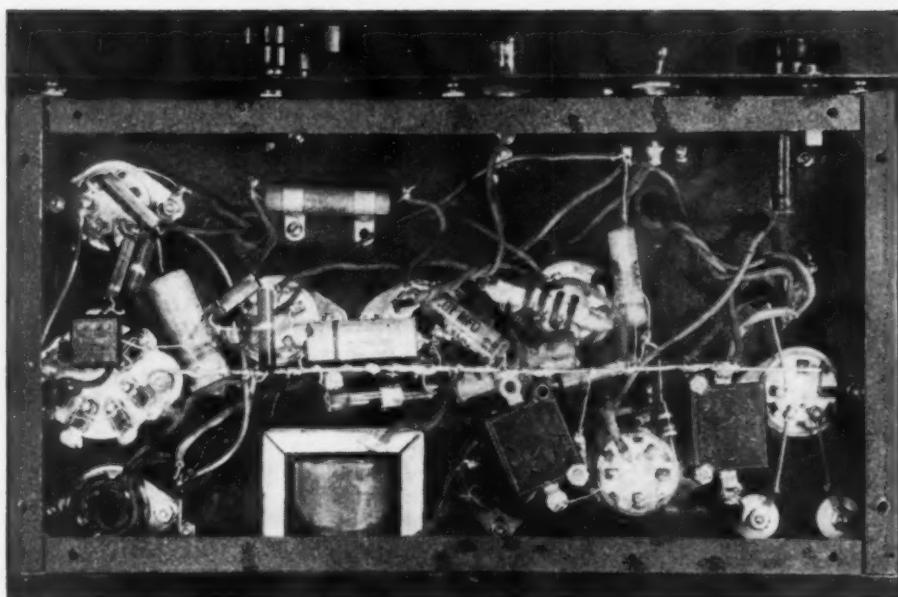Construction of oscillator grid coil (L_1).



Under chassis view shows location of miscellaneous components.

The power supply requires little comment. It supplies 500 volts at 100 ma. for the amplifier, and 350 volts at

100 ma. for the oscillator and buffer. A common transformer and filter choke are used, with separate recti-


fiers for the two voltages. The choke is in the negative lead. The high-voltage portion of the supply uses a 5U4G, the low voltage a 5Y3GT.

Operation

It is best to get the electron-coupled oscillator operating first. Plug in the oscillator coil, the form-mounted r.f. choke in the plate circuit, and the 802 and VR-105 tubes. Apply filament voltage and allow about 15 minutes for the 802 to reach its normal operating temperature. Then turn on the plate voltage. Adjust the slider on the VR-105 dropping resistor until the tube ignites, as indicated by the familiar blue glow. It would be a good idea to check the current drawn by the VR-105; for best regulation, this should be about 30 ma. Next, set the oscillator tuning condenser to about 90% of full capacity. Tune the receiver or frequency meter to 3500 kc. and adjust the 50 μ fd. trimmer across the oscillator coil until the signal is heard. The high frequency end of the band should then be checked; 3650 kc. should fall at about 10% of full capacity.


(Continued on page 76)

Fig. 1. Complete schematic diagram for transmitter. Oscillator plate coils, A or B, or crystals plug into coil socket shown.

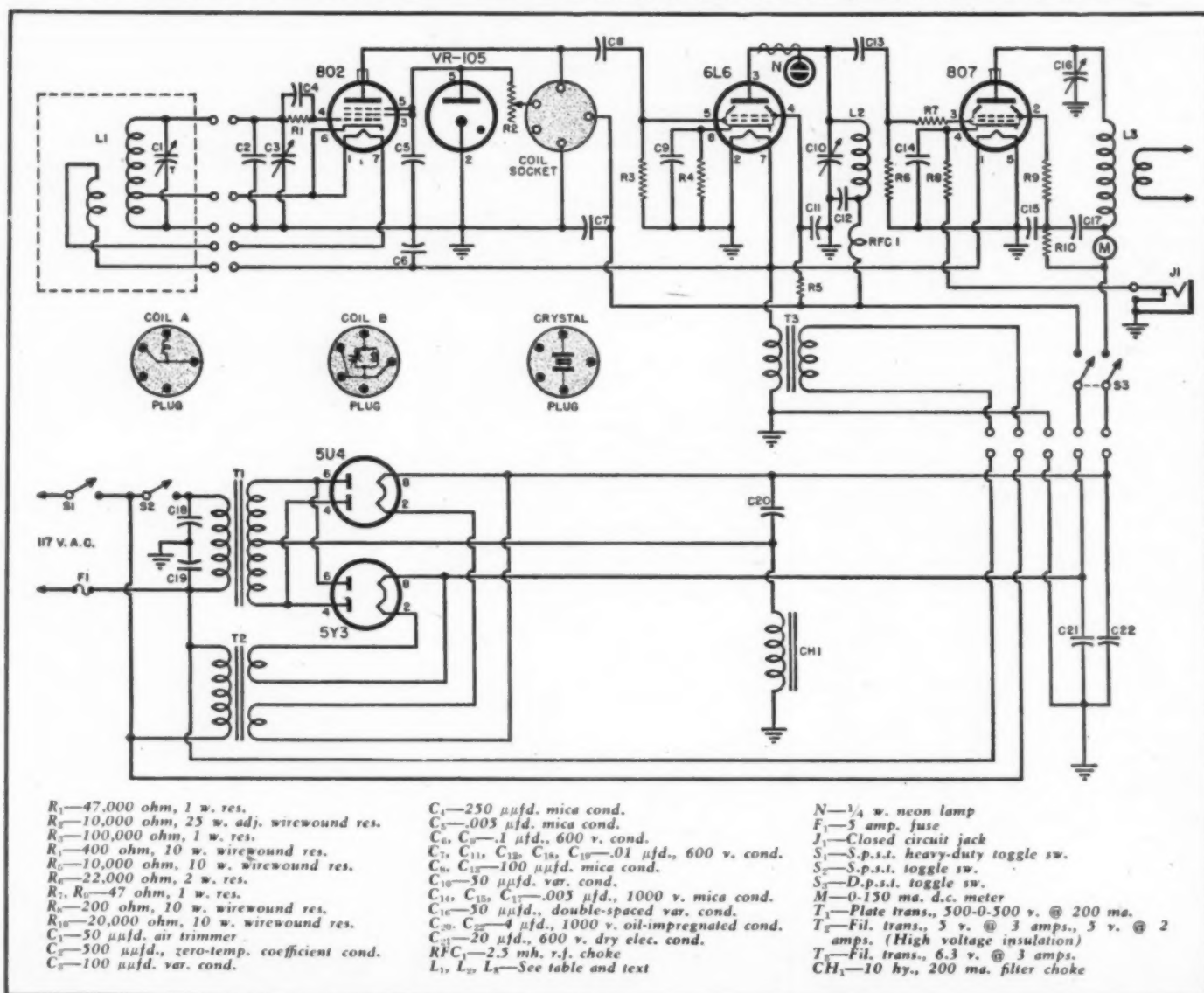

International **SHORT-WAVE**

Compiled by **KENNETH R. BOORD**

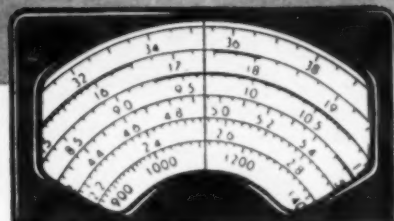

THIS month we salute a southern *Good Neighbor* of the British West Indies—the new *Radio Trinidad*, VP4RD, Port-of-Spain, Trinidad, B.W.I.

William MacLurg, general manager, Trinidad Broadcasting Company, Ltd., 11B Maraval Road, Port-of-Spain, sent us this data on VP4RD (this call sign will be changed shortly to a "Z" call sign):

The name of *Radio Distribution* has been associated with broadcasting in the Colony of Trinidad for so long that it is perhaps not surprising that some people in that island have been wondering whether *Rediffusion* would be closing down when *Radio Trinidad*, station of the Trinidad Broadcasting Co., Ltd., commenced operations in the Colony. Such is by no means the case.

The Trinidad Broadcasting Co., Ltd., and Radio Distribution (T'dad), Ltd., are two entirely separate and distinct companies, each operating a public service. These services, however, are complementary.

Rediffusion, which operates extensively in Great Britain and the Colonies, does not normally originate programs; the origin of programs is primarily a function of the broadcasting organization, and it is the job of a wired broadcasting service—such as *Rediffusion*—to see that those programs are brought to the listeners' homes with the best possible quality and freedom from interference. The universality of radio broadcasting has resulted in a general state of interference and restriction in quality of reproduction from which wired distribution systems have comparative immunity. This is particularly true in densely populated areas, where electrical and man-made interference are rife, and *Rediffusion* provides listeners with a means of overcoming this type of interference by connecting them to the studio by a direct wire.

In a recent presidential address to the Institution of Electrical Engineers, Sir Noel Ashbridge, M.I.E.E., now Assistant Director General to the British Broadcasting Corporation, stated that wired broadcasting, that is, *Rediffusion*, was the inevitable outcome of the present limitations of ordinary broadcasting. It is for this reason that the two services exist—to provide a high-quality entertain-

ment service in densely populated areas, and broadcasting via *Radio Trinidad* is the natural medium for providing a Colony-wide service.

Each company is managed by a man with considerable experience in his own specialized field. W. A. MacLurg, general manager of the Trinidad Broadcasting Co., Ltd., has been with the BBC for 15 years, and A. Cross, general manager of Radio Distribution (T'dad), Ltd., has been in the service of the Rediffusion Company in the United Kingdom and elsewhere for 17 years. Also on the staff of *Radio Trinidad*, as studio manager, is Gerard V. de Freitas, long associated with ZFY, "The Voice of Guiana," Georgetown, British Guiana.

Thus, there are now in Trinidad two radio companies, with entirely separate but complementary functions, and with a single purpose: *Public Service*.

Radio Trinidad was officially opened on Sunday, August 31, by His Excellency the Governor, Sir John Shaw, K.C.M.B. The program included greetings and musical messages from other radio stations in the Caribbean area; a special Trinidad edition of "Caribbean Carnival" from

the BBC; "This is Trinidad," a picture in words and music of the Colony of Trinidad and Tobago; "Evesong" from the Cathedral of the Holy Trinity, Port-of-Spain, conducted by the Very Reverend Beardmore, O.B.E., Dean of Trinidad; "Music from Trinidad," singers, musicians, bands, and local artists; and other features.


Radio Trinidad began its career as a "new voice in the air" with four main objectives: 1. To give the people of Trinidad and Tobago the sort of radio service they want. 2. To co-operate with Government and other official bodies and with radio services such as the BBC in the spreading of news, knowledge, and information. 3. To provide an effective and efficient radio advertising service for those who take time on the station for this purpose. 4. To provide a radio service of higher technical quality.

Officials of the station pointed out that "These objectives can best and mostly quickly be achieved if you, the people of Trinidad and Tobago, remember that this is *your* radio service and that the station invites and indeed is very anxious to receive suggestions and criticisms . . . *Radio*

(Continued on page 149)

Sample QSL card which is being sent out by "Radio Trinidad," Port-of-Spain.

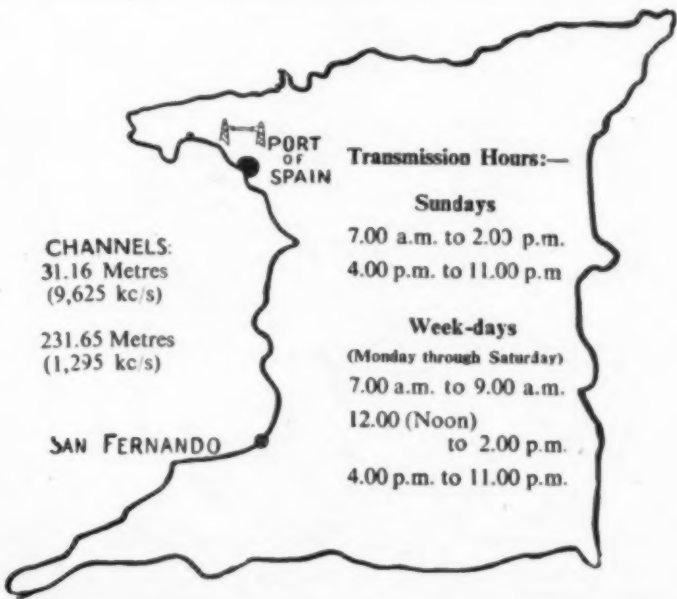QSL FROM "RADIO TRINIDAD", BRITISH WEST INDIES



CHANNELS:
31.16 Metres
(9,625 kc/s)

231.65 Metres
(1,295 kc/s)

Transmission Hours:—
Sundays
7.00 a.m. to 2.00 p.m.
4.00 p.m. to 11.00 p.m.

Week-days
(Monday through Saturday)
7.00 a.m. to 9.00 a.m.
12.00 (Noon) to 2.00 p.m.
4.00 p.m. to 11.00 p.m.

HANDS THAT SEE



The students' first contact with radio is in the Science Room where the instructor is shown teaching them theory of electricity and magnetism. Standard textbooks are used and classroom notes are taken, in Braille, on the machines shown.

N. Y. Institute for the Blind prepares students for their ham license exams.

AN HOUR'S ride from downtown Manhattan, on picturesque Pelham Parkway, is the New York Institute for the Education of the Blind. Founded in 1831, the school has grown with great strides, so that today, through the efforts of a former student, it proudly

boasts of a modern, topnotch radio section. Happily responsible for the rapid growth and establishment of this phase of the school's curriculum is that former student, who is now instructor of the radio department. The sequence of instruction, methods of demonstration, and a myriad of lesser problems had to be overcome, for Robert W. Gunderson had no pattern or example to follow except that of determination to succeed at his task.

Now after 15 years of activity, requiring many evenings and weekends of hard work, students go through



Combination circuit and Braille demonstration board is the means by which the theory is applied to actual practice. This system is analogous to the well-known block diagram in radio.

The next, and natural, step is to learn construction techniques. Here the instructor helps the student learn the proper handling of the soldering iron for wiring a radio chassis.





With theory and construction techniques mastered, the students are instructed in the operation of the school's high fidelity audio network. While the instructor supervises, Vito cleans the cutting table and Al maintains the proper level on unit.

the radio section of the Institute at the rate of 10 per year. Theory naturally comes first, but instructional technique must necessarily be different. The blind literally "see" with their ears and sensitive fingers, so textbook data and instruction manuals must be set in Braille, from whence it is translated orally by the teacher. Small machines, called Braille Writers, and faintly resembling a typewriter, are often used for classroom note work.

From theory classes, the student studies circuit applications with the demonstration boards designed and built by the instructor, and patterned after the well-known Dynamic Demonstration Board. Using these enlarged, Brailled, block diagrams, the student learns the component parts and their placement in circuits. Actual practice is soon begun, and students begin learning the proper handling of tools and the correct construction techniques. Starting first with simple breadboard receivers or amplifiers, they soon advance to building finished units that look and operate as well as any commercial product.


If the student hasn't been bitten by the "ham" bug from the beginning, he certainly has by now, so concurrent code instruction and practice is interspersed throughout the course. By the time the boys (and an occasional girl) are well up on theory, they also possess a code proficiency high enough, or better, to meet license requirements, and

(Continued on page 179)

After winning his coveted ham license, this senior student goes on the air with a two-meter portable rig which he built.



December, 1947

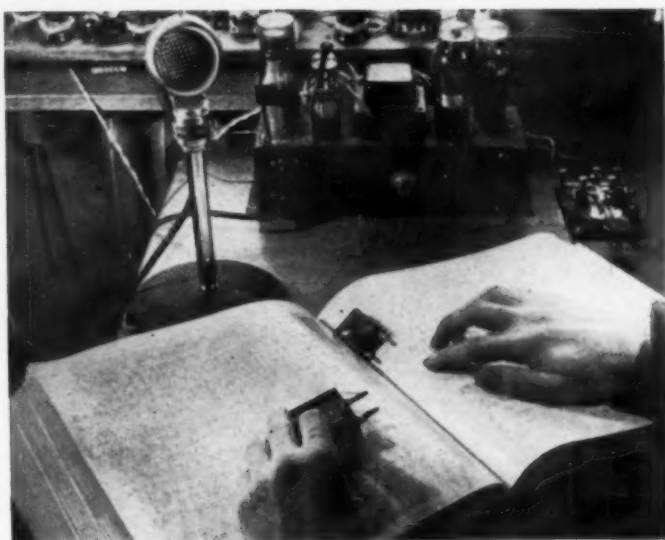

By now every student has been bitten by the urge to become a "ham." In the textbook translated to Braille, our student studies the frequency control of a transmitter by use of a crystal. Note the Braille frequency markings on the crystal.



Keeping the station log is also done in Braille. The sheets are shellacked to retain the raised dots and then bound into a permanent form. Operator is shown checking time for entry.


A fine example of the excellent workmanship seen at the school is the instructor's pet transmitter. The rig was built entirely by Mr. Gunderson, including drilling of chassis and panels.



Practical RADIO COURSE

By

ALFRED A. GHIRARDI

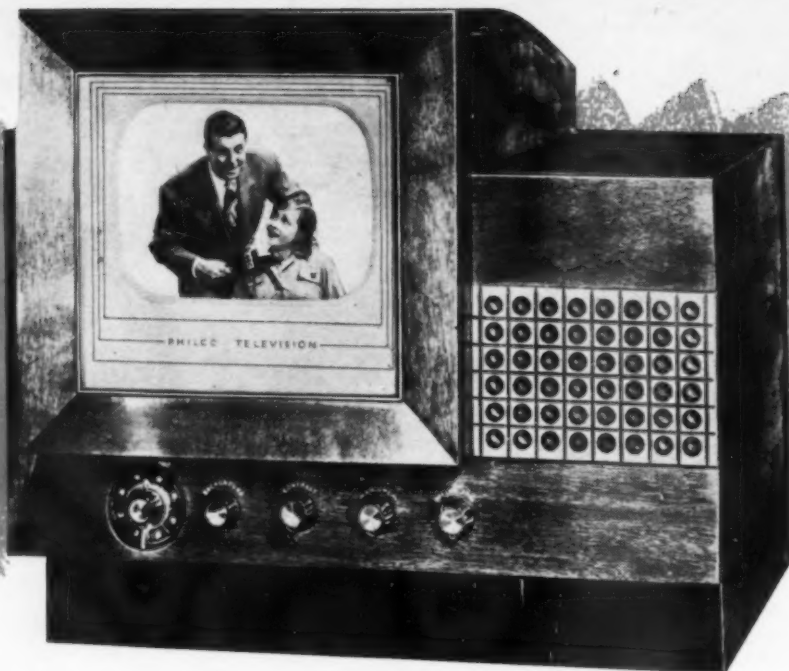

The new Philco Model 1000 table receiver which features a ten inch picture tube, automatic level control, and electronic tuning control.

IN ORDER to make a nationwide television broadcasting system possible, certain uniform video and audio transmission and reception standards have been set up by the FCC and the RMA for use in the United States. These have been modified several times during the past few years, but it is likely that those recommended most recently will remain in effect for some time to come. The picture can still be improved a great deal without changing these standards by making refinements within the system. Designers of new television broadcasting transmitters, as well as manufacturers of postwar television receivers for black-and-white picture reproduction, are now employing them as their standards of television engineering practice. A knowledge of the composition of television signals, and familiarity with a few of these standards, is necessary for a clear under-

Part 57. Analysis of the composite video signal and the characteristics of the basic elements that make up the sound and video channels of a TV receiver.

standing of the bandpass acceptance response characteristics required in the sound and video i.f. amplifiers of modern television receivers. It will, therefore, be well to first obtain a clear understanding of the modulation characteristics and bandwidth requirements of the *video* (picture) and the accompanying *audio* (sound) signals.

The Composite Video Signal


The signal generated by the camera tube in the television broadcast studio is employed to *amplitude-modulate* the video carrier of the television transmitter. The composite video signal is really a combination of the pic-

ture signal and those produced by several associated scanning and synchronizing circuits that are necessary to the system.

For transmission of the present standard 525-line black-and-white type of picture interlaced at 30 frames (60 fields) per second, the composite amplitude-modulated video signal actually involves a range of sideband frequencies extending to approximately 4.5 mc. above, and below, the video carrier frequency employed, in order to convey all the image information ranging from the very large objects in a scene (which result in relatively low modulation frequencies) to the very small details (which result in much higher modulation frequencies). In practice, the range of sideband frequencies transmitted is limited to approximately 4 mc. as this has been found to be adequate.

If conventional full double-sideband AM transmission were employed for the video signal, a frequency channel $2 \times 4 = 8$ mc. wide would be required for it. In order to economize on the radio spectrum necessary to accommodate a sufficient number of television broadcast transmitters in a given service area, the bandwidth required by the composite video signal of each transmitter is greatly reduced below this value by employing for it a modified form of single-sideband transmission known as *vestigial sideband transmission*. It is important that this type of transmission be clearly understood, for it is responsible for the peculiar and unusual shape of the band-

Fig. 1. Ideal video (picture) transmission characteristics.

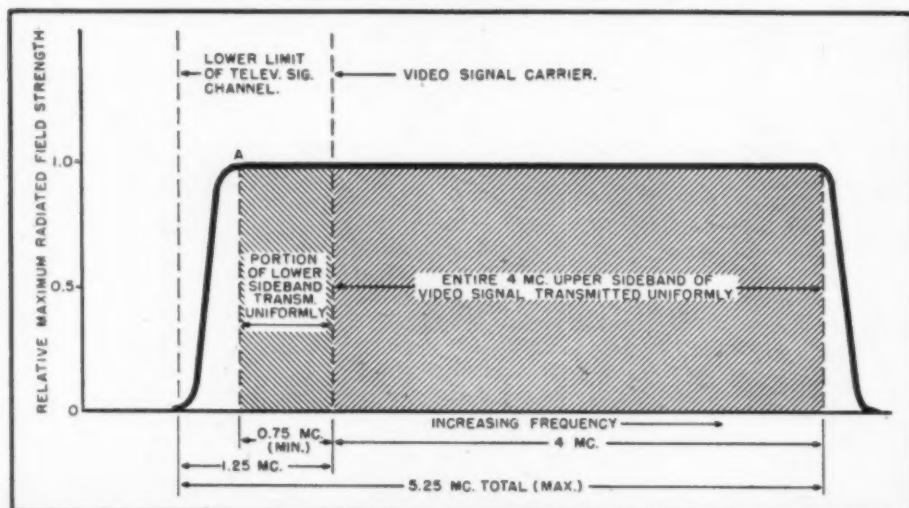

pass acceptance response characteristic required in the video i.f. amplifier of a television receiver.

Vestigial Sideband Transmission of the Video Signal

The standard ideal video transmission characteristic is illustrated in Fig. 1. As shown, the video carrier frequency is set 1.25 mc. above the low-frequency limit of the transmitting channel assigned to the television station. It will be observed that all the modulation components in the entire upper sideband (up to 4 mc. from the video carrier frequency) are transmitted uniformly. Those in the lower sideband are partially suppressed. Only those lower sideband components of frequencies up to about .75 mc. from the carrier frequency are transmitted uniformly. Those of a frequency between about .75 and 1.25 mc. from the carrier frequency are partially attenuated (as shown by the sharp drop at the left of point A in Fig. 1) by means of suitable filters in the transmitter so that a negligible amount of energy at these frequencies is radiated. Those of a frequency greater than 1.25 mc. from the carrier frequency are entirely suppressed (observe that the transmission characteristic drops to zero value at the 1.25 mc. point). Therefore, since these higher-frequency components of the lower sideband are rejected at the transmitter, *single-sideband* transmission results for the higher video modulation frequencies above about .75 mc. and double sideband transmission takes place only for the lower video modulation frequencies between zero and about .75 mc.

This partial suppression of one side-

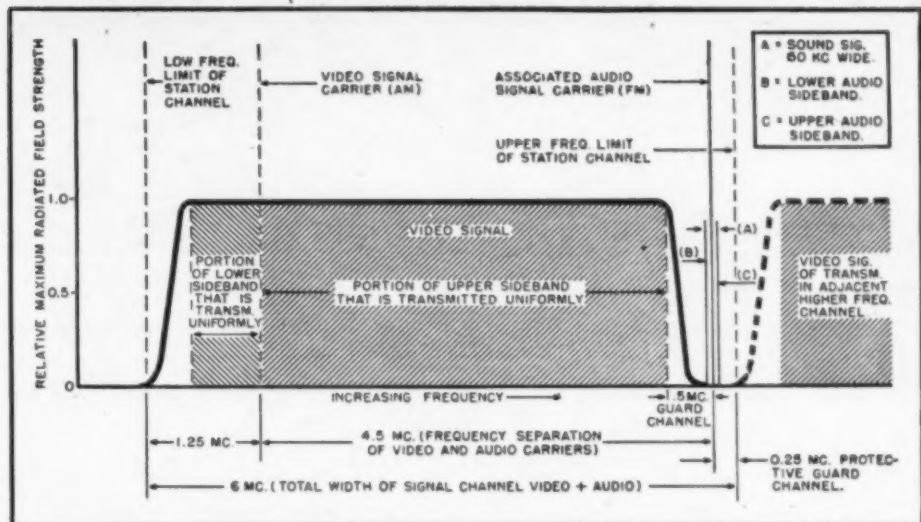


Fig. 2. Video-audio division of channel and relative positions of the video and audio signals (and their transmitted sidebands) in the 6-mc. wide television transmitter channel.

band is known as *vestigial* sideband transmission, and it serves the very useful purpose of making it possible to satisfactorily effect transmission of the desired intelligence without need for employing nearly as wide a frequency channel as would be required if full double-sideband transmission were employed.


Vestigial sideband transmission can be used in television because the video signal consists of a series of various types of pulses. Since the function of each pulse is to actuate a circuit in the receiver in order to produce a visual action, only one-half of each pulse

cycle is actually necessary. In fact, single sideband transmission (transmission in which one sideband is completely suppressed and only the other is transmitted) would serve satisfactorily for the video signal if it were not for the fact that removal of the entire lower half of the signal would introduce phase shifts that would ruin the picture. Therefore, it is necessary to remove only that part of the lower sideband portion of the signal which will not cause a serious shift in phase. The amount removed in the standard transmission characteristic illustrated in Fig. 1 has been found to fulfill this requirement.

The fact that a part of the lower sideband is transmitted along with the

¹ Because of technical limitations in transmitter filters, it is not practical to suppress the entire lower video sideband. Consequently, a portion of this sideband is transmitted.

Fig. 3. Block diagram illustrating functional operation and the two separate i.f. channels in conventional postwar television receiver.

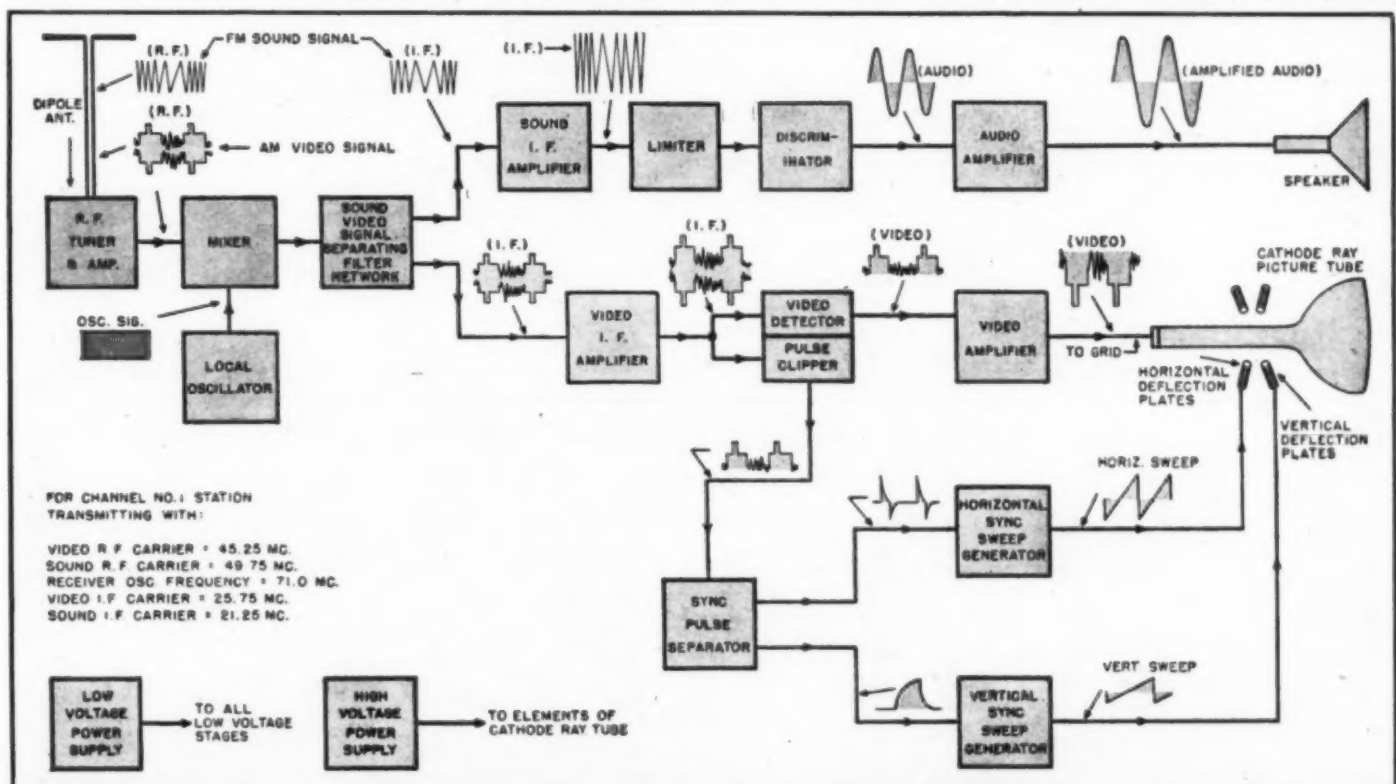

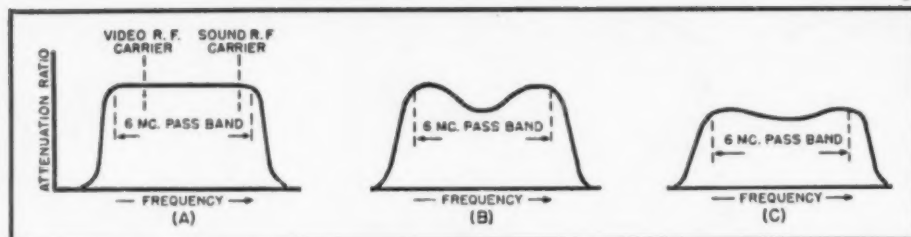


Fig. 4. Three band acceptance characteristics for the r.f. tuning circuits in a TV receiver.

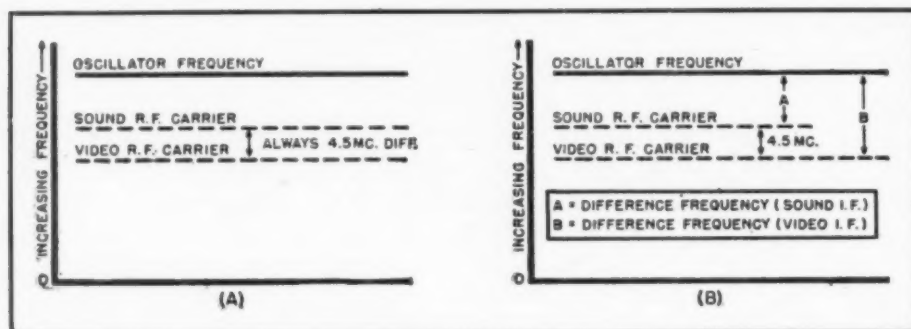


Fig. 5. (A) Relation of local oscillator, sound r.f. carrier and video r.f. carrier frequencies in a television receiver. (B) Relation between the "difference" frequencies produced during frequency conversion, giving rise to the sound i.f. carrier and video i.f. carrier frequencies.

full upper sideband actually results in an over-emphasis of the low modulating frequencies, since the energy of the low frequencies of the partially suppressed lower sideband adds to that of the low frequencies of the upper sideband. To avoid this over-emphasis, the tuned circuits of the video i.f. amplifier in the television receiver must be designed to provide an unusual form of bandpass acceptance characteristic that attenuates the video carrier frequency 50% (see Fig. 7.). This compensates for the over-emphasis of the low modulating frequencies at the transmitter and results in substantially flat response (for the complete system) over the entire video modulation-frequency band.

The Audio Signal

Simultaneously with the viewing of the scene to be televised, a microphone picks up the sound which attends the scene and converts it into equivalent electrical variations which are employed to modulate a separate carrier

employed for transmission of the sound (audio) portion of the television program. *Frequency modulation* is now employed for the sound program, with a swing of ± 25 kc. defined as 100% modulation. A system capability of 50 to 15,000 cycles is used and pre-emphasis having a time constant of 75 microseconds is employed. This practice has been standardized by the FCC for use in America.

Television Transmission Channels

The television frequency channels allocated by the FCC for use by commercial television broadcasting stations in the United States have been revised several times. Present regulations provide for the establishment of thirteen numbered channels each 6 mc. in width. These are located in two bands in the v.h.f. portion of the radio spectrum. Six of the channels lie in the 44 to 88 mc. band. The other seven

² In addition, the frequency band between 480 and 496 mc. has been allocated for use by transmitters engaged in transmission of experimental color television.

lie in the band of higher frequencies between 174 to 216 mc.² The lower and upper frequency limits of each of these 13 channels, together with the Channel Number assigned to each, are tabulated herewith for reference:

CHANNEL NO.	FREQUENCY LIMITS
1	44-50 mc.
2	54-60 mc.
3	60-66 mc.
4	66-72 mc.
5	76-82 mc.
6	82-88 mc.
7	174-180 mc.
8	180-186 mc.
9	186-192 mc.
10	192-198 mc.
11	198-204 mc.
12	204-210 mc.
13	210-216 mc.

Accommodating the Video and Audio Signals Within the Television Signal Channel


Although several methods have been proposed for transmitting both the video and audio signals on the same carrier, the practice now in vogue in the United States is to transmit the two signals simultaneously but by means of separate carriers differing in frequency by a definite amount. The relative position of these carriers in the 6 mc. wide spectrum of the frequency channel allocated to the television transmitter, and the division of the complete channel into the relative portions devoted to the video and audio signals and their respective transmitted sidebands has been standardized by the FCC and will now be discussed.

Video-Audio Division of a Television Channel

By regulation, the carrier frequency of the video signal is made 1.25 mc. higher than the lower-frequency limit of the station channel. This positions the video carrier near the low-frequency end of the station channel, as shown in Fig. 2.

In order to prevent the sound signal from causing audio interference with the low-frequency sideband of the video signal of the transmitter operating in the next adjacent channel of higher frequency, an adequate separating *guard channel* must be provided between them. This protective guard channel is provided by locating the sound carrier .25 mc. (250 kc.)

Fig. 6. Chart showing the oscillator frequency (Osc.), video and sound intermediate frequencies ($V_{i.f.}$, $S_{i.f.}$) and video and sound image frequencies ($V_{i.}$, $S_{i.}$) for television signals (V, S) in the six television transmission channels from 44 to 88 mc.

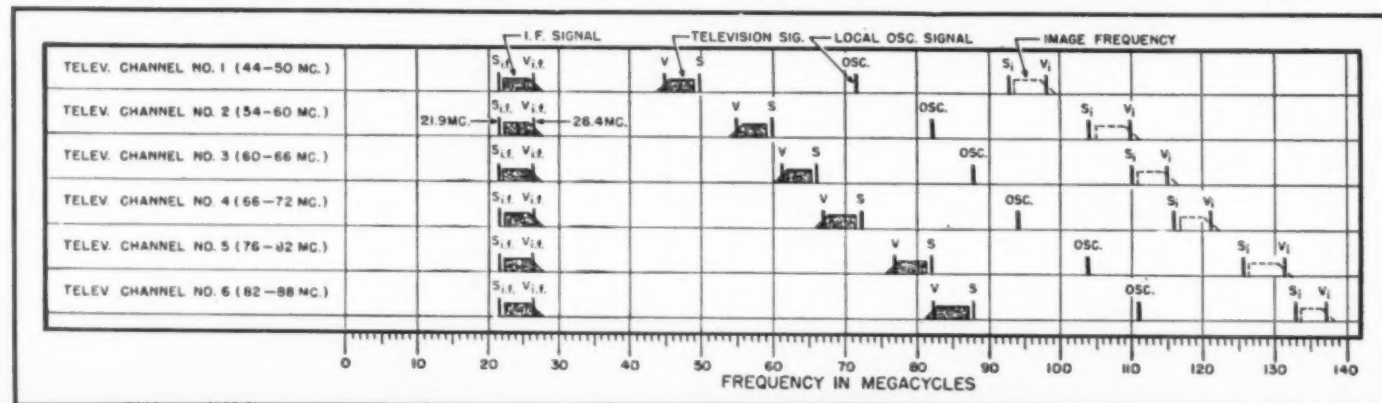

NEW!

in 1,000 pages:

**All data and basic knowledge
in radio and electronics
digested into 12 sections...
in a complete, quick to find,
easy to read, handbook form.**

Plan every operation in radio and electronics with the *Radio Data Book*. This new radio bible will be your lifelong tool... you will use it every day, on the board, at the bench, in the field! Use it for construction, troubleshooting and testing. The RADIO DATA BOOK will be your invaluable aid in design, experiment and in layout. It will help make your production better, faster and easier. In any and every operation in radio and electronics, you will use the RADIO DATA BOOK!

CONTENTS

Each section is a COMPLETE coverage of its subject... 12 sections... 12 books in ONE! 1000 pages... Schematics... Accurate photographs... Specially prepared drawings... White on black charts... Diagrams... Isometric projections and exploded views.

Section 1. THE 150 BASIC CIRCUITS IN RADIO.

Every circuit is analysed and explained in a Johnny-on-the-spot reference for any occasion.

Section 2. COMPLETE TEST EQUIPMENT DATA.

Know more about the test instruments you now have... Find the new ones you want to buy... They're All in here—impartially described!

Section 3. TESTING, MEASURING AND ALIGNMENT.

Simplified operation of the Oscilloscope... See what's happening inside any radio circuit... Dynamic alignment—AM, FM and TELEVISION made easy with the Oscilloscope... Scientific use of the Vacuum Tube Voltmeter, Signal Generating Equipment and other basic instruments.

Section 4. ALL ABOUT ANTENNAS.

AM-FM-Television... design, installation, characteristics, construction and feed.

Section 5. SOUND SYSTEMS.

Planning, installing and servicing a PA System. A complete chapter on every component... How to select and combine components... estimating costs... even acoustic requirements!

Section 6. ELECTRICAL AND PHYSICAL CHARACTERISTICS OF RADIO COMPONENTS.

Know the size, the power, the shape! A quick reference on the construction and design of any circuit or equipment.

Section 7. COMPLETE TUBE MANUAL: Receiving, transmitting and Commercial.

A flick of the pages brings you to all the data and ratings of any tube model!

Section 8. CHARTS, GRAPHS AND CURVES.

Quick calculation devices... Plotting curves, nomographs, rules and tables for speedy solutions to radio problems.

Section 9. CODES, SYMBOLS AND STANDARDS.


Handy reference to all radio symbols and abbreviations; code symbols, phrases and characters... Where you want them... When you want them!

Section 10. 50 TESTED CIRCUITS DESIGNED FOR OPTIMUM PERFORMANCE.

Find any circuit you want with complete parts lists and specifications... One tube receivers to complete AM, FM and Television receiver circuits... Amplifiers... Transmitters... Test Equipment and Control Circuits... All with the latest engineering refinements.

Section 11. DICTIONARY OF RADIO AND ELECTRONIC TERMS.

Section 12. RADIO BOOK BIBLIOGRAPHY.

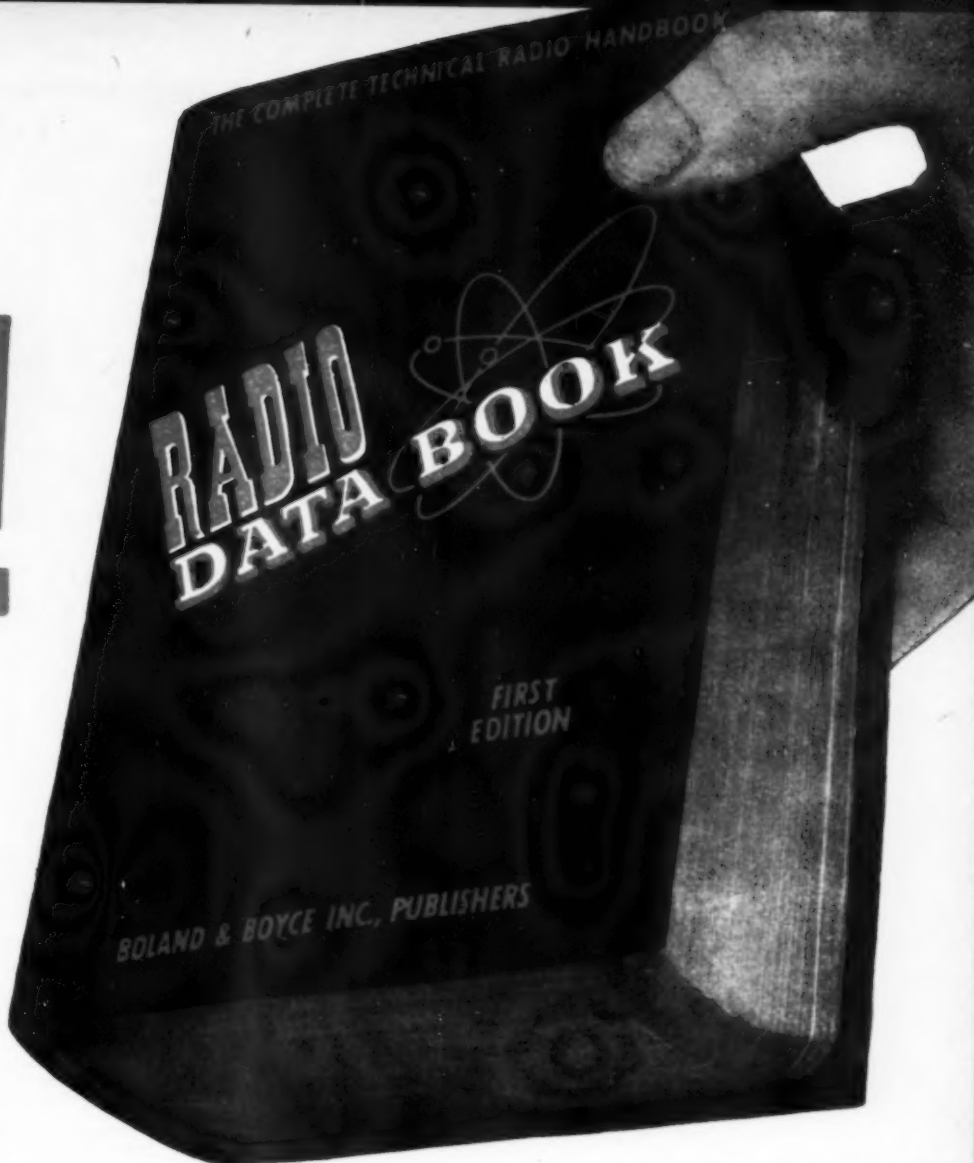

Handsomely bound in RED and GOLD

The RADIO DATA BOOK is a work of complete authority, prepared by engineers with many years of practical experience. They have been assisted by the Boland & Boyce staff of editors skilled in preparing electronics manuals for the U. S. Signal Corps for many years. These men have worked for several years gathering material for this book... all the knowledge of radio principles and operation... all the statistics... all the newest developments in electronics... every possible angle and detail. Eighteen months were spent digesting this material into the most concise, the clearest, and the most readable form. The result is this invaluable manual... The RADIO DATA BOOK. Whether you use this book for general reference, for scientific instruction, or for education, one thing is certain—the practical help, the daily usefulness you will derive from it will prove to be worth many, many times its astonishingly low price!

Advanced Sale... first printing, Only 10,000 available... To make sure to get your RADIO DATA BOOK, mail your order **NOW!**

12 complete books in one only \$5.00! Less than 42c per book

MAIL THIS COUPON TODAY

BOLAND & BOYCE INC., PUBLISHERS

460 BLOOMFIELD AVE. MONTCLAIR 3, N. J.

Please send me a copy of

THE RADIO DATA BOOK Enclosed is \$5.00.

NAME

ADDRESS

CITY ZONE

STATE

BOLAND & BOYCE INC., PUBLISHERS

BA Bargain Scoops!

52 OHM COAX CABLE

**BRAND NEW 60 Foot COILS
COMPLETE WITH CONNECTORS..... \$1.25**

It's genuine Amphenol RG-8/U—use it in place of RG-8/U. Has smaller diameter (.332), less capacity between center conductor and shield, less weight, easier to handle than RG-8/U. Rated at 1100 watts at 30 Mc. Supplied complete with standard Amphenol 83-1SP- (PL 259) connectors attached at each end.


No. 4A496—60 ft. coil with connectors..... **\$1.25**
Any number coils connect together with 83-1J connectors (below)

Extra Connectors



For use with above

Choice Each..... **35c**

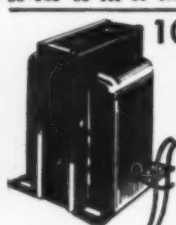

10 Hy. - 200 Ma.

Thordarson Filter Choke

200 ohm D.C. resistance, 2000 V. RMS; Size 3 3/4" sq. x 4 3/4" high. Wt. 5 1/2 lbs. Has 12" leads at side.

No. 13A266
Special Each..... **\$1.88**

80, 75 and 40 Meter CRYSTALS, 10 for \$3.95

In FT 243 holders, cut from highest quality quartz, accurately ground and acid etched. Frequency marked on each within 2 KC. Sorry we must sell them in ass'ts. our pick of frequencies—but you can't go wrong! There are plenty of choice frequencies for 80, 75 and 40 meters or for doubling to 20 and 10 meters in each ass't. Every one guaranteed to be an active oscillator.

Stock No. 21T3991
Ass't. of 10 only..... **\$3.95**

OIL FILLED CONDENSERS

10 mfd. 1000 volts C.D.
Dykanal TJU List \$12.00
No. 17A268
Spec. Ea..... **\$1.95**

8 mfd. 1000 volts Sprague
List \$10.80
No. 18A367
Spec. Ea..... **\$1.45**

5 mfd. 600 volts Sprague List \$7.00
No. 18A366
Special Each..... **65c**



JOHNSON VARIABLE




Dual section, 200 mmfd. per section, 2000 V. breakdown. Spacing .045". Type 200FD20.

List \$10.
No. 18A510 Special Ea..... **\$2.95**

Johnson variable, dual section, 304 mmfd per section. Spacing .045". Type 300ED20. List \$9.95.
Stk. No. 18A509, Special Each **\$3.45**

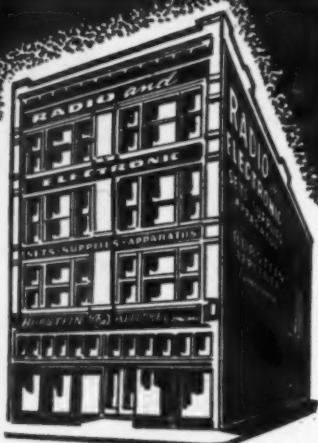Our terms: Cash with order or COD with 20% deposit please. Add Postage



HANDSET TS13

Combines a 200 ohm carbon mike and 2500 ohm ear phone with butterfly switch for "listen" and "talk". Has 6 ft. flexible rubber cord with 1 each PL55 and PL58 plugs attached. Attractive bakelite case, light weight.

Ideal for interphone outfits for home or industry, mobile and many other applications. Made to rigid Signal Corps spec.

A Truly Outstanding Surplus Bargain. Every One BRAND NEW.

No. 17A407, Special Each..... **\$3.95**



\$250 Value For 99c



CURVED NEEDLE NOSE

6" Crescent Tool Co. Drop forged "Crestaloy" steel, cadmium plated. Very handy for close quarters. At this price, every tool kit and bench should have one.

Compact Rechargeable STORAGE BATTERY



Willard .2 Volt in Spill-Proof Clear Plastic case. Only 2 3/4" square and 6" high—(about the size of the ordinary #6 dry cell) make it applicable for a wide range of uses where battery power is needed. Rated at 24 AH. Gangs nicely for other voltages in multiples of 2 volts.

Shipped dry. Uses standard battery electrolyte available everywhere. Every One Brand New. While They Last, **\$1.95**

No. 5A133, Special Each

The "Tops" in Headphones

At a Fraction of Original Cost

8000-ohm impedance, highly sensitive. Best quality Alnico magnets in molded black bakelite cases, concealed terminals. Headband fully adjustable, leather covered spring steel. 12" cord with PL54 plug attached at side out of way. Jack and rubber cord supplied to extend length to 5 1/2 ft.

Extremely lightweight, only 9 oz., with removable rubber ear cushions of comfortable design. Made to Air and Signal Corps specs. Brand New—a 13.50 Value.

Stk. No. 17A37, Special Per Pair **\$2.49**



**Did You
Get It?**

The New
B-A Catalog
No. 471



BURSTEIN-APPLEBEE
Company
1012-14 MCGEE STREET,
KANSAS CITY 6, MISSOURI

below the upper frequency limit of the station channel, as shown at the right of Fig. 2.

Since the video signal upper sideband to be transmitted is approximately 4 mc. wide (see Fig. 1), this leaves a guard channel approximately .5 mc. (500 kc.) wide between the upper limit of this sideband and the carrier of the associated sound signal (see Fig. 2) for prevention of audio interference with the associated video signal, and vice versa.³

It is apparent that with the television channel divided up as shown in Fig. 2, the amplitude-modulated video signal with all its sideband frequency components that are to be transmitted, the frequency-modulated audio signal with all its sidebands that are to be transmitted (deviation of ± 25 kc. defined as 100% modulation), and the necessary guard channels for prevention of self and adjacent-channel audio interference with the picture are all nicely confined within the 6-mc. transmission channel limit assigned to each television station. It will be observed that these standards set the frequency separation between the video and audio carriers of any one television transmitter at the definite, fixed value of 4.5 mc. For a very good reason that will be pointed out later in this discussion, the current postwar standards recommend that all television transmitters be operated with the video carrier frequency 4.5 mc. below that of the audio carrier, as illustrated in Fig. 2.

Before leaving this phase of the subject it will be interesting to examine Fig. 2 in order to determine what the use of vestigial sideband transmission for the video signal actually accomplishes in the matter of reducing the width of the transmission channel required for each television broadcast transmitter. If regular, full double-sideband transmission were employed for both the video and the sound signals, a channel $.25 + 4.5 + 4.5 = 9.25$ mc. wide would be required for each television transmitter in operation. By employing vestigial sideband transmission for the video signal, the station channel width is reduced to 6 mc. This represents a reduction of approximately 33 1/3%. This decrease in required station channel width makes it possible to operate that many more television broadcast transmitters in a given locality within the present assigned 44 mc. to 88 mc. television broadcast band.

Basic Elements of a Television Receiver

Television receivers are usually of the superheterodyne type, in order that all the important advantages inherent in this type of receiver may be

* It is not necessary to make the guard channel between the audio carrier and the video signal of the adjacent-channel transmitter of higher frequency as wide as this because the extreme portion of this transmitted adjacent-channel video signal which the audio channel adjoins is that which is not intended to be used by the television receiver tuned to receive its picture program. Consequently audio interference with it, if it occurs, does no harm. Accordingly, this guard channel is made only 0.25 mc. wide.

RADIO NEWS



Brand New Automatic Direction Finder

RADIO COMPASS

SCR-269F Complete with Component Parts Less Power Supply **\$75.00**

This equipment comes complete with 17-tube superheterodyne receiver which is tunable from 200-1750 KC in three bands. A complete instruction book for operation and maintenance accompanies this equipment.


BC 433G RECEIVER

Complete with tubes. **\$29.50**
used, in good condition.

Azimuth Control

49¢

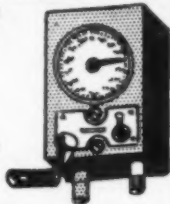Dial calibrated, 360° face, ideal for antenna rationalizing indicator.



T-17 CARBON MICROPHONE
89¢
Like new.

BC-654

Transmitter & Receiver

With tubes and xtals, used, in good condition. The frequency range of both transmitter and receiver is continuous from 3700 to 5800 KC; all stages gang tuned by anti-backlash worm gear dial mechanisms. **\$12.50**

PYRANOL CAPACITATOR



\$2.95

General Electric.
1 MFD.
5,000 VDC.

4" x 4 1/2" x 3 3/4".

DYNAMOTOR DA-3A

\$1.50

Input.
28 V.D.C.
10.5 AMPS
Output.
300 V.D.C.
260 AMPS
150 V.D.C.
.010 AMPS
14.5 V.D.C.
5 AMPS
Shipping Wt.
25 Lbs.

Butterfly Condensers

Oscillator assembly 76 to 300 MC with acorn tube socket mounted on condenser. **\$1.95**

Type B, frequency range 300 to 1000 megacycles. **95¢**

antenna condenser 105-330 MC. **\$1.95**


Oscillator 105-330 MC. **\$1.95**

TRANSMITTER TUNING UNIT BC-375

Approximately 65 MMFD cond., coils RF chokes, dials, assorted mica condensers, 2500 WVDC. Over \$50.00 parts! **\$1.95**

DYNAMOTOR UNIT PE-101-C

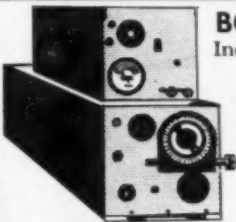Duo output Dynamotor, input voltage 12 to 24V., output voltage 400V. at 135 ma, 800V at 20 ma, and 9 V. at 1.1 amp. **\$2.95**



BC-AR230 Transmitter

Including 4 tubes and Rf Amps. meter.

BC-AL229 Receiver

Including 6 tubes. Used in aircraft.

BOTH UNITS ONLY \$9.95

Overload Relay

\$1.95



Patter and Brumfield. Relay 1, 5,000 ohms, coil current 10 MA., Relay No. 2, 110V, 60 Cy, AC coil, S.P.D.T.

POWER TRANS.

\$1.95 110V. 60 cy. Sec. 1: 4V at 16 Amps. Sec. 2: 2 1/2 V at 1.75 Amps. Ideal for 2x2 and 826 tubes. Hermetically sealed. size 6" x 3 1/2" x 4 1/4".

IF TRANS.

95¢

Mounted in aluminum shield can 1500 KC. with air trimmer. impedance coupled type.

Variable Resistor

2500 ohm. **49¢**
100 W.



FILAMENT TRANS FORMERS

Toggle Switch

39¢

D.P.D.T. 30 Amps, in black Bakelite case.

FM Radio and Transmitter BC-620-A, 20 MC - 27.9 MC

\$9.95

This Xtal controlled FM set has 13 tubes and has dual Xtal controlled channels. It also contains built-in Fil. and Plate Meter. Tubes used: (4) 1LN5, (1) 1LC6, (1) 1LH4, (2) 1291, (4) 1299, (1) 1294. Ideal for communication between Trucks, Boats, etc. Used, in good condition. Less power supply. Wt. 38 lbs. Complete with carrying case and diagrams.

30MC IF TRANSFORMER

29¢

Slugged Tune.


Condensers

Cap. MFD	Working Volt	Your Cost
1	1000 oil	44¢
8	600 oil	95¢
2	600 oil	49¢

Squirrel Cage Blower

\$7.50

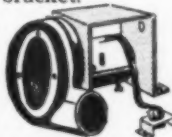2" outlet, 110 AC, 60cy Silent Ball Bearing Motor, with mounting bracket.



Sockets for acorn tubes.....	\$.19
Powdered iron 3/8 slug.....	.10
Jacks, PL55, PL68.....	.15
Asst. mica condensers.....	1.95
3 lbs. asst. hardware.....	1.00
Pin straightener for min. tubes....	.49
Ear phones, 2000 ohms, used.....	.95
Johnson sockets, No. 210, 25W....	.39

CORONA BALLS Dozen 10¢ Each

High-Speed Photo Flash Tube 10,000 Flashes

12,000,000 lumens light output. Stops all action. Ignition coil included on back of bulb. 10,000 flashes. Diagrams furnished. **\$8.95**



TUBES

813	5.95	872A	1.95
VR150	.69	9004	.49
955	.65	9006	.59
9002	.89	50B5	.89
RK60	.95	VT127A	
9001	.89		2.95
6J4	1.50	35W4	.69
5 FP7	1.95	3AP1	1.95
7BP7	2.95	3BP1	1.95
9LP7	3.95	6J5	.49
6N7	.89	5BP1	3.95
		6H6	.59
1T4	3Q5	6SN7	.59
3S4	5W4		
6SA7	1G5		
12H6			
6SN7			

44¢


WRITE FOR FREE BULLETIN!

Hershel Radio Co.

5249 GRAND RIVER • DETROIT 8, MICH.

20% DEPOSIT REQUIRED ON ALL ORDERS

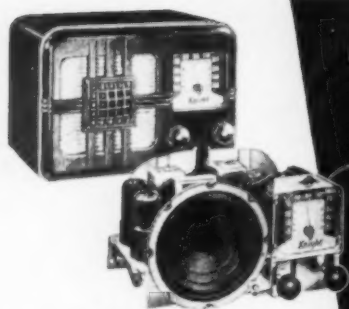All Orders **Minimum Order \$2.00** Michigan Customers Add 3% Sales Tax



Low-Cost Knight "Ranger" 5-Tube Kit Complete with Cab- inet, Loop Antenna and Tubes

It's here! The first ultra-modern 5-Tube AC-DC Superhet kit at so low a price! Here's what you get—full broadcast band coverage (550–1600 Kc.); built-in loop antenna; latest 5" PM dynamic speaker; handsome walnut plastic cabinet. Unbelievably easy to build; no special tools required. Sockets are riveted in place on chassis base; just assemble, wire and slip into cabinet. Outstanding for power and tone quality. Highest grade components only. Complete with all parts, tubes and full instructions. Nothing like it at the price! Shpg. wt. 10 lbs. **\$14.95**
No. 83-275. Complete, only.....


RADIO BUILDERS and EXPERIMENTERS!

ALLIED is Your Headquarters for Radio Kits!


ALLIED and the Radio Builder

The typical ALLIED-Knight Kits presented here are the result of over 20 years of experience in engineering efficient, easily-assembled kits. Every kit is proved for circuit design, good mechanical layout, and high quality components. **KNIGHT** Kits are easiest to assemble: complete instructions include both pictorial and schematic diagrams; panels are drilled, screenprinted and calibrated; chassis is formed and all holes are punched for you—no holes to drill; every last part required is included. When you buy a **KNIGHT** Kit, you get top design, top quality and top value.

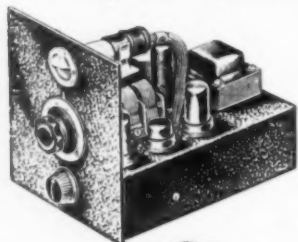High-Fidelity Kits for Radio Reception or Record Playing




TRF BROADCAST TUNER. An easy-to-build high-fidelity TRF Tuner Kit. Features broad band reception for higher fidelity than obtainable in standard superhet circuits. Linear diode detection for quality demodulation; separate diode AVC for constant signal. Cathode follower output circuit. "Magic Eye" tuning. Vernier dial, 0–100, 5–1 ratio. Built-in power supply. Complete with all quality parts, including 5 tubes plus rectifier, punched chassis (10 x 6½ x 3") and panel, matched coils and detailed 4-page instruction booklet. For 110–125 volt, 60 cycles AC. **\$24.25**
83-221. NET, only.....

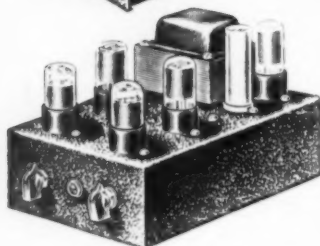

10-WATT HI-FI AMPLIFIER. One of the finest high-fidelity audio amplifiers ever designed for home construction—a perfect companion for tuner above, or for use with crystal phono pickup. Inverse feedback for wide response ± 1.5 db from 20 to 10,000 cps. Minimum distortion. High impedance input; volume and tone controls; large output transformer matches any 6–8 ohm PM speaker. Complete with all quality parts, including 4 tubes plus rectifier, punched chassis (10 x 6½ x 3"), and detailed 4-page instruction booklet with large, clear schematic and pictorial diagrams. **\$21.75**
83-222. NET, only.....

POPULAR 2-METER TRANSCEIVER. It's easy to build this powerful, compact 2-meter transceiver. Fine engineering brings unusually high output efficiency. Supplies current for single button carbon mike. Output transformer for any PM speaker or headphones. Requires 250 v. at 75 ma., and 6.3 v. at .65 amp. for power. Kit complete with all parts: punched and formed cadmium plated chassis, 5 x 9 x 2", clearly marked 6 x 9" steel front panel with black crackle finish, tubes, wire, solder, etc. Includes easy-to-follow instructions. Requires Amateur license to transmit. Kit complete, less mike, speaker and power supply. **\$18.25**
83-220. NET, only.....

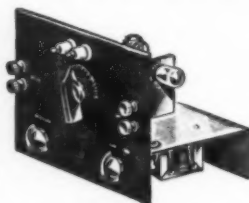

For Additional **KNIGHT** Kits, see ALLIED'S 164 Page **FREE Catalog!**

ALLIED RADIO

Everything in Radio
and Electronics

ALLIED RADIO CORP., Dept 1-M-7
833 W. Jackson Blvd., Chicago 7, Ill.

- ☐ Send Kit No. 83-275
- ☐ Send Kit No. 83-221
- ☐ Send Kit No. 83-222
- ☐ Send Kit No. 83-220
- ☐ Send FREE 164-Page ALLIED Catalog.

Name.....
Address.....
City..... Zone..... State.....



secured. They employ a number of basic functional units arranged in the sequence illustrated in the block diagram of Fig. 3.

Whether or not a tuned r.f. amplifier stage is employed ahead of the mixer as shown in Fig. 3 depends upon the price of the receiver, preferences of the designer, etc. There are several reasons for this. (1) At the very high frequencies (44 to 88 and 174 to 216 mc.) allocated to commercial television broadcasting the usefulness of an r.f. amplifier stage is not as great as it would be in a receiver designed for the very much lower AM broadcast frequencies of 535 to 1605 kc., since the gain and adjacent-channel selectivity contributed by a t.r.f. amplifier stage at these v.h.f. is comparatively small. (2) Image-frequency rejection is not as important a problem in present-day television receivers as it is in receivers designed for other services, because the standard i.f. values recommended for use in both the video and audio i.f. amplifiers throw all possible image frequencies well outside of the television bands and into the frequency channels employed by a comparatively few low-powered transmitters used for other services. (3) Because the television transmitting distances are short, and the signal voltages at the receiving antennas therefore are comparatively high, the gain that would be contributed by an r.f. amplifier stage is not of great importance. For these and several other reasons which need not be gone into here, most television receivers do not employ a separate tuned r.f. amplifier stage but couple the composite television signal received by the dipole receiving antenna to the input circuit of the mixer tube through a tuned r.f. coupling transformer. In such receivers, the tuned r.f. portion referred to is the coupling and tuning circuit between the antenna and the mixer grid.

Since the composite television signal (video plus audio) encompasses a frequency bandwidth of 6 mc. (see Fig. 2) the r.f. and mixer tuning circuits must be designed to have a band acceptance characteristic at least 6 mc. wide⁴ if both the video and sound signals are to be passed. Fig. 4A illustrates such a characteristic (ideal) that accepts all the desired frequencies uniformly, and that sharply attenuates the unwanted signals of adjacent transmitting channels. It is impossible to attain this ideal flat-topped, steep-sided characteristic in practice, so a compromise is necessary. By employing over-coupling be-

(Continued on page 173)

⁴ The smaller table-model television receivers which employ small diameter cathode-ray tubes having picture screen widths of the order of 5 or 7 inches do not require as sharp an image as is necessary when the larger C-R tubes are used. The sharpness of the reproduced image is a function of the bandwidth of the video signal applied to the picture tube. Consequently, since extremely fine picture detail is not necessary in such receivers, it is not necessary to reproduce the higher modulating frequencies of the video signal. Therefore the r.f. tuning circuits can be made more selective by employing a band-acceptance width of only 4 or 5 mc. instead of the full 6 mc. required for receivers that employ the larger C-R tubes.



Your enjoyment climbs to new altitudes through radio and television achievements of RCA Laboratories.

RCA LABORATORIES—your "magic carpet"

to new wonders of radio and television

More and more people will go sight-seeing by television as the number of stations and home receivers increases. Eventually, television networks will serve homes from coast to coast . . . bringing you the news as it happens . . . sports events . . . drama . . . vaudeville.

Many of the advances which have made possible these extended services of radio-electronics, in sound and sight, originated in research conducted by RCA Laboratories.

Recent RCA "firsts" include: ultra-sensitive television cameras that give startling clarity to all-electronic television . . . tiny tubes for compact, lightweight portable radios . . . "picture tube" screens for brilliant television reception.

In other fields of radio-electronics, RCA has pioneered major achievements—including the electron microscope. Research by RCA Laboratories goes into every product bearing the name RCA or RCA Victor.

PIONEERING

Scientists and research men who work in RCA Laboratories made many vital contributions in helping to win the war through application of radio, electronic, radar and television techniques. Their skills now are devoted to peacetime applications of these sciences.

At RCA Laboratories the electron microscope, radar, all-electronic television (featuring the projection system for the home) and many other new instruments of radio, including hundreds of new electron tubes, were developed to improve and to extend the services of radio around the world.



RADIO CORPORATION of AMERICA

It's
NEW!



Basic
\$59⁵⁰
Kit

ESPEY Television Training Kit

Learn television through this unique "assembly line" procedure. Modern circuits and postwar design make up-to-the-minute training an absolute necessity. This ESPEY television training kit, available in several fundamental stages, will help you understand and gain a working knowledge of TELEVISION—the latest development in electronics. FREE with every kit—a new type of pictorial instruction book, giving easy-to-follow, step by step method. No previous knowledge of television necessary to build—and LEARN from—this ESPEY kit.

FEATURES

- 18 tubes, including 15 miniatures.
- 3 stage, stagger tuned piz i.f.
- 21.25 Mc sound i.f. Trap tuned
- Balanced FM discriminator.
- Portable—weighs only 17 lbs.
- Uses 3" low-cost cathode ray tube. Magnifier makes 4" picture.
- Can be aligned with ordinary test oscillator and V.T. Voltmeter.

BASIC KIT—includes all i.f., power, blocking oscillator transformers, chokes, ceramic capacitors, speaker, and sockets riveted into place on punched and welded chassis. All tubes and required resistors and capacitors are easily-obtainable types available through Distributors everywhere.

FOR FURTHER DETAILS WRITE TODAY TO:

ESPEY MANUFACTURING COMPANY, INC.
528 EAST 72ND STREET-NEW YORK 21, N.Y.

Compact E.C.O.

(Continued from page 64)

If the oscillator is operating well, which it should if the coil data has been closely adhered to, the buffer may be tuned. Plug in the 6L6 and either the 3.5 or 7 mc. buffer plate coil. When the circuit is in tune, the neon bulb on the front panel will glow brightly. Next, remove the r.f. choke from the oscillator plate circuit and plug in the other oscillator plate coil and the 14 mc. buffer plate coil. Set the oscillator to 3600 kc. and tune the mica trimmer inside the oscillator plate coil for the brightest glow of the neon lamp. This adjustment will hold for the entire 14 and 28 mc. bands, since a large reserve of excitation is available.

The final amplifier is tuned for minimum plate current in the usual way. The unloaded plate current should be 10 to 20 ma. on the 3.5, 7, and 14 mc. bands, and about 40 ma. at 28 mc. The amplifier can be loaded to 100 ma. without trouble. Refer to the coil table for the proper coils to use for any particular band. The output link is suitable for coupling to a low impedance line, such as would feed a center-fed doublet, or to a separate antenna coupler.

The stability of the oscillator has been checked against a secondary frequency standard, and after a one hour warm-up period, did not drift more than 500 cycles. Jarring the cabinet heavily will "wobble" the frequency slightly, but the unit will always return to its original frequency. The unit was placed on an inexpensive sponge rubber kneeling pad, which fortunately, measured just 8" x 14". This made the v.f.o. insensitive to any but the severest shocks.

The rig was intended to drive a kilowatt amplifier, but the performance and versatility were so acceptable that no further experimentation was felt necessary.

The 807 may be plate and screen modulated very easily. About 25 watts of audio at 5000 ohms is necessary.

-30-



Check Pin Connections & Tube Data Instantly!

Two new and amazingly handy slide rules tell you at once the location and nature of pin connections, filament voltage, filament current, and uses for 176 radio tubes. Radio or electronic engineers, servicemen, students can't afford to be without these pocket-sized time-savers. SEND \$1.00 IN CASH OR MONEY ORDER TODAY and receive both prepaid by return mail. Your money back if not satisfied.

WRITE FOR QUANTITY PRICES

HARRY LANGSAM,
12 S. 12th Street, Phila. 7, Pa.
☐ I enclose \$1.00. Please send both Radio Tube Pin Data Rules.
☐ Send Quantity Prices.
Name _____
Address _____
City _____ State _____

Learn and Earn! TELEVISION

RADIO F. M. COMMUNICATION

offer profitable occupation for both men and women. You learn by actual work, how to build and operate, and fit yourself for a higher pay job. Write for catalog.

Approved for Veterans

HOLLYWOOD SOUND INSTITUTE

1040-A N. Kenmore

Los Angeles 27




"Look at Ray's new antennal
A doublet!"

NEVER!..NO, NEVER!

NOT IN ALL THE HISTORY OF RADIO, AN OFFER LIKE THIS!

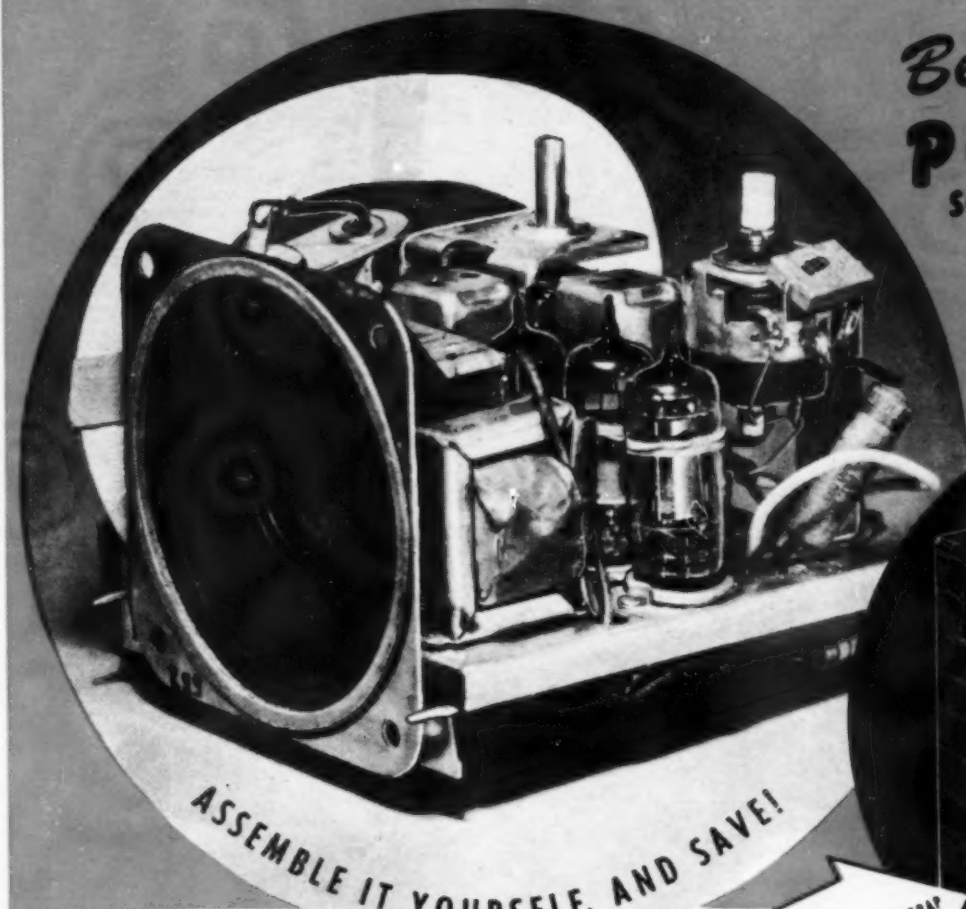Belltone PORTABLE Self-powered Battery Radio KIT



ASSEMBLE IT YOURSELF, AND SAVE!



BELLTONE GIVES YOU PLENTY OF
SIMPLIFIED DIAGRAMS AND INSTRUCTIONS!

You get the Case, Knobs, Antenna, Tubes
EVERYTHING!...

(EXCEPT WIRE, SOLDER, BATTERIES)*
1 Set of Batteries at only \$2.55

We urge you to bear in mind that this is NOT, definitely NOT, an ordinary portable, but a tiny, wonderful, beautiful, powerful set—which you can easily build yourself—quickly. Wait till you see the attractive case, covered in simulated leather, with adjustable shoulder strap. You'll want several. Use them as gifts.

INCLUDED
THIS BEAUTIFUL, SHOULDER-STRAP
CARRYING CASE WITH POLISHED
BRASS FITTINGS.

IT'S TINY
6 1/2" HIGH BY 4 1/2" WIDE
BY 4 1/2" DEEP. THAT'S ALL!

HERE'S WHY THE SET IS SO
EXTRAORDINARY AT THE PRICE!

It has a 3 1/2" ALNICO V PM speaker. Uses standard, easy-to-get, long-lasting batteries—easy to change. It plays with the lid open or closed. Has 4 tubes. Weighs 3 1/2" lbs. (approx.) when complete and operating, case and all!

only
\$14⁹⁵—

WE PAY THE
POSTAGE ANYWHERE
IN THE U.S.A.

USE THIS ORDER COUPON
NOW! START BUILDING
YOUR SET RIGHT AWAY!

BELLTONE RADIO & TELEVISION CORP. DEPT. P
583 Ave. of Americas New York 11, N. Y.

Sirs: Send me _____ portable kits for which I am
enclosing ☐ MONEY ORDER ☐ CHECK for \$ _____
☐ Battery Kit @ \$2.55

SEND TO _____


ADDRESS _____

CITY _____ STATE _____

BELLTONE RADIO AND TELEVISION CORP.
583 AVE. OF AMERICAS, NEW YORK 11, N. Y.

BUILD THIS 8-TUBE RADIO-AMPLIFIER • COMPLETE KIT—ONLY \$29⁹⁵

DELUXE CONSOLE CABINET \$39⁹⁵

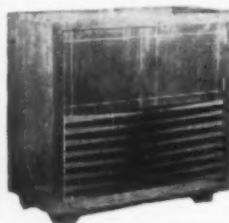


- SLIDE AWAY CHANGER COMP.
- RECORD ALBUM COMPARTMENT
- BEAUTIFUL, ALL WALNUT CONSTRUCTION

This is the first time we have been able to offer a beautiful floor model console, RADIO-PHONO cabinet. Finest all walnut construction; hand rubbed finish, 34" long, 33" high, 16" deep. Holds 12" speaker, large record compartment. Slide away changer compartment will accommodate changer of the Webster 56 class and smaller. Receiver compartment is 15x14x7 1/2 inches. Will accommodate our Model PRK-10 kit; advertised here. Dealers, here is your chance to buy good cabinets at the right price. Convert those low-priced sets into radio-phono combinations. Weight 50 lbs. Net, \$39.95.

Price with Two Post Oak Changer.....\$56.95
IF DESIRED, WE CAN FURNISH THIS IN BLOOMINGDALE AT \$10.00 EXTRA.

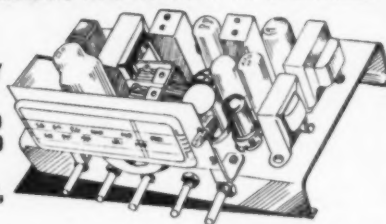- A COMBINED BROADCAST SUPERHET RADIO CHASSIS AND 15 WATT P. A. SYSTEM
- HEAVY DUTY 12" P.M. SPEAKER
- CROW 8" SLIDE RULE DIAL. 2 GANG COND.
- REG. BROAD. 550 TO 1700 KC. HI-FIDELITY PUSH PULL 6V6—TWIN TONE CONTROLS
- INPUTS FOR CRYSTAL OR DYN. MIKES AND PHONO-PICKUP. WE FURNISH EVERYTHING TO BUILD THIS DELUXE CHASSIS
- WHY NOT ORDER THE CONSOLE ON THE LEFT, WITH YOUR PRK-10




Here is something new in radio. A real 15 watt power amplifier with bass and treble controls. Has extra gain stage for crystal or dynamic mikes. And on the same chassis, a standard superhet radio receiver. We furnish all parts, knobs, escutcheon plate and tubes: 6SA7, 6SK7, 6SR7, 6SN7, 6SJ7, two 6V6 and 5Y3. No cabinet. Extra care in designing the power supply section assures low hum level, making this unit ideal for recording as well as P.A. use. We furnish everything as well as schematic diagram and photos of the completed chassis. Weight 35 lbs.

PRK-10 Radio-Amp. Kit with 12" P.M. speaker. With tubes....Net \$29⁹⁵

PRK-10X Radio-Amp. Kit with tubes and \$30.00 value 15" Cinnaudagraph speaker.....Net \$42⁹⁵

PERSONAL PORTABLE KIT, \$10.95

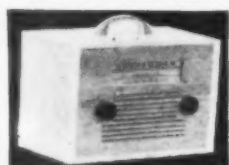


- 4-Tube Broadcast Superhet
- Priced Complete with Batteries
- Dynamic Speaker • Slide Rule Dial

PERSONAL PORTABLE KIT MODEL K-PX. Small size leatherette covered case 9x5 1/2x5. Easy to build. Operates on self contained B and A batteries. Rec. Broadcast 550 to 1600 K.C. Incorporates a standard superhet circuit with avc. Has 3 inch Alnico five PM speaker. Priced complete with batteries, working AC DC receiver kit. Diagram, photos and tubes included. Has 2 gang cond. Everyone should have one of these personal portables. Everything furnished. Kit K-PX.....Net \$10.95

Diagram and tubes 1R5, 1R5, 1T4 and 384. Not AC DC, but straight battery operated. Has 2 gang cond. Everyone should have one of these personal portables. Everything furnished. Kit K-PX.....Net \$10.95

3-WAY PORTABLE KIT, \$17.95

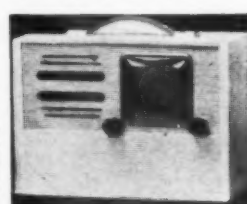- 4 Tubes Plus Disc Rectifier
- 300 Hour Battery Pack Included
- Beautifully Built Portable Case



Build this powerful, 4-tube, 3-way portable kit. Operates on 110 volts AC or DC or self contained batteries. Receives broadcast 550 to 1650 K.C. Incorporates a standard superhet circuit with AVC and loop Ant. Has Alnico 5 PM Speaker, 2 gang condenser. All Parts and batteries are furnished including tubes Disc Rectifier, 1R5, 1T4, 1R5 and 384. Has attractive leatherette portable cabinet size 7x9x9. Weight 14 lbs. Kit Model 3-ZA. Net \$17.95

5-Tube AC-DC Broadcast Kit, \$9.95

BEAUTIFUL 10" PLASTIC CABINET
LOOP AERIAL • VERNIER DIAL
DYNAMIC SPEAKER • EASY TO BUILD



Kit Model P-85. We have finally been able to achieve our goal. Here it is. A good 5-tube broadcast AC DC superhet radio receiver for less than ten dollars. The beautiful 10 inch plastic cabinet is made of the finest material. The chassis is of the standard accepted superhet design. 456 KC. AVC and 5 inch Alnico 5 PM speaker. Attractive vernier dial. Two gang tuning condenser. Loop ant. We defy anyone to offer a better working AC DC receiver kit. Priced complete with diagram, photos and tubes including 12BE6, 12BA6, 12AT6, 50B5 and 35W4. Nothing else to buy. You can't go wrong on this value. Kit Model P-85.....Net \$9.95
SUPERHET. 4-Tube, 1 1/2-90 Volt FARM RADIO KIT complete, less 1000-hour battery; similar cab. to Model P-85. Model PB-48.....Net \$9.95

12-WATT AMPLIFIER KIT, \$10.95



PUSH PULL 6V6 OUTPUT TUBES
GAIN FOR MIKE AND PICK-UP
EVERYTHING FURNISHED. EASY TO WIRE
FINE TONE QUALITY

KIT MODEL AC-12. 12 watt amplifier kit. Ideal for high quality record player as well as public address or recording amplifier. Matched component parts, ready punched chassis pan. One control fades from phono to microphone. Gain enough for crystal or dynamic microphone, 100 mil power transformer, for 110 volt AC 60 cycle operation. Priced complete with tubes: 2-6V6, 6SN7, 6SH7 and rectifier. Diagrams and photos furnished. Kit AC-12. Net \$10.95. 12" Alnico 5 PM speaker \$6.95 extra; crystal microphone and desk stand \$4.95 extra.

RECORD PLAYER \$9.95

POWERFUL SINGLE RECORD PLAYER KIT Z-26. Housed in an attractive leatherette covered cabinet. Latest 78 RPM rim drive motor and light weight pick-up. Ready wired and tested 70L7 type tube amplifier. Tone and volume control, 5" PM speaker (Alnico V). This kit easily slips together. Priced complete with tubes and hook-up instructions. Kit Z-26.....Net \$9.95



PORTABLE RECORD PLAYER KITS




KIT MODEL J-41. Our leader record player kit. Fine tone, low needle scratch; includes two-tone leatherette covered portable case, rim-drive photo motor, high output crystal pick-up and 6" Alnico 5 PM speaker. 70L7 ready wired and tested amplifier. No wiring to do, just mount the parts in the case. Has the tone and volume controls. Net \$14.95

Kit Model J-41.....Net \$14.95
KIT MODEL J-42. Has a beautiful alligator covered portable case (similar in appearance to the J-41), Alnico 5 PM speaker and ready wired and tested push-pull 117L7 amplifier. This player is powerful with good tone and low needle scratch. Separate tone and volume controls. Slips together in only a few minutes. Has single post automatic record changer; plays 10 1/2" or 12 1/2" records, automatically. Net \$29.95

Kit Model J-42.....Net \$29.95
KIT MODEL J-43. Includes two-tone leatherette case (similar in appearance to the J-41), spring-wound photo motor, 6" Alnico 5 PM speaker and ready wired and tested push-pull 384 amplifier. High output crystal pick-up. Priced complete with batteries; operates on self-contained batteries, requires no external power. Kit Model J-43.....Net \$15.95

RADIO-PHONO COMB. KIT, \$24.95

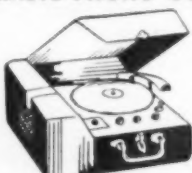

1650 K.C. has tone control, loop antenna, 6" Alnico 5 PM speaker. Tubes 12SA7, 12SK7, 12SQ7, 50L6 and 35Z5. Simple diagram furnished. Kit Model R-12. Wt. 20 lbs.Your Cost \$24.95

PORTABLE RADIO RECORDER KIT \$54.95

\$50.00 value for only \$54.95. We furnish every part to build a powerful radio and dual speed recorder. The attractive leatherette case houses the sensitive superhet broadcast radio and General Industries R90L 33 1/2 and 78 RPM dual speed recorder; play back mechanism. The 6 tube receiver and amplifier is all on one chassis: 12SA7, 12SQ7, 12SK7, 12SL7, 50L6 and 35Z5. 35L6 push-pull output; plus disc rectifier. Has plenty of gain for crystal or dynamic mikes. Has 6" heavy duty PM speaker and tone control. Kit G-31, everything complete, with tubes and diagram. \$54.95. Crystal mike and desk stand \$4.95 extra. This is without a doubt one of the best values in kits we have ever offered. Wt. 40 lbs.



15 IN. SPEAKER, \$9.95

Juke Box speaker scoop of the year. Made by cinnaudagraph. Reg. Dealers net \$39.00. Has 12,000 ohm field easily excited in bleeder circuit. 15 ohm voice coil.....\$9.95

20-WATT UTILITY AMP. KIT, \$17.95

Build this 20 watt utility 110 volt AC, 20 Watt power amplifier. Ready punched aluminum chassis, size 12 x 6 x 2 1/2 inches. Has two input circuits, one mike and one phono. Mike stage has 135 DB gain, for crystal or dynamic mike. Has bass and treble controls. Designed for use with PM speakers; has 8-16 ohm output transformer. All parts, controls, transformers and easy-to-follow diagram furnished, including tubes: 2-6SN7, 6J5, 2-6L6GA, 5Z5. Kit Model 20-LX. Net.....\$17.95




6-110 VOLT UTILITY AMP. KIT, \$29.95

Model 20-LX6 20 watts output. Similar in appearance to the model 20-LX except on slightly larger chassis. Has same tube line up and input circuits. Has power supply that will work on 6 Volt DC, or 110 Volts AC. Equipped with super heavy duty vibrator. Has output voltage to run a reg. AC phono motor when used as a 6 volt unit. All parts tubes and easy to follow diagram furnished. Net \$29.95. Ship. weight 30 lbs. Latest 12 in. P.M. Alnico, V speaker, 12 watt. Net.....\$6.95
Crystal mike and desk stand.....7.95

Combo-Radio-Phono WL3-R

Offered with walnut cabinet with hinged lid. Latest rim drive phono motor, crystal pick-up and complete kit of parts to build a conventional five-tube AC-DC superhet with loop and condenser gang. Receives broadcast 55- to 1650 KC. We furnish everything including tubes: 12BE6, 12BA6, 12BE6, 12AT6, 50B5, 35W4, WL3-R.....Net \$19.95
WL-3. Same as WL3-R except is record player only. No radio. Has wired and tested amplifier and speaker. Slips together in a few minutes. WL-3.....Net \$14.95

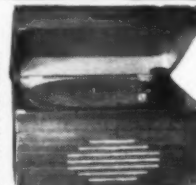

McGEE RADIO COMPANY

WRITE FOR CATALOG SEND 25% DEPOSIT—BALANCE C.O.D.
1225 McGEE ST., KANSAS CITY, MISSOURI

HOT SPECIALS IN P.M. SPEAKERS

12" P.M. 7 oz of A.V.
18 watt only.....\$6.95
All are guaranteed.

12" 5 oz. Alnico 5 P.m. Speaker.....12 watt Net \$3.95
10" 5 oz. Alnico 5 P.m. Speaker.....10 watt Net 4.95
8" 3.15 oz. Alnico 5 P.m. Speaker.....8 watt Net 3.49
8" 2.15 oz. Alnico 5 P.m. Speaker.....6 watt Net 2.95
6" 2.15 oz. Alnico 5 P.m. Speaker.....6 watt Net 1.95
RED HOT SPECIAL—6" 5 oz. Alnico 3 Square P.m. Speaker \$1.49; 10 for.....\$13.50

GENERAL ELECTRIC 5 1/2" P.M. \$1.95
5 1/2" G-E 1.5 oz. Alnico 5 P.m. Speaker with output transformer for 50L6 \$1.95 (mount for either 6 or 6 1/2" speaker.) Scoop price \$1.95; 10 for.....\$17.50

CHOICE OF 3 1/2", 4" or 5" P.M. \$0.99
3 1/2", 4" or 5" P.m. Speaker with 1 oz. Alnico 5 magnet. Your choice \$0.99 each. Order all you need. May never again be sold at this price. All brand new and guaranteed perfect. Choice of 3 1/2", 4" or 5" 1 oz. Alnico 5 P.m. Speaker. Scoop Price.....99c each

DYNAMIC SPEAKERS

6 1/2" 1000 ohm Field Speaker.....\$2.49
5" 3000 ohm Field Speaker.....1.89
5" 1000 ohm Field Speaker.....1.89
5" 450 ohm Field Speaker.....1.89
4" 450 ohm Field Speaker.....1.89
4x6" 450 ohm Field Speaker.....1.89

LAST MINUTE SPECIALS

Solar Genuine Tubular electric cond. All are fresh stock, just received from Solar. Guaranteed one year.
30 MFD. 450 volt tub.....Each 49c
15 MFD. 450 volt tub.....Each 42c
10 MFD. 450 volt tub.....Each 39c
10% discount on orders of 50 Solar tub. or more.
Thordarson power transformer scoop T 70R62 or T 44915 for 60 cycle 115 AC. 700 volts C.T. at 145 mliis. 6.3 v. 4.amps. and 5 v. 3amps. Scoop price \$3.49
Spring wound phono motor with all hardware turntable crank etc. reg. \$6.50 value.....\$3.98
Thordarson filter choke. 200 mill. 10 henry; fully shielded. Most beautifully made choke you ever saw. Weight 5 pounds. Scoop price \$1.99. 5 for \$3.50
R-32 Victor etc., replacement power transformer. Made by Utah. Upright mounting. Has all windings 1 1/2, 2 1/2, 5 etc.....Net 4.95
100 assorted 1/2 4 1/2" side carbon resistors; non-insulated type.....Net 1.10
G-E Plastic AC cord; with molded cap 6 1/2 foot 8 foot.....19c
Utah VPR-1 50 mill. strap mounting choke; 30 henrys. This is the standard size as used by 4, 5 and 6 tube radios.....Net Price .49
Auto serial closeouts
4 section. Top Cowl less lead.....\$0.69
3 sect. 6A side cowl, 30" lead.....1.79
4 sect. 90" side cowl, 30" lead.....2.79
72" ICA Uni-mount with lead.....1.79

MALLORY Standard size 4 prong vib. Has 8 points yet is a non-spring. For those heavy drain auto sets. Scoop Price \$1.99 each; 10 for.....\$19.90
DELCO off set 4 prong vib. net \$1.49; 100 mill. 6.3 volt flush mounting power trans. \$2.49; 55 mill. upright 6.3 power trans. net \$2.49; Astatic pickup arm with L40 crystal, made for automatic changers and does not have mounting sleeve, net \$1.29; 10 for.....\$12.90

1948 MODEL—MIKE-BROADCASTER ONLY \$7.95

Broadcasts 800 to 1500 KC from either a phonograph pick-up or a crystal or dynamic mike. Makes any radio receiver a P.A. system, record player or recording amplifier. Gives broadcast quality. Has fader control from mike to record, simulating a regular broadcast station. This is a powerful model; using 2-35L6, 12SJ7 and 35Z5 tubes. Priced with tubes and connecting instructions. Works on 110 volts AC-DC. Crystal mike and desk stand \$4.95 extra. Model DE-5 truly a de-luxe mike-phonoscillator.

MIKE-OSCILLATOR 800 to 1500 KC

Mike Oscillator model C-4. Not only does the unit work as a phono-osc., but has added gain stage for a crystal mike. Priced complete, wired and tested with 3 tubes and fader control. Net \$4.95. Crystal Mike.....\$4.90 extra

3-TUBE PHONO. OSC. ONLY \$3.95

Model DE-4—Phonograph oscillator. Broadcasts from 800 to 1500 KC. Gain for any crystal pick up. A new powerful circuit is used to assure plenty of power. Has variable gain control for proper modulation. Priced with tubes ready to operate, two 50B5 and 34W4. Model DE-4 Net.....\$3.95

ELECTRIC DRILLS \$19.50 UP

Finest type of construction. Jacobs Chucks. For 110 volt AC operation.
1/4 in. 3000 RPM.....\$19.50
1/4 in. 800 RPM.....27.00
1/2 in. 400 RPM.....29.50

SUPERHET BROADCAST TUNER for connection to phono amp. or P.A. system.

Compact chassis 5x3 1/2x3 inches. May be mounted inside the record player cabinet. Requires only three connections to amplifier. Uses 6SA7 or 12SA7, 6SK7 or 12SK7 and crystal diode. Complete with tubes, loop antenna, dial and instructions for connecting to any amplifier. Net \$7.95. Specify if tuner is to be used with AC or AC-DC type amplifier.



CATHODE RAY TUBES BRAND NEW

3BP1.....Net \$2.95
3AP1.....Net 2.95
5CP1.....Net 3.95
5BP1.....Net 3.95
5FP1.....Net 3.95
7BP1.....Net 4.95
9LP1.....Net 4.95

75% of All the Tubes You Use at 49c Ea.
Guaranteed Standard Brands. Cartoned and Uncartoned

1B4	6SA7	1216	25L6GT	78
1B5	6SC7	12J5GT	25Z6GT	80
1B5	6SD7GT	12SA7	26	11A
1T4	6SF5	12SG7	27	50L6
3Q4	6SF7	12SH7	35L6GT	50L6
381	6SG7	12SJ7	35W4	12A6
514G	6SH7	12SK7	35Z3	14B6
5Y3GT	6SK7	18L7GT	35Z4GT	70L7
6AC7	6SK7	12SN7GT	35Z5GT	117L7
1852	6SL7GT	12SQ7GT	39/44	
6C5	6SN7GT	12SR7	41	
6C6	6SQ7GT	14A7	42	
6D6	6SR7	12B7	43	
6F6GT	6V6GT	14B6	45	
6H6	6X5GT	14C7	50B5	
6A5	12A7	14H7	55	
6K6GT	12BA6	14Q7	76	
6K7	12BE6	14R7	76	
6L7	12C5	14S7	77	

49c

69c

99c

12" 20 Oz. 20 Watt PM.....\$4.98
10" 20 Oz. 20 Watt PM.....4.45
8" 20 Oz. 15 Watt PM.....3.95
All are latest Alnico 3 PM with smooth working cones. Guaranteed.
10% Discount on orders of 10 speakers or more.

SPECIALS IN TUBULAR CONDENSERS

Cornell Dubilier .05 Mfd. 600 volt condenser. Scoop Price \$0.09 each. 100 for.....\$7.50
Solar Sealites .05 Mfd. 400 volt condensers or .01 400 volt \$0.07 each. 100 for.....\$5.00

600 VOLT TUBULARS, MANUFACTURERS TYPE

Guaranteed all good brands condensers: .001, .005, .01, .02, .05, all 600 volt. Any size \$0.08 each. 100 assorted for.....\$6.50


POPULAR F.P. ELECTROLYTICS

In Alum. Cans. Easy Twist. Mounting all small size.
10 x 10 x 10 Mfd. \$0.49
450 volt.....\$0.49
30 Mfd. 450 volt......49
20 Mfd. 450 volt......39
20 Mfd. 200 volt......10
Mfd 330 volt......20
Mfd. 25 volt......39
30 x 40 Mfd. 400 volt.....\$0.49
40 x 40 Mfd. 250......39
40 x 20 Mfd. 150......39
volt 20 Mfd. 25 volt......39

TUBULAR ELECTROLYTICS

In paper tubes with pig tail leads
Cornell-Dubilier, 8 Mfd. 450 volt \$0.39 each. 100 for.....\$32.50
Cornell-Dubilier, 10 Mfd. 450.....\$0.59 each. 5.25
Aerovox, 8 x 8 Mfd. 450 volt. \$0.49 each. 10 for 4.90
Aerovox 20 x 20 Mfd. 150 volt. \$0.39 each. 3.50
Sprague, 50 x 30 Mfd. 150 volt. \$0.49 each. 4.25
Solar 50 x 30 Mfd. 20 Mfd. 25 volt \$0.59 each. 4.90
10 for.....4.90

G.I. RECORDER MECHANISMS

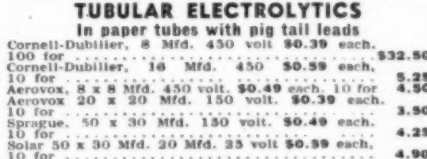

Latest 1947 General Industries recording assemblies with 4 ohm magnetic cutters and crystal play back.
Model R70-L-78 RPM. Net.....\$24.50
Model R90-33 and 78 RPM. Net.....28.95
Model R130-L—Automatic changer with cutter, 78 RPM. Net.....40.10

RADIO TUBE SCOOP OF THE YEAR

39c each—100 assorted for \$35.00

12SA7GT	6K7GT	6SA7GT	12AT6	11A
12SQ7GT	6A8GT	6SD7GT	12BE6	1T4
12SK7GT	6V6GT	6SQ7GT	12BA6	384
35L6	6K6GT	6SK7GT	35W4	3Q4
50L6	5Y3GT	25L6GT	50B5	1R5
35Z5	6Q7GT	70L7GT	35B5	185
		117L7GT	117Z3	6SN7GT
			6X5GT	

These tubes are boxed and branded HYVAC. All are guaranteed best quality, full replacement.

REGAL AC-DC AND BATTERY \$22.95 PERSONAL RADIO

"HOTTEST PICK ME UP RADIO IN AMERICA"

NO TALLER THAN A PEN

NET EACH \$22.95

IN LOTS OF 3 \$21.95

Regal Model 747—3 way personal radio. Receives broadcast 550 to 1650 KC. Small size only 4x5x8 inches. However, uses full size parts with 2-gang condenser and loop. Priced complete with 4 miniature tubes and disc rectifier. These sets are only slightly larger than the smallest personal radio. Volume and tone like a big set. Kit of batteries \$2.05 extra.



Automatic Record Player

Includes Maguire two post automatic record changer. Wired and tested two tube 117L7 amplifier. Tone and Volume controls. Alnico V. PM speaker. Only a few minutes required to mount changer and amp. A Real value.
Model J-74..Net \$22.95



MECK PEE WEE SUPER \$11.95

Meck. 5 tube superhet; using miniature tubes. Small plastic cabinet (7x4x5"), 2 gang condenser, loop antenna, Alnico 5 PM speaker. This is a red hot value in a small radio receiver; broadcast 550 to 1650 KC. Priced with tubes; ready to play.

Model 800B, Black plastic cabinet.....\$11.95
Lots of 3.....\$10.95
Model 800W, White plastic cabinet.....\$12.95
Lots of 3.....\$11.95
Weight 5 lbs.

MECK FM CONVERTER \$14.95

It's sensational. Makes any regular AM (ordinary radio) radio receive FM Signals (88 to 108 Mc.). Just announced by John Meck Industries. Order your sample today. Dealers Net \$15.95. Same cabinet as Pee Wee shown above.
Lots of three.....\$14.95

1948 MODELS OF KARADIOS

"For Your Car"
Karadio Model 80-A—The greatest radio ever offered to the ham; covers broadcast 80, 40, 20 and 10 meter bands. Here is your chance to get a communications type car radio easy to mount under dash. Has R.F. stage; separate FM speaker. Designed for 6 volts D.C. input. Band 1—530 to 1700 KC; Band 2—3 to 1.3 MC; Band 3—14 to 30 MC. Net Price.....\$79.50

Karadio Model 80-B (airport model). Similar in appearance to model 80-A; except covers different frequency. Band 1—150 to 450 KC; Band 2—535 to 1700 KC; Band 3—2.4 to 6.9 MC. Input six volts D.C. Net.....\$62.50

Karadio Model 1200—A fine broadcast (535 to 1700 KC) car radio. Compact size makes for easy installation (5 1/2x2 1/2x3 inches). Input six volts D.C. Has tuned R.F. stage; separate 6" PM speaker and conventional high gain superhet circuit. Similar in appearance to Model 80; shown above.
Net Price.....\$38.95

WIRE RECORDER—RADIO—P.A.

ALL IN ONE PORTABLE CASE

McGEE'S 1948

ADD-A-UNIT

10" P.M. SPEAKER


3 NEW MODELS

ADD-A-UNIT PORTABLE PA SYSTEM RECORDER-RADIO. This unit is offered as a slip-together kit. All components need only be mounted together to make a high quality sound system, Radio-Disc or Wire Recorder. The broadcast radio tuner may be added to any model. The portable case is leatherette covered and snaps together for easy carrying. The 12 watt AC amplifier (Model AC-12W) is wired and tested ready to play. Priced complete with tubes; 2-6V6, 6SN7, 6SK7, and 7Y4. Has tone control and fader control, gain for either dynamic or crystal mike. Has heavy duty 10" PM speaker. This amplifier is ideal for a public address system and record player; or for recording.

Model SK-1 PA SYSTEM, RECORD PLAYER: Includes portable case, wired and tested 12 watt amplifier (Model AC-12W), 10" PM speaker and latest single post record changer. Model SK-1 Net \$45.95; Crystal Mike \$4.95; Broadcast Radio Tuner.....\$7.95

Model SK-2 PA SYSTEM AND DISC RECORDER: Includes portable case, 12 watt amplifier (Model AC-12W), 10" PM speaker and General Industries R-90-L dual speed recorder and play-back mechanism. Model SK-2 Net \$54.50; Crystal Mike \$4.95; Broadcast Radio Tuner.....\$7.95

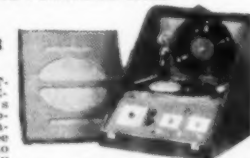Model SK-3 PA SYSTEM AND WIRE RECORDER: Includes portable case and 12 watt amplifier (Model AC-12W), 10" PM speaker and Webster Model 79 wire recorder mechanism with 15 minute speed of recording wire. This is the last word in public address and recording machines. Model SK-3 Net \$79.50; Crystal Mike \$4.95; Broadcast Radio Tuner.....\$7.95



McGEE RADIO COMPANY


WRITE FOR CATALOG

SEND 25% DEPOSIT—BALANCE C.O.D. 1225 McGEE ST., KANSAS CITY, MISSOURI


ORDER YOUR AIRCRAFT COMMAND RECEIVERS FROM McGEE

BRAND NEW BC-453, 200 TO 500 K.C., WITH TUBES.....	\$6.95
BRAND NEW BC-454, 3 TO 6 M.C., WITH TUBES.....	\$4.95
NEAR NEW BC-454, 3 TO 6 M.C., WITH TUBES.....	\$3.95
BRAND NEW BC-455, 6 TO 9 M.C., WITH TUBES.....	\$4.95
NEAR NEW BC-455, 6 TO 9 M.C., WITH TUBES.....	\$3.95
BRAND NEW BC-946 (broadcast), 550 TO 1500 K.C., WITH TUBES & INST.....	\$12.95

These command receivers have proven to be one of the best values in war surplus. We continue to get repeat orders. Hams and experimenters buy them to convert to other frequencies and for use as they are made. Designed for 28 volts DC input and easily converted to AC-DC operation, etc. For your convenience, we will include with each receiver a diagram of the BC 454. As all of command receivers are similar, this will assist you in becoming familiar with them. Weight 8 lbs. Priced with tubes, three 12SK7, 12SR7, 12K8, 12K6.

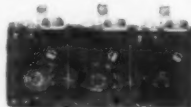

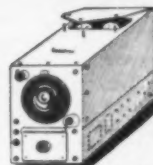28 Volt Dynamotor for 453, etc..... \$0.95
Triple remote control head for SCR-274 (BC-453, BC-454, BC-455)..... \$1.95
Flexible cable for tuning SCR-274..... .79
Mounting Rack for three receivers..... 1.95



SUPER VALUES IN AIRCRAFT COMMAND TRANSMITTERS!

NEAR NEW BC-696, 3 TO 4 M.C., WITH TUBES.....	\$3.95
BRAND NEW BC-457, 4 TO 5.3 M.C., WITH TUBES.....	\$5.95
NEAR NEW BC-457, 4 TO 5.3 M.C., WITH TUBES.....	\$3.95
BRAND NEW BC-458, 5 TO 7 M.C., WITH TUBES.....	\$5.95
NEAR NEW BC-458, 5 TO 7 M.C., WITH TUBES.....	\$3.95
BRAND NEW BC-459, 7 TO 9.1 M.C., WITH TUBES.....	\$5.95

This really fits the ham's dream. Ideal for a 55 watt transmitter with 575 volts at 250 MA plate supply, or VFO to drive a high power rig. It's a companion unit to the 454-455-453 series aircraft receivers. Made by Western Electric and really rugged. The oscillator will hold the frequency, even under rough operating conditions. Has

12J5 M. O. and 2-1625 (807) in parallel as final P. A.; or buffer to feed into a high power rig. Built-in crystal dial calibration checker. Antenna loading inductance. Priced with tubes and crystal. For your convenience a diagram of the BC-457 will be sent you. All of the command transmitters are essentially the same hook-up.



ORDER YOURS WHILE THEY ARE STILL AVAILABLE



G.E. SERVO-AMP. SALVAGE


\$1.95 EACH
Two for \$3.50

G.E. Servo amp Salvage Scoop. This item is ideal to tear up for the pieces, General Electric Servo amplifier, has 14 octal tube sockets, 5 small neon lamps. Lots of condensers, resistors and controls. Salvage value more than the purchase price of this unit. Weight 15 lbs. Brand new. Priced less tubes \$1.95; 2 for.....\$3.50

NAVY ARB RECEIVER, \$19.95

195 K.C. THRU 9 M.C.
INCLUDES BROADCAST BAND

You can convert this over easily to a good ham receiver. It's one of the hottest values in surplus receivers. 28 volts DC input. Covers 4 bands. 195 kc to 9 mc. This is a deluxe type superhet receiver; note that the frequency coverage includes the standard broadcast band. Has 4 gang tuning condenser; can be converted to a 110 volt AC receiver. Priced complete with tubes: 12SF7, 12SA7, 3-12SF7 and 12A6. Has dial built on front of chassis. Electric driven or manual band change switch. Weight 28 lbs. Size 6x7x15 inches. ARB Near new condition, with tubes and dynamotor. Net.....\$19.95


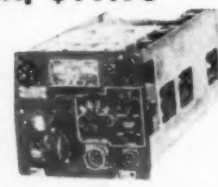


ARMY PARTS SALVAGE

\$249 TWO FOR \$449

28 VOLT DYNAMOTOR, \$1.99 EXTRA

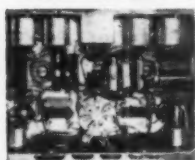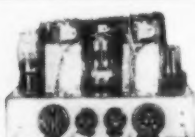Another red hot value in salvage. All kinds of good useable parts in this unit. Con. Res. Relays, Modulation trans. and tubes VR150, 12J5 and 1625. Brand new and in factory carton. Originally designed to modulate the BC 457 W.E. Transmitter. You can find many uses for this. BC-456 Modulator scoop, price.....\$2.49




BOTTOM VIEW

3" CATHODE RAY SCOPE, \$14.95

BC-929 A Radar Indicator Scoop. This unit could be rebuilt into a fine test scope. It is an ideal size. 8x9x14 priced with tubes 2-6SN7, 2-6H6, 6G5, 6X5 and 2X2. This is a red hot buy. However you will have to change the power trans. for 60 cycle use. Guaranteed to be in good condition. Scoop Price.....\$14.95

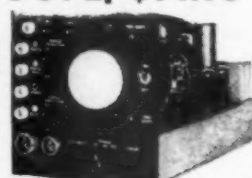Weight 20 lbs. Has 3 in. Cr Tube. We have a few BC-929 Radar Scoops. Brand new in factory cartons at \$19.95 each.



10 TUBES FOR \$2.79

5-6V6GT and 5-6SN7GT
—All are J.A.N. Guaranteed Perfect.

R-89 \$6.95



R-89/ARN-5 Glide Path Receiver 11 tube superhet. Formerly used for blind landing. Adaptable for many uses. Receives 326 to 335 MC. Contains six relays, 11 tubes 7-6A15, 12SR7, 2-12SN7, 2SD7. Size 13x5x8. Weight 12 lbs. A beautiful piece of equipment. Has three crystals. Priced complete with xtals and tubes. R-89/ARN-5 Near new condition. Net.....\$6.95

NAVY GLIDE PATH SCOOP \$3.95



tion \$3.95; 2 for.....\$6.95


Navy model ZA Glide path receiver. Has 3-6V6 tubes; several controls, transformer and handy case; size 6x7x12 inches. Ideal for salvage, near new condition.....\$6.95

NEW BC-1206 \$5.95

Designed to receive A-N beam signals. 24-28 vdc. Tube complement: 14H7, 14A7, RF, 14H7, 14J7, 14A7, 14H7, IF amplifier; 14H7, detector and 1st audio; 28D7, output. 195 to 420 KC 4" high x 4" wide x 6 1/2" long. Weight 4 lbs.



RCA SCOOP, \$12.95

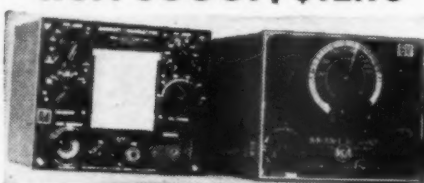


RCA AVT-112 Transmitter; pictured to the left; Brand new RCA aircraft transmitter. Crystal controlled, 2500 to 6500 KC. Designed for 6, 12 and 24 volt DC and 350 volt DC input. 9 tubes; 6AF6 dual tuning indicator, 6V6 Pierce oscillator, 6V6 P.A., 2-6V6, as plate modulators and 6SL7 tuning indicator amplifier. This is the nicest piece of equipment you have ever seen. 6x6x3 1/2 inches and weighs 6 pounds. Every ham or ham to be should have one of these. All brand new with tubes (less crystal) and complete instruction book. This unit covers 80 meters and 3105 and 6210 aircraft bands. Your Net.....\$12.95
RCA AVR-20A Aircraft Receiver; pictured to the right; small light weight, companion unit to the AVT-12A. A full 3 gang superhet, covering 2300 to 6500 KC, with tubes 6K8, 6ST, 6FT, and 6B8. Brand new, factory cartoned. This is a beautiful, compact piece of receiving equipment. RCA AVR-20A Receiver. Net. \$12.95
RCA AVT-12A Transmitter and RCA AVR-20A Receiver. Both for only.....\$24.95

RCA SALVAGE SCOOP \$2.95

RCA Radio Salvage Scoop. We have a few hundred of the AVR-20A receivers described above, in used condition. They have been stored in a damp place and are slightly molded. However, they have all of the tubes and parts and are not mutilated. Ideal for salvage. Service men: the 6K8, 6ST, 6FT and 6B8 are worth more than the price of the whole unit. With the tubes, you can't go wrong. AVR-20A Salvage only. Net. \$2.95 Two for.....\$4.95

AM-26 \$1.49

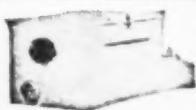AM 26 interphone amplifier. This unit is nice for parts salvage and the aluminum case is usable for receiver building etc. Size 9 1/2 x 4 1/2 x 5". Has two transformers, four tube sockets, three filter condensers, three position panel switch, toggle switch, and many small parts. All are in perfect condition. \$1.49; 2 for \$2.49



VIBRATOR SCOOP \$1.99



Heavy Duty Vibrator—Made for 6-110 volt amplifiers. Freq. 60 CPS. Scoop price.....\$1.99
135 ma 6-110 volt conventional power transformer, with all windings; will run phono motor. \$5.95
(Use with above vibrator.)

VEEDER ROOT METER



Counts number of feet of trailing wire antennae; number turns when winding on coil; applicable for many uses; beautiful bakelite case, jeweled dial, pilot light enclosed, 3 position switch, counts up to 1000. Each.....95c

McGEE RADIO COMPANY

WRITE FOR CATALOG SEND 25% DEPOSIT—BALANCE C.O.D.
1225 McGEE ST., KANSAS CITY, MISSOURI


BRAND NEW

BC-645 I.F.F. FACTORY CARTONED
450 Megacycle—Transmitter—Receiver

\$9.95

★ COMPLETE WITH 15 TUBES ★ DIAGRAMS ★ CONVERSION SUGGESTIONS

Two for \$19.00

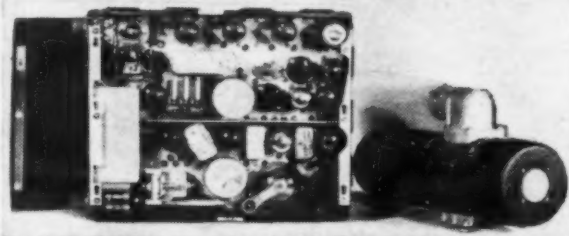

ARMY BC-645 I.F.F. UNIT. Early in the war when radar picked up a plane, there was no way of knowing whether it was friendly or not. That was before BC-645 was invented. BC-645 sent out a signal that identified the plane as American. It probably saved more lives than any other piece of electronic equipment made. With some modifications the set can be used for 2-way communication, voice or code, on the following bands: ham band 420-450 mc., citizens radio 460-479 mc., fixed and mobile 450-460 mc., television experimental 470-500 mc. Equipment capable of doing the jobs of the modified set sells for hundreds and hundreds of dollars. The 15 tubes alone are worth more than the sale price. 4-7FT, 4-7HT, 2-7E6, 2-6P6, 2-955 and 1-WE316A. It now covers 460 to 490 mc. Each BC-645 is shipped with a Belmont factory printed conversion diagram, showing how to make AC power supply modulator and how to make Transmitter and Receiver changes. Most Hams and experimenters already have the few parts necessary. New BC-645 with tubes less power supply. Shipping weight 25 lbs.

12 VOLT DC DYNAMOTOR. PRODUCES ALL VOLTAGES FOR THE OPERATION OF THE BC-645 Each \$2.95

EXTRA 316A TUBES 99¢


BC-654

TRANSMITTER RECEIVER

\$12.95

TWO FOR \$25.50

USED BUT GUARANTEED GOOD

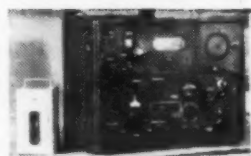

ORDER YOURS WHILE THEY ARE STILL AVAILABLE

Portable voice and CW transmitter and receiver for portable, mobile, and fixed station operation. 7-tube superheterodyne receiver with 3.5 microvolt sensitivity on voice and 0.5 microvolt sensitivity on CW and 100 milliwatts undistorted power output. 455 KC IF. Uses 3-1N5GT, 1-A7GT, 2-3Q5GT, 1-1H5GT tubes. 6-tube transmitter, with antenna tuning network. Colpitts thermal compensated oscillator, class C final with 2-307A tubes in parallel, and crystal oscillator for checking frequency every 200 KC. 25 watts output on CW and 11.2 watts output on voice. Frequency range, transmitter and receiver, 3800 to 5800 KC. Ideal for Hams. Comes complete with cover; furnished with all tubes necessary for the operation of the trans. and rec. Less power supplies. These units are used but in good condition. Shipping weight 50 lbs.

\$12.95; 2 for \$25.00

BC-654 Less all tubes and crystal.....\$7.95
654 VIBRATOR POWER PACK 6 OR 12 V.D.C. INPUT \$4.95 EXTRA.


ARC-4

TWO RECEIVERS, ONE TRANSMITTER ALL IN ONE UNIT IDEAL FOR 2 METERS

SCOOP PRICE

\$19.95

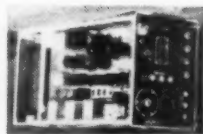PRICED COMPLETE WITH 20 TUBES—AND 12-28 VOLT DYNAMOTOR




FOUR CHANNELS CRYSTAL CONTROLLED. ARC-4 for VHF frequencies 140 to 144 megacycles. There are 7 tubes in the transmitter: 832, two 1614, two 6V6 and two 6L6. The receiver section has 13 tubes: two 6AC7, four 6N7, three 12SJ7, two 12SQ7 and two 12A6. The unit is actually two receivers and one transmitter in one piece. One receiver is for stand-by use. Has built on dynamotor for 12 or 24 volt DC operation. Priced complete with tubes and four crystals and dynamotor. Hams convert this for two meter operation. It's a scoop at this price. Used, but guaranteed to be in good condition.

LORAN

R-65 RECEIVER INDICATOR SCOPE

28 TUBES HAS G.E. 100 KC. CRYSTAL 3BP1 Scope Tube


\$24.95

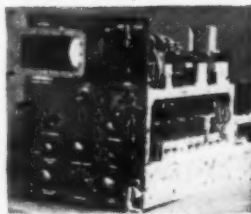

R-65 APN-9—Loran Receiver indicator scope. A compact Airborne unit. Priced complete with 28 tubes. 6SK7, 6SN7, 2X2, etc. Has 3 inch scope tube 3BP1. This unit has many possibilities. More parts, coils and controls than you can imagine. Has a 100 KC. General Electric crystal. Pictured with case removed. Size 9x12x16. Weight 35 lbs. These units have been in aircraft but we guarantee them to be in good condition.

Net \$24.95—Two for \$46.95

SELSYN INDICATORS \$2.95

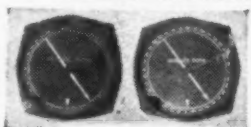

Selsyn indicators, 5" diameter. Will operate on from 15 to 24 volts 60 cycle AC. Model I-82A can be used as either selsyn transmitter or selsyn receiver. Scoop Price, \$2.95, 2 for \$5.49



SWITCH POT SALVAGE 99¢ 3 for \$2.50

PACKARD BELL PRE-AMP. \$1.99




Housed in a handy aluminum case 5x4x5, priced complete with tubes 6SL7, 28D7, has many usable parts. Relay and control PL8 plug and patch cord.

BC-412 SCOPE BRAND NEW FACTORY CARTONED

\$49.95

BC-412-612. Oscilloscope. Brand new factory carton, weight 200 lbs. This unit is the most ideal war surplus scope. Works on 110v 60 cycle AC. Only simple changes (conversion in many radio magazines) necessary to convert to a laboratory test scope. Has twin heavy duty plate supplies and tubes 5BP4 5" scope tube, 6-6L6, 2X2, 5T4, 2-6SJ7, 6SC7, 6H6, etc. Schematic diagram with each unit. This may be the last time we have a scope in a scope like this. Net\$49.95

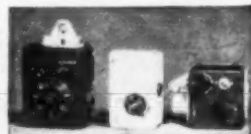Left to Right
New Remote Control Head and volume control CW, MCW sw. for BC-455-B 6 to 9 MC receiver.



Scoop Price, \$0.99
BC-631-13 Jack Box, NEW. Has 10M gain control and Jones 6 screw terminal block. Salvage Price.....\$0.29
Salvage Scoop BC-732-A Radio Control Box. Toggle switch, volume control and 6 position single pole cam-operated switch; phone jack. Scoop Price, \$0.49
HEAD PHONES. 10,000 ohms. Imp. Civilian Types. Standard length cord \$1.29 each.
VOLUME CONTROL SPECIAL. 1 Meg tapped with switch. 10 for \$4.00.

RECORD CHANGERS

GENERAL INSTRUMENT
single post, small size, deluxe model as used on many '47 model \$400 combinations. Shuts off on last record. Scoop price \$17.95.



Require two-post with permanent needle. Shuts off on last record. Scoop price \$11.95.
OAK deluxe model twin post changer. This is a finely tooled job. Net \$19.95.
AERO single post. Has push button off and on and reject switch. A small size changer. Net \$13.95.
Individually designed made to fit walnut bases may be had for any of the above changer for \$2.49 extra.

McGEE RADIO COMPANY

WRITE FOR CATALOG

SEND 25% DEPOSIT — BALANCE C. O. D. 1225 McGEE ST., KANSAS CITY, MISSOURI



If you haven't sent us
your name and address,
do it now and be
sure of getting
our monthly
**BARGAIN
BULLETIN**
and all special
Deals we offer

NO CHARGE—
IT'S **FREE!**

MAIL THIS
COUPON TODAY

OLSON

RADIO WAREHOUSE INC.
73 E. Mill St., Dept. 105, Akron, O.

Sure, put me on your List.
I want to save time and money.

- ☐ I have a Service Shop.
- ☐ I am an Amateur or Experimenter.

NAME _____

ADDRESS _____


CITY _____ STATE _____



CIRCUIT PAGE


(FOR PARTS LIST SEE PAGE 92)

RADIO NEWS, DECEMBER, 1947

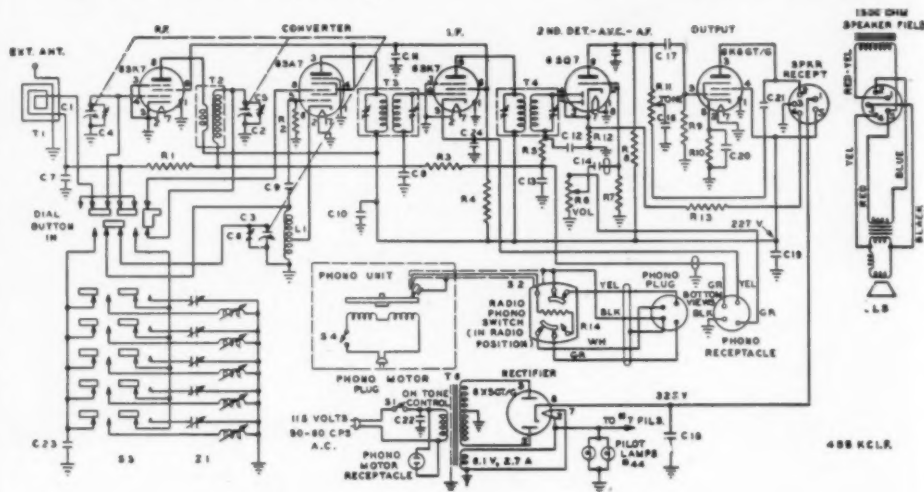HOFFMAN MODEL A500


RADIO NEWS, DECEMBER, 1947

ZENITH MODELS 6D014, 6D029

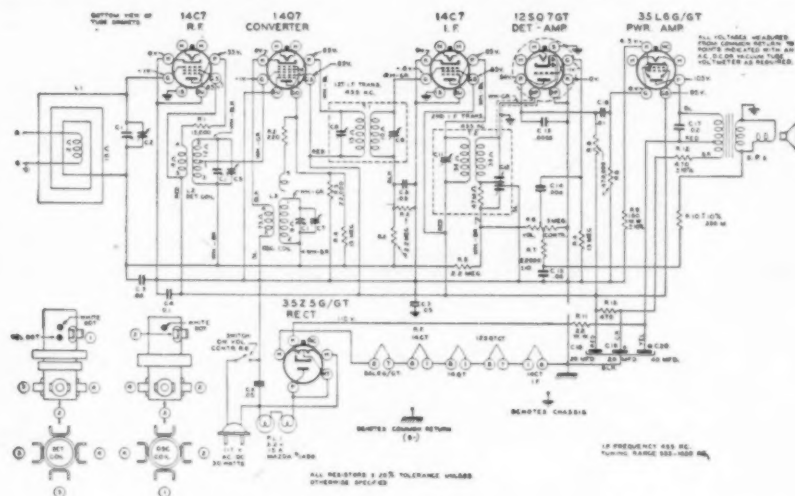

RADIO NEWS, DECEMBER, 1947


STEWART-WARNER MODEL 9003-B

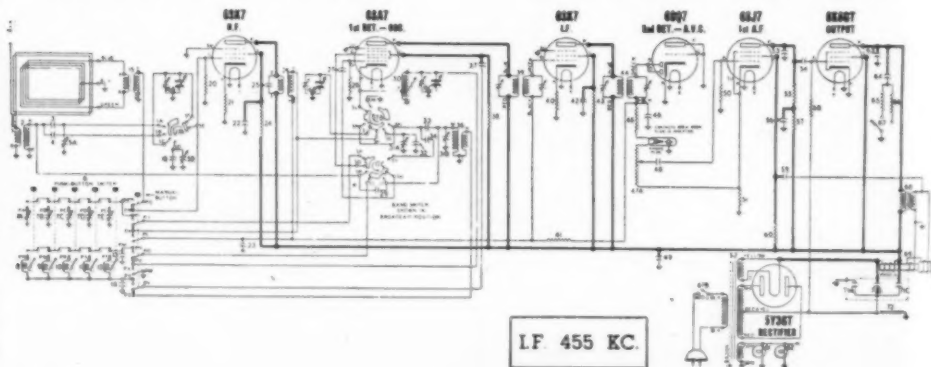

Here, and on following pages, are circuit diagrams and parts lists of many new postwar radio receivers. Radio News will bring to you other circuits as quickly as possible after we receive them from manufacturers.


RADIO NEWS, DECEMBER, 1947

ADMIRAL MODEL 7C63, CHASSIS 7C1

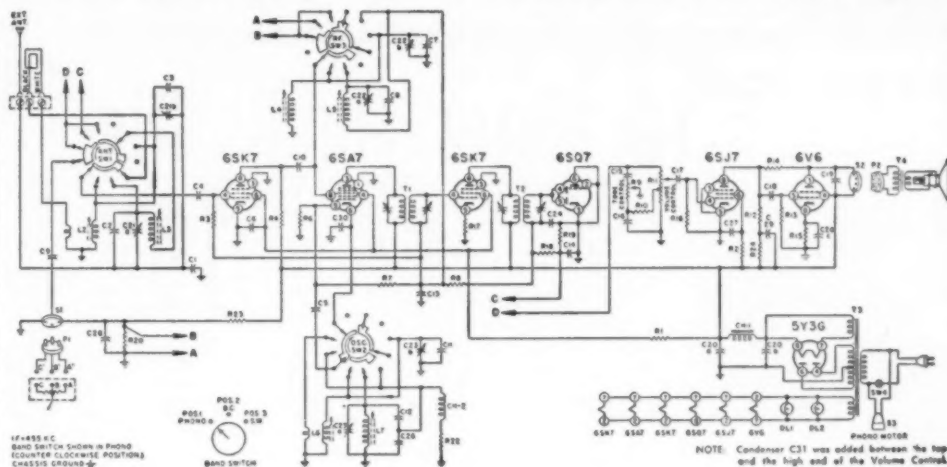


RADIO NEWS, DECEMBER, 1947

WESTINGHOUSE MODEL H-133

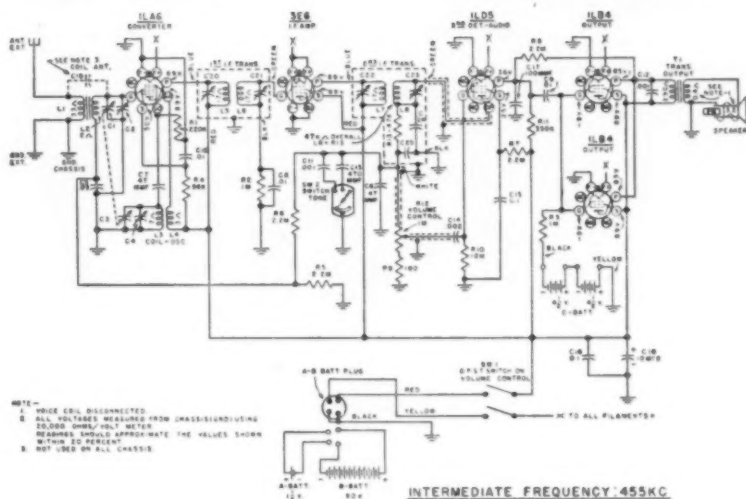

RADIO NEWS, DECEMBER, 1947

ARVIN MODELS 150TC, 151TC

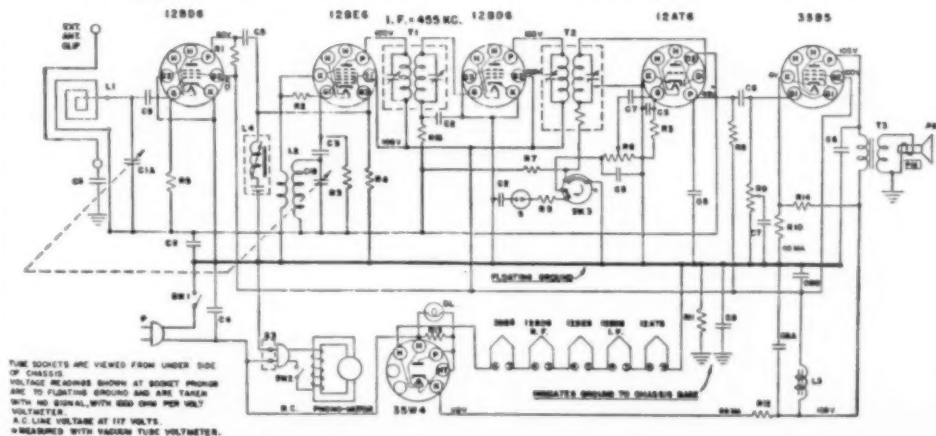

it's new
it's timely




it's **FREE!**

Lafayette's new Radio Supplement and Gift Guide

HERE ARE SOME TYPICAL LAFAYETTE BARGAINS

Phono and Amplifier Case

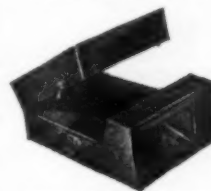

Handsome airplane luggage type case, lightweight and sturdy. Will hold phonos built to play 10 or 12 inch records, with space for 6" spkr. and amp. circuit. 13x14" mtg. panel. 19 x 13 3/4 x 7 1/2" overall. 8 lbs.

X19444 Your Cost, Only.....\$6.95
10 for.....\$53.00

TRUTEST 67 1/2 Volt Battery

A powerful miniature "B" battery for portable radios, hearing aids, etc. Can be used in place of similar Burgess, Minimax, RCA, etc. batteries. 2 1/16 x 1 3/8 x 3 1/8". 1 1/2 lbs.



XP5737.....\$1.29

Sensational Tube Values



872A.....	\$1.79
G1 8020.....	3.45
Elmac 15 E.....	1.95
327 A.....	2.95
VT-127 A.....	2.95
78P7.....	3.95
954.....	.39
Trutest Battery.....	1.29

Lafayette Radio
RADIO WIRE TELEVISION, INC.

100 Sixth Avenue, New York 13, N. Y.
542 E. Fordham Rd. Bronx 58, N. Y. 24 Central Avenue Newark 2, N. J. 130 Federal Street Boston 10, Mass.

MAIL THIS COUPON TODAY

Lafayette Radio, Dept. RL-7
100 Sixth Ave., N.Y. 13
Rush Free Supplement and Gift Guide No. 885.

Enter my order for X19444.....

XP5737.....

I Check () M.O. tube(s).....

NAME.....

ADDRESS.....

CITY.....ZONE.....STATE.....

R&M Radio

MORE FOR YOUR MONEY—
SATISFACTION
GUARANTEED—

Large, complete stocks—prices at absolute minimum—and
GUARANTEED EQUIPMENT Look at the prices on these war-
surplus items:

10 Meter Mobile.....\$19.50 2 or 6 Meter Rig.....\$17.50
BC-375E 17.50 ART-13 68.50

IMMEDIATE DELIVERY ON EVERY ITEM

TRANSMITTERS & RECEIVERS FOR

10 Meter Mobile Rig

WAR SURPLUS SCR-274-N COMPLETE ONLY

Conversion Book Supplied Free
gives details for low-cost,
easy conversion to

- 10 METER MOBILE RIG
- 20—40—80 METER BANDS

\$19.50



**FREE
CONVERSION BOOK**

**COST GOV'T
OVER \$600.00**

This sensation of all surplus is not only an ideal 10 Meter Mobile Rig! It's a complete amateur radio station! Here are a few more ways to use the equipment included in this Command Set. The transmitter VFO driver stage gives your BC-375-E higher RF output—as high as 150 watts. Make swell standby receivers with the BC-348 on round-table "rag chews." You get all this equipment: 3 Receivers—190-550 kc, 3-6 and 6-9.1 mc; two transmitters, 4-5.3 mc, 5.3-7 mc; four dynamotors—28 volts DC input; 1 modulator with carbon mike input; two tuning control boxes; one antenna coupling box with r-f ammeter; antenna relay and 5000 volt 50 mmfd. WE vacuum condenser (antenna relay can be used with most rigs); and a complete set of tubes for each unit—29 POP-ULAR TUBES in all. Mechanical cables for remote tuning of receivers supplied for \$1.00 extra.

MOUNTS

SCR-274-N COMMAND SET

FT-220-A	Rack for 3 receivers, with plugs	\$2.50
FT-221-A	Shock Mounting for FT-220-A	.75
FT-222-A	Mounting for Control Box BC-450	.30
FT-225-A	Shock Mounting for modulator BC-456	.60
FT-226-A	Rack for 2 transmitters, with plugs	2.25
FT-227-A	Shock mounting for FT-226-A	.75
FT-228-A	Mounting for Control Box BC-451-A	.20
FT-229-A	Shock Mounting for an- tenna relay BC-442-A	.60
Total		\$7.95

SPECIAL—Complete set of mounts for
SCR-274-N with plugs \$5.00

BC-348 RECEIVER

FT-154	Shock Mount with plug PL-Q103	\$2.25
--------	----------------------------------	--------

SCR-522 TRANSMITTER-RECEIVER

FT-488	Mount for transmitter- receiver	\$1.75
FT-498	Mount for dynamotor	1.25
Set		\$3.00

BC-375-E TRANSMITTER

FT-107	Mount for dynamotor PE-73-C	.75
FT-115-B	Individual rubber shock mount for top of trans.	.35
FT-151-A or C	Shock Mount for BC-375 Transmitter	2.25
Set		\$3.35

PLUGS: We have plugs available for all the
above equipment separately. Just name
your plug, each only .75c


INSTRUCTION BOOKS—MANUALS

BC-348	\$1.25	SCR-522	\$1.25
BC-375	1.00	BC-221	1.00
SCR-274-N	1.50	SCR-269-G	1.00



**COLLINS
ART-13
TRANSMITTER
Complete
\$68.50**

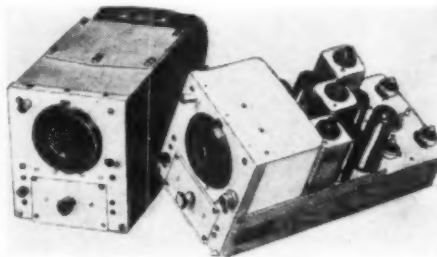Rated at over 100 watts, one of the most
compact and neatest xmtrs ever built, com-
plete with tubes and plugs; freq. range 2-18
mc. FREE schematic diagram furnished.
Dynamotor DY-17.....\$17.50
Remote control for xmtr.....\$3.00
**COMPLETE TRANSMITTER
with accessories\$89.00**



SUPER-HET RECEIVERS


Ideal Stand-By or Companion for Your
Shack—
75 meter receiver BC-454 **EACH \$5.50**
40 meter receiver BC-455
Easily adapted to 10 meter reception.
Airway weather stations BC-453 190-550 kc.

ALL THREE FOR \$14.50

Free Conversion Book with 2 or more sets.

SCOPE TUBE 5CP7 BRAND NEW \$2.98

ANTENNA SWITCHES

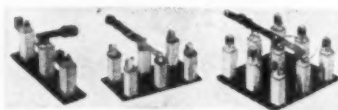

19c 29c 75c



**\$14.50 FOR
TRANSMITTER ONLY**


Transmitter complete with tubes, plugs and
one tuning unit.

COMPLETE BC-375-E transmitter, with
five tuning units, antenna loading unit,
dynamotor, plugs, and all tubes, only

\$24.50

FREE The complete unit has over
Conversion \$1,000.00 worth of standard
BOOK radio parts and cost govt. over
\$1,800.00 . . . one of most popu-
lar surplus items ever offered at such a low
price . . . and **GUARANTEED.**

OUTPUT 40 WATTS

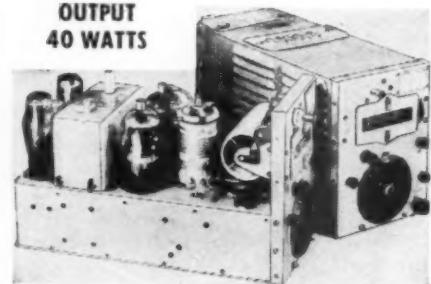

FAMOUS VFO DRIVER

BC-457	75 Meter VFO Driver	\$6.00
BC-458	40 Meter VFO Driver	\$6.00

Transmitters are complete with tubes,
schematic diagrams, and data for con-
version.

BOTH FOR \$10.00

CONTROL BOX BC-451 89c

Telegraph key, 2 mike
jacks, 4 position se-
lector switch, and nu-
merous other parts.





R & M RADIO CO.

CONVERSION BOOK SHOWS HOW


We've been deluged with requests for schematic diagrams covering various war surplus equipment conversions. This book, complete with diagrams, instructions, and discussion, covers the basic sets—SCR-274-N, BC-375-E, SCR-522, and BC-348. Our engineers have worked out many new ways of eliminating the worries and headaches of conversion.

\$2.00

TELEVISION SCOOP-BC 788

AC powered, needs only standard 50 mills 60 cycle transformer to replace present 400 cycle transformer; entire set usable as T.V. receiver with minor RF assembly changes. Has 6 I.F. stages, 30 mc. broad band width, 6AG5 tubes; stages mounted straight line; may be cut out intact to fit any set. One of the best 420-450 mc. SuperHet Receivers obtainable today. Schematic diagram furnished.

\$14.50

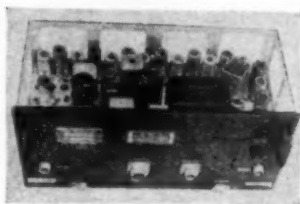

2 METER OR 6 METER RIG


AAF SCR 522

AAF SCR-522 designed to operate from 100-156 mc. makes ideal 2 meter rig (or 2-way mobile radio). Only two small changes incorporated converts to 6 meter operation. As mobile radio telephone unit the dynamotor can be converted to an engine-driven, self-excited generator or coupled to 1/4 hp. AC motor for ground station power supply.

Transmitter and Receiver complete with tubes **\$17.50**

Trans-Rec., tubes, dynamotor, control box, plugs and conversion diagram book—


\$24.50 GUARANTEED

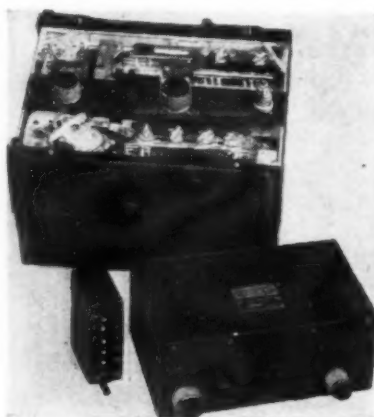


NAVY TRANSMITTER TYPE GP 7

Rated at over 125 watts, designed to cover from 350 to 9050 kc. with plug-in tuning units; one of the few transmitters on surplus market built of standard parts, making it a very unusual buy. Limited quantities. Transmitter, tubes, and tuning unit—

ONLY \$17.50

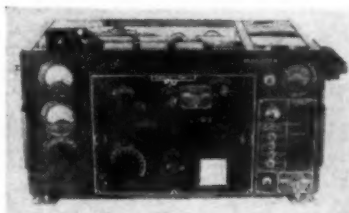

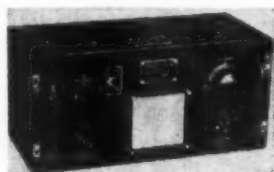TUNING UNITS—FIVE FOR \$10 OR \$2.50 EACH



The following are available:

TU-5B 1500—3000 kc. TU-9B 7700—10,000 kc.
TU-6B 3000—4500 kc. TU-10B
TU-7B 4500—6200 kc. 10,000—12,500 kc.
TU-8B 6200—7700 kc. TU-26B 200—500 kc.

We have several hundred sets of five tuning units to a box, all different.

FOR ONLY \$10.00 PER BOX

If you desire special tuning units, they are **\$2.50 EACH**

SAVE MONEY AND SAVE TIME — SATISFACTION GUARANTEED

R & M RADIO COMPANY
1426 N. QUINCY STREET • ARLINGTON, VIRGINIA

HEADPHONE ADAPTERS MC-385

From high to low impedance, 4000 ohms to 600 ohms. Contains matching transformer.

30c each, 4 for \$1.00

Headphones

69c

HS-33 with cord and plug, 600 ohms — Used, in A-1 condition.

Carbon Mike T-17


Used, in A-1 condition

\$1.00



HEADPHONE EXTENSION CORDS 25c

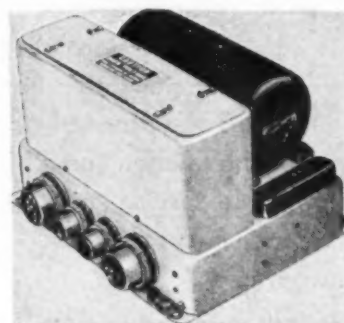Approx. 72" long, rubber covered, with JK-26 and PL-55 plugs.



SPEECH AMPLIFIER

Modulator for Transmitter,
High Voltage DC Power Supply


Model unit, BC-456-A or V with dynamotor DM-33-A, plugs and tubes. Approximate weight 17 lbs. Tube line-up, 12J5GT, 1625, VR150 and many other parts that make this an ideal purchase for spare parts alone. Diagram furnished.

\$2.75

ANTENNA

RELAY

\$2.45

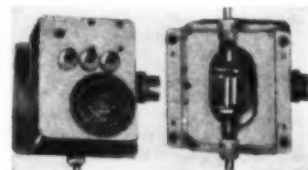

BC-442-A, SWITCHING RELAY, ANTENNA CURRENT INDICATOR with 19.5 millivolt movement, current transformer and thermocouple, 50 MMFD vacuum condenser, fixed, 5000 volt rating, (CAN BE USED WITH ANY RIG).

SPECIAL ON ANTENNAS

A 40-foot, heavy duty, light tubular steel, five section, telescopic antenna mast. Collar of each section has 3 guy wire points and uses cotter pins or bolts to secure sections. An ideal mast for mounting UHF directional arrays, television mast or all purpose antenna.

\$19.50 each; two for \$35.00

SAVE COD CHARGES BY REMITTING IN FULL

or send 25% deposit on all orders. Shipment is from our nearest warehouse—East, Mid-West, or West Coast—thereby saving you time and money.

All orders shipped best way, prices F.O.B.

**R & M RADIO COMPANY, Dept. RH-D7,
1426 N. Quincy St., Arlington, Va.**

☐ Send Conversion Book. ☐ \$2 inclosed. ☐ Send C.O.D.
Send FREE catalogue on
☐ Xmtr. Kits. ☐ Receiver Kits. ☐ Tube Bargains.
☐ I am a licensed amateur. ☐ Beginner.

Name _____

Address _____

City _____

Zone _____ State _____

distinguished service
record of the famous
WALDEN-WORCESTER
Socket Wrenches



SINCE Walden-Worcester made the first tool kits to go into the first automobiles, the products of this company have been compiling an enviable service record. Today Walden-Worcester Socket Wrenches are:

- Extra thin walled but 60% stronger
- Used by all major air lines
- First with precision forming
- Favorites for auto assembly
- First to use "Power-Packed" alloy steel
- First with new spring-lock design
- Protected with bright chrome finish



SET WW 21

The highest quality socket wrenches and attachments in all standard drives are also available in complete sets. Write Dept. 26 for further information.



STEVENS-WALDEN, INC.


Worcester • Massachusetts

Over Forty Years of Master Toolmaking

What's New in Radio

PICKUP ADAPTER

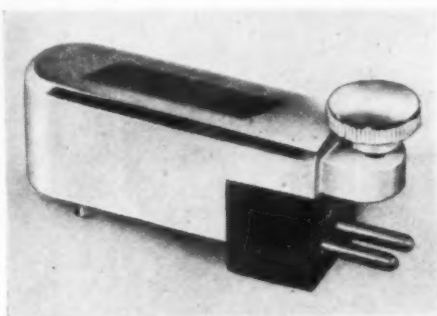Technical Products International of New York has recently developed a new "Vibromaster" type M Adapter which adapts the *Western Electric* 5A



arm to accommodate *General Electric* Variable Reluctance or *Pickering* 120M cartridges.

The adapter is interchangeable with 9A heads and provides a correct balance when used with the 5A arm and either the *GE* or *Pickering* cartridges. No soldering is necessary for attachment to cartridge lugs. Output of the cartridges at 10 cm. per second, stylus velocity is 25 millivolts for the *Pickering* and 11 millivolts for the *GE*. Since both of these units are high-impedance, the leads at the rear of the 5A arm should be opened and fed directly to grid or preamplifier.


Additional information on this adapter will be furnished upon request to *Technical Products International*, 453 West 57th Street, New York 19, New York.

WESTON TUBE CHECKER

A new proportional mutual conductance tube checker, designated the *Weston* Model 798 Type 5, has been announced by the *Weston Electrical Instrument Corporation* of Newark, New Jersey.

This new instrument tests not only all receiving tubes but will also handle voltage regulator tubes and low power thyatron tubes as well.

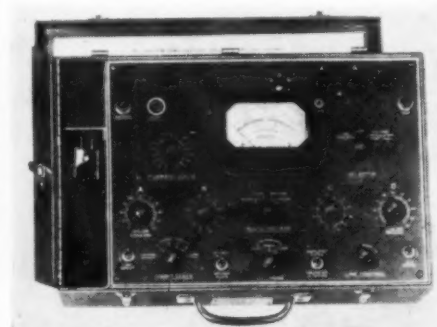A new differential frequency system, used in this instrument, provides proportional mutual conductance



readings under conditions which closely resemble actual operation. "Good-Bad" readings are also provided. 60-cycle a.c. potentials are used on tube

elements, thereby approaching the zero plate load conditions most desired for mutual conductance tests. A separate internal 5 kc. signal is applied to the control grid, and the resulting plate component of the high frequency signal is measured on a rectifier meter.


Since the normal plate current of the tube does not pass through the meter circuit, all types of tubes can be tested without overloading, in spite of widely varying characteristics. Three signal voltages of only .75, 1.5 and 3 volts provide mutual conductance ranges of 12,000, 6000, and 3000 micromhos, without overdriving, or tube damage which might result from the use of a higher signal voltage. A hot neon test is provided for checking leakage between tube elements.

Full details on the Model 798 Type 5 may be secured from *Weston Electrical Instrument Corporation*, 617 Frelinghuysen Avenue, Newark 5, New Jersey.

LIGHTWEIGHT ELECTRIC PLANTS

D. W. Onan & Sons, Inc., of Minneapolis, Minnesota, have developed a new line of lightweight electric plants designed for heavy-duty service.

This new CK line of plants is char-

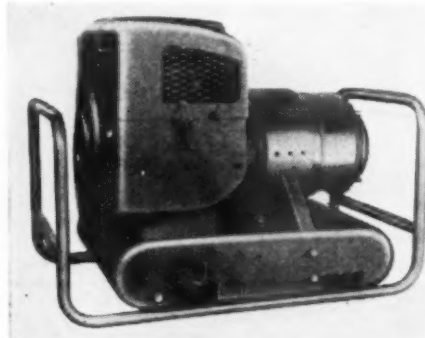

acterized by low cost operation, one kwh. output per quart of gasoline, and air-cooling.

One outstanding model in the line is the 5CK-115M weighing only 272 pounds. This 5000 watt plant employs the new *Onan* "CK" air-cooled, 4-cycle, two-cylinder gasoline engine.

The line is available in 60 or 50 cycle a.c. (2000 and 3000 watts) and d.c. (5000 watts, and 3500 watt battery charger) in stationary or portable types, with either manual or electric starting.

Correspondence concerning this line should be addressed to the Advertising Department, *D. W. Onan & Sons, Inc.*, Minneapolis 5, Minnesota.

PERSONALIZED METERS

Assembly Products, Inc., has just introduced a line of meters which should be of interest to amateurs.

A complete range of milliammeters and voltmeters, both a.c. and d.c., are being offered. These clear plastic meters may be obtained with the owner's

RADIO NEWS

**3rd
Smashing
Month**



ROCK BOTTOM PRICES!
ON ALL TOP QUALITY ITEMS

**25 Pounds of Radio
Parts and Assemblies**

We are swamped with tons of samples and odds and ends which cannot be placed in our regular stock. We must dispose of this useful merchandise immediately to give us elbow room. Buy 25 pounds of parts and assemblies at the ridiculously low price of **\$3.00**

Assortment Values

100 brand new assorted paper tubular by-pass condensers **\$3.85**
100 carbon and W.W. resistors —1/2, 1, 2, 5, 10 Watt —brand new stock..... **\$1.95**
105 ft. assorted spaghetti tubing. 35-3 ft. lengths for **\$1.00**

**JUST
ARRIVED!!!**

**General Industries phono-
motor and turntable!**

Model LX or MX (your choice) 78 R.P.M., rim drive, self-starting induction motor, 9 inch turntable. For 115 volt 60 cy. **\$2.95**

ASTATIC PHONO PICKUP
ARM with crystal cartridge. For 10" or 12" records. Sturdy die-cast construction, brown finish, curved. **\$1.45**

ALNICO P. M. SPEAKERS!
3" ... **\$1.29** 5" ... **\$1.49**
4" ... **1.39** 6" ... **1.59**

TUBES !!

Every tube we sell is guaranteed to be exactly the same as those you ordinarily pay 2 to 3 times as much for. No "off" brands, seconds, or used tubes. Your money back if not satisfied.

1A5	6J5	6SR7	12SK7
1H5	6J6	6V6	12SN7
1LC6	6S8	7E5	12SR7
5U4	6SA7	7N7	30
5Y3	6SD7	12A6	31
2C26	6SG7	12C8	35W4
6AL5	6SH7	12H6	39/44
6C4	6SK7	12J5	80
6C5	6SN7	12SH7	VT-52
6H6	6SQ7	12SJ7	

Your Choice

50c

1A7	6J7	12AT6	25Z6
1G4	6K7	12BA6	35L6
1G5	6X5	12BE6	35Z5
1N5	6Y6	12SF7	50B5
1R5	7F7	12SG7	2051
1S5	7Y4	12SQ7	VR105
1T4	12AH7	14B6	VR150
3Q5			

Your Choice

60c

1LH4—\$1.00	6SL7—\$0.75	955—\$0.75
1LN5—1.00	25L6—.75	956—.75
3B24—1.00	35Y4—.75	9001—.75
6AB7—.75	50L6—.75	9003—.75
6AG5—.75	117L7—1.00	9006—.50
6AC7—.75	826—1.00	2C40—1.00
6AG7—1.00	954—.75	2AP1—1.95
6L6—1.50		

Special Customers Bonus:

Deduct 10% from all tube orders of \$20.00 or over.

Special Purchases!!
LIMITED SUPPLY ONLY
ALL ITEMS SUBJECT
TO PRIOR SALE
Order Now!

Brand New Meter Bargains

Sangamo 0-50 DC MA, both sides center, 3" round..... **\$3.00**
Triplet 0-15 RF Amps 3" round **3.00**
Aero Freq. Meter 380-420 cycles per sec.: 125V 3" round **3.00**
McClintock 0-5 MA, 3" round. **3.00**
McClintock Triple Range: 0-15 DC MA, 0-300 DC-DC MA 3" Square Face..... **3.00**

**High Speed Drill
Sets (#0-45)**

45 Straight Shank High Speed Drills Graduated from .0810" to .2280". 45 drills for **\$7.25**

RG 8/U Coaxial Cable, 100 feet for.... **\$2.85**

RG 22/U Coaxial Cable, 100 feet for.... **4.85**

F.M.—I.F.'s

20.7 MC double iron core tuned I.F.'s. Four to a complete set. Use them for F.M. or Video. Can easily be trimmed down to 10 MC with a single ceramic condenser. Set of four matched I.F.'s. **\$3.98**




Xtal Phones

200-600 Ohms. Unusually Sensitive. Less Rubber pads. Used. Guaranteed perfect working order. **50c** ea. 10 for \$4.00

Bakelite

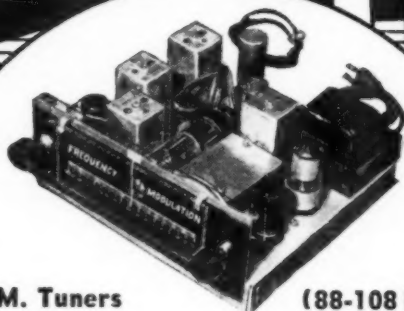Brown, 1/2 inch sheets—plain, no holes or marks. 36x36—weight 32 lbs.—per sheet **\$9.45**
36x42—wt. 35 lbs. per sheet **\$10.95**



F. M. Tuners

(88-108 MC)

Armstrong Circuit, 8 Tubes: 1 R. F., Mixer osc. 2 I. F.'s, 1 Limiter, 1 Disc. Rectifier, Tuning Eye (Not Furnished). 3 Gang Tuning Condensers built in 110V A.C. 300V Power Supply, 300 ohm dipole input. Each unit checked and guaranteed. Completely wired, ready to plug in. Supply Limited.

\$24⁹⁵

With 7 Tubes

**Broadcast
Band TRF
KIT**

\$6⁹⁵

Less cabinet, includes speaker, tubes, wound antenna coil, etc.

Most amazing 2 tube circuit on the market, provides 4 tube operation. Has nearly as much sock as ordinary 6 tube superhet. Ideal for the beginner, student or hobbyist. Can be built in several hours.

**Short Wave
Xmitter Kit
(2-30 MC)**

\$4⁰⁰

Companion to SW Receiver. Also uses 12SN7 and 6SL7 for four Tube Regenerative Circuit. Chassis, 2 Tubes, Resistor, Condensers, etc. included in Hardware Diagram. All for \$4.00. This easy to build set.

2-in-1 VALUE:

Learn code the ONLY practical way! Learn by building your own kit! **\$4⁰⁰**

**Practice Code
Oscillator
(Audio)**

Kit includes two tubes, sockets, chassis, key, resistors, condensers, wire, hardware, diagram, etc.

Buy Now!

**Short Wave
Receiver Kit
2-30
MC \$4⁰⁰
Only**

STUDENTS, HOBBYISTS, BEGINNERS!
This kit is the hottest experimental deal on the market. Two dual triodes, 6SL7 and 12SN7, give four tube operation. Kit includes: chassis, variable condenser, slugs, tuned coils, wire, sockets, resistors, condensers, etc., but speaker, everything but speaker, everything but speaker, everything but speaker!

All items listed subject to prior sale! TERMS: Cash with order, F.O.B. Chicago, Ill. Please remit postage charges. MANUFACTURERS: Write us your requirements.

IRVING JOSEPH

220 S. Halsted St.,

Chicago 6, Ill.

Lower Prices United Surplus Lower Prices

SAVE UP TO 50%!

• Phantom Antenna Unit

Mounted in round metal can, size 3 in. D. 6 1/4 in. L. Contains air trimmer, jewel lite, 2-20W resistors, amphenol male connector, iron slug tuned coil and 2 metal binding posts. Ideal as dummy ant. on 40M and 20M for low-power rigs. Each \$0.89

• Antenna—Fishpole Type

8 sections extends to 128 inches. Phosphor bronze conductor thru center makes positive contact to all sections. (AN-131-A)..... Each \$1.09

• Antenna—Telescopic Whip

AT-59 TRC-7. 27 1/4 inches fully extended. Has standard Amphenol co-ax male connector as a base mounting. Knocked-down size 15 1/4 in. Each \$0.69

• Tuning Units for B.C. 375

T.U. 26B and C.....\$1.19
T.U. 10B..... 1.79
Cases for above units.....Each .49

• V.H.F. Tuning Assembly

Tuning Condenser, acorn tube socket fil. bypass and two fil. R.F. chokes all mounted on Polystyrene subpanel. Drilled and tapped for 6-32 machine screw mounting. Size 1 3/4 in. x 3 1/2 in. Ideal for 2-meter transceiver, etc..... Each \$0.89

• Radio Compass Receiver Unit

BC-433 G. (less tubes) Part of SCR-269. Has 400 Cycle power supply (115V). Limited Quantity.....Each \$9.95

✓ CHECK THESE PRICES . . .

✓ Frequency Meters

6-inch square industrial type. GE with external Impedor. 58 to 62 cycles and 55 to 65 cycles. (Specify scale desired)..... Just \$11.95

✓ A.C. Ammeters

0-5 Full Scale calibrated 0-50 amps. GE and Burlington 3-inch round (less 50-amp shunt)..... Just \$2.49

✓ Insulators

Assortment, all-porcelain or isolantite-Ant., Spacer, Stand-off and feed thru. All new and usable. 15 insulators. Only \$1.00

✓ Selenium Rectifier

Dual unit. 7.1 V.A.C. 115 Cycles input. 1.7 V.D.C. @ 2.4 to 4 amp output. Plansteel. Ideal for converting battery sets to A.C. Only \$0.69 Each

✓ Head and Chest Sets

Consists of one phone and one breast microphone cord and plug. (Used.) Special at \$0.69 per set.

✓ Bias Meter

(1-97A) Used with teletype equipment. Has zero center meter which reads to 115 V.D.C. and 100 M.A. DC Right or Left. Mounted in sturdy steel case, 5" H., 7" L., 4 1/4" D. Contains cond., trans., and other useful parts. Diagram included. Marion Meter. A buy!..... Only \$5.45

✓ I.F.F. Unit V.H.F.

Uses 11 tubes in receiver and xmitter. New. With Dynamotor and tubes. Many useful parts and relays. Limited Quantity..... Only \$12.95

VIBROPACK (PE-125 BX)

12V and 24V.D.C. input, 475V @ 200 MA. D.C. output. Draws 7.2 amps at 24V and 15.2 amps. at 12V. A heavy-duty unit—built and rated for continuous service. Uses 2-RK 60 rectifiers, tubes incl. Limited Quantity! Shipping Wt. Approximately 80 Lbs. Only \$12.95

SAVE UP TO 50%!

BRAND NEW MERCHANDISE

\$2.00 minimum order, f.o.b. Chicago. 25% deposit. Balance C.O.D.

Money-Back Guarantee . . . if merchandise is not as specified




United Surplus Materials

3313-19 W. OGDEN AVE.

CHICAGO 23, ILL.

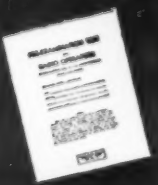PRE-EXAM TESTS FOR Commercial Radio Operator FCC LICENSE EXAMINATIONS



DON'T TAKE A CHANCE—AVOID FAILURE ON FCC COMMERCIAL RADIO OPERATOR LICENSE EXAMINATIONS!
USE NILSON'S COMPLETE PRE-EXAMINATION TESTS AND COACHING SERVICE Enables You To

Rehearse the FCC license examinations
Practice the procedure
Practice the multiple-choice examination methods used by FCC

Check your knowledge
Locate your weak points
Correct your weak points before taking the actual examination

Prepared by Arthur R. Nilson, Famous Co-author of Nilson and Hornung's
RADIO OPERATING QUESTIONS AND ANSWERS
Cleveland Institute of Radio Electronics, RN-12 Terminal Tower, Cleveland 13, Ohio

Cleveland Institute of Radio Electronics
RN-12 Terminal Tower, Cleveland 13, Ohio
Please send information about Pre-Exam Tests.

Name.....
Address.....
City..... Zone..... State.....

amateur call letters on the dial. These meters are easily illuminated from the rear by a light bulb located outside the instrument case and behind the panel. Light directed on the rear of



the case is piped through the plastic and diffused softly on the front of the dial scale.

Where front illumination is preferred, the clear plastic front casts no shadows on the dial and permits complete freedom in the choice of types of lighting.


The meters are supplied in the popular 3 1/4" rectangular size.

A circular describing this meter line is available upon request to Assembly Products, Inc., Chagrin Falls, Ohio.

HI-FI SPEAKERS

A new line of deluxe speakers, especially designed for extended range use in installations requiring efficient sound reproduction have been introduced by Permoflux Corporation of Chicago and Glendale.

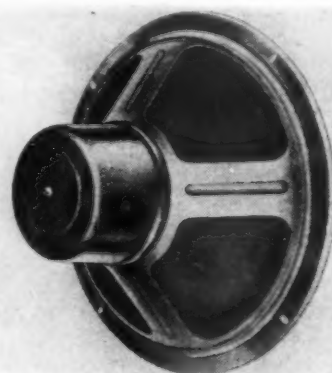Ranging in size from 10" to 15", these Hi-fidelity De Luxe speakers come in both permanent magnet and electro-magnet types, with power handling capacity up to 25 watts. The



PM type features a heavy ring magnet and oversize voice coils. With suitable baffling the audio range of these units is approximately 30 to 12,000 c.p.s.

Permoflux Corporation, 4900 West Grand Avenue, Chicago, Illinois, or 236 South Verdugo Road, Glendale 5, California, will supply full details on this new line, upon request.

SAFETY CARRYING CASE

Simpson Electric Company of Chicago has developed a new Roll Top Safety Case for housing the company's (Continued on page 120)


NOW AVAILABLE FOR IMMEDIATE SHIPMENT!

The New Model

777

20,000 OHMS PER VOLT!!

SET TESTER

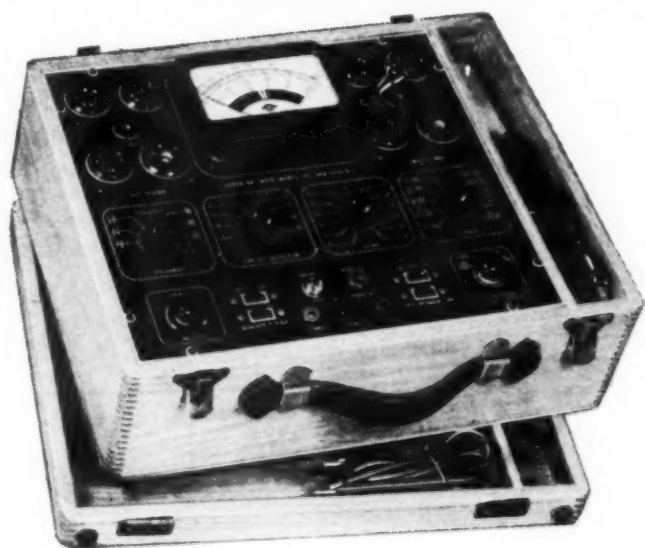

Specifications:

- Tests all tubes including 4, 5, 6, 7, 7L, Octals, Loctals, Television, Magic Eye, Thyratrons, Single Ended, Floating Filament, Mercury Vapor Rectifiers, New Miniatures, etc. Also Pilot Lights.
- Tests by the well-established emission method for tube quality, directly read on the scale of the meter.
- Tests leakages and shorts of any one element against all elements in all tubes.
- Tests both plates in rectifiers.
- Tests individual sections such as diodes, triodes, pentodes, etc., in multi-purpose tubes.
- New type line voltage adjuster.
- **D.C. VOLTS:** (At 20,000 Ohms Per Volt)
0 to 7.5/15/75/150/750/1,500 Volts
- **A.C. VOLTS:** (At 10,000 Ohms Per Volt)
0 to 15/30/150/300/1,500/3,000 Volts
- **D.C. CURRENT:**
0 to 1.5/15/150 Ma. 0 to 1.5 Amperes
- **RESISTANCE**
0 to 2,000/20,000/200,000 Ohms 0 to 50 Megohms
- **DECIBELS:** (Based on zero decibels equals .006 Watts into a 500-Ohm line.)
-10 to + 18 D.B., + 10 to + 38 D.B., + 30 to + 58 D.B.)

A super-sensitive, complete all purpose testing laboratory, this versatile analyzer will quickly and accurately test all tubes. The extremely high sensitivity of the V.O.M. section (20,000 ohms per volt on D.C. and 10,000 ohms per volt on A.C.) will enable you to:

1. Measure A.V.C. Voltages at the grid return of tubes.
2. Measure plate or grid Voltages in resistance coupled amplifiers.
3. Measure grid driving Voltages in amplifiers and phase inverters.
4. Measure minute leakage Voltages and currents in R.C. amplifiers.
5. Measure diode rectifier Voltages in second detectors.
6. Measure squelch Voltage in noise reduction circuits.
7. Align discriminator in F.M. sets.
8. Analyze automatic frequency control circuits.
9. Align F.M. receivers by measuring the grid voltage in the limiter stage.
10. Measure the Voltage at the grid of picture tubes for proper television alignment.

Model 777 operates on 90-120 Volts 60 cycles A.C. Housed in beautiful hand-rubbed cabinet. Complete with test leads, tubes charts and detailed operating instructions. Size 13" x 12½" x 6".

\$59⁹⁵
**NET
PRICE**

20% DEPOSIT REQUIRED ON ALL C.O.D. ORDERS


GENERAL ELECTRONIC DISTRIBUTING CO.

DEPT. RN-12 98 PARK PLACE, NEW YORK 7, N. Y.

"ARROW" leads with Better Buys!

ARMY AIRCRAFT RECEIVER Model BC-946-B

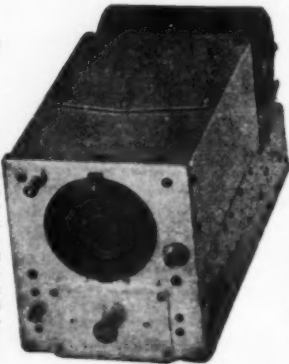Broadcast band from 520 to 1500 Kc; sensitive 6 tube receiver for the broadcast band with calibrated dial. Has one RF and two IF stages with iron core coils and air trimmers. "Perfect" for car radio, home radio, portable or P.A. tuner. BRAND NEW complete with six tubes and instruction manual in sealed carton, less dynamotor. Each... **\$12.95**



CROSS POINTER INDICATOR

Two 0-200 microampere movements, three inch case, many applications, A-1 condition. SPECIAL, each... **\$3.95**

RADIO RECEIVERS

BC-453-A: 190-550 kc, complete with tubes: BRAND NEW IN ORIGINAL CARTONS... **\$6.95**
used... **\$4.95**
BC-454-A: 3-6 mc; complete with tubes: BRAND NEW IN ORIGINAL CARTONS... **\$5.95**
used... **\$3.95**
BC-455-A: 6-9 mc, complete with tubes: BRAND NEW IN ORIGINAL CARTONS... **\$5.95**
used... **\$3.95**

TRANSMITTERS (274N Series)

All Brand New in Original Cartons
Complete with Tubes and Crystal

BC-690-3-4 Mc... **\$7.95**
BC-457-4.5-3 Mc... **5.95**
BC-458-5.3-7 Mc... **5.95**
BC-459-7-9.1 Mc... **5.95**

DYNAMOTOR

DM 32A. Each 95c; 3 for... **\$2.00**

AN18/APT-10

Pre-amplifier model K-1, designed to raise output level of magnetic type microphone, complete with 2 tubes 6SL7GT and 28D7 and hand switch, brand new in original cartons.

Each **\$1.95** 3 for **\$5.00**

REMOTE CONTROL BOX

BC-450-A... **\$1.95**

ARB AIRCRAFT RADIO RECEIVER

The ARB is a six tube, four band, superheterodyne Aircraft Radio Receiver with built-in dynamotor, designed for the reception of MCW (tone or voice) or CW within the frequency range 195 Kc to 9.05 megacycles. Used... **\$16.95**


Automatic Frequency Control Unit



Western Electric type used for controlling frequency for teletype and telephone work, complete with 3-6SJ7 and 2-6H6 tubes. Complete unit, brand new in original box... **\$4.95**

BC-929-A

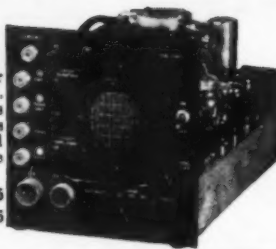Contains power supply 110 V, 400 cycles, has 7 tubes such as 3CP1, brand new, complete with tubes. Each... **\$17.95**
Used, ea. **14.95**



APS-15

Has 45 tubes, one 5" scope tube, one 2" scope tube, has 3 meters, 4 power supply units 110V 400 cycles, complete with tubes. Each... **\$39.50**

BENDIX COMPASS RECEIVER MN-26

Remote control commercial type navigational receiver. Indicates direction of any desired transmitting station. 3 bands—frequency range: 150 Kc to 1500 Kc; has 12 6 V. type tubes. Brand new, original cost **\$24.95**
\$600. Now

Accessories for above unit:
Loop MN-20... **\$6.95**
MN-28 Control Box... **5.95**
MN-52 loop control unit... **1.95**

T-17B HAND MIKE

BRAND NEW... perfect carbon hand mikes, light wt., 200 ohms, single button, press to talk switch, 5 ft. rubber cord, plug, dust cover. ONLY... **69c**

VHF RECEIVER BC-701

Frequency range 170-180 Mc; IF 30.5 Mc; complete with 11 tubes; self-contained power supply; brand new in beautiful wooden carrying case... **\$9.95**

NAVY GLIDE PATH RECEIVER

Bolt type, complete with 3 6C6 tubes and tune from 90 to 95 Mc; operates from 12 or 24 V. Brand New... **\$2.95**

VHF TRANSMITTERS

T-26/APT-2-450-710 mc... **\$12.95**
T-27/APT-3-85-135 mc... **14.95**
Above transmitters are amplitude modulated radar transmitters. Complete with all tubes such as 829, 832, 931, 6AC7, 6AG7, 5R4GY. Also 110 volt 400 cps. power supply. Brand new in original cartons. Manuals included.

GF12 and RU 17 NAVY RECEIVER and TRANSMITTER

Complete with receiving and transmitting coils, junction box, control boxes, plugs, power supply, instruction manual and spare parts which include tubes. Freq. Range: 200 Kc to 14 Mc. Brand new in original carton. A real buy... **\$24.95**

GO-9

Navy type low and high frequency transmitter with power supply and tubes. Operates from 200 Kc to 18,100 Kc; requires 115V, 800 cycles. Used. Complete with tubes... **\$39.50**

HAND-TYPE MICROPHONE RS-38

Carbon type, with PL-68 plug, brand new... **\$1.95**
Used... **1.00**

OXYGEN MASK MICROPHONE T44C


Used with SCR-522, magnetic type complete with JK-26 and PL-179. Used, A-1 condition... **95c**
Wholesalers, dealers, institutions and other quantity purchasers... Write, Wire, Phone for Quantity Prices. All shipments F.O.B. Chicago—20% Deposit Required on all orders. Minimum order accepted \$5.00.

WRITE FOR OUR COMPLETE CATALOG

DEPT. C

RCA AVT-112A—Aircraft Transmitter

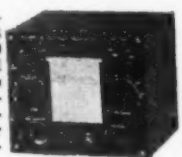For radio-telephone communication; for 6, 12 or 24 volt source freq. range from 2,500 to 6,500 Kc. Small in size and wt. (wt. 6 lbs.). Complete with 6 tubes, oscillator circuit, power amplifier modulators, dual tuning indicator and amplifier, with instruction manual, less crystal... BRAND NEW IN ORIGINAL CARTONS—ONLY... **\$12.95** each



Altimeter Transceiver RT-7/APN-1

Frequency 418-462 Mc FM, with 14 tubes: 3-12SJ7; 4-12SH7; 2-12H6; 1-VR150; 2-955; 2-9004; 27 V. Dynamotor, used in working condition... **\$7.95**

RECEIVER-POWER SUPPLY UNIT

For the APN-4 indicator; complete with 16 tubes: 110 V, 400 cycles. BRAND NEW... **\$10.95**
Used... **\$7.95**

SETCHELL CARLSON RADIO RECEIVER

Designed to receive A-N beam signals. 24-28 vdc 21.6 watts. Tube complement: 14H7 or 14A7, RF amplifier; 14H7 or 14J7, mixer; 14A7 or 14H7, IF amplifier; 14R7, detector and 1st audio amplifier; 28D7, output amplifier. 195 to 420 kc. 4" high x 4" wide x 6 5/8" long—wt. 3 lbs., 4 oz. Used, A-1 cond... **\$2.95**
BRAND NEW... **\$5.95**
in original carton

RADIO TRANSMITTER and RECEIVER APS-13

Light weight air-borne radar system, radio transmitter and receiver APS-13; tube complement: 5-6J6, 9-6AG5, 1-VR105, 2-D21, unit is brand new, complete with tubes, the tubes alone are worth more than this LOW PRICE OF ONLY... **\$10.95**

GLIDE PATH RECEIVER R-89/ARN-5

Glide Path Receiver used in the Instrument Landing System covering the frequency range 332 to 335 mc; complete with the following tubes: 7-6AJ5, 1-12SR7, 2-12SN7, 1-28D7, and including three crystals 6497KC, 6522KC, 6457KC units are in A-1 condition for ONLY... **\$8.45**

BC-733 D LOCALIZER RECEIVER

Freq. 108-110 Mc; Tube complement: 10 tubes—1-12SQ7, 2-12SR7, 1-12A6, 1-AH7GT, 2-12SG7, 3-717A; NOW ONLY... **\$6.95**

SCR-522 TRANSMITTER and RECEIVER

The standard very-high frequency airborne receiver transmitter. 100 to 156 megacycles. 4 channels selected from remote control box. Used, as is... **\$14.95**
"Complete with Tubes." ONLY... **\$19.95**
Excellent Condition, \$19.95

BC-625

VHF transmitter, frequency range 100-156 Mc., four channels. Part of SCR-522. Complete with tubes less crystals. Used, good condition. ea. **\$6.95**

BC-624

VHF Companion receiver for above transmitter. Complete with tubes less crystals. Used, good condition. Diagram with either unit included. Each... **\$8.95**

VEEDER-ROOT METER AND CASE

Counts up to 1000. Each... **95c**

WESTON OUTPUT METER No. 687

3 scales 0-50. A-1 Condition. ONLY... **\$5.95**

ARROW SALES, INC.

MAIN OFFICE

59 WEST HUBBARD ST., CHICAGO 10, ILL.

Telephone SUPERior 5575

SOUTH SIDE BRANCH
8310 SOUTH HALSTED ST.

NORTH SIDE BRANCH
1802 NORTH HUMBOLDT BLVD.

"ARROW" leads with Better Buys!

BC-645 TRANSMITTER-RECEIVER

BRAND NEW... 15 tubes interrogator-transmitter designed for airborne use, 435 to 500MC frequency range, 5 tube tuned line transmitter with 30 Watts peak-impulse power output on either two channels. With some modifications the set can be used for 2-way communication, voice or code, on the following bands: ham band: 420-450mc; fixed and mobile: 450-460mc; citizens radio band: 460-470mc; television experimental: 470-500mc; complete with all tubes, including WE Doorknob tube. Size 10 $\frac{1}{2}$ "x13 $\frac{1}{2}$ "x4 $\frac{1}{2}$ ". Net wt. only 25 lbs. Your cost..... only

\$995

TWO FOR ONLY : : : \$19.00

DYNAMOTOR FOR ABOVE Model PE-101-C.....\$2.95

ANTENNA RELAY UNIT BC-442

With antenna current meter, antenna transfer relay with 3 stand-off lead-in terminals. A-1 condition. Only **95c**

TRANSFORMER

High voltage scope transformer, 90V 60 cps primary; 6400 V secondary; 4 stand-off terminals.....each **\$2.95**

ANTENNA TRANSFER SWITCH SW-225

Triple-pole double-throw, mounted on bakelite base with nine 2" porcelain stand-off mounts. BRAND NEW..... **59c**

BC 732 CONTROL BOX

With 6 position, selective switch, volume control and toggle switch.....each **59c**

COAXIAL CABLE

26 ft. of Coaxial Cable RGU8, 52 ohm..... **89c**

OUTPUT TRANSFORMERS

6V6.....39c

FILTER CHOKES

All Fully Enclosed

3.7 H. @ 145 MA. DC., 125 ohms DC. Res. 4 MTG. Studs, each..... **59c**

100 mi 10H..... **59c**

I-70-D TUNING METER

Milliammeter for indicating resonance of tuned station. NEW.....each **49c**

400 CYCLE AUTOSYN MOTOR

Ideal for indicating direction of antenna systems—BRAND NEW.....each **\$2.95**

HEADPHONES

Signal Corps, 8000 ohms and 200 ohms, each.....used **79c**

RADIO PARTS

Assorted—100 mica condensers..... **\$1.19**

100 Resistors $\frac{1}{2}$ to 1 watt..... **95c**

100 Tubular bypass condensers, assorted..... **\$4.69**

.01 to .1, all 600 Volt..... **29c**

Electrolytic condensers..... **29c**

50-30, 150 Volt.....each **29c**

$\frac{1}{2}$ Meg. Volume Controls..... **\$3.00**

2" shaft with switch, 10 for..... **\$1.95**

$\frac{1}{2}$ Meg. Volume Controls..... **\$1.95**

2" shaft without switch, 10 for..... **\$1.79**

Crystal Pick-up, new light wt.....each **\$1.79**

BATTERY FOR "GE" PORTABLES

2-volt Willard type 27/2 the exact replacement in Pre-War Model LB 530 "GE" Portable Radios. Plastic case, size 3 $\frac{1}{2}$ "x3 $\frac{1}{2}$ "x5 $\frac{1}{2}$ " high. Shipped dry. Uses standard battery electrolyte. List value \$8.75.

BRAND NEW! Your Cost..... **\$1.95**



Large model, 5 inch diameter, only.....

\$295

SELSYN INDICATORS

For use with beam rotators for indication of direction of beam. Operate from 15-24V. 60-cycle AC supply.



Small model, 3 inch diameter, only.....

\$245

AC-DC TEST SET



For testing resistors, condensers, chokes, open and short circuits; complete with instruction manual and test leads. BRAND NEW in metal carrying case.

\$295 each

NEW BC 223 AX TRANSMITTER

801 Oscillator and 801 Power Amplifiers, 2—46 modulators and 1—46 speech amplifier; 4 Xtal Frequencies and Master Oscillator on selector switch 10 to 30 watts output. Tone voice or C.W. Mod. Ideal for Ham Use. Black wrinkle case. Tubes included. packed in original cases, less crystals, only **\$14.95** Shipping weight 125 lbs.

ARC 4 TRANSMITTER and RECEIVER

For operation VHF frequencies in range of 140-144 mc. Four channel crystal controlled, manufactured by Western Electric—12V. operation. Complete with crystal and dynamotor. Used. Good condition..... **\$24.95**

GE METER

C-10 amps., DC.....each **\$2.29**

INTERPHONE AMPLIFIER

Comes in an aluminum cabinet 9 $\frac{1}{2}$ "x4 $\frac{1}{2}$ "x5 $\frac{1}{2}$ ". DC output at 60MA. less tubes. Yours for only..... **95c**

LP-21 ADF LOOP

Low impedance loop, good for direction finder, one Selsyn motor, one Selsyn transmitter, freq. range of loop 100 Kc to 1750 Kc.; BRAND NEW..... **\$6.95** in original cartons, each.


PE-117 UNIVERSAL POWER SUPPLY

6 or 12 volt input; output 145 volts and 90 volts; less vibrator, voltage regulator and rectifier tube; ideal mobile power supply unit; excellent condition, each..... **\$2.95**

MONTHLY SPECIAL

VHF Radar Transmitter T-85/APT-5

Radar unit T-85 is an amplitude modulated transmitter. Frequency range 300 Mc-1500Mc. Power output 10-30 watts. Complete with two heavy duty 110 V. 60 cps. filament transformers. Tube lineup is as follows: 1—631; 2—6AC7 Video Amplifier; 1—6AG7 Video Amplifier; 1—6L6 Video Amplifier, 2—829B modulators, 1—6AG7 voltage control, 1—3C22 lighthouse oscillator, a set of locher wires are included to measure the approximate frequency. Instruction manual included. Brand new in original cartons..... **\$24.95**

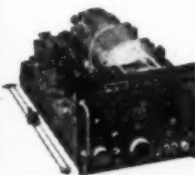

AM-61 Indicator Amplifier



18 tubes including two VR 105; 6L7GT; 6SN7GT;

with blower motor, brand new in original carton, with metal cover, each..... **\$9.95**

TUBES

6V6 12BE6
6X5 6SG7
6AG7 12A6
35W4 12C8
12AT6 6SJ7
12SR7 12SL7GT
1625 6A6
Amperite 10T1
12J5 10AC Neon
6AT8 12K8
6SF7 VR-105 6H6
5R4 6SN7 36 6G6G

49¢

SCOPE 3AP1.....\$1.19 3FP7.....\$1.19
TUBES 5FP7.....1.98 7BP7.....1.98

SPRAGUE PULSE FORMING NETWORKS



Used in small radar modulators, available in 3 sizes, 67 ohms impedance. 7.5 Kilowatt rating.
H-603, one micro second, 200 pulses per second..... **\$1.95**
H-601, 3 micro seconds, 200 pulses per second..... **\$2.95**
H-602, 16 micro seconds, 60 pulses per second..... **\$3.95**
ALL THREE ABOVE FOR ONLY.....\$5.95

Transmitting MICA CONDENSERS

.0008 at 5000 VDC.....24c .00005 at 3000 VDC.....19c

OIL-FILLED CONDENSERS

25 MFD at 1500 VDC.....59c
25 MFD at 15,000 VDC.....\$6.95
1 MFD at 1000 VDC.....59c
1 MFD at 3000 VDC.....59c
4 MFD at 600 VDC.....25c

WAVE METERS

Freq. range: 22 to 30 meg.....\$24.95
Freq. range: 37 to 53 meg.....24.95
Freq. range: 155 to 230 meg.....24.95
AC operated, complete with carrying case and magic eye for tuning indicator, veneer tuning dial.

CRYSTALS

10 crystals from 2 meg. to 8 meg.....\$2.95
Power Converter Unit PE-104A for BC-654.....\$4.95
Each only.....

ARROW SALES, INC.

MAIN OFFICE

59 WEST HUBBARD ST., CHICAGO 10, ILL.

Telephone SUPERior 5575

NORTH SIDE BRANCH

1802 NORTH HUMBOLDT BLVD.

SOUTH SIDE BRANCH
8310 SOUTH HALSTED ST.

BASIC 10" TELEVISION KIT

1. Sound IF Transformers (2)
2. Converter Transformer
3. 1st PIX IF
4. 2nd PIX IF
5. Cathode Trap
6. Discriminator Transformer
7. 3rd and 4th PIX IF
8. Video Series Peaking Coil
9. Video Shunt Peaking Coil
10. Video Series Peaking Coils (2)
11. Video Shunt Peaking Coils (2)
12. Filament Chokes (5)
13. Power Transformer
14. 13 Channel "Front End"
15. Deflection Yoke
16. Width Control
17. Horizontal Linearity Control
18. Yoke Mounting Hood
19. Focus Coil
20. Iron Trap Magnet
21. Horizontal Output Transformer
22. Vertical Output Transformer
23. Horizontal Blocking Oscillator Transformer
24. Vertical Blocking Oscillator Transformer
25. Horizontal Synchronizing Discr. Transformer
26. Horizontal Output and H.V. Transformer
27. Stamped Chassis.

All are exceptionally well known parts. In fact they lead the television field. All these major components cost you only.....

\$125⁰⁰

R.F. POWER SUPPLY

- 6 K Volt Unit completely wired.. **\$17.95**
10 K Volt Unit completely wired.. **\$24.95**

LAST MINUTE SPECIALS!

- 866A rectifier.....2 for **\$1.50**
S.C. J-45 code key with cord...3 for **\$1.00**
10 ft. 7 cond. viny. cable.....4 for **\$1.00**
Dual .1/7500 V. oil cond.....each **\$1.11**

25% deposit, balance C.O.D.

Please include sufficient payment for transportation. Over payment will be refunded

Write to Dept. R-12

*Holiday Greetings to
All Our Friends*

Standard Parts Corp.

235 MAIN ST. HEMPSTEAD, N. Y.

Parts Lists

(FOR CIRCUIT DIAGRAMS APPEARING ON PAGES 82 AND 83)

ARVIN MODELS 150TC, 151TC

Part No.	Code and Description.
C20060-222	R ₁ —2200 ohm, 1/4 w. res.
C20060-223	R ₂ —22,000 ohm, 1/4 w. res.
C20060-106	R ₃ —10 megohm, 1/4 w. res.
C20060-224	R ₄ —22 megohm, 1/4 w. res.
C20060-105	R ₅ —1 megohm, 1/4 w. res.
C19927	R ₆ —1 megohm vol. control
C20060-225	R ₇ —2.2 megohm, 1/4 w. res.
C20060-474	R ₈ —47 megohm, 1/4 w. res.
C19928	R ₉ —5 megohm tone control & sw.
C20060-151	R ₁₀ —150 ohm, 1/4 w. res.
C20060-334	R ₁₁ —33 megohm, 1/4 w. res.
C20060-220	R ₁₂ —22 ohm, 1/4 w. res.
C20060-331	R ₁₃ —330 ohm, 1/4 w. res.
C20070-123	R ₁₄ —12,000 ohm, 1 w. res.
C20060-104	R ₁₅ —1 megohm, 1/4 w. res.
AD21111-1	C _{1A} , C _{1B} —Var. cond. & pulley assembly
C20067-503	C ₂ —05 µfd., 200 v. cond.
C20065-500	C ₃ —00005 µfd., 500 v. mica cond.
C20068-503	C ₄ —05 µfd., 400 v. cond.
C20065-251	C ₅ —00025 µfd., 500 v. mica cond.
C20068-103	C ₆ —01 µfd., 400 v. cond.
C20068-502	C ₇ —005 µfd., 400 v. cond.
A21349	C _{8A} , C _{8B} —50/30 µfd., 150/150 v. elec. cond.
C20068-104	C ₉ —1 µfd., 400 v. cond.
AD21169-1	L ₁ —Antenna loop & cover assembly
AC21187-1	L ₂ —Osc. coil assembly
AC21107-1	L ₃ —Filter choke assembly
AC21158	L ₄ —I.f. trap
AC21097-1	T ₁ —First i.f. coil
AC21098-1	T ₂ —Second i.f. coil
AC21099-1	T ₃ —Output trans.

HOFFMAN MODEL A500

Part No.	Code and Description.
4500	R ₁ , R ₂ , R _{3A} —22 megohm, 1/2 w. res.
4501	R ₄ —22,000 ohm, 1/2 w. res.
4502	R ₅ —2.2 megohm, 1/2 w. res.
4503	R ₆ —10,000 ohm, 2 w. res.
4504	R ₇ —47,000 ohm, 1/2 w. res.
4804	R ₈ —5 megohm pot.
4505	R ₉ —10 megohm, 1/2 w. res.
4506	R ₁₀ —47 megohm, 1/2 w. res.
4507	R ₁₁ —560 ohm, 1/2 w. res.
4805	R ₁₂ —25 megohm pot. with sw.
4508	R ₁₃ —47 ohm, 1/2 w. res.
4509	R ₁₄ —330 ohm, 1/2 w. res.
4400	C ₁ , C ₂ , C ₃ —388/388/150 µfd. var. cond.
4100	C ₄ , C ₅ , C ₆ —Trimners (Part of var.)
4000	C ₇ , C ₈ —105 µfd., 200 v. cond.
4101	C ₉ , C ₁₀ , C ₁₁ , C ₁₂ —100 µfd. mica cond.
4102	C ₁₃ , C ₁₄ , C ₁₅ —05 µfd., 400 v. cond.
4103	C ₁₆ , C ₁₇ —005 µfd., 600 v. cond.
4200	C ₁₈ , C ₁₉ , C ₂₀ —20/20/20 µfd., 450/450/25 v. elec. cond.
4104	C ₂₁ —001 µfd., 600 v. cond.
4105	C ₂₂ —01 µfd., 600 v. cond.
4004	C ₂₃ —500 µfd. silver mica cond.
5200	L ₁ —Osc. coil
9012	L ₂ —10" electrodynamic speaker
6001	S ₁ —On-off sw. (on tone control)
6000	S ₂ —Radio-phonograph sw.
5224	S ₃ —Pushbutton sw. assembly
5212	T ₁ —Phono motor sw.
5203	T ₂ —Ant. loop
5204	T ₃ —Shielded r.f. coil
5000	T ₄ —Input i.f. trans.
55200	T ₅ —Output i.f. trans.
	T ₆ —Audio output trans.
	T ₇ —Power trans.
	Z ₁ —Pushbutton tuning assembly

WESTINGHOUSE MODEL H-133

Part No.	Code and Description.
RC10AE224M	R ₁ —220,000 ohm, 1/4 w. res.
RC10AE105M	R ₂ , R ₃ —1 megohm, 1/4 w. res.
RC10AE563M	R ₄ —56,000 ohm, 1/4 w. res.
RC10AE225M	R ₅ , R ₆ , R ₇ , R ₈ —2.2 megohm, 1/4 w. res.
RC10AE101M	R ₉ —100 ohm, 1/4 w. res.
RC10AE106M	R ₁₀ —10 megohm, 1/4 w. res.
RC10AE334M	R ₁₁ —330,000 ohm, 1/4 w. res.
V-3564	R ₁₂ , SW ₁ —1 megohm vol. control & sw.
V-3569	C ₁ , C ₂ , C ₃ , C ₄ —2-gang var. cond.
RCP10W2503A	C ₅ —05 µfd., 200 v. cond.

RCM20A470K RCP10W4103A

Part No.	Code and Description.
RCP10W6102K	R ₁ —2200 ohm, 1/4 w. res.
RCM20A471K	R ₂ —22,000 ohm, 1/4 w. res.
RCP10W6202A	R ₃ —10 megohm, 1/4 w. res.
RCP10W2104A	R ₄ —22 megohm, 1/4 w. res.
RCM20A101M	R ₅ —1 megohm, 1/4 w. res.
V-3581	R ₆ —1 megohm vol. control
V-4723	R ₇ —2.2 megohm, 1/4 w. res.
V-3567	R ₈ —47 megohm, 1/4 w. res.
V-3582	R ₉ —5 megohm tone control & sw.
V-3576	R ₁₀ —150 ohm, 1/4 w. res.
V-3577	R ₁₁ —33 megohm, 1/4 w. res.
V-3578	R ₁₂ —22 ohm, 1/4 w. res.

Part No.	Code and Description.
C ₈ , C ₉ , C ₁₀	—47 µfd. cond.
C ₁₁ , C ₁₂	—01 µfd., 400 v. cond.
C ₁₃ , C ₁₄	—001 µfd., 600 v. cond.
C ₁₅	—470 µfd. cond.
C ₁₆	—002 µfd., 600 v. cond.
C ₁₇ , C ₁₈	—1 µfd., 200 v. cond.
C ₁₉	—100 µfd. cond.
C ₂₀	—10 µfd., 150 v. elec. cond.
C ₂₁	—4.7 µfd. cond. (Not used on all chassis)
L ₁ , L ₂	—Antenna coil
L ₃ , L ₄	—Osc. coil
T ₁	—Output trans.
First i.f. trans.	
Second i.f. trans.	

ZENITH MODELS 6D014, 6D029

Part No.	Code and Description.
63-590	R ₁ —15,000 ohm, 1/4 w. res.
63-579	R ₂ —220 ohm, 1/4 w. res.
63-591	R ₃ —22,000 ohm, 1/4 w. res.
63-976	R ₄ —15 megohm, 1/4 w. res.
63-600	R ₅ —2.2 megohm, 1/4 w. res.
63-1335	R ₆ —5 megohm vol. control
63-644	R ₇ —22,000 ohm, 1/4 w. res.
63-597	R ₈ —470,000 ohm, 1/4 w. res.
63-1237	R ₉ —150 ohm, 1/2 w. wirewound, res.
63-776	R ₁₀ —330,000 ohm, 1/4 w. res.
63-1450	R ₁₁ —22 ohm, 1 w. wirewound, res.
63-1222	R ₁₂ —470 ohm, 1 w. res.
63-1449	R ₁₃ —470 ohm, 1 w. res.
22-1356	C ₁ —3-gang var. cond.
22-629	C ₂ —Broadcast ant. trimmer (on C ₁)
22-827	C ₃ —05 µfd., 200 v. cond.
	C ₄ —1 µfd., 200 v. cond.
	C ₅ —Broadcast det. trimmer (on C ₁)
	C ₆ —05 µfd., 200 v. cond.
	C ₇ —Broadcast osc. trimmer (on C ₁)
	C ₈ —First i.f. primary trimmer (on T ₁)
	C ₉ —First i.f. sec. trimmer (on T ₁)
	C ₁₀ —Second i.f. trans. primary trimmer (on T ₂)
	C ₁₁ —Second i.f. trans. sec. trimmer (on T ₂)
	C ₁₂ —0005 µfd., 600 v. cond.
22-1362	C ₁₃ —004 µfd., 600 v. cond.
22-1361	C ₁₄ —04 µfd., 400 v. cond.
22-196	C ₁₅ —01 µfd., 600 v. cond.
22-1379	C ₁₆ —02 µfd., 400 v. cond.
22-1519 or 22-1551	C ₁₇ , C ₁₈ , C ₁₉ —20/20/40 µfd., 150/150/150 v. elec. cond.
S-11124	L ₁ —Wavemagnet assembly
S-12877	L ₂ —Det. coil assembly
S-9578	L ₃ —Osc. coil assembly
95-960	T ₁ —First i.f. trans. assembly
95-958	T ₂ —Second i.f. trans. assembly
100-90	PL ₁ —3.2 v., .15 amp. pilot light
49-549	SP ₁ —5" PM speaker

ADMIRAL MODEL 7C63—CHASSIS 7C1

Part No.	Code and Description.
61A1-1	R ₁ —12,000 ohm, 5 w. res.
60B8-225	R ₂ —2.2 megohm, 1/2 w. res.
60B8-474	R ₃ , R ₄ , R ₅ —470,000 ohm, 1/2 w. res.
60B20-103	R ₆ —10,000 ohm, 2 w. res.
60B8-223	R ₇ —22,000 ohm, 1/2 w. res.
60B8-106	R ₈ —10 megohm, 1/2 w. res.
60B8-105	R ₉ —1 megohm, 1/2 w. res.
75B1-8	R ₁₀ —2 megohm tone control
60B8-273	R ₁₁ —27,000 ohm, 1/2 w. res.
75B2-2	R ₁₂ —1 megohm vol. control & sw. (tapped at 500,000 ohms)
60B8-335	R ₁₃ —3.3 megohm, 1/2 w. res.
60B14-391	R ₁₄ —390 ohm, 1 w. res.
60B8-106	R ₁₅ —10 megohm, 1/2 w. res.
60B8-101	R ₁₆ —100 ohm, 1/2 w. res.
60B80224	R ₁₇ —220,000 ohm, 1/2 w. res.
60B8-104	R ₁₈ , R ₁₉ —100,000 ohm, 1/2 w. res.
60B14-104	R ₂₀ —100,000 ohm, 1 w. res.
60B8-473	R ₂₁ —47,000 ohm, 1/2 w. res.
65B7-33	C ₁ , C ₂ , C ₃ —1000 µfd. mica cond.
65B1-31	C ₄ —35 µfd. silver mica cond.
65B1-28	C ₅ —25 µfd. silver mica cond.
65B7-17	C ₆ , C ₇ —100 µfd. mica cond.
65B6-4	C ₈ —50 µfd. ceramic cond.
64B1-22	C ₉ —05 µfd., 400 v. cond.
65B1-27	C ₁₀ , C ₁₁ —65 µfd. silver mica cond.
65B1-13	C ₁₂ —420 µfd. silver mica cond.
65B7-5	C ₁₃ —200 µfd. mica cond.
65B1-14	C ₁₄ —200 µfd. silver mica cond.

RADIO NEWS

LEARN
EITHER

Electricity OR Radio

IN A FEW WEEKS

in the GREAT SHOPS of COYNE

NOT "Home Study" Courses
...All Practical Training and
Necessary Theory Given in
Our Famous Chicago Shops!

Why spend years learning Electricity or Radio, when COYNE prepares you for good jobs in either field in a few short weeks? Our training not only saves time; you're ready to step into the better pay that much sooner. You make rapid progress because you work under expert instructors here in our great shops. We do not teach by mail. Select course you prefer and send coupon TODAY!

ELECTRICITY



Including Industrial Electronics


Big future in Power Plant Work, Motors, Armature Winding, House and Factory Wiring, Industrial Electronics, Home Appliances, Lighting, Auto Electricity, Electrical Maintenance — all covered at COYNE. Here you get "all-around" Electrical training!

TRAIN ON REAL EQUIPMENT

You use, test, repair full-size apparatus — just like you'll later handle on the job. Previous experience unnecessary.

FREE ELECTRICAL BOOK

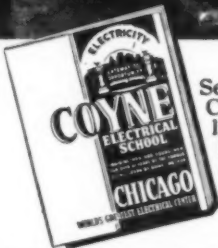Send now for big, illustrated book on COYNE Electrical Training. Many large pictures of our shops. Tells about Free Lifetime Employment Service to Coyne graduates. Other vital facts. Check coupon for "ELECTRICITY" and mail today.



RADIO including SOUND and TELEVISION

If you prefer Radio, COYNE gives quick, practical training in Radio Construction, Testing, Repair; also Public Address, Sound Systems, FM, Television. Many branches of Radio open to you.

Want to be Your Own Boss?

Hundreds of Coyne graduates have successful Radio shops of their own. We show you how to start, how to build for a lifetime future. No previous experience required to take Coyne Radio Course.

FREE RADIO BOOK

Check coupon for "RADIO" to receive our big FREE book of photos and facts about Coyne Training in Radio, Sound and Television. Describes the vast new opportunities in this field, and how we make it easy to get ahead. Rush coupon NOW.



COYNE HAS BEEN TRAINING MEN SINCE 1899

For nearly 50 years, the great shops of COYNE have been turning out men and young men trained for better jobs in practical fields. Coyne graduates hold responsible positions in many leading electrical and radio firms.



B. W. COOKE

ADDED TRAINING in **ELECTRIC REFRIG-ERATION** included with either course

NON-VETERANS who are short of cash can finance their tuition and pay it in easy monthly payments after graduation.

VETERANS! Coyne is authorized to accept veterans for G. I. training. Coupon brings bulletin.

COYNE ELECTRICAL SCHOOL
Dept. 97-81H
500 S. Paulina Street, Chicago 12, Ill.

CHECK COUPON FOR ELECTRICITY OR RADIO—MAIL NOW!

B. W. COOKE, Director,
COYNE ELECTRICAL SCHOOL,
500 S. Paulina St., Dept. 97-81 H. Chicago 12.
Send me your BIG FREE BOOK—for the course checked below, and tell me about your special plans to help me. This does not obligate me and no salesman will call.

☐ ELECTRICITY ☐ RADIO

NAME.....

ADDRESS.....

CITY.....


STATE.....

Another Christmas Special!



FREE Clarostat metal cabinet with every kit of 10 standard controls and 5 standard switches—your choice of sizes..... **\$9.05**

MECK DISC RECORDER \$79.00

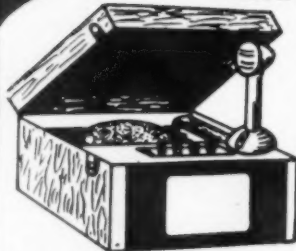

For the latest in modern engineering, The John Meck Industries (Audar) portable disc recorder combines a transformer type amplifier with excellent volume and tone quality. Records cut and played back at 33½ or 78 RPM. Complete with crystal mike and cutting and play-back needles..... **\$79.00**

Weight 35 lbs.

MODEL 79—WEBSTER WIRE RECORDER

Foundation Unit



Especially designed for the experimenter, amateur and engineer for building a complete magnetic recorder or adding a wire recorder to a sound system. Physical specifications: 10½" x 8¾" x 5½" (3½" below main plate, 2" above). Net weight 10 lbs. **\$52.92**

Net.....


ALUMINUM BLANK CHASSIS

7x9x2, Natural Finish.
List \$1.70.....Net **\$1.02**
7x11x2, Natural Finish.
List \$1.82.....Net **1.09**
5x9x3, Black Wrinkle.
List \$1.82.....Net **1.09**

8x17x3, Black Wrinkle.
List \$3.20.....Net **\$1.90**
10x14x3 Black Wrinkle.
List \$3.12.....Net **1.86**
10x17x3, Black Wrinkle.
List \$3.38.....Net **2.00**

13x17x3, Black Wrinkle.
List \$5.00.....Net **\$3.00**
6x9x5, Black Wrinkle.
List \$2.00.....Net **1.20**
6x9x5, Black Wrinkle.
List \$3.00.....Net **1.84**

"ULTRA MIKE" WIRELESS MICROPHONE

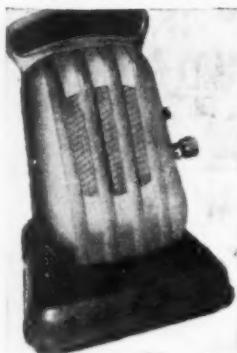

This unit with your regular radio and NO extra interconnecting wires will provide superior results as a

- CALLING SYSTEM
- PUBLIC ADDRESS
- DETECTOPHONE
- BABY OR INVALID WATCHER

The "Ultra Mike" is light—economical to operate—completely self contained—no connections to power lines—portable. Complete with batteries, tubes, etc. **\$6.63**

YOUR COST.....Special **\$6.63**

F.O.B. Chicago



MECK FM CONVERTER — \$14.95

Just announced by John Meck Industries... sensational! AM radio (regular) receives FM signals (88 to 108 MC). Dealers **\$15.95**

Net.....

Lots of 3...\$14.95

Webster Changers


Model 50....\$21.17
Model 56.... **26.66**
Model 70.... **42.34**

Mort's Radio Shack

630 W. RANDOLPH STREET

CHICAGO 6, ILL.

Permoflux SPEAKERS

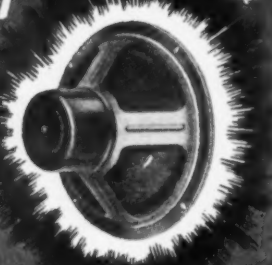

YOUR JOBBER CAN SUPPLY YOU!

Permoflux quality and dependability—the same as supplied to the major set manufacturers—is your assurance of complete customer satisfaction. You'll find Permoflux Speakers easy to install and readily available in both PM and Electrodynamic types. You'll find too, that it pays to give your customers "tops in tone" with a Permoflux Replacement Speaker.

TWO COMPLETE FACTORIES TO SERVE YOU

PERMOFLUX

WRITE FOR FREE BULLETIN

PIONEER MANUFACTURERS OF PERMANENT MAGNET DYNAMIC TRANSDUCERS

PERMOFLUX CORPORATION

4900 WEST GRAND AVE., CHICAGO 39, ILLINOIS
236 SOUTH VERDUGO ROAD, GLENDALE 5, CALIFORNIA

64B1-20
65B7-22
64B1-24
64B1-25
64B1-12
64B1-10
67C6-25

C₁₈—1 µfd., 400 v. cond.
C₁₆—250 µfd. mica cond.
C₁₆—02 µfd., 400 v. cond.
C₁₇—01 µfd., 400 v. cond.
C₁₈—003 µfd., 600 v. cond.
C₁₉—01 µfd., 600 v. cond.
C_{20a}, C_{20b}, C_{20c}—30/30/20 µfd., 350/350/25 v. elec. cond.

66A1-3

C_{21a}, C_{21b}—3-40 µfd. dual trimmer
C_{22a}, C_{22b}, C_{22c}, C_{22d}—3-40 µfd. trimmer

66B8-1

65B5-34

64B1-32

64B1-28

64B1-20

65B7-5

64A3-4

AD120

AD116-1

AC105-2

AD116-2

AB100-1

AD116-3

AC101-1

74A3

AB103-1

72B7

72B8

80B1

98A19

STEWART-WARNER MODEL 9003-B

Part No. Code and Description.
502186 1—Loop antenna
502110 2—S.w. antenna coil
502166 3—82 µfd., 500 v. cond.
502164 4—670 µfd., 500 v. cond.
502910 5A, 5B—2-15/10-40 µfd. trimmer assembly
502120 6—Pushbutton sw.
502910 7A, 7B, 7C, 7D, 7E—Trimmer assembly for push-button tuner

502907

502908

502909

502161

502165

502112

502122

502119

502182

502468

502127

502157

502133

502132

502295

502113

502159

502130

502411

502114

502108

502182

502167

502163

502111

502151

502466

502102

502125

502135

502157

502467

502103

502131

502271

502117

502150

502157

502468

502128

502174

502160

502152

502133

502410

502132

502134

502405

502135

110629

502150

502154

502291

502127

502118

504206, 504208, 504124

504205

504205, 5042107, 504125

502207

502137

8—340-1000 kc. coil
9, 10—650-1300 kc. coil
11, 12—975-1600 kc. coil
13—270 µfd., 500 v. cond.
14—1000 µfd., 500 v. cond.
15—Broadcast antenna coil
16A, 16B, 16C—Var. gang cond.
17A, 17B, 17C—Bandswitch
18—39 µfd., 500 v. cond.
20—4.7 megohm, ¼ w. res.
21—560 ohm, ¼ w. res.
22—05 µfd., 400 v. cond.
23—1 µfd., 200 v. cond.
24—100,000 ohm, ¼ w. res.
25—10 µfd., 500 v. cond.
26—Broadcast r.f. coil
27—50 µfd., 500 v. cond.
28—22,000 ohm, ¼ w. res.
29—2 µfd., 500 v. cond.
30—Broadcast osc. coil
31A, 31B—2-15/2-15 µfd. trimmer assembly
32—39 µfd., 500 v. cond.
33—68 µfd., 500 v. cond.
34—430 µfd., 500 v. cond.
36—S.w. osc. coil
37—01 µfd., 400 v. cond.
38—33,000 ohm, 1 w. res.
39—First i.f. trans.
40—220 ohm, ¼ w. res.
41—2.2 megohm, ¼ w. res.
42—05 µfd., 400 v. cond.
43—68,000 ohm, ½ w. res.
44—Second i.f. trans.
45—47,000 ohm, ¼ w. res.
46—260 µfd., 500 v. cond.
47A, 47B—500,000 ohm vol. control & sw.
48—004 µfd., 600 v. cond.
49—05 µfd., 400 v. cond.
50—4.7 megohm, ¼ w. res.
51—2200 ohm, ¼ w. res.
52—Power trans.
53—110 µfd., 500 v. cond.
54—02 µfd., 400 v. cond.
55—220,000 ohm, ¼ w. res.
56—1 µfd., 400 v. cond.
57—100,000 ohm, ¼ w. res.
58—470,000 ohm, ¼ w. res.
59—25 µfd., 400 v. cond.
60—2.2 megohm, ¼ w. res.
61, 62—6.3 v., 250 ma. dial lamp
63—004 µfd., 600 v. cond.
64—05 µfd., 600 v. cond.
65—4700 ohm, ¼ w. res.
66—560 ohm, ¼ w. res.
67—Tone control sw.
68—Output trans. for M-504205, R-504205, D-504205 speaker
69—6" electrodynamic speaker
70—Cone & voice coil for R-504205, M-504205, D-504205 speaker
71A, 71B, 71C—20/20/10 µfd., 25/400/400 v. elec. cond.
72—330 ohm, 2 w. wirewound res.

-50-

The New Model 257

ELECTRONIC ANALYZER

**THE MOST COMPLETE MULTI-RANGE,
MULTI-SERVICE UNIT EVER DESIGNED!!**

**IT'S A HIGH FREQUENCY A.C.
VACUUM TUBE VOLTMETER**

(A true A.C.-V.T.V.M. employing a 1-A3 Diode which together with a resistance-capacity network is built into a specially designed Polystyrene High Frequency Probe).

IT'S A D.C. VACUUM TUBE VOLTMETER


(At 11 megohms input resistance).

IT'S A CAPACITY METER

IT'S A REACTANCE METER

IT'S AN INDUCTANCE METER

IT'S A DECIBEL METER

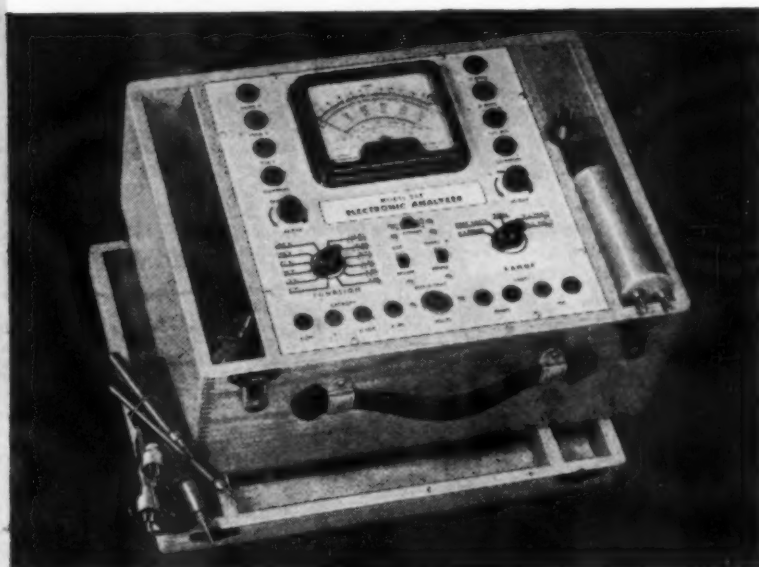

IT'S A 1000 OHMS PER VOLT V.O.M.

Measures D.C. Voltages (at 1,000 ohms per volt) up to 3,000 volts, A.C. Voltages (at 1000 ohms per volt) up to 3000 Volts, D.C. current up to 15 amperes, Resistance up to 1000 megohms.

Sixty, yes Sixty—separate ranges are provided by this most versatile unit ever designed.

Specifications:

A.C. V.T.V.M. VOLTS: (Input resistance—10 megohms shunted by 8 micromicrofarads. Freq. Range—50 cycles to 500 Megacycles.) 0 to 3/15/30/75/150/300 Volts.

D.C. V.T.V.M. VOLTS: (At 11 Megohms Input Resistance) 0 to 3/15/30/75/150/300/750/1500/3000 Volts.

D.C. VOLTS: (At 1,000 Ohms Per Volt) 0 to 3/15/30/75/150/300/750/1500/3000 Volts.

A.C. VOLTS: (At 1,000 Ohms Per Volt) 0 to 3/15/30/75/150/300/750/1500/3000 Volts.

D.C. CURRENT: 0 to 3/15/30/75/150/300/750 Ma. 0 to 3/15 Amperes.

RESISTANCE: 0 to 1,000/10,000/100,000 Ohms; 0 to 1/10/1,000 Megohms.

CAPACITY: (In MFD) .0005—.2, .05—20, .5—200.

REACTANCE: 10 to 5M (Ohms), 100—50M (Ohms), .01—5 (Megohms).

INDUCTANCE: (In Henries) .035—14, .35—140, 35—14,000.

DECIBELS: —10 to +18, +10 to +38, +30 to +58.

The Model 257 comes housed in a beautiful hand-rubbed oak cabinet complete with test leads, V.T.V.M. probes and instructions. Size: 6½" x 10¾" x 14".

\$64⁵⁰ Net

AVAILABLE FOR IMMEDIATE SHIPMENT FROM STOCK—20% DEPOSIT REQUIRED ON ALL C.O.D. ORDERS


MOSS ELECTRONIC DISTRIBUTING CO.

DEPT. RN-12 229 FULTON ST.
NEW YORK 7, N.Y.




ESSE Specials!

WILLARD LEAD ACID CELLS

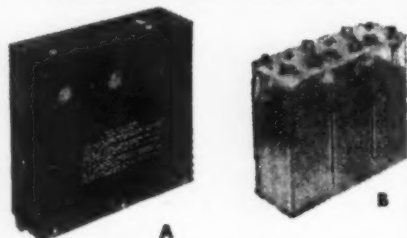


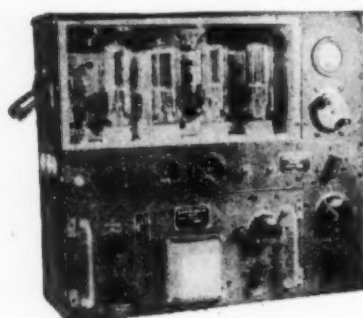- (A) 6 V. (In metal carrying case).....\$4.00
 (B) 6 V. (New) (Dry-charged)..... 3.00
 2 V. (New) (Dry-charged)..... 1.00
 (Add electrolyte specific gravity 1.625)
 (Drugstore)



BC-375E GE MOPA TRANSMITTER

with one tuning unit, choice\$17.50

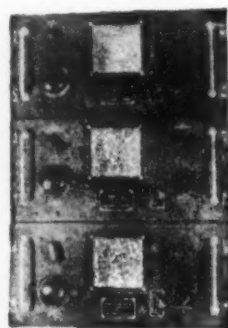

BC-375 TUNING UNITS

- TU-6B,
 TU-5B,
 TU-7B,
 TU-8B,
 TU-10B,
 TU-9B,
 TU-26B
 \$2.25


Antenna tuning unit BC-306A.....\$3.95
 Dynamotor PE-73C..... 4.95

HEADPHONES



HS-33 Headphones (New).....\$1.60
 HS-30 Headphones with cushions. Low impedance..... 2.25

(HRU) DC POWER SUPPLY

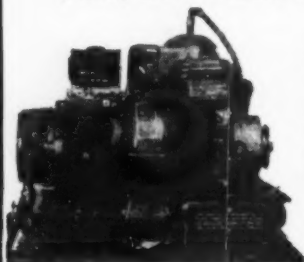


24-28 V. at 70 amp. 2000 watts gasoline engine generator with electric starter. Power supply which can be used to operate 24-28 V. equipment, to

start airplane engines, to charge batteries, as a welding machine, lighting system, or for an amateur radio station. Height, 21½"; Width 17½"; Length, 24½" and weight, 115 lbs.\$59.50

TELRAD 18-A FREQUENCY STANDARD

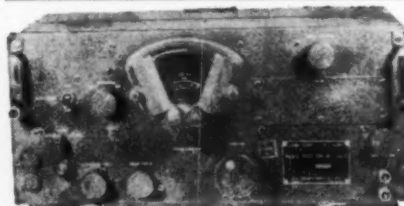Checks signals in the range of 100 Kc. to 45 Mc. with a high degree of accuracy. Self-contained power supply for 110, 130, 150, 220, and 250 V. 25-60 Cy. A.C. Complete with tubes, dual crystal, and instruction book. Brand new. One \$24.95 of the best buys on the surplus markets.



BC-348 COMMUNICATIONS RECEIVER, \$49.50

6 bands, 200-500 Kc. and 1.5-18 Mc. 2 stages RF, 3 stages IF, BFO, crystal filter, manual or AVC. Complete with tubes and 24 V. dynamotor. These receivers have been thoroughly checked in our workshop and found in excellent condition.

BC-348, 110 V. AC power supply, including simple conversion instructions. Complete with tube..\$8.95



COLLINS AN/ART-13 TRANSMITTER

A compact, light-weight, modern, high-powered transmitter. Frequency range 2-18-1 Mc. on any of its 11 autotune crystal controlled or master oscillator channels. December 1946 "Radio News" gives conversion data for converting 24 V. DC operation to 110 V. AC. All of these are in exceptionally fine condition, tested in our labs. Weight, \$88.50 67 lbs. (Dynamotor included).....

ALL EQUIPMENT ADVERTISED HEREIN IS UNCONDITIONALLY GUARANTEED TO THE CUSTOMERS' SATISFACTION TO THIS EXTENT: RETURN ANY ITEM ADVERTISED WITHIN FIVE DAYS AFTER DELIVERY FOR FULL REFUND EXCEPT TRANSPORTATION CHARGES (BOTH WAYS).

SELSYN INDICATORS



Selsyn Indicator (operates from 15-25 V. 60 cy. AC supply).
 5" model.....\$2.85
 3" model..... 2.00




BEAM ROTATING MOTORS

Used to rotate your beam antenna

Motor with mounting plates, etc.

\$14.50

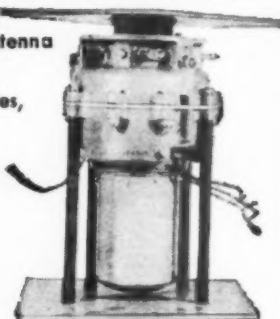

Motor only, 24-28 V.


\$9.95



- Power Supply (transformer 110 V.-30V.) (New).....\$4.95
- Telegraph keys (New)..... .45


ELECTROMODE HEATER..\$29.50

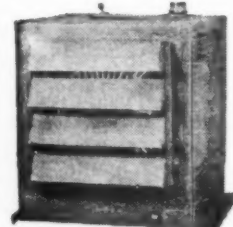This is a heater used to heat the trucks of the SCR-299 mobile units—which proved highly successful during the war. Operates from 110 V. AC or DC. 1,500 watts. Contains blower unit for forced air heating which can also be used for fan during warm weather. Thermostatically controlled with motor protect Thermatron. Can be used for room heating.




T-17-B CARBON MICRO-PHONES

(handmike)
 (New)..\$1.35

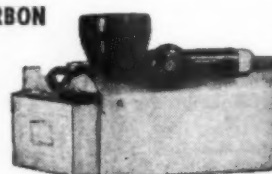

Headphone Extension Cords.....\$0.75


AIRCRAFT SUPPLIES

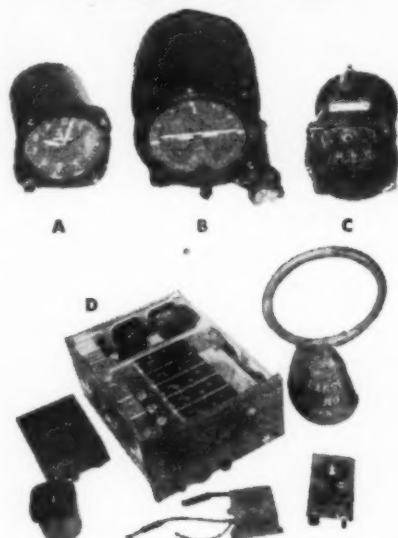

- (A) Sensitive Altimeters.....\$9.00
 (B) Gyro-horizons.....7.50
 (C) Magnetic Compasses.....6.00
 (D) MN-26 Radio Compass (New).....69.50
 SCR-269F Radio Compass (New).....69.50

LANDING LIGHTS

24 V. retractable
 600 watts. \$3.95

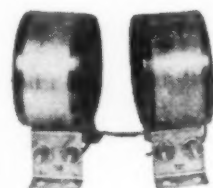

TUBE HEATERS

Can be used for various purposes.
\$0.75



Westinghouse
 O-500 Milliamps
 or O-10 Milliamps
 meters, choice
\$3.50



- SCR-522 Transmitter and Receiver. (Closing Out).....\$9.50
 RCA AVT-12A Aircraft Transmitters. (Closing Out).....3.00
 BC-929-A. (Closing Out).....4.00




SETCHELL-CARLSON Receiver BC-1206-C

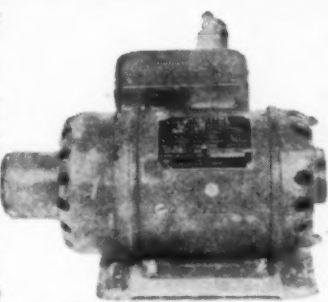
24-28 V. DC. Tubes, 3—14H7; 1—4R7; 2—8D7; 195-400 Kc. Size, 4"x4"x6 5/8" wide. 4 lbs. With manual. (New, in cartons).....\$5.95

MG-149F Inverter

(Holtzer-Cabot Elect. Co.)
 Input 24 V. DC 36 amps.
 Output 115 V. 400 cv.
 AC, 500 V. A. Output at 90% P. F.....\$5.00



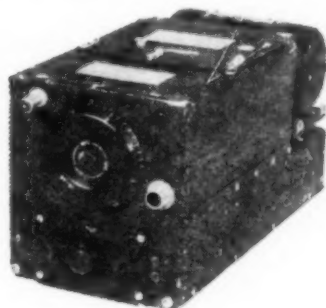PE-103 Generator. Dynamotor power supply. Operates from 6 or 12 V.; delivers 500 V. DC at 160 Ma. (Brand New).....\$8.95
 SCR-274N Command Set (ARC-5) components




Modulator with dynamotor.....\$2.75
 Receiver, 190-550 Kc. (BC-453-A).....3.25




Transmitter, 3-7 Mc. (BC-966-A).....\$3.25

ARB (CRV-46151) AIRCRAFT RADIO RECEIVER

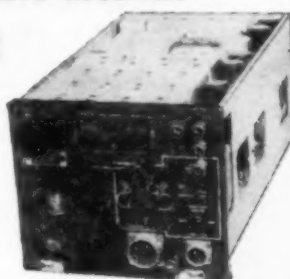6-tube, 4 band, super-heterodyne receiver with built-in dynamotor. Designed for reception of MCW (tone or voice) or CW within the frequency range 195 Kc. to 9.05 Mc. We bought a car-load of these in order to sell them at this price.....\$16.50



GENERATOR CONTROL BOX

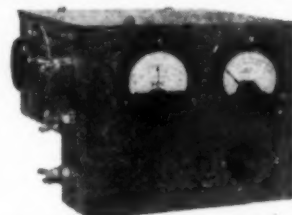

Contains one 2 1/2" round 0-300 AC voltmeter and one 2 1/2" round 30-0-30 DC ammeter. Also plug, switch, relay, condensers and choke coil. (New).....\$5.85

RECTIFIER RA-63-A

Battery charger or rectifier or power supply units. 110 V. 60 cy. input; 12 V. 8 amp. output. (New) \$19.75



BC-221 Frequency Meter

Covers 125-20,000 Kc. Battery or 110 V. AC vibrapack operated. Beautiful equipment. \$39.95

CONDENSER

(Aerovox) 1 Mfd. 10,000 V.....\$21.50



Radio Co.
 130 W. New York St.
 Indianapolis 4, Ind.

Unless Otherwise Stated, All of This Equipment Is Sold As Used
CASH REQUIRED
WITH ALL ORDERS
 Orders Shipped F.O.B. Collect



Specials!



OXYGEN TANKS

Aviators oxygen breathing bottles. Withstands 500 lbs. pressure. Non-shatterable. Choice of two above types A or B.....\$6.95




BC-1158 TRANSMITTER AND MODULATOR


Made by Bendix for airborne operation. Designed for remote control. Power source 28 V. DC input. (Not included). Operates in any place in the 53-60 Mc. and 80-88 Mc. frequency band. Is crystal controlled (crystals not included). Has RF stages, amplifier and driver section, contains 4-B15's and 10-12SN7 tubes, 1-0/150 DC millamp Weston meter which can be switched to various circuits. Has exhaust fan for ventilation. Can easily be converted to operate on several frequency bands. Size \$27.50 12"x8"x18", 45 lbs. Limited quantity.....\$27.50

INTERPHONE AMPLIFIER

Type AM-26/AZC

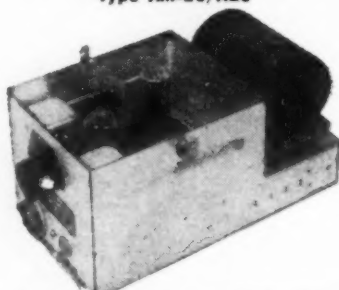

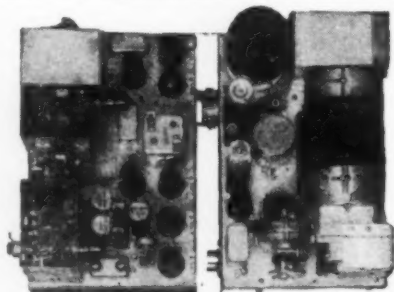
with 28 V. DC dynamotor. Contains 2-12A6 and 2-12J7 tubes. Easily converted for phonograph or intercommunication amplifier.....\$1.75



BC-966-A IFF


Approximately 2 meter frequency operation. 14 tubes, 350 V. DC dynamotor, 12 V. DC. input. Contains voltage regulators and many other fine parts. Worth more for parts than price asked...\$4.75

APQ-13 RECEIVER

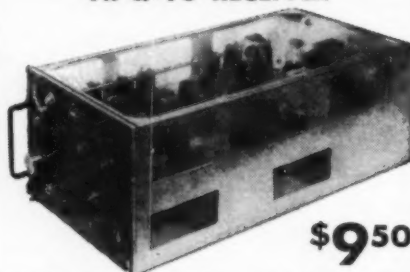

\$950

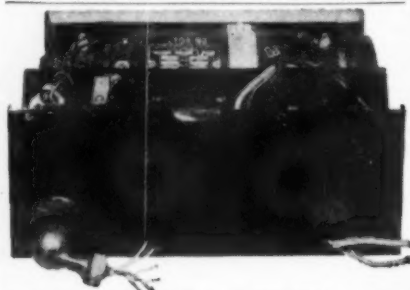17 tubes, 13 precision resistors, potentiometers, condensers, transformer, knobs, switches, pilot light, fuses.....\$9.50



Dynamotor unit MG-1A for SCR-522 transmitter and receiver.....\$3.75


DETROLA AIRCRAFT RECEIVER

28 V. DC operated, 200-400 Kc. Good condition.



\$375

TUBE CHECKER

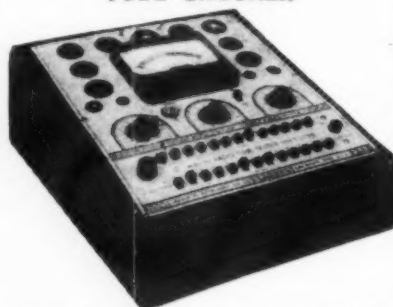


(Universal Instrument Co.) Counter model 501. Tests all tubes in use today. Brand new with manual and factory guaranteed.....\$37.50

ALL EQUIPMENT ADVERTISED HEREIN IS UNCONDITIONALLY GUARANTEED TO THE CUSTOMERS' SATISFACTION TO THIS EXTENT: RETURN ANY ITEM ADVERTISED WITHIN FIVE DAYS AFTER DELIVERY FOR FULL REFUND EXCEPT TRANSPORTATION CHARGES (BOTH WAYS).


BC-357

MARKER BEACON RECEIVER

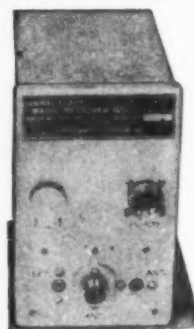Ideal for controlling remote circuits for model aircraft, boats, etc. Operates from 75 Mc. Signal easily altered to 2 meter band. Tubes used and included: 12C8 and 12SQ7. Also sensitive relay. Circuit diagram included inside case. Size, 5 1/2"x3 1/4"x5 1/4". For 24 V. DC operation. \$1.95




IF AMPLIFIER STRIP

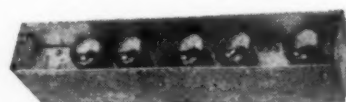

19 Mc. contains 5 Western Electric 7-17A tubes. \$3.95


T-39/APQ-9 RADAR TRANSMITTER

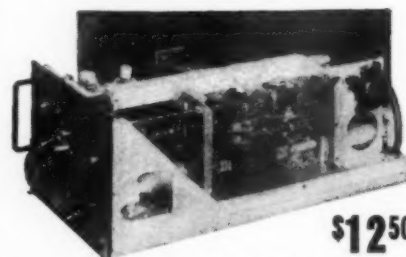

\$1250

Contains many excellent parts for the VHF experimenter such as a cavity oscillator using 2-RCA 8012 tubes rated at full output to 500 Mc. Tubes are forced air cooled by 24 V. DC motor, which is easily converted for 110 V. AC operation. Other valuable parts such as a pair of 807's, 2-6AC7, 1-931 and 1-6AG7 tubes, ceramic switch, potentiometers, gears, revolution counter, etc.


APN-1 RADIO ALTIMETER

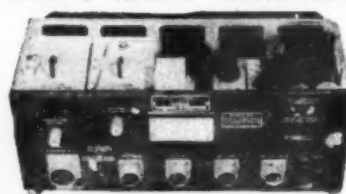


A complete 460 Mc. radio receiver and transmitter which can be converted for ham or commercial use. Tubes used and included: 4-12SH7, 3-12SJ7, 2-6H6 1-VR150, 2-955, 2-9004. Other components such as relays, 24 V. dynamotor, transformers, pots, condensers, etc. make this a buy on which you cannot go wrong. Complete as shown in aluminum case 18"x7"x7 1/4". \$8.95



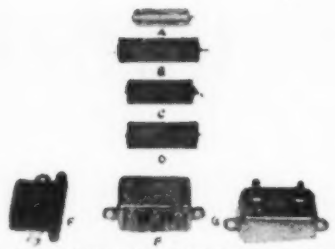
(A) Lapp 800-lb. safe working load insulators. \$0.95
(B) Lapp heavy duty insulators with strap mounts.....1.65



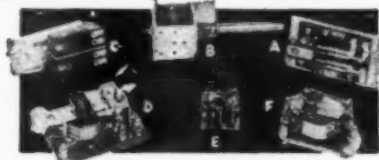
- (A) Condenser, .14 Mfd. 50 V. (metal clad). (New) 100—\$2.50
 (B) Condenser, .16 Mfd. 150 V. (filter condenser). (New)20
 (C) Condenser, .05 Mfd. 400 V. (New)05
 (D) Condenser, .1 Mfd. 400 V. (New)05
 (E) Condenser, .3 Mfd. 50 V. DC (Bathtub). (New)05
 (F) Condenser, 3x.1 Mfd. 400 V. DC (Bathtub). (New)05
 (G) Condenser, (Aerovox) .02 Mfd. 600 V.05



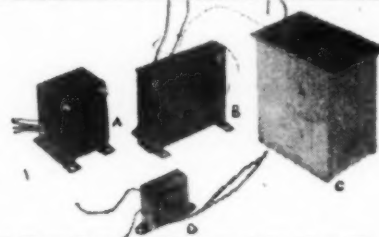- (A) Relay (R.M.) 110 V. 60 cy. A. operated DPST. (New) \$0.75
 (B) Relay, 110 V. 6 cy. AC plunge type for door interlock. (New)85
 (C) Relay, (Clare) 50 V. .6045 amp. 11,300 ohms with 2 micro-switches. (New)75
 (D) Relay, (Leach) type 1253-DEW, 24 V. DC 150 ohms DPST (New)50
 (E) Relay, 6 meg. 5000 ohm DC resistance SPDT85
 (F) Relay, (Leach) type 1127-FR 110 V. 60 cy. DPST. (New)75



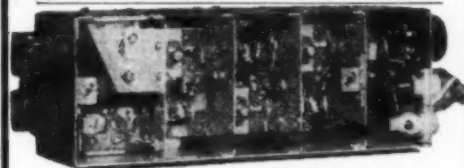- (A) Filament Transformer, 110 V. 60 cy. pri.; Sec. 5 V. and 6 V. Center Tapped (cased). (New) \$0.95
 (B) Transformer 110 V.-30 V. (New). Made by Esso for beam motor 4.95
 (C) Power transformer completely cased. 110 V. 60 cy. pri.; Sec. has 600 V. CT 105 Ma. Also 5 V. at 3 amp. plus 2.5 V. at 5 amp. and a 6.3 winding. (New) 1.65
 (D) Transformer for Selsyn beam indicators 1.95




ARR-1 RECEIVER, 334-358 MC. \$4.95
 Ideal for mobile receiver or converter on 2 or 6 meter band. Contains 4-954 type acorn tubes, connectors, etc.



WIRE

- (A) 3 stranded conductors inside of a shield, about 30" long. Each \$0.10
 (B) 2 conductors of stranded wire, each strand about No. 8 gauge rubber covered twisted and cloth braid outer cover. ft. .07
 (C) Heavy duty rubber covered, 2 stranded conductors, flexible. Ideal for 110 V. AC power leads to heavy electrical machinery. ft. .10
 (D) 3 Conductors of No. 20 enameled cotton covered wire, color coded, completely shielded, moisture and fungus proof. Ideal for Intercom work. 50 ft. and 250 ft. rolls. ft. .03
 (E) 4 strands of braided wire, each rubber covered and color coded, one strand being shielded, cotton and cambric outer wrapping. ft. .05
 (F) Same as above, except the complete cable shielded. Minimum wire order 100 feet. May be assortment of above wire. ft. .07 1/2

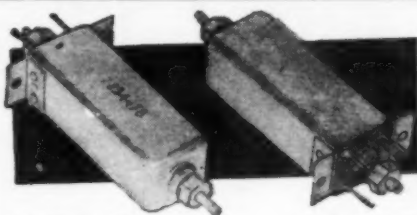
- (F) Condenser, .25 Mfd. 400 V. (New) \$0.05
 (G) Condenser, .125 Mfd. 400 V. (Metal cased) (dual condenser) (New)05
 (H) Condenser, 1.75 Mfd. 50 V. (New)05
 (I) Condenser, .3 Mfd. 600 V. (metal cased). (New)05




IF Transformer, 19.2 Mc. ea. \$0.20



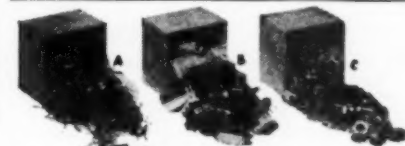- (A) Throat Mikes 7 for \$1.00
 (B) Jeweled Pilot Assembly. Candelabra, screw base for 110 V. lamp. Mounts in 1" hole. (New)25
 (C) Telegraph key J-37 (New)35
 (D) Phone Jacks for PL-55 Plug 107 1/2
 (E) National Velvet Vernier dial drive, 6-2 reduction ratio75
 (F) Ceramic grooved coil forms. 5" length, 2" diameter, 30 grooves15
 (G) Millin 807 tube shields25
 (H) 813 tube shields35



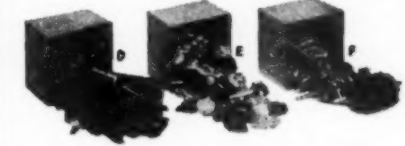
- (A) Resistor kit composed of 150 or more assorted wattages. Containing various resistors of up to 10 megohms. Many with gold bands. An honest-to-goodness bargain. Box \$2.65
 (B) Condenser Kit. Contains assortment of 25 various condensers including 2-2Mfd. 600 V. filters, 1-1000 Mfd. 15 V. filter 4-1 Mfd. 400 V. paper by-pass, 3-3-gang midge trimmers, etc. 2.65
 (C) Hardware Kit containing about 5 lbs. of radio hardware including nuts, bolts, washers, shafts, gears, grommets, lugs, screws, spacers. It is a gold-mine of invaluable parts 1.95



- (D) Resistor mounting lugs and terminal strip kit. Assorted sizes and snappers. Many, Many \$11.00
 (E) Tube Socket Kit. 25 or more assorted sockets having various usable sizes 1.50
 (F) Switch Kit containing assortment of 10 rotary and toggle switches 1.25



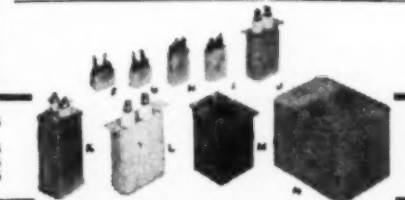- (A) Condenser (Solar) 10 Mfd. 1000 V. (New) \$2.00
 (B) Condenser (GE Pyranol) 8 Mfd. 1000 V. DC. (New) 1.75
 (C) Condenser (Chi. Ind. Cond. Corp.) 4 Mfd. 2000 V. (New) 2.50
 (D) Condenser (Cornell-Dubilier) 1 Mfd. 4000 V. (New) 3.00
 (E) Condenser (Chi. Ind. Cond. Corp.) Dual 8.5 Mfd. 1000 V. (New) 3.50



- (J) Condenser, (GE Pyranol) 2 Mfd. 600 V. (New)50
 (K) Condenser, 2 Mfd. 600 V. (Aerovox). (New)35
 (L) Condenser, 4 Mfd. 600 V. DC (GE Pyranol). (New)50
 (M) Condenser, 4 Mfd. 300 V. (New)35
 (N) Condenser, 30 Mfd. 330 V. AC (GE Pyranol). (New) 3.00




A. RESISTOR

Wire wound adjustable divider resistor. 100 watt, 5,000 ohms. (New) ea. \$0.40

B. BL-SELENIUM RECTIFIER

110 V. AC input; 110 V. DC output. .75 amp. rating. 1.35

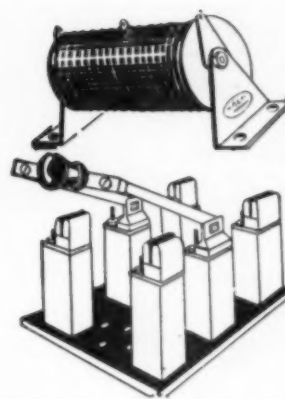C. Antenna Switches, double pole, double throw Size 8x4x2" (New) 2.00
 Same as above, except SPST, size 8x4x2" (New) 1.00



FUSES

Cartridge type, packed 10 to a box.

6 Amp. 250 V. Non-renewable. Box \$0.40



3 Amp. 250 V. Non-renewable. Box \$0.40

30 Amp. 250 V. Renewable. Box .75


3 Amp. 250 V. Renewable. Box .75

Buss fuses, type 3AG, 10 amp. glass fuses, ea \$0.02

Per hundred. 1.35

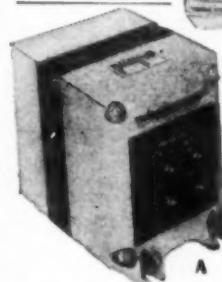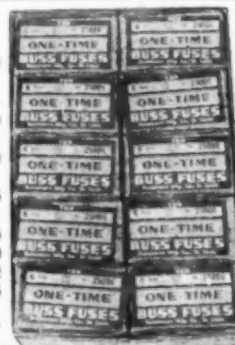

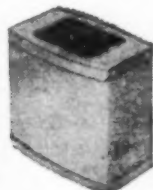
- (A) Thoradson Transformer type T-45920, Pri. 220 V. 60 cy.; Sec. 530 V. Center Tapped \$4.95
 (B) Filament Transformer GE 746/175; 110 V. 60 cy. Sec. 6.3 V. at 13 amps and 6.3 V. at 1.2 amp. 2.95



Rectox Rectifier

32 V. AC input, 24 V. DC output, 5 amps. (New).

\$3.75

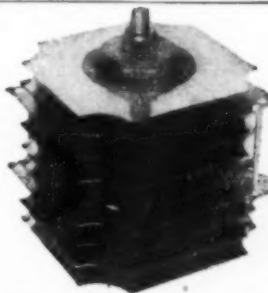

- Sylvania Crystal type 1N29 \$0.35
 AN/PRS-1 Mine Detector. (New) 9.50
 SCR-625 Mine Detector. (New) 67.50



Radio Co
 130 W. New York St.
 Indianapolis 4, Ind.

Unless Otherwise Stated, All of This Equipment Is Sold As Used
CASH REQUIRED
WITH ALL ORDERS
 Orders Shipped F.O.B. Collect

Available Again!



135-24

AND BETTER THAN EVER BECAUSE IT'S STEATITE!


It's good news that the popular JOHNSON 135-24 Stand Off Insulator is again available—good news, too, that it is now made of STEATITE!

STEATITE, a highly efficient insulating material, superior in every respect to porcelain, is now also being used in the manufacture of several other standard JOHNSON insulators.

Why is STEATITE better? Because its dielectric losses are but a fraction of that of porcelain.

While STEATITE assures lower loss insulation at any frequency, it is outstandingly efficient on the high frequencies. There is only a slight increase in price for JOHNSON insulators of STEATITE.

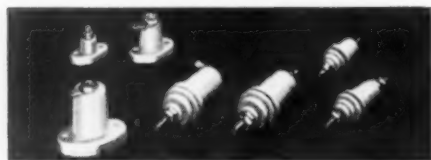Available, in addition to the popular JOHNSON 135-24 Stand Off Insulator shown above, are the following JOHNSON insulators:



135-20		135-42
135-20J	135-40	135-42J
135-22	135-40J	135-44
135-22J		135-50

SEE THEM AT YOUR JOBBERS!

New Catalog On Request

JOHNSON
a famous name in Radio
E. F. JOHNSON CO. WASECA, MINN.

DON'T BE A DAGWOOD

Wipe the sleep out of your eyes and wake up to new business opportunities awaiting alert men.

YES, it is always the same with our comic friend, Dagwood. He's late to start, flies off to work in a whirlwind of frantic haste, only one object in mind day after day—get to work on time. Not that we decry the fine trait of promptness, but the daily routine of getting to work which offers no variations is liable to be a hazard to business progress.

If you are in the habit of following an identical routine every morning, catching the same bus, sitting in the same seat, driving down the same street, walking to your store from the same direction—shake yourself loose, snap out of it, upset your jigsaw puzzle and start putting it together afresh each day. For instance, try this antidrum prescription.

MONDAY: This morning get away just ten minutes earlier. Sure it's the toughest day in the week to get going. That Sunday of lolling around, relaxing, playing, has put you out of the mood for working. This is the morning you think how nice it will be after you've retired and don't have any Monday mornings to worry about—ever. It's a tough one to face anyway, so why not shock yourself into action with that ten minutes earlier start. After all, what's ten minutes in a lifetime. It may be the most profitable ten minutes you will spend all week. Why? How are you going to use it? Well, let's call it the weekly "spy game." To play this ten minute game you'll need: 1. A list of addresses of competitive stores (be sure to include chain and department stores). 2. A note book. 3. A good pair of eyes, and 4. A curiosity that outdoes any child you know. If you're driving, the game may cover more territory. If you're riding on a bus or streetcar, this necessitates getting off at a different corner than usual. If you're walking, it means changing your usual route—the additional fresh air will do you good anyway.

Now you've made up the list of your competitors so you can drive or amble past their stores, in order of appearance, working on toward your own shop in an organized fashion. As you pass each store, you stop long enough to take a good look. What do you see? Does the over-all store front look the same as the last time you saw it, or has the owner painted or reconstructed? Has he put up a new permanent painted or electrified sign or a new valance decoration on his show window? Get out your note book and pencil, brother, if he has and jot down just what's happened. Now take a long searching look through the show window. What's he featuring? A new product you didn't know he han-

dled? A new way of displaying an old product? New display cards? New sales messages? New lighting? No, no, don't just criticize. Examine and pick out the good points. Jot 'em down and make a note of how it occurs to you that you might do it better. He's after the same dollars you're hoping to pile in your till. What has he done that you can improve on? Sure, maybe you do think he's a dope, but give the devil his due when he comes up with a good one. Maybe you've had a chance to peek inside. What's that—new display tables, a new coat of paint, new lighting fixtures? "Well, well—he's not going to outsmart me" say you. Don't trust your memory, make notes of what you see that's good. Sure, make notes of what you see that's bad, too, and be certain you're not doing the same thing.

Time's up. That extra Monday morning ten minutes has given you a glimpse of a lot of things you'd have missed if you dashed right down to your own shop.

Now as you approach your own store you start to make mental comparisons. You've spotted some things you're going to do to your shop right away—after all here it is first thing Monday morning and there's no time like the present to get off on the right foot to arrange to trap the prospects who may go to buy from your competitor because of what you saw a few blocks away.

TUESDAY: This morning as you fling open your store door you glance with satisfaction at that fresh idea in the window, inspired by yesterday's spy game. Not bad—maybe a few finishing touches you can put on it today. This morning you're holding a meeting with your accounting department. Maybe it's a talk with yourself or maybe with an employee who handles these vital details for you. You're going to say "By this morning we have completed our summary of last week's business and the month to date. Let me see those comparative figures. How much business did we do last week on radios, on traffic appliances, on heavy appliances, on specialty sales? How much have we done this month vs. last month to date? What was our margin of profit on each category? How does our inventory stand? What were the cash sales? Did credit business or accounts receivable stay in balance with our cash sales? What is the total of accounts payable?"

Now you know just where you're going to place your selling effort for the rest of the week. Now you know just what element in your business

BLEEDER RESISTOR

50,000 ohm 100 watt.....**89c**



VERNIER TUNING GEAR BOX

18:1 and 36:1 Ratio. Ideal for osc. tuning section of SCR-522.....**\$2.49**

SELENIUM RECTIFIERS Full Wave Bridge Type

INPUT	OUTPUT	
up to 18v A.C.	up to 12v D.C.	1 Amp. \$1.95
up to 18v A.C.	up to 12v D.C.	5 Amp. 4.45
up to 18v A.C.	up to 12v D.C.	10 Amp. 7.45
up to 18v A.C.	up to 12v D.C.	15 Amp. 9.95
up to 18v A.C.	up to 12v D.C.	30 Amp. 14.95
up to 36v A.C.	up to 28v D.C.	1 Amp. 3.45
up to 36v A.C.	up to 28v D.C.	5 Amp. 7.45
up to 36v A.C.	up to 28v D.C.	10 Amp. 12.45
up to 36v A.C.	up to 28v D.C.	15 Amp. 18.95
up to 115v A.C.	up to 100v D.C.	25 Amp. 2.95
up to 115v A.C.	up to 100v D.C.	6 Amp. 6.95
up to 115v A.C.	up to 100v D.C.	5 Amp. 19.95

HALF WAVE TYPE

up to 196v A.C.	up to 158v D.C.	.075 Amp. \$1.95
up to 395v A.C.	up to 350v D.C.	.075 Amp. 2.95
up to 396v A.C.	up to 330v D.C.	.110 Amp. 3.95

DYNAMOTORS

(Ideal for Mobile)

Input: 6 or 12 volts.
Output: 500 VDC at 160 ma.
Voltage Regulated and Filtered.
PE-103 (slightly used).....**\$5.95**

Input: 24-28 volts. Output: 150 VDC at 10 ma. 14.5 VDC at 5 amp.
Voltage Regulated and Filtered.
DA-3A (slightly used).....**\$4.95**

RCA-158 OSCILLOSCOPE

Brand New—110v 60 cyc. 5 inch tube. Complete ready to operate. Regular price much higher. Limited Quantity**\$99.50**

SCR-522 100-156 MC.

RECEIVER AND TRANSMITTER

Licensed for Railway and Taxicab Use

The ideal all-purpose transmitter-receiver for work in the 100-156 mc. spectrum. Four channel push-button operation, crystal-controlled, AM, phone, mobile or fixed station service. Ideal for amateur, aircraft, marine, railroad, taxicabs, police and experimental. Amplitude modulated—High transmitter output. Receiver has 10 tubes and transmitter has 7 tubes including two 832's. 60 cycle operation. Complete conversion instructions and schematic furnished with each unit. Tube complement—2-832; 3-12A6; 1-6G6; 2-6557; 1-12J5GT; 1-12C8; 1-9002; 3-9003; 1-12AH7-GT and 3-12SG7. Complete with tubes.....**\$14.95**

BC-375-E TRANSMITTER

Operates from 200 kc—12.5 mc complete with all tubes, dynamotor, six tuning units and one antenna tuning unit.

LIKE NEW.....**\$39.50**

OIL CONDENSERS:

Standard Brands, A-N Inspected

All Ratings, D.C.

1mfd. 600v. \$0.35	2mfd. 2000v. \$1.75
2mfd. 600v. .35	3mfd. 2000v. 2.75
4mfd. 600v. .60	4mfd. 2000v. 3.75
8mfd. 600v. 1.10	15mfd. 2000v. 4.95
10mfd. 600v. 1.15	1mfd. 2500v. 1.25
1mfd. 1000v. .60	25mfd. 2500v. 1.45
2mfd. 1000v. .70	5mfd. 2500v. 1.75
4mfd. 1000v. .95	15mfd. 3000v. 1.95
8mfd. 1000v. 1.95	1mfd. 3000v. 2.25
10mfd. 1000v. 2.10	25mfd. 3000v. 2.65
15mfd. 1000v. 2.25	5mfd. 3000v. 2.85
20mfd. 1000v. 2.95	1mfd. 3000v. 3.50
24mfd. 1500v. 6.95	12mfd. 3000v. 6.95
25mfd. 2000v. 1.05	2mfd. 4000v. 6.95
5mfd. 2000v. 1.15	1mfd. 5000v. 4.95
1mfd. 2000v. .95	1mfd. 7000v. 2.95

SPECIAL! 2 mfd. 3000v.....**\$4.45**

TUBES (Brand New)

Army-Navy Inspected

1B24... \$ 4.95	311... \$ 1.98
2AP1... 2.25	371B... 5.95
2C40... 1.19	450TH... 39.95
2D21... .89	703A... 7.95
2V3G... 1.25	705A... 3.95
2X2... .84	715B... 7.95
3AP1... 3.00	721A... 4.35
3BP1... 2.95	726/AC... 7.50
3E29... 2.95	801... 1.49
5BP1... 3.95	802... 1.98
5BP4... 4.95	803... 8.95
5CP1... 3.95	804... 9.95
5JP1... 11.95	805... 4.95
5LP1... 8.95	806... 14.95
5R4GY... .98	807... .95
5Y3... .41	808... 2.95
6AB7... .99	809... 1.50
6AC7... .99	810... 5.95
6AG5... .99	811... 1.95
6AG7... .99	812... 3.15
6AJ5... .99	812H... 6.90
6AK5... .90	813... 8.95
6AL5... .99	814... 4.45
6AR6... 1.29	815... 3.95
6B4G... 1.29	826... 2.25
6C4... .69	829-A-B... 3.00
6C5... .49	832... 2.25
6F6... .89	833A... 39.50
6F6G... .59	834... 2.95
6J4... 1.60	835... 2.95
6J5... .65	836... 1.75
6J6... .89	837... 2.50
6L6... 1.23	838... 3.95
6L7... .98	841... 1.20
6N7... 1.02	861... 69.50
6SH7... .59	866... .75
6SL7... .89	872A... 2.50
6SN7... .69	884... .98
6SR7... .89	885... .98
7A4... .81	902... 2.25
7F7... 1.25	913... 3.00
7L7... 1.59	954... .75
9JP1... 3.95	955... .75
10Y... .98	956... .75
12X3... 1.50	957... .75
15E... 1.50	958... .75
HK24G... 1.75	959... .75
28D7... .98	1005... .69
30... .75	1616... 2.95
35T/TG... 3.50	1619... .75
VR90... .75	1624... .90
VR105... .75	1625... .75
VR150... .75	1626... .75
100TH... 7.95	8001... 6.49
100TS... 3.00	8003... 9.95
211... 1.25	8005... 4.95
75T... 2.95	8011... 1.95
250TH... 14.95	8016... 1.65
257B... 6.49	8025A... 4.95
304TH... 9.95	1654... 1.98

TRANSFORMERS—115 V 60 CYC. HI-VOLTAGE INSULATION

1600v at 4ma; 700v at 150ma; 6.3v at 9A... \$8.50
3710v at 4ma; 2x2.5v at 3A... 9.95
2500v at 10ma... 6.50
2150v at 15ma... 6.50
1750v at 4ma; 6.3v at 3A... 7.95
1540v at 4ma; 340-0-340 at 240ma... 7.60
550-0-550v at 150ma; 5v at 3A; 2x6.3v at 5 amp... 7.95
500-0-500v at 100ma; 5v at 3A... 4.95
442-0-442v at 1000ma... 9.95
425-0-425v at 150ma; 6.3v at 7.5A; 6.3v at 3A; 5v at 3A... 5.95
400-0-400v at 200ma; 5v at 3A... 4.95
350-0-350v at 150ma; 6.3v at 6A; 5v at 3A; 78v at 1A... 4.95
350-0-350v at 35ma-XLNT for VOLT-DBLR... 1.49
300-0-300v at 65ma; 2X 5v at 2A; 6.3v at 2½A; 6.3v at 1A... 3.49
325-0-325v at 120ma; 10v at 5A; 6.3v at 7A... 3.49
350-0-350v at 85ma; 2X 5v at 2A; 6.3v at 6A; 6.3v at 3.75A... 7.50
250-0-250v at 100ma; 2X 6.3 at 4A; 6.3v at 5A; 6.3v at 1A... 4.95
2.5v at 2A; 5v at 3A... 2.95
2.5v at 10A... 3.25
5v at 115A... 9.95
5v at 190A... 17.50
6.3v at 6.6A... 3.25
6.3v at 3.1A... 1.95
6.3v at 21.5A; 6.3v at 2A; 2.5v at 2A... 6.95
1600v @ 2 ma; 2.5v @ 1.75A; 6.3v @ .6A... 9.95

FILTER CHOKES

HI-VOLTAGE INSULATION

4 Hy at 250ma... \$1.98	12 Hy at 300ma... \$3.95
10 Hy at 250ma... 2.49	15 Hy at 100ma... 2.95
10 Hy at 400ma... 4.95	15 Hy at 125ma... 3.25
12 Hy at 100ma... 2.95	30 Hy at 70ma... 1.95
4 Hy at 600ma... 5.95	1 Hy at 5 Amps... 6.95
10 Hy at 200ma... 1.98	15 Hy at 75ma... 1.49
200 Hy at 12ma... 1.39	10/20 Hy at 85ma... 1.95

HIGH CAPACITY CONDENSERS

4000 mfd.—18WVDC... \$1.95
4000 mfd.—30WVDC... 2.95
1000 mfd.—15WVDC... .99
2000 mfd.—50WVDC... 1.95

ART/13 MODULATION KIT

Consists of driver, speech amplifier, sidetone amplifier assembly and modulation transformer. With complete diagram for the famous ART/13 transmitter. **\$8.95**
SUPER BUY at.....

PORTABLE F M TRANSMITTER

(SONOBUOY)

Operates on standard 67½v Minimax and 1½v Flashlight cells. Frequency 72 mc (easily doubled to 144 mc). Complete with 5 tubes and diagram. (Less batteries.)
EXCEPTIONAL BUY at.....**\$12.95**

GIBSON GIRL TRANSMITTER

(SCR-578B)

Emergency life transmitter. 100% complete; includes balloon, hydrogen generator, kite, signal lamp, antenna and instruction manual. Self-powered merely by turning crank. Automatically transmits S.O.S. on 500 cycles. **\$29.95**
FULLY GUARANTEED.....

ALL PRICES SUBJECT TO CHANGE WITHOUT NOTICE

All merchandise guaranteed. Mail orders promptly filled.

All prices F.O.B. New York City. Send money order or check.

Shipping charges sent C.O.D. Minimum order \$5.00.

RADIO HAM SHACK Inc.
63 DEY STREET • NEW YORK 7, N. Y.

ATTENTION!

INDUSTRIALS—LABS—
SCHOOLS—AMATEURS

Let us quote on components and equipment that you require. We have too many items to be listed on this page. Place your name on our mailing list now for new catalog.

Senco Successfully Continues Buyers Dividend Plan To Include An Exclusive Radio and Radio Phonograph Combination Buy

4 TUBE AC-DC SUPER- HETERODYNE RADIO



featuring
Angle Dial
for easy
tuning

This model is a four tube superheterodyne receiver, AC-DC, giving six tube performance by the use of multi-purpose tubes, covering the frequency range of 530 to 1600 kilocycles and incorporating the features of beam power output, super-sensitive, high efficiency, permanent-magnet dynamic speaker, automatic volume control, and numerous other features producing improved performance. Complete with tubes...

\$13.95

5 TUBE AC SUPERHETERODYNE RADIO PHONO COMBINATION



This model is a five tube superheterodyne receiver, giving seven tube performance by the use of multi-purpose tubes, covering the frequency range of 540 to 1700 kilocycles Standard Broadcast and incorporating the features of beam power output, tone control on both radio and record player operation, super-sensitive, high efficiency, permanent-magnet dynamic speaker, automatic volume control, loop aerial and numerous other features producing improved performance. Complete with tubes...

\$29.47

100,000 RADIO TUBES

Every Tube guaranteed. Every Tube in carton.

Type	Each	Each	Type	Each	Each
1U5	36	30	7AF7	44	35
1V	45	40	14K7	44	35
1L4	53	49	12AGT	45	37
2A3	65	55	12AT6	50	45
2A2	72	72	12BA6	50	45
3A4	69	59	12BE6	50	45
3Q5GT	79	70	12C8	49	45
5U4G	80	40	12SGT	49	39
5W4GT	40	38	12K7GT	45	39
5Y3GT	40	35	12K8	65	59
5Y4G	40	37	12Q7GT	45	39
6A7	50	45	12SA7GT	40	32
6AA6GT	50	44	12Q7GT	40	32
6AC7	55	50	12SK7GT	45	35
6AK5	79	69	12SJ7GT	55	50
6AQ7 6AK7	89	79	26	39	30
6B7	55	49	27	42	37
6C5GT	55	45	41	40	35
6C6	45	32	42	42	38
6C8Q	45	37	43	54	49
6D6	45	37	45	39	39
6F6GT	45	39	47	49	39
6H6GT	45	39	58	49	39
6J5GT	45	39	57	45	39
6J7GT	42	38	58	45	39
6K6GT	45	39	71A	39	29
6K7GT	45	40	75	59	39
6L6	95	89	76	45	39
6Q7GT	47	39	77	40	32
6U7G	40	35	78	40	32
6VAGT	45	40	80	40	38
6X5GT	49	40	83V	99	89
6SA7GT	45	37	84 6Z4	45	36
6SJ7GT	44	37	85	49	45
6SK7GT	44	37	25L6GT	49	39
6SL7GT	45	37	25Z5	45	45
6SN7GT	49	47	25Z6GT	45	39
6S07GT	44	37	35W4	43	40
6S0T	45	39	25Z3	44	35
6ZY5G	45	39	25Z5GT	43	39
7B6	44	35	35L6GT	45	39
7B7	44	35	50L6GT	50	45
7C8	44	35	11Z23	55	45
7C7	44	35	11Z26GT	99	89
7V4	44	35	50B5	42	32
7X7	44	35	32L7GT	59	49

AC PHONO MOTOR AND PICKUP 60 cycles, 115 volts with Turntable. **\$4.35** Complete



OUTPUT TRANSFORMERS

50L6	45 ea.
3Q5	45 ea.
6V6	50 ea.

SPEAKERS

4" P.M. Speaker	\$1.19
5" P.M. Speaker	1.15
6" P.M. Speaker	1.55
8" P.M. Speaker	2.75
12" P.M. Speaker	
Alnico 5 Magnet	5.49
Set of 100 assorted insulated resistors popular	\$1.79
ohmages, 1/2, 1/4 & 1 watt.	
500 ohm V.C. with Switch 2 1/4" Shaft. Popular	ea. \$0.40
40 x 40 Electrolytic Cond. 150V.	.49
50 x 30 Electrolytic Cond. 150V.	.49
Mallory—6 Volt 4 Prong Auto Vibrator	1.19 ea.
2 Volt V-brator	.99 ea.
829 Push Pull twin-unit. Beam power amplifier	\$1.49 ea.
tube	

25% Deposit on All Orders—Bal. C.O.D.
All Prices F.O.B. New York City
WRITE FOR LATEST BULLETIN

**SENCO RADIO INC. 96 WARREN ST
BEEKMAN 3-6498 NEW YORK 7, N.Y.**

EASY—TECHNICAL—INTERESTING LEARN THE E-T-I WAY

Electronic Technical Institute
A Resident School

Learn RADIO-ELECTRONICS
APPROVED FOR TRAINING UNDER GI BILL

Electronic Technical Institute combines use of daily laboratory training in construction and design of FM and AM transmitters and receivers—2-way radio. Vitalized classroom work includes training with SOUND MOTION PICTURES. Previous experience not necessary to enroll. Approved for veterans, and payment plan offered for non-veterans. 5-hour morning or afternoon classes and evening classes from 7 to 10 P.M. Many earn additional income in spare time by installing or repairing transmitting or receiving equipment in yachts, homes, and automobiles. We have a free student placement service for your convenience.

Advanced training courses include preparation for passing commercial F.C.C. examinations. Resident evening classes in Amateur Radio, also Amateur Radio Correspondence Courses.

ELECTRONIC TECHNICAL INSTITUTE

771 VENICE BLVD., RN-11 Richmond 9573 LOS ANGELES 15, CALIF.

should occupy the precious manhours you and your staff have to spend for the rest of the week. This early Tuesday morning meeting with your accounting department has given you readings on your trade winds so you know just how to apply pressure to the helm of your commercial ship to keep it on course toward success. You'll never drift into bankruptcy if you'll look your business barometers squarely in the face every Tuesday morning.

WEDNESDAY: Here is the middle of the week. Time to call in the advertising and sales promotion manager. Are plans ready for the special promotion that's going to capture the dollars of next weekend's consumer spending? What seasonal opportunities are ahead? How are you going to make the most of national events which are shaping the thinking of the public? Has the window display, the store decoration, been planned for next week? Today's the day to plan it because it is going to take all the time you can spare from selling on Thursday and Friday to get the props together.

"How long since we've had a direct mail campaign?", you ask. "Have you checked Joe and Jim and Bill from the jobbing houses to find out whether there are any cooperative ad deals coming up?" "Let's take a look at all the advertising we are doing this week and get ready to brighten it up and make it sharper for next week?"

Yes, Sir, here's Wednesday morning and you're turning the spot light on your own advertising and sales promotion activities. You're being just as critical of your own efforts as you were of that "awful looking ad the Jones Appliance store ran yesterday."

Better get to it. A week is slipping quickly away. Never let it be said you failed because you were just too late or just too lazy to attract customers by fresh, sparkling advertising.

THURSDAY: "Phew! I sure don't like the smell of this place this morning," you snort as you swing wide the portal. Is that so? What do you think the customers say to themselves? This is the day, Mister, to start doing something about cleaning up the store. Time to freshen the air, dust, polish, sweep. Sure you do it every day—or do you? Maybe just a once over lightly, eh? This is the day you're going to do some digging—regular white glove inspection stuff. Not much of the week left to welcome customers you know. By gosh, there's not going to be a whiff of old cigar butts, a finger-printed piece of chromium, a dust smeared cabinet, or fly-specked piece of glass in your business shop when this day's over! You know you get so used to looking at your store day after day you get to the point where you don't notice grime creeping up on it. The only way to make sure you're strictly on the gleaming side is to pull yourself up short at this Thursday morning inspection, look at everything as though you'd never been in there before—then dig, brother, dig.

SPRAGUE TRADING POST

SWAP—BUY OR SELL

FOR SALE—Mark II transmitter-receiver converted for 6 volt operation, \$40; Jackson comparison oscillator and cycle counter \$18; Master teleplex code oscillator, \$25; E. A. McCall, 3504 E. 26th St., Kansas City 1, Mo.

FOR SALE—Weston 777, tube checker, emission type with chart for all newest type tubes, \$45. Frank D'Anna, 2154 E. 2nd St., Brooklyn 23, N.Y.

WANTED—25B8 tube, A. V. Philbin, 6218 Palo Pinto, Dallas, Texas.

FOR SALE—BC-342 receiver complete, \$50; also power supply 1250-1000-800 volts d-c @ 300 ma little used, \$50. Robert Cockrell, 207 W. Washington Ave., Madison 3, Wis.

FOR SALE—BC-348S in good condition, converted per Jan. QST, complete with speaker, shockmount 8" meter, external power supply, etc. \$75 or trade for ART13 in good condition. Hastings Sharp, Hackley School, Tarrytown, N.Y.

WANTED—To buy radio service shop or store preferably in the South or will go in partnership. Have all the necessary equipment and know how of F.M. Ben Roller, P.O. Box 156, Nashville, Mich.

FOR SALE—Ultraphone UHP-2, compact 2 meter transmitter and receiver; 30 watts input, used less than 10 hours, complete with tubes, \$60. J. Barrett, 1410 Custer Drive, Erie, Pa.

FOR SALE—Radio books: Understand Radio by Watson & Welch, \$1.50; Electrical Engineering Handbook, 966 pages, \$2.50; Radio Engineering by Fernan, 600 pages, \$2.50; Drakes Encyclopedia of Radio and Electronics, \$3. Will give book from Radio Craft Library series with every book sold. Dan & Ted's Radio Shop, 4355 S. Honore, Chicago 9, Ill.

FOR SALE—Pair of RK-63's similar to 250th—never used, \$15 ea. E. P. Sadler, 90 Chippewa Rd., Tuckahoe 7, N.Y.

FOR SALE—Complete outfit for home recording and playback assembly with microphone, turntable, pickup, tubes, recording arm, etc. \$35. Paul Engelby, Box 32, Briceville, Minn.

TRADE—One 110V, 500W, D-C, gasoline driven generator, new and 2 EES-A phones, good. Want Hallcrafters S-201T or similar receiver, good. Don Schleich, 133 1/2 W. 5th Ave., Columbus 1, Ohio.

WANTED—Radio test equipment, must be reasonable. Best Radio, 3349 Fulton, Cleveland 9, Ohio.

SALE OR TRADE—Pair of 2 meter transceivers one AC or vibrator powered, other AC. Complete with tubes, speaker mike, etc. What have you? Peter Porath, 186 Everett St., Fond du Lac, Wisconsin.

FOR SALE—Viewtone television chassis, complete with 19 tubes and C.R.T. unaligned, \$75. G. Pollack, 1424 Walton Ave., New York 52, N.Y.

YOUR OWN AD RUN FREE

The Sprague Trading Post is a free advertising service for the benefit of our radio friends. Providing only that it fits in with the spirit of this service, we'll gladly run your own ad in the first available issue of one of the six radio magazines in which this feature appears. Write CAREFULLY or print. Hold it to 40 words or less. Confine it to radio subjects. Make sure your meaning is clear. No commercial advertising or the offering of merchandise to the highest bidder is acceptable. Sprague, of course, assumes no responsibility in connection with merchandise bought or sold through these columns or for the resulting transactions.

Dept. RN-127, SPRAGUE PRODUCTS COMPANY
North Adams, Mass.

(Jobbing distributing organization for products of the
Sprague Electric Co.)

FREE! This Giant Sprague TEL-U-HOW WALL CHART

—from your Sprague Distributor

Ask your nearest Sprague jobber for your copy of the SPRAGUE TEL-U-HOW WALL CHART. Just the thing for hanging on the wall of your shop. Its professional appearance impresses customers. The material it contains will help you do jobs easier, better, faster.

Beautifully lithographed in colors, size 22" x 28", the chart includes handy service application data; diagrams and descriptions of common circuit troubles involving capacitors; general replacement data on electrolytics; formulas; transformer, resistor and capacitor color codes; schematic; and similar invaluable service information. Everything is arranged for quick, easy reference. Popular Sprague Capacitors and Koolohm Resistors are illustrated. Don't miss it!



WANTED—Camera, any type, describe. Will trade radio parts, tubes or what do you want? Harry Gursh, 147 Chester St., Brooklyn 12, N.Y.

FOR SALE—Andrea 7" television kit wired, with cabinet. Good performance—local buyer preferred. I. Joseph, 548 Sheffield Ave., Brooklyn 7, N.Y.

FOR SALE—New power level/voltmeter, range in decibels: -8, -4, 0, 4, 8, 12, 16, 20, 24, 28, 32. Range in A.C. Volts: 1.5, 6, 15, 60, 150; in bakelite case 3 1/2 x 6" with meter and range switch, \$16; also one Jensen electro dynamic speaker with transformer, \$5. Both for \$20. J. H. Reinhart, 27 Church St., Lonaconing, Md.

WANTED—P. A. equipment 20 watts or more—mention price and condition. Best Radio Shop, 3349 Fulton Road, Cleveland 9, Ohio.

FOR SALE—18 tube, 6 band Midwest receiver with 12" Utah speaker, 4.6 to 857 meters, good condition. Will accept vibroplex speed key, featherweight XTAL phones and/or cash. H. Lull, 2352-27 St., Long Island City 5, N.Y.

SALE OR TRADE—Thordarson multi-tap modulation transformer 125 watt, T11M76. Want small V.O.M. such as Simpson hammett or Triplet 660H. R. E. Kurtl, 13159 Montville, Detroit 6, Mich.

FOR SALE—ACRO chassis cradle; clamps, set of straight clamps, used very little, \$5.00; RME 45 receiver, latest model, good conditions, \$140.00; Gen. Test Equipment Co. Pen-Oscil-Lite used very little, \$4. Robert Greenen, 518 Liberty St., Aurora, Ill.

FOR SALE—Vomax VTVM, \$50; G-E TC-3, 1946 tube tester; 1947 Jackson 640 signal generator, \$40; Rider's manuals 12 and 13, \$25; Sam's Photofacts, 1946-47, 1 through 20, \$22.50. Also have coils, conductors, etc. H. J. Hass, Osakis, Minn.

WANTED—New or used Hallcrafters SX-25 or SX-28A. State price and condition. H. A. Braun, Box 392, Beverly Hills, Calif.

FOR SALE—New RCA 158 oscilloscope. Cash or will trade for h.f. sig. gen. vacuum tube voltmeter, Leica lenses or photographic equipment. Beverly Hills Radio Co., 9138 West Olympic Blvd., Beverly Hills, Calif.

WILL TRADE—B-10 bubble sextant in perfect condition. Want BC-348 receiver or what have you. E. McNamara, 6901 W. Outer Drive, Detroit 19, Mich.

SELL OR TRADE—Three tube midgap hearing aid, \$20; new Navy RBZ portable 5-13 m.c. receiver and 100-200 a.c.-d.c. power pack. Want BC-728-A portable or any good two meter transceiver or handie-talkie or what have you? A. V. Perilli, 137 Grove St., West Roxbury, Mass.

FOR SALE—Rider's manual III all pages intact, like new \$7.50 postpaid. William Bashta, 113 Bennett St., E. Syracuse, N.Y.

FOR SALE—Barr ultra short wave transceiver DB-3, \$15. Want p.a. equipment or what have you? Best Radio Shop, 3349 Fulton St., Cleveland, Ohio.

FOR SALE—Meissner analyst nearly new, \$85 or will trade for good communications receiver. M. W. Wardman, Gen. Del., Guernsey, Wyo.

WANTED—Silver 906 signal generator, good oscilloscope and Silver Vomax. Will pay cash or trade Hickok signal generator 191X. C. D. Justis, Box 86, Newport, Del.

FOR SALE—Used spring wound instructor-graph, deluxe, code machine with earphones, key, built in battery oscillator and 10 rolls of tape (1 to 10), \$20. Raymond L. Lemay, 32 1/2 Oxford St., Lewiston, Maine.

FOR SALE—Slightly used S-20-R communications receiver, like new, \$50. Norman H. Schauld, 412 Vandall, Collinsville, Ill.

FOR SALE—Radio shop equipment; Superior tube tester 450, \$28; Superior VOM push button, \$25; all wave signal generator, \$25; stock of new tubes at half price; also condensers and resistors. C. E. Hinesman, 149 Manville, Bowling Green, Ohio.

WANTED—Information as to where Jefferson Travis 350A surplus radios may be purchased. Will sell Mark 2 transceiver, \$35; 8C-R 610, \$25; mobile FM receiver, \$29; 150-500 kc RCA receiver; AC power supply and preselector, \$40. E. R. Balak, 2224 Edgar Road, Linden, N.J.

FOR SALE—Radio News, Feb.-Aug., 1947; all 1946 and 1945; May-Sept., 1944, \$4; also Radio Craft, Jan.-Aug., 1947; Jan.-May, July, Nov. and Dec., 1946; Mar. and June-Dec., 1946; \$2.50. Dan & Ted's Radio Shop, 4355 S. Honore St., Chicago 9, Ill.

WILL TRADE—German made Wheatstone bridge, various tubes and crystals, also Ghirardi's Modern Servicing; Audel's Radioman's Guide; Sterling's, Radio Manual and Rider's, Frequency Modulation. Want good tube tester, signal generator or a VTVM. William McKay, 2 Arlington Place, Buffalo, N.Y.

WANTED—2 BC-1016 ink code recorders, 110 volts, 60 cycle a-c, new or working used condition, 3/4" paper tapes for same. Also copies Electronics 1941 to date. Ohio Radio Television, Box 1171, Lakemore, Ohio.


FOR SALE OR TRADE—Complete Sprayberry course without equipment, \$45, or will trade for good voltohmmilliammeter or other test equipment. What have you? J. A. Rhilinger, 77 Oakton Ave., Dorchester, Mass.

FOR SALE—BC-348-N, 110v a-c phone or speaker, new with phones, \$55; receivers from BC-634, 1 1/2 mc to 8.5 mc, 1 1/2 v. B power, \$15. Want instructions on converting A18-13 for mike key and speaker. Opal Watkins, R.R. 3, Ellijay, Ga.

FOR SALE—Oscillator, 50 kc to 110 mc, 6 bands, 1% accuracy, \$20; McElroy tape recorder and amplifier, \$25; Wollensak 3", f3.5 enlarger lens, \$25; Mercury II, \$70; Argus Speed Printer, \$10—all new. J. Bourke, 148 Winthrop St., Brooklyn, N.Y.

ASK FOR SPRAGUE CAPACITORS and *KOOLOHM RESISTORS by name!

*Trademark Reg. U. S. Pat. Off.

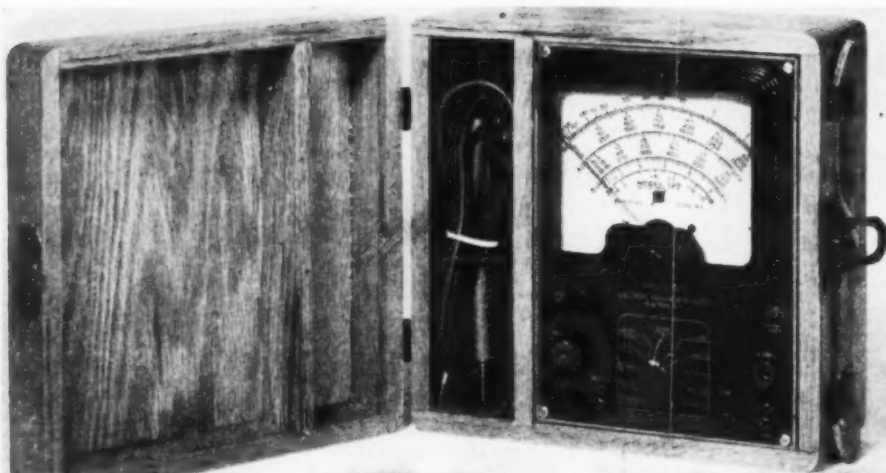

E.M.C. Gives Maximum Measurement Value Per Dollar

COMPARE Model 120 with ANY other 20,000 ohms per volt instrument!

Model 120 Gives you—

1. WIDEST resistance range (.2 ohm to 300 megs.)
2. HIGHEST AC voltage sensitivity (10,000 ohms/volt)
3. LOWEST PRICE \$29.95 for open face model, \$34.95 for Model 120-P. (portable)

FOR FURTHER INFORMATION WRITE TODAY TO: DEPT. R

ELECTRONIC




MEASUREMENTS

CORPORATION

423 Broome St., New York 13, N. Y.

TELEVISION COIL KIT

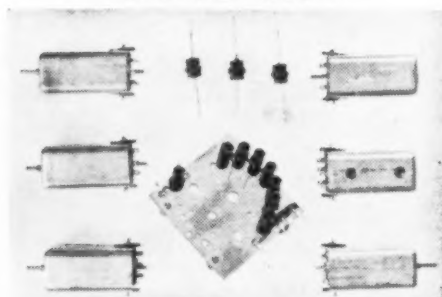

Complete **\$23⁵⁰**

LOOK AT THESE FEATURES!

- * Video IF Bandwidth of 4.25 MC that can operate ANY size picture tube with maximum resolution.
- * Five stages Video IF permeability tuned with sound and adjacent channel rejection traps in shielded cans.
- * 6 Channel RF Tuner, permeability tuned mounted on switch assembly plate.
- * FM Sound Discriminator for TRUE FM.
- * Can provide Video Operation for 10, 12, 13 or 20-inch picture tube upon further construction.
- * Video Peaking Chokes to maintain bandwidth.
- * Detailed Construction Manual & Parts List with every kit, for 20 Tube, 7 in. Television Set.
- * Continued Service Bulletins.

ORDER DIRECT OR THRU LOCAL DEALER
TERMS

Shipped Parcel Post prepaid on receipt of check or money order. Or P.P. Collect on receipt of 25% deposit with order, balance COD.

RAY-LECTRON CO.

706 Tenth Avenue
BELMAR, N. J.


Get a new ELECTRIC SOLDERING IRON

FREE

and assemble your own

MAGI-KLIPS

RADIO & ELECTRONIC EXPERIMENTER'S KIT

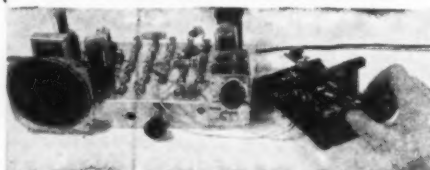

This is the same MAGI-KLIPS Kit—complete with all parts—that we sell ready assembled for \$29.75.

In knocked-down form with full instructions for assembly it is now available at the new low price **\$19.75**... complete with a new Electric Soldering Iron—the ideal iron for wiring your unassembled MAGI-KLIPS Kit.

Remember, you buy 18 different experiments with your MAGI-KLIPS Kit. You actually teach yourself radio and electronics and have a lot of fun at the same time.

RADIO RECEIVER, HOME BROADCASTER, PHOTOELECTRIC RELAY, CODE PRACTICE OSCILLATOR, SIGNAL TRACER, REMOTE CONTROL RELAY, Phonograph Transmitter In: communication Amplifier, Code Transmitter Radio Frequency Oscillator, Telephone Line Amplifier, Electronic Switch, Phonograph Amplifier, Temperature Control Relay, Contact Detector, Electronic Metronome, Interval Timer (one-shot), Interval Timer (repeating).

Send for your copy of FREE booklet, "Electronics Made Easy."

DEER & TAYLOR COMPANY

Dept. N 1342 Milvia St. Berkeley 9, Calif.

FRIDAY: Time's running out. One chance for success out of 52 for the year has almost slipped away. Let's make this early Friday morning a supplier's review session. Let's see what salesmen have called this week. What did they have to offer? Did you make notes of their suggestions or were you too busy when they stopped in? Did they just pass the time of day, or did you only get a rough idea of some plan they had? If you haven't kept notes on their proposals, better rush out right now and get yourself a note book so next week you won't miss a bet, so next week you can jot down inspirations which need consideration after hours and might lead to expansion of your business. Right now is a good time to run through that stack of letters and circulars that you've been piling up on the corner of your desk all week. Maybe in the heap is a proposition from a current supplier or a new company you'd better investigate thoroughly. No telling when the mailman is going to whisk a hot deal through the door. Sure, you get loads of circulars, printed matter, but remember, friend, somebody has given a lot of thought, a lot of time and has spent good cold cash to send them to you. Maybe one of these pieces will give you an opening to boost your sales in a way you'd never thought possible.

SATURDAY: Brace yourself, brother! Here's the last fling, the pay-off day of the week. Get in early and bright. Stop across the street this morning and take a good look at your store. Is the stage set to make the best impression you can hope for on those Saturday shoppers? Window gleaming clean? Sign in order? How does everything look inside? Orderly? Set to command attention to the items you want featured this Saturday? Now take a good look in the mirror. Shaved? Shirt clean? Tie straight? Suit pressed? How about the expression? Smile muscles working well? Straightforward, earnest look-in-the-eye mechanism in order? Eager-to-serve expression all oiled up? Frame of mind ready to withstand silly questions by the hundred, ready to counter with hard-hitting sales clinching statements about every piece of merchandise in the store? How does the help react this morning? Have you greeted them with your best "Let's go and hit 'em hard" manner, pleasant, encouraging, inspirational? Yes, this is "let's take a look at ourselves" morning. This is the day we give ourselves a thorough going over, a slap on the back and a firm grip on our patience and good manners.

So, a week has been ended as the last light flickers out on Saturday night.

It's been a good week, a progressive week. If you keep alert by challenging some important side of your business each day—then doing something about it, you're on the tides which lead to a prosperous business.

-30-

RADIO NEWS

**Prepare
NOW**

for a Better Job in RADIO ENGINEERING



**Don't Delay—
Write Today!**

In This New World of Electronics Better Training Means Better Opportunities!

TODAY, the new war-developed techniques offer greater opportunities than ever existed in the early days of broadcasting! Micro-Wave Relay Systems, Television, FM Broadcasting, Mobile Communication Systems for Trains, Automobiles, Busses, Trucks, many Industrial Applications—these are just a few of the new techniques which offer marvelous, exciting opportunities to you who are alert—and are qualified!

Let Cleveland Institute Take Over Your Personal Up-Grading Problem! Qualified, competent instructors, ample, personalized instructional aids, orderly, progressively arranged study assignments in recognized, approved technical texts—these are only a few of the many superior advantages of CIRE's plan of personalized spare-time home study training for professional self-improvement.

CLEVELAND INSTITUTE COURSES OFFER COMPLETE TECHNICAL TRAINING RANGING FROM LOW-LEVEL TO COLLEGE-LEVEL.

- A. Master Course in Radio Communication.** Covers complete preparation for broadcast station employment including preparation for FCC License Examinations.
- B. Advanced Course in Radio Communication Engineering.** A college-level Radio Engineering Course.
- C. Specialized Television Engineering.** Including post-war Television Techniques.

All Courses Include
The Remarkable Workbooks of Instructional Aids, prepared by the instructing staff of Cleveland Institute.
Choose the course best suited to your needs—Start with the section you are qualified to enter—Use the economical CIRE "Pay-As-You-Go-Plan."

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

Contractors to the Canadian Broadcasting Corporation

RN-12 Terminal Tower

CLEVELAND 13, OHIO

Approved for Training under "G-I Bill of Rights"

ENROLL FOR INDIVIDUAL SECTIONS OF COURSES, IF YOU PREFER.

If you need only highly specialized training, you can study one or more of the following sections instead of a complete course.

1. Mathematics of Radio.
2. Fundamentals of DC and AC Theory.
3. Essentials of Radio Communication.
4. Communication Networks.
5. Advanced Radio Telephony for the Broadcast Operator.
6. Audio and Radio Components and Systems (Design of Receiver and Transmitter Equipment).

(MAIL THIS COUPON)

Cleveland Institute of Radio Electronics, RN-12, Terminal Tower, Cleveland 13, Ohio.
Gentlemen: Please send information about your home courses in Radio Electronics.

NAME
ADDRESS
CITY
ZONE STATE
I desire training in ☐ A ☐ B ☐ C
I have had experience in broadcasting ☐ servicing ☐
operating ☐ mfg. ☐ CAA ☐ Army-Navy ☐
amateur ☐ other I am a
High School Grad. ☐ College ☐ Degree
☐ Check here for Veteran Enrollment Information.

**How To Pass
FCC
LICENSE
EXAMINATIONS**

CLEVELAND INSTITUTE
OF RADIO ELECTRONICS
Terminal Tower - Cleveland, Ohio

**Don't Delay—
Write Today!**

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

Contractors to the Canadian Broadcasting Corporation

RN-12 Terminal Tower

CLEVELAND 13, OHIO

Approved for Veteran
Training under
"G-I Bill of Rights"

Get your FCC Commercial Radio Operators' LICENSE NOW!

IT'S EASY IF YOU FOLLOW OUR PLAN!

Thousands of new jobs are opening up—FM, TELEVISION, MOBILE COMMUNICATIONS SYSTEMS, are only a few of the radio fields which require licensed operators.

TIME IS IMPORTANT TO YOU!

You can get your License quickly with NILSON'S MASTER COURSE in RADIO COMMUNICATION and exclusive CIRE Workbooks of Instructional Aids. Saves you many hours of random, undirected study.

Assures a MINIMUM of time in getting your ticket.

FREE BOOKLET tells you the Government Requirements for all classes of commercial licenses—Sent immediately upon receipt of coupon.

MAIL THIS COUPON

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
RN-12 Terminal Tower, Cleveland 13, Ohio

Gentlemen: Please send information about your Home Study Course for preparation for FCC Commercial License Examinations. (Does not cover Amateur License Examinations)

Name
Address
City Zone State
☐ If a Veteran check here

Chicago

INSTRUMENTS

Quality at Low Cost!



POCKET VOLT-OHM-MILLIAMMETERS FOR ONLY \$5.25

Anyone can now own a good volt-ohm-milliammeter. There is a Chicago V.O.M.A. priced at only \$5.25. Chicago "Featherweights" that slip easily into the pocket are the original miniature radio test instruments. They are popular throughout the world.

For years, Chicago Instruments have given radio men accurate, dependable service. And because of simplicity of design and freedom from "gadgets" we have been able to hold down prices to a fraction of what you would normally pay for instruments of similar quality.

Chicago Instruments are available in a variety of ranges and sensitivities. You may see them at your Suppliers or get the complete details by writing for Bulletin No. 10.



Recording of Sound

(Continued from page 50)

The on-off toggle switch, pilot lamp, phone jack, and sensitivity control are all mounted on the front panel. All other miscellaneous parts, such as bypass condensers, resistors, etc., are mounted as close to their respective circuits as possible in order to reduce interaction between stages and avoid unnecessary troubleshooting after the completion of the unit.

The location of the two 7B7 lock-in tubes makes interstage shielding unnecessary. However, if the reader employs some other layout, especially a non-metallic chassis and panel, interaction (and feed-back) may be experienced. If this does happen, it will be necessary to mount an upright sheet-metal baffle between the power supply components (transformers and chokes) and the tuning condenser and other r.f. components. Interaction usually is noticed first at the high frequency end of the dial. Most readers will prefer to buy factory-made r.f. coils (both the antenna and interstage units) rather than winding them at home, since such manufactured coils may be obtained quite readily and are reasonably priced. They are designed to have a high Q and are completely adjusted. Several manufacturers supply these coils already mounted in shield cans of the proper size. Those readers having an assortment of shield cans may use the unshielded coils. However, one must bear in mind, when shielding an r.f. coil, that the smaller the diameter of the shield in respect to the diameter of the coil, the lower will be the Q, and consequently a lower gain will be experienced. A diameter ratio of approximately two-to-one and a length ratio of one and one-half-to-one is recommended.

The filaments of the tubes and the panel lamp should be connected to the 6.3 volt section of the transformer combination, using twisted leads to insure freedom from 60 cycle hum. These leads should be dressed close to the chassis, as far as possible from grid or plate leads. The reader must not forget to ground one heater terminal to the chassis by means of a short, direct connection.

The use of inexpensive 1 ampere filament transformers as the power transformer was made possible by the use of dry disc rectifiers, which have no filaments to draw current. It is a good practice to connect the primary of the improvised power transformer to the line, and check the filament circuit for voltages, before completing other power supply wiring.

The two line bypass condensers (C_{12} and C_{13}) aid materially in elimination of line hum, and these units must not be excluded.

The screen grids should be wired with a 100,000-ohm, 1-watt resistor (R_3-R_6) in series with the positive side (Continued on page 110)

CHICAGO INDUSTRIAL INSTRUMENT CO., 536 W. ELM ST. CHICAGO 10, ILL.



Dial Belt Kits

Ne-O-Lite Tester

Alignment Kit

Phono Turntable Stand

G-C SERVICEMEN'S DIAL BELT KITS

Easy to install. The best belts for all sets. Supplied in kits of assorted popular belts with steel box.

No. G-25—Kit of 25 belts. List.....\$6.70

G-C NO. 5024 ALIGNMENT KIT



Complete alignment and neutralizing kit of 30 different tools, in leatherette case.

List.....\$19.95



G-C PHONO TURNTABLE STAND

Steel stand on which you can place any phono turntable; ideal for repairmen; easily adjusted; sturdy steel construction. No. 5205—List.....\$6.65

G-C NE-O-LITE TESTER



For testing fuses, appliances and any electrical circuits. 90 volts to 550 V., A.C. or D.C.

No. 5100—List.....50c

Available at all leading distributors
WRITE FOR YOUR CATALOG TODAY!
RADIO DIVISION, DEPT. H

GENERAL CEMENT Mfg. Co., Rockford, Ill., U.S.A.
Manufacturers of over 3,000 products
Sales offices in principal cities

Radio Parts Distributors

SENSATIONAL VALUES!

Nationally Known Brand	
8" PM SPEAKER.....	\$2.09
5 for.....	\$13.75
10" PM SPEAKER.....	3.25
5 for.....	\$15.50

100 Ass't

1/2 Watt Resistor Kit.....	\$1.69
5B84 Television Scope Tube.....	\$3.79

CONDENSER SPECIALS

10 mfd., 25 V.....	23c—10 for \$1.90
20 mfd., 150 V.....	34c—10 for 2.75
40 mfd., 150 V.....	38c—10 for 3.10
8 mfd., 450 V.....	34c—10 for 2.75
16 mfd., 450 V.....	50c—10 for 4.10
20-20 mfd., 150 V.....	59c—10 for 4.70
50-30 mfd., 150 V.....	68c—10 for 5.40
500M Controls with Switch.....	Ea., 59c
10 for.....	\$5.50

We carry a full line of tubes, batteries, speakers, amplifiers, test equipment, hardware, controls, etc.

FREE!



Write for R.P.D.'s latest bulletin for more sensational Values!

Terms: Remittance with order plus postage or 25% deposit, balance C.O.D.

Radio Parts Distributors

925 E. 55th St., Chicago 15, Ill.

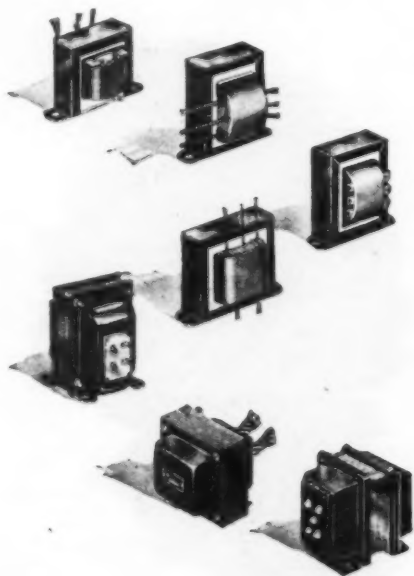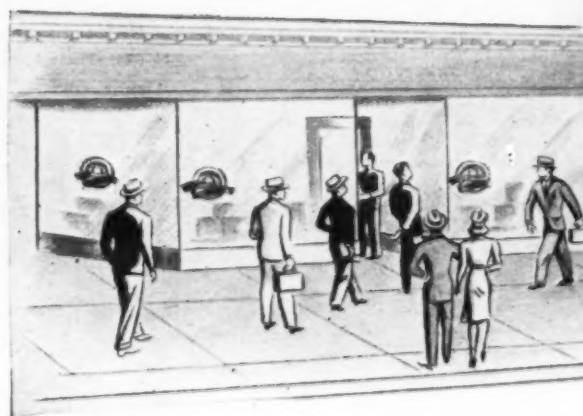where you see the
name **STANCOR**
you can count on
SERVICE



The famous black-and-yellow STANCOR emblem stands for SERVICE . . . in guaranteed transformer performance . . . and in the friendly helpfulness of the Authorized STANCOR Distributor . . . who stands behind the product he sells. . . . Yes, wherever you see the STANCOR emblem you know you will find the most complete selection of Replacement and General Purpose Transformers . . . advanced designs . . . and the universal application that make STANCOR first with radio service men. . . . You bet you can look to STANCOR . . . for the standard of performance that assures you of satisfied customers.

standardize on **STANCOR**



TRANSFORMERS

STANDARD TRANSFORMER CORPORATION • 1500 N. HALSTED ST., CHICAGO 22, ILL.

BC-947A ONE KILOWATT HIGH FREQUENCY TRANSMITTER


This relay-controlled transmitter includes a 115V, 60 cycle power supply, protected by 3 magnetic circuit breakers, that alone is worth more than the price we are asking for the whole rig, even on today's surplus market. On the front panel are six 3 1/2" GE or Weston meters, including 250 MA, 50 MA, 1000 MA, 150V AC and 1500V DC at 1000 ohms per volt for screens and plate. The rack-type 21"x15"x36" unit contains six amplifier and rectifier tubes aggregating over \$60.00 at WAA current wholesale prices. Western Electric's price to the government was \$1500.00. Shipping weight 500 lbs. Your cost, as is, only \$69.95.

AT LAST YOU CAN AFFORD A LABORATORY STANDARD SIGNAL GENERATOR

The famous Measurements Corp. Model 78B, 5 Tube Laboratory Standard Signal Generator (currently selling new, F.O.B. Boonton, N. J., for \$310.00 net), is available in perfect condition for 25 to 60 cycle, 115 V AC operation. Until now this is the sort of top-flight lab equipment that discriminating buyers have only vainly hoped would be released at a bargain price. Worth every cent the manufacturer asks, but available F.O.B. Buffalo while our limited supply lasts, for only \$79.95.

Such companies as Admiral Corp. and John Meck Inc. have ordered from us and repeated many times on these 78 generators for use in their labs and production line testing.

"REMEMBER THAT A STANDARD IS ONLY AS RELIABLE AT ITS MAKER."

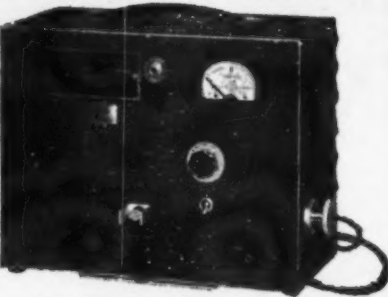

Model 78-B Standard Signal Generator. Two Frequency Bands between 15 and 250 megacycles.

5" "80" RADAR P.P.I. OSCILLOSCOPE, complete with 9 tubes. This unit contains magnetic deflection yokes and a Selsyn motor and has a self-contained power supply designed to run on the AC supply on LST or PT boats. The most satisfactory scope available for navigational radar or panoramic television applications. Uses 807 tube in final power stage that provides yoke deflecting current. Your cost—\$39.95. **"80" RADAR ECHO BOXES, THE PERFECT CALIBRATED CAVITY WAVEMETER—\$10.00.**

5 INCH RADAR OSCILLOSCOPE BC-412. Easily converted by a few hours work to a first class lab scope or to an excellent home television receiver using the instructions in the August 1947 RADIO NEWS. Furnished with a brand new 5BP4 tube for the television application and a brand new 5BP1 for the scope application. Specify your choice. Your cost.....\$59.95



LORAN INDICATOR OSCILLOSCOPE, complete with 26 tubes and a 5" cathode ray tube. government instruction manual included—\$39.95.

2 INCH OSCILLOSCOPE EQUIPPED WITH 2API TUBE.....\$9.95
5 INCH RECEIVER INDICATOR SCOPE. This unit, originally sold by Western Electric for \$2500.00 includes a 13 tube receiver with 7 IF stages; 3 tube multivibrator sweep generator; 2 tube sweep amplifier; video amplifier; pedestal impulse and sweep generator, and 115 volt, 60 cycle supply with 2x2 for high voltage. Supplied with at least 29 of the original 40 tubes, including a new separately crated scope tube. Makes a wonderful laboratory instrument and is better adapted for television conversion than any other war surplus item. Your cost.....\$69.95

GENERAL ELECTRIC RT-1248 15-TUBE TRANSMITTER-RECEIVER


TERRIFIC POWER—(20 watts) on any two instantly selected, easily pre-adjusted frequencies from 435 to 500 Mc. Transmitter uses 5 tubes including a Western Electric 316A as final. Receiver uses 10 tubes including 955's, as first detector and oscillator, and 3-7H7's as IF's, with 4 slug-tuned 40 Mc. IF transformers, plus a 7H7, 7E6's and 7F7's. In addition unit contains 8 relays designed to operate any sort of external equipment when actuated by a received signal from a similar set elsewhere. Originally designed for 12 volt operation, power supply is not included, as it is a cinch for any amateur to connect this unit for 110V AC, using any supply capable of 400V DC at 135 MA. The ideal unit for use in mobile or stationary service in the Citizen's Radio Telephone Band where no license is necessary. Instructions and diagrams supplied for running the RT-1248 transmitter on either code or voice, in AM or FM transmission or reception, for use as a mobile public address system, as an 80 to 110 Mc. FM broadcast receiver, as a Facsimile transmitter or receiver, as an amateur television transmitter or receiver, for remote control relay hook-ups, for Geiger-Mueller counter applications. It sells for only \$29.95 or two for \$53.90. If desired for marine or mobile use, the dynamotor which will work on either 12 or 24V DC and supply all power for the set is only \$15.00 additional.

ARMY BC-312 COMMUNICATIONS RECEIVER

This receiver covers the frequency range of 1.5 MC to 18 MC in six direct reading bands. The dial, that is driven with split gears to prevent backlash, has 4500 logging divisions per band with approximately 600 divisions on the 20 and 40 meter ham bands and 1000 divisions on 80 meters. Two stages of RF before the converter in this set give it a very high signal to noise ratio and maximum sensitivity. Outstanding features of this receiver are: BFO with pitch control, send-receive relay, jacks on the front panel for headphones and speaker output, and mike and key inputs. All tubes are standard 6 volt types. This receiver was designed to withstand rough usage in the field and for operation from vehicles while in motion, so it is ruggedly constructed and contains a dynamotor power supply—Your cost—\$49.95. Conversion kit to 110V AC is available for \$6.50.

RT1463 7 TUBE AMPLIFIERS containing 3-7F7, 1-7Y4, 3-7N7, 4 potentiometers, numerous resistors, filter and bypass condensers, filter chokes, power and audio transformers, and six sensitive plate relays. A military development that provided amazing stepless control proportional to correction required, for ailerons, rudder and elevator, in the original application. A control amplifier of the ordinary type would deflect the rudder by some arbitrary amount when the ship was blown off the course to port or starboard. The result would either be that the correction was insufficient and the plane continued off course, or the correction would be too great, starting a series of tackings that would greatly increase fuel consumption and elapsed time in reaching the objective. This phenomenal unit, with its 3 amplifier and six 5000 ohm relays in bridge circuits, will accurately control any 3 operations, related or unrelated, in minutely adjustable uniquely quantitative variations in either forward or reverse directions. 9"x7"x8" black crackle aluminum case. Brand new in original carton \$12.95, or used \$9.95.

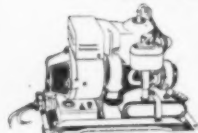PE-109 32-VOLT DIRECT CURRENT POWER PLANT



This power plant consists of a gasoline engine that is direct coupled to a 2000 watt 32 volt DC generator. This unit is ideal for use in locations that are not serviced by commercial power or to run many of the surplus items that require 24-32V DC for operation. The price of this power plant is only \$59.95. We can also supply a converter that will supply 110v AC from the above unit or from any 20-32V DC source for \$29.95.

SERVICE MEN

Check This Column for Lowest Prices on Quality Parts
TUBES: all types in stock, 60% off on all tubes if ordered in lots of 10 or more.

RESISTOR KITS—100 assorted 2 watt resistors—only \$1.95.
TRANSFORMERS—All types in stock. **AUTO-TRANSFORMERS:** Steps up 110v to 220v, or steps down 220v to 110v—\$1.95.
FIL. TRANS. 6.3v, 20 Amps.—\$1.95; Universal Output Trans. 8 Watt—89c; 18 Watt—\$1.29; 30 Watt—\$1.69. **AUDIO TRANSFORMERS:** S. Plate to S. Grid. 3:1—79c; S. Plate to P.P. Grids—79c; Heavy Duty Class AB or B, P.P. Inputs—\$1.49; Midset Output for AC-DC sets—69c; **MIKE TRANSFORMER** for T-17 Shure microphone, similar to UTC oncure type—\$2.00. Stanoor SB or DB mike to line or grid—\$1.95.

POWER TRANSFORMERS—Half-shell type, 110V, 60 cy. Centertapped HV winding. Specify either 2.5 or 6.3V filament when ordering.

For 4-5 tube sets—650V, 40MA, 5V & 2.5 or 6.3V.....\$1.49
 For 5-6 tube sets—650V, 45MA, 5V & 2.5 or 6.3V.....1.75
 For 6-7 tube sets—675V, 50MA, 5V & 2.5 or 6.3V.....1.98
 For 7-8 tube sets—700V, 70MA, 5V & 2.5 or 6.3V.....2.35
 For 7-8 tube sets—700V, 70MA, 5V & 6.3 (25 Cycle).....3.60
 For 8-9 tube sets—700V-90MA, 5V-3A, 2.5V-3.5A.

2.5-10.5A2.85
 For 9-11 tube sets—700V, 5V & 6.3V-4A.....2.85
 For 9-15 tube sets—600V, 150MA, 5V & 6.3V.....2.95

CONDENSERS—PAPER TUBULAR 600 WV., .001, .002, .005—3c; .01, .05—3c; .1—10c; .25—25c; .5—35c; **ELECTROLYTICS:** 8mfd 200v—20c; 10mfd 35v—20c; 30mfd 150v—25c; 20/20mfd 150v—35c; 30/20 150v—45c; 50mfd 150v—43c; 8mfd 475v—34c; 16mfd 350v—65c; **OIL CONDENSERS:** 4mfd 600v 49c; 2mfd. 600v. 29c 3X.1mfd 600v—29c.

FILTER CHOKES: 200, 300, 400, 500 ohm light duty—59c; 200 or 300 ohm heavy duty—99c; 250 ma 35 ohm, made for U.S. Navy, fully shielded—\$1.95; 75 ohm 125 ma—25c or 25 for \$4.25; "Meissner type" tapped filter chokes—25c; 8 amp. iron core A filter—25c; Choke-condenser combination, ideal to replace any size speaker field when installing PM speaker—79c.

110V. CIRCUIT BREAKERS of Magnetic type: Following Current Ratings in Stock: 1.25, 3, 4, 8 Amps. Please specify. \$1.95 each.

Seven Assorted I.F. Transformers—\$1.95; Five Assd. Oscillator Coils—69c.

SPEAKERS—PM dynamic type—4"—\$1.55; 5" \$1.55; 6"—\$1.95; 8"—\$3.95; 10"—\$5.95; 12"—\$7.50.

SELENIUM RECTIFIERS—Dry disc type 1 1/4" 1", 1.2 Amp. maximum, suitable for converting DC relays to AC. for supplying filament source in portable radios, converting DC meters to AC applications, and also may be used in low current chargers 90c.

METER RECTIFIER—Full wave, may be used for replacement, in construction of all types of test equipment—\$1.25. Half Wave—90c.

MICROPHONES—All nationally known brands. Bullet crystal—\$5.45; Bullet Dynamic—\$7.45; Mike Jr.—60c; Handy Mike—90c; Lapel Mike—93c; SHURE T-17 MIKES, with push to talk switch—99c.

20 ASS'D COIL FORMS, including 11 Mic, 3 polystyrene, and 6 fiber, all useful sizes—50c.

VARIABLE CONDENSERS: 350 MMFD, 5 gang—\$1.95; 4 gang—\$1.49; 3 gang—83c; 2 gang—79c; 7.5 to 20 MMFD, 1750v spacing, extra long shaft Hammarlund—69c; miniature variables, 25 MMFD—39c; 50 MMFD—49c; 75 MMFD—59c; 100 MMFD—69c; 140 MMFD—79c.

TRANSMITTING RF CHOKES, 4 PIE, 350 Ma.—25c or 5 for \$1.00.

INTERRUPTION FREQUENCY COILS for super-regenerative receivers or the tremendously popular FM adapters for standard broadcast sets. Iron core with a resonant frequency of 50 KC—39c; 100 KC—29c.

30 MC IF TRANSFORMERS, double slug tuned—25c.

VIDEO AMPLIFIER PLATE COILS—Slug tuned—25c.

REMOTE CONTROL UNIT: Aluminum case 4x3x2" containing 2 potentiometers, triple pole switch, 4 knobs, gear mechanism, counter and phone jacks—59c.

MODULATION TRANSFORMERS—10 watt, metal case 99c; 30 watt, open-type, \$1.95; 40 watt, cast aluminum case, \$2.95; Class "B" input transformers, cast aluminum case, \$1.95; Transceiver audio transformers, 65c; Transceiver modulation transformers, 65c.

PUBLIC ADDRESS AMPLIFIERS—25 watts peak output. This unit has separate input circuits for microphone and phono. The gain of the microphone circuit is 122db. The phono circuit has a gain of 82db. The frequency response is flat from 50 to 12,000 cycles. A \$65 value for only \$32.

Miniature pillers set contains one of each of the following: Needle nose, flat nose, parrot nose, standard nose. All contained in a leatherette case. Your cost—\$1.98.

ATR battery eliminator—Handy for servicing car radios or any other purpose requiring 6 or 12v at 14 amps. Net price—\$36.

SOCKET WRENCH SET consisting of 5 sockets ranging in size from 5/16 to 1/2" and a handle—79c.

AUTOMATIC WIRE STRIPPERS will strip up to 1000 wires per hour, a handy tool for any service job—\$3.92.

Six Foot Asbestos Insulated Flat Iron Cord, one end has a male plug, the other end has a standard flat iron socket. Your price—70c each or 10 for \$5.

LINE FILTERS—110v—each unit contains two 2 mfd. oil filled condensers and a 15 amp. iron core choke. This filter has innumerable uses such as oil burner line filter, etc. A ten dollar value for 99c.


Crystal pick-up, phono motor and turntable—\$5.25.

FLUORESCENT LIGHT BALLASTS. Single 30 or 40 watt, \$1.69; Dual 40 watt High Power Factor—\$3.75.

HEADPHONES—Highest quality Signal Corps headsets with 12' cord and plug \$1.25, 5' rubber covered patchcords with phone plug and socket—45c.

BC-221 FREQUENCY METERS with calibrating Crystal and calibration charts. A precision frequency standard that is useful for innumerable applications for laboratory technician, service man, amateur, and experimenter at the give away price of only \$39.95.

BC-221

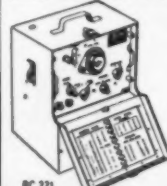


BUFFALO RADIO SUPPLY, 219-221 Genesee St., Dept. 12N, BUFFALO 3, N. Y.

CABLE ADDRESS BUFRAD

RADIO NEWS

RADIOMEN'S HEADQUARTERS * WORLD WIDE MAIL ORDER SERVICE!!!

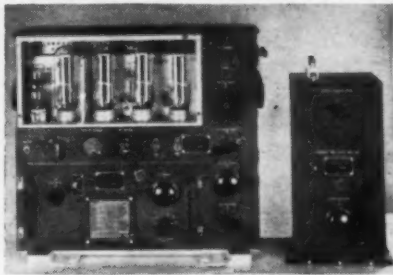Minimum order \$3.00—All prices subject to change—25% deposit with COD orders.



GENERAL ELECTRIC 150 W. 11 TRANSMITTER

Cost the Government \$1800.00
Cost to you \$44.50!!!!

This is the famous transmitter used in U.S. Army bombers and ground stations, during the war. Its design and construction have been proved in service, under all kinds of conditions, all over the world. The entire frequency range is covered by means of plug-in tuning units which are included. Each tuning unit has its own oscillator and power amplifier circuits—all designed to operate at top efficiency within its particular frequency range. Transmitter and accessories are finished in black crackle, and the milliammeter, voltmeter, and RF ammeter are mounted on the front panel. Here are the specifications: FREQUENCY RANGE: 200 to 500 KC and 1500 to 12,500 KC. (Will operate on 10 and 20 meter band with slight modification.) OSCILLATOR: Self-excited, thermo compensated, and hand calibrated. POWER AMPLIFIER: Neutralized class "C" stage, using 211 tube, and equipped with antenna coupling circuit which matches practically any length antenna. MODULATOR: Class "B"—uses two 211 tubes. POWER SUPPLY: Supplied complete with dynamotor which furnishes 1000V at 350 MA. Complete instructions are furnished to operate set from 110V AC. SIZE: 21 1/2 x 23 x 9 1/4 inches. Total shipping weight 200 lbs., complete with all tubes, dynamotor power supply, five tuning units, antenna tuning unit and the essential plugs. These units have been removed from unused aircraft but are guaranteed to be in perfect condition.


fer coils and condensers, and antenna tuning circuits—all designed to operate at top efficiency within its particular frequency range. Transmitter and accessories are finished in black crackle, and the milliammeter, voltmeter, and RF ammeter are mounted on the front panel. Here are the specifications: FREQUENCY RANGE: 200 to 500 KC and 1500 to 12,500 KC. (Will operate on 10 and 20 meter band with slight modification.) OSCILLATOR: Self-excited, thermo compensated, and hand calibrated. POWER AMPLIFIER: Neutralized class "C" stage, using 211 tube, and equipped with antenna coupling circuit which matches practically any length antenna. MODULATOR: Class "B"—uses two 211 tubes. POWER SUPPLY: Supplied complete with dynamotor which furnishes 1000V at 350 MA. Complete instructions are furnished to operate set from 110V AC. SIZE: 21 1/2 x 23 x 9 1/4 inches. Total shipping weight 200 lbs., complete with all tubes, dynamotor power supply, five tuning units, antenna tuning unit and the essential plugs. These units have been removed from unused aircraft but are guaranteed to be in perfect condition.

BENDIX SCR 522—Very High Frequency Voice Transmitter-Receiver—100 to 156 MC. This job was good enough for the Joint Command to make it standard equipment in everything that flew, even though each set cost the Gov't \$2500.00. Crystal Controlled and Amplitude Modulated—HIGH TRANSMITTER OUTPUT and 3 Microvolt Receiver Sensitivity gave good communication up to 180 miles at high altitudes. Receiver has ten tubes and transmitter has seven tubes, including two 832's. Furnished complete with 17 tubes, remote control unit, 4 crystals, 24 volt dynamotor and the special wide band VHF antenna that was designed for this set. These sets have been removed from unused aircraft and are guaranteed to be in perfect condition. We include free parts and diagrams for the conversion to "continuously variable frequency coverage" in the receiver. The cost of this unit is only \$37.95.

BRAND NEW 12 VOLT DYNAMOTOR for SCR 522—\$12.00, 24 volt dynamotor—\$6.00. Used SCR 522, less dynamotor, remote control unit and antenna—as is—\$19.95. Wide band VHF antennas—\$1.95.

BRAND NEW BC 348 COMMUNICATIONS RECEIVER

Featuring coverage from 200 to 500 Kc. and 1500 to 18,000 Kc. on a direct reading dial with the finest vernier drive to be found on any radio at any price—high sensitivity with a high degree of stability—crystal filter—BFO with pitch control—standard 6 volt tubes. Contains a plate supply dynamotor in a compartment within the black crackle finished cabinet, the removal of the dynamotor leaves plenty of room for the installation of a 110V, 25 or 60 cycle power supply. These receivers, which make any civilian communications receiver priced under \$200.00 look cheap and shabby by comparison, are only \$69.95 brand new. Power supply kit for conversion to 110V 25 or 60 cycles, is only \$8.50 additional.

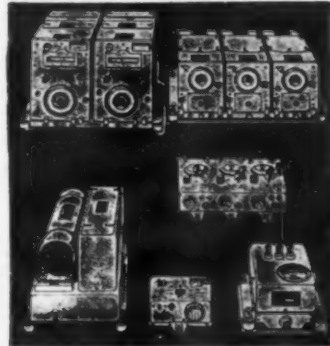


SCR-274N COMMAND SET

The greatest radio equipment value in history.

A mountain of valuable equipment that includes 3 receivers that use plug-in coils, and consequently can be changed to any frequencies desired without conversion. Also included are two Tuning Control Boxes; 1 Antenna Coupling Box; four 28V. Dynamotors (easily converted to 110V. operation); two 40-Watt Transmitters including crystals, and Preamplifier and Modulator. 29 tubes supplied in all. Only a limited quantity available, so get your order in fast. Removed from unused aircraft and in guaranteed electrical condition. A super value at \$29.95, including crank type tuning knobs for receivers.

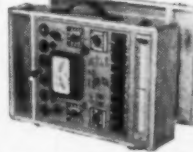1948 MODEL MUTUAL CONDUCTANCE TUBE TESTER\$49.95



No possibility of good tubes reading "Bad" or bad tubes reading "Good" as on dynamic conductance testers or other ordinary emission testers. Attractive panel and case equal to any on the market in appearance. . . . Large 4 1/4" meter. . . . Calibrated micromho scale as well as a Bad-Good scale. . . . Front panel fuse. . . . Individual sockets for all tube base types—voltages from .75 volts to 117 volts and complete switching flexibility allow all present and future tubes to be tested regardless of location of elements on tube base. . . . Indicates gas content and detects shorts or opens on each individual section of all octal, octal and miniature tubes including cold cathode, magic eye and voltage regulator tubes as well as all ballast resistors. Name of the nationally known manufacturer withheld because of special price offer.

Model "C"—Sloping front counter case. . . . \$49.95
Model "P"—Handsome hand-rubbed portable case. . . . 54.95
Built-in roll chart with either of above \$5.00 extra.

SUPER SPECIALS YOU CAN'T NEGLECT

GOVT. AUDIO AMPLIFIER using 6V6's. 2 mike inputs and output at various impedance taps brought to jacks at rear panel. 9" high x 9" long x 6" deep. Shipping weight 18 lb. 2 Tech manuals and tubes included.—\$4.95.
Headphone Scoop—HS30 headsets in guaranteed perfect condition. Rubber earpieces included. 59c per pair OR 3 PAIRS FOR \$1.00.

RT-1579 consists of a three stage (cascade 6SJ7's and 6F6 output stage) high gain, high fidelity amplifier with 60 cycle, 110V power supply on the same 13 1/2 x 14 1/2 chassis, which is protected by a substantial steel cover over tubes and parts. Made by Western Electric with typical quality components such as a husky power transformer and oil condensers, this unit is obviously intended to give years of trouble-free service with no more need for repairs than a telephone. Disconnecting one wire each, from the special input and output filters, will result in as high a fidelity amplifier as can be obtained. Your cost with tubes, diagram and parts list included—\$14.95.

We also offer the **RT-1579** with a Raytheon Magnetic Voltage Regulator already installed beneath the cover. Imagine an amplifier complete with tubes, built to Western Electric quality standards, and immune to line voltage variations besides, making it perfectly suited for the most difficult industrial, circus, carnival, or commercial installations, offered for a total price of only \$19.95, our price for both units.

IMMEDIATE DELIVERY ON THESE SUPER-SPECIALS IN TEST EQUIPMENT!

MODEL 431

AC-DC Volt-Ohm-Milliammeter
Volts DC: 0-30/300/1500, at 2000 ohms-per-volt
Volts AC: 0-15/150, at ohms-per-volt
Milliamperes DC: 0-150
Ohms: 3000/300,000
Employs sensitive 425 microampere square meter, on aluminum panel. Two jacks are used for all ranges, by means of rotary selector switch. In handsome steel case, with snap-on carrying strap, complete with test leads. Shipping weight, 4 lbs.

YOUR COST, \$15.00



SIMPLEX VOLT-OHM-MILLIAMMETERS

These two instruments are housed in bakelite cases, and employ 2-inch meters.


MODEL 371

Volts DC: 0-3/15/30/300
Milliamperes DC: 0-25
Ohms: 0-10,000
With self-contained battery.

YOUR COST, \$4.55

MODEL 312

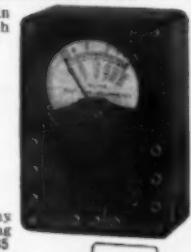Volts AC and DC: 0-25/50/125/250
Milliamperes AC and DC: 0-50
Ohms: 0-100,000
Capacity Meter: -.05 to 15 Mfd.
This instrument operates from any 110V AC or DC outlet. Shipping weight, 2 lbs. YOUR COST, \$5.85



MULTI-RANGE AC-DC VOLT-OHM-MILLIAMMETER WITH OUTPUT RANGES

MODEL 458

Volts DC: 0-5/10/50/100/500/2000, 1000 ohms-per-volt
Volts AC: 0-12.5/25/125/250/1250
Milliamperes DC: 0-1/10/100
Milliamperes AC: 0-2.5/25/250
Ohms: 0-1000/200,000/2,000,000
Output: -5 to +55 Decibels
Overall Accuracy: -1%



5 1/2 INCH RECTANGULAR METER

with two-tone aluminum scale, set at a 45° angle for easiest reading. Special-treated aluminum panel, mounted on a wrinkle finish welded steel case, equipped with rubber feet and collapsible handle for portability. Complete with self-contained battery and test leads. Shipping weight, 8 lbs.

YOUR COST, \$25.20

FEATHERWEIGHT MINIATURE MODELS

Just slightly larger than a pack of cigarettes, though they feature high accuracy, large, easily readable scales, and rotary-switch range selection. Average weight, only 12 oz.; shipping weight, 2 lbs.

MODEL 450

Volts DC: 0-5/10/50/500/1000, at 1000 ohms-per-volt
Milliamperes DC: 0-1
Ohms: 5000/50,000/500,000

YOUR COST, \$10.60

MODEL 451

Volts DC: 0-10/50/100/500/1000
Volts AC & Output: 0-10/50/100/500/1000
Ohms: 0-500,000

10,000 ohms-per-volt on all ranges
Condenser is built-in for output ranges

YOUR COST, \$14.50

MODEL 452

Volts DC: 0-10/50/100/500/1000
Ohms: 200/20,000/200,000/2,000,000
10,000 ohms-per-volt on all ranges
Has sensitive 100 microampere meter

YOUR COST, \$14.50



BUFFALO RADIO SUPPLY, 219-221 Genesee St., Dept. 12C, BUFFALO 3, N. Y.
CABLE ADDRESS BUFRAD

END OF YEAR LEOTONE SPECIALS

RADIO HARDWARE TREASURE. Approx. 1000 screws, nuts, washers, hugs, etc. for many radio needs. \$9.49

ALNICO MAGNETS
Powerful ALNICO MAGNETS in many sizes and shapes always in stock. Write for latest fully descriptive illustrated supplement.

UTC "OUNCER" INPUT TRANSFORMERS (1/2"x1 1/4"). Dynamic mike or low impedance pick-up to grid. ea. \$9.49
12 for 5.00

EXPERIMENTAL TUBES. 20 asstd. receiving types for testing, research, etc. Fil. tested. \$1.00

3" MAGNETIC SPEAKER for Majestic portables or general replacement. \$2.25

HANDY RADIO PARTS KITS
#2—SPEAKER CONES; 12 asstd. 4" to 12" moulded and free-edge (magnetic incl.). Less voice coils. \$2.00
#3—MOULDED BAKELITE CONDENSERS; 50 asstd. .00001 to .2 mfd. 200-600 WV. Clearly marked. 2.95
#4—TUBULAR BY-PASS CONDENSERS; 50 asstd. .001 to .25 mfd. 200-600 WV. Standard brands. 2.49
#5—KNOBS; 25 asstd. set screws, spring and push button. Wood and bakelite.98
#10—VOLTAGE DIVIDERS; 10 asstd. multi-tapped. High wattages included. 1.98
#20—SPEAKER REPAIR KIT. Save time and money with this professional kit. Contains: 25 paper rings, 25 voice coil forms, 10 spiders, 3 yds. felt strips, 20 chamolite leather segments, kit of 16 shims and tube of cement. 2.49
#27—PRECISION RESISTORS (Weston, Shallicross, etc.) ±1% wire-wound. 10 asstd. ohmmages to 400 K. 1.98
#28—ROTARY SELECTOR SWITCHES. Six asstd. standard makes. Incl. multi-deck and ceramic insul. 1.75

TUBES: Perfect condition, but not in sealed cartons. Most types in stock at up to 50% off list. Every tube guaranteed 90 days. \$0.29
#42, 45, 75, 76, 77, 78, 80, 89, 5Y3, 6H6 or 6K739
#35, 36, 37, 39, 84, 5Y4, 6C5, 6F5, 6J7, 6N7, 6U7, 6SA7, 6SK7, 12SA7 or 12SK7.49
#1A7, 1H5, 1N5, 1R5, 6U5, 6X5, 7A7, 7C5, 7CB, 7Y4 or 8059
TUBE CARTONS: Plain white. Per 100 \$1.25
GT size (1 1/2" sq. x 3 1/4") Per 100 1.49
Medium size (1 1/2" sq. x 4 1/4") Per 100 1.49
Large size (2" sq. x 5") Per 100 1.75

RCA VICTOR POWER TRANSFORMER for models R-32, 45, 52 or 75. Unshielded. \$5.95

VARIABLE CONDENSERS. 2 gang. 365 mfd. Ball bearing shaft; O.D. 3/4"x1/4". \$0.75

BENDIX AMPLIFIER (Line of Sight) 115 V. 400 cycle. Contains: power trans., 3 audios, 6 oil condensers, plus other components worth many times the price. Black crackle finish case. 7"x5 1/4"x4" Shpg. wt. 9 lbs. \$1.95

CRYSTAL MICROPHONE UNITS. Famous make, sensitive diaphragm type. Small size (1 1/2" O.D., 1/2" deep) ideal for REGULAR or CONTACT MIKE or PILLLOW SPEAKER. Rubber shock mtd. metal frame. Less housing. \$0.69

AUDIO TRANSFORMERS—3:1, DC. Resist.: 800/7000. Hermetically sealed. 2x1 1/2"x1 1/2". \$0.69

LINE TRANSFORMER (intercom., P.A., phone, etc.) Impedance: Pri. 250 ohms; Sec. 8 ohms with 5 equal taps. —16 to 0 db. 2" O.D., 2 1/2" high.69

5 V. TELEGRAPH KEY AND BUZZER (W.E.). Fully adjustable platinum contacts. 1/2" bakelite base. \$1.25
Key only39

Get on our mailing list—Always something new!
PROMPT SERVICE ON ALL SPEAKER AND PHONO PICK-UP REPAIRS
Minimum Order \$2.00—20% Deposit Required on All Orders. Please Add Sufficient Postage. WRITE DEPT. RN-12

LEOTONE RADIO CO.
MAKERS OF CONES AND FIELD COILS
65-67 DEY STREET, NEW YORK 7, N.Y.
WORTH 2-0284-5
12,000 SQ. FT. OF RADIO PARTS

of the power supply. A .1 μ fd. condenser (C_3 - C_4) should be connected between the screen grid and ground, to bypass to ground all fluctuations resulting from the radio frequency action on the electron stream inside the tube. This r.f. fluctuation, were it allowed to reach the d.c. power supply, could easily produce oscillations or other unwanted disturbances in the amplifier.

Plate circuit connections should follow, and it is well worth emphasizing again, that plate leads should be kept close to the chassis. The incorporation of the two resistor-condenser plate filters (R_1 - C_1 and R_2 - C_2) aid substantially in reducing interaction between stages.

The cathode circuit should now receive our attention and the two 100-ohm bias resistors (R_3 - R_4) should be connected between the cathodes of the tubes and the 10,000-ohm potentiometer (R_5) which is used as a sensitivity control. The two condensers C_3 and C_4 should be connected between the cathodes and ground to smooth out the r.f. fluctuations.

The germanium diode is furnished with tinned pigtailed, and no soldering precaution is necessary other than that which one would exercise in connecting a resistor.

The power supply should present no problem other than the correct connections to the selenium rectifiers. The positive terminal of the Sylvania NC5 rectifier is marked "CATH." It is from this terminal that we get the positive d.c. output. Normally, these rectifiers are used directly from the power line but in our voltage doubler application complications will be introduced with respect to grounding of the chassis, etc. The use of two filament transformers connected as previously explained overcomes this problem, as well as supplying an isolated source of filament voltage.

Testing

Assuming that the wiring has been in accordance with the schematic diagram (Fig. 2), we are now prepared to test the unit. This testing can be successfully accomplished using a good volt-ohmmeter and a signal generator. More advanced testing can be per-

formed using an oscilloscope and an electronic voltmeter.

The signal generator need only cover the broadcast band (550 to 1600 kc.), since the tuner employs no i.f. amplifier. Should the reader not have access to a test oscillator of any kind, broadcast station carriers may be used conveniently. It is best to select three stations, one near the lower end of the broadcast band, one near the middle, and one near the high end. For this testing only, use the shortest antenna which will deliver good signals.

The reader should allow $\pm 10\%$ tolerance on all resistance or voltage measurements mentioned in the paragraphs which follow, unless otherwise stated. Step 1 in the testing and calibration program is a resistance check of the power supply. Connect the ohmmeter from point "A" (Fig. 2) to chassis. The resistance should be 50,000 ohms. Should the reading obtained be in excess of the $\pm 10\%$ allowed, check the filter condenser C_{18} for a shorted condition, and the bleeder resistor R_{13} for an open condition.


Connect the primary of the power supply to the 115 volt line and test voltages present at the filament of the tubes. This should be 6.3 volts. Having satisfied ourselves of the presence of the correct filament voltages, attention should be transferred to the plate supply. The d.c. voltage present at point "A" should be 250 volts, and at both plates should be 240 volts. The screen grid terminals should measure 100 volts.

We are now ready to apply our test signal. Connect a pair of high impedance headphones to the phone jack. Connect the output of a 400 cycle modulated r.f. generator to the antenna and ground posts of the tuner and adjust the frequency of the generator to 1500 kc. Also rotate R_1 of amplifier fully clockwise. The moving contact arm should now be located at the end of the potentiometer which is connected to the 100 ohm cathode bias resistors. If this is not so, change the end connection.


Rotate the tuning condenser (C_1) until the rotor plates are located at minimum capacitance (completely

(Continued on page 114)

Fig. 6. Under chassis view of t.r.f. tuner shows location of component parts.

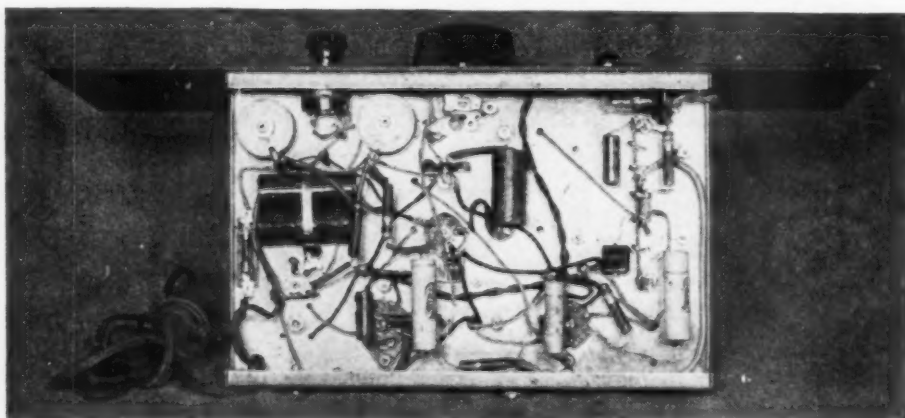

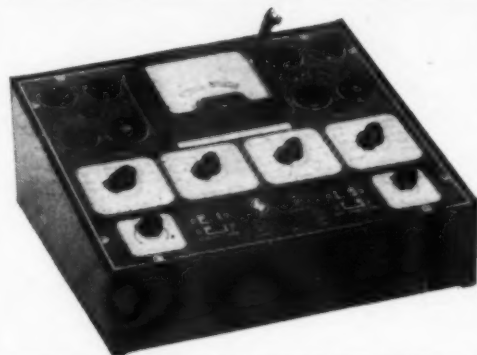MONEY BACK GUARANTEE We believe units offered for sale by mail order should be sold only on a "Money-Back-If-Not-Satisfied" basis. We carefully check the design calibration and value of all items advertised by us and unhesitatingly offer all merchandise subject to a return for credit or refund. You, the customer, are the sole judge as to value of the item or items you have purchased.



The New Model 60-T TUBE and SET TESTER

A COMPLETE TUBE TESTER

Tests all tubes including the new post-war miniature lectals such as the 12AT6, 12AU6, 35W4, 50B5, 117Z3, etc. • Tests by the well-established omission method for tube quality, directly read on the scale of the meter. • Tests shorts and leakages up to 3 Megohms in all tubes. • Tests leakages and shorts of any one element against all elements in all tubes. • Tests both plates in rectifiers. • Tests individual sections such as diodes, triodes, pentodes, etc., in multi-purpose tubes.

\$49⁸⁵
NET PRICE

Model 60-T operates on 90-120 Volts 60 Cycles A.C. Housed in sloping leatherette covered cabinet. Comes complete with test leads, tube charts and detailed operating instructions.

A COMPLETE MULTI-METER

- 6 D.C. Voltage Ranges: 0 to 7.5/15/75/150/750/1,500 Volts
- 6 A.C. Voltage Ranges: 0 to 15/30/150/300/1,500/3,000 Volts
- 4 D.C. Current Ranges: 0 to 1.5/15/150 Ma. 0 to 1.5 Amps.
- Low Resistance Ranges: 0 to 2,000 Ohms (1st division is 1/10th of an ohm.)
- 2 Medium Resistance Ranges: 0 to 20,000/200,000 Ohms
- High Resistance Range: 0 to 20 Megohms
- 3 Decibel Ranges: -10 to +38, +10 to +38, +30 to +58 DB.

EXTRA: WE CAN NOW SUPPLY THE MODEL 60 HOUSED IN A BEAUTIFUL HAND-RUBBED OAK CABINET. COMPLETE WITH PORTABLE COVER MAKING IT SUITABLE FOR EITHER BENCH OR OUTSIDE USE. ONLY \$2.75 ADDITIONAL. SPECIFY MODEL 60-C

The New Model 650-A A.C. Operated SIGNAL GENERATOR



- Operates on 110-120 Volts 50 to 60 Cycles A.C.
- R.F. Frequencies from 100 Kc. to 35 Mc. on Fundamentals in 5 bands by front panel switch manipulation. One additional band provides Harmonics from 30 to 105 Mc.
- Audio Modulating Frequency—400 Cycles Pure Sine Wave Distortion less than 2%.
- Attenuation Features a newly designed 3-step ladder type of attenuator (T pad). The first step provides lowest output and can be multiplied by 10 and by 100 by turning the multiplier switch.

• Hartley Excited Oscillator Electron coupled to a Buffer Amplifier. Frequency stability is assured by modulating the amplifier stage.

Complete with coaxial cable, test leads and instructions. Heavy gauge grey crystalline cabinet with beautiful two-tone etched front panel. Size 9 1/2" x 10" x 6".

\$39⁹⁵
NET

THE PREMIER BANDSPREAD DIAL SIGNAL GENERATOR

EXCLUSIVE FEATURE! The "PREMIER" Model 570 is the ONLY low-priced Signal Generator with a MICRO-MASTER BANDSPREAD DIAL, equivalent to a scale length of approximately 60"—a major feature for logging, sharp and critical tuning.



Air Trimmers on All Bands Triple Copper Plated Shielding

EFFECTIVE LINE FILTER—pure 400 cycle modulation (less than 5% distortion). Range 75KC-50MC on fundamental, and 50-150 MC on 3rd harmonic, useful for aligning FM and Television Receivers. Accuracy better than 1%. A.C.—115 volts, 50-60 cycles. Overall size—12"x12 1/2"x5 1/2". Shpg. wt. 21 lbs. Complete with co-axial cable and operating instructions.

\$54⁷⁵
NET

The New Model 670 SUPER METER

A Combination VOLT-OHM-MILLIAMMETER plus CAPACITY REACTANCE, INDUCTANCE and DECIBEL MEASUREMENTS

D.C. VOLTS: 0 to 7.5/15/75/150/750/1500/7500. A.C. VOLTS: 0 to 15/30/150/300/1500/3000 Volts. OUTPUT VOLTS: 0 to 15/30/150/300/1500/3000. D.C. CURRENT: 0 to 1.5/15/150 Ma.; 0 to 1.5 Amps. RESISTANCE: 0 to 500/100,000 ohms, 0 to 10 Megohms. CAPACITY: .001 to .2 Mfd., .1 to 4 Mfd. (Quality test for electrolytics) REACTANCE: 700 to 27,000 Ohms; 13,000 Ohms to 3 Megohms.

INDUCTANCE: 1.75 to 70 Henries; 35 to 8,000 Henries. DECIBELS: -10 to +18, +10 to +38, +30 to +58

THE MODEL 670 COMES HOUSED IN A RUGGED, CRACKLE-FINISHED STEEL CABINET COMPLETE WITH TEST LEADS AND OPERATING INSTRUCTIONS. SIZE 5 1/2" x 7 1/2" x 3".

\$28⁴⁰
NET



The New Model 450 TUBE TESTER

Speedy operation—assured by the newly designed rotary selector switch which replaces the usual snap, toggle, or lever action switches.

SPECIFICATIONS

- Tests all tubes up to 117 volts
- Tests shorts and leakages up to 3 Megohms in all tubes.
- Tests both plates in rectifiers.
- New type line voltage adjuster.
- Tests individual sections such as diodes, triodes, pentodes, etc., in multi-purpose tubes
- Noise Test detects microphonic tubes or noise due to faulty elements and loose internal connections.
- Uses a 4 1/2" square rugged meter.
- Works on 90 to 125 volts 60 cycles A.C.

EXTRA SERVICE—May be used as an extremely sensitive condenser Leakage Checker. A relaxation type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.

\$39⁵⁰
NET




GENERAL ELECTRONIC DISTRIBUTING CO. Dept. RN-12, 98 Park Place
NEW YORK 7, N. Y.



THE NEW

HEATH 5" OSCILLOSCOPE

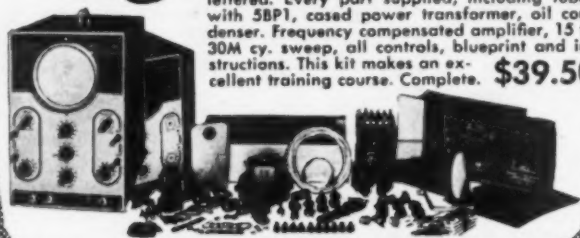Complete kit to build a beautiful 5" scope, cabinet, chassis and panel punched, formed and lettered. Every part supplied, including tubes with 5BP1, cased power transformer, oil condenser. Frequency compensated amplifier, 15 to 30M cy. sweep, all controls, blueprint and instructions. This kit makes an excellent training course. Complete. **\$39.50**




RCA RECEIVER MODEL ARB

A brand new Navy communications type receiver with BROADCAST BAND. Covers 200 KC to 9.1 MC continuous, has two RF stages, electric motor band switching, complete with calibrated dial, 6 tubes, control head, remote control box, 24 volt dynamotor, and circuit diagram.

\$29.50

LIMITED
QUANTITY
AVAILABLE

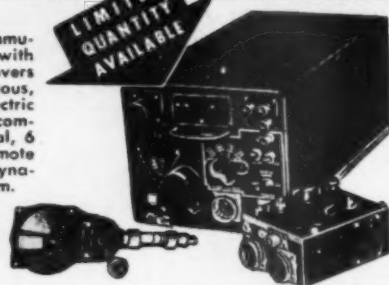

OIL FILLED CONDENSERS

CAP	WVDC	PRICE	CAP	WVDC	PRICE
5	400	\$.39	1.	1000	\$.49
5-5	400	.79	2.	1000	.69
4	400	.49	4	1000	.90
5	600	.59	8	1000	1.00
8	600	1.00	8-8	1000	1.95
2.5-2.5-5	600	1.50	.25	1500	.49
5-5-5	600	1.95	1.5	1500	.79
8-8-8-8	600	3.95	.1	3000	1.20
5-5	600	1.00	.25	3000	1.30
.1	1000	.29	.05	7500	2.50
.25	1000	.39			

BC 438 FREQUENCY METER


A beautifully constructed frequency meter, built by Link for Western Electric, 5 tube, AC OPERATED, covers 195 to 215 MC, comes complete with tubes, standard crystal, calibration chart, circuit diagram, in used condition. The excellently filtered 110V AC power supply alone worth our price of..... **\$14.50**



Only 40 available

BRAND NEW ARMY AIR FORCE ASTROGRAPH

The case of this unit makes the finest tool and service kit ever designed. Plywood construction, 14x11x10" high, with 8 covered compartments in the bottom for repair parts, leather handle, steel reinforced covers, hinged lid. Also excellent as case for radio phonograph, movie projector, camera, shell case, fishing kit, picnic kit, etc. The astrograph itself, (which cost the government \$125.00) makes an excellent contact printer, and can be used as a foundation for enlarger, strip map holder, etc. The case alone worth twice the give-away price of..... **\$3.95**

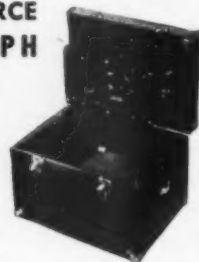

OIL FILLED BATHTUB CONDENSERS

200 Volt in .5, .1, dual .5 MFD.....	20 for \$1
400 Volt in .1, dual .1, triple .1, .2, .25, .5, 1, MFD.....	15 for \$1
600 Volt, .1 dual .1, triple .1, .25 dual .25, .5, 1.....	10 for \$1

PUSH BUTTON TUNER

This beautifully constructed unit was used on an Army FM receiver. A ten push-button assembly operating four gang silver plated tuning condenser drum dial manual tuning. Brand new. Shipping weight, 10 lbs..... **\$2.50**




SPECIALS

Selsyn Indicators 5" Brand New \$2.95
PE 104A power supplies operate from 6 or 12 volt input — output 84V plate 1.4 volt filament \$4.95
Ceramic Variable Condensers 50 MMF screw driver adj. Special 5 for \$1.00
Lip Microphones T-45 in original sealed cartons \$1.00
Thermocouples for RF Ammeters, 3 for \$1.00
10 henry 50 ma Filter Chokes 2 for \$1.29
5BP1 Cathode Ray Tubes \$2.49
5BP1 Socket79
Synera Motors 55DG Brand New, per pair \$6.95
Kit of Screw Driver Type Potentiometers 10 for \$1.00
Kit of Metal Tubular Bypass Condensers 20 for \$1.00
Kit of Relays, excellent types 5 for \$2.50

DYNAMOTORS

Consists of electric motor operating generator on same shaft. Many applications — operating radios from storage battery — using as motor.
Dynamotor A — Input 12 volts, output 1000 volts at 350 MA, **\$7.95**
Shipping weight, 72 lbs.
Dynamotor B — Input 6 or 12 volts, output 350 volts, 160 MA. **\$5.95**
Shipping weight, 30 lbs.
Dynamotor C — Input 28 volts, output 220 volts at 60 MA. **\$1.50**
Shipping weight, 6 lbs.

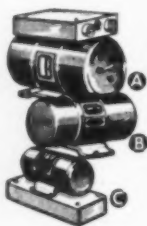

BC 457A TRANSMITTER

Brand new transmitters covering 4-5.3 MC. Contains M.O. 1625, two 1625's as P.A., these make excellent VFO from conversion in May 1946 CQ. Complete in original cartons with tubes..... **\$4.95**




ELECTRONIC KIT

Experimenter's paradise. Five lbs. of new condensers, transformers, coils, switches, sockets, resistors, selenium rectifier, earphones, etc. Parts for dozens of experiments. Shipping weight, 6 lbs. **\$1.00**



MINIATURE HEADPHONES

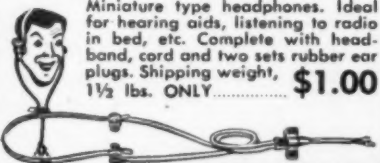Miniature type headphones. Ideal for hearing aids, listening to radio in bed, etc. Complete with headband, cord and two sets rubber ear plugs. Shipping weight, 1 1/2 lbs. ONLY..... **\$1.00**



BC 306 ANTENNA TUNING UNIT


GE unit from BC 375 matches 150 watt transmitter to antenna. Brand new..... **\$2.95**



RG-B/U FLEXIBLE COAXIAL CABLE


Only **4¢** PER FT.

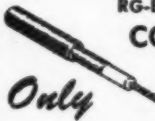Ideal for feeding any antenna up to 1 K.W. All frequencies up to 250 MC. Brand new any length. Lowest price ever offered.



TUNING UNIT

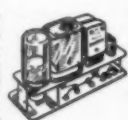
The heart of the Army Walkie Talkie. Contains transmitter crystal and tank coil, receiver coil, tuning condenser and crystal; ideal foundation for small set. Shipping weight, 1 lb. **\$1.00**



BC 223 TRANSMITTER

One of the most desirable military transmitters, 4 crystal-controlled frequencies and master oscillator. Meters for Osc., Ant., and total current. Uses 46 speech amplifier, 2-46 modulators, 801 each as oscillator and power amplifier. Practically no conversion necessary: plug in crystal, mike and connect power supply and it's ready to operate. Brand new with one tuning unit and circuit diagram. (less tubes)..... **\$12.95**

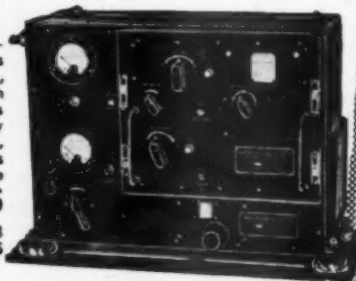Vibrator Power Supply PE 125 for BC 223 (12 V. operation) new \$9.95



NO ORDERS UNDER \$2. • • WE WILL SHIP C.O.D.



The HEATH COMPANY

BENTON HARBOR, MICHIGAN



WORLD'S FINEST SURPLUS BARGAINS..



THE NEW HEATHKIT VACUUM TUBE VOLTMETER KIT

The most beautiful VTVM ever offered now available in kit form. Every part supplied: all punched, lettered and formed.

A balanced bridge circuit, 11 megohms input resistance, measures both AC and DC electronically. Ranges 3-30-100-300-1000 volts AC or DC. Ohmmeter .1 ohm to 1000 megohms. Includes DB scale. Complete with tubes, 500 microamp meter, cabinet, blueprints, and instructions. Shipping Wt., 8 lbs.

BUILD IT YOURSELF AND SAVE 2/3 COST

\$24.50

TELEVISION CONDENSER

Aerovox hyvol .05 MFD at 7500 volts Limited quan. **\$2.50**




OUR BEST CONDENSER BUY

An ideal power supply filter has 2.5 MFD., 2.5 MFD., and 5 MFD., sections at 600 V. working. All oil filled, extra special **95c**

CONDENSER SPECIAL

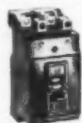Brand new Cornell-Dubilier 2 MFD. 600 V. oil filled filter condensers, porcelain insulators. **3 FOR \$1.00**




G.E. CIRCUIT BREAKER

Protect your equipment at one-fourth of cost, new G.E. 50 amp. 220 V. circuit breakers **\$2.95**

4 Gang CONDENSER

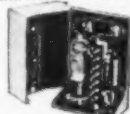A silver plated 147 MFD. per section variable tuning condenser — long 1/4" shaft, an outstanding surplus buy **\$1.00**



AIRCRAFT INTERPHONE AMPLIFIER

New BC 347C using 6F8 tube with tube socket, transformers, diagrams, etc. **\$2.95**

2 1/2" VOLTMETER

Ideal for making pocket tester, scale 0-3 D.C. volts, made by Weston and Simpson. Tester diagram and Multiplier Resistors for 30-300 V. D.C. included **\$1.95**



MILITARY CONVERSION POWER TRANSFORMER




Especially for 24 volt receivers. Supplies 500 volts C.T. at 50 MA, 5 V. at 2A. and 24 V. at 1/2 amp. To convert command sets without rewiring **\$2.95**

MODEL BC 375 TUNING UNITS

These units need no introduction but ours are brand new with the cabinet, which is ideal for a receiver case, at the lowest price yet. State model number preferred and we will ship as close as we can.

At least a \$30.00 value in parts for

\$2.49

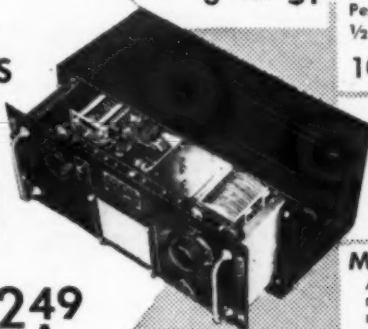

TRIMMER CONDENSER KIT

10 brand new variables 12 MMF to 50 MMF ceramic insulated. **\$1.00**



VITREOUS RESISTOR KIT

Five and ten watt units. **15 FOR \$1**




455 KC I.F.'s

Dual slug tuned square can. **3 FOR \$1**



BATHTUB CONDENSER KIT

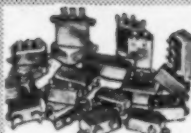.1 MFD. to 1. MFD. up to 600 Volt. **20 FOR \$1.00**




TRANSMITTER CRYSTAL KIT

4 mounted crystals between 2 MC and 3 MC. **4 FOR \$1**



SOCKET KIT

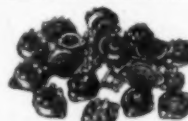20 beautiful octal, octal and miniature sockets. **20 FOR \$1**



R.F. CHOKE KIT

Perfect sizes from 1/2 to 2 1/2 MH. **10 FOR \$1**



POWER RHEOSTAT KIT

All knob types in 25 and 50 watt I.R.C., etc. **5 FOR \$2.95**



MICA CONDENSER KIT

An excellent assortment with silver mica and regular. All color coded or marked. **25 FOR \$1.00**



MODEL BC 728 PUSH BUTTON RECEIVER

An excellent portable push button permability tuned receiver covering 2-5 Mc. Easily converted to broadcast band, operates from 2 or 6 volts with six tubes. PM speaker — two vibrator power supplies slightly used. Only 100 available **\$14.95**




CERAMIC CONDENSER KIT

20 beautiful condensers all marked or coded, many zero temp. coef. types. **20 FOR \$1.95**



RESISTOR KIT

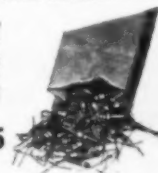The best available all insulated color coded in 1/2-1-2 watt sizes. **100 FOR \$1.95**



BC 645 GENERAL ELECTRIC TRANSMITTER-RECEIVER

A beautiful brand new tranceiver operating in the 450-500 Mc range. Comes with 15 new tubes (list price tubes alone \$58.00) and all conversion data and diagrams. Covers 420-450 ham band, citizens two way communications band, mobile ham band, and Exp. television band. Cost government over \$400.00. Our price complete. **\$14.95**



BC 733 RECEIVER
A Western Electric 10 tube receiver cover 100-120 Mc. complete with 10 tubes, crystals, etc. Used condition. **\$7.95**

NO ORDERS UNDER \$2.00 WE WILL SHIP C.O.D.

2 FOR \$27.00

FREE

T30 Throat Microphone with each order over \$10.00.



The HEATH COMPANY
BENTON HARBOR, MICHIGAN

 Living Room Concerts	<i>More Economical</i>	 Airport & Train Announcements	<i>Cannot Tangle</i>	 Broadcast Station Monitoring
<i>Longer Playing Time</i>	Now Available! 8 HOURS OF CONTINUOUS PLAY ON THE MAGNETAPE* RECORDER!			<i>30 Second Rewind</i>
 Industrial Factory Work Music	 <p>Now — record and play back on this amazing instrument any sound that can be heard, and many that cannot — from a concert hall symphony, to the beat of your heart. Simple interchangeable capstans provide a choice of three tape speeds for high fidelity, medium fidelity, or up to 8 hour voice recording. The ideal recorder and playback unit for home, office, industry, and broadcast station.</p> <p>Write today for our free illustrated technical catalog featuring our complete series of Magnetape Recorders, and accessory equipment. Send 25¢ in stamps or coin for our new booklet, "Elements of Magnetic Tape Recording — and 999 Applications." * Trademark</p>			 Conference Recording
<i>Quieter Operation</i>	 Copying Valuable Disc Records			<i>Easy Editing</i>
 Passenger Entertainment	<i>Improved Response Range</i>	 Recorded Lectures		<i>Complete Automatic Erasing</i>

AMPLIFIER CORP. of AMERICA

398-2 Broadway, New York 13, N. Y.

"You can really solder with a G-E Handy Iron"

THAT'S what Mr. ReQua says about his G-E Handy iron. "It gives fast, continuous heat, lets me solder rapidly," he states. "It's ideal for the average repair job around the house. The more I use it, the more I like it."

Mr. ReQua has reason to like his Handy iron. For it has same design as G-E industrial irons, yet is lightweight, easy to use, built to last. See the G-E Handy iron at your dealer's today. If your dealer does not have them order direct, giving us your dealer's name. Dept. D667-4, Apparatus Department, General Electric Company, Schenectady, N. Y.

Free: "How to solder" manual with every iron.



George ReQua, hobbyist and home craftsman.

GENERAL ELECTRIC

THE SIMPLEST FM CONVERTER



Models
1002A
1005A

Converts 40-50Mc FM Tuners and receivers to 88-108Mc operation. Simple to attach and adjust. No power required. Hundreds now in use all over U.S.

Model 1002A List \$10.00

FM INTERFERENCE TRAP FOR TELESSETS

Eliminates FM and amateur interference from tele image by absorption of interfering signal. Two adjustments provide for elimination of signals in 80-115Mc and 40-60Mc Ranges.

Model 1005A List \$10.00

CRYSTAL CONTROL FOR FM TV AND BC RECEIVERS

Send 25c (no stamps) for booklet describing applications of quartz crystal control for local oscillator of your home receivers.

See Your Local Parts Jobber
or write for information

CRYSTAL DEVICES CO.
1819 Broadway, NEW YORK 23, N. Y.

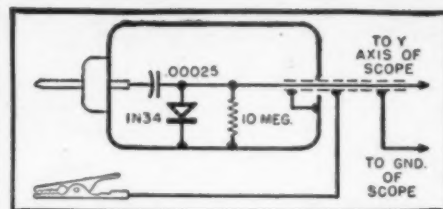


Fig. 7. The r.f. probe.

open). Adjust output of the signal generator until a signal is heard in the headphones. To adjust the amplifier, vary the trimming condensers located on the main tuning condenser C_1 until the signal is loudest. As the signal increases above the comfortable listening point, reduce signal strength by lowering the output of the signal generator. In cases where a radio station carrier is used in place of a signal generator, the signal strength may be reduced by shortening the antenna wire.

More advanced readers may adjust the unit with the aid of an oscilloscope. The amplitude of the wave represents the measured voltage output and at the same time the distortion of the amplifier may be visually inspected. To do this properly, proceed as follows:

Step 1. Connect output of signal generator to the antenna-ground input of the amplifier.

Step 2. Connect ground of scope to chassis of amplifier.

Step 3. Connect generator, scope, and amplifier to line and warm up for 15 minutes to stabilize these units so that accurate measurements may be taken.

Step 4. Connect the circuit shown in Fig. 7 in series with the Y axis input of the scope and the antenna ground of the amplifier, and note the audio waveform on the scope. Inasmuch as this represents the output of the generator, the reader will have an excellent source of comparison as we proceed with our stage-by-stage visual alignment.

Step 5. Transfer the probe to the grid of the first 7B7 tube and note the waveform and voltage gain on the scope. An amplification of about 1.5 should be experienced.

Step 6. Transfer the probe to the plate of the first r.f. tube, adjust the trimmer of the first stage tuning condenser C_1 until the amplitude of the waveform present on the screen of the oscilloscope reaches maximum. This waveform should be the same shape as that noticed directly from the generator. If any noticeable distortion of this waveform is experienced, readjust R_2 . If readjusting R_2 does not clear up the defect, check R_1 for correct value of resistance and check C_2 for either an open or shorted condition. Another possible source of distortion is that C_3 may be open. This would most likely cause oscillation and reduce the stage gain. This distortion procedure also holds true for the second r.f. stage.

Step 7. Proceed to align and check the next stage of the unit in the same

RADIO NEWS

manner, moving the probe to the plate of the second r.f. tube.

Step 8. To complete the visual alignment, we shall discard the r.f. probe and connect the Y axis input of the scope to the junction of C_{10} and C_{11} . The waveform now present on the screen of the scope is that of the audio output from the detector. The waveform at this point should be comparable to that witnessed at the first and second r.f. stages. The trimmer on the third stage tuning condenser (C_3) should be adjusted for maximum amplitude.

Step 9. With the scope connected as in **Step 8**, readjust the three trimmers of the tuning condenser C_1 for maximum output. The over-all gain of the amplifier at 1000 kc. is approximately 1200.

Although the tuner described is sensitive enough to pick up strong signals with a random length of wire, we strongly urge the use of the best possible antenna. For maximum efficiency, a long wire, well insulated, and mounted outdoors as high in the air as possible, is recommended. A simple single wire is entirely adequate.

(To be continued)

Signal Generator

(Continued from page 59)

upon the setting of the "Modulation" panel knob (R_{10}) at power line frequency rate, thus eliminating the need for special synchronizing conditions between signal generator and oscilloscope.

As a result of this frequency modulation action, the output signal is varied above and below its center frequency. The fixed oscillator signal is proximity mixed with the variable oscillator output. Because of the heterodyne action, the output frequency delivered by the signal generator is any possible combination of 40 megacycles plus and minus the frequency to which the main dial is set. (For example: When the main dial is set to 10 mc., frequency modulated outputs are obtained at 30 mc. and at 50 mc. The first is 40-10 mc.; the second, 40+10 mc.) To determine the dial setting required for any center frequency needed for FM alignment, it is only necessary for the operator to add or subtract the desired frequency mentally to (or from) 40 mc., and then to set the main dial of the generator to either this sum or difference frequency. Either one of these settings will give output on the desired center frequency.

The range of frequency-modulated center frequencies delivered by the Model 906 is 90 kc. to 210 mc.

The unit becomes an emergency beat-frequency audio oscillator when the main dial is tuned to the vicinity of 40 megacycles. (With "Modulation" switch set to FM, and sweep width set to zero). This is because the heterodyne beat note between the fixed- and variable-frequency oscil-

TELEVISION


Sensational ASSEMBLY UNIT



For the first time — a 10" Flat Surface Screen Picture unit available in assembly form. This is not a kit but a complete assembly. Picture is 51 square inches.

Also available

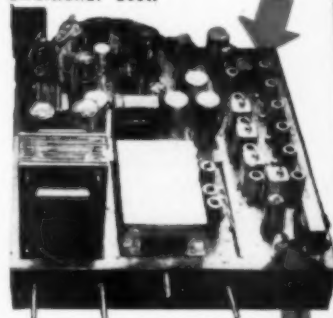A 12" Screen picture, 75 square inches, at a slight additional cost.



Superior performance is obtained with a new IF Video & Sound Strip (pat. pend.), aligned, wired, pre-tuned tubed and tested. All the above circuits are contained on one chassis, ready to use when delivered. This unit designed and constructed by engineers. Licensed by Western Electric & Radio Corporation of America.

Easier to operate than your home radio.


10" FLAT SURFACE

C R TUBE INCLUDED

\$229.50

51 SQ. IN. PICTURE COMPLETE WITH ALL TUBES AND COMPONENTS

PRICE F.O.B. OUR FACTORY

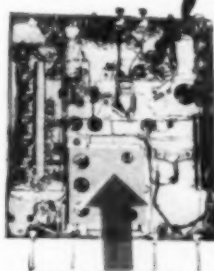

FRONT END

IF STRIP

ALSO AVAILABLE

12" C R TUBE INCLUDED

\$259.50

75 SQ. IN. PICTURE COMPLETE WITH ALL TUBES AND COMPONENTS

PRICE F.O.B. OUR FACTORY

GUARANTEED

To operate to your satisfaction when simple directions are followed.

- FRONT END will handle 13 Television Channels. It is so flexible that any number of channels from 1 to 13 can be used. We are now supplying channels 2 - 4 - 5 - 7 - 9 - 11 - 13 with this front end. Install the other channels as desired. Aligned and tested, ready to use when delivered. Merely connect B plus, filament and output I.F. leads to the television chassis. It is not necessary to make any R.F. alignments.
- 29 RCA Tubes included plus 10" flat faced CR tube or 12" CR tube
- Heavy Duty RCA 6.8 oz. slug 12" PM speaker
- Specially designed dipole antenna with 60 foot lead in.
- 4.5 mc band width for greatest picture definition.
- Approximately 10,000 volts second anode potential for better contrast and brightness.
- 5 IF picture stages
- 2 sound IF stages with Limiter and Discriminator
- High fidelity obtained with FM sound reproduction
- Overall chassis size 17"x19"x3"
- Complete pictorial and schematic diagrams supplied with assembly
- IF frequency — Audio 21.6 Picture 26.1
- Only nationally advertised components used in our assembly.

TERMS: 10% WITH ORDER — BALANCE EXPRESS COLLECT

TELEVISION ASSEMBLY CO.

540 BUSHWICK AVE.
BROOKLYN 6, N. Y.

TEST UNIT 1-35-E

One of the component units required to test the "Walkie Talkie" Transmitter and Receiver BC-611. Consists of a 4" rectangular multi-range meter. Switching facilities. Microphone, receiver, earphone. R.F. oscillator, audio oscillator, crystal, test socket, pin jacks, test terminal cable & plug. Comes in cabinet with removable cover 9" wide, 14" long & 5" high with Technical Manual and circuit diagram. Full scale ranges of 3 & 150 V D.C.; 1.5, 15, 60 & 600 MA D.C.; and 60 & 1 A.C. Suitable for modification into a versatile radio test unit. **\$13.50**

NET FOB, N.Y.

BC-1072-A RADAR TRANSMITTER

150 to 210 Megacycles. Operates off 115 volt, 60 cycle power line. This unit can be adapted to a 2 meter band transmitter but its chief value is for the parts it contains.

BLOWER. 115 volt 60 cycle 28 watts .38 1525 R.P.M. A.G. Redmond.

VARIAC. Gen. Radio type 200 B 115 volt input 135 volt 1.5 amps. Max. output.

TUBES. 2-5U4G; 1-807; 1-2X2; 1-6SN7; 1-6J5; 1-6X6; 2-9000; 2-926.

METER. Simpson, 3 1/2", round, 0-5 Kilovolt and 0-10 M.A. D.C.

TRANSFORMERS. 1—with primary variable from 0-135 volt, secondary from 0-3500 volt; 1—with primary 117 volt secondary 6.3 V at 1.2 Amp. 275 volt center tap at each side, 5.0 volt at 5; Amp.; 1—with 117 volt primary, secondary 4 volt at 16 amp. and 2.5 volt at 1.75 amp.

Consists also of many other parts, relays, transformers, circuit breakers, interlocks, resistors, chokes, too numerous to itemize.

Complete in metal cabinet 18"x20" by 17 1/2"; net wt. 150 lbs. **\$22.50**

NET FOB, N.Y.

FILAMENT TRANSFORMER. G.E. 110 volt, 60 cycle input, 2.5 volt 40 Amp. Output 100 KVA 3 KV. Insulation. @ \$2.75 each. Ten for... **\$17.50**

STEP DOWN TRANSFORMER. J.E. 115 volt 1.15 volt 60 cycle primary 20 volt, 10 Amp. secondary, mounted in watertight box. @ \$3.95 each. Ten for... **\$39.50**

VARIABLE RHEOSTAT. Ward Leonard 2" Class, 20 ohms 4.05 Amps. Complete with all hardware @ \$3.50 each. Ten for... **\$35.00**

INVERTER PE-206-A

INPUT: 27.5 Volt 38 Amps D.C.
OUTPUT: 80 Volts 500 V.A. 800 cycle 1.0 P.F.
1 phase 6000 R.P.M.
Manufactured by the Leland Electric Co., Type 2DA. Complete with filter, carbon pile regulator, selenium rectifier, etc., with circuit diagram and handbook of maintenance instructions. Dimensions 13" L x 10" H x 6" W. **NET FOB, \$6.50**

POWER LEVEL INDICATOR

Weston Model 695 Type 3 A. A rectifier type voltmeter with 5 ranges of 1.5, 6, 15, 60 and 150 volts and

A multirange DB meter for a zero signal level of 6 milliwatt on a 500 ohm line. Arranged to indicate -8, +4, "0", +10, +16, +20, +24, +28, +32 DB at "0" on the DB scale or a total spread of 56 DB.

A plate fastened on back of instrument gives instructions and conversion data for use on other than 500 ohm circuits.

Dimensions 3 1/2"x3 3/4"x3 1/4". **NET... \$19.50**

D.C. MOTOR—Permanent Magnet Type 10,000 R.P.M. Delco Type 3569370 27.5 Volt D.C. 2 1/2", Long (1/2 shaft) x 1" W x 1 1/4" High. **\$4.95**

PANEL METERS

Signal Strength ("S") Meter—Simpson 25, 3 1/2", rd fl bake case. Use this on the plate circuit of your receiver to show the relative strength of incoming signals. Sc calibrated—0 to 100 DB above 1 microvolt. 3 MA Zero right mvt with translucent sc, for internal ac illumination from rear of meter. Comp with socket lamp and leads. For further details refer to pages 164-165 & Fig. 730 B of Radio Amateur's Handbook. **\$4.50**

Decibel Meters—Weston 301, Type 12, 3 1/2", rd fl bake case, minus 10 to plus 6, 6 M.W., 600 ohms; General purpose type 0.5—0.7 Second to final reading, 45-62% overthrow, 5000 ohms internal resistance at ODB. **\$8.50**

—W.H., RC-35, minus 10 to plus 6, ODB equals 1.807 V, 6 M.W., 600 ohms, 3" square. **\$4.50**

Totalizing Hour Meters—G.E., 3 1/2", rd fl bake case; Up to 9,999.9 hrs. Operates on 10-12 volt, 60 cycle. Ideal for counting the total hours of operation of the power tubes on transmitter etc. **\$3.50**

—Industrial Timer Corp., Indicates up to 9,999.9 hrs for 50 or 60 cycle operation on 105 to 135 volts. Black scale 3" rd fl bakelite case, Clamp mounted. **\$4.00**

Frequency Meters—J.B.T., 3 1/2", rd fl metal case 58-62 cycle, 5 reed, 100-150 volts. **\$4.50**

—J.B.T., 30-F, Dual range covers Frequency ranges from 48-52 cycles and 52 cycles. Dual element. Vibrating Reed type, 115 volt, 3 1/2", rd fl metal case. **\$5.95**

D.C. Voltmeters—W.E., 500 V, 1000 ohms per volt, 3 1/2", rd fl bake case, concentric style. **\$5.00**

—Weston 301, 3 1/2", 4 K.V. with external pre-resistor. **\$8.50**

—W.H., NX-35, 1.5 KV with 1000 ohm per volt, ext prec wire wound resistor & mtg clips, 3 1/2", rd fl bake case. **\$7.25**

—W.H., NX-35, 20 KV with ext prec wire wound 1000 ohms per volt resistor and mtg clips. **\$21.00**

D.C. Milliammeters—G.E., DO-41, 30 MA, 3 1/2", rd fl bake case. **\$3.25**

—G.E., DO-41, 50 MA, black scale, 3 1/2", rd fl bake case. **\$3.25**

—G.E., DO-41, 200 MA, 3 1/2", rd fl bake case. **\$3.25**

D.C. Microammeters—W.E., 100-0-100 microampere, approximately 950 ohms resistance, 3 1/2", rd fl bake case, concentric style. **\$4.50**

—Triplet, 100 ua mvt, approx 500 ohms resist, sc cal 0-3, 0-15 & 60 V MA, 4" Rect fl bake case. Knife edge pointer. **\$5.50**

—G.E., DO-41, 200 microampere mvt, Knife edge pointer, ac mtd "Set Carrier" supp with paper V.O.M.A. ac, 3 1/2", rd fl bake case. **\$4.95**

A.C. Voltmeters—W.H., NA-35, 15 V, (100 MA) 3 1/2", rd fl bake case. **\$3.95**

—W.H., NA-35, 150 V (10 MA) 3 1/2", rd fl bake case. **\$5.50**

All items are Surplus-New-Guaranteed. C.O.D.'s not sent unless accompanied by 25% Deposit. Orders accepted from rated concerns, public institutions, etc., on open account.

The above is only a partial listing of the many items we have in stock. Send for free circular. MANUFACTURERS, EXPORTERS, DEALERS—we invite your inquiries.

MARITIME SWITCHBOARD

336 Canal Street New York 13, N. Y.
Worth 4-8217

lators then lies in the audio-frequency spectrum. The instrument is not recommended for regular, continuous use in this manner, however, since it was not designed expressly for this application, and frequency stability accordingly is not too good at the low audio frequencies.

Attenuator. The r.f. signal from the oscillators is delivered to the attenuator through coupling condensers C_1 and C_2 . R_2 is the "fine control" potentiometer of the attenuator unit and is operated by means of the panel knob labelled "Microvolts."

The attenuator is of standard ladder-type design, except that it has been made a 4-step, instead of conventional 5-step unit, in order to minimize the detrimental effect of shunting capacitances and to reduce "strays" which are inescapable in any 5-step attenuator.

While the attenuator is not unusual in appearance, being of the same general design so frequently shown in print by instrument designers and technical authors, we point out here that the actual fabrication of an efficient attenuator is not so simple as first inspection of the circuit might lead one falsely to conclude. Attenuator design is a definite art acquired, it would seem, by long experience and "know how." Considerable cutting and trying were necessary after the fundamental design work, in order to evolve the successful attenuator in the signal generator shown here.

The "Multiply By" switch, S_1 , enables the operator to select any one of four r.f. output voltage ranges which multiply the "Microvolts" (R_1) setting by 1, 10, 100, or 1000. These ranges each may be multiplied by a further factor of 10 when the output r.f. voltmeter has been set to its "X10" deflection.

In order to standardize the attenuator, provision has been made in other signal generators for adjusting the oscillator r.f. output voltage so that exactly 1 volt r.m.s. (as indicated by a

self-contained v.t. voltmeter which is the basic hallmark of any true signal generator) is applied to the attenuator input. In order to obtain 1 microvolt from the instrument, it then becomes necessary to attenuate to the extent of 1,000,000 to 1. This is not an easy operation to accomplish efficiently, and the 1-volt standardizing voltage probably has been justified only by the onetime difficulty in producing a reliable v.t. voltmeter for voltages under 1 volt. In the Model 906 design, a signal input of .1 volt to the attenuator is used on all except the 0-100,000-microvolt and 0-1 volt ranges. This is a very important improvement, since stray radiation from the signal generator is reduced by a factor of 100 times at low oscillator voltages (strays decrease as the square root of the oscillator output voltage). Oscillator output is controlled by means of potentiometer R_3 , operated by the "Meter" knob on the front panel.


The r.f. output of the generator is the voltmeter reading times the "Microvolts" potentiometer setting times the "Multiply By" setting of the attenuator step switch.

The "Hi-Output" jack, J_1 , delivers continuously variable r.f. output, controlled by "Microvolts" potentiometer R_2 . This r.f. output voltage is 0 to 0.1 volts r.m.s. when the meter is set to "X1" by means of "Meter" potentiometer R_3 —and 0 to 1 volt when the meter is set to "X10."

R. F. Voltmeter. The vacuum-tube voltmeter employed in the instrument to standardize the attenuator is a special version of the "Vomax," the all-purpose v.t. voltmeter manufactured by the same company. The indicating meter may be seen in the upper right-hand corner of the front panel in Fig. 1, its scale only visible through a panel window, small to hold down "strays."

The balanced v.t. voltmeter circuit includes 6AL5 tube V_1 , 6J6 tube V_2 , and the indicating meter, M . The voltmeter is capacitance coupled to

Fig. 3. Internal view of the signal generator. Easily seen are the small, efficient tubes; shielding; unique mechanical arrangement to insure short leads; and simplified assembly. The coil switching turret is seen on the left-hand side.

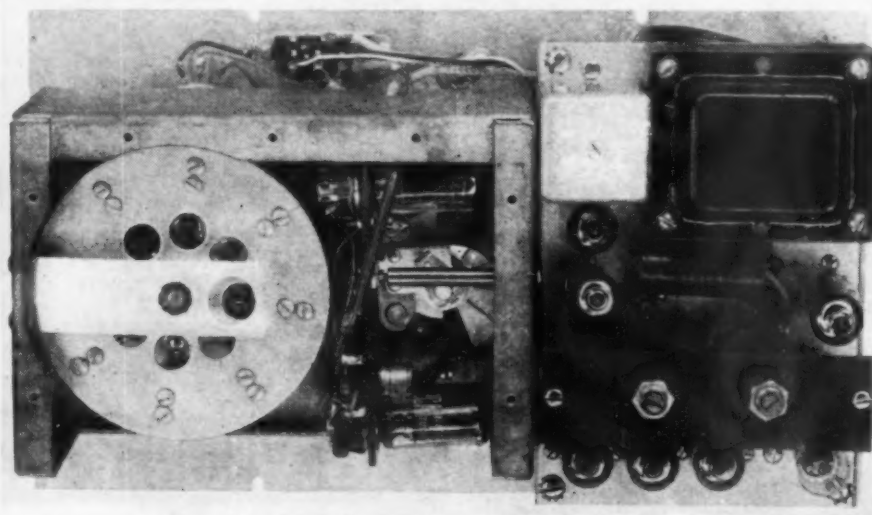

RADIONIC offers Immediate Delivery!

It's **RADIONIC**
for **RELIABILITY**

**UNBELIEVABLE
VALUES**
on Brand New Radios
and Accessories

ALL GUARANTEED

•
**Chancellor
RADIO**

- Television Kits and Components
- Radios
- Test Instruments
- Parts and Accessories
- Inter-Communicators
- Disc and Wire Recorders
- Public Address
- Amateur Equipment
- Tubes
- Record Changers
- Technical Books

**TERMS: 25% deposit—
Balance C.O.D. or full
remittance with order.**

Edwards **NEW FIDELOTUNER**

FOR MAXIMUM F-M LISTENING PLEASURE

**CONNECTS to
ANY RADIO
RECEIVER or
SOUND AM-
PLIFIER for F-M**



**\$31⁵⁰
NET**

New and revolutionary tuning principle* makes EDWARDS FIDELOTUNER the most efficient F-M converter on the market today! All the great advantages of F-M reception are yours with this compact, efficient new tuner. Covers full F-M Band 88-108 Mc. VHF insulation throughout. Easy finger-tip tuned. Slide-rule dial illuminated. Local reception antenna included. Walnut veneer cabinet. Beautiful proportions—11" wide, 6 3/4" high, 6" deep. Complete with five tubes plus Selenium Rectifier. Shipping weight 7 1/4 lbs. for 105-130 V. A.C. Tube lineup: 6J6—2 6SA7—6SH7—6H6.

YOUR NET COST.....\$31.50
*Patent Pending.

- Edward's High Q Tuning Lines.
- Full FM band coverage.
- 88-108 MC.
- Connects to any Radio or Amplifying System (old or new).
- 5 tubes plus Selenium Rectifier.
- 3 IF Stages including Limiter Stage.
- Real Discriminator Circuit for maximum realization of F-M possibilities.
- Permeability Tuned IF and Discriminator K Trans.
- VHF Insulation throughout.
- Easy Finger-tip tuning.
- Slide Rule Dial.
- Local Reception Antenna included.
- 105-130 Volt 60 Cycle A.C. Operated.

(*Patent Pending)

FIDELOTUNER
Edwards

RADIONIC CATALOG FREE ➔

IT'S A MUST FOR ALL SERVICE DEALERS, AMATEURS, EXPERIMENTERS, INDUSTRIALS, INSTITUTIONS AND GOVERNMENT AGENCIES.

**RADIONIC EQUIPMENT
COMPANY**

TRIBUNE THEATRE ENTRANCE • 170 NASSAU ST., N. Y. 7, N. Y.

CABLE "CHANSIOR"

TELEPHONE: WOrth 2-0421

MAIL TODAY

**RADIONIC EQUIPMENT CO., Dept. 512
170 Nassau Street, New York 7, N. Y.**

Send immediately your free catalog listing products of Radio's leading manufacturers of parts and equipment, and numerous special items at bargain prices.


NAME.....

STREET.....P.O. BOX...

TOWN.....ZONE...STATE.....

SPECTACULAR VALUES IN BRAND NEW RADIO PARTS ELECTRONIC EQUIPMENT from MID-AMERICA

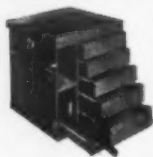Never before such amazing values in brand-new radio parts and electronic equipment. Shown here are but a few samples from Mid-America's vast stock. Order these money-saving values now! And ask for Mid-America's big catalog that lists thousands more at unbelievably low prices!



SENSATIONAL SPARE PARTS CHEST! Loaded with all brand new parts and 53 popular tubes. Thousands of resistors and condensers, transformers, hardware, everything! Has completely wired 15-tube amplifier for 110 V. 60 Cycle operation; use for audio, television, control circuits, oscilloscope, etc. Sturdy chest 30 1/2" high; ideal for parts storage and work-base. MA-2096. . . . **\$49.50**

FM TRANSMITTER



SPECIAL FOR AMATEURS AND EXPERIMENTERS! Complete AN/APN-1 FM transmitter-receiver for 420-460 MC. Used as indicator for altitudes up to 4000 feet but readily adapted for signalling, control circuit etc. Contains dynamotor for operation from 27.5 volts. Complete with all 14 tubes: 2-12H6, 2-955, 2-9004, 4-12SJ7, 3-12SH7, and VR-150-30. MA-1259. **\$13.95**

SUPER-HET RECEIVER BC-733-D

BC-733-D 10-tube crystal-controlled superhet receiver complete with 3-717A, 12SQ7, 12A6, 2-12SG7, 12AH7, and 2-12SR7 tubes. Set includes full complement of 6 crystals for operation in 108.3-110.3 MC range. Receiver CAA type-certified (TC-1045) for lateral blind landing guidance. Operates from either 14 or 28 VDC dynamotors (not supplied). Parts value exceeds our low price many times. MA-2163. **\$9.95**

SPECIAL! PUSH-BUTTON TUNING UNIT



50 mmf variable condenser operated manually or by cam action. Ten chrome-plated push-buttons 1 1/4" from plate. Each button is positive action DPST with automatic release. Unit has ten removable 100 mmf air padders, one 25 mmf air padder. Mounting plate will take 6/32 and 8/32 screws. MA PBS-10. . . . **\$1.79**

MARKER BEACON RECEIVER

COMPACT MARKER BEACON RECEIVER BC-1023-A for FCC-approved 75-MC modulated signals. Tubes (6SQ7, 6U6GT, 6SC7, 12SH7). Operates from aircraft 12-14 VDC supply. Ready to install. Experimenters use relay circuit in set for remote control of equipment. Aluminum cabinet with shock mounts; 5 1/4" x 5 1/4" x 3 7/16". MA-2107. **\$4.45**



High Frequency Antenna AN-104-B

Used with SCR-522, ARC-5 and 274-N; approximately 1/2-wave on 100-156 MC. Very sturdy, use anywhere; a real buy for amateurs. A pair make an excellent broad-band receiving dipole for FM and television. Coaxial connector in base. MA-2153. . . . **79c**

PERMEABILITY TUNER for broadcast band. Replaces 3-band cond., antenna, r.f., oscillator coils. Adjustable coils. 455kc output dial cord drive. Wiring diagram supplied. MA-2162. **\$1.39**

FREE CATALOG

Order now—right from this ad! Send 25¢ deposit—we ship C.O.D. for balance plus postage. Write, too, for Mid-America's big, complete catalog that lists hundreds and hundreds of hard-to-get items—ALL AT UNBEATABLE LOW PRICES! Mail orders and catalog requests to store address—Dept. E-127

MID-AMERICA CO. Inc.

STORE 2412 S. MICHIGAN AVE. CHICAGO 16, ILL. WAREHOUSE 2307 S. ARCHER AVE. CHICAGO 16, ILL.

the signal generator circuits through condenser C_4 .

One-half of the 6AL5 acts as the shunt-diode signal rectifier; the other half provides contact potential balance. One-half of the 6J6 tube is the d.c. meter amplifier; the other half provides stabilization.

Potentiometer R_{21} is the zero-set control for the v.t. voltmeter. Potentiometer B_{22} sets the meter range ("X1" = 0.1 volt; "X10" = 1 volt). For improved stability of this electronic voltmeter circuit, and in order to minimize grid current flow and to protect meter M against burnout due to possible overload, the 6J6 tube, V_2 , is operated at reduced plate voltage through a voltage divider comprised by resistors R_{23} and R_{24} . Also, the heaters of the v.t. voltmeter tubes are operated at reduced voltage through the dropping resistor, R_{25} .

Output Terminal Box. The 3-foot, permanently-attached, shielded output coaxial cable of the Model 906 is terminated with a shielded 3-post terminal box, which delivers the metered-output signal voltages from much less than 1 to 100,000 microvolts. In addition to extending the shielding of the instrument just as far as practicable to the point of signal delivery, the output terminal box provides a constant output impedance of 15 ohms.

A .02 μ fd. isolating condenser, C_1 , permits connection to be made directly to amplifier plate circuits and to other high-voltage d.c. points, without damaging any portion of the attenuator in the signal generator. The inclusion of this condenser inside the terminal box makes unnecessary the common bad practice of picking up any convenient, unshielded junk-box condenser when the signal generator must be isolated (as far as d.c. is concerned) from the device into which its signal is being fed.

With this output arrangement, the operator may take his signal directly from across 15 ohms, or through the insulating condenser.

AM Modulator. Standard 400-cycle amplitude modulation is available within the instrument when the "Modulation" switch is thrown to its AM position.

The heart of the AM modulator is the 400-cycle, stabilized output audio oscillator which includes 6AU6 tube V_4 , and 6C4 tube V_5 . The operating frequency of this oscillator is set and stabilized by a Wien bridge comprised of resistors R_{27} , R_{28} , R_{29} , condensers C_{11} and C_{12} , and the stabilizing lamp, PL_{11} .

A buffer amplifier, designed around 6C4 tube V_6 , isolates the audio oscillator from varying load effects and thereby further stabilizes the modulation operation.

The 400-cycle amplitude modulation is variable from zero to over 100 percent by means of potentiometer R_{30} . This modulation percentage control is seen in the lower left-hand portion of the front panel.

Power Supply. The internal a.c. power supply is conventional, being

comprised principally of power transformer T_1 ; 6X4 rectifier tube V_7 ; and the filter sections CH_2 , R_{31} , C_{20} , C_{21} , and C_{22} .

The power supply components, together with the audio-frequency modulator and v.t. voltmeter components, are mounted on a separate aluminum chassis, as may be seen in Fig. 3.

A line-frequency (50 or 60 cycles) voltage, for the frequency modulator, is delivered by the voltage divider made up of resistors R_{32} and R_{33} in series and R_{34} in parallel with R_{32} , when switch S_2 is set to FM position.

The r.f. line filter, connected between the power transformer primary and the line plug (see Fig. 2), will be discussed in the next section.

Shielding and Filtering. The purpose of any signal generator is to deliver a metered and controlled, modulated or unmodulated, signal directly to the point of use. The signal from a good instrument does not arrive by any other paths at all except through the generator output cable, and does not leak past the controlling attenuator. Any signal, or portion thereof, which passes directly from the oscillator to the point of use, detouring the meter and attenuator circuits and the output cable, is unmeasured and serves to impair the accuracy of tests and measurements made with such a generator. One usual path of such stray signals is over the power line from signal generator to receiver (or other device under test). Another is direct radiation of the signal through the intervening space between the signal generator and point of use. This latter radiation generally takes place directly from the oscillator and is occasioned by ineffective shielding.

In order to prevent direct radiation, the shielding of the Model 906 has been worked out most carefully. The two radio-frequency oscillators, the frequency modulator, and all of the associated circuit components are housed inside a single, substantial metal shield box. This is a thick, multiple copper-plated chamber. All leads entering this box are shielded and filtered. Edges of the shield box cover overlap the box flanges, and the cover is fastened tightly to the box by means of some 14 screws placed at a number of points—many more than are required for purely mechanical reasons. The box itself is insulated from the instrument panel by means of heavy steatite spacers. By preventing metallic contact between the shield box and instrument panel, except at selected points, loop circuits are avoided and the oscillator field is confined.

The attenuator ladder section is separately shielded; and, as may be seen from an examination of Fig. 2, leads to this section and to potentiometer R_2 are individually shielded.

The front panel of the signal generator is laminated of steel and aluminum in order further to reduce radiation in the wide frequency range of the instrument. The enclosing cabinet is made of steel, this metal being


HOT RADIO VALUES at SUN RADIO!



BC-221 FREQUENCY METER

A heterodyne frequency meter complete with tubes, crystal, calibration chart and guaranteed accuracy of .01% or 500 cycles, whichever is greater. Better than two dial division per kc. Fundamental ranges are 125-250 and 200-400 kc. Can be used with 110 volts AC power pack, batteries or vibrapack. Makes a fine signal generator or converts to VFO. These are slightly used but Guaranteed.

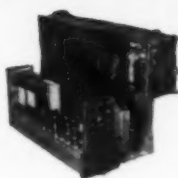
\$37.50
 A1.....
 With Modulation.....\$54.50



WAVEMETER

We're closing out the last few of these precision wavemeters which tune from 150-210 mc and which contain a high quality resonant cavity wavemeter, oscillator, heterodyne amplifier, electric tuning eye, complete with 19 tubes, 110v AC power supply. The tubes alone far exceed your close-out costs of

\$17.95
 only.....

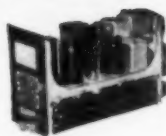


SPERRY AMPLIFIER

Brand new Servo amplifier containing two beam power output tubes (1632) similar to 2516, two twin triodes (1633 and 1634) similar to 6SC7, two mica condensers, dozens of color coded half-watt resistors, two dual and four section bathtub condensers, three transformers, two wafer switches, one volume control, four octal sockets.

\$3.95
 Easily convertible..

100 WATT BENDIX TRANSMITTER TA12

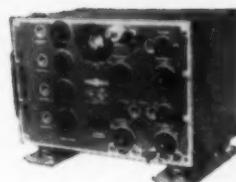

CHECK THESE VALUES: Three 807 tubes, four 125K7, one 2-inch 5-amp. RF meter, four Separate Master oscillators. (These can be easily changed to cover 20-40-80 meters and by using crystal for the 10-meter band you will have a complete coverage transmitter.)

Four separate output tanks.

One 4-position selector channel switch having seven sections which changes the ECO, IPA and output tanks simultaneously. All the controls are mounted on the front panel. The housing is cast aluminum; shields and case are sheet aluminum. Dimensions 11x12x15 inches, weight 35 1/4 lbs. Complete, simple instructions for conversion

\$49.95
 furnished. Complete with tubes

CRYSTALS!

In the greatest purchase of radio transmitting crystals ever made by one wholesaler in the history of the Radio Parts Industry, Sun Radio acquired title to over a half million dollars (\$500,000) of Army Surplus precision built, exactly tooled crystals in moisture-proof, shock-proof holders. These gleaming new crystals manufactured by the world's finest crystal makers (RCA, Bliley, Western Electric, etc.) are offered at the lowest prices that you have ever seen. . . . Anywhere! These crystals are marked with Army frequencies and Sun Radio will supply translation with shipment. To expedite forwarding of orders we pack all shipments of 20 crystals or less in cloth shipping containers . . . and all shipments guaranteed perfect . . . but it's no wonder with the beautiful shock-mounted holders. Fundamental frequencies are as follows:

CRYSTALS WITH A MILLION USES

FRACTIONS OMITTED

412kc	423kc	434kc	444kc	459kc	474kc	488kc	498kc	509kc
413	424	435	445	462	475	490	501	511
414	425	436	446	463	477	491	502	512
415	426	437	447	466	479	492	503	515
416	427	438	448	468	481	493	504	516
418	429	440	451	469	483	494	505	518
419	430	441	453	470	484	495	506	519
420	431	442	457	472	485	496	507	522
422	433	443	458	473	487	497	508	523

49¢ EACH

I.F. FREQUENCY STANDARDS

450kc	459.259kc
451.388kc	461.111kc
452.777kc	464.815kc
454.166kc	465.277kc
455.556kc	

99¢ EACH

CRYSTAL FREQUENCY STANDARDS

98.356 KC

Easily altered for 100-kc. Standard. Mounted in low-loss 3-prong holder.....

\$4.49

For Crystal Controlled Signal Generators

525 KC

526.388	533.333
527.777	534.722
529.166	536.111
530.555	537.500
531.944	538.888

99¢

ASSORTED MISCELLANEOUS CRYSTALS

FRACTIONS OMITTED

370kc	375kc	379kc	383kc	387kc
372	376	380	384	388
374	377	381	385	

priced at a fraction of the cost of their holders alone

39¢

FOR HAM AND GENERAL USE

FRACTIONS OMITTED

390kc	394kc	398kc	404kc	408kc
391	395	401	405	409
392	396	402	406	411
393	397	403	407	

79¢


★ Payment with order.—Enclosed 20¢ for postage and handling.—Minimum order—\$2.00 plus postage.—Please specify alternate choices or "no substitutes."

SUN RADIO

OF WASHINGTON, D. C.

938 F STREET, N. W. WASH. 4, D. C.

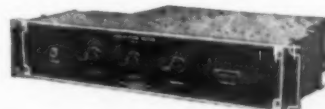All Items F.O.B. Washington, D. C. All orders \$30.00 or less cash with order. Above \$30.00—25 per cent with order, balance C.O.D. Foreign orders cash with all orders, plus exchange rate.




110 VOLT AC SUPERHETERODYNE RECEIVER

This crystal fixed frequency receiver comes with full conversion instruction for variable tuning of all ham bands and broadcast. A highly selective superheterodyne receiver, 110 V.A.C. power supply built in. Uses the following tubes: 6K7—RF Amplifier; 6K8—Mixer and Oscillator; 6K7—I.F. Amplifier; 6F7—Detector and A.V.C.; 6C8—Output and Noise Suppressor; 80—Rectifier. Dimensions: 3 1/2 x 19 x 11 1/2 inches. Comes complete, brand new, with one set of coils and

\$16.95
 two sets of tubes.....

Extra set of coils.....\$2.95


A.C. VOLT-METER \$3.49

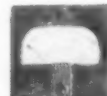

Brand new G.E. 3" square panel motor 0-150v, ideal for checking primary voltage.



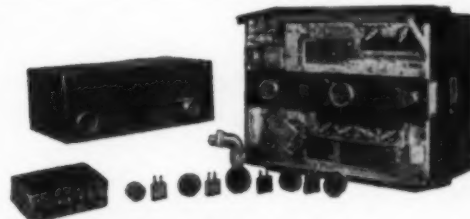D.C. MILLIAMMETER
 Brand new General Electric 2" round panel meters 0-300.
\$2.97



SCR-522 VHF XMTR-RCVR

The finest all-purpose equipment on the surplus market. Don't confuse these with other incomplete and abused 522s. Sun Radio offers electronically perfect and guaranteed 522s . . . AND COMPLETE with 10-tube superhet receiver with squelch circuit, 7-tube Xmtr., remote control box, 28-volt dynamotor (can be converted to 110V operation), 4 crystals and all cable connectors, but less cables.

\$24.95



TS13 HANDSET

Combining a 200-ohm carbon mike and 2500-ohm earphone with butterfly switch for listen and talk. Has 6' flexible rubber cord, with 1—P155 and PL68 plugs attached.

\$2.95
 New.....



BC 684 F.M. 35 WATT TRANSMITTER

Brand new, complete with eight tubes, crystal control 10 channel pushbutton, non-linear modulation coil . . . less coverplate, crystal and power supply.....

\$17.95

used especially to minimize low-frequency radiation (non-magnetic shields are not efficient at low frequencies).

Transmission of radio-frequency energy back into the a.c. power line is prevented by the power line filter. This is a multi-section unit composed of inductors L_1, L_2, L_3 and L_4 , and condensers $C_{23}, C_{31}, C_{25}, C_{26}, C_{27}$, and C_{28} . All of the filter coils, and condensers C_{25} and C_{26} are housed in the shield box seen to the right of the power transformer in Fig. 3. The other filter components are mounted under the shield box, beneath the power supply sub-chassis. Diagram-wise such a filter looks simple indeed. In cold fact its design is but one of the many headaches encountered.

Shielding is completed by the terminal box on the end of the output cable. This unit extends the instrument shielding right up to the receiver or other device to which the signal is to be delivered, provided the shortest possible leads are employed between the terminal-box binding posts and the receiver.

The manufacturer claims strays from the Model 906 signal generator to be less than 0.1 microvolt at 90 kc., rising slowly to never more than 2 microvolts at 30 mc. Actual tests on production models of this instrument, however, have shown less than 0.2 microvolt stray transmission up to 35 mc.

-30-

What's New

(Continued from page 88)

Model 250 volt-ohm milliammeter.

The instrument is permanently fastened into the Roll Top Case which is made of heavily molded bakelite and is large enough to provide a compartment for leads beneath the instrument. The front is covered by a Roll Top Panel, a sliding cover of narrow bakelite segments on a backing of cloth. A flick of the finger opens or closes the roll top. A heavy leather carrying handle completes the assembly. The case is so designed that the Model 260 may be easily serviced for battery replacement.

Further information on this unique housing may be secured from *Simpson Electric Company*, 5208 West Kinzie Street, Chicago, Illinois.

COMBINATION TESTER

A new combination signal tracer and electronic volt-ohmmeter has been introduced to the trade by *Coastwise Electronics Co., Inc.* of Los Angeles.

This recent addition to the company's "Ferret" line of test instruments is known as the Model 730 and features a germanium crystal probe developed during the war and recently released for commercial use. The probe is light in weight and because no tube is required measures only $\frac{1}{2}$ " in diameter.

The new tester is capable of testing a full audio range from 0-20,000 cycles, and provides r.f. measurements up to 110 mc. The v.t.v.m. measures a.c. or d.c. on seven scales from 0-3000 volts. The ohmmeter has a range of from



0-10 megohms center-scale on seven bands.

Catalogue sheets on the Model 730 are available from *Coastwise Electronics Co., Inc.*, 130 North Beaudry Avenue, Los Angeles 12, California.

KNOB KITS

Of particular interest to the radio serviceman is the *General Cement Mfg. Co.*'s announcement of a new line of knob kits for radio applications.

These kits are made up of molded plastic knobs of a new modern design

Fahnestock Clips



RADIO'S GREATEST CONVENIENCE



FAHNESTOCK SPRING BINDING POST GRIPS THE WIRE BY THE ACTION OF A SPRING

No tools required to make the connection. Grips the wire with just the right pressure for good electrical contact. Simply press down, insert the wire and let go. Does not injure wire, hence connection can be made or opened as often as desired. Available in large variety of types and sizes to fit any radio purpose and any requirement as to position, space or method of attachment. You will find them in the better sets.

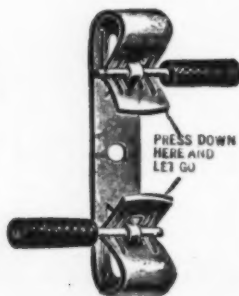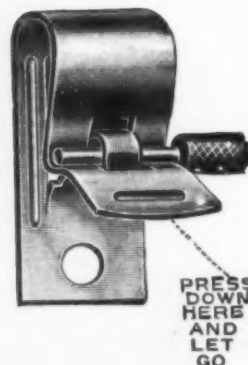Positive contact; cannot jar loose. Brass or bronze—nonrusting.



FAHNESTOCK ELECTRIC COMPANY, Inc.

46-44 ELEVENTH STREET
LONG ISLAND CITY 1, N. Y.

Dept. 12

Please send us at once, Descriptive Literature, Prices and Delivery Schedule on

FAHNESTOCK CLIPS

For
Name
Address
City State

GIVE YOURSELF THE FINEST... XMAS PRESENT EVER




What better time to give yourself the Receiver or Test Equipment you've always wanted... especially when Walter Ashe's big "Surprise" trade-in allowance on your used equipment means really important money-saving. So make your selection right now. Tell us what you have to trade. We'll respond with an extra liberal offer that's sure to please you. Act today. Wire, write, phone or use the handy coupon below.

"DO YOUR XMAS SHOPPING EARLY"

To make sure of pre-Christmas delivery place your order now! Despite the holiday rush Walter Ashe will continue to ship the same day... often the same hour... following receipt of your order!

ATTENTION RADIO SERVICEMEN... DEALERS!

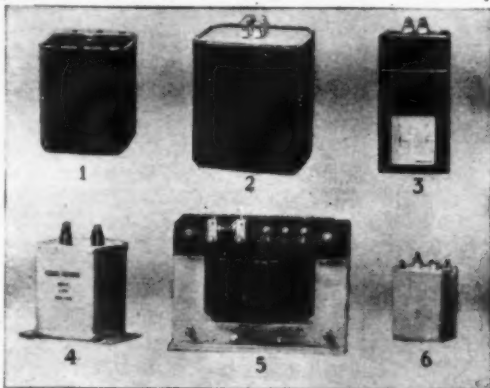For amazing bargains in top condition, slightly used Test Equipment, contact Walter Ashe right away. Write for details or check and return the coupon.



ARMY SURPLUS HEAD- PHONES

Type HS-16A Army Surplus phones. Canvas Web Headband and long standard type cord. Packed in original overseas shipping boxes. **\$1.47**
Shpg. Wt. 3 lbs. Only

ALL THE BIG NAME BRANDS OF TEST EQUIPMENT

Hickok	Du Mont
Jackson	Feller
Precision	Meissner
Simpson	Triplet
McMurdo Silver	R.C.A.
Special Products Co.	Billiey
Industrial Equipment	Weston
Cornell Dubilier	Sprague
Coastwise Electronic	Supreme
Waterman	Superior

"ZERO BEAT" by Walter Ashe

No matter how busy I am I make a point of spending a part of each day on the sales floor. This enables me to keep in close touch with the preferences of our customers, including the young fellows who are buying equipment for the first time as well as the old-timers who have been doing business with us since 1922. Often the newcomer will volunteer, "My dad said I could get it at Walter Ashe," while the "regular" acknowledges, "I know I can always get here what I want... when I want it. My reply to both is, "Depend on us to stock what you want and need at all times. And that's a promise!"

Prices subject to possible change

YOUR FAVORITE RECEIVERS IN STOCK

Hallcrafters 8-38	\$ 47.50
Hallcrafters 8-40A	51.50
Hallcrafters 8X-42 (less speaker)	275.00
Hallcrafters 8X-43 (less speaker)	160.50
Hammarlund HQ-129X (with speaker)	18.15
Hammarlund 8PC-400X (with speaker and pwr. supply)	318.25
National HRO-7T (less speaker and pwr. supply)	279.00
National NC-240DT (less speaker)	225.00
National NC-173 (less speaker)	179.50
National NC-57	89.50
National NC-46 (less speaker)	97.50
Pierson KP-81 (complete)	367.65
RME-45 (with speaker)	118.70
RME-84	58.70
RME VHF-152A	86.60
RME DB-22A	66.00

WE ALSO CARRY A COMPLETE STOCK OF TRANSMITTERS

SURPLUS EQUIPMENT BARGAINS

- #1—Filter Choke, 4 Hy, 300 MA, 40 ohms. Shpg. Wt. 12 lbs. **\$ 4.95**
- #2—Plate Transformer, 1400/1200 VCT, 200 MA, Pri. 115 VAC. Shpg. Wt. 18 lbs. **7.95**
- #3—Dual Choke, 12 Hy, 200 MA per section, 150 ohms. Shpg. Wt. 17 lbs. **4.95**
- #4—Filter Condenser, 2 Mfd. at 4000 VDC. Shpg. Wt. 7 lbs. **4.50**
- #5—BCA Modulation Xformer. For tubes up to 10,000 ohms. P to P. Sec. #1 450 Ma for beam tubes plates. Sec. #2 80 Ma for screen grids. Shpg. Wt. 55 lbs. **14.95**
- #6—Filter Choke, 4.5 Hy, 150 MA, 70 ohms. Shpg. Wt. 5 lbs. **1.29**


S. B. CARBON HANDMIKE

Regular T-17B SURPLUS carbon mikes as used by the AIR FORCES during the WAHL 300 ohm, with push-to-talk switch, cord, and plug. Brand New in original over-seas shipping boxes. Shpg. Wt. 3 lbs. Only **69c**



COMING! AND SOONER THAN YOU THINK!

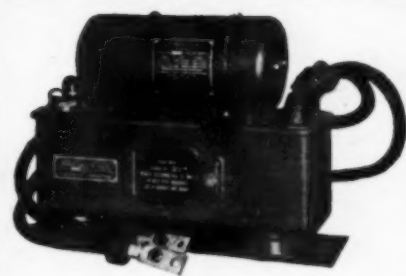The new, bigger, better Walter Ashe Catalog, featuring all that's new and best in Radio and Electronics. For "priority" delivery on your free copy ask to have your name placed on our mailing list.



PE-103 DYNAMOTOR

WALTER ASHE still has that ideal power supply for your emergency set-up or mobile rig. Brand new in original overseas shipping crates, genuine SURPLUS PE-103 DYNAMOTORS that deliver 500 Volts D.C. at 160 Ma. with either 6 or 12 volt D.C. input. Get yours while the fast-dwindling SURPLUS supply lasts. Shpg. Wt. 81 lbs. Only **\$9.95**

OTHER SUPER BARGAINS IN SURPLUS EQUIPMENT

- | | |
|---|--|
| Belayn Motors, 115 VAC
60 Cy. Large continuous
duty type. Shpg.
Wt. 25. \$12.50
HV By-Pass Condenser,
Mica .002 X 3000
VDC. Shpg. Wt. 1/2.50
Filter Condenser, 3 MFD.
X 440 VAC good for
1500 VDC. Shpg. wt. 3
..... 1.50
Plate Transformer, 2500
VCT, 150 MA, Pri. 115
VAC. Shpg. Wt. 18. 9.95
Filament Transformer, 5
VAC at 25 Amps. Pri. 9
115 VAC. Shpg. Wt. 9
..... 6.15
Filter Choke, 8 Hy, 500
MA, 55 Ohms. Shpg.
Wt. 25. 11.85 | Plate Transformer, 1400/
1200 VCT, 200 MA,
Pri. 115 VAC. Shpg.
Wt. 18. \$ 7.45
Filter Choke, 6 Hy, 1200
MA, 27 ohms. Shpg.
Wt. 94. 17.95
Swinging Choke, 2 to 6
Hy, 500 MA. Shpg.
Wt. 38. 11.85
Dual Filament Xformer,
Two 5 VAC X 5.25
Amp. Secs. Pri. 115
VAC. Shpg. Wt. 8. 1.95
Plate Xformer, 3200 VCT
at 525 M. A. Pri. 115
VAC. Shpg. Wt. 55. 29.95
Modulation Xformer, 30
Watts, Pri. 5000 Ohms
CT. Sec. 1750/2000/
2250, Common B plus.
Shpg. Wt. 8. 2.00 |
|---|--|

IMPORTANT REMINDER!

Place your order now for the 1948 issue of ARRL "RADIO AMATEURS' HANDBOOK" and EDITORS AND ENGINEERS' "RADIO HANDBOOK."

Remember your trade-in's worth more at the Walter Ashe store. So get Walter Ashe's offer before you make that trade.

TIME
PAYMENTS
AVAILABLE

WOJWD WOULH W0WTH W0NRF
WOIYD W0PGI W0QDF W0KES

Remember your trade-in's worth more at the Walter Ashe store. So get Walter Ashe's offer before you make that trade.

WALTER ASHE RADIO CO.

1125 Pine St., St. Louis 1, Missouri

☐ Am interested in the following top condition, slightly used Test Equipment (list preference)

☐ I want to trade (describe used equipment)

for (show make, model of new Receiver desired or other equip.)

☐ Reserve my copy "Radio Amateurs' Handbook."

☐ Reserve my copy "Radio Handbook."

☐ Enter my name on your "priority" list to receive the big, new Walter Ashe Catalog when issued.

NAME

ADDRESS

CITY

ZONE

STATE

Walter Ashe
RADIO CO.
1125 PINE ST. • ST. LOUIS 1, MO.

All Prices
F.O.B.
St. Louis

MAIL
COUPON
TODAY

December, 1947



RCA VICTOR EYE WITNESS TELEVISION RECEIVERS

Flat Face Pictures, 13 Channels.
Model 6217S—7" Set.....\$296.80
Model 6307S—10" Set.....432.60
Model 6417V—10" Console, including Television,
Automatic Gramophone, F.M. and A.M. radio...\$488.00
Prices above include original RCA factory installation in
their service areas as well as guaranty for 12 months on
the set and kinescopes. City sales tax where applicable
added.

LATEST TELEVISION COMPONENTS

Part No. Price
47204X RCA FRONT END consisting of a complete television 13 channel tuning assembly including tubes, coils, switch, input converter, IF transformer, and fine tuning connectors, ready to attach to a suitable IF input.....\$97.50

TELEVISION I-F AND VIDEO COIL KIT

47204X1 RCA IF and Video coil kit contains all the necessary IF and video coils for a complete 4 megacycles wide band-pass as well as the sound IF and discriminator transformers for a complete television set.....\$33.00
I.F. Video frequency—25.75 MC
I.F. Sound frequency—21.25 MC
47201D1 Deflection YOKE for use with 7DP4, 10DP4, 15DP4 magnetically deflected tubes.....13.75
47201D2 Deflection YOKE for use with 5TP4 projection kinescope.....14.90
47201X1 Yoke mounting hood for above yokes...2.75
47202D1 Magnetic focusing coil for 5TP4, 10BP4, 15DP4 for use in series with divider...9.10
48202D1X Magnetic focusing coil for same as above but 10,000 ohm D.C. resistance...9.90
47203D1 Ion trap magnet for tubes 7DP4 and 10BP4.....6.50
47211T1 Horizontal output transformer with 9000 volt kick-back output for 2nd anode...16.85
47208T8 Horizontal blocking sync. discriminator transformer as used in RCA AFC circ...4.75
47208T8 Horizontal blocking oscillator transformer UTC high perm. iron, SPECIAL...2.75
47201R1 Horizontal width control for use with 7DP4, and 10BP4 or 15DP4.....1.30
47201B1 Spherical mirror for use with 5TP4 in projection systems.....150.00
47201P2 Aspherical correcting lens to use with above mirror.....50.00
47204T2 Vertical output transformer.....9.00
47208T2 Vertical blocking oscillator transformer RCA.....5.70
475218 FRAME with shatterproof glass and rubber mask for use with 12AP4 tube...8.00
475300 H.V. capacitor, .03 mfd 7500 volt working, grounded negative GE Pyranol...3.75
475301 H.V. capacitor, .1 mfd 7500 volt working, grounded negative GE Pyranol...7.50
475302 H.V. capacitor, 2x.1 mfd 7000 volt working, grounded negative GE Pyranol...9.00
475303 H.V. capacitor, .05 mfd 16000 volt working, grounded negative Sprague...9.90
475305 TRANSVISION 7 inch Television Kit, all parts and tubes included.....159.50
475306 Transvision 12" Television Kit.....289.50
473007 Thoradson Transformer, 15000 Volt AC and filament winding as required.....27.00

RCA HIGH FREQUENCY SWITCH AND COIL ASSEMBLY

RF unit, used in TRK12 RCA television receivers consisting of 5 band range switch with shield plate and mounting studs, including 5 polystyrene antenna coils, permeability tuned, each consisting of primary ring, secondary coil and primary mica capacitors. The assembly can be used in TELEVISION, F.M. and other HIGH FREQUENCY APPLICATIONS.
CATALOG No. 5210—Special price.....\$5.60

RCA VARIABLE TUNING CERAMIC CAPACITOR

To be used in conjunction with the above switch assembly 2-4.5 MMFD.
CATALOG No. 5211—Price.....\$2.10

CATHODE RAY TUBES

Type	Make	List Price	Your Price
5BP1	DUMONT	\$24.75	\$ 7.95
5BP4	RCA	27.50	7.95
5CP1	PHILLIPS	24.50	7.95
5JP4	DUMONT	90.00	7.95
7DP4	Projection RCA	67.50
7DP4	RCA	49.95
7EP4	DUMONT	23.25
7GP4	RCA	24.25
9AP4	RCA	62.50
10BP4	RCA	49.50
12AP4	RCA	75.00
15AP4	DUMONT	129.50
20BP4	DUMONT	270.00

All tubes are brand new, perfect, in factory sealed cartons, late production.
Send 50 cents for complete catalog including diagrams for RCA, G.E., Dumont, Andrea and Viewtone Television Receivers.

World's First Specialized House in Television.

TELETRONICS SERVICE AND SUPPLY CORP.

264 WEST 40TH STREET NEW YORK 18, N. Y.
Phone Pennsylvania 6-8730

and are available in walnut and ivory patterns. Four kits are available; 35 assorted push-on knobs and needle cup; 28 assorted spring knobs and needle cup; 24 assorted set screw knobs and needle cup; and 30 assorted all type knobs and needle cup.

Further information, illustrated literature, and prices on these knob kits are available from *General Cement Mfg. Co.*, 919 Taylor Avenue, Rockford, Illinois.

PORTABLE ANALYZER

A new test instrument, the Model 10 "Rangemaster," has recently been introduced to the trade by *Bradshaw Instruments Company* of Brooklyn.

Designed especially for servicemen and hams, this new instrument features three direct reading capacity ranges, and a separate ohmmeter which permits the measurement of leakage as well as capacity.




Three a.c. current ranges capable of measuring up to 15 amps., and a 1 volt a.c. range which may be used as a sensitive output indicator for alignment work are also included. Twenty-two separate ranges are incorporated in the meter which is available in either kit or assembled form.

Full information may be secured by writing Dept. P., *Bradshaw Instruments Company*, 942 Kings Highway, Brooklyn 23, New York.

NEW PICKUP UNIT

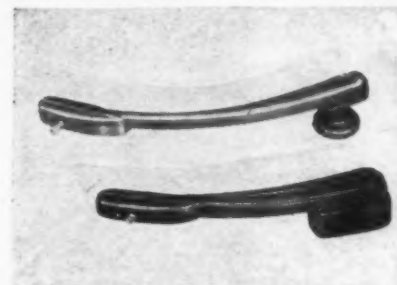Amplifier Corp. of America is in full scale production on the new *General Electric DL 1RM 6C Variable Reluctance*



tance Magnetic Pickup which is furnished with tone arm and permanent jewel-tipped needle as a complete unit.

The new pickup unit is available in two styles, the *Studio Transcription Model 160GE* which will play records up to 16" in diameter, and the *Program Phono Model 120GE* which takes conventional records up to 12" in diameter.

Although originally developed for use with *Amplifier Corp. of America's ACA-100GE amplifier*, these pickups may be used with any sound system properly equipped with the necessary preamplification.

The company points out that these new arms offer the user less record wear because of the soft needle suspension, less distortion because of the soft spring jewel mounting, less needle scratch because of response only to

A tour of inspection of RCA Victor's television receiver factory highlighted the recent visit of 37 radio set manufacturers to Camden, New Jersey for the two-day television clinic conducted by the company. Here, L. W. Teegarden (left), Vice-President in charge of RCA Tube Department displays a ten-inch kinescope to F. M. Sloan (center) and Harold Schaefer of Westinghouse.



Now

YOU CAN HAVE IMPROVED NO-DRIFT FM
in the Sensational New 1948

MIDWEST RADIOS

**NEW SERIES
16*
SUPER DELUXE
AM-FM
CHASSIS**

Here is the finest radio Midwest has ever produced in its 28 years of manufacturing—a world-ranging, 5-band radio with improved Midwest No-Drift FM . . . plus Standard Broadcast and 3 short wave bands, Television Audio Switch-over, and Color-Ray Tone Selection. The Series 16* Super De Luxe Chassis is a powerful, magnificently-toned radio that challenges comparison for performance, sensitivity, selectivity, and advanced engineering features. Supplied with satin stripe copper finish panel—ready to mount in your present cabinet. Send today for the FREE 1948 Midwest Radio Catalog. Buy your radio direct from the manufacturer on Easy Terms and 30 Days Trial and SAVE!



**14½"
PANASONIC
SPEAKER**

**5
WAVE
BANDS**


**SERIES
16 CHASSIS USES ALL
THESE LATEST-TYPE TUBES**

**30
DAYS
TRIAL**

**LOW
FACTORY-
TO-YOU
PRICES**

**EASY
TERMS**

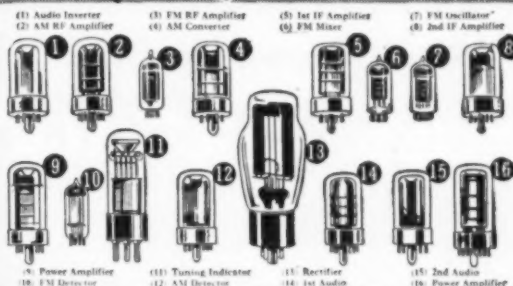A COMPLETE LINE OF FINE RADIOS AND RADIO-PHONOGRAPHS . . . Available in Separate Chassis Like the Powerful Series 16* AM-FM Model above, or in beautiful Radio-Phonograph Consoles like this:



Scores of NEW Features such as the Exclusive MIDWEST TRI-MAGNADYNE COIL SYSTEM and COLOR-RAY TONE SELECTION



SYMPHONY GRAND AM-FM RADIO-PHONOGRAPH CONSOLE with NEW Intermix AUTOMATIC RECORD CHANGER

Our Finest! A superbly beautiful musical instrument . . . a masterpiece of furniture design and radio engineering that offers the sensational Midwest NO-DRIFT FM, Automatic Intermix Record-Changer, Exclusive Color-Ray Tone Selection, World-ranging 5-Band Reception, Television Audio Switch-Over, and many more new and exclusive features.

MIDWEST RADIO CORP.

Dept. 37-M • 909 BROADWAY • CINCINNATI 2, OHIO

Rush for Free Catalog!

FILL IN COUPON AND MAIL TODAY OR JUST
SEND YOUR NAME AND ADDRESS ON 1c POSTCARD

MIDWEST RADIO CORP.
Dept. 37-M, 909 Broadway
Cincinnati 2, Ohio

Gentlemen: Please send me your new FREE catalog
and details of your liberal 30 Days Trial.

Name _____
Address _____
City _____ Zone _____ State _____

Studio Quality AMPLIFIERS

WITH CUSTOM-BUILT FEATURES

Design of Bardwell & McAlister's New Commercial Amplifiers embodies the principles which have been proven in custom-built units developed in the Motion Picture Industry, where quality is requisite. Fully licensed.

12w. models operate up to 8 indoor speakers, effectively cover outdoor audience of 2500.

25w. models operate up to 16 indoor speakers, effectively cover outdoor audience of 8000.

Designed & fabricated by manufacturers of high quality Sound & Recording Equipment for the Motion Picture Industry. Union made.

2 to 4 high gain input channels and 2 to 4 high or low gain radio or phonograph input channels.

High fidelity reproduction at any setting of volume controls up to full rated output with less than 4% distortion.

Frequency response flat within 1/2 db from 50 to 10,000 cycles.

Output impedances 500, 250, 16 & 8 ohms. Overall gain 105 db. Hum level 85 db below full output.

With or without professional "T" type bass and treble equalizers.

Write today for informative catalog & Technical data.
Dealer inquiries invited.



ELECTRONIC DIVISION
BARDWELL & McALISTER, INC.

BOX 1310, HOLLYWOOD 28, CALIFORNIA

12

Columbia

DECEMBER SPECIALS

22 GA. SOLID PLASTIC HOOKUP WIRE

A real value—solid copper conductor with 1/64" plastic insulation overall. Available in a variety of colors. Sold in 500 ft. coils only.

LIST PRICE
\$4.90
500 Ft. Coil

TWISTED PAIR INTERCOM WIRE

Same construction as above, but furnished as twisted pair. Can be used for intercom systems, alarm systems, and many other uses.

LIST PRICE
\$3.75
250 Ft. Coil

THREE CONDUCTOR TWISTED WIRE

As above

LIST PRICE
\$5.60
250 Ft. Coil

18 GA. SOLID PUSH-BACK WIRE

18 gauge solid tinned copper conductor with 1 celanese serve and lacquered rayon braid overall.

LIST PRICE
\$1.25
100 Ft. Coil

18 GA. 2 CONDUCTOR ELECTRICAL INSULATED WIRE—POSJ

Underwriters approved. For small appliances such as lamps, radios, etc. Parallel rubber covered rip cord.

LIST PRICE
\$8.45
250 Ft. Spool

The Above List Prices Are Subject To Regular Trade Discounts

Wire For Your Special Net Prices!


We carry in stock for immediate delivery many types of wire and cable in gauges of from 23 to 2. In addition to various types of multi-conductor cable for many uses. We also manufacture cord sets and cables to specifications. Send us your inquiries for prompt attention.

FREE

Write for our complete, illustrated catalog!

COLUMBIA WIRE & SUPPLY CO.
5740 NO. ELSTON AVE.
CHICAGO 30, ILLINOIS

CUT HOLES FAST IN RADIO CHASSIS

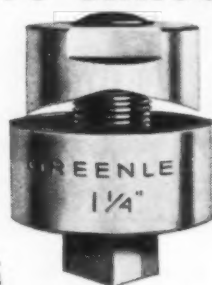

WITH A GREENLEE RADIO CHASSIS PUNCH

• GREENLEE Punches make this tough job easy. Merely turn with an ordinary wrench... make accurate, clean holes in a hurry. No reaming or tedious filing. There's a GREENLEE punch for each of these sizes: 1/8"; 3/16"; 1/4"; 5/16"; 3/8"; 1/2"; 5/8"; 3/4"; 1"; 1 1/8"; 1 1/4"; 1 1/2"; 1 3/4"; 2"; 2 1/4"; 2 1/2"; 3"; 3 1/2"; 4"; 4 1/2"; 5"; 716 1/2"; 717"; 71

"TAB"

That's A Buy

• NEW GUARANTEED



NEW WILLARD PLASTIC STORAGE BATTERY NON-SPILL

BB54/ER27-2.
2V/30Amp hrs

BALL Indicator Type
FOR SCR593/728A GE
Portables
Shipped Dry

"TAB" SPECIAL \$1.79
TWO for \$3.30

Bottle acid pt. 49¢; quart 95¢
One gal (95 oz) (REXP) only... 2.95
STORAGE BATTERY BB206/U WILLARD Non-spill 2V/26Amp hrs. SPECIAL \$1.25; TWO for \$2.25; TEN for \$10.00.

BATTERY BURGERS 3V/F2BF/1947 date... \$0.25
Test Set Supreme 542 VOM/24 ranges *LN... 15.95
Test Set Triumph 324 ACDC/VOM/10 ranges... 10.59
TS Same as WESTON 497 VOM&Case... 19.95
Test Set Supreme 537 VOM/8 ranges... 10.95
Tuning Indicator for FM dual microamp... 2.95
VOLTAGE REGULATOR RAYTHEON
inpt taps 95-130V/60cy. Outpt115V/
1.25A Cased, Tropicalized 0.5% Regulation... 10.95

VOLTAGE Regulator Relay Rack, inpt
adj tape 198to242V/50-60cy. Outpt220V/
500Watts; 0.5% regulation rugged down
Tropicalized new (Lpt125)... 29.95

Same unit with isolation Transf... 39.95
110-115V at 1000Watts.

BENDIX GYRO SERVO COMPLETE... 4.95
PARABOLIC ANTENNA COMPLETE with
motor, drives and Selsyn New... 16.95

BEAM MOTOR & SELSYN & STAND... 10.95
AUTOSYNS Type 5/115V/60cy new... 2 for 18.00

Autosyns AY1&5/24-28V/60/400cy... 3.95
AUTOSYN Compass 360° Indicator... 7.95

Crystal Diodes 1N34 @ \$1.39... 5 for 5.75
Crystal Diodes 1N21 or 1N26 @ \$1... 3 for 3.25

Crystal Diodes 1N23 or 1N28 @ \$1... 3 for 2.80
WIRE power & lighting Navy 110... 1.50

FOXBORO GRAPHIC 115V/60c strip recorder... 39.95
I-222 Crystal calib Signal Generator Freq-
meter, Monitor, 801&5 & 45to7mc's
dual osc, covers IF ranges FM & Tele-
vision 2nd,3rd,4th harmonics useable to
230mc's Six tubes, 115V/60cy inpt Cpte... 39.95

TRANSFORMERS 115V/60 cycles input:
15000V, 35ma/\$15.95; 1200VCT 300ma... \$5.95

500VCT/60ma, 6.3V/4A/\$1.49; 1100VCT/212ma... 6.50

700VCT/120ma, 6.3V/2.4A, 5V/2A-\$2.69... 2 for 5.00

1350VCT/150ma, 6.3V/5A, 5V/2A cased UTC... 7.50

640VCT and 1540V/250ma/\$4.95... 2 for 8.95

1100VCT/150ma, 6.3V/3A, 5V/3A HVins... 3.95

2500V/15ma/\$5; 5V/115A, Kenyon... 7.95

1000VCT/110ma, 6.3V/5A, 5V/3A, 4x6.3V/5... 4.25

1000V/45ma, 795VCT/80ma, 3x5V/3A, 6.3VCT/
1A, 6.3V/3A Hmtdly cased HVinsltd... 7.95

772V/2.5ma, 2.5V/3A/\$3.95; 1230V/262ma... 5.95

3200VCT/200ma, 780VCT/200ma, 12VCT/5A... 12.95

7.5VCT/6.5A, 6.3VCT/3A/\$3.75; 10V/8A/12KV... 6.95

1600VCT/250ma/\$4.25; 30V/4A... 3.25

160VCT/120ma, 10V/3.25A, 2.5V/10A, 6.3 VCT/
2A, 5V/3A HLLCRFTR-610/HVinsltd... 5.95

115 or 230V/50-60cy/1400Watt... 14.95

110 or 220V to 220 and 440/190Watt... 4.50

AUTO Transf 115/160/170/180V/1.95A... 2.95

230 or 117/112/103/93V/7amp GE... 12.95

MODULATION Transf PParallell 6L6-807's to
RF 807's/2000ohm load-cased... 2.95

CHOKE 20hy/100ma; 98c 50hy/150ma... 1.49

CHOKE Swinging 15-29hy/150ma... 2.95

12hy/300ma/\$2.95; 12hy/500ma/95ohm... 9.95

15hy/400ma or 20hy/300ma/15KVins... 7.95

3hy/40ma/3 for \$1; 0.5hy/100ma... 4 for 3.98

3hy/400ma/\$2.75; 8hy/200ma... 2 for 2.09

8hy/150ma new UTC, Cracked Bklt T Bd... .09

UTC LVM11/30Watt Autoformer UTC... 2.95

VACUUM CONDENSERS:
GE 60MMF/7500V... 2.95

GE 100MMF/7500V... 4.95

JEN 50MMF/2000V... 6.95

GTD OIL CONDENSERS:
16mfd/600WVDC \$1 @... 2 for 1.59

4mfd/600WVDC... .49

10mfd/600WVDC \$1.25 @... 2 for 1.89

20mfd/600WVDC \$2.50 @... 2 for 3.98

2mfd/330VAC/1000WVDC... 2 for 1.89

4mfd/330VAC/1000WVDC... 2 for 2.50

15mfd/330VAC/1000WVDC... 3.00

2mfd/2000WVDC... 2 for 3.98

3mfd/2000WVDC... 2 for 5.98

4mfd/3000WVDC... 5.00

5mfd/5000WVDC... 10.00

4mfd/5000WVDC... 15.00

2mfd/12500WVDC... 25.00

1mfd/25000WVDC... 75.00

8mfd/660VAC/2000WV... 2.95

.0025mfd/25KVWKC... 4.95

"IF" TELEVISION&FM Dbl slughtened Hi-freq
design, Constant Q, 11.4 to 13.4mc's... Two for \$ 0.98
COAXIAL RG22U dual 95ohm line 50 ft... 2.49
DIAL TELEPHONES COMPLETE with HAND-
SET WESTERN ELECTRIC *LN @ \$11 Two for 19.95
SPEAKERS PM4 Alnik5/\$1.30; 5" size... 1.45
TRUMPET Reflex Reentrant projector 35to55 watts
with W.E. head complete... 29.95
WE 125to250Watt multi-cellular NINE
DRIVER Trumpet complete-Navy... 125.00
WE DRIVERS PM heads 25to55Watts @... 11.00
WE Diaphragms ES671349 for Drivers... 3.95
RCA Bull Speaker *LN... 14.95
SPEAKER PM 12"Hivduty&outpttransf & box... 9.95
HEADPHONES HS30, 79c ea. Two sets... 1.50
WSTGHSE & GE 150VAC MTR 2 1/2" B' Cad... 3.50
MICROSWITCHES 2 for 39c... TEN for 1.49
5 MFD/600 WVDC COIL & BRKT... 2 for .88
HRO/RAS3 NAVY COMPLETE WORKS... 285.00



PRECISION RESISTORS I.R.C. SHALLCROSS MPCO, INST. RES. CO. OHMITE, WE, for METERS BRIDGES, AMPLIFIERS

*1/2% **5% ***10% (REST 1%)
20000** 4300** 5100** 12000**
30000** 84000** 150000** 220000**
245000** 250000** 950000** 1155

ABOVE SIZES 30c each astd... 10 for \$1.98

1	2	3	4	5
6	10	12	20	25
30	37	45	55	60
70	80	100	101	107
120	125	150	160	165
182.4	200	209.4	220	230
240	250	266	280	286
300	320	340	400	426
440	452	480	500	520
540	550	580	600	612
640	700	750	800	850
900	910	1000	1030	1100
1110	1150	1175	1200	1250
1260	1330	1350	1500	1600
1650	1800	1900	1960	2000
2080	2142*	2300	2400	2485
2490	2500	2600	2635	2800
2850	2860	2900	3000	3100
3290	3500	3730	4000	4300
4440	4444	4500	4720	4850
4985	4900	5000	5025	5210
5270	5500	5730	6000	6300
6500	7000	7500	7613	7700
7950*	8000	8250	8500	9000
9710	10000	10500	12000	14600
15000*	17000	18000	19000	20000*
21500	23000	30000*	40000	50000
60000	68000	75000	80000	91000
95000	100000	120000	130000	150000

ABOVE SIZES each 45c... 10 for \$3.00

147000 150000 166750 175000 185000

201000 229000 250000 254000 265000

268000 294000 314000 333000 333500

400000 402000 420000 422000 458000

478000 500000 575000 600000 654000

700000 750000 900000

ABOVE SIZES each 60c... 10 for \$5.00

950000 1MEG 1.200 2MEG 2.855

3MEG 3.673 4MEG 4.230 4.250

4.5MEG 5.3MEG 9.050 10MEG 11.55

12.83 20MEG

ABOVE SIZES each 90c... 10 for \$6.95

Victoreen Vacuum Precision Resistors

.53MEG 1MEG 1.5MEG 2MEG 3MEG

3.75MEG 0.25to1% accy Hivolt... ea. \$1.00

IRC NAVY PRECISION 1MEG 1/501% MF. 1.69

IRC NAVY PRECISION 2MEG 1/501% MF. 1.69

Caged... 4.95

WESTON 456 Twin Galvoma 4" accy 1/401%

Hidamping 40-0-40&10-0-10ma... 14.95

EE5/WE Telephone complete *LN... \$10.95

EE55 Telephone Test Set... 19.95

H23/TS13 Telephone Handset... 2.95

TGSB Communications Key, hdphone and mike... 6.95

VIBROPLEX Key used \$3.95; NEW... 5.75

MIKE WE Navy push to talk and plug... .98

CFT RCVR 250-1500KC *LN... 30.00

AN/AP13 HF RCVR less tubes *LN... 5.95

COILS Hallicrafters BC610/H14/47 to 52... 20.00

TU49/3 to 4mc's for VFO and Data info... 2.50

TU47, 48, 50, 51, 52 tuning units-HT4 @... 3.95

AN/CRW-2 RCVR, Dynmtr less tubes... 2.95

ART/13 AMPLIFIER \$2.95; with tubes... 5.95

VIBRAPACK MALLORY 12Vinpt/225V/60ma... 3.95

T17B MICROPHONE push button and plug... .89

STROBOFLASH Dual, SC 1503 aircraft set inpt
12V complete power supply, Cables batteries
and 2 Krypton Hi intensity lamps... 89.95

STROBOFLASH Krypton Lamp & Ign Transf... 7.95

* * * * *

\$2 Min. order FOB N.Y.C. Add Postage all orders
and 25% deposit. Worth 2-7230. Send for catalog.

Specialists in International Export, School, College
& Industrial trade. Money Back Guarantee.

ELECTRONIC PARTS •

"TAB" FOR TUBES

1E7G	.89	6SL7	.69
1L4	.98	6SN7	.58
1P5G	1.08	6V6	.60
2A5	.60	6X5	.75
2X2	.81	6Y6G	.87
2X3G	.75	7C5	1.00
3A4	.52	12A5	.60
3B7/1291	.49	12AH7	1.00
384	.43	12K8	.84
5R4G	.70	12SA7	.58
5T4	.97	12SG7	.82
5U4G	.63	12SK7	.69
5W4	.69	12SR7	.69
5Y3G	.41	12SC7	.62
5Z3	.55	35L6	.62
5Z4	.89	35Z5	.52
6AB7	.89	50L6	.64 954
6AC7	.65	30	.74 955 & Socket .90
6AG5	.97	80	.41 956
6AC7	.90	15E	1.95 958A & B .90
6AK5	.75	8C24/24G	.74 991
6AL5	.81	100T8	2.90 128H7
6B4G	1.20	VR105	.74 1299/3D6 .49
6B8G	1.00	VR150	.74 1613
6C4	.65	2C26	.74 1616
6C5	.48	2C40/446A	.88 1625
6C8	.73	3B24	.74 1641/RK60 .49
6C8G	.74	304TL	5.95 2050
6D6	.61	307A	3.25 9002
6E5	.69	450TL	18.00 9004
6F6	.69	WL531	25.00 9006
6F7	1.20	5D21	19.00 3AP1
6F8	1.26	6AR6	1.28 3BP1
6G5/9H5	.90	703A	3.95 5AP1
6G6	1.08	717A	.85 5BP1
6H6	.58	723	2.95 5BP4
6J4	1.45	725	2.95 5CP1
6J5	.62	807	1.38 5FP7
6J6	.54	808	2.00 7BP7/1813
6J7	.81	813	0.90 V7127
6K2	.66	815A	2.28 631P/8N4
6K8	.81	826	1.45 CK1006
6L6	1.15	829B/3E29	2.90 2J21
6L7	.97	836	1.47 2J32
6N7	1.20	837	2.25 2J55
68A7	.43	864	.60 2K29
68C7	.84	866 & 8	1.00 20X672
68C7	.84	872A	2.75 199098
68J7	.63	931A	1.87 289881
CE206		CE215	805
2RA6	3.95	2RA15	10.80 845



For breakages and open filaments no guarantee.

MAZDA 86/115V Bulb 10 for \$1.45;

49/2V/60ma... 10 for \$0.90

44/0.3V/250ma 10 for \$0.94;


Neon NE20/51... 10 for 1.00

BC451 or BC450/SCR274 Control box... each 1.95

EXTRA SPECIAL!

STEEL

Instrument Cases

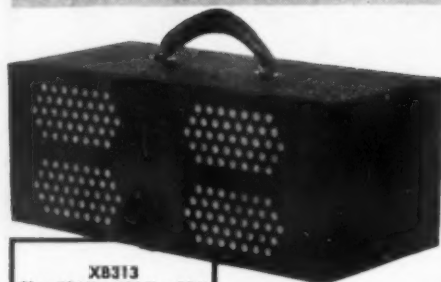

XB313
Size 8 3/4" x 7 1/2" x 18"

ONLY \$1.00

XB312
Size 8 3/4" x 11 1/2" x 18"

ONLY \$1.50



BLACK wrinkle finished steel cases for use on oscilloscopes, V. T. Voltmeters, Amplifiers, Portable Transmitters, Receivers, Test Equipment, etc. Supplied with smooth black 1/8" thick masonite panel, nickel plated screws and brackets. The two sides are perforated for ventilation. Case has strong, genuine, split leather handle.

Make your own special equipment and give it that professional appearance. Order several in both sizes as supply is limited.

• Shipping weight each approximately 8 lbs. Terms orders under \$5.00 full amount with order. Larger orders 20% with order balance C. O. D. Include sufficient money for Parcel Post, unused balance refunded. Minimum order \$3.00.

WRITE FOR OUR LARGE GENERAL CATALOG OF SUPER BARGAINS.

BUYERS SYNDICATE

786 CAREW STREET, SPRINGFIELD, MASS.



Fig. 8. High-gain, ghost-free reception is obtained with a single channel antenna, consisting of director, dipole, and reflector.

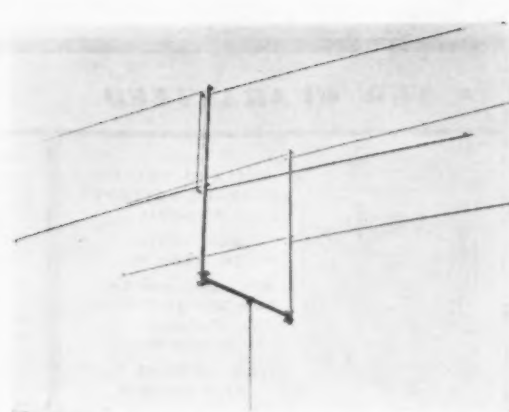


Fig. 9. This stacked array consisting of two dipoles with respective reflectors, provides good directivity without displaying excessive selectivity characteristics at the video receiver.

Because many urban locations require the use of these highly directional antennas to obtain adequate, ghost-free, interference-free reception—the technician should be familiar with the more popular and practical types.

Regardless of their unusual design and appearance, however, all kinds of highly directional antennas are sited and oriented according to the *Basic Procedure of Installation* (Table 1).

Since a degree of directivity is obtained when either a director or a reflector is used with a single dipole, a combination of both director and reflector with a dipole (Fig. 8) provides much greater directivity. Although originally designed by *Workshop Associates* for single-channel operation, the antenna can be used for reception of adjacent channels with fairly good results.

A variation of the dipole-and-reflector antenna is the *RCA* stacked array (Fig. 9) consisting of two dipoles, one above the other, with their respective reflectors. Also known as a *double-doublet*, the array is directional without too-sharp selectivity thus permitting the antenna to be tuned to any of the six television channels (1 to 6). A variation of this

array is the *TACO* dual dipole-and-reflector (Fig. 10) used here at a high elevation not only to provide strong, ghost-free signals but also to overcome local "noise" interference of an industrial district; a good example of the importance of antenna height for adequate reception.

Although widely used in suburban areas, so-called "broad-band" antennas, or *folded dipoles*, are seldom satisfactory for urban installations, particularly in commercial or industrial locations in large cities—because they are not sufficiently directional to eliminate ghosts or reflected images.

The goal of high directivity on every channel with a single antenna can only be achieved through use of one of the rotatable antenna assemblies now on the market. A dual-element type developed by *Farnsworth* (Fig. 11) has one dipole for reception of channels in the popular "lower" television band (44 to 88 megacycles) and a much shorter dipole for reception of channels in the "upper" band (174 to 216 megacycles). Motor driven, with precision control of direction, the arms rotate in a complete circle so that the dipoles can be directed broadside to any desired television station on any channel. Few television cus-

Fig. 10. Dual dipole and reflector installed at a high elevation to insure ghost-free reception with minimum of interference from surrounding district.

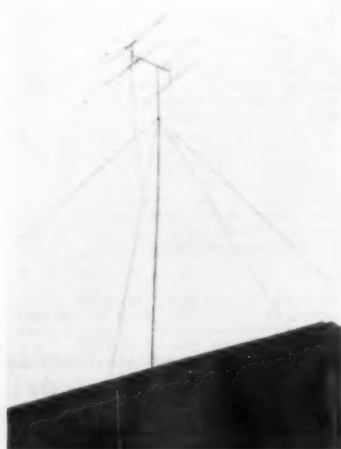


Fig. 11. A dual-element rotatable dipole antenna provides high directivity on all television channels. A precision motor control is used to provide for the accurate tuning of several different and widely separated television stations.





IN BUYING RADIO PARTS Demand This SEAL of QUALITY of America's Radio Storehouse



LOWEST PRICES • HIGHEST QUALITY • NO WAR SURPLUS

GENERATOR CONDENSERS



PHILCO part No. 61-0177—5 mfd.— $\frac{1}{2}$ " x $\frac{1}{2}$ "—4" lead-slotted mounting strap for easy installation—Standard Merchandise—not war surplus—Present list price \$1.00.
Our special—
ever 85% off **14c**

OUTPUT TRANSFORMERS

Clean stocks—long leads—mounting feet—made to fit where you need them.
For 6F6-6K6—to 4 ohm voice coil—size 2" x $\frac{1}{2}$ " x $\frac{1}{2}$ "
50L6-35L6-25L6 to 4 ohm voice coil $\frac{1}{2}$ " x $\frac{1}{2}$ " x $\frac{1}{2}$ "
Specify quantity of each type you need at.....



49c

CATHODE CONDENSERS



10 Mfd. at 25 working volts— $\frac{1}{2}$ " x $\frac{1}{2}$ " tubular type—aluminum cans—overall cardboard sleeve—tinned leads—quality construction by a national manufacturer—backed by the famous R. S. & E. guarantee—list price 73c. Priced to make you money at 12c each lots of 10 for 108 for 900

MIDGET I. F. TRANSFORMERS



400-500 Kc range— $\frac{1}{2}$ " square x $\frac{2}{3}$ " high—ceramic based mica trimmers—high gain iron cores—pep up old receivers—ideal for new construction. List price \$2.10—up to 88% discount—stock up now for future use.

Each **29c** Dozen **339** Hund. **2500** red

AEROVOX GL 8-600




Genuine Aerovox 8 mfd.—600 volt working—inverted screw mounting—aluminum can $\frac{1}{2}$ " x $\frac{1}{2}$ "—6" insulated leads. List Price \$4.00—quantity limited—order now on this one time item at only **99c**

CHICO. MODEL 451A AC-DC Volt—Ohm— Milliammeter



A dependable instrument of wide utility—sensitivity 1000 ohms per volt.
Ranges: Volts AC, DC, and Output Ranges, 0-10/50/100/500/1000.
Ohms full scale, 500,000.
Ohms center scale, 7200.

NET complete with batteries **1490**

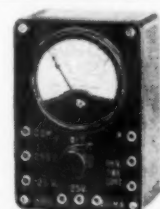

CHICO. MODEL 312 Volt—Ohm— Milliammeter

An economy pocket meter featuring a 2" moving vane meter.
Reads: AC-DC volts, 0-25/50/125/250;
Mills AC-DC, 0-50;
Ohms, 100,000;
mfd. .05-15.
Jacks provide range selection.

NET Complete with cord and plug..... **675**

Start Your Own RADIO SERVICE SHOP as low as **9950**

Complete Starting-in Business Stocks of
**TEST EQUIPMENT, TUBES,
PARTS, TOOLS, EVERYTHING**

Write, Wire, Phone for Full Details

PHONO PICKUP CRYSTALS

Standard types—Set Manufacturers close-out—**all Guaranteed**



Webster F2—Replaces L26-L40-L70 etc.—pin type terminals—1 oz. pressure—1 volt output—5000 cycle cu
List price \$5.00—you pay us.....

149



SHURE P93—W57A—pin type terminals— $\frac{3}{4}$ oz. pressure—1.6 volt output—6000 cycle cut off.
List price \$4.45—our Special.....

198



Astatic L-70—new postwar design—solder terminals— $\frac{1}{4}$ oz. pressure—1 volt output—4000 cycle cutoff.
List price \$5.55—we quote you.....

198

Pep-Up PHILCO CHANGERS

At last! All the parts you need to restore brilliant tone and volume to "sick" changers! You'll need all three items—sell your customer a 100% reconditioning job—Selenium cell only, no holder **\$1.80**
Sapphire needle only, no mirror **\$1.20**
Special original equipment lamp **27c**
RECONDITIONING KIT—all three above **321**
items—postpaid—special at.....



RADIO RULE

Here is a clear 6" plastic rule—a necessity for radio students, draftsmen, hams, all who desire cleaner, more precise work—National advertised at \$2.00. Order yours today postpaid only..... **35c**

SEND FOR FREE CATALOG

MULTI-RANGE MILLIAMMETERS

Two types—for A.C. or D.C. measurements

MODEL 671—for A.C. current. Seven switch selected ranges of 0-5, 10, 25, 100, 250, 500, and 1000 milliamperes.
MODEL 675—for D.C. current. Eight switch selected ranges of 0-1, 5, 10, 25, 100, 250, 500, and 1000 milliamperes.
Here are two meters you can't afford to pass up—just the thing for radio servicing, transmitter trouble-shooting, general lab and experimental work.
A One-Time only Special buy at



795

TRIPLET 606B-VOLTAGE TESTER



Checks voltage and polarity. Range: 0-440 AC-DC volts—definite indications for 115, 220, and 440 volt lines. Separate polarized vane for AC or DC indication. Built in test leads. Excellent for checking wiring, fuses, general factory installation and maintenance. Every plant—every electrician needs several at this low price. Regular net 16.67
Special at..... **895**



TRIPLET VOLTMETERS

Panel meters by Triplet! Top quality instruments—new—boxed—five popular types—priced right—your chance to get those meters you've always wanted—

MODEL 332—0-150 A.C. volts—3" round flush mounting black brass case.
MODEL 231—0-150 A.C. volts—2" round flush mounting bakelite case.
MODEL 237—0-150 A.C. volts—2" square flush mounting bakelite case.
MODEL 221—0-30 D.C. volts 2" round flush mounting bakelite case.
MODEL 324—0-400 D.C. volts—3" round projection mounting—bakelite case.
Supply limited—order now—list models you desire. **EACH**

295

RESISTANCE LINE CORDS



Standard 3 terminal 135 ohm AC-DC cords—sturdy construction—flexible—5 $\frac{1}{2}$ ' long—complete with plug—for sets having approximately 60-75.2 volts drop in the filaments—Regular list price 1.17—

Only 33c

Include full remittance with orders of \$3.00 or less. Include 25% deposit with all C.O.D. orders of \$3.00 or more. All shipments sent express collect if postage is not included. Prices subject to change without notice.

BE SURE TO INCLUDE SUFFICIENT POSTAGE. EXCESS WILL BE REFUNDED.

RADIO SUPPLY & ENGINEERING CO., Inc. 129 SELDEN AVE. DETROIT 1, MICH.

CHRISTMAS SPECIALS

A Large Stock of Scarce Items
All Items NEW Unless Indicated (U)
All USED Items Clean and Tested



Ideal Rig for Low Power Amateurs, Emergency Nets, Portable, etc. Can be Powered by Batteries, A.C. Power, or Handcrank Generator.

BC474A Trans. Rec., P.O. SCR288 Field Set 3500-6300 kc., fone-c.w., Rec'r tubes, 1N5GT, 1A7GT, 1D8GT, 3A8GT; Trans. Tubes, 3-6V6GT's.	
NEW with tubes and manual (R.C.A.)	\$37.50
USED with tubes—good cond. (R.C.A.)	27.50
Key (R.C.A.)	\$1.50
Mike (R.C.A.)	2.50
Filter	2.00
Cable	1.00
4 Legs	1.00
Bag	1.50
GN44A Handcrank Generator and stand	4.95
SCR288 complete with antenna, etc.	57.50
SCR284A, 3800-5800 kc.—Complete set	59.50
BC654A Trans. Rec. Tubes, Xtal	19.95
PI 104A 6-12 volt vibrapack	\$5.95; (U)
PE103A 6-12 volt dynamotor	8.95
CD501A cable for PE103A-BC654A	1.95
GN45A Handcrank Generator and stand	4.95
BC224 Rec. 200-500, 1500-18,000 K.C., 12V	59.50
BC348 Mounting Base. Postpaid	2.50
BC348 Outlet Plug PL-C103. Postpaid	.80
BC348 Mounting Base and outlet plug. Postpaid	3.00
BC1206C Rec. 195-420 K.C. Tubes (Setchell-Carlson)	5.95
GENERAL ELECTRIC 8RB8B7 Tungar Bath. Chgr., 12 battery, 12 amp. or 24 battery, 6 amp.	67.50
BC357J Beacon Receiver, 75mc. tubes, for remote control, opening doors, etc., sensitive relay	3.45
RBL-3 Rec. 15-600 kc., 115V. A.C. tubes, man'l.	44.00
MARK II Trans. Rec., 12V Dynamtr, 2 head sets and mikes, key, ant., etc. 80 and 40 and 2 meters	39.00
BC221 Frequency Meters, tubes, xtal	57.50
TC59, 1500-12000 k.c. trans. rec. tubes 115V. A.C. (U)	109.00
RG59U Coaxial cable—50 ft. min. (per ft.)	.07
HS-23 8000 ohm headset	1.29
HS-33 600 ohm headset	1.29
HS-30 Earplug headset and matching transmr.	1.50
HS-23 8000 ohm headset (U)	.79
H23U Handset	3.45
TS-13 Handset	3.45
TRIMM commercial 17,000 ohm headset	4.25
Found powered chest set \$3.95 each, pair	7.50
Sound Powered headset \$16.00 each (pair)	30.00
200FD20 Johnson var. dual condenser	1.19
MC1855 BUD 100 MMF midget Var.	.69
23mfd. 2,000 volt photoflash capacitor	10.00
1 amp. variac (Clean) (U)	7.95
80 V.A. Sola constant volt transmr. 115V. 60 cycle A.C. (U)	13.50
BC605D Interphone amplifier, tubes	3.95
VT tube conversion chart—Postpaid	1.00
Glazed ceramic lead-thru insulator 1 1/4" diameter, 35c each—3 for	1.00
115 Volt, A.C. Blower from BC1072A	5.95
16MM, 24 volt magazine gun cameras f3.5 lens	24.50
Signal Box Kites. Postpaid	2.50
4E27 Tube Ppd.	\$6.50
811 Tube Ppd.	3.00
829 Tube Ppd.	3.25
75TL Tube Ppd.	3.00
815 Tube Ppd.	3.50
VT-127A Tube	3.50
VT-225 for BC654A	Postpaid
Postpaid	2.00
872A Tube Ppd.	3.50
R-100 Receiver, 560-1500 KC; 3.5-20 mc, 115V A.C., D.C., or battery	55.00
SCR522 Rec. Trans. 28V Dyn. tubes, ant., plugs, etc.	70.00
SCR542 Rec. Trans. 12V Dyn. tubes, ant., plugs, etc.	70.00
SCR522 Rec. Trans. 28V Dyn. tubes, ant., plugs (U)	34.50
Indoor Telephone wire—twisted pair 250 ft.	5.00
MALLORY G369 Vibrapack, 12 volt input	3.95
MALLORY F.P. Elect. Cond. 4x10 mfd. 400V.	.79
Power transformer 660-0-660 @ 350 m.a., 6.3V @ 2.7 amps, 2.5V @ 1.75 amps, 5V @ 4 amps.	10.00
Power transformer 650-0-650 @ 200 m.a., 18V @ 1 amp.—sealed	7.50
Buzzer, 6 Volts A.C. or D.C. Postpaid	1.00
EE8-B Telephone set \$16.00 each	29.50
EE-8 Telephone set (U), \$9.95 each; (Pair)	19.00
Vibrators for PE104A power supply. Postpaid	2.00
LS104 Reflex trumpet speakers 25 watt	30.00
Min. orders \$2.00, prices FOB Pasadena. 25% deposit on all orders.	

PHOTOCON SALES

1060 N. Allen Ave. Pasadena 7, Calif.

tomers, however, appreciate the need for directivity as a means of obtaining ghost-free reception. Despite good engineering design, such antennas are likely to prove expensive toys instead of useful instruments for fine reception.

(To be continued)

Publicity Means Sales

(Continued from page 43)

will be a long, slow process to get most of your prospects to the point where they know that the "Ideal Appliance Center" is run by the Mr. Milligan they read about in the papers.

Here is an example. You win the annual golf meet of the local Elks Club. The newspaper story says: "Stewart Milligan, local radio merchant, yesterday walked off with the gold cup at the annual Elks Club golf meet . . ." If the reader has seen a sign saying, "Milligan's Appliance Center," the reference to your being a radio merchant rings a bell. Otherwise, the name "Milligan" means nothing to him and this sort of publicity is lost. The same thing is true along every type of personal publicity. Get full benefit from it, if you can, by associating your name with the name of your store.

3. Select your audience carefully on every story you plan to send to newspapers or radio. You have a rather definite buying area that includes the great majority of your prospects. In a small town, it may mean the whole town and rural areas for thirty miles


around; in a big city, it might be only one square mile. You must concentrate your efforts in your sales area if they are going to pay off.

Suppose your store is located in Elgin, Illinois. The *Chicago Daily News* may be read by 30% of your prospects, while the Elgin paper is read by 90%. Even though the Chicago paper's total circulation is twenty times that of the local paper, the latter is likely to do you more good. So, if you must choose where to send a story about yourself or your business (as in the case of a feature-type story that only one paper will use) you'd be wiser to place it in Elgin. Mere volume of circulation does not necessarily mean effectiveness.

In most respects, the publicity handling will be the same for the dealer in a small town as for one in a big city. The first has his local newspapers, either small dailies or weeklies, while the second is likely to have a community newspaper or two which serve the people in his own buying area. In almost all respects, these community newspapers are edited and prepared in the same way as small town papers, and will use publicity from a dealer in the same way.

For the dealer in a medium sized city, which is not large enough to have community newspapers but is too large to have newspapers with a community tone, the acquisition of space for the dealer's publicity is likely to be more difficult. It must compete with a broader scope of other material—world and national news, as well as a greater area of local sources. In this case, the news value of the dealer's

The reflecting parabola at the left, mounted on the terrace of the Waldorf-Astoria Hotel in New York, was used to receive television picture signals beamed from a similar microwave relay link transmitted on a roof of the New York Hospital, two miles away, when operations at the hospital were televised by RCA Victor for the benefit of members of the American College of Surgeons who recently held an annual clinical congress at the hotel. The experiment was hailed as a demonstration of the contribution television may make to surgical education.

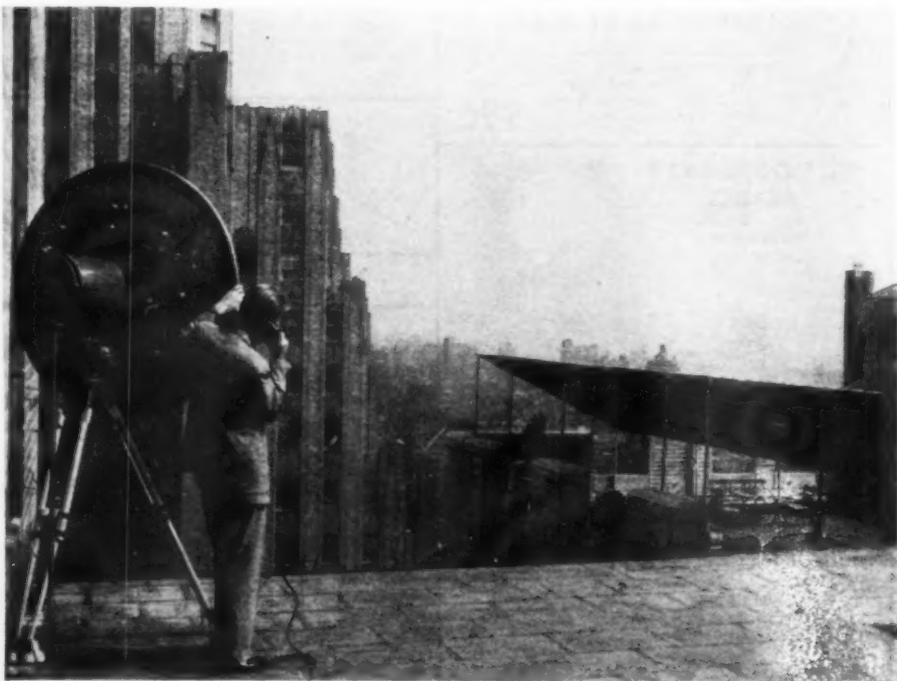

THE FINEST QUALITY

"Communications"

AT LOWEST PRICES



TUNING UNITS

From BC191 and BC375 TU
6B—3,000 kc to 4,500 kc, TU
9B—7,700 to 10,000 kc, TU
10B—10,000 to 12,500 kc, TU
22B—350 to 650 kc. Will supply
closest unit to specified freq. at
time of shipment. Each... \$2.75

From TCE and GP-7. Ideal
basis for ECO rig. Ranges: A
350-800kc, B 800-1500kc, C 1.5-
3mc, E 4.525-6.5 mc, F 6.2-
9.05mc. Complete
set of 5... \$11.00

Units C or E, Each... \$2.75
Units A, B, E, Each... \$2.00

GIBSON GIRL EMERGENCY XMTR: SCR578A

Transmits automatic SOS signal on 509
kc emergency wave. Can be manually
keyed to transmit additional information.
No batteries required. Hand
cranked... \$25.00




TEST SET 159TPX

Measures frequency between
150 and 200 Mc. by heterodyne
method. Pwr. output of xmtr
can be measured directly. Meas-
ures DC voltages up to 500 V.
Operates on 110 V, 400 cy, but
mere replacement of power xfmr
makes it operable on 110 V, 60
cy. Complete with tubes, crys-
tal, calibration chart. New... \$49.50




INTERFERENCE REDUCER, BC 736 H

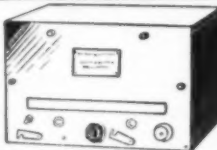Used to reduce interference in
radio receiver BC 403 D.
Many uses. Tubes: 3—6AC7,
1—5T4, 1—6H6,
1—6AG7... \$14.50




R4-ARR2 RECEIVER

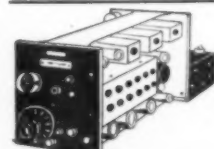UHF receiver (approx. 300 Mc.)
with following tubes, 7—9001's,
3—6AK5's, 1—12A6.
New... \$17.50
W/dynamotor... \$19.20
Less dynamotor, but w/xmtr for
filaments... \$15.50



MOTOR DRIVEN SWITCH

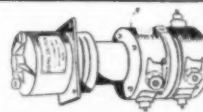Switch operates at 1800 rpm.
using internal 24 VDC motor.
Switch is DPDT, and was origi-
nally designed for automatic
switching of Yagi radar an-
tennae... \$2.00



AN/PRS-1 MINE DETECTORS

New and complete. For detection of both metallic and non-
metallic materials hidden underground. Includes earphones,
speaker, amplifier, spare tubes. Another "Communications"
buy... \$12.75
With Batteries... \$21.65



HEADSETS

Dynamic mike and headset combina-
tion. A high quality, efficient unit,
used in B-19 tank Xmtrs. Mike and
phones complete, new... \$2.85

HS 30 HEADSET: A featherweight
headset with insert type phones that
cut background noises to a minimum.
Low impedance (500 ohms) assures
efficiency and high fidelity... \$.85

Matching transformer to match 500
ohms to 5000 ohms output... \$.35

HS-15 headsets:
8000 ohms im-
pedance, rubber cushions. Comes with 8'
cord and plug PL 55. New... \$1.95

Used, in good condition... \$.63



RADIO-SONDE XMTR. T-49 AMT1

Operates on 72.2 Mc. Good unit for port-
able fly-weight XMTR or walkie-talkie.
May be modified for 6 or 2 meter opera-
tion. In its own container. New, Complete,
with 3A5 tube... \$2.75

MICROWAVE PLUMBING

10 CENTIMETER

Sand Load (Dummy Antenna) wave guide
section with cooling fins, app. 23" high... \$28.00
Rigid Coax Directional Coupler CU-90/U/P
20 DB drop, has short right angle, about
8".... 5.50
Coax Rotary Joint with mounting plate... 8.00
Dipole Antenna in Lucite Ball for use
w/Parabola... 5.00
Flexible Coaxial Connector, rigid coax to
rigid coax 1/2" diam... 2.50
10 CM Dipole and Reflector with Type "N"
Fitting... 2.75
Waveguide to flexible coax coupler (RG 18
U), with flange. Gold plated. App 10"
high... 17.50
Rigid coax shorted section CU-40/A/P... 5.00
Stub-supported rigid coax, gold plated, 9'
lengths. Per 1/2' length... 5.00

3 CENTIMETER

Wave Guide Sections 2.5' long, silver plated
with choke flange... 5.75
Wave Guide 90 deg bend E Plane 18" long... 4.00
Wave Guide 90 deg bend E plane with
20DB directional coupler... 4.75
Wave Guide 18" long "S" curve... 2.00
Rotary wave guide in/out choke to choke
joint... 6.00
Rotary Coupler choke input; round guide
output... 5.25
S-Curve Wave Guide 8" long cover to choke
Wave Guide 2.5' long, silver plate, 180 deg
bend choke to cover... 5.95
Duplexer Section using 1B24... 10.00
Wave Guide 5' length per foot... 1.50
Pick-up loop with adjustable tuning section,
used in duplexer... 1.50
3 CM Wavemeter Maquire 1539TFX... 15.00
3 cm. stabilizer cavity, tunable transmission
type. Model 1551 (TEF 11 GA)... 20.00

1.25 CENTIMETER


Wave Guide Section 1' cover to cover... 2.00
T Section choke to cover... 4.50
Mitred Elbow cover to cover... 3.00
Mitred Elbow and "S" sections choke to
cover... 3.50
Flexible Section 1' long choke to choke... 3.00
Tunable Cavity with Coax input and output... 6.00

CONNECTORS

UG 21/U, Type "N," Male... .85
UG 86/U, Gold Plated... .95

MICROWAVE TEST EQUIPMENT

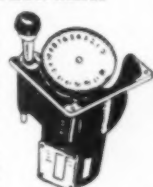Wave guide experimental kit.
Consists of: One direct-read-
ing wavemeter, app 2600-3400
mc. (cavity type); One dum-
my load w/crystal probe; One
line stretcher; full wave; two
wave guide to RG 18/U coax
couplers; two 1' sections w/
flanges. Complete... \$250.00



10 CM ECHO BOX, com-
plete with micrometer adjust
cavity and resonance indicat-
or. Type TS 238/GP. With
calibration chart... \$105.00

10 CM WAVEMETER, Model "SL." Micrometer
adjust cavity with micro-ammeter resonance indi-
cator. Includes 115 VAC operation converter sec-
tion. In grey metal carrying case, complete with
cables & spares. Made by Western Electric... \$135.00

W.E. 1138A. Signal generator, 2700-2900 Mc.
range. Lighthouse tube oscillator with attenuator
and output meter. 115 VAC input, reg. Pwr. supply.
With circuit breaker... \$50.00

MOTOR GEN. P.U. 43 A

Input: 24-28 VDC @ 62 A. Output: 115 VAC,
7 A, 800 CPS... \$15.00

MICROWAVE TUBES

3J31 (1cm)... \$17.50
Magnet for 3J31... 8.00
2J12 (10cm)... 25.00
Magnet for 2J32... 10.00
2J38 (10cm with Magnet)... 37.50
WE700A (L band)... 45.00
WE720BY (8 band 1000 KW)... 25.00
2K25-723AB Klystron... 7.75
QK 50, QK 60, QK 62 Tun-
able packaged Magnetrons
(10cm)... ea. 45.00
Small Quantities of Other Types




Write for information

TRANSFORMERS

(All primaries 117 V, 60 ey)

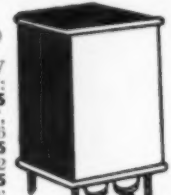Filament Xfms:
No. 5058: sec. No. 1: 6.3 V
@ 2 A CT; sec. No. 2:
6.3 V @ 2 A CT... \$2.45
No. 5126: 5 V @ 3 A CT,
5 V @ 3 A CT, 5 V @ 6
A CT... \$3.25
No. 5100: 6.3 V CT @ 1.2
A, 5000 volt test... \$2.45
No. 5085: 6.3 V NCT @ 6
A, 6.3 V NCT @ 1.5
A... \$1.95
No. 5057: 6.3 VCT @ 1 A, 5 VCT @ 3 A, 5
VCT @ 3 A... \$2.75
No. UX 6899: 5 V @ 5.5 A, 5 V @ 5.5 A,
29000 V test... \$24.50



VIBRATOR TRANSFORMER

Input: 24 V, 12 V, or 6 V. Output: Two 120 V
windings @ .175 KVA. Plus 11 V winding.
Ea... \$1.50

SPECIAL SPECIAL

Transformer to supply filaments of equip-
ments using 12-volt tubes. Input: 117 V
60 ey, Output: 26 Volts @ 2 A... \$1.50

CHOKES

6 Hy @ 150 Ma... \$2.00
6 Hy @ 300 Ma... 4.50
1 Hy @ 800 Ma, 7.5 ohms... 8.95
Dual choke, 2-2 Hy, @ 100 ma... .90
Dual choke, 7 Hy @ 75 Ma, 11 Hy @ 60
Ma... 1.95

DYNA- MOTORS

PE 73 CM. Pow-
er supply for BC
375 Input: 28 V
DC. Output:
1000 VDC @ 350
Ma. Starting re-
lay, filter, etc... \$4.95

Mfrs: Write for
quantity, prices
and discounts on
above item.
BD 77KM, Pow-
er supply for BC
191. Input: 14 V
DC. Output 1000
VDC @ 350 Ma. New, with spare fuse links,
etc... \$5.95

PE 101C, Input: 13/26 VDC @ 12.6/6.3 A. Out-
put: 400 VDC @ 135 Ma, 800 VDC @ 20 Ma.
(9VAC @ 1.12 A)... \$3.40
PE 86 N, Input: 28 VDC. Output: 250 VDC @ 60
Ma. Westinghouse w/Filter... \$1.95
Without Filter... 1.60
PC 77, Input: 12 VDC. Output 275 VDC @ 110
Ma. 500 VDC @ 50 Ma... \$3.25
DAG 33 A, Input: 18 VDC @ 3.2 A. Output: 450
VDC @ 60 Ma... \$2.45
DM 33 A, Input: 28 VDC @ 7 A. Output: 540
VDC @ 250 MA. Power supply for modulator
for SCR 274 N... \$3.95
Dyn. Model 23350, Input 27 VDC @ 1.75 A. Out-
put: 285 VDC @ 75 Ma... \$1.75
DM-21: In 14VDC 3.3A Out 235VDC 90 ma with
filter... \$2.59
DM-25: In 12VDC 2.3A Out 250VDC 50 ma... \$2.49
DM-34: In 14VDC 2.8A Out 220VDC 80 ma... \$2.49
DM-42: In 14VDC. Out 515/1030 VDC 215/260
ma and 2/8VDC... \$3.95
BD-77 input 14VDC output 1000V 350ma DC \$5.95
Motor-Gen. PU43/A Input: 24-28 VDC, @ 62 A.
Output: 115 VAC @ 7 A, 800 Cycles/sec... \$15.00

OIL CONDENSERS

.25 mf @ 20000 VDC... \$17.50
1.5 mf @ 6000 VDC... \$12.50
Aerovox... \$12.50
10 mf @ 25KV... \$75.00
01 mf @ 25 KV... \$20.00

MICA

.08 mf @ 1500 VDC. Sprague
MX60... \$11.50
.03 mf @ 2000 VDC, CD... \$12.75
551A-50... \$12.75
045 mf @ 2000 VDC, Sangamo
G1... \$12.75
00015 mf @ 20 KV, Aerovox 1970-404... \$25.00
0001 mf @ 20KV, Sangamo G3... \$25.00
0051 mf @ 15KV, Sangamo G4... \$25.00
006 mf @ 10 KV, Sangamo G3... \$17.50
002 mf @ 15 KV, Sangamo... \$20.00
Isolating Capacitor, Cornell-Dubilier PL 1417,
106-110 mmf @ 10KV AC (peak). Each... \$3.50
MFRS: Send your requirements for bathtubs,
Micas, Hardware, resistors and connectors.




All merchandise guaranteed. Mail orders promptly filled. All prices, F.O.B. New York City.
Send Money Order or Check. Shipping charges sent C.O.D.

COMMUNICATIONS EQUIPMENT CO.

131 N. Liberty St., New York City 7, N. Y.

Digby 9-4124

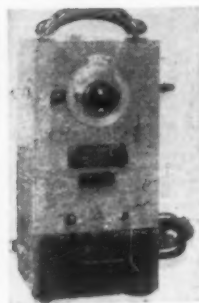LEEDS THE HOUSE YOU HAVE KNOWN FOR 25 YEARS



BC-438 FREQUENCY METER

110 volt AC operated, range 195 to 215 megacycles; complete with tubes, crystal, calibration curves and schematic: **\$9.95** only

RC-1086A-UHF 2 Band Receiver, battery powered Tubes 2-957, 1-1D8GT. Very easily adjusted to 2 meters. In wooden case, with schematic. **\$3.95**

MICA CONDENSERS

Aerovox, type 1590-H-220 low loss, bakelite case; capacity 0.4 Mfd 600v EFF. 18 amps at 3000 KC; 25 amps at 1000 KC. Special **95c**
01 Mfd 600v DC postage stamp type **5c**
15 ass't silver mica, special **95c**

VARIABLE CONDENSERS

100 Mfd double bearing, silver plated. Isolantite insulation; can be ganged either end. **29c; 10 for \$2.50**
25 Mfd balanced stator one hole mtg. Isolantite insulation, polished plates; Swell for UHF. **29c; 10 for \$2.50**
110v Pilot assemblies **39c**
ARC-5 Banana plugs silver plated; doz. **10c**
Antenna plug 46-PS-1 for 522A **15c**
FT-243 Crystal holders **15c**
FUSES-B AG 1/100 amp Inst type; doz. **50c**

General Radio Power Transformer

550-0-550 V at 100 Ma. **6.3 V** at 3 amps. **\$1.95**
5 V at 3 amps.

Relays G.E. high current, 24v coil, 2000 amp. contacts. **39c**
Sigma plug-in type 5-prong, 200 ohm. **1 Ma DC** **95c**
300 ohm twin leads, outdoor or indoor, 100 feet. **\$2.95**
Circuit Breaker, Heineman, 3-5-25-35-65 amp. **95c**
50 Millivoltmeters, basic movement, can be used for any range, with use of shunts and resistors. **\$1.95**

RADIO TRANSMITTER & RECEIVER APS 13

Tunes 410-420 megacycles; light weight airborne Radar, 17 tubes, including 5-6J6; 9-6AG5; 2-2D2; 1-VR105 and 30 megacycle LF strip. **\$11.95**
All for



OIL FILLED CONDENSERS All Standard Brand—Guaranteed

16 Mfd. 400v DC WE. 95c	8 Mfd. 1500v DC. \$3.25
0.05 Mfd. 600v DC dvr. 15c	10 Mfd. 1500v DC. \$3.50
0.1 Mfd. 600v DC. 15c	7 Mfd. 330v AC. \$1.25
2 x 0.1 Mfd. 600v DC. 25c	7.5 Mfd. 330v AC. \$1.25
1 Mfd. 600v DC. 25c	1.78 Mfd. 200v AC WE 25c
2 Mfd. 600v DC. 40c	1 Mfd. 5000v DC. \$2.95
10 Mfd. 600v DC. 95c	0.1 Mfd. 7500v DC. \$1.50
3 Mfd. 1000v DC. 39c	2 x 0.1 Mfd. 7500v DC \$2.00
2 Mfd. 1000v DC. 79c	0.2 Mfd. 8000v DC. 95c
0.5 Mfd. 15000v DC. 25c	2 Mfd. 10000v DC. \$17.50

General Radio Co., VARIACS

200-B 170KVA 0-135v output, 1 amp. **\$12.50**
V-5 860KVA 0-135v output, 5 amp. **\$18.50**
V-SMT 860KVA 0-135v output, 5 amp. **\$25.00**
V-10 1.725KVA 0-135v output, 10 amp. **\$33.00**
V-10MT 1.725KVA 0-135v output, 10 amp. **\$40.00**

NATIONAL CO. PRODUCTS

ACN Vernier dial 5 x 7 1/4 **\$2.98**
AR-16 air spaced exciter coils, for 5-10-20-40-80 meters; end, center or swinging link **\$1.15**
XB-16 Socket for above **33c**

Complete stock of NATIONAL CO. Receivers
Condensers, dials and other parts ON HAND.
Catalog on request

Crystal Mike, guaranteed perfect. Use for replacement of your shot mike. Less holder. Special **89c**
Octal socket, low loss bakelite molded in metal ring, 1 1/4" diameter **5c**
Octal socket, Isolantite molded in metal ring, 1 1/4" diameter **8c**

WIRE WOUND POTENTIOMETER

100,000 ohm, precision made G.R. type; 25 watt, 6" diameter. Brand new. **\$1.95**
Our supply of chassis, panels and cabinets, black crackle finish, are priced LOW—as usual.



If not rated 25% with order, balance C.O.D. All prices F.O.B. our warehouse New York. No order under \$2.00. We ship to any part of the globe.

LEEDS RADIO CO.

Dept. RN12
75 VESEY STREET
Cortlandt 7-2612 New York City 7

releases must be especially high, and the material prepared with greater care to make it rate space in the papers. A story that appears will reach not only the dealer's buying area but other sections which ordinarily would be considered out of his zone. Such publicity can very greatly expand the area from which he draws his sales.

There are other factors that will determine your selection of an audience. One publication may reach a large group of low-income families, while another reaches a smaller group of high-income families. In all probability, the audience you reach in the second publication will provide more sales and larger ones. Home owners usually are better prospects than apartment dwellers, women generally make more decisions on radios and appliances than men, and so on. Keep these points in mind in planning publicity.

4. At the same time, cover all reasonable possibilities. Unless a story is naturally limited to one paper (for example, you have a proposal for a new license law which calls for the support of a newspaper and cannot effectively be proposed to all papers simultaneously) give it to every paper and radio station which might use it. Not only will this assure you the fullest possible coverage, but it will protect your relations with the papers and stations. Be sure that all get the story at the same time. (Methods for handling news releases will be discussed later.)

5. Always remember that the foundation of the reputation you are trying to build is fair play. Ballyhoo alone, not based on a sound business policy, builds up a name to the point where, when unsound practices cause trouble, they are played up in the press and in conversation beyond normal proportions because of the prominence of the person involved. Select from your business practices some special feature, develop a slogan or identifying phrase, such as "You're sure of satisfaction at Milligan's" or "We're as near as your phone," and use this in your advertising. Then let it be a theme—not used—but implied whenever appropriate, in your news releases.

6. Good publicity springs from activity. Doing things makes news. For personal publicity that will reflect to the advantage of your store, join local civic groups, instigate plans for local improvement, talk before business groups, work with news-making committees, be active in church and social organizations. For business publicity, do things that are different; offer a free orange squeezer to every dark-eyed, blonde woman in the circulation area of the newspaper in which you place the story; give a bottle-warmer free to every veteran of World War II upon the birth of his first child. These things not only will attract attention to you through regular publicity channels, but they'll make real friends of the people who receive the free item.

7. Develop a sense for news. If

From: Your name
Name of Store
Address
Telephone

For Immediate Release
(or indicated time of release)

If you have dark eyes and blonde hair, and are under 30, you're due for some easy squeezing.

Milligan's Appliance Center, 84 Main Street, is giving every girl between 16 and 30 who has these striking features a newly patented orange squeezer, to introduce the new item. Stewart Milligan promises to take care of all who qualify anytime Thursday between 8:30 a.m. and 6 p.m.

Note: Any traces of recent peroxide rinses will disqualify applicants, Milligan said.

Fig. 1.

you should employ a one-armed veteran to sell refrigerators, there is a real human-interest in the fact he can demonstrate how to remove ice cubes—and it will show how easy the refrigerator's trays are to handle. Many events and plans that come up normally can be developed into news, if you'll cultivate the sixth sense of watching for them.

8. Co-ordinate your publicity with your advertising. This doesn't mean that you should try to get the editor to run a story every time you place an ad. Many editors resent this, and as a general rule the larger the paper the more dangerous this practice becomes. Instead, plan your advertising to take advantage of stories appearing in the papers. If you run a unique sale, for instance, get the stories into the papers, then come out with your ads. Also establish a theme for your store's policy, perhaps based on the slogans mentioned earlier, and use this theme in both publicity and advertising.

9. Know how to handle the mechanics of publicity. The method of preparing a publicity release is shown in Fig. 1. When the story covers more than one page, end each sheet with the end of a paragraph, and then mark "(more)" at the bottom of each page except the last.

Except where an unusual feature that will attract attention is involved (as in the story shown in Fig. 1) get all essential facts into the first paragraph, answering the questions "who," "what," "when," "where," "why." If the story in Fig. 1 were written in ordinary news style, it might start like this:

"All girls between 16 and 30 who have blonde hair and dark eyes will receive a newly patented orange squeezer free Thursday at Milligan's Appliance Center, 84 Main Street. The offer is made to introduce the new device, according to Stewart Milligan."

Except when the story must not appear before a certain time for a legitimate reason, mark the story "For Immediate Release," thus permitting the editor to use it whenever he wishes.

Pictures accompanying your story should be on 8 by 10 inch glossy paper. Of course, they should be clear and sharp and have as much reader-interest as it is possible to put into them. A picture of a beautiful girl examining a new refrigerator is far more likely



(Above photo taken at servicing bench of the Heppe Co., Phila.)

ALL 16 RIDER MANUALS!

Ever stop to think how many successful servicing shops, with which you are personally acquainted, have complete sets of Rider Manuals? Ever notice how many photographs of servicing benches, illustrating success stories in magazines, show all Rider Manuals?

This is more than coincidence. It is irrefutable evidence of how Rider Manuals profitably meet the day-in-day-out data needs of busy shops.

Now, consistent with "Seventeen years of Continuing Service to the Servicing Industry," Rider has further ANTICIPATED your needs by establishing the "24 Hour Data Service" explained below.

Here is further justification for the faith of the many thousands of servicemen

who have depended upon and benefited by the time-saving, authoritative, money-making data supplied by Rider Manuals.

It is such informed publishing which has resulted in Rider Manuals pouring out profits for servicemen year after year after year. It is such progressive services which suggest you be sure your shop has the sign of successful servicing—all sixteen Rider Manuals.

* Rider Manual data is the OFFICIAL AUTHORIZED servicing data right from the service departments of the companies that made the sets. No one knows better than the manufacturer what servicing procedures are best for his product. This is the basis for the authority and the success of Rider Manuals.

NEW

24 HOUR DATA SERVICE

On November 30, 1947, we instituted our new photostat service to supply you with information on any newly issued, or old, receivers. For 10c (stamps are OK) we will send you the schematic, voltage data and parts list and everything else which will fit on the two pages. Additional manufacturers' data is 5c a page with a maximum charge of 35c for everything up to seven pages. If the manufacturers' data requires more than seven pages, each additional page is 3c. Here is a way to get whatever service data you need between Rider Manual publication dates.

**ADDING FURTHER WEIGHT TO THE VALUE OF OUR
"SEVENTEEN YEARS OF CONTINUING SERVICE
TO THE SERVICING INDUSTRY"**

VOL. XVI SHOULD BE OVER YOUR SERVICE BENCH, NOW!

Volume XVI is the first to be issued under our new three-volumes-a-year publishing schedule which brings you systematically-bound, authoritative servicing data at the earliest practical date.

It contains data from 94 manufacturers—a greatly increased percentage of "clarified-schematics"—a generous number of photographs on small table models and a separate "How It Works" book, in addition to the usual authoritative information you have come to depend upon in previous Rider Manuals—and this is made available to you in Volume XVI at the greatest possible economy; less than a penny a page. Your jobber has Volume XVI in stock now—Enjoy the benefits of its use—get it today!

768 Pages
Plus
"How It
Works" Book
\$6.60



RIDER MANUALS—16 VOLUMES

Volume XVI.....	\$ 6.60
Volume XV.....	18.00
Volume XIV to VII (each Volume)	15.00
Volume VI.....	11.00
Abridged Manuals I to V (one volume)	17.50
Record Changers and Recorders	9.00
Master Index (covering Volumes I to XV)	1.50

JOHN F. RIDER PUBLISHER, Inc.
404 Fourth Avenue, New York 16
Export Agent: Rocke International Corp.
13 E. 40th St., N.Y.C. — Cable ARLAB

RIDER MANUALS *Mean* **SUCCESSFUL SERVICING**

TELEVISION HEADQUARTERS

TELEVISION FOUNDATION KIT

The television foundation kit consists of the most essential (and expensive) parts needed in the construction of a television receiver starting with the high voltage power supply, for the picture tube, right through to the antenna. The kit contains the high voltage picture tube transformer (for five or seven inch tube), 2X2 filament transformer, low voltage transformer for the receiver, cathode ray filament transformer, filer choke, 6.3 filament transformer for the 16 six volt tubes along with the five volt transformer for the 5U4. The two high voltage filter condensers, blocking oscillator, transformer all R.F.'s sound and video I.F.'s peaking coils, discriminator transformer. Rectine, tubes 2X2 and 5U4, the picture tube 5BP4, an all aluminum Elinor dipole antenna are also included. Of course there is the easy-to-follow 26-page instruction book with a large 12 by 18 schematic diagram. The instructions include television theory, circuit functions, explain scanning, give preliminary voltage measurements, parts layout and final adjustment of the television receiver which facilitates easy alignment without the use of elaborate test equipment. The only knowledge necessary to build this set is the ability to read a simple schematic diagram. Most radio men will have many or all of the minor parts not included in the foundation kit. **\$34.75**

Remaining set of necessary tubes. **\$16.95**

RAY-LECTRON COIL KIT

INCLUDES:

1 Oscillator Tank Coil, 1 Antenna Coil, 6 RF Tuning Coils, all mounted on Switch Assembly Plate; 5 Video IF Coils, Shielded Permeability Tuned; 1 Shielded Discriminator Coil; 3 Video Peaking Coils, and Instruction Manual containing Circuit Diagram for 20 Tube Seven Inch Picture Tube Set, together with detailed Assembly Instructions, and Parts list.

The design of these Coils makes it possible to obtain satisfactory operation within the ENTIRE service range of ANY Television Sta- **\$23.50**

tion, Complete

NEW TELEVISION COIL KIT 510

Build a 10" or 15" television receiver. Complete kit of permeability tuned video IF, RF, and Sound Coils for high quality television receiver designs. Contains all necessary coils for 3 stages 4mc. wide video, 2 stages sound, discriminator, peaking, oscillator, and RF. Complete instructions included. **\$9.95**

Priced at Only

ALL CHANNEL R. F. UNIT

For use in Building your own custom-made Television Receiver — Any size or type Transvision all-channel R.F. unit is factory pre-wired and tuned for 7 channels* (covers all channels in lower and higher bands in any single area operating presently or in the future). Average sensitivity 20 microvolts; has R.F. stage before oscillator; complete with 3 tubes: 1-6AK5, 1-6AK6, 1-6C4; input impedance 300 ohms, balanced to ground. Size—9½" deep, 4½" high. **\$31.95**

6½" wide. Net.

CATHODE RAY TUBES

5BP1	\$3.95	5TP4	\$34.00
5BP4	4.95	76P4	19.40
2EP4	18.95	9AP4	50.00
7DP4	21.60	10BP4	39.60
12AP4	\$60.00		

NIAGARA COMPONENTS

CONDENSERS

CF 45—1 mfd—3500 volt DC	\$1.98
CF 48—.05 mfd—2500 volt DC	1.09
CB 18—.25 mfd—4000 volt DC	2.95
ER25AD—dual 25 mmf per sect. variable condenser	2.04

SOCKETS

11 prong isolant scope socket	\$0.59
Octal socket	.12
Special hi. voltage socket for 2X2	.59

TRANSFORMERS

TS.6—Scope transformer—2500 v. @ .4 a., 2.5 v. @ 1.75 a., 6.3 v. @ .6 a.	\$9.95
TS.5—Western Electric—D303184—hi. volt 4200 v. @ 9 ma lo. volt. 640 v. @ 200 ma—fil. 6.4 v. @ 5 a., 5.4 v. @ 3 a., 5.1 v. @ 3 a., 2.5 v. @ 1.75 a.—complete television hi. & lo. volt. trans. in one compact oil filled unit—will handle any television tube	12.95
TCH 2—Scope transformer 1750 v. @ 4 ma and matching fil. trans. 6.3 v. @ .8 a., 2.5 v. @ 1.75 a.	7.95
TCH 3—W. E. Scope trans. 2500 v. @ 10 mil and matching fil. trans. 6.3 v. @ 2 a. and 2.5 v. @ 3 a.—combination	9.95
HF 16—Filter choke 10 hy @ 150 ma.	1.95
LD 2—25 ma R.F. choke	.59

MISCELLANEOUS

Trimmer—single 3—30 uuf.	\$0.20
dual 5—50 uuf.	.33
13" X 17" X 3" steel chassis cadmium plated	1.95
High voltage wire—50 ft. roll	1.00
Peaking coil	.45

Write for Complete Catalog

NIAGARA RADIO SUPPLY CORP.

160 Greenwich St.

New York 6, N. Y.

to be used than a picture of the refrigerator alone. Each picture must have a caption, written on a separate piece of paper and attached to the edge of the picture in such a way that it can be removed easily without damaging either the caption or the photograph. Be sure the caption contains all essential information, including the addresses of persons shown. Before using a picture for publicity or advertising, get a signed note from everyone who appears in the picture, granting permission for such use. This will avoid serious legal embarrassment.

Address the story and/or picture to the editor who is most likely to use it—city editor, women's editor, financial editor, etc. If it is convenient, have the story delivered to the newspaper office. Otherwise mail it, being careful to protect pictures from damage.

Except in the special instances already mentioned, send the same story

to all outlets. In the case of pictures, however, when more than one pose or idea is available, send a different picture to each paper. When each paper gets a different picture, mark each "This Picture Exclusive" so the editor will know his competitors will not carry the same one.

Publicity is not a competitor to advertising—it is a supplement. Everything you send out as publicity must have real news value to the publication that receives it, or it will not be used. Make every story and every picture as close to the highest journalistic standard as possible.

The chief requirements for a highly effective publicity program are imagination, alertness, and a little effort. When well done, it can bring surprisingly great returns over a long period. Add it to your bag of merchandising tricks.

—30—

HIGH FREQUENCY ALLOCATIONS REVISED

By Kenneth R. Boord, ISW Department

ON October 2, after nearly 5 months of deliberation, the International Radio Conference of Atlantic City (New Jersey, U.S.A.) completed its work and representatives of the 78 nations taking part signed the International Radio Regulations of Atlantic City. The Atlantic City Regulations will replace the regulations adopted at the 1938 Cairo Conference, and will go into effect January 1, 1949, except for those below 27,500 kc. Allocations below 27,500 kc. will go into effect on a date to be set by the Conference for approval of new frequency list, which will meet in March of 1949; present estimate of the effective date is September 1949.

The Provision Frequency Board (PFB) will meet in Geneva, Switzerland, in January 1948, to begin preparation of the new International Frequency List. There will be a permanent International Frequency Registration Board (IFRB) in Geneva, to consider future assignments, after the new frequency list goes into effect. Headquarters of the International Telecommunications Union will be moved from Berne to Geneva.

The International Conference on High Frequency Broadcasting concluded its sessions in Atlantic City on September 27. Since this was a preliminary conference, no final documents were signed. A full-scale International Conference on High Frequency Broadcasting will convene in October 1948 in Mexico City. In March 1948, a Planning Committee of this Conference will meet in Geneva, to draft a frequency assignment plan for all high frequency broadcasting stations. The plan drafted will be presented for consideration and revision at the Mexico City Conference.

By the International Radio Regulations of Atlantic City, (1) high frequency broadcast, (2) tropical broadcast, and (3) amateur allocations were made as given in the accompanying table.

Region 1—Europe, Africa, Near East, Asiatic USSR, and Mongolian Peoples Republic.

Region 2—The Americas.

Region 3—Asia (except as noted under Region 1) and Oceania.

The allocations given in the table are worldwide except where otherwise indicated. (Asterisks indicate bands shared with other services in the same region.)

As has been indicated in the table, from 50 to 100 kilocycles will be added to each of the broadcasting bands between 6 and 17 megacycles. In the amateur allocations, major changes will be the addition of a 21-megacycle band, deduction of 50 kilocycles from the 14-megacycle band, and reduction of the width of the 7-megacycle band in Regions 1 and 3.

HIGH FREQUENCY BROADCASTING

Kc.	Region
*3900-3950	3
*3950-4000	1 and 3
5950-6200	All
*7100-7150	1 and 3
7150-7300	1 and 3
9500-9775	All
11,700-11,975	All
15,100-15,450	All
17,700-17,900	All
21,450-21,750	All
25,600-26,100	All

TROPICAL BROADCASTING (Usable in Tropical Zone Only)

Kc.	
*2300-2495	
*3200-3400	
*4750-5060 (except 4995-5005)	
AMATEUR	
Kc.	
*1600-2000	Portions may be assigned in restricted areas, if it will not interfere with Loran.
*3500-3800	All
*3800-3900	Regions 2 and 3.
*3900-4000	Region 2.
7000-7100	All
*7100-7150	Exclusive in Region 2, shared with Broadcasting in Regions 1 and 3.
7150-7300	Region 2, also shared usage in China and New Zealand.
14,000-14,350	(In USSR, 14,250-14,350 is also allocated for fixed services)
21,000-21,450	All
*26,960-27,230	Region 2, Australia, New Zealand, South Africa.
28,000-29,700	All
Mc.	
50-54	Regions 2 and 3, South Africa and Rhodesia.
144-146	All
146-148	Regions 2 and 3.
220-225	Region 2.
*420-450	All
*450-460	Regions 1 and 3.
1215-1300	All
2300-2450	All
*3300-3500	Regions 2 and 3.
*3500-3900	Region 3.
5650-5850	All
5850-5925	Region 2.
10,000-10,500	All

—30—



XMAS GREETINGS TO FRIENDS AND CUSTOMERS

SETCHELL CARLSON RADIO RECEIVER BC-1206-C

Designed to receive A-N beam signals. 24-28 vdc. Tube complement: 14A7, RF, 14H7, 14J7, 14H7, IF amplifier: 14R7, detector and 1st audio: 28D7, output, 195 to 420 KC 4" high x 4" wide 6 3/4" long. Weight 4 lbs. Priced At Only..... \$1.98



Complete set of tubes..... \$2.89

NEW, STANDARD BRAND TUBES

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
1A3	0.98	6SL7	0.89	417A	19.95
1A7GT	1.10	6SN7GT	.89	446A	2.60
1B2A	4.50	6X4	.89	703A	7.50
1G4	.98	6SR7	.89	705A	4.95
1G6	.98	6SS7	.75	713A	1.65
1H4G	.98	6U5	.98	715B	4.95
1L4	1.10	6V6GT	.99	717A	.75
1R4/1294	1.29	6Y6G	.89	723A/B	9.95
1T4	1.10	6X4	.89	812	1.95
1H5	.99	6X5	.89	801A	.75
1N5GT	1.10	7A7	.75	802/RK25	1.49
1N21B	.35	7C4	1.50	803	8.95
1LNS	1.92	7C5	.89	807	1.25
1R5	1.10	7F7	1.25	808	2.95
1S5	1.10	7L7GT	1.39	809	1.50
2A3	1.39	10Y	1.50	811	1.95
2C22	.98	12A6	.89	812	3.25
2C26A	.75	12AH7	1.10	812H	6.90
2C34	1.15	12AT6	1.10	813	8.95
2C40	2.60	12BA6	.89	814	4.49
2C44	1.75	12BE6	.89	815	2.25
2D21	.75	12C8	.89	826	1.75
2E22	1.50	12J5	.69	829B	3.95
2E23	3.25	12K5	1.25	830B	5.25
2E30	2.25	12SA7GT	.99	832A	2.25
2J32	20.00	12SG7	.89	833A	34.50
2J33	20.00	12SM7	.89	836	1.15
2J36	20.00	12SJ7	.79	837	2.50
2JB51	4.95	12SK7	.89	838	3.75
2K2	.84	12SL7	1.10	841	1.20
3A4	.98	12SL7GT	1.10	842	3.75
3B7	.98	12SQ7GT	.99	860	3.00
3B22	4.95	12SR7	.79	861	50.00
3B24	1.95	12X3	.98	866A	.75
3D6/1299	.89	14A7	1.10	872A	2.25
3E29	2.95	14B7	1.10	874	1.95
3Q4	1.10	14H7	1.25	884	.49
3Q5GT	1.10	14J7	1.25	891	.75
3S4	1.10	14R7	1.10	954	.75
4C35	7.95	15E	1.50	955	.75
5R4GY	1.15	23D4	.49	956	.75
5T4	1.25	23D6	.98	957	.75
5U4	.98	24G	1.35	958A	.75
5V4Q	.98	25A6GT	.75	959	.50
5W4	.98	25L6GT	.75	981	.50
5Y3	.60	25Z5	.75	1005	.39
5Y4Q	.59	25Z6	.98	1006	.95
5Z3	.89	28D7	.75	1613	.75
5Z4	.89	30	.78	1614	1.75
6AB7/1853	.99	32L7	1.50	1616	2.95
6AC7	.99	34	.98	1619	.98
6AG5	.99	35L6GT	.75	1624	.98
6AG7	.99	35Y4	1.10	1625	.98
6AK5	.99	35W4	.69	1851	1.25
6AL5	.99	35Z3	.99	2050	.90
6AQ5	.98	35Z5	.69	2051	.90
6AT6	.75	36	1.10	3514	3.95
6AU6	.89	37	.69	3515	.49
6B4	1.25	38	.98	3516	3.25
6B6G	.99	39/44	.99	8011	4.95
6B8	.99	41	.69	8012	4.95
6C4	.64	45	.64	8016	1.49
6C5	.51	46	.65	8020	5.95
6C6	.75	47	.90	9001	1.15
6C21	12.95	50B5	1.89	9002	.98
6D6	.75	50L6GT	.75	9003	.98
6F4	1.25	70L7	.89	9004	.98
6F5	.51	71A	.69	9005	.98
6F6	.95	75	.69	9006	.69
6F6G	.80	75T	2.95	HF100	6.95
6F7	1.25	76	.75	HY69	1.75
6F8	1.10	77	.75	HY75	1.25
6G6	1.10	78	.75	HY611	1.25
6H6	.69	79	1.10	OZ4	1.25
6J4	1.50	80	.53	RK60	1.25
6J5	.59	82	.98	RK72	8.50
6J6	.89	83	.98	T20	1.95
6J7	.89	83V	.98	TZ40	2.95
6K6	.69	84	.75	V700	6.90
6K7	.79	85	.89	VR78	.75
6K8	1.25	100T8	3.00	VR90	.75
6L6	1.25	117L7	1.89	VR105	.75
6L6G	1.20	117Z3	.89	VR150	.75
6L7	.98	117Z6GT	1.10	Z225	1.95
6N7	1.25	121A	2.65	902	2.95
6Q5	.98	205B	4.50	913	3.00
6Q5G	.98	211	1.25	2AP1	2.25
6Q7	.89	215A	3.00	3AP1	3.45
6R7	.98	217C	7.50	3BP1	2.95
6SA7	.90	250R	3.95	5BP1	3.95
6SC7	.85	274B	1.50	5BP4	8.45
6SF5	.79	304TH	9.85	5CP1	3.95
6SG7	.89	307A	6.25	5FP7	4.50
6SH7	.65	371A	3.00	7BP7	7.95
6SJ7GT	.69	371B	3.00	7BP4	14.95
6SK7	.79	394A	4.50	7EP4	18.95

No Mail Order For Less Than \$5.00

TUBE KITS

Complete set of tubes for SCR-522

\$17.95

Complete set of tubes for BC-348

\$7.95

Complete set of tubes for BC-312

\$7.95

Specify Model Numbers

Combination Offer

Both Items

\$225



HS-16 HEADSET

- 8000 ohms Hi-impedance
- Noise proof
- Most sensitive phone built
- May be used as a sound powered intercom.

Light, durable, efficient. Molded neoprene earcups shaped to completely envelop entire ear. Adjustable steel headband extends or retracts. Especially suited to hams, commercial operators, aircraft pilots, recording engineers and many others. Can be used with simplex Xtal to make complete radio receiver.

\$1.89

Original Cost \$25.00
4 foot extension cord.....\$0.49

CARBON THROAT MICROPHONE

This microphone will work into any 200 ohm impedance input circuit. Has adjustable strap to fit any neck. In operation this microphone is strapped around the throat thereby facilitating full freedom of both hands and head movement. Ideal for ultra high frequency mobile work for hams. Can also be used as a hi-grade Carbon Mike by simply drilling three holes in case. Sensitivity of this mike equal to mikes costing \$10 and \$15. Supplied with strap, 10" cord and plug. Your cost.....



49c

POWER!! POWER!!

Niagara can supply a power supply kit which will completely power the ARC 5 Transmitter used as a VFO or any one of the ARC 5 receivers. All basic components included for delivering 300 v. @ 150 milli. & 24 v. or 12 v. for the filaments—no rewiring of equipment necessary. This kit will also power the BC-348, BC-312, and the BC-1206. A good buy at \$7.50.

Master Oscillator MI-19427-B

This unit was built for R.C.A. Add a final—becomes a complete transmitter with signal shifter. 2-20 mc—also FM—only a few cycles drift from cold start. Complete with regulated power supply and heavy duty deluxe rack. Illustrated flyer giving complete description, technical summary and specifications available upon request.

COMPLETE (less tubes)..... \$225.00

MINIATURE TUBE PULLER

Niagara solves your miniature tube breakage problem with this new sensational invention. Tubes may now be easily extracted or placed into those hard-to-reach places, without the fear of breakage or burning of hands. This new invention incorporates a heat resistant rubber cap with aluminum body and handy thumb-operated plunger release. Be sure to get yours today. Money back guarantee. Only 88c

ANTENNA LEAD IN BOWLS

Made of genuine Pyrex—3" in diameter; brass rod 3/8" long—complete with hardware and waterproof rubber gaskets. Special—\$1.49

WESTINGHOUSE MN OVERCURRENT RELAY

Adjustable to .4 amp. Has automatic 110 v. AC reset—glass encased—perfect for any overload application where tube damage must be avoided.

A Steal—\$12.95

BAT HANDLE SWITCH

Mfgd. by Cutter-Hammer—10 amp. SPDT with neutral position—Perfect for rotary beam control—a positive steal at.....29c

FLEXIBLE ANTENNA MAST BASE

For Mobile Antennas, will handle up to 50 pounds.

This ends the vibration and breakage problems in mounting either receiver or transmitter antennas in moving vehicles—16" in length, 3/4" in diameter. Extra Special while they last. \$1.89

DO YOU OWN AN SCR-522?

We have a complete power supply containing all the necessary parts down to the line cord, pilot light switch & terminal blocks & delivers the following voltage—300 v. D.C. @ 250 milli. 150 v. of regulated bias and sufficient 12 v. to operate the tubes of both receiver and transmitter. Complete at the amazingly low price of.....\$14.95

Model 200-EA. 5-ELEMENT 2 METER BEAM KIT. Folded di-pole driven element. All-aluminum construction. Feed with low impedance coaxial cable. Amateur net price.....\$8.40

BC-348 Owners CONVERTER for Broadcast Band

Convert that BC-348 without any alteration in your circuit. Our special converter takes power from receiver. Just tune your set to 450 kc. and forget it. All tuning is done on a converter panel covering 550 to 1600 kc.—double conversion means High Sensitivity. Excellent Fidelity and Higher Selectivity—complete basic kit with schematic and full instructions—less chassis dial and tuning knobs. Terrific Buy at.....\$6.50

Selsyn Motors Synchronous Type

Pair in Series for 110 v. AC
Type I—5 1/4" long, 3" dia.—50 v. AC. 50 cy.—4 lbs.....\$9.95 pr.
Type II—6 1/4" long, 4 1/4" dia.—115 v. AC. 50 cy. 11 oz.....\$12.95 pr.
Type III—2 1/2" long, 2 1/2" dia.—50 v. AC. 50 cy. 11 oz.....\$6.95 pr.

SYNCHRO—DIFFERENTIAL

Model #1943—C78249-CAL-11280 Bendix Aviation 115 v.—60 cy. 6" length to end of shaft x 4 1/4" diameter.....\$9.95

XTALS

We can supply power xtals of any frequency ground to .02 tolerance in any type of holder for any surplus or standard transmitters or test equipment as well as any receiver IF frequency. Prices on request—write to our engineering department.

Sperti RF Vacuum switch used as antenna switch in the ART 13—9200 v. peak 8 amps.....\$1.95



20% Deposit on all orders unless rated. We prepay freight on \$100.00 orders in U.S.A.

NIAGARA RADIO SUPPLY CORP.

160 Greenwich St. New York City 6, N. Y.

Write for latest Bulletin 12-RN

All prices F.O.B. New York City.

EDWARDS FIDELOTUNER FOR MAXIMUM F-M LISTENING PLEASURE!



Edwards Fidelotuner, in cabinet, as shown,
ready for your F-M listening pleasure...

Size 11" long, 6" wide, 6 3/4" high

CONVERTS
ANY RADIO
RECEIVER or
SOUND
AMPLIFIER
for F-M

New and revolutionary tuning principle* makes EDWARDS FIDELOTUNER most efficient F-M CONVERTER on the market today! All the great advantages of F-M reception are yours, with this compact, efficient new tuner. Covers full F-M Band 88 to 108 Mc. Five tubes plus selenium rectifier.

\$31.50
net

SLIGHTLY HIGHER
WEST OF ROCKIES

*patent pending
DISTRIBUTORS! Some
territories still open. We
invite inquiries.
WRITE FOR LITERATURE

EDWARDS F-M RADIO CORP.
168 Washington Street
New York 6, N.Y.

FIDELOTUNER
Edwards

Ten Meter Transmitter

(Continued from page 61)

and, what will prove to be rather annoying, will cause slight capacities (such as that existing between the adjusting screwdriver and ground) to detune the final. When the transmitter has a load connected, this detuning effect will not be serious because the final tank circuit becomes broadly resonant. No effect of unbalance in the oscillator tank circuit will appear since one side of this circuit is at ground r.f. potential.

The oscillator and final amplifier tank coils are wound on 1/2" polystyrene rod, dipped in polystyrene coil dope to insure no change of inductance, and are soldered directly to the tank condensers. The tank circuits can then be installed as complete units. These circuits were designed to be rather broadly resonant so that any crystal, over a small band of frequencies, could be plugged in without the necessity for retuning. The antenna link is just three or four turns of wire around the center of the final tank coil with the ends soldered onto the antenna terminals. The number of turns should be determined experimentally since it will depend upon the type of antenna used.

There will be a certain amount of interaction between coils L_2 and L_3 due to the periodically changing magnetic fields set up by them. By placing the coils axially perpendicular to one another this effect can be minimized. The oscillator plate tank circuit is effectively across the grid of the final amplifier so that if there were sufficient coupling between coils an oscillation condition would be initiated in the amplifier and the crystal would no longer control the transmitter frequency. Such a condition could easily cause the transmitter to be operating outside of the 10 meter amateur band, which is an FCC offense for which the operator is held responsible.

The cathode coil and condenser for the tri-tet oscillator can be seen directly inside the chassis near the crystal socket in Fig. 4. If a 40-meter crystal is used the cathode capacity should be about 50 μfd . Somewhat greater driving power is available when the oscillator doubles rather than quadruples so it is desirable to use a 20-meter crystal, which will probably mean changing the cathode capacity. This can best be determined by trial. The cathode coil (L_1) consists of 40 turns of No. 26 enameled wire close-wound on 1/4" diameter polystyrene rod and dipped in polystyrene coil dope. It may be found that more power from the oscillator can be obtained by changing the number of turns on this coil. The coil should not be dipped until the proper operating condition has been found.


The meter switch has four positions which will read as follows: (1) Oscillator plate current, (2) Final amplifier

RADIO NEWS

More than
2000
up-to-the-minute
RADIO and ELECTRONIC
PARTS
in this just-off-the-press
ICA CATALOG
Standard Items
NEW ITEMS
New Prices

FREE

SEND
FOR
YOURS
TODAY

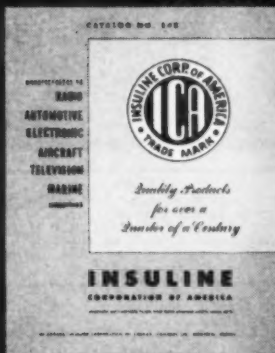

NOTE: The new sensational ICA self-service MERCHANDISER IS READY!

Write and learn how to get one FREE

insuline
CORPORATION OF AMERICA
Insuline Building - Long Island City 1, New York
More than a quarter-century of Quality production

INSTRUMENTS

AT NEW LOW PRICES!
SAVINGS UP TO 30%!

SIMPSON model 230 pocket-size volt-ohm-milliammeter. Formerly \$24.75.

REDUCED.....to **\$19.85**

SIMPSON model 240. The famed "Hammeter." With test leads. Formerly \$26.50.

REDUCED.....to **\$21.75**

APPROVED model A-200 Signal Generator. 100 Kc.-75 Mc. Formerly \$49.50.

REDUCED.....to **\$39.50**

WATERMAN model S10A - 2" oscilloscope. Regularly \$66.00. **SPECIAL PRICE \$55.00**

ELECTRONIC DESIGNS model 100 V.T.V.M. Complete with probe. Reg. \$59.85.

SPECIAL.....**\$52.50**

SUPERIOR model 1553 volt-ohm-milliammeter. Made for Signal Corps. Reg. \$24.75.

SPECIAL.....**\$20.00**

NOW IN STOCK!

SPEKTI "WALKIE-TALKIE"

2-way hand-held radio with a punch! Weighs only 3 1/2 lbs. Brand new design. 144-148 Mc. Ideal for point-to-point communication up to 12 miles, 3 miles in flat country; ham fests, field days, volunteer, emergency work, pleasure boating, flying, racing. 2 watts input to RF stage. 135 volts of B battery. Size: 10x3x2". Complete with 2 tubes, less batteries. Net. **\$34.50**

RADIO CITY model 655A insulation tester. Up to 10,000 megohms. Reg. \$94.50 **SPECIAL \$72.50**

SYLVANIA Modulation Meter X-7018. For monitoring % modulation of AM transmitters. Frequency range up to 54 Mc. Net Price **\$34.75**

SPECIAL TUBE BARGAINS

35Z5GT—Sylvania—56c.	10 for \$5.25
35L6GT—Sylvania—66c.	10 for \$6.25
43—National Union—74c.	10 for \$6.95
3J—R.C.A.—66c.	10 for \$6.25

— MAIL ORDERS FILLED PROMPTLY —

Please Send 25% Deposit with C.O.D. Orders

**SCENIC RADIO
& ELECTRONICS CO.**

53 Park Place Dept. D.C. New York 7, N.Y.

WELLS' TUBE SPECIAL OF THE YEAR!



**The 826—60 Watt UHF
Transmitting Tube..... 49c**
(LESS THAN THE PRICE OF A RECEIVING TUBE)

Accustomed as we are to excellent values in Government radio equipment, we were amazed at the remarkably low price at which we were able to get these 826's. The regular Amateur net price is \$9.25 and worth it! So you can see why we're calling this the TUBE SPECIAL OF THE YEAR. Build your new rig around the 826. Order plenty of spares as we doubt if you will be able to duplicate this price when our stock is gone.

UHF Operation up to 250 MC.

The 826 will perform beautifully in your 2 meter rig as well as on the lower frequency bands. Use it as a final amplifier, modulator, doubler, buffer, or oscillator. In fact, the 826 is good for practically any R.F. or audio application.

826 Specifications


These tubes are standard make, brand new, JAN inspected, and packed in their original cartons.

At our low price, 826's can be shipped only in boxes of 4 for \$1.96. Add 25c for each box of 4 tubes for prepaid shipment to any part of the continental U. S.

		<u>Power Output</u>	<u>Watts</u>
Max. Plate dissipation	60 watts		
Filament volts	7.5		
Filament amps.	4	Class C amp.	86
Max. plate voltage	1000	Class C plate mod.	53
Max. plate current	125 m.a.	Class B telephony	22
Approx. grid drive	6 watts	Grid modulated	25
Max. freq. full rating	250 mc.		

Tube Sockets for the 826

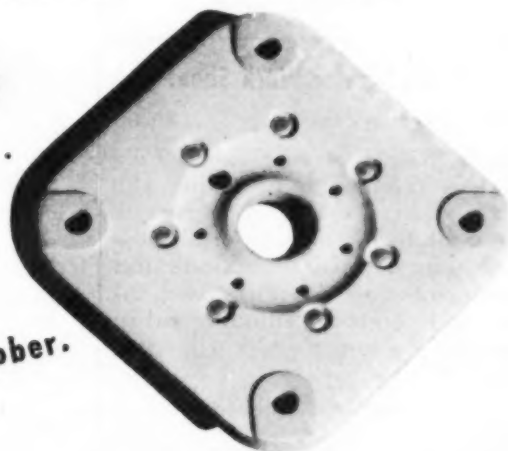Ceramic tube sockets for 826, 829B and 832 tubes . . . only 50c each.



Order directly from us or through your local Parts Jobber.

WELLS
SALES, INC.

Write for Amateur Catalog H200C
Containing Hundreds of Money Saving Values

320 N. LA SALLE ST., DEPT. R-12, CHICAGO 10, ILL.

NEW! SECOND EDITION!

"Radio Service Standard Rate Book"

Price \$1.00

Comprehensive pricing system and code of ethics covering each type of radio in six separate sections, outlining general service procedures and rates for various types of repair service. Retail prices on standard parts, tubes and crystal cartridges, plus flat rates for pick-up, delivery, estimates, and alignment. 54 pages—plastic spiral binding—opens flat. Many other features.

"Trouble Tracing in A.C.-D.C. Radio Receivers"

Price \$1.00

Down to earth servicing data, easily read and understood. All material devoted to the servicing of A.C.-D.C. sets. Test cases, parts analysis, alignment procedures, repair procedures plainly written with technical terms held to a minimum. 50 pages.

"Radio Service Record"

Pad—100 Job Tickets...\$1.25

Book of 100 repair tickets consisting of customer's receipt, repair tag, permanent record card. Bound with spiral steel binder. Opens flat, numbered in groups of 100. Space is provided for dealer's rubber stamp. Size $9\frac{1}{2}'' \times 4'' \times 1\frac{1}{4}''$.

Sample available

"Radio Service Work Sheet"


Pad—50 Sheets...\$0.60

Show your customer full details on his repair job including the little things that are never brought to his attention. 38 possible minor repair check-offs and plenty of space for parts used, labor, tubes, etc. A valuable aid in gaining customer good will. Size $8\frac{1}{2}'' \times 11'' \times 3\frac{3}{8}''$.

Sample available

At Your Radio Parts Jobber
or write

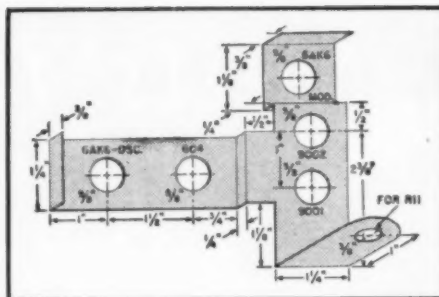OELRICH PUBLICATIONS
4135 N. Lawler Ave., Chicago 41, Ill.



HAMS! EXPERIMENTERS! Look at these EXCLUSIVE "G&G" BUYS!

ARMY AIRCRAFT RECEIVER— BC-946-B

Covers 520 Kc. to 1500 Kc. Broadcast Band. 6 Tubes: 3—12SK7, 1—12SR7, 1—12A6, 1—12K8. Designed for dynamotor operation; can be easily converted to 110 volt or 32 volt use. Two IF Stages. Three-gang tuning cond. BRAND NEW, in sealed carton, with tubes and instruction manual, less dynamotor..... **\$12.95**
Dynamotor DM-32A..... **\$1.95**

RADIO RECEIVERS

All Brand New in Original Cartons

BC-453-A 190 to 550 Kc. complete with tubes **\$7.95**
BC-454-A 3.1 to 6 Mc. complete with tubes... **5.95**
BC-455-A 6 to 9.1 Mc. complete with tubes... **5.95**

40-WATT VFO DRIVER

BC-696A 3 to 4 Mc..... **\$7.95**
BC-457A 4 to 5.3 Mc..... **5.95**
BC-458A 5.3 to 7 Mc..... **5.95**
BC-459A 7 to 9.1 Mc..... **6.95**

TERRIFIC VALUE!

24-VOLT STORAGE BATTERY, BRAND NEW!

Made by Delco. 12 cells, heavy duty, very rugged. Shipped dry, uses standard sulphuric

acid electrolyte. **VERY SPECIAL \$14.95**

6-VOLT STORAGE BATTERY. Navy Standard BRAND NEW. 15 ampere-hour rating. **\$4.95**

SETCHEL-CARLSON

BEACON RADIO RECEIVER BC-1206-C

Receives A-N beam signals, operates on 24-78 V DC. 5 Tubes: 3—14H7, 14R7, 28D7. Tunes 195 to 420 Kc. Size 4"x4"x6 1/2" wide. 4 lbs. Slightly used, A-1 condition. **\$4.95**
Each..... **\$4.95**
Same as above, BRAND NEW, in original carton..... **\$7.95**

PE-104-A VIBRATOR POWER SUPPLY

Works on 6 volt or 12 volt battery. Supplies 84 volts and 51 volts DC, also 1.4 volts "C" bias. Size 7"x4"x3 1/2". Fits BC-654 (SCR-284) exactly. Can be used to operate many types of receivers now on market. **ALL BRAND NEW, very low price \$4.95**

LM-7 Freq. Meter

195 to 20,000 Kc. modulated, complete with tubes and crystals, less power supply. Navy type, used, good condition..... **\$39.50**
Less calibration book.

BC-412 OSCILLOSCOPE (Modified to BC-612)

With very little effort you can convert this 5" C.R. Oscilloscope to first class laboratory instrument! ALL BRAND NEW, in original sealed crate. Contains 13 tubes: 6AC7, 6—6L6's, 2—6SJ7's, 879, 5T4, 6A6, 5BP4, C.R. Tube, 110 V 60 cycle. Shpg. wt. 200 lbs. Only **\$59.50**

ALLIANCE PHONO MOTOR, special **\$2.75**
ASTATIC CRYSTAL PICKUP, with L-26 crystal cartridge **\$1.79**

80 VOLT A.C.

INVERTER

Sig. Corps PE-206A. Terrific Value! 80 Volts AC Output, 800 cy. 28 V DC Input 6000 RPM. Complete with Filter. Value \$100.00. Your Cost..... **\$6.95**

BC-645 XMTR RECEIVER 15 TUBES 435 TO 500 MC

The electronic equipment that saved many lives in the war. Set can be modified to use for 2-way communication, voice or code, on following bands: ham band 420-450 mc, citizens radio 460-470 mc, fixed and mobile 450-460 mc, television experimental 470-500 mc. 15 tubes (tubes alone worth more than sale price): 4—7F7, 4—7H7, 2—7E6, 2—6F6, 2—955 and 1—WE316A. Now covers 460 to 490 mc. Brand new BC-645 with tubes, less power supply in factory carton. Shipping weight 25 lbs.

PE-101C DYNAMOTOR for above..... **\$2.95**

BRAND NEW! ULTRA HIGH FREQ. TRANSMITTER AN/APT5



1500 Mc. Transmitter, complete with following tubes: 2—6AC7, 1—6L6, 2—829, 1—931A, 1—6AG7, 1—522 Ultra High Frequency tube, complete with Ultra High Frequency Cavity, blower to cool the 522, Time Delay Relay, 2 filament transformer condensers, and many other component parts for Ultra High Frequency. Has Frequency Checker, complete Lecher Wires, with Slider, and Sensitive Bulb for checking wave length. Operates on 115 Volt AC for filaments only. No plate supply included. Tubes alone worth much more than our price for transmitter—only \$11.95! Shipping weight 118 lbs. in original wooden case with instruction book. **\$11.95**

RADAR OSCILLOSCOPE APN-4, 27 TUBES!

Very special value! Easily converted to service scope. Contains 27 tubes: 7—6H6, 1—6SJ7, 18—6SN7, 1—SCP1 C.R. Tube. Complete with cover. ALL BRAND NEW, in original sealed crate! Shipping weight 106 lbs.

RECEIVER AND POWER SUPPLY FOR APN-4. Another Smash Value! Contains 16 Tubes: 1—6SN7, 1—6SL7, 1—6H6, 4—6SK7, 1—VR105-30, 1—6SJ7, 2—2X2, 1—3U4G, 3—6B4G, 1—6SA7. All BRAND NEW and in perfect working order. In original sealed crate. Shpg. wt. 80 lbs. Special Combination Price, Scope, Receiver & Power Supply..... **\$69.00**

TRANSMITTER

BC-223-AX

Ideal for 80-meter band! 801 osc., 801 P.A., 2—46 modulators, 1—46 speech amp., 4 xtal freq. and master osc., on selector switch. 10 to 30-watt output, tone, voice or C.W. Black wrinkle case, complete with freq. chart and tubes in original cases, less xtals. BRAND NEW, exceptionally low price, shpg. wt. 80 lbs. **\$14.95**

QUANTITY PRICES

Inquiries welcomed from institutions, wholesalers, dealers, large users... Phone, write, wire for quantity prices.

Please include 25% Deposit with order—Balance C.O.D. Minimum order \$3.00.

G&G RADIO PARTS SERVICE
53 VESEY STREET - NEW YORK 7, N.Y.

BRAND NEW!

\$975

2 for \$1895



FAMOUS SCR-522 V.H.F. XMTR-RCVR 100 to 156 Mc.

10-tube xtal controlled superhet rcvr, extremely sensitive; 7-tube xmtr, temperature stabilized. Delivers 15 Watts. Used on AAF and RAF planes—now yours at tiny fraction of original cost! Easily converted to 110 volt 60 cy. operation. Complete with 17 tubes, A-1 condition only..... **\$14.25**
TWO FOR..... **\$27.90**

Dynamotor power supply for SCR-522 above, BRAND NEW..... **\$3.95**

WESTERN ELECTRIC FIELD PHONE SET EE-8

Leather case, with handset, generator, ringer, etc. Requires 2 flashlight cells. Wonderful value! Good used. Each..... **\$8.95**

TWO FOR..... **\$16.50**

HEADPHONES—All Brand New!

Individually packed, complete with phone plug. HS-33 600 ohms, in lots of 3..... **\$1.85 each**
HS-23 2000 ohms, in lots of 3..... **1.65 each**
HS-30 headphones, with earplugs, LOTS OF 12..... **44c each**

HANDSET

Cradle-type handset with butterfly switch, unbreakable black plastic, 4-ft. 3 wire cable, BRAND NEW, individually packed, each..... **\$2.75**
Same as above but slightly used, each..... **\$1.65**

HANDMIKE T-17

Shure model T-17 mike, 200-ohm carbon single button, with press-to-talk switch, 5-ft. rubber cord and plug. BRAND NEW, individually packed, in lots of 3, each..... **88c**

FREQUENCY METER CABINET

For BC-221 Series freq. meters. BRAND NEW! 3 compartments. Massively built. 14 1/2"x10 1/2"x10". Value \$20.00. Yours for only..... **\$2.95**

WILLARD 6-VOLT STORAGE BATTERY

27 amp. hrs. 3-cell battery, transparent plastic case, very specially priced..... **\$4.50**

WILLARD 2-VOLT BATTERY

20-amp. hrs. similar to above, but single cell..... **\$2.75**

ONE-QUART BOTTLE BATTERY ELECTROLYTE

Made by Willard, for above storage batteries. 1 quart sufficient for two 2-volt cells. Hermetically sealed. SPECIAL, per qt. bottle **95c**


7-PRONG 2-VOLT RADIO VIBRATOR for Portable and Farm Sets Replacement for GE LB 530..... **\$1.65**

140MMFDMIDGET TUNING CONDENSER Long shaft Lots of 3, each **44c**

118 MMFD TRANSMITTING CONDENSER Very Special Ham Value! 31 plates, Airgap .109" overall length 4 1/8", ceramic insulation, normal list price \$11.85..... each **99c**

BEEDE DC METER, new, black oak-lyte case, 3" round 0-1000 DC Ma. Special **\$1.95**

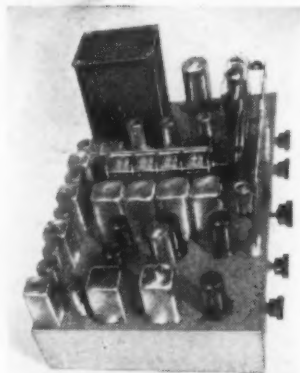
COLLINS NOW OFFERS YOU 3 TOP QUALITY PRODUCTS IN FM



FM/AM TUNER—17 tubes custom built on direct order available with extra accessories on request such as: bass and treble tone controls, 500-ohm output transformer, pre-amplifier for G.E. or Pickering pickup cartridges and many others. The only tuner which gives high fidelity A.M. as well as FM.



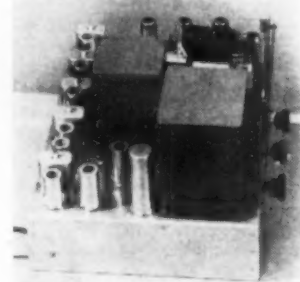FM TUNER—11 tubes same circuit and components as FM section of combination tuner above. 3 IF stages, 2 limiters, Armstrong FM. Available as chassis unit (\$87.50), with rack panel (\$94.50), and in cabinet as illustrated (\$97.50).



FM RECEIVER—A complete 15-tube FM receiver unit with high fidelity audio stages and output transformer requiring only a loud-speaker for operation. New, miniature tubes used throughout. Response of entire receiver: 2 DB variation, 35 to 20,000 cycles. Power output 8 watts. Provision for phonograph input. Price: \$186.50.

Technical data sheets on the above available. For the best in FM write:


**COLLINS AUDIO
PRODUCTS CO. INC.**

126 Park St. Westfield, N. J.
We 2-4390

fourth harmonic of the crystal. This cannot be over-emphasized because any other harmonic would cause operation of the transmitter outside of the 10 meter band. Next, the 6C4 amplifier must be neutralized. To do this, remove the plate voltage from the amplifier by unsoldering the lead to the amplifier plate current meter switch position, set the meter switch to position 2 and the multimeter to the 10 ma. scale, and rotate C_s through resonance. With the neutralizing condenser C_s all out there should be a slight variation in the amplifier grid current. By increasing the neutralizing capacity the grid current variation should become smaller as C_s goes through resonance until no grid current variation is observed. When this condition is reached, the amplifier is completely neutralized. After resoldering the plate connection, set the meter switch to position 3 with the multimeter on the 100 ma. scale and again rotate C_s through resonance. Quite a pronounced dip should be observed, going from 20 ma. when out of resonance to 2 or 3 ma. at resonance. When the antenna is clipped onto the antenna terminals the minimum plate current should rise to 15 or 18 ma. It may be necessary to vary the number of turns on the antenna link to properly load the amplifier.

With the plug for the crystal microphone inserted in the mike connector the transmitter is ready for operation. The transmitter frequency should be checked on a receiver to make certain that the transmitter is on 10 meters. If an oscilloscope is available it could be used to determine the optimum setting of the audio gain control. If one is not available, the best setting of the audio gain can be determined by listening to the transmitter on a nearby receiver. It is recommended that the top and bottom covers of the transmitter be removed when operating, to provide for proper ventilation.

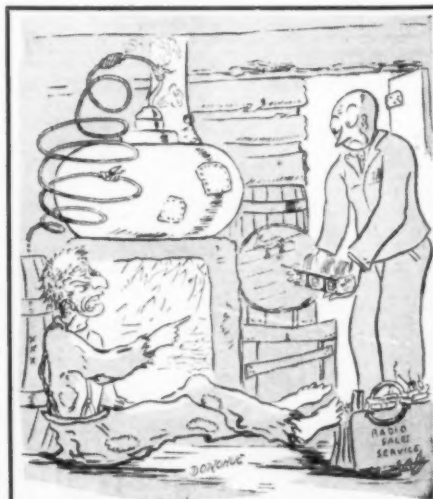Care should be taken when plate voltage is measured in position 4 of the meter switch that the multimeter is set to at least the 250 volt scale to avoid damage to the meter.



"Of course I ordered one—but that ain't no condenser!"

TECHNICAL KO's

Power Xformer Thordarson No. 92R21 780 VCT @ 200 MA, 5V @ 3A, 6.3V @ 5A.....	\$6.50
Power Xformer Stancor No. P6335 700 VCT @ 120 Ma, 5V @ 3A, 6.3V @ 5A.....	4.95
Scope Xformer Pri 115V 60 CY. Sec 3400V @ 15 MA.....	4.95
Power Supply Chassis with 600 VCT 60 Cy. Xfrm, 2-4 MFD, 500V Cond., etc.....	4.95
.01—150V—Paper.....	60 for 1.00
.02—1600V Paper.....	10 for 1.00
.1—600V Paper.....	10 for 1.00
.002, .005—600V Mica.....	.08
Chokes, Thordarson 12H-80 Ma DC-250 ohm....	1.09
Resistor Kit— $\frac{1}{2}$ & 1 W 100 assorted.....	2.00
Condenser Kit—.01—.00001—100.....	3.00
Bathtubs—3X .1, .5, .1 etc. 400V & 600V 10 for.....	.89
Rect. Selenium, G. E. 28V, 300M.....	.50

6V6 Metal.....	\$.89	6L6.....	\$.95
5Y3GT.....	.45	12K8.....	.85
12SQ7.....	.45	5BP1.....	3.35


OIL-FILLED G. E., C. D., ETC.		TRANSMITTING MICAS	
30 MFD	330 V AC \$2.35	.0015	5000 V \$.95
10	600 V .80	.002	2500 V .27
8	600 V .70	.003	2500 V .33
8	1000 V 1.75	.001	2500 V .18
4	600 V .50	.004	2500 V .36
4	1000 V 1.00	.00005	2500 V .11
2	1000 V .60	.0005	2500 V .15
.1	7500 V 3.25	.002	3000 V .66
.5	2900 V .40	.00005	5000 V .95
.12	15000 V 6.95	.00025	5000 V .95
.25	4000 V 2.75	.00072	5000 V .95
.25	6000 V 4.00	.0008	5000 V .95

\$2.00 min. order F.O.B., N.Y.C. Add postage.
50% deposit, balance C.O.D. with all orders.
Manufacturers inquiries invited.

TECHNICAL RADIO PARTS CO.

265 Greenwich St. Dept. N-7 N. Y. T., N. Y.

More Capacity PER CUBIC INCH

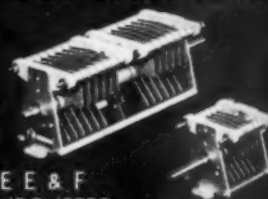

TYPE E & F
CONDENSERS

Rugged and compact, JOHNSON Type E and F condensers for medium and low power transmitters have more capacity per cubic inch and occupy less panel space for their rating than any other condenser on the market.

FEATURES

Heavy aluminum plates .032" thick, with rounded edges for maximum voltage rating. . . . Heavy aluminum tie rods $\frac{1}{4}$ " diameter for frame strength and rigidity. . . . Steatite insulation. . . . Stator mounted above to reduce capacity to ground. . . . Heavy phosphor bronze contact springs, cadmium plated. . . . Center contact on dual models. . . . Chassis or panel mounting. . . . Stainless steel shafts. . . . Front and rear shaft extensions permit ganging. In addition to mounting foot shown, removable single hole brackets are furnished so condenser may be inverted from position shown, or other components mounted above.



JOHNSON

a famous name in Radio

E. F. JOHNSON CO. WASECA, MINN.

RADIO NEWS

VALUABLE EASY-TO-BUY ELECTRONICS

Authorized WAA Electronics Distributors

EASTERN

Automatic Radio Mfg. Co., Inc.
122 Brookline Ave.
Boston, Mass.

Carr Industries, Inc.
1269 Atlantic Ave.
Brooklyn, New York, N. Y.

Tobe Deutschmann Corp.
863 Washington Street
Canton, Mass.

Electronic Corp. of America
353 West 48th Street
New York, N. Y.

Emerson Radio &
Phonograph Corp.
76 Ninth Ave.
New York, N. Y.

General Electric Co.
Bldg. 267; 1 River Road
Schenectady, N. Y.

General Electronics, Inc.
101 Hazel Street
Paterson, N. J.

Hammarlund Mfg. Co., Inc.
460 West 34th Street
New York, N. Y.

Hytron Radio & Electronics Corp.
76 LaFayette Street
Salem, Mass.

Johanns & Keegan Co., Inc.
62 Pearl St.
New York, N. Y.

Newark Electric Co., Inc.
242 West 55th St.
New York, N. Y.

Radio Parts Distributing Co.
128 West Olney Road
Norfolk, Va.

Smith-Meeker Engineering Co.
125 Barclay Street
New York, N. Y.

Standard Arcurus Corp.
99 Sussex Ave.
Newark, New Jersey

Sylvania Electric Products, Inc.
Emporium, Pa.

Technical Apparatus Co.
165 Washington St.
Boston, Mass.

Tung-Sol Lamp Works, Inc.
95 Eighth Ave.
Newark, New Jersey

W. & H. Aviation Corp.
Municipal Airport
Rochester, New York

MIDWESTERN

American Condenser Co.
4410 N. Ravenswood Ave.
Chicago, Ill.

Belmont Radio Corp.
3633 S. Racine Ave.
Chicago, Ill.

Electro-Voice, Inc.
Carroll & Cecil Streets
Buchanan, Michigan

E. F. Johnson Co.
206 Second Ave., S. W.
Waseca, Minnesota

SOUTHERN

Navigation Instrument Co., Inc.
P. O. Box 7001, Heights Station
Houston, Texas

Southern Electronic Co.
611 Baronne St.
New Orleans, La.

PACIFIC

Cole Instrument Co.
1320 S. Grand Avenue
Los Angeles, Calif.

Hoffman Radio Corp.
3761 S. Hill Street
Los Angeles, Calif.

large stocks...

wide selection...

quick delivery, too!



MANUFACTURERS

WHOLESALE — JOBBERS

See these WAA Authorized Distributors for *your* share! Their inventories include many types of unused electronic devices, tubes and equipment.

Purchasing of surplus electronic tubes, devices and equipment has been simplified to a high degree. These WAA Approved Distributors were selected on a basis of their ability to serve you intelligently and efficiently.

Write, phone or visit your nearest Approved Distributor for information concerning inventories, prices and delivery arrangements. Fill your needs—NOW—while inventories still permit large purchases and wide selection. You'll find you can "Save with Surplus."

OFFICE OF AIRCRAFT AND ELECTRONICS DISPOSAL WAR ASSETS ADMINISTRATION



Offices located at: Atlanta • Birmingham • Boston • Charlotte
Chicago • Cincinnati • Cleveland • Denver • Detroit • Grand Prairie,
Tex. • Helena • Houston • Jacksonville • Kansas City, Mo. • Little Rock
Los Angeles • Louisville • Minneapolis • Nashville • New Orleans • New
York • Omaha • Philadelphia • Portland, Ore. • Richmond • St. Louis
Salt Lake City • San Antonio • San Francisco • Seattle • Spokane • Tulsa

1377


Customer Service Centers in these and many other cities.

139

GOVERNMENT SURPLUS

We have on hand a large selection of Radio and Electronic Equipment purchased from the United States Government, and solicit your inquiry on practically any equipment or component parts used in the Army or Navy. Listed below are only a few of the many items we now have in stock.

Gasoline engine generating plant, FE-182, 0.4 kva @ 0.8 power factor 7.5 kw, 120/208-volt, three phase, 26-ampere unit. It consists of a Willys Model G-P gasoline engine and miscellaneous engine auxiliaries directly connected to an alternator with built-in exciter. Export packed with spare parts and tools. Full instructions. Weight 1035 lbs. New.....\$699.00
Scope, 2" 110 V 60 Cycle input. Control unit BC-1266. 15 tubes including 5CP1. Has all power supplies built in except for 300 Volt amp. B voltage. Can be easily converted to service 250 p.e. Shipping weight 100 lbs. Our price.....39.95

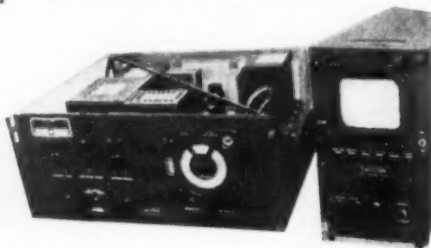

Indicator 1-22A. Has Selsyn with indicating tone. Relay. Containing tubes 1-6E5, 4-6SL7G7, 1-6V6G, 1-6SN7GT, 1-100TH. Assorted breakers, high voltage condensers, etc. Good for antenna and transmitter control and remote modulator basic kit, 110 V 60 cyc.....26.95
SAVE EIGHT DOLLARS! Purchase both of the preceding items, packed in original shipping case and crate.....58.90
Handset TS-13, 200 ohm carbon mike and 2500 ohm ear phone with butterfly switch. Has 6 ft. rubber cord with 1 PL-53, PL-68 plugs attached. Bakelite case, 11 1/2" weight.....2.95
SCR-522 Receiver Transceiver. One of the finest and most economical 2-meter rigs you can buy today. Now available for a small fraction of the original cost. Covers 100-156 MC. Ideal for aircraft communication control and taxi-cab radio. Furnished with 17 tubes.....19.95
Lineman's pole climbers with straps and pads Safety Belt with strap. State belt sizes.....4.50
Strap, adjustable from 4' to 5' with snap-on hooks. Heavy duty webbing 2" wide. For strapping console in trucks, etc.....5.75
Asbestos gloves. Suitable for welders, hot material handlers. Heavy duty. Sizes 10 & 11......29
Clipboard, 8 1/2 x 11" full length clip and cover. New.....1.25
Spark Plug Suppressors—6 for......89
Box of 50......35
SHURE Featherweight, crystal pickup New 2.25
RG8/U Coax. 52 ohm, 50' and over. Per ft. 300 ohm twin lead transmission lines. 23' or more. Per ft.....2.89
7 conductor cable, heavy duty, 24' 4 stranded. Rubber covered. Connector on both ends......025
14 conductor heavy duty. Rubber covered cable 213 stranded 50' roll. Receptacle on one end.....3.95
Terminal lug tinned copper 5/16" hole. Per 100.....3.95
Terminal lug tinned copper 24. Per 100......50
Pilot lamp socket bayonet base, 18" lead. 2 for......39
Fusetron, 10 amp plug style 2710 Bussman. 4 for......19
Kit of tubes, 25 all new. Satisfaction guaranteed or money refunded.....6.95
Resistors, 1/2 watt. Kit of 100, assorted.....1.89
45 V. BA-26 Heavy Duty "B" Batteries 8x 4 1/2 x 7 1/2". Date of mfg. May, 1945, or later. Carton of 4 for.....2.75
6 V. Lantern Battery, 25x25x37 1/2". Date of mfg. June, 1945, or later. Box of 30.....7.29
Fluorescent kitchen units. 2 tube 20 watt. Just plug in.....
Standard Typewriters. L. C. Smith, Remington Underwood. Shipped subject to your inspection. Reconditioned. Perfect shape.....59.50

SPECIAL \$25.00 OFFER

On a deposit of \$5.00 we will ship you C.O.D., Freight Collect, a large quantity of Government surplus Radio Items subject to your inspection and approval. If, after inspecting, you are not more than satisfied, return to us. Freight Collect, and all it will have cost you will be freight charges one way. You should be able to dispose of a few of the items that you may not need for the entire cost. This is the cheapest way we can sell you War Surplus Radio Material. Our warehouses are filled with thousands of choice Government Surplus Radio Items. Lots of them we do not have in sufficient quantity to advertise nationally and the cost of inventorying, itemizing, corresponding, etc., would only increase their cost; therefore, we make this offer. If you wish to mention a few items you desire, we will endeavor to include them in this assortment.

Above prices F.O.B. Baltimore
Minimum Order \$2.00

The Abell Distributing Company
5 E. Biddle St. Baltimore 2, Md.


Send for our Flyer—
Name interested in

10.7 mc. I.F. Transformers

(Continued from page 55)

ameled copper wire spaced symmetrically as shown. The individual windings are divided, that is, the primary winding has 10 closewound turns and the secondary winding has 12 closewound turns spaced 3/8" from 7 closewound turns spaced 3/8" from 5 closewound turns. The primary winding is spaced 3/8" from the secondary. This division of turns of each winding is purposely done in order to accommodate the length of travel of the "slugs," get the necessary mutual relationship between windings, and eliminate any undesirable disturbances that may result in having the "slugs" too close to one another. Both coils are wound in the same direction with the topmost ends of each winding being connected to the plate and grid terminals respectively. The coil windings are connected directly to the coil form soldering lugs; the primary terminals at the base and the secondary terminals at the top. The secondary coil connections are transferred to the base by means of rigid conductors so placed as to lie midway between the shield can and the coil form. The fixed capacitance of each winding is a 50 µfd. tubular, ceramic condenser, which is enclosed within the shield. Both tuning "slugs" are grounded by soldering a lug to the stationary nut in which the threaded member of the "slug" rotates and connecting this lug to the ground terminal. This is shown in Fig. 1 at the extreme right of the finished coil; the top right lug being the one that is soldered to the top "slug" assembly. Once the windings have been satisfactorily placed upon the form they should be given a thin coat of liquid polystyrene coil dope

Fig. 3. Mechanical details of 10.7 mc. I.F. transformer construction.

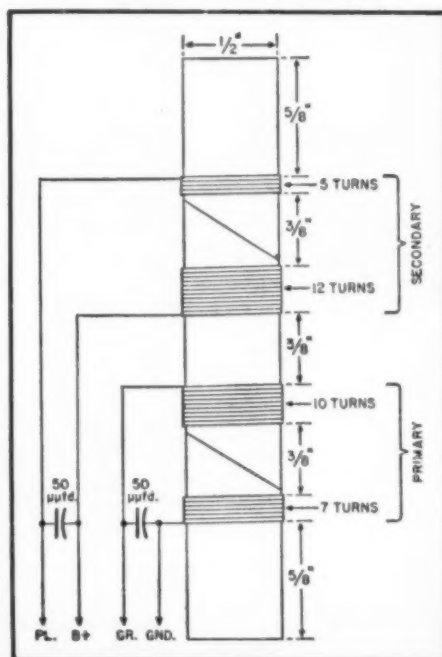


STAR TUBE- CHECKER

MODEL TE-1

\$29⁹⁵

Best
Buy
Today

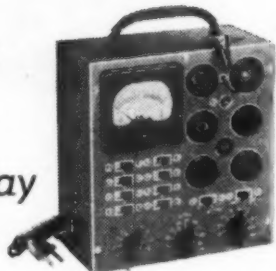

No other checker like it for size, quality, price. Individual pin switch arrangement enables calibration of any tube made... now or in the future. NON-OBSOLESCENT. Provides line check. Rugged, portable metal cabinet measures only 7" x 8" x 3 1/2" and weighs only 6 pounds net. Extremely easy to operate. Complete charts provide data for checking 570 tubes.


Order one today from your dealer,
or write to:

STAR MEASUREMENTS CO.

442 East 166th St., New York 56, N. Y.

HIGH, WIDE and ECONOMICAL*

It's the new
**UNIVERSITY
TWEETER**

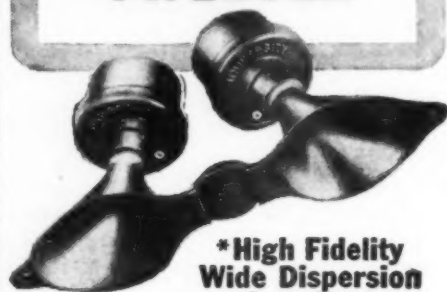

***High Fidelity
Wide Dispersion
Low Cost**

It's the new UNIVERSITY Tweeter! Extends the range of any cone speaker to 15,000 cycles. Install it in your present equipment by merely attaching two wires to the voice coil terminals of the existing speaker, without creating any electrical unbalance. Simply connect, listen and enjoy. Twin units provide 100° horizontal and 50° vertical dispersion. Three models to choose from—walnut cabinet type, and single or dual unmounted types. Priced from \$20.00. Write today for complete details to UNIVERSITY LOUDSPEAKERS, INC., 80 South Kensico Avenue, White Plains, N.Y.

University Loudspeakers



GOLD MINE for Radio Service Dealers

FM *Pilotuner*



6 1/4" high,
8 3/4" wide,
5 1/4" deep

- Sell while you service! Enjoy bigger business and bigger profits with the amazing, new FM PILOTUNER that adds FM to any radio at all — yet retails for only \$29.95.
- Every service call is now a potential PILOTUNER sale for you! Demonstrate it — leave it in the home on trial. And watch the volume and profits roll in with the miracle unit that has set a new standard of superior FM performance!
- Yes... here is your golden opportunity, Mr. Radio Service Dealer! Join the growing number of alert service dealers who are placing reorders weekly for the PILOTUNER! Stock the FM PILOTUNER now — and start reaping extra dividends.

Write today for full details on the FM PILOTUNER!

PILOT RADIO CORPORATION, 37-06 36th ST., LONG ISLAND CITY, N. Y.
Makers of PILOTONE VINYLITE RECORDS • PIONEERS IN SHORT WAVE • FM • TELEVISION

"TELEVISION SPECIALISTS"

Announcing—

NEW TELEVISION—FM SWEEP GENERATOR

THE NEW TELE-SWEEP—Available now at all leading radio distributors. The Vision TELE-SWEEP is designed specifically for visual alignment of FM and Television Receivers.

- Sweep Width 500 Kc to 10 Mc.
- Mean Frequency Range—5 to 100 Mc, 170 to 216 Mc.
- Electro-mechanical Sweep Mechanism.
- Supplied complete with instruction booklet, test leads and RF probe.

Write for circular giving complete details. Price . . . \$68.50 net.

TELEVISION PARTS

- **NEW TELEVISION COIL KIT 510**—Build a 10" or 15" television receiver. • Complete kit of permeability tuned video IF, RF, and Sound Coils for high quality television receiver designs. Contains all necessary coils for 3 stage 4mc. wide video, 2 stages sound, discriminator, peaking, oscillator, and R.F. Complete instructions included. Price at Only . . . \$9.95
- **TELEVISION COIL KIT 500 A**—including 10 matched coils for low cost 7" television receiver design described in booklet. Only . . . \$4.95
- **CR TUBE POWER SUPPLIES**—2 to 30 Kv AC and RF supplies.
- **MAGNETIC DEFLECTION** components for 7 & 10", 15 & 20" CR Tubes.
- Many other items which will interest the television experimenter.

ALSO DESIGN DATA

"Design and Construction of a Modern 5 or 7" Television Receiver"
New 2nd Edition

More Pages, Greater Detail, Drawings, Photographs, Designed for Good Performance, Simplicity, Economy. For Experimenters, Servicemen . . . any technicians that prefer to build their own.

"Design and Construction of a Visual Alignment Sweep Signal Generator"

Build a Television Sweep Generator, inexpensive, simple . . . yet professional in performance. A "must" for servicemen . . . for alignment of Television Receivers.

Included with each booklet is an 11 x 17" working diagram.

SEND FOR OUR LATEST PARTS LIST



P. O. Box No. 52, Kew Gardens 15, N. Y.

Enclosed is \$ (check or money order).

Quantity

.....Television Receiver Bklet. \$1.75 ea.

.....Sweep Signal Generator Bklet. . . \$1.75 ea.

.....Television Receiver Coil Kit 500A . . \$4.95 ea.

.....Permeability Tuned Coil Kit 510. \$9.95 ea.

.....Send circular on the Tele-Sweep.

Name

Address

City Zone

State

Order direct or through your local distributor!

142

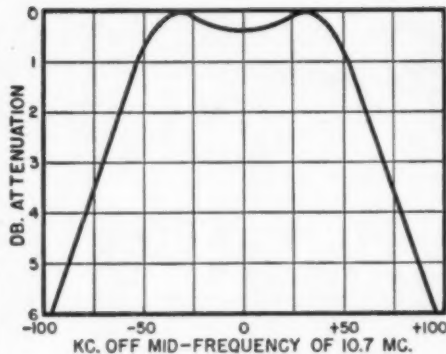


Fig. 4. Over-all characteristic curve of i.f. amplifier. Instruments used were Ferris model 16C signal generator and General Radio model 726A vacuum tube voltmeter.

before attempting to solder the ends to the lugs.

A typical two-stage 10.7 megacycle i.f. amplifier circuit, using the transformers just described, is shown in Fig. 2. The circuit is of conventional design and possesses no unusual features besides the generous use of .01 μ fd. mica condensers and 100-ohm, $\frac{1}{2}$ watt resistors in the plate and screen voltage supply circuits. The use of these components helps considerably in reducing interstage oscillations and spurious responses.

The attenuation versus frequency curve for such an amplifier is shown in Fig. 4. This is an over-all characteristic for the entire amplifier consisting of three transformers and two pentode amplifier tubes. To obtain such a characteristic, the amplifier must be aligned stage-by-stage, using the following procedure: Connect the output of a frequency-modulated signal generator (in the 10 mc. range) to L_1 and connect a vacuum tube voltmeter across the plate load resistor, R_5 . As the frequency, at constant output, of the signal generator is varied in 10 kilocycle steps on either side of the 10.7 mc. midfrequency, the readings of the vacuum tube voltmeter are noted. Adjust the inductive tuners of the transformer, L_1 , L_2 , until a symmetrical characteristic curve, similar to the one shown in Fig. 4, is obtained. Repeat the process for each additional stage by merely moving the connections of the vacuum tube voltmeter across to the plate load resistor of the next tube in the amplifier. The characteristic curve obtained by succeeding tests should not lose the general shape of the one obtained in the first stage. An increase in gain should be the only outstanding difference. Should the characteristic of two stages together not coincide with the characteristic obtained from one stage alone, it will be evidenced by a nonsymmetrical curve. Such nonsymmetry will appear such that the "peaks" will not be equally spaced or do not have the value of minimum attenuation. Correct adjustment of the tuning "slugs" will correct such misalignments. It must be borne in mind that after the first transformer has been properly aligned, just as much care must be exercised in aligning succeeding trans-



REVOLUTIONARY NEW INSTRUMENT
FOR COMPLETE RECEIVER TESTING!

Signalette

MULTI-FREQUENCY GENERATOR

Generates R.F., I.F. and AUDIO Frequencies, 2500 cycles to over 20 megacycles, using new electronic multivibrator radar principle. Completely self-contained—fits coat pocket or tool chest. Just plug into A.C. or D.C. line and check receiver sensitivity, audio gain, R.F. and I.F. alignment, auto radio aerial peaking, shielding, breaks in wires, stage by stage signal tracing, tube testing by direct comparison, etc., etc. Sturdy construction, handsome appearance! See at your dealers or write for details.

RECOGNIZED JOBBERS—WRITE FOR DETAILS OF TERRITORY OPEN!

PRICE
\$9.95

AT DEALER
OR F.O.B.
CINCINNATI

CLIPPAID INSTRUMENT


LABORATORY, INC.

Dept. N
1125 Bank Street
Cincinnati 14, Ohio

Practically Everyone in Radio

Reads RADIO NEWS

SEND IN YOUR SUBSCRIPTION TODAY

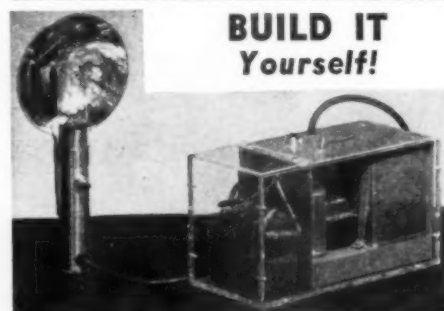

BUILD IT
Yourself!

Now! A FLASH GUN:

Good for 50,000 Shots

Build It Yourself for 1/2 REGULAR COST!

- Think of it! A regular, fine completely portable Electronic Photo Flash Gun—certified value \$250.00—now yours, in kit form, for only \$89.50! Complete Kit
- All you need to do it yourself is a pair of pliers, a screwdriver and soldering iron.
- When assembled, gun is completely portable, each bulb is good for 25,000 to 50,000 shots, reduces cost of flash pictures to fraction of a penny. Simple to put together. Chassis already stamped. All parts guaranteed. Intricate parts already pre-assembled, tested. Pre-synchronized for magnetic tripper at factory. Interchangeable with flash bulb apparatus! Each wiring diagram included. 100 Watt Seconds output. Recharged storage battery. Weight only 12 1/2 lbs. Bulbs, battery, reflector, leatherette case included. Order NOW. Send check or money order for \$89.50 for the kit or send \$10 NOW, balance C.O.D. on delivery, plus postage today! For \$15 we will contract to have it assembled for you, ready for use, ready for action. Fully guaranteed.

ELECTRONIC PRODUCTS

Dept. A 141 Broadway New York 6, N. Y.

RADIO NEWS

A Once-in-a-Lifetime Opportunity to Buy

TRANSMITTING AND SPECIAL PURPOSE

TUBES

AT PRICES THAT SEEM UNBELIEVABLE!

Check this list of Transmitting and Special Purpose Tubes! Then check our prices! Never before — and perhaps NEVER AGAIN — will you have such an opportunity to get exactly what you need at such prices. Every tube BRAND NEW — IN

ORIGINAL FACTORY PACKAGES AS PURCHASED BY THE U.S. GOVERNMENT. Manufactured by WESTINGHOUSE, WESTERN ELECTRIC, GENERAL ELECTRIC, R.C.A., EIMAC, H. & K., others equally reliable. We repeat

ALL BRAND NEW (JAN) IN ORIGINAL UNBROKEN FACTORY PACKAGES AS PURCHASED BY U.S. GOVERNMENT!

1B24	\$ 2.95 ea.
2AP1	\$ 1.95 ea.
2C22	\$.79 ea.
2J22	\$15.95 ea.
2J32	\$15.95 ea.
2J38	\$15.95 ea.
2J48	\$15.95 ea.
3CP1	\$ 1.95 ea.
4J26	\$15.95 ea.
5AP1	\$ 2.95 ea.
5D21	\$ 9.95 ea.
5JP2	\$ 3.95 ea.
5J23	\$15.95 ea.
5J29	\$15.95 ea.
6J6	\$.49 ea.

24G \$.69 ea.
Type H.F. Triode; Max. power output 90W. Max. operating freq. 300 M.C. A rare bargain.

V.T.25A (10 spec.) ...	\$.69 ea.
V.T.52 (45 spec.)	\$.69 ea.

V.T.158A	\$ 4.90 ea.
128A	\$29.95 ea.
250R	\$ 4.95 ea.
371A	\$ 1.47 ea.
388A	\$ 4.95 ea.
417A	\$ 9.80 ea.
446A	\$.74 ea.
WL530	\$39.50 ea.

WL531 \$29.95 ea.
Type Kenotron Vacuum Rectifier, Air Cooled. Inverse Peak Volts, 50,000. Peak Amps. 75.

705A	\$ 1.85 ea.
713A	\$ 3.85 ea.
714AY	\$ 9.80 ea.
715B	\$ 3.95 ea.
723A-B	\$ 2.95 ea.
724A-B	\$ 1.95 ea.
725A	\$12.50 ea.
726A	\$ 4.75 ea.

803	\$ 4.90 ea.
804	\$ 3.75 ea.

832A \$ 1.47 ea.
Type Push-Pull R.F. Beam Power Amplifier. Max. Power Output 26W.

841	\$.69 ea.
-----------	------------

WL869B \$29.95 ea.
Mercury Vapor Rectifier. Inverse Peak Volts, 20,000. Peak Amps, 10.

954	\$.49 ea.
1616	\$ 1.47 ea.
1625	\$.49 ea.
1626	\$.49 ea.
1641/RK60	\$.85 ea.
2051	\$.49 ea.
7193	\$.39 ea.
8011	\$.98 ea.
8025	\$ 2.95 ea.

HOW TO ORDER

While we have a large stock of every number listed, all tubes are offered subject to prior sale. Remit with order, or send 20% if to be shipped C.O.D. Open account to

rated firms. Min. order accepted, \$3.00.

Many other types are in stock. If what you need is not listed, write us concerning your requirements.

RADIO PARTS OUTLET INC.

Our 27th Year

Reference, Dun & Bradstreet or American National Bank, Chicago.

Dept. V-102
4305 No. Lincoln Ave.,
Chicago 18, Ill.

NOW! END WORRY...MESS... UNCERTAINTY OF STORAGE BATTERIES!

Enjoy **PERFECT** Radio Reception When Servicing
Car, Marine and Aircraft Radios!

NEW Electro
ELECTRICAL AND RADIO EQUIPMENT

Model "A" POWER SUPPLY

DC Output

Operates latest type auto
radios with solenoid tuning
and tone controls . . . also 12 volt marine and aircraft radios.

Height, 7 $\frac{3}{4}$ "
Width, 7 $\frac{3}{4}$ "

Length, 11 $\frac{1}{4}$ "
Ship. Wt. 31 lbs.

Always dependable! Reserve power
a-plenty! Big, heavy duty transformers and
chokes — large capacity condensers, for
exceptional voltage regulation — instan-
taneous power for solenoid operation. Two
separately filtered DC output sources: in
parallel supply 6V at 15 amps. series, 12V
at 7 $\frac{1}{2}$ amps. Separately 6V at 7 $\frac{1}{2}$ amps.

Compact. Sturdy. 18-gauge
steel construction. Handsome
blue Hammerloid finish.
Comes completely equipped
including 6' rubber cord and
plug. Vastly superior and
costs no more than batteries
for equal service.

Send for complete description of this up-to-the-minute power supply.


ELECTRO PRODUCTS LABORATORIES

Pioneer Manufacturers of Battery Eliminators

549 West Randolph Street

Chicago 6, Illinois

ILLINOIS CONDENSER CO. NOW HAS UMP!

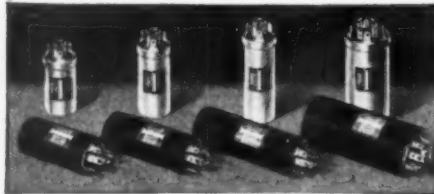

Type Ump

A popular replacement twist prong line of
Compact, Hermetically Sealed, efficient, dry
electrolytic condenser, is now a member of
the ILLINI line of highest quality capacitors.

The "Illini" UMP capacitors are now avail-
able at your local jobber. Our latest catalog,
listing complete Illinois line, will be mailed to
you upon request.



ILLINOIS CONDENSER CO.
1616 NORTH THROOP STREET • CHICAGO 22, ILL.



TELEPHONE NETWORK

for accurate
Television
Installation

**Brand New 2-way telephone set for
installation adjustments and all 2-way
communication**

Set consists of head and
chest units (2 each).
Shipped to you in orig-
inal carton.

Only \$6.95 PER SET

BUTTERFLY TUNERS

80 to 300 MC. 300 to 1000 MC.

New in cartons. **\$1.89**

PHOTO CELL AMPLIFIER

110V. 60 cy. panel type has Micro Ammeter on front
panel with tubes 6V6, 6J7, 45, 80.

VRI05 **\$11.95**

SPEAKERS

12" Dynamic 6000 Ohm speaker only **\$3.95 each**

SERVICE KIT

Kit includes assortment of:

- 1 pr. head-phones or lip
- 100 Resistors, $\frac{1}{2}$ and 1-
- watt.
- 50 Condensers, paper,
- mica, electrolytic & can.
- 10 Switches, Toggle, Gang
- & Rotary.
- 100 ft. Spaghetti, various
- sizes.
- 12 Knobs, round and bar.
- 2 lbs. Hookup wire.
- 20 Fuses.
- 6 Volume Controls.
- 10 Tube Sockets.
- 1 lb. Hardware (screws,
- nuts, lugs, etc.).
- 10 Wire Wound Resistors,
- 10 & 25 watt.
- 25 Connectors, Plugs, Ties.
- 10 Jacks (Phone) & Tip.
- 12 Padder Condensers.
- 12 Terminal Boards.
- 25 Ceramic Insulators.
- 2 Panel Lights (1 neon).
- 1 Screw Driver.
- 1 Tube Puller.
- 2 Allen Wrenches.
- 2 Panel Fuse Holders.
- 4 Binding Post Strips,
- and many other valu-
- able items.

Your Cost **\$9.95** Complete

New 1947 Circular Available. Write Today

AMERICAN SALES CO.

1811 W. 47th St.

Chicago 9, Ill.

formers. For, no matter how desir-
able a characteristic has been obtained
for all but one of the transformers,
the maladjustment allowed in this one
transformer will be definitely reflected
upon the over-all amplifier character-
istic.

After the entire amplifier has been
aligned stage-by-stage, *minor* adjust-
ments of the tuning "slugs" can be
made to improve the final character-
istic. After these final adjustments, a
drop or two of collodion or polystyrene
coil dope placed upon the threaded
"slug" mounts will preserve their set-
tings.

-50-

Automatic Key

(Continued from page 51)

matic dots and automatic dashes; the
dots are made exactly as heretofore
described; however, when the keying
arm is in the dash position it closes
the micro-switch S_1 . This switch is
mounted snugly against the keying
arm on the dash side; only a slight
movement of the lever in the dash
direction is required to close the
switch. Closing this switch places C_2 ,
in addition to C_1 , across the relay, prior
to closing the relay circuit. The total
capacity across the relay, in this posi-
tion, is three times as much as it was
on the dot side, consequently the relay
will stay in three times as long for
dashes as it will for dots. This is the
correct relationship. After S_1 is closed
the keying lever then makes connec-
tion with contact B . The relay opera-
tion, in this instance, is the same as in
the dot position except for the differ-
ence in timing.

It should be noted that the key does
not consume any power except when
actually operated. It can be left
plugged into the power outlet at all
times.

Components

The relay used in the model illus-
trated has a 5000 ohm coil with double-
pole, double-throw contacts. (Potter
& Brumfield type LM 11). However,
any double-pole, double-throw relay
with a coil of from 5000 to 10,000 ohms
and with adjustable contacts and
spring tension, can be used. The range
of the speed control R_1 is wide enough
to compensate for this change. The
physical size of the relay should be as
small as possible if a compact key is
desired.

The condensers C_1 and C_2 are in a
single can. This can has three 10 μ fd.
units in it. The can is the negative
side for both condensers. One 10 μ fd.
unit is for C_2 , the other two units are
paralleled and used for C_1 .

The rectifier is a 100 milliamperere
dry disc selenium cell rectifier. These
units are very compact and are ideally
suited for use in apparatus of this
type.


Construction

Placement of parts is not important.
The unit can be made in any size or

RADIO NEWS

Announcing THE NEW ADDITION TO OUR RADIO SCHOOL

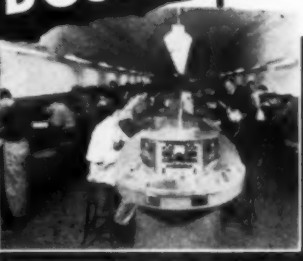**OWN YOUR OWN
RADIO SHOP
BE YOUR OWN BOSS**



**WITH A THOROUGH EDUCATION
FROM OUR COMPLETE RADIO SCHOOL**

Radio (and its allied fields—electronics, television, radar) now looms as a major industry in the United States offering a constant and ever-expanding field of wealth and opportunities. Each new development points the way toward further improvements and an increasing demand for men and women, specialized in this field.

The Radio courses offered by the Tyler Commercial College are highly specialized to enable you to enter many branches of radio, both as your vocation or your profession. The present courses listed represent a partial list of the extensive and complete training offered by the Tyler Commercial College who have had over 30 years experience in the Radio Training Field.

They invite you to examine the content of their catalogue and determine for yourself how radio training at Tyler Commercial College will enable you to find your own place in one of the many interesting and profitable jobs in the vast radio industry.

TYLER COMMERCIAL COLLEGE
115 South College Tyler, Texas

APPROVED BY
VETERANS ADMINISTRATION



GENERAL RADIO COURSE

The course in General Radio is designed to provide a broad foundation for careers in the technical radio field. Among the various job objectives are Radiotelephone Operator (broadcast, police, or airline), Radiotelegraph Operator (marine, zone police, or airline), and Radio-Electronics Technician (industry). Success in qualifying for F.C.C. Radiotelephone or Radiotelegraph License is a requirement for graduation; therefore, an extensive study of radio theory, essential radio mathematics, and laws and regulations governing radio communications is included in preparation for operator license examinations.

Average Time to Complete Course . . .
12 Months

RADIO MAINTENANCE AND REPAIR COURSE

The Radio Maintenance and Repair Course offers preparation for a career as radio receiver repairman, sound-system technician, and radio service shop operator. Accurate, up-to-the-minute knowledge of radio principles and practice is essential for future success in this important field of radio. After a thorough introduction to radio and electrical principles, emphasis is directed to modern trouble-shooting methods, notable "signal-tracing." A section on facsimile receivers, frequency-modulation (FM) receivers and television sets is provided to bring the repairman up-to-date on recent developments. A wide range of topics is covered in this course, all of which are important to the modern repairman.

Average Time to Complete Course . . .
10 Months

Send for Free Catalogue

For full details and catalogue regarding this unique school, write to The Tyler Commercial College, Radio Department, RN, 115 South College, Tyler, Texas.

Attach this to your letter head or card.

MAIL TODAY

A STATE APPROVED
INSTITUTION

In New Jersey...
...it's **VARIETY**

Sensationally New

TRANSVISION

12" TELEVISION KIT

STANDARD MODEL—

Picture size 7 1/2 square inches. 22 tubes and 12 inch picture tube. High fidelity FM sound reproduction. Advanced television circuit provides exceptionally clear pictures. **DE-LUXE MODEL**—with Super Built-in FM Radio.



12" Standard Television Kit \$289.50*
12" DeLuxe Television—FM Radio Kit..... 359.50*
7" Television Kit 159.50*
(*Complete with tubes, less cabinet)
Cabinet for 12" Television Receiver..... 44.95
REPUBLIC 7" TELEVISION KIT LESS CABINET \$165.00

Complete Line of Television Components
Dealers' Prices on Request.

NEW! PREMIER Model 570 MICROMASTER Band Spread Dial SIGNAL GENERATOR



For testing and aligning BROADCAST, SHORTWAVE, FM and TELEVISION RECEIVERS. Exclusive Band Spread Dial geared to the tuning condenser and main dial, giving a total scale length of approximately 60 inches. Three-color dial directly calibrated in Kilocycles and Megacycles. Range: 75 KC—50MC. Size: 12 1/4" x 12" x 5 1/2".

COMPLETE WITH TUBES AND **\$54.75**
CO-AXIAL CABLE. NET

ELECTRIC MOTOR KIT and BOOK

Complete, everything provided, including two batteries, quality construction, precision parts, attractively packaged. **\$3.99** Ea.

Quantity Prices on Request

Tapped Oscillator Coils for 12SA7-6SA7..... 15c each; 10 for **99c**
Dual 30 mmf. Air Trimmers, 10 for **69c**
69c; 50 mmf. Air Trimmers.... 10 for

Bargain! Guaranteed!


100 Assorted Bypass Condensers 600V
Value \$11.00. **\$6.95**
SPECIAL.....

SUPERIOR Model 670

Super-Meter

A Combination Volt - Ohm Milliammeter plus Capacity Reactance Inductance and Decibel Measurements.

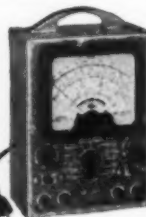Complete with test leads and instructions **\$28.40**



Full line of Weston-R.C.P.-Supreme
Superior-R.M.S.-Test Equipment

Write Dept. RN-12. 20% Deposit with order required.
Please add sufficient postage. Excess will be refunded.

Variety ELECTRIC CO., Inc.
601 Broad St., Newark 2, N. J.

shape that meets the needs of the builder. In the model illustrated, all parts were mounted on a bakelite baseboard and panel, and insulated from the metal case. It should be remembered that one side of the electric power line is connected to the ground side of the circuit. The following precautions should be taken to lessen danger of shock or short circuits. If a metal box is used, it should be insulated electrically from all parts. Another method is to connect the power cord with its ground side connected to the metal box.

The keying lever shouldn't present any problem. As previously stated, it is merely a spring arm pivoting between two contacts. The illustrations should clear up any difficulties. If a more elaborate key is desired, the movement on a standard "Bug" should be studied. It can be duplicated in the average workshop with little effort. The only advantage this movement has over the spring arm is the fact that separate tension adjustments are available for dots and dashes. With a spring arm the over-all tension can be adjusted but the tension will be the same for both dots and dashes. This, however, is not a disadvantage; it is the correct adjustment for any type of side operating key.

In conclusion, a word might be said about operating this key. When used as a straight "Bug," that is with automatic dots and manual dashes, anyone proficient in the operation of a standard mechanical "Bug" can sit down and operate this key without further ado. Mastering the automatic version is a different story. A considerable amount of practice is required. Such practice is well worthwhile, inasmuch, as it is almost impossible to distinguish the key transmission and a tape transmission when the key is correctly and skillfully operated.

-30-

FRICION DRIVEN DIALS

PLASTIC dials that are friction driven at the rim often develop flat spots or "lows" along the perimeter and, as a result, sometimes stick at these spots.

This can be corrected by applying the requisite number of layers of cement to the low spots. Do not attempt to fill up the hollow with one application of glue as it will not harden properly and will subsequently drop out of shape. Apply several thin layers, allowing each to dry, until the spot is built up. M.A.



Within the Industry

(Continued from page 30)

Radio Distributing Corporation, a wholly owned subsidiary of Zenith Radio Corporation.

Mr. Nangle joined the company in 1944 after having served with the Army-Navy Expediting Production Agency. Prior to the war, he had been in radio sales for nine years, beginning his radio career at the Boston Store in Chicago.

* * *

LEO G. SANDS, formerly a sales engineer with the Bendix Radio Division of Bendix Aviation Corporation, has been promoted to the post of District Sales Manager of mobile radio sales, with headquarters in Chicago.



In his new post, Mr. Sands will coordinate the sales activities of the Chicago branch office as related to railroad radio equipment and v.h.f. two-way radio systems for taxicabs.

Mr. Sands was formerly in charge of the company's branch office in Kansas City and joined the Bendix Radio Division in 1946 after serving as an electronics engineer with Curtiss-Wright Corporation at Bloomfield, New Jersey. From 1942 to 1944 he was foreman in radar maintenance for the War Department at Sacramento Air Depot in California.

* * *

WALTER J. NILES was recently elected to the post of president of Frederick Hart & Co., Inc., manufacturers of sound-on-film recorders and other electronic equipment.

Mr. Niles, who succeeds Charles R. D'Olive, joined Hart a year ago as vice-president and general manager. He joined the company after serving as general manager of International Business Machines Company's plant No. 2 at Poughkeepsie.

He has been closely associated with the electrical and electronics manufacturing fields throughout his business career.

* * *

WILLIAM HATTON, well-known engineer in the field of international telephone communications, has been named Director of Manufacture of the International Telephone and Telegraph Corporation and its world-wide manufacturing and sales affiliate, the International Standard Electric Corporation.



In his new post, Mr. Hatton who has been associated with I. T. & T. and its affiliated companies since 1919, assumes, in addition to his present duties as Director of Engineering, full re-

STATEMENT OF THE OWNERSHIP, MANAGEMENT, CIRCULATION, ETC., REQUIRED BY THE ACT OF CONGRESS OF AUGUST 24, 1912, AS AMENDED BY THE ACTS OF MARCH 3, 1933, AND JULY 2, 1946

Of RADIO NEWS, published Monthly at Chicago, Ill., for October 1, 1947.

STATE OF ILLINOIS } ss.
COUNTY OF COOK }

Before me, a Notary Public, in and for the State and county aforesaid, personally appeared Arthur T. Pullen, who, having been duly sworn according to law, deposes and says that he is the Business Manager of the Radio News and that the following is, to the best of his knowledge and belief, a true statement of the ownership, management (and if a daily, weekly, semiweekly or triweekly newspaper, the circulation), etc., of the aforesaid publication for the date shown in the above caption, required by the act of August 24, 1912, as amended by the acts of March 3, 1933, and July 2, 1946 (section 537, Postal Laws and Regulations), printed on the reverse of this form, to wit:

1. That the names and addresses of the publisher, editor, managing editor, and business managers are:

Publisher, William B. Ziff, 185 North Wabash Avenue, Chicago 1.

Editor, Oliver Read, 185 North Wabash Avenue, Chicago 1.

Managing editor, Wm. A. Stocklin, 185 North Wabash Avenue, Chicago 1.

Business manager, Arthur T. Pullen, 185 North Wabash Avenue, Chicago 1.

2. That the owner is: (If owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding one per cent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a firm, company, or other unincorporated concern, its name and address, as well as those of each individual member must be given. (Ziff-Davis Publishing Co.), 185 North Wabash Avenue, Chicago 1.

William B. Ziff, 185 North Wabash Avenue, Chicago 1.

B. G. Davis, 185 North Wabash Avenue, Chicago 1.

A. Ziff, 185 North Wabash Avenue, Chicago 1.

S. Davis, 185 North Wabash Avenue, Chicago 1.

3. That the known bondholders, mortgagees, and other security holders owning or holding 1 percent or more of total amount of bonds, mortgages, or other securities are: (If there are none, so state.) None.

4. That the two paragraphs next above, giving the names of the owners, stockholders, and security holders, if any, contain not only the list of stockholders and security holders as they appear upon the books of the company but also, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting, is given; also that the said two paragraphs contain statements embracing affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner; and this affiant has no reason to believe that any other person, association, or corporation has any interest direct or indirect in the said stock, bonds, or other securities than as so stated by him.

5. That the average number of copies of each issue of this publication sold or distributed, through the mails or otherwise, to paid subscribers during the twelve months preceding the date as shown above is..... (This information is required from daily, weekly, semiweekly, and triweekly newspapers only.)

Arthur T. Pullen
(Signature of business manager.)

Sworn to and subscribed before me this 25th day of September, 1947.


[SEAL] George H. Fisher.

(My commission expires December 17, 1950.)

FREE!

THE GREAT NEW COMPLETE

CONCORD Radio Catalog

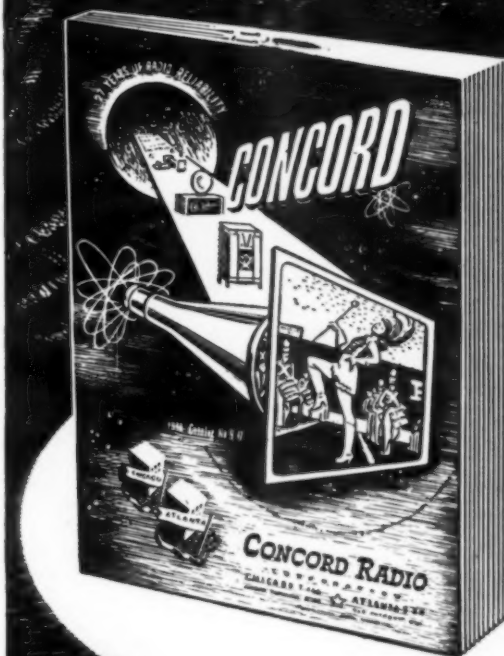

**RADIO PARTS
RADIO SETS
AMPLIFIERS
TESTERS
ELECTRONIC
EQUIPMENT
HAM GEAR**

**160
VALUE-PACKED
PAGES**

MAIL COUPON BELOW FOR FREE COPY

It's ready now—the new Concord Radio Catalog offering the greatest, latest and most complete presentation of radio, electronic and television equipment and supplies in radio history! Just off the press, this new Concord catalog is packed from cover to cover with thousands of items to fill every radio and electronic need—Radio Parts, Radio Sets, Amplifiers, Sound Systems, Test Equipment for every purpose, Record Players, Record Changers, Television Equipment, Ham Gear, Kits, Receivers, Transmitters—160 pages of everything and anything in Radio and Electronics. Complete showing of Amplifiers and Sound Equipment—including famous Concord Multi-Amp Add-A-Unit Amplifiers. Special bargain section offers hundreds of money-saving values in top quality, standard-make parts—including scores of new items from nationally-famous makers. Immediate shipment from stocks in two huge Concord warehouses centrally located in CHICAGO and ATLANTA. Mail the coupon now for your FREE copy.

WANTED—TRADE-INS ON COMMUNICATIONS EQUIPMENT—Depend on Concord for highest trade-in values on communications receivers. Write, phone or call to tell us what you have—or send it in for free appraisal.

TIME-PAYMENT PLAN—Buy your Radio and Electronic Equipment from Concord on EASY PAYMENTS—Communications Receivers, Transmitters, Radios, Radio-Phonos, Sound Equipment, Test Equipment. Write us your needs.

CONCORD

RADIO CORPORATION
LAFAYETTE RADIO CORPORATION

CHICAGO 7 ATLANTA 3
901 W. Jackson Blvd. 265 Peachtree Street

Concord Radio Corporation, Dept. E-127
901 W. Jackson Blvd., Chicago 7, Ill.
Yes, rush FREE COPY of the comprehensive new Concord Radio Catalog.

Name.....

Address.....

City..... State.....

AMATEURS—YOU CAN'T LOSE with Leo's "Globe King" 275 Watt XMTR Kit



**90-Day Money
Back Guarantee**

Use it for 90 days
— If you're not
completely satis-
fied, return it and
your money will
be refunded.

IN STOCK for FAST DELIVERY

Nothing like it on the market! Gives top performance on C.W. and four—6 through 80 meters. Contains RF Exciter section, RF Final, Speech Amplifier and Modulator, and Dual Power Supply section. When wired by our engineers all you have to do is plug it in, hook up your mike and antenna, and you're on the air. COMPARE THESE FEATURES—six meter band at no extra cost—front panel control of link to final input—voltage controlled OSC and buffer stages—provisions for ECO—new speech modulator circuit, modulate up to 350 watts—dual power supply for OSC, huf and R.F. stage—most compact Xmtr on the market, stands 28 1/4" high—available complete or in individual sections. Write for details. Available on Leo's easy Payment plan. And remember, Leo offers you MORE for your present Xmtr or receiver. In many cases it will be enough for the down payment. Complete with all parts, tubes, meters, cabinet, 1 set of coils:

Kit Form Wired As Low As
\$356.45 \$376.45 \$70 Down




**Immediate
Delivery
On This
Fine Rig**

WRL Globe Trotter XMTR Kit

Amateurs the world over are praising the performance of this high quality, low cost rig. It's a 40 watt input kit including all parts, power supply, chassis panel and streamlined cabinet. Write for export prices.

Cat. No. 70-300 less tubes..... \$69.95
Cat. No. 70-312 same as above, wired..... \$79.50
1 set of coils, meters, tubes, extra..... 17.15

NEW BC-459-A XMTR

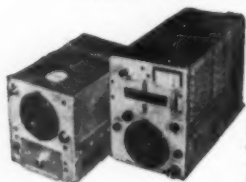

Brand New—120 Watts
Input. Tunes 7 mc to
9.1 mc 1235 osc. Two
1625's (12 volt 807's)
in final. Complete
with tubes and crystal,
each \$5.95

VFO and XMTR

Brand new CBY-52232.
Navy version of 274-N.
Tunes 2.0 to 3.0 mc. Similar
to BC-459-A. Will
tune 4.0 mc with little
change. Complete with
tubes and crystal, only
..... \$5.95

VFO and XMTR

BC-457A Xmtr. Tunes 4
to 5.3 mc. Nearly new in
good condition. Similar to
BC-459-A. Complete with
tubes and crystal.
A steal at \$3.95

VFO and XMTR

Popular 3.0 to 4.0 mc.
Navy version of 274-N.
CCT-52208 with 3500 KC
crystal and tubes. Similar
to BC-459-A. Near new.
While they last \$4.95

BC-654—Xmtr-Receiver, used. 25 watts output.
13 tubes; 3800 to 5800 KC; phone and C.W. Regular
\$351.00 value.

Fine for 80..... \$12.95

BC-654—Brand New Xmtr. Receiver; with spares; in
original crate, Export Packed..... \$22.50

PE-104—Receiver Power Pack for above..... \$4.95

New PE-103 Dynamotor

Brand new, in original Signal Corps packing; delivers
160 mils at 500 volts; operates from 0 or 12 volts
d-c; complete shock-mounted assembly includes breakers,
switches, relays, filters, and cables..... \$9.95

New 304TH Tube at..... \$4.95 each

For the fastest
service and the
best deal write
Leo, WOGFQ —
744 West Broad-
way, Connell
Bluffs, Iowa



sponsibility for the system-wide co-ordination and development of manufacturing methods.

GEORGE F. DEVINE is the new Commercial Engineer for *General Electric Company's Specialty Division* at Syracuse, New York.



Responsible for the performance, appearance specifications, and quality control of the division's products, Mr. Devine will make his headquarters at the company's Electronics Park in Syracuse.

He has been employed by *General Electric* since 1935 and prior to his most recent appointment worked on the design of the company's line of home receivers.

During the war, Mr. Devine was assigned to naval ordnance projects and in 1945 received the Naval Ordnance Development Award for his work on anti-submarine electronic devices.

P. R. MALLORY & CO., INC., of Indianapolis has appointed two new representatives to cover sales territories in the southern states.

Grady Duckett of Atlanta will serve *Mallory* distributors in North Carolina, South Carolina, Georgia, and Florida.

The Texas, Oklahoma, and Louisiana territory will be serviced by Porter Holland of Dallas, Texas.

JOSEPH A. McLAUGHLIN has been selected to fill the post of East Central Regional Manager for the *Crosley Division of Avco Manufacturing Corporation*.



For the past two years Mr. McLaughlin has served as Brooklyn Sales Manager for the *Crosley Distributing Corporation*. He is a veteran of 18 years in the radio and appliance business and during the war served with both Army and Navy as an industrial specialist in connection with radio and radar manufacture and procurement.


GENERAL ELECTRIC COMPANY is currently sponsoring a traveling FM workshop for the purpose of educating radio technicians for the better servicing of FM radio receivers.

The company has scheduled 33 meetings during the 35 state visit of the caravan during which time special technical and educational FM demonstrations are being held in metropolitan areas.

Experienced *GE* commercial and engineering personnel are accompanying the FM caravan.

WESTINGHOUSE ELECTRIC CORPORATION has announced the promotion of two key members of the Company's

Wire, Tape, & Disc RECORDERS

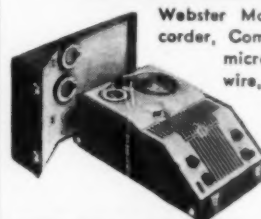

Webster Model 80 Wire Recorder, Complete with crystal microphone, 3 spools of wire, and tubes. Ready to record and play back, only

\$149⁵⁰



The Audar portable disc recorder cuts and plays records at 33 1/2 and 78 RPM with high fidelity. Complete with crystal microphone, cutter, and pickup.

FOR ONLY **\$79⁰⁰**

All prices F.O.B. Cleveland
25% deposit on C.O.D. orders

Write for Our Free Catalog
of Recorders and Accessories

ACME ELECTRONICS CO.

6523 Euclid Ave.

Cleveland 3, Ohio

SPECIAL AT WARNERS

Carbon resistor kits—over 100 assorted values and sizes (uninsulated.)..... \$1.39.

All standard brand and type receiving tubes—any quantity—50% off. Write in your needs.

AC line cords..... 17c.

Can electrolytics 25 mfd. at 300 WV 49c.

Famous-make auto radio antennas. Telescope or whip type—50% off. 66 inch \$2.48. 68 inch \$2.73. Write for others.

Punched chassis 5 tube 8 1/2x4x1 1/2.. 15c.

6 tube chassis with octal wafer sockets 11x5x2 1/4..... 25c.

Send in your name and address for our mailing list.

Bargains galore. **10% CASH REQUIRED WITH ORDER**

WARNER RADIO CO.

631 Market Street, Philadelphia 6, Pa.

Priced for Quick Disposal
CW-3 WILCOX

RADIO RECEIVERS \$12.75 EACH

Express Collect

While they last—Any Quantity

Superhet circuit 1900-16500 K.C.; 110 Volt 60 Cycle A.C.; one stage R.F.; B.F.O., noise and sensitivity controls; audio output limiter; rack mounting; complete with coil; complete set spare tubes; original crates.

Dept. M

AMERICAN MDSE. MART

411 Finance Bldg.

Philadelphia 2, Pa.

extensive education and training program.

Henry N. Muller, Jr., former manager of graduate student training, has been promoted to the post of manager of the entire educational department. His former position will be filled by Guy Kleis who previously served as supervisor of the engineering training program.

In his new position, Mr. Muller will supervise both the university relations and graduate student training programs. The graduate student training course, managed by Mr. Kleis, is a combination of work assignments and classroom study programs that bridge the gap between college and the industrial world.

—30—

International Short-Wave

(Continued from page 65)

Trinidad is your station and we want to give you a broadcasting service to which you will be proud to put the Colony's name."

The staff of *Radio Trinidad* includes a number of highly skilled men who have worked in broadcasting for many years and whose business it has been to arrange program schedules that would be satisfactory for listeners. Daily programs have been designed to include a number of old and familiar favorites to those who have been *Redifusion* subscribers in Port-of-Spain, but these are new to listeners in other parts of the islands. There are many new features for all listeners.

The station is equipped with a transmitter which delivers 2 kw. of fully-modulated power to the antenna system which, on medium-wave, is a simple "T" aerial. The transmitter design follows conventional lines, with the exception that a unique feature is the ability to switch rapidly from one frequency to an alternative frequency. The transmitter is built to work on 1295 kcs., medium-wave, and also on 6.085 and 9.625, short-wave, in the 49- and 31-meter bands, respectively.

Telephone lines provided by the Trinidad Consolidated Telephone, Ltd., connect the transmitter at Caroni to the studios in Port-of-Spain. These lines are specially treated so that the quality of the programs originating in the studios at Broadcasting House does not deteriorate because of the length of the lines over which the signals have to pass before modulating the transmitter.

An emergency generating plant of 15 kw. capacity is installed at Caroni so that the service will not be seriously interrupted in the event of a breakdown in electric supply. There is also an emergency 500-watt transmitter which can operate on all three frequencies. This transmitter is being operated normally as an alternative service on 9.625, radiating the same

TRAIN FOR GOOD PAY IN A FIELD THAT ISN'T CROWDED!

**New! Different! Easy to Understand!
Opportunities Everywhere!**

Learn ELECTRIC MOTOR REPAIR

**This Big Training Course Book Teaches You
Every Step of the Work . . . for Only
\$5 Complete**

Get where the real profits are—in Electric Motor Repair! There are more motors than any other type of electrical equipment. Good repair men are scarce and well paid. Now, for the first time in modern training history, you can learn this work at home, QUICKLY, in spare time, for only \$5. **ELECTRIC MOTOR REPAIR**, the big new 570-page training course book is especially written for beginners. No previous experience is needed. Start training now for better pay and big opportunities in a field that isn't crowded.

**Based on this big book alone, you can
TRAIN FOR PROMPT, PROFITABLE SERVICE ON
PRACTICALLY ANY MOTOR IN COMMON USE!**

**570 Pages
Over 900
Special
Illustrations
and Diagrams**



**PRACTICE
FROM IT
for 5 full
days!**

ELECTRIC MOTOR REPAIR book teaches you the work from the very beginning. Over 900 specially prepared diagrams and pictures make your training easier and **TWICE AS FAST**. You learn every step of the work from motor trouble diagnosing to repair—from simple motor cleaning and adjustments to complete rewinding. Covers every type of motor in common use and BOTH mechanical and electrical motor control systems. Quick reference guides show exactly how to handle specific jobs. When a certain type of motor comes in for repairs, just look it up. The book shows exactly what to do, exactly how to do it. Unique Duo-Spiral Binding divides book into 2 sections so that both text and related illustrations can easily be studied together.

"BORROW" IT AT OUR RISK!

ELECTRIC MOTOR REPAIR is the ideal, easy-to-understand book for beginners. Hundreds of motor repair shops use it for training new helpers and for daily use at the bench. Send coupon today! Practice from *Electric Motor Repair* for 5 full days. If not more than satisfied—if you're not fully convinced that, at last, here is the ideal training for YOU, just send the book back. Every cent of your money will be cheerfully refunded AND NO QUESTIONS ASKED!


5-DAY MONEY-BACK GUARANTEE

Dept. RN-127, Murray Hill Books, Inc.,
232 Madison Ave., New York 16, N. Y.

☐ Send me a copy of "ELECTRIC MOTOR REPAIR" for which I enclose \$5 (\$5.50 foreign); or ☐ send book C.O.D. for this amount (no foreign C.O.D.'s) and I will pay postman \$5 plus postal charges when he delivers it to me. If book is not satisfactory for any reason, I'll return it within 5 days and you guarantee to refund my \$5.


Name
Address
City & Zone State

**YOU
CANNOT
LOSE!**

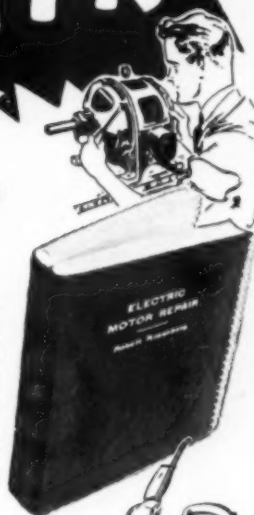

THE MASTERS CHOICE!

SUPREME MODEL 504B TUBE AND SET TESTER

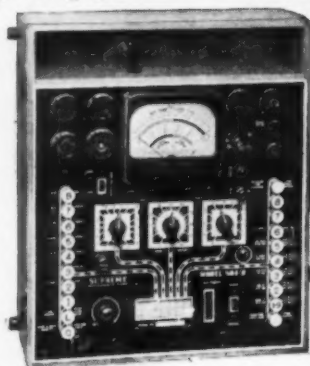

Any craftsman distinguishes himself by the appearance of his tools and equipment. For 19 years SUPREME equipment has identified thousands of successful radio service engineers. SUPREME equipped repair shops distinguish themselves for their professional appearance, dependability, and profitable operation.

One among the complete group of SUPREME radio testers is the Model 504B Tube and Set Tester.

- **METER**— large 4-inch square-face meter, 500 microamperes.
- **SPEED**— push-button operated.
- **FLEXIBLE**— simple, yet Universal Floating Filaments feature insures against obsolescence.
- **SIMPLICITY**— roll chart carries full data for tube setting. No roaming test leads when using multi-meter—only push a button.

SPECIFICATIONS

DC VOLTS — 1000 Ohms per volt: 0-5-25-100-250-500-1000-2500.
AC VOLTS — 0-5-10-50-250-1000.
OUTPUT VOLTS, 0-5-10-50-250-1000.
OHMMETER, 0-200-2000-20,000 Ohms
0-2-20 Megohms

Condenser Check:

Electrolytics checked on English reading Scale at rated voltages of 25-50-100-200-250-300-450 volts.

Battery Test:

Check dry portable "A" and "B" batteries under load.

SUPREME

SUPREME INSTRUMENTS CORP.
GREENWOOD, MISS.
U. S. A.



See the complete SUPREME line.
Write for new SUPREME catalogue
No. 447

programs simultaneously with the 1295 kcs. medium-wave transmitter. In the event of a breakdown in the main transmitter at Caroni, the emergency transmitter will be tuned to work on 1295 kcs., thus ensuring continuation of the medium-wave service while the main transmitter is being repaired.

In addition, the station is equipped with the latest type of "outside" broadcast equipment and soon will receive a central control desk together with independent balance and control units for each of the new studios now being built at Broadcasting House. These balance and control units will enable the producers of each "live" program in the studio to adjust the tonal balance of the program to their satisfaction before the signal is further amplified and routed via the control desk to the Caroni transmitter.

Other equipment includes high-efficiency recording apparatus for both 33 $\frac{1}{3}$ and 78 r.p.m., playbacks, and a portable short-wave transmitter for use in reporting topical events or in giving running commentaries on sports at places where telephone lines may not be available.

The station currently is operating on 1295 kcs., 231.65 meters, medium-wave, 2 kw., and on 9.625, 31.16 meters, short-wave, 500 watts. (Actually, the 31-m. transmitter is being logged in the United States on approximately 9.645.)

Schedule is week days at 0600-0800,* 1100-1300, and 1500-2200; Sundays at 0600-1300, 1500-2200. News is relayed from the BBC at 0600, 1100, 1500, and 2000; local news is given at 0700 and 1755, but on Sundays the latter period is devoted to "Caribbean Review," in which the Caribbean Commission gives news of its activities and lets each part of the Caribbean area know what is doing in other parts. (Incidentally, this program is to be broadcast from almost every station in the West Indies and in four different languages.) Radio Newsreel is relayed from the BBC daily at 1600, and there are children's programs daily at 1615-1700.

As a general rule, all broadcasts are in English, but there is Hindustani for Indian listeners on Sundays at 1230-1300 in "The Indian Hour," and at 1900-2000 on Saturdays. Occasionally, short paragraphs may be given in Dutch or French.

Reception reports are welcomed, and will be verified if correct. An IRC is required. QRA is Radio Trinidad, Broadcasting House, Port-of-Spain, Trinidad, B.W.I.

Trinidad has an area of 1864 square miles and its estimated (1945) population is 546,088. It is the most south-

* (Note: Unless otherwise indicated, time herein is American EST; add 5 hours for GCT. Time is indicated on the basis of a 24-hour clock, that is, 1 a.m. is 0100, 1 p.m. is 1300, etc. All times indicated as 1200 through 2400 fall in the p.m. so in order to convert the times, subtract 12 hours from figures over 12 to get the p.m. time. "News" refers to newscasts in the English language. "V" following a frequency means that the frequency varies.)

Etude's December Special

WILCOX CW3 RECEIVERS

Self contained 117 Volt 60 Cycle power supply. Sensitivity control, B.F.O., Noise control. Uses 2-6K7, 1-6K8, 2-6C8, 1-6SN7, 1-80.

Complete with full instructions for converting to a four band receiver, 2 kits of tubes, Manuals, etc. Brand New in original Crates. No coils or crystals. **\$13⁹⁵**

Worth the price for the tubes alone.

We just received some more

BC-348 RECEIVERS

Converted to 117 Volt 60 Cyc.

A.C. Ready to Plug In and Use

- Heaters are completely rewired to 6.3 volt winding on power transformer
- Separate Power Switch
- AVC, STANDBY, MVC (Combined manual control operates RF & Audio Gain)
- Crystal Filter
- Beat Freq. Osc.
- Dual Phone Jack output 4000 ohms, with 300 ohm tap available internally
- High Ratio Vernier drive with Precision stability, no Backlash
- Six Bands cover ranges from 200 to 500 Kc. and 1.5 to 18 Mc.

We have a limited quantity of these excellent receivers at this special price. Send 20% deposit on all C.O.D. orders. **\$58⁵⁰** COMPLETE With 5 Tubes

Write for Bulletin describing other Etude specials and bargains

ETUDE ELECTRONIC LABORATORIES

Main Office 1133 Findlay Ave., New York 56, N. Y.
Retail Store 366 E. 167th St., New York 56, N. Y.

ORDER NOW

100' rolls shielded grid wire. \$ 1.95

TS13 Telephone Handsets. \$ 3.95

Kilowatt, 75 Ohm Amphenol Twin Lead, per 100 ft. \$ 7.20

Complete stock of 80 and 40 meter MONITOR Crystals in holders, any frequency within 1 KC each \$ 2.80

3 Gang 410 Mmfd. Per Sect. Cond. Excellent quality \$ 2.95

National ACN Dials \$ 3.00

24G Transmitting Tube \$ 1.00

2C40 Lighthouse Tube 95c

2" PM Speaker (Bakelite Cased) Used in Walkie Talkie \$ 1.95

LM 13 Portable frequency meter boxes in canvas case (New) \$ 1.25

SIREN, Commercial type hand operated, very loud noise, gov't cost \$21.00. Spec. \$ 4.95

Send for Our Special Bulletin of Government Surplus Items

DOW RADIO

1759 E. COLORADO ST. PASADENA 4, CALIF.

Pasadena Phone—SYcamore 3-1196

Los Angeles Phone—RYan 16683

PRACTICAL TECHNICAL TRAINING FOR YOU

Specialize in Electronics, Radio, Electricity, Refrigeration, Heating and Air Conditioning, or Welding. Prepare in one year for position as Technician, or in two additional years secure your B.S. Degree in Electrical Engineering with major in Machinery or Electronics.

Write for booklet "Career Building"

MILWAUKEE SCHOOL of ENGINEERING
"A Technical Institute"

RN-1247, N. Broadway and E. State, Milwaukee, Wis.

FREE 8-PAGE FOLDER... Get this

FOR EVERY HOBBYIST, CRAFTSMAN, AND HANDY MAN AROUND THE HOME. Simple step-by-step illustrations explain how to tin soldering irons, bind and solder wire splices, unite metals, etc. No obligation, just send us your name and address today. We'll mail your soldering folder without charge.

UNGAR Electric Tools, Inc.

P.O. Box 2255-F, Terminal Annex, Los Angeles 54, Calif.



erly of the West Indies, lying off the north coast of South America. Attached to it for administrative purposes is the island of Tobago with an area of 116 square miles and an estimated population of 25,358. Capital is Port-of-Spain. Both import and export trade are heaviest with the United States. Of 1,192,844 acres on the island of Trinidad, 348,850 are cultivated. Products are mostly asphalt, oil, with derivatives therefrom. The island's great asphalt lake of 114 acres is immensely valuable and seems inexhaustible.

As we wind up our visit to *Radio Trinidad*, we extend the very best wishes to its staff with the fervent hope that VP4RD may continue to make its services of real and lasting value to the Colony.

★ ★ ★ Saigon Report

J. Pipon, head of the English Department of *Radio Saigon*, 198, Rue Chasseloup-Laubat, Saigon, French Indo-China, informs me that the station is extremely pleased with the reports received on the special broadcast of March 16, dedicated to readers of this department. Verification cards have been sent to all those who furnished correct reports, Mr. Pipon advises. However, those cards mailed around April 5 appear to have been lost in transit, and duplicate cards are now being forwarded by the station.

Here is a summary of reports received by *Radio Saigon*, as of August 9, on the March 16 special broadcast for RADIO NEWS readers:

United States—California, 7; Pennsylvania, 6; Ohio, 3; New Jersey, 2; Illinois, 1; Maine, 1; Massachusetts, 1; Connecticut, 1; West Virginia, 2. *New Zealand*—29. *Australia*—10. *Canada*—2. *India*—2. *England*—2. *Sweden*—2.

"Reports from California, Illinois, and Ohio all say that reception was excellent," Mr. Pipon comments, "while listeners in other parts of the United States write that reception was quite variable. The broadcast was picked up easily in New Zealand and in most parts of Australia. Reports from India also specified good reception, but listeners in Sweden and England could hardly hear us, apparently." (Reception in Continental Europe and the British Isles was hindered greatly by interference from *Radio Wien*, Vienna, on the 11.78 frequency.)

★ ★ ★ Spanish Project

Through the courtesy of Eddy Copper-Royer, Comptoir International de Publicité, New York and Paris, we offer readers these interesting excerpts from an interview Mr. Copper-Royer had with Senor don Valentin Ruiz Senen, Madrid, Spain, president of the Compania de Radiodifusion Intercontinental, with regard to the projected super-powered Spanish station to be located on Fernando Poo Island, off the West Coast of Africa: "As a matter of fact," said Senor

Radio Parts Company *presents*

TOP Radio and Phonograph VALUES

★ 5-TUBE AC-DC SUPERHET RADIO

With built-in loop antenna, in attractive black plastic cabinet, fine quality.


For only \$13.95 ea.

Three for \$13.50 ea.

★ THE HOLLYWOOD PORTABLE PHONOGRAPH

Three-tube amplifier, high gain crystal, fine phono motor, 4" speaker. In attractive leatherette covered carrying case.

Only \$13.95 ea.
Three for \$13.50 ea.

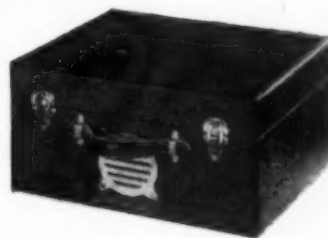

★ THE CONQUEROR RADIO PHONOGRAPH COMBINATION

5-tube AC-DC radio. High Gain Crystal Pickup. Smooth Running Phono Motor. In attractive High Finish Wood Cabinet.....\$24.95 ea.

Three for.....\$23.95 ea.


This Month's Specials



EAR PLUG TYPE HEADSET

Designed to fit in user's ears. Headband can be set to fit the head. Magnetic phones, complete with cord and holding clip.

An Exceptional Buy.
\$1.99 ea.

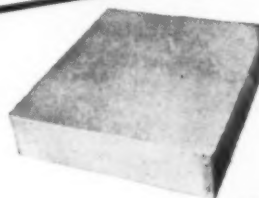

BUILDER'S CHASSIS

Just the thing for your television set, scope, or large amplifier. Measurements, 17x15x4". \$2.49 ea. Six for.....\$2.39 ea.

Send for Our Latest Catalog

Radio Parts Company

612 W. RANDOLPH - Dept. 0 - CHICAGO, ILL.

**More
MONEY
in your
POCKET**



when you carry the handy Jensen Saleskit.

Radio Servicemen who take the Jensen Phonograph Needle Saleskit on service calls say they would not be without it. This handy kit, shown above, helps demonstrate fine needles, sells on sight, adds \$\$\$s to your income.


Contains 3 Jensen Concert Needles retailing at \$1 each, and 3 Jensen Genuine Sapphire Needles

at \$2.50 each. Needles are beautifully packaged. Adds profit to every call. What's more, Jensen phonograph needles augment your work, assure full, clear tone of the instruments you repair, make all records sound better.

Generous discounts to servicemen boost your income. **WRITE TODAY** for complete details.

JENSEN INDUSTRIES, Inc., 331 SOUTH WOOD ST. • CHICAGO 12, ILL.

SENSATIONAL SELLER!

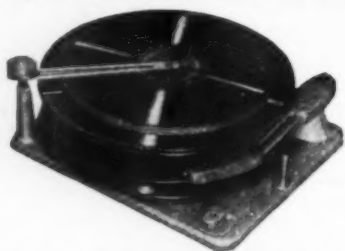

LAKE DELUXE CHANGER

Revolutionizes the Industry!
A Sensational Seller!

11 Outstanding Features:

- Positive Intermix
- Service Adjustments Eliminated
- Minimizes Record Wear
- Single Knob Control
- Plays ALL Records
- Pick-up arm may be grasped at any time and changer will not be thrown out of adjustment
- Resonance-free ball bearing tone arm
- Easily operated—any child can do it
- Completely Jam-proof
- Records Gently Lowered on Spindle—not dropped
- Automatic Shut-off on last record

Dimensions: 13 1/2" W x 12 1/4" D x 7 3/8" H.
No. 116A.....**YOUR NET \$28.73**

SERVICEMEN—RETAILERS
Write for our new, illustrated 16-page catalog NR-116. It's free. Get on our mailing list!
Write for our Special Catalog on Microphones, Amplifiers and Sound Equipment!

Lake Radio Sales Co.

615 W. Randolph Street

DEPT. A

Chicago 6, Ill.

R-L SPECIALS for IMMEDIATE delivery

RADIO PHONOGRAPH COMBINATION



Finished in beautiful brown leatherette with a 5-tube superheterodyne radio and 5" speaker.
Size of Cabinet—14" wide x 9" high x 12" deep.
SPECIALLY PRICED at..... \$23.50 net

6 FOOT AC CORDS & PLUGS

Pure rubber No. 18-2 conductor. Specially priced in lots of 24 or more..... **12 1/2¢ ea.**

WRITE FOR NEW FREE PARTS BULLETIN

**R-L
Electronic Corp.**

731 West Washington Boulevard
Dept. N Chicago 6, Illinois

Ruiz Senen, "we decided the construction of a 200,000 watt broadcasting station would be located on Fernando Poo Island, such station to give a world-wide service covering Europe, Africa, North and South America and as far as the Philippine Islands. The first steps which have been taken up to the present time is the constitution of Compania de Radiodifusion Intercontinental, formed with a capital of 24,000,000 pesetas.

"After studying the whole problem, we found that the best location for a perfect distribution of our broadcast would be around and in the equatorial area. This is one of the reasons for which Fernando Poo Island seems to be one of the best locations on which to build high sound projectors reaching all over the Atlantic area. The broadcasting power will be 200,000 watts in the antenna, but as such will not have a round radius but will be directed, the power which will reach the countries where the antenna will be beamed will be around 160 kw., based on the same principle as Americans realized for two intercontinental broadcasting stations in California, securing a complete and full service to Korea, Manchuria, and Japan.

"Distances do not exist, and when the Fernando Poo station—which will be called 'Radio Atlantica'—is on the air, radio listeners in San Sebastian, Madrid, Pamplona, London, Milan, Stuttgart will hear it as well as a local station. The wave to be used will be as short as possible, probably in between the 13- and 17-meter bands in daytime, and 25- to 30-meters at night.

"Regarding the Spanish Government's attitude toward this great enterprise," added Senor Ruiz Senen, "it could not be more enthusiastic and satisfactory. Understanding the international interest in such an enterprise and the prestige of the Spanish nation which will bring under such form, at the disposal of all the nations, a powerful instrument of exchange, the Government granted a concession to build and operate this station. The Governor General of Guinea, Senor Bonelli, took a very important part in establishing the conditions under which the station is going to be built and will have to be operated, up to the point that he authorized the construction in a large area of 60 acres located at Musola. The Compania de Radiodifusion Intercontinental, to which the concession has been granted, is looking forward and will create offices everywhere in the principal economic centers such as New York, Buenos Aires, Brussels, Lausanne, Milan, Lisbon, Paris, and so on. There will be a delay of 18 to 19 months before the first broadcast can be on the air. Programs will be recorded every day in the principal centers of the United States, in London, and so forth; then they will be shipped by air to Fernando Poo. This will give to the programs the imme-

RADIO NEWS

diate reaction of all international artistic activities and the station will in such a way broadcast the best radio production in all lines.

"To conclude," said Senor Ruiz Senen, "in this dynamic time in which the whole world tries to reorganize an international economy and a great cultural and commercial exchange between the nations, I am proud that Spain will give one of the best instruments to help a return to peace and prosperity and with its high idiom, maintain the constant and tense attention which will carry a cultural spirit which is eternal."

Mr. Copper-Royer states that this is the first time since 1936 that American equipment is going to Spain. An order has been placed with a well-known concern in the United States for two 5 kw. transmitters—one of which will be delivered to Madrid, the second to Fernando Poo. These transmitters will be used by Compania de Radiodifusion Intercontinental to establish a direct circuit between the head office in Madrid and the station in Musola. It is probable that the 200 kw. transmitter will also be ordered from the United States, especially since this is the only country where such powerful equipment has already been constructed, he adds.

Verification Data

HHCN sent letter-*verie*, signed by Carl Etienne, 55 Ave. Christophe, Port-au-Prince, Haiti, it was stated that the station is authorized for 5 kw. but is using only 100 watts at present; may change frequency soon to escape bad aircraft QRM, and will notify verieholders of such change. (Arthur)

LRA verified for Paul Kary, Pennsylvania, a special transmission of Argentine folklore music, heard July 19, and dedicated to delegates of the Telecommunications Conference in Atlantic City, New Jersey, U.S.A.; transmission was over commercial transmitters LQD, 19.400, and on 18.150; it was stated LRA is extremely interested in receiving reports on programs and signals; regular schedules are given as LRA-5, 17.720, 1500-1530 on Fridays only; LRA-1, 9.690, relaying medium-wave LRA at 0800-2200; the program of LRA-5 on Fridays is a special one from the Ministerio de Relaciones Exteriores y Culto, directed to all American countries. QRA is LRA, Radio del Estado, Palacio de C. y Telecomunicaciones, Del Jefe de la Division de Radiodifusion, Buenos Aires, Argentina.

Radio Club Argentino, Av. Alvear 2750, Buenos Aires, Argentina, desires reports on the signals of LRA-1, 9.690, and says each correct report will be verified by QSL card. (Courtesy ARRL)

The Navy Department in Washington is sending out verifications on reports of reception last winter of NAVE, aboard the *Mount Olympus*, flagship of the Antarctic Expedition.

HIIR, La Voz de Fundacion, San
December, 1947


METROPOLITAN

is the largest specialized testing instrument house in the country. We carry approximately 5,000 testing instruments in stock of all nationally advertised brands. The items listed below are only a few selected models offered at specially attractive prices in order to meet the present day demand for good merchandise, at fair prices. All units factory guaranteed for one year and available for immediate delivery from stock.

The New
Model B-45

Battery
Operated

SIGNAL GENERATOR

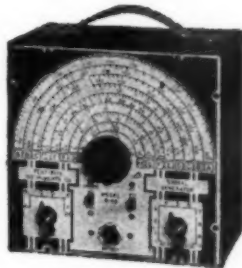

for servicing AM, FM and Television Receivers. R.F. frequencies from 150 Kilocycles to 50 Megacycles (150 Kc. to 12.5 Mc. on Fundamentals and from 11 Mc. to 50 Mc. on Harmonics). Complete with shielded test lead, self-contained batteries and instructions.

Net.....\$27.75

The Model 689-IF WESTON OHMMETER



A convenient, pocket size ohmmeter for checking circuits by the resistance and continuity method. The energy for the resistance reading is supplied by a self-contained 1.5 volt No. 2 standard large flashlight cell. Built to meet U. S. Army Requirements for Accuracy and Durability!

This Ohmmeter also has a double range 0-10 and 0-1000 ohms for the accurate measurement of low resistance values.

Model 689-IF comes complete with operating instruction, test leads and LEATHER CARRYING CASE.

List price \$25.50
Our Price.....\$14.85




The New Model 111 AC-DC QUALITY MULTITESTER

A new pocket-size volt-ohm-milliammeter with features never before available in an instrument of this size and price.

D.C. Voltmeter: 0-5-50-250-500-2500 volts, A.C. Voltmeter: 0-10-100-500-1000 volts. Output Voltmeter: 0-10-100-500-1000 volts. D.C. Milliammeter: 0-1-10-100 milliamperes. D.C. Am-

peres: 0-1-10 amperes. Ohmmeter: 0-500-100,000 ohms; 0-1 megohm. Decibel Meter: -8 to +55 db. The scale is calibrated for line of 500 ohms impedance. For other impedances correction charts are supplied. Model 111P, in portable case (not illustrated) including testing leads and complete instructions.....\$19.85

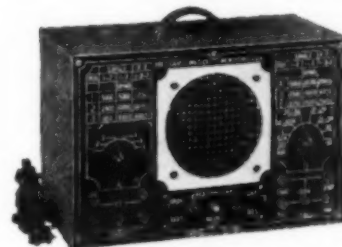Model 111A, open-face, as shown, complete with instructions.....\$16.85



The New Universal

COMBINATION TEST SPEAKER

A new combination test speaker plus resistor substitutor; plus condenser substitutor; plus resistor tester; plus condenser tester; plus output meter.

A MUST FOR EVERY RADIO SERVICE MAN AND ENGINEER

No need to carry the speaker to your shop in servicing any radio from the small mid set to the most elaborate console. Any output tube or tubes can be matched simply by rotating input switch to listed tube and rotate field switch for proper impedance and proceed with testing. External voice coil connection permits testing of set-speaker to determine if output transformer is open or shorted. Field impedance: 500, 1000, 1500 and 2500 ohms at 175 Ma.

This unit comes housed in a rugged, battleship gray, crackle-finished steel cabinet, with operating instructions, size 7"x11"x5", operates on 110 V., AC, 60 cyc. Complete.....Net price \$27.50

Model 570 PREMIER
Band Spread Dial

SIGNAL GENERATOR

AIR TRIMMERS ON ALL BANDS
TRIPLE COPPER PLATED SHIELDING
EFFECTIVE LINE FILTER
Pure 400 cycle modulation
(less than 5% distortion)



Range 75KC-50MC on fundamental, and 50-150MC on 3rd harmonic, useful for aligning FM and Television Receivers.

Accuracy better than 1%. A.C.—115 volts, 50-60 cycles.

Overall size—12"x12 1/2"x5 1/2".
Complete with co-axial cable and operating instructions.

\$54.75
NET

SPECIAL VALUE!

National Union 5-BPI Picture and Oscilloscope Tube—Brand New, Guaranteed—Reg. list price \$375
\$24.75. Our SPECIAL Price.

ORDERS FILLED SAME DAY RECEIVED!

TERMS: 20% Deposit, Balance C.O.D. Or Full Payment with Order.

SEND FOR FREE CATALOG

Write for Information about New Metropolitan Time Payment Plan


We repair all types of Testing Equipment.

Inquire about amazingly high allowance for your used Test Equipment.

Metropolitan ELECTRONIC & INSTRUMENT CO.

Dept. RN-12, 42 WARREN STREET, NEW YORK 7, N. Y., U. S. A.

RADIOMEN!
GET THIS
Brand New! Valuable Book
OF "150 NEW
RADIO DIAGRAMS
EXPLAINED"
FREE



10 to 1 Satisfaction GUARANTEE

"I personally guarantee that at the end of 1 year from date of receipt, my Applied Practical Radio set will have earned for you at least 10 times its cost, or you may return it and I'll return every cent you paid."

B. W. Cooke, Pres.



Here's a sensational "get acquainted" offer! This big, new book, "150 New Radio Diagrams Explained" is yours, absolutely FREE! It contains circuits and data on the latest Radio and Television sets. Easy-to-read, 8 1/2 x 11" size, with full instructions on how to read and use diagrams. Belongs in every radioman's kit.

HOW TO GET YOUR FREE BOOK


You get this book Free just for looking over—without cost or obligation—the sensational new 3-volume Coyne set "APPLIED PRACTICAL RADIO." It's just off the press. Here's everything you want to know about radio, from basic principles to up-to-the-minute Television and FM! P.A. short-

wave, aviation-auto radio, multibands, tele-transmission, etc., all clearly explained. Shows how to construct, install, service all types of apparatus. Step-by-step photos break equipment down before your eyes! Newest testing methods. Hundreds of subjects, almost 1000 pages, 600 illustrations, diagrams. Written for home training and field reference—so complete, so up-to-date and practical that every man interested in radio should see it.

SEND NO MONEY You can see how much this set can mean to your future, without cost or obligation. I'll send "APPLIED PRACTICAL RADIO" postpaid, for you to look over for 7 days FREE—and with it, the Radio and Television Diagrams book as an outright Gift! This book is yours to keep free whether or not you decide to keep the 3-VOLUME SET!

Coupon is Not an Order—Just a Request to See the Set Free

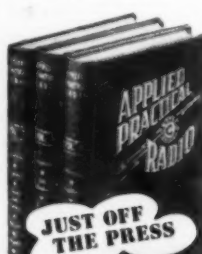YOU ARE NOT BUYING THE 3-VOLUME SET WHEN YOU SEND THIS COUPON. You are merely asking to see the books free for 7 days. This coupon becomes an order only if you decide to keep the set after 7 days' Free Examination. Free Book Offer is limited—so mail coupon today.



FREE BOOK COUPON

B. W. Cooke, Pres., Coyne Electrical & Radio School
 500 S. Paulina St., Dept. 97-T3, Chicago 12, Illinois
 Send me the NEW 3-Volume Coyne Set "APPLIED PRACTICAL RADIO." Also send me the book "150 New Radio Diagrams Explained" which I am to keep FREE whether or not I keep the 3-book set. I'll either return the 3-book set in 7 days and owe nothing, or pay \$3 within 7 days and \$3 a month until \$10.75 is paid—or I'll send the cash price of \$9.75. You also include FREE one year of Consultation Service.

NAME AGE

ADDRESS

TOWN ZONE STATE

() Check here if you want to pay postman cash price of \$9.75 (you save \$1.00) on delivery. Same Money-Back Guarantee after 7 days' trial.

Cristobal, Dominican Republic, verified by nice yellow card with photo of studio and transmitter building on one side; QRA is Broadcasting HIIR, La Voz de Fundacion, % Luis F. Alberti, Director, San Cristobal, Ciudad Benemerita, Cuna de Trujillo, Republica Dominicana. GBSS, *Queen Elizabeth*, verified on prepared form and with letter; not permitted to state type of transmitter used, but gave power as 400 watts on phone; antenna is single-wire vertical; uses 17.640 when working WOO, and 17.600 when working GBC, Rugby; also uses 13.210, 8.830, and 4.412.15, latter only when within a few hundred miles of port; wants reports on all these frequencies. It is suggested that DX-ers follow shipping news in metropolitan papers (such as the *New York Times*), and send reports to New York when ship docks; QRA is HMS *Queen Elizabeth*, Cunard White Star Liner, Radio Station GBSS (aboard), % E. D. Walker, Technical Operator, West 50th Street Pier, New York, New York, U.S.A. PUH, Rio de Janeiro, Brazil, 20.750, verified; QRA is "Radiobras," Companhia Radiotelegrafica Brasileira, Caixa Postal 500, Rio de Janeiro, Brazil; verification was on prepared form. QRA of Sendergruppe Rot-Weiss-Rot is ISB-Radio-Sektion, Seidengasse 11, Wien VII, Austria. (Kary)

Club Notes

New Zealand—Harold J. Barr, Hon. National Secretary, New Zealand DX Club, informs us that the official bul-

letin of that group, "The N.Z. DX-Tra," is now being published in Auckland in conjunction with the Headquarters of the Club. Material for the bulletin should be addressed to "The N.Z. DX-Tra Committee," 9, Westmere Cresc., Westmere, Auckland, W. 2, New Zealand. Any inquiries regarding membership and so on, however, should still be addressed to Mr. Barr at 10, Koraha Street, Remuera, Auckland, S.E. 2, New Zealand.

United States—A complete worldwide SW log has just been issued by the Newark News Radio Club, 215 Market St., Newark 1, New Jersey. It is one of the most thorough compilations I have seen; subscribers receive it for \$1. Compiled by James J. "Jimmy" Hart and M. F. "Matty" Williams, short-wave editors of NNRC, the log contains three sections—stations listed by frequency; stations listed by countries and cities; and last minute tips. Appended is a list of low-frequency police stations, compiled by Robert Knox.

This Month's Schedules

Albania—ZAA, 7.852, Tirana, has news at 1515. (Miers)

Algiers—Radio *Algerie*, 11.835, is heard in French to close at 1700, fair to good signal. (Pelland)

Andorra—Radio *Andorra*, 5.980, is heard to 1800 or later. (Pelland) Good level in Pennsylvania; announces "Aqui Radio Andorra" in Spanish and "Ici Radio Andorra" in French (Kary) At 1600 now gives a program of re-

Counting the photons, or light particles, arriving from a star is the unusual occupation in which I. M. Levitt (left) and William Blitzstein were engaged when this photograph was made at the Flower Observatory in Highland Park, near Philadelphia. A photometer of their own design, which is the first astronomical device to count such photons, is used by the two scientists in their experiments. Levitt is shown adjusting the photomultiplier tube attached to the eyepiece of the telescope, while Blitzstein is seen tabulating results obtained with two RCA Electronic Time Interval Counters, used to count electron impulses generated by the phototube.




U. S. GOVERNMENT SURPLUS SURPLUS SPECIALS

SIGNAL GENERATORS

15 to 25 mc.
and
190 to 230 mc.

SPECIAL
\$22⁹⁵

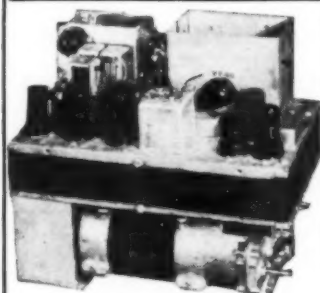

I.F.F. RECEIVER & TRANSMITTER

Complete with 14 tubes

EACH \$5⁹⁵

C6J TUBES

Gas Filled	6.4
Maximum Anode Amperes	350
Nominal D.C. Output Volts	18
Filament:	2.5
Amps	40 Secs.
Volts	1250
Heating Time	77
Peak Inverse Volts	— 2
Peak Anode Current	— 2
Critical Grid Voltage	— 2
Cond. Mercury Temp. Limits	40° to 65° C.
Height	9 1/8"
Width	2 1/16"
Base: 4 Pin #412	

PRICE EACH \$3.95

OUTPUT TRANSFORMERS

Type No. 900885
CRV—30528
PRI—5000 Ohms
Sec. #1 500 Ohms Modulator
Sec. #2 600 Ohms Sidetone

RESISTANCE

PRI—120 Ohms
Sec. #1—20 Ohms
Sec. #2—5 Ohms

NEW, EACH 49^c

VIBRO-PAC Model 125 AX

12 or 24 volts new,
complete with vi-
brators and tubes.
500 volts output at
160 milliamperes.
New

\$4⁹⁵

BEACON RECEIVERS

BC-1206-C

NEW EACH **\$4⁹⁵**

USED EACH **\$2⁹⁵**

GOOD CONDITION

Dynamotors 49^c
12 OR 24 VOLT EACH

B.D. 77 DYNAMOTORS

12 V. input; 1000 V.
output, 6 V. input, 450
V. output, 350 MA.

\$4⁹⁵
EACH

INVERTERS

27 V. input, 115 V. 400 cycle
output at approximately 1500
watts.

NEW, EACH \$7⁹⁵

3-TUBE AMPLIFIER

Using 2—1N5 and
1—1G6.
Complete with tubes....

\$2⁹⁵

FIELD TELEPHONES

EE8 PAIR **\$10⁰⁰**

GRAB BOX

Approximately 10
lbs. of miscellaneous
radio parts. All us-
able—All new.
BOX EACH **\$1⁰⁰**

All Orders F.O.B. DETROIT, Shipped RAILWAY EXPRESS

No order under \$3.00—Please send check or money order.
Orders shipped C.O.D. subject to 25% advance deposit.

RADIO CENTER


2530 E. DAVISON AVE. DETROIT 12, MICH.

AMPHENOL


ROTARY
BEAM

SIGNAL SQUIRTER

moves the world
into your back yard

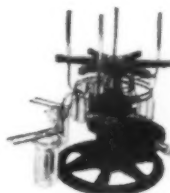

Deluxe Rotator

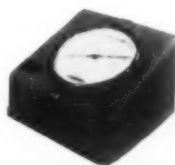

Direction Indicator

The Signal Squirrel gives your rig the power to punch through to the four corners of the globe. Offering full performance on ten and twenty meters, for transmission and reception, it is comprised of two three-element arrays each coupled to the line with a separate inductive coupling. Match between antenna and line is simplified. Assembly and installation are easily accomplished. No tedious adjustments are required.

Ready-to-assemble kit includes: Rotator with mounted Inductostub assembly, direction indicator, center section, elements and insulators with all hardware ready for installation.

See your jobber, or write direct
for complete data.

Manufactured under Mims patent 2,292,791.

You Get These Advantages with Signal Squirrel:

- Unlimited rotation either direction
- Inductostub matched coupling
- Two band operation
- Deluxe rotator
- Positive position lock
- High forward directivity
- High front-to-back ratio
- Rigid low-loss elements
- Easily tuned
- Durable and efficient
- Non-resonant transmission line

To assure top antenna performance, thousands of amateurs look to Amphenol for: Twin-lead transmission line, line spreaders, Silicone compound, stand-off and screw eye insulator, plastic window pane, as well as microphone connectors, sockets and other top quality radio components.



AMERICAN PHENOLIC CORPORATION

1830 S. 54th AVE., CHICAGO 50, ILLINOIS

COAXIAL CABLES AND CONNECTORS • INDUSTRIAL CONNECTORS, FITTINGS AND CONDUIT • ANTENNAS • RADIO COMPONENTS • PLASTICS FOR ELECTRONICS

PEAK XMAS SPECIALS

SPECIALS OF THE MONTH

Cornell-Dubilier .002 to-loss Meca—3500 \$2.00
WV—7500 VT—Xtra Bargain, 69c ea. 3 for

Industrial—3 Mfd.—3000 v. oil capacitor \$3.95
with Porcelain Insulators

G.E. 2" SCOPE


This compact unit only 4 1/2" x 2 1/2" x 6 1/2" ideal for modulation indicator etc., has focus intensity and other brilliance controls—Uses 2AP1, CRT and 9006 rectifier. We supply complete instructions with each scope. Rectifier built in—need only transformer delivering 350-400 v. 6.3, 1 amp for operation. Very simple changes. Comes \$4.95 with 9006 but less 2AP1..... only \$2.49



2AP1

S.C. TEST SET (I-114)

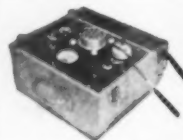In portable wood case 6"x6"x10", including cover not shown, with Weston 0-150 v. AC. Meter has 2 switching ckts and comes complete with test and line cables. A Buy At Only \$3.95 Same with other make meter..... \$3.25



HERE'S A CUTIE

This G.E. tiny but accurate meter is only 1 1/2" sq. Basic 0-1 ma. Scales for "S" or field strength meter, etc. Only \$3.95



Spert RF Vacuum switch used as antenna switch in the ART 13—9200 v. peak 8 amps..... \$1.95

2 KW Antenna Changeover relay DPDT isolantite insulation—110-220 v. 60 cy. input—rigid construction..... \$7.95

RCA POWER TRANSFORMER

770 v. CT 100 ma. 6.3 v. 2a., 5 v. 3 A.—4 1/2" x 4" x 3 1/2"..... \$3.75

MISCELLANEOUS SPECIALS

2-11 mfd Butterfly Cond..... \$0.59
CD 16 mfd 450 v..... .59
Kit 50 mica Cond..... 2.39
Kit of 5 relays..... .99
Aerovox 1000 mfd 25 v..... .79
5 A. 110 v. AC MAG CKT BRKR..... .89
1.5 hy 250 ma Choke..... .79
HS30 HI imp. phones..... .88

1% PRECISION RESISTORS, IRC, SHALLCROSS, ETC.

2000 ohm	\$3.9 ea.	50,000 ohm	\$4.9 ea.
2500 ohm	39 ea.	95,000 ohm	49 ea.
5000 ohm	39 ea.	100,000 ohm	69 ea.
8500 ohm	39 ea.	750,000 ohm	89 ea.
10000 ohm	39 ea.	1 meg.	95 ea.

OIL CONDENSERS, G.E., C.D., AEROVOX, etc.
4 mfd.—600 v. DC..... \$0.59
10 mfd.—600 v. DC..... .95
16 mfd.—600 v. DC..... 1.35
2 mfd.—1000 v. DC..... .79
4 mfd.—1000 v. DC..... .95
2 mfd.—1500 v. DC..... 1.25

I. R. C. WIRE WOUND RESISTORS

10 Watt		20 Watt	
25 ohm		50 ohm	
40 ohm		100 ohm	
84 ohm	15c each	150 ohm	20c each
400 ohm		300 ohm	
470 ohm		1000 ohm	
1325 ohm		2700 ohm	6 for \$1.00
1900 ohm		5000 ohm	
2000 ohm	6 for \$1.00	7500 ohm	
4000 ohm		10000 ohm	\$1.00
20000 ohm		20000 ohm	

Assortment of 20 above..... \$2.50

METERS

2" G.E.—5 MA..... \$1.95
2" G.E.—1.2 MA..... 2.50
3" G.E.—15 MA..... 2.95

SELENIUM RECTIFIERS

Full wave—36 volt input, 28 volt output, 6 ampr..... \$8.45
Special each

If not rated, 25% with order, balance C.O.D.—Discount 10% on any item ordered in lots of 10.

PEAK ELECTRONICS CO.

188 WASHINGTON ST., DEPT. MR
NEW YORK 7, N. Y.

cordings for Belgium; *English* period, formerly 1600-1630, is either discontinued or at a new time. (Pearce) Probably is around 1800.

Angola—Radio Clube de Angola, Caixa Postal 229, Luanda, Angola, Portuguese West Africa, in verifying by Spanish letter, listed CR6RA, 11.035, 400 watts; CR6RC, 11.730, 150 watts; CR6RL, 16.172, 1 kw.; CR6RN, 9.742, 1 kw., and additional frequencies were given as 9.500 and 7.299. (Nilsson) Correct frequency of CR6RL is 15.895. (Kary) Output is 1 kw. (Laubscher) The 9.472 channel is heard with good level in Newfoundland, 1300-1600, while the 15.895 outlet, in parallel, is poor. (Puddle) CR6RB, 9.165, is still being logged in Australia, fair signal, to closing at 1400 with Portuguese National Anthem. (Gillett)

Australia—Radio Australia recently revised schedules. The Eastern North America "morning" beam went back to old time of 0800-0915, over same frequencies, VLB, 9.54, VLC7, 11.84. The "evening" beam to Eastern North America is now 1645-1815 on VLA7, 17.800, with VLC9, 17.84, in parallel to South America; news at 1745. The "morning" West Coast beam is now 1000-1115 on VLA8, 11.76, VLB9, 9.615; "evening" West Coast transmission now begins 15 minutes earlier, that is, runs 2330-0045, radiated from VLA5, 15.32, VLC7, 11.84, VLG6, 15.24. (Worris, Balbi) The Forces' program runs 2200-2300, VLB5, 21.540, VLC9, 17.840, VLG6, 15.240; on Saturdays and Sundays runs 2100-2300 with VLA9, 21.600, added; to Europe, 0100-0145, VLC9, 17.840; to Tahiti, 0100-0145, VLG6, 15.240, and on Saturdays VLA6, 15.200, is added; to British Isles and Europe, 0200-0315, VLA6, 15.200, VLB10, 11.740 (except Saturdays), with VLC9, 17.84, used 0245-0315 only. To New Caledonia, 0245-0345, VLC4, 15.320, VLG3, 11.710; to Forces, 0330-0700, VLA6, 15.200, VLB10, 11.740; to Asia, 0355-0700, VLC4, 15.32, VLG10, 11.760, with VLB10, 11.740, used 0700-0900, and VLC4, 15.32, used 0700-0750. To Europe, 0900-1000, VLA6, 15.200, VLG10, 11.76; 0930-1000, VLB4, 11.810; 1500-1615, VLG4, 11.840, and others.

Striking of the clock at Melbourne's post office building is heard often these days in Radio Australia transmissions. (Worris)

VWL3, 11.830, Perth, is scheduled 2230-0500. (Nankervis) May run to 0515 or 0530 on occasion.

Austria—Blue Danube Network, 7.220, Salzburg, is often good level in Britain at 0030 with news; call sign seems to have changed from KOFA to KZCA (?). (Pearce)

Azores—Ponta Delgada, 11.090, has excellent signal in Newfoundland around 1300-1530. (Puddle)

Bechuanaland—ZNB, 5.900, is being heard again in Australia just prior to closing at 1430 with "God Save the King," recorded music with occasional announcements. (Gillett) Location is Mafeking.

Belgian Congo—Leopoldville ap-

SCHUH'S RADIO PARTS

Guaranteed Satisfaction!

BC 610 Components... Modulator Decks
Less modulation transformer. Completely wired..... \$14.95

RA-20 Powerpack Converts BC 312 Receiver to AC Operation. Powerpack fits right into dynamotor compartment. Also for external use with BC 348, 314, 224, and 455, 456, 457 aircraft receivers. Primary: 110-120 VAC 60 cycles; Delivers: 250 VDC @ 95 mls; 12 V @ .3 amps; 12 V CT @ 2 amps..... \$7.95

BC324 (12 volt BC 348) used in good condition with RA20 power supply..... \$45.00

FILTER KITS

11HY @ .600 amp herm sealed choke and 2 condensers 2mfd @ 5000 volts. Only \$15.95
11HY @ .600 amp herm sealed choke and 1-8mfd @ 2500 VDC condenser. Only \$12.25
8HY @ .250 amp herm sealed choke and 2 condensers 8mfd @ 1000 VDC. Only \$5.95

15Ft. Length RG8U Co-Ax Cable with connector on each end. Special..... 69c
MC MURDOS SILVER... Full line of equipment carried... see McMurdos Silver page in this issue.

TERMS: 30% with order. Balance C.O.D.

All Shipments F.O.B. Chicago

SCHUH'S RADIO PARTS

1253 Loyola Avenue • Chicago 26, Ill.

HAMS! RADIOMEN!

LOOK AT THESE CHOICE GOVERNMENT SURPLUS ITEMS:

HEWLETT PACKARD Audio Generator Model 205A, 20 to 20,000 cycles. Excellent cond. \$149.95
CONTROL UNIT RM-25. A 8 1/2" rack mount, telephone communication unit. Talk with 4 stations. Remote receiver, Xmitter control. New..... 13.95
COMBINATION TUBE TESTER AND VOM. PRECISION Model 920. Excellent cond. 49.95
WESTON 772 ANALYZER. Excellent condition POCKET REGGIE J. G. Biddle, 500v 50 meg. with case..... 49.95
WHEATSTONE BRIDGE RUBICON ±1040. Never Used..... 49.95
SIGNAL GENERATOR, WICKCO Model 177K. Excellent condition..... 54.95
CONTROL UNIT BC-1162. Wavemeter 150 to 210 mc. 110v 60 cycle power supply. 19 tubes included..... 16.95
FILTER CHOKE 9H-450MA 3.5KV Weco..... 4.95
SCR 522 local control box. No cable needed. .015mfd600V SOLAR Transoil ±XTIM..... 2.49
4mfd 500V. can, lugs, impregnated paper..... .39
TUBES JAN Inspected. Cartoned..... 7.95
307A..... \$2.89 6J8..... \$0.79 810..... 1.89
RESISTOR KIT 100 assorted 1/2 watt..... 1.89
CONDENSER KIT 40 assorted. Bargain..... 1.89
METER 0-1MA Scale 0-20KV, 3 1/2" GE ±D041..... 3.49
RELAY 12V Heavy Duty 50 AMP SPST Cont..... .69

SPECIAL \$10.00 BARGAIN ASSORTMENT

Useful assortment of parts, tubes, complete units.

Satisfaction guaranteed. A Real Buy!

REQUEST FLYERS, SEND POSTAGE ON CASH ORDERS


EASTERN ELECTRONIC SALES

31-B Cedar Drive Baltimore 20, Maryland

TONE • COLOR PERFORMANCE

St. Louis

RUGGED MIKE

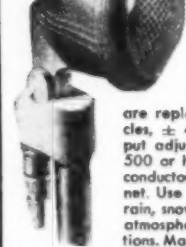

New! ST. LOUIS is ready with a really rugged dynamic microphone that will last a lifetime, for all component parts are replaceable. Range: 40-9000 cycles, ± 4 db. Variable impedance output adjustable by switch to low, 200, 500 or high impedance. 15 ft. double conductor shielded cable. Alnico V magnet. Use in or out doors in all weather, rain, snow, coastal regions, tropics, salty atmosphere, rough and extreme conditions. May be dropped successively without failure. Immediate delivery in grey, maroon, green, blue, chrome. Ask your dealer or write today for full details.

Licensed under U. S. Pat. American Tel. & Tel. Co. and Western Elect. Co., Inc.

St. Louis Microphone Company

2726-28 Brentwood Blvd. St. Louis 17, Mo., U. S. A.

pears to have replaced OTC2, 17.745, with OTM2, 9.745, in the 1530-1645 beam to Britain and British Colonies in Africa; news at opening. The 11.645 channel, although not announced, is sometimes heard in parallel.

Brazil—ZYB-7, 6.095, Sao Paulo, is heard evenings from around 2030. (Pelland) PSF, 14.685, Rio de Janeiro, heard with test program in Portuguese to 1700 daily; signs off with Brazilian National Anthem. (Hart via NNRC)

British Guiana—ZFY, 6.000, Georgetown, sends an excellent signal to Newfoundland around 1530-2000. (Peddle)

Burma—Rangoon is scheduled 0115-0145, 2015-2030 on 9.54; 0915-1015 (English session) on 6.035, news at 1000. (Radio Australia)

Celebes—Makassar's 9.265 channel is scheduled 1730-1830, 2300-0130, 0500-0930. (Nankervis) *Is complete schedule.*

Ceylon—Radio SEAC, 15.23, is heard on West Coast with weak signal around 0900; 15.12, in parallel, is much stronger. (Baxter)

The 15.120 outlet has excellent signal in the East on Sundays, 1230-1430, during the special beam to the United Kingdom.

China—XGOY, Chungking, recently replaced 15.170 with 1.913 in the North American beam, 0745-0835, and in the beam to Europe at 0845-1045; 7.152 is still announced as in parallel. News at 0800 (relayed from XGOA, Nanking), 0900, 1000. XGOY's 9.663 outlet has an improved signal here in the East in the China-South East Asia beam, 0535-0735, news at 0600. The 11.913 beam to America, 0745-0835, has terrific CWQRM and it may be that XGOY will move shortly to the 49-m. band, (approximately 6.145) where it was heard last winter. It is also likely that soon transmissions will be one hour later than the schedule just given; this also applies to times of English newscasts. Other Chinese outlets may be similarly affected.

XORA, 11.725, Shanghai, has English hours at 0400-0500, news at 0430.

Canton's 11.65 outlet carries news (relayed from XGOA, Nanking) at 0800.

XGIO, approximately 8.450, Shanghai, is reported heard irregularly, usually around 0830 with items at dictation speed; leaves the air normally around 0940.

XMAG, 4.275, Nanking, is heard in New Zealand at 0600 with AFRS programs. (Gray)

Paul Dilg, Monrovia, California, informs us that recently XNCR, 7.495, one of the Communist-controlled stations, was heard at 0740 with news, and signing off at 0800. The outlet on about 6.070 gives a call of XGHT, which is the old Hatan call sign; this channel relays XNCR to 0800 and then continues to 0900. There is a third Communist-controlled relay outlet, XGNC, around 6.470 (varies), which also relays XNCR to 0800, then,



25-Watt Re-entrant Speaker with Jensen Driver Unit and UTC Line-Matching Transformer

IN ORIGINAL, SEALED FACTORY CARTONS


Only \$21.60 Net

• We have just received our final shipment of this outstanding PA Speaker. First shipment sold out in a few days. Stock up now. You will not be able to buy this Army Surplus item in future. Specifications: 20" overall. Horn 13" dia. Metallic diaphragm voice-coil assembly (Jensen).

Driver unit alone weighs 9 lbs. UTC Line-matching Transformer 250, 500, 1000 and 2500 ohms. Speaker is fitted with mounting swivel, lock-nut and sleeve for attachment to standard pipe stand. Unquestionably one of the best surplus buys ever offered. BRAND NEW, IN SEALED CARTONS.

BC-221 FREQUENCY METER, WITH A-C POWER SUPPLY KIT AND MODULATION KIT AND CIRCUIT DIAGRAM

Now—AT LAST—you can get a BC-221 Frequency Meter with a complete kit of parts for an A-C Power Supply, plus another kit of parts for a Modulator, for about half the former price of a complete modulated instrument. You can convert the BC-221 Frequency Meter in a jiffy—and use it for receiver aligning, etc. Wiring diagrams are included with each kit. Only a few on hand. This may be your last chance to buy the BC-221. PRICES: BC-221 Frequency Meter with tubes, crystal and calibration charts, \$39.95. A-C Power Supply Kit and Diagram, \$5.85. Modulation Kit and Diagram, \$2.50. Any item sold separately if desired.

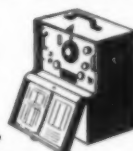

SUPER SPECIALS FOR DECEMBER ONLY

Desk-Stand Telephone Mike. FI-Unit. Long rubber-covered cord \$1.95 net
GE 1-Mfd. 6000v Pyranol Condensers. Ceramic Insulators. Brand new \$4.95
Signal Corps Telegraph Keys. Bakelite Base. Close Out special 4 for \$1.00
Navy Spare Parts Chest. Allied with Anest parts. Hundreds sold. Only few left \$4.95

SURPLUS TRANSFORMER SPECIALS

• Filament Transformer. 6.3v at 2a. Pri.-110v 60 cycles. Upright type. Fully shielded in black metal can. Brand New. \$1.25 net. Cat. #A-101
• Audio Transformer. Stancor. Single Plate to P-P Grids. Unused. Brand New. \$1.25 net. Cat. #A-102
• Oscilloscope Transformer. Jefferson. 2000v at 10 ma. Fully encased and shielded. Stand-off insulators on top. Upright type. Diagram included. Brand New. \$5.95 net. Cat. #A-103
• Plate & Fil. Xmr. Chicago Transformer Co. 270-CT-270 at 145 ma., 6.3v at 4a., 5v at 3a. 110v 60 cycle pri. Upright type. Fully encased. Long leads. Brand New. \$3.25 net. Cat. #A-105
• HEAVY DUTY XMR. Chicago Transformer Co. CT-11124. Will deliver 382v DC at 220 ma. Secondaries: 746-CT-746v. at 220 ma., 6.3v at 4.5a. 5v at 4a. Pri.-117v 50 to 60 cycles. Fully encased. Standard horizontal mounting. Leads through bottom. LIMITED QUANTITY. Brand New. Only \$4.95 net. Cat. #A-106
• HV Transformer—SUPER SPECIAL. Western Electric. 625-CT-625v at 202 ma. Also additional secondary at 18 volts. Primary—117v 60 cycles. Totally shielded, in gray lacquered case with mounting studs and ceramic insulators. Upright type. Brand New. Only \$5.95 net, while limited quantity lasts. Cat. #A-107
• Plate & Fil. Xmr. Stancor type P-4078. 350-CT-350v at 70 ma., 6.3v at 3a., 5v at 2.5a. Universal mounting. Leads thru bottom. Fully encased. Brand new. Only \$2.85 net. Cat. #A-109

CHOKES

• Thordarson T-45557. 290 Ma. Upright type. Fully encased. Long leads through bottom. Brand new. Original cartons. \$3.45 net. Cat. #A-115
• Thordarson Special Signal Corps choke in beautiful gray lacquered upright shielded case with soldering lugs at bottom. 6-hy at 75ma. Sig. Corps Type 5567a. In original factory cartons. Only \$1.49 net. Cat. #A-116

LOW-LOSS INDUCTANCE 69¢



SILVER-COATED WIRE ON PYREX GLASS FORM

A beautiful Inductance—32 turns #18 silver-coated wire on a 2 1/4" dia. Pyrex form, with bakelite rod thru center for rotating coil. BRAND NEW. In original sealed cartons. 69¢ each, or a standard box of 12 for only \$6.85!! Limited stock.

* SEND 20% DEPOSIT. BALANCE C.O.D. 4-HOUR MAIL ORDER SERVICE.


OFFENBACH & REIMUS CO.

372 Ellis St., San Francisco 2, California

'Phone ORdway 3-8551

BEST SURPLUS—BEST CONDITION—BEST APPEARANCE—

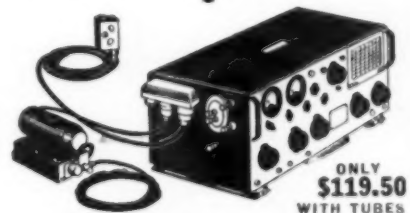You Can NOT Buy Better Surplus For Less Money Because The Electrical, Mechanical and Physical Condition Determines The Price. For 100% Top Quality Our Prices Are LOWEST !!!



Collins Art-13 Transmitter

• Look just like new. Perfect Operating Condition. We have the finest lot of these sets ever sold as surplus. Range 2000-18,000kc. in 10 channels, voice and CW or MCW. 100 Watts Output on Four. This famous Auto-Tune Xmr is sold complete with Tubes, Dynamotor, Control Box and Cable Connectors. OUI PRICE \$119.50 Net

YOU GET LESS IF YOU PAY LESS!!!

ONLY A FEW LEFT

BC-645 \$9.95

This 15-tube set will operate on frequencies for Citizens' Radio, Amateur, etc. Tubes alone worth \$25.00 net. Too well known to require description. Be safe. Order yours TODAY!! Our Price ONLY \$9.95

12/24V. DYNAMOTOR PE-101C. SUPPLIES ALL POWER FOR BC-645. 400V. 135MA. DC. ALSO 9V. 1.2a. AC. ONLY \$9.95 NET

BIG BARGAIN !! 6L6 AMPLIFIER

• Not war surplus, but a manufacturer's over-stock. Sold for less than the net cost of parts. Complete, ready to operate, in gray crackled cabinet. Made for 24-hour continuous service. Big, husky power supply. All new parts throughout, new RCA tubes. Relay and counter (counts up to 10,000 record playings). Input for magnetic or crystal pickup, or 600-ohm phone line for wired music systems. Separate tone, treble and bass controls. A SUPER BUY!! Only \$49.50 net. (List \$147.50.)

5-GANG VARIABLE CONDENSER

.000365 each section, 6" long overall, 3/8" shaft. Spade lug mounts. Scarce item. ONLY \$2.98 net.

Here's how
University
can help you plan

QUICKER... AT LOWER COST!

The logical approach to any sound system planning problem is to first select the speaker or speakers capable of proper coverage and quality of reproduction. Once the speakers have been decided upon, the selection of the correct size amplifier becomes a routine matter of totalling the powers required for the individual speakers. The many UNIVERSITY speakers now available readily solve this problem. Included are speakers for every class of service—low power, super power, directional, radial, explosion-proof, submergence-proof, high fidelity, paging talk-back and others.

BETTER SOUND SYSTEMS

WITH LESS POWER!

University speakers require minimum amplifier power. Having a higher conversion efficiency, they deliver more acoustic output per watt input, than any other speaker of comparable size and weight.

WRITE TODAY FOR THIS HANDY SPEAKER SELECTION CHART—NO OBLIGATION!

APPLICATION	SPEAKER MODEL	FUNCTION	POWER (APPROX.)	MIN. NO. SPEAKERS
OFFICES STORES STOCK ROOMS	108 OR 109	Paging and announcing. Substitute for low efficiency speakers in intercom systems.	1.3 watts per 1000 sq. ft.	1
	108	Same as above, but distribution 360°		
	109	Voice and music. Distribution 360°		
FACTORIES (light assembly) SHIPPING— RECEIVING	108 OR 109 WITH MAN 109	Paging and announcing. Same as above, but distribution 360°	1.3 watts per 1000 sq. ft.	1.2
	109 WITH MAN OR RPH 12	Voice and music. Same as above, but distribution 360°		

UNIVERSITY LOUDSPEAKERS, INC.
80 South Kensico Avenue, White Plains, N. Y.



MODEL 108
PRICE \$34.00



MODEL 109
PRICE \$37.00

University Loudspeakers

FOR QUICK RESULTS—EVERYTHING IN RADIO
USE RADIO NEWS CLASSIFIED PAGES
Only 20c per word; minimum of 10 words

PRE-HOLIDAY CLEARANCE

SPEAKERS

5" P.M. Alnico 5 Magnet, \$1.09 each
6 for \$6.00

6" P.M. 2.15 oz. Alnico 5 Magnet, \$1.69 each
6 for \$9.00

All other sizes in stock, at money-saving prices.

WIRE

400 ft. (approx.) of wire in assorted colors and gauges, solid & stranded in 2 to 4 foot lengths, per pkg. 99c

Volume Controls

1 MEG volume control with switch and long shaft, ea. 49c
6 for \$2.75

15 Assorted Volume and Tone Controls (less switches) \$1.95

RESISTOR KIT

100 Insulated Resistors, 1/2, 1 & 2 Watt \$1.95

PHONO SUPPLIES

Crystal Pickup Arms... \$1.98
Phono Motor and Turntable 2.95
I.F.'s 455 KC... 39c

CONDENSERS

Tubular Paper (600 V. Test)

Mfd.	Price Ea.	Per 100
.01	.08	\$ 6.50
.02	.08	6.50
.05	.10	8.00
.1	.12	9.00
.25	.17	13.50
.001	.08	6.50
.002	.08	6.50
.005	.08	6.50
.006	.08	6.50
.5	.26	22.50

"Illinois" Electrolytics

Mfd.	VDC	Price each
10	25v	.30
100	25v	.48
12	50v	.34
16	150v	.36
20	150v	.38
24	150v	.38
30	150v	.40
50	150v	.48
8	450v	.38
10	450v	.42
16	450v	.54
20	450v	.60
40	450v	.80
100	15v	.45

"Illinois" Duals

16-16	150v	.50
20-20	150v	.52
30-30	150v	.60
40-20	150v	.60
50-30	150v	.68
8-8	450v	.68
10-10	450v	.74
20-20	150v	.84

10% discount on all electrolytics if purchased in lots of 10 or more. Mica Condensers, all sizes, 8c each.

Minimum Order \$2.00—20% with Order. Balance C.O.D.—WRITE FOR CATALOG.
TWO CONVENIENT PLACES FROM WHICH TO ORDER. PLEASE ADDRESS DEPT. A12

ELECTRONIC DISTRIBUTORS, INC.

620 W. Randolph St., Chicago 6, Ill.

ELECTRONIC PARTS CORP.

436 W. State St., Milwaukee 8, Wisc.

like XGHT, continues to 0900 close-down. XNCR drifts from 6.020 all the way to above 6.080.

Curacao, PJCI, 7.250, Willemstad, is fine level in Newfoundland, 1730-2000. (Peddle) Widely heard.

Czechoslovakia—Prague has revised schedules; news is at 1245 on 11.840, and at 1445 and 1645 on 9.553; the 9.553 transmitter closes at 1700 with announcement that Prague will be back on 15.35 to North America in English and Czech at 1800-1900. (Pearce) It is possible that by now the North American beam will have returned to time of 1900-2000, which was the schedule last winter.

Denmark—Danmarks Radio, Copenhagen, is scheduled over OZF, 9.520, 1145-1545; and over OZH, 15.165, 1100-1430; uses 6 kw. (Mattsson) OZH2, 15.320, Skamlebak, is heard Sundays 0700-0800 when VLC4 is off this frequency. (Legge via NNRC)

Dominican Republic—HI2T, 11.900, La Voz del Yuna, Ciudad Trujillo (formerly at Monsignor Nouel), is heard evenings in parallel with 7.275; bad QRM from CXA10, Uruguay, and CE1190, Chile. (Legge via NNRC)

Egypt—SUX, 7.863, Cairo, has a good to excellent signal with slight QRM in Newfoundland, 1515-1630 closedown. (Peddle)

Ethiopia—Addis Ababa's 19-m. outlet (approximately 15.057) has not been reported as heard lately. Formerly closed at 1500.

Finland—Helsinki's 15.190 and 9.505 outlets have news daily at 0715; poor signals in Britain; sign-off is 0725. (Harrison) Similar reception in Newfoundland. (Peddle) Also scheduled with news for 1925 but not reported as heard lately.

France—Paris appears to be using 11.7 to North America, 1915-2015, announced to have power of 100 kw. but in Florida it is not as strong as the parallel stations on 11.845, 9.55, 15.35. (Worris) Official schedules to North America are given as 1700-1715, 15.24, 15.35, 17.85; 1915-2015, 9.55, 11.845, 15.35.

French Indo-China—Radio Saigon is being heard in Sweden on 18.397 from 1030. (Nilsson) This transmission is beamed to France and is heard on West Coast; call is FZS, which is Saigon's phone station. (Dilg)

The 11.78 channel is again audible here in the East, evenings. Opens at 1830 with "La Marseillaise"; news is scheduled for 1945, and sign-off is around 2005. In latter part of transmission is buried usually by carrier from the U.S. outlet on 11.79. Parallel frequency is officially listed as 6.165.

English news periods of Radio Saigon are at 1945, 0500, 0900. (Kary) Final closedown for the day is at 1015. (Park)

Hanoi has replaced 9.645 with announced 6.048; gives call as "Radio France in Hanoi." News at 0700, off around 0755. (URDXC)

French Morocco—Rabat's 9.080 channel is heard on West Coast at

RADIO NEWS

0145-0500. (Nankervis) Is also scheduled for around 1315-1905.

French West Africa—Radio Dakar, 11.715, is being heard in Eastern United States to around 1800 close-down. (Pelland) Widely heard with good level.

Germany—DTSP, 15.105, was heard at 0900 recently in a point-to-point broadcast; very good level. (Pelland)

AFN, 6.080, heard on West Coast signing on at 2300, heard as late as 1500 through bad CWQRM. (Nankervis) Full schedule believed to be 2200-1700; Hamburg, 6.115, runs 0000-1600; Leipzig, 9.73, 2200-1700; Berlin, 6.070, 2200-1700; Baden-Baden, 6.320, 2230-1730. (Short Wave Listener, London)

Iceland—Reykjavik, 12.235, is still used occasionally for special broadcasts from this country; if anyone picks up this one, reports may be addressed to Horst Egilson, Secretary, Ríkisutvarpid (Iceland State Broadcast Service), Reykjavik, Iceland. (Short Wave Listener, London)

India—AIR, Delhi, has replaced the 100 kw. station on 11.850 with 11.830, 10 kw., call is VUD4. AIR schedules remain primarily the same.

Iran—EPB, Radio Teheran, 15.100, is still being heard well in Eastern United States with news at 0715, then music and announcements to sign-off at 0730. (Pelland) EQB, 6.155, is scheduled 2230-2315, 0930-1400. (Short Wave Listener, London) Tabriz, 12.180, is heard in Britain around 1240 to 1300 closedown with military march; uses some western recordings. (Pearce)

Iraq—HNF, 6.780, Baghdad, reported at 1330 with Arabic music. (Short Wave Listener, London) Is heard in Britain at 1530 with Eastern type programs; has time signals on hour and half hour; fair strength. (Harrison)

Ireland—Radio Eirrean, 9.595, is good level in Newfoundland with news 1610-1630. (Peddle)

Italy—Radio Italiana has replaced 9.63 with 15.120 in the North American daily transmission 1910-1940, news at 1930; fair to good signals; 11.81 is announced in parallel; the 15.12 transmitter appears to be on the air (in Italian) at least an hour prior to beginning North American program; on Mondays at 1910 presents a request musical program for U.S. listeners. Gives QRA as Italian Broadcasting System, ROI, Rome, Italy. (Worris) Transmitter may be at Milan.

Jamaica—ZQI, 3.48, has good signals in Pennsylvania to nightly sign-off at 2200; has local and world news at 2100. (Glenn) Signs on at 1930. The 4.950 outlet is scheduled 1600-1730, with world news at 1715.

Japan—WLKS, Kure, the British Occupation Forces' Station, has moved to 6.065; relays news from *Radio Australia* at 0400. (Gray) Schedule is 1630-0830, Saturday to 0900. (URDXC)

The AFRS outlet in Tokyo on 6.015 is again being heard here in the East,

December, 1947

SHURE Proudly Presents



SONODYNE

A MULTI-IMPEDANCE DYNAMIC MICROPHONE

Here is *the* microphone in its class—a high output moving-coil dynamic that was designed to out-perform...out-smart...out-last even higher-priced microphones. The "Sonodyne" features a multi-impedance switch for low, medium, or high impedance—plus a high output of 52 db below 1 volt per dyne per sq. cm. It has a wide-range frequency response (up to 10,000 c. p. s.) and semi-directional pickup. Mounted on swivel at rear, can be pivoted 90°.

SONODYNE—Model 51—Code: RUSON

Shure Patents Pending

SHURE BROTHERS, Inc.

Microphones and Acoustic Devices


225 West Huron Street

Chicago 10, Illinois

Cable Address: SHUREMICRO

SHURE

YOU GET Big VALUE AT D & H

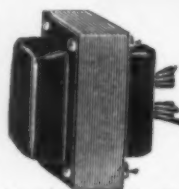

SPECIAL! POWER X FORMERS WHILE THEY LAST


Quantities limited, so act fast and get in on this real transformer deal. All standard brands—individually boxed.

50X—50MA 5 and 6.3 Filaments.....	\$1.34
75X—75MA 5 and 6.3 Filaments.....	1.65
60CB—6000 C.R. Tube Xformer.....	7.49

CHOKES

40C—40MA	\$0.49
50C—50MA58
85C—85MA58
125C—125MA92
160C—160MA	1.32

WEBSTER • Model-79

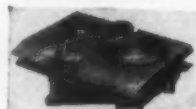

FOUNDATION RECORDER UNIT

Complete wire transporting mechanism, a triple-purpose recording head (records, erases and plays back), an oscillator coil, a 15 minute spool recording wire, and an instruction sheet with suggested circuit diagram. Takes any standard Armour type recording spool and will make continuous recordings up to a full hour.

Your cost **\$52.92**

FILAMENT XFORMER

2F—2.5-10 Amps	\$1.49
----------------------	--------

PUSH-PULL INPUTS

1PP—Med. Plate to PP Grids—LoZ.....	.88
2PP—Med. Plate to PP Grids—HiZ.....	.72

INTERSTAGE

11S—PP Plates to PP Grids (20,000 Ohms) ..	2.76
21S—PP Plates to PP Plates	1.56

OUTPUT XFORMERS

10T—25L6—35L658
20T—Universal—10 watt72

M15 Webster Phono Motors.....	5.10
Alliance Phono Motors.....	3.75
Auto Antennas (Side Cowl) Your Cost.....	1.19

BC-654A RECEIVER-TRANSMITTER

Use it for While They Last

- PARTS
- TUBES
- TRANSMITTER
- RECEIVER

\$14.95

as is less dynamotor
One-third deposit with order, balance C.O.D.,
F.O.B. shipping point.

ASK FOR OUR EASY TIME PAYMENT
PLAN ON SUPREME TEST EQUIPMENT

It's D & H for Dependable
Parts Service

D & H

RADIO
PARTS
DIVISION

DISTRIBUTING CO., Inc.

311 S. Cameron St., Harrisburg, Pa.
31 East Lee St., Baltimore 2, Md.

fair to good around 0600-0700; sometimes announces Tokyo-Yokohama.

JKG, 9.695, carries sports events (in Japanese) irregularly around 2200-0230, not daily.

Java—PMW is a new outlet of Radio Batavia heard on 17.630 beaming to Middle and/or Near East from 1200-1245 in English and Arabic; news at start. The "Voice of Free Indonesia," 11.001, has news at 1200. (Nilsson) PMW is heard on West Coast. (Dilg)

The Indonesian news agency, Antara, broadcasts daily by "CQ" call around 8 megacycles, giving the latest news of the Far East. (Miers) Schedule was not given.

Radio Raja Indonesia is now on 9.355 from 9.405; scheduled 0930-1130; no English, only Indonesian dialects. (URDXC)

Korea—A new station in this country is reported as JBBK, Pyongyang, 4.400, Russian-controlled, scheduled 0300-0800. (URDXC)

Lebanon—Radio Beirut, 8.036, is heard in Sweden signing off in French at 1600. (Nilsson) Also heard in Newfoundland, good signal but some CWQRM. (Peddle)

Luxembourg—Radio Luxembourg's 6.090 channel was recently heard in French in Rhode Island at 0020, very good signal. (Pelland) The 9.525 outlet has been heard on West Coast, testing around 0040-0100. (Nankervis) Also has been testing on 15.350.

Malaya—In a letter to Paul Kary, Pennsylvania, the British Far Eastern Broadcasting Service, P.O. Box No. 434, Singapore, Malaya, advises that Radio Malaya was the original BMA radio. "We shared studios for a short time from December 1945 to February 1946, but we are an entirely separate organization with our own studios and transmitters now. Radio Malaya serves the local population of Malaya, and B.F.E.B.S. broadcasts on shortwaves only to non-British territories in South East Asia, outside Malaya, so our angle of program approach differs. We relay many BBC programs from London" Schedules give the Orange Network on 11.735, 6.77, daily, 0030-0130, 0300-1200, news at 0100, 0400, 0645, 0900 (Radio Newsreel), 0915, 1100, 1145; the Purple Network on 15.30 and 9.69, daily, same schedule. English portions on both networks are identical. Program summary is carried by both networks at 0330 on Wednesday, Thursday, Friday. The 9.69 channel is experimental and is subject to change.

Monaco—Radio Monte Carlo, 6.130, is heard in Britain with some fading around 0230; has man and woman announcers. (Pearce) This outlet was supposed to increase power in July but so far it would appear this has not been effected.

New Caledonia—Radio Noumea has returned to its old frequency of 6.208 from 6.160; closes down at 0500. (Cushen)

New Guinea—Biak, 7.200, Dutch New Guinea, signs off at 0630 with

Gasoline driven 110V. 60 Cycle AC Generators. You'll never see another bargain like this. 2500 Watts, 115 v. 60 cycle, New \$250. Slightly used \$200. Briggs and Stratton Engines. 1000 Watts, 115 v. 60 cycle, New \$175. Briggs and Stratton Engines.

600 Watts, 115 v. 60 cycle, New \$85. Slightly used, \$50.00. Wisconsin Engine.

Tylon steel ladder towers, 50 foot, new, complete with mounting base guy wire and insulators, hardware, wrenches, rope (320 ft.) gin pole and instructions, everything but the labor \$100.00 each. Four \$75.00 each. In 3 wood boxes, 550 lbs.

Tuning control knob for SCR-274N and ARC-5 radio receivers, BC-946, BC-453, BC-454, BC-455 and Navy versions. Also contained in this kit are Allen wrench, Phillips Head screw driver and a metal tube puller for removing those hard-to-get-at tubes. Priced at \$1.00 a kit, 3 kits for \$2.00. Postage paid.

When Bigger and Better Bargains are offered, Van Norman will offer 'em.

VAN NORMAN Radio Supply Co.

Naperville, Illinois Naperville, 613R1

SEND 10¢

For a T-30 Throat Microphone and our Big Bargain Catalog on Surplus Radio Parts, or Catalog Sent Free on Request.

We just bought 200,000 pounds of Navy Electronic and Radio Spare parts. This is really a swell bunch of merchandise, transformers, resistors, chokes, condensers, relays, insulators and plenty of other choice items including Meters of all types.

Send that dime today.

QUINN'S GADGET SHOP
2253 E. 14th St., Oakland 6, Calif.

MOBILE TRANSMITTERS

Used—Mfd. by KAAR—Uses instant heating HY-65 osc., HY-65 RF, HY-65 Mod. Self-contained 6 Volt Vib. Supply, push to talk & Ant. relays. Full simple instructions for conversion to 10 meters. Complete with tubes, power supply, dust cover & shock mounts.

\$50.00 f.o.b. L. A.

ALVARADIO • 903 S. Alvarado
Los Angeles 6, Calif.

TRADING NEWS

"The Advertising Paper For All Radiomen"

Published monthly and distributed

FREE to OVER 25,000 HAMS and SERVICEMEN—
CLASSIFIED ADS 7c Per Word—Quick Results!

Get on Mailing List TODAY

TRADING NEWS

P. O. Box 7012, Lafayette Sta., Norfolk, Va.

Ask for **ELECTROPARTS** Chemicals

"The Finest At The Lowest"

Write for Latest Catalog 1-17, Dept. H
GLENDALÉ CALIFORNIA

"A Perfect Day" Sign-on is 0500. Uses both Dutch and *English*, many American recordings. Speech modulation is poor. (Gray)

New Zealand—Frequencies allocated to New Zealand's National Broadcasting Service are 6.080, 9.540, 11.780, 15.280. The service should get under way by some time this month. Already tests have been heard irregularly. (Continued on page 190)

Voice Controlled Relays

(Continued from page 57)

and switchless break-in operation is maintained. The gain control R_6 is adjusted to permit positive operation of the relay without maintaining high enough gain so that any extraneous noises actuate the control circuit. In radio-telephone operation it is desirable to keep the gain as low as possible and talk closely into the mike in a normal voice, to prevent the receiver loudspeaker as well as other sounds from automatically throwing the transmitter on the air. Placing two or more sensitive relays in series will permit the unit to perform a multiplicity of operations.

Utilizing a voice controlled relay in conjunction with a transmitter increases the over-all percentage of efficiency. For, when there are pauses or short silent periods, the equipment is placed in power-saving "standby" until the instant that modulation recommences.

The "master control" switch in Fig. 3 is a five-position, three-pole affair and serves the following purposes:

Position 1 disconnects the a.c. line and the entire unit is off.

Position 2 connects the a.c. line to the unit, turning the heaters of all tubes on, while keeping the high voltage off the unit. Position 2 also shorts R_{10} and C_6 , the time delay constants. This is the standby position, when the transmitter is to remain in "standby" for long periods.

Position 3 is the full automatic voice control. The heaters are on, the high voltage is applied, the time constants are in normal and the bias is correct for V_4 . Ready to operate.

Position 4 removes the major portion of the bias from V_4 by shorting the potentiometer R_{11} . This keeps the relay closed and independent of audio input to V_4 . This is for adjustment, for maintenance, or for the use of the unit as a preamplifier without relay control.

Position 5 grounds the grid of V_4 , keeping audio from actuating the relay. A key inserted in the jack provided for the purpose shorts the bias control and operates the sensitive relay as an ordinary keying relay for c.w. operation. Another set of contacts can be added to the switch making it a four-pole, five-position affair, and the extra set of contacts can be used to disconnect the power from the final modulators while in the 5th or c.w. position.

December, 1947

Now... a low-cost transcription quality crystal pickup!



Cartridge requires only ½ ounce stylus force. Sapphire stylus can be removed and replaced without tools.

This is sensational news! The BR-203 crystal pick-up offers unequalled characteristics—and at low-cost!

- Maximum stylus life due to highly compliant mounting and low stylus force . . . almost impossible to chip.
- High output.
- Internal equalization.
- Flat frequency response.
- Low distortion.
- Only ½ ounce stylus force required.
- Stylus removable and replaceable without tools.
- Low stylus talk.
- New crystal mounting keeps crystal effective in high humidity.
- Tests show cartridge unharmed after 15 minutes in boiling water.
- New PN crystal will withstand temperatures as high as 250°F.

For the complete story on this latest Brush Development, write TODAY!


THE **Brush**
DEVELOPMENT CO.

3405 Perkins Avenue • Cleveland 14, Ohio, U.S.A.

MAGNETIC RECORDING DIV. • ACOUSTIC PRODUCTS DIV.

INDUSTRIAL INSTRUMENTS DIV. • CRYSTAL DIVISION

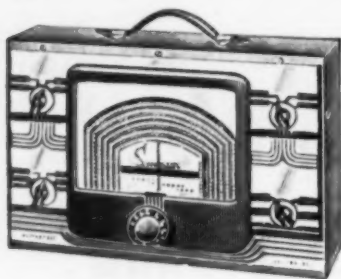Take the "Guess-so" out of your SERVICING



A good signal generator is a "must" for every service technician. Jobs come off the bench in half the time and net profits take a healthy rise. In this class of instruments we recommend and stand back of the —

SIMPSON MODEL 315 SIGNAL GENERATOR

because of its in-built accuracy, high stability, minimum leakage and excellent wave form. Big 9" meter dial with knife edge pointer. Modulation 30% at 400 cycles. Vernier controls. Electron coupling. Six ranges: 75-200, 200-600, 600-1700 kcs and 1.5-4.5, 4-12, 10-30 mcs. Freq. accuracy 1%. Price complete \$67.35. Extra for 220v 50 or 60 cyc. \$7.50. Shipping weight, 20 lbs.

EASTERN MODEL 600 A.M. 6 VOLT FIXED/MOBILE TRANSMITTER



A well built job that will operate efficiently in the 10 Meter band from either 6v DC or AC. Output 10 watts intermittent or 7.5 watts continuous on phone. 2E30 crystal oscillator and doubler, 2E30 P.A., 2E30 modulator, 024 rect. Range 27-30 mcs. Zero stand-by current. Push-to-talk and switching relay. Shock mounting. Weight 5 lbs. Designed to work portable, mobile or fixed as desired. Price less tubes, crystal and microphone \$62.50.

ACT FAST IF YOU WANT 'EM!

● TUBES

807	\$1.35	1T4	\$5.59
TZ40	1.85	5R4GY	.95
HK24	.79	6AC7	.69
1625	.49	6AG7	1.05
955	.45	All brand new!	

15-E's...\$1.95

An ideal VHF triode for 144 mcs. and above. Plate dissipation 20 watts. Extremely low interelectrode capacities. Max. ratings to 600 mcs.

● **CRYSTALS**—Mounted crystals in FT-243 Holders with 1/2" pin spacing — these are armed forces surplus sold at the unheard-of price of 95c ea. See our adv. in November RADIO NEWS for list of frequencies. Frequency accuracy guaranteed. Also thousands of unmounted crystals at 3 for \$1.00. Name your frequency — the chances are we have it!

● **COMPONENTS** — Johnson No. 210 sockets 29c, Acorn ceramic tube socket 19c, 550 ohm, 50 watt potentiometers (similar to 1RC PR-50) \$1.74, Aladdin IF Transformers GA-101, Polyiron cores, 465 kcs., Converter 98c, Aladdin IF Transformers GA-201, Polyiron cores, 465 kcs., Diode, 98c, Same per pair \$1.75.

● **COAXIAL CABLE** RG-11/U 10c per foot, 100 feet or more 8 3/4c per foot.


Terms: 20% cash with order — Balance C.O.D. If "not in stock" we'll refund by check — not credit slip.



**ELECTRONIC
MARKETERS, Inc.**

200 VARICK STREET, NEW YORK 14, N. Y.

Phone: WAtkins 4-9488

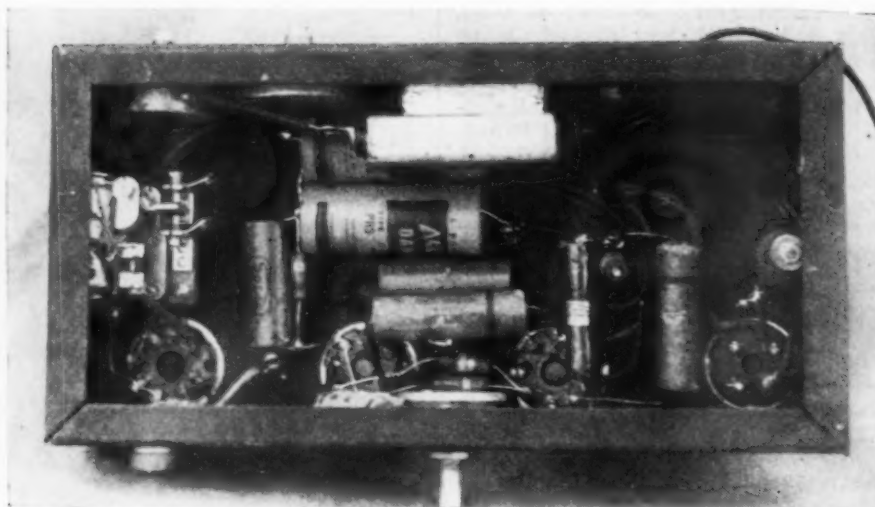

Under chassis view of the voice controlled relay unit. This particular piece of equipment was used to drive a paging system. Schematic diagram is shown in Fig. 2.

The relay contacts, in transmitter control operation, are perhaps best connected in the exciter circuit to permit complete and instantaneous break-in operation with a minimum of mechanical operations.


An interesting unit is diagrammed in Fig. 4. This unit is now under construction and installation. It is to be installed in a wire recorder. The relay contacts will be used to start the wire motor and automatically turn it on and off as the voice operates it. In the office it can be used by an official as a dictating machine. The recorder is placed in the "record" position and concealed in some convenient corner or closet. The microphone is plugged in as it would normally be and all the user has to do is pick up the microphone and start talking. This starts the motor pulling the wire. The time delay constants will keep the motor running for as long as desired after the dictation is stopped. Experiment has shown that a four second delay is adequate for dictation. No switches for the busy executive to bother about. Everything is automatic. No discs to

replace. Then at the end of the day, the secretary rewinds and plays back the wire recorder. The machine is used as it would normally be used without the addition of the automatic voice controlled relay unit. The measurements of this unit will be small enough to permit it to be easily fitted inside the wire recorder case. It uses a 6J7 pentode amplifier and a 6SN7 rectifier and relay control tube. The power is taken right off the wire recorder supply. The grid of the 6J7 is connected through a coupling condenser to the plate of the output tube of the recorder amplifier.

There are many uses suggested by the unit. The relay can be made to operate a counting device or a stepping relay. Being a sound-operated device it can be made to operate an alarm circuit when a pre-determined audio level is reached. This is designed for the ham, the experimenter, the serviceman, the public address system, the engineer, the laboratory, the office, the production plant, or for the gadgeteer. It can be a necessity or it can be a toy.

—30—

Fig. 4. Schematic diagram of unit that is now under construction. It is the author's intention that this piece of equipment control the operation of a wire recorder.

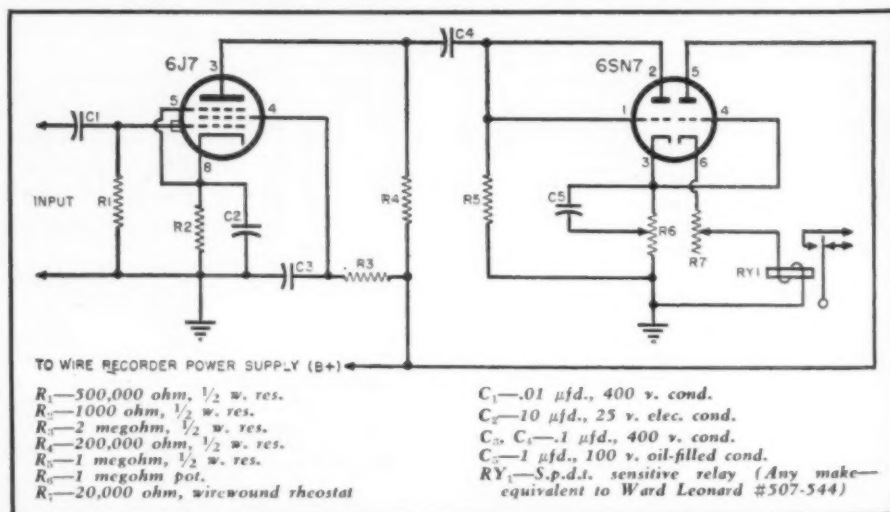

BUILD YOUR OWN SIGNAL TRACER

and Save!!



MODEL CA-12 Kit includes ALL PARTS assembled and ready for wiring, circuit diagram and detailed operating data for the completed instrument.

\$24⁸⁵ NET

We are pleased to announce we have obtained an exclusive franchise to distribute the well known Model CA-12 Signal Tracer in kit form. The Model CA-12 sells regularly for \$34.85, here is your opportunity to save \$10 with the added advantage of complete familiarity of design and operation made possible when you build your own instrument.

THE MODEL CA-12 KIT COMES COMPLETELY ASSEMBLED. Can be wired in 30 minutes. Components and circuit guaranteed to meet the following:

FEATURES:


- ★ COMPARATIVE INTENSITY OF THE SIGNAL IS READ DIRECTLY ON THE METER—QUALITY OF THE SIGNAL IS HEARD IN THE SPEAKER.
- ★ SIMPLE TO OPERATE—ONLY ONE CONNECTING CABLE—NO TUNING CONTROLS.
- ★ HIGHLY SENSITIVE—USES AN IMPROVED VACUUM-TUBE VOLT-METER CIRCUIT.
- ★ TUBE AND RESISTOR CAPACITY NETWORK ARE BUILT INTO THE DETECTOR PROBE.
- ★ BUILT-IN HIGH GAIN AMPLIFIER—ALNICO V SPEAKER.
- ★ COMPLETELY PORTABLE—WEIGHS 8 POUNDS—MEASURES 5½" x 6½" x 9".

20% DEPOSIT REQUIRED ON ALL C. O. D. ORDERS

GENERAL ELECTRONIC DISTRIBUTING CO. Dept. RN-12, 98 Park Place
New York 7, N. Y.

Amazing Bargain in Diagram Manuals

Here are the diagrams and service help you need to simplify and speed-up all radio repairs. Use these low priced *most-often-needed* diagram manuals to service radios faster, better, easier, and save money and time. For the trivial price of \$2.00 for most volumes, you are guaranteed of having in your shop and on the job, needed diagrams and essential repair data on 4 out of 5 sets you will ever service. Details on special offer below. Rush *no-risk trial coupon* today or see these manuals at your jobber.

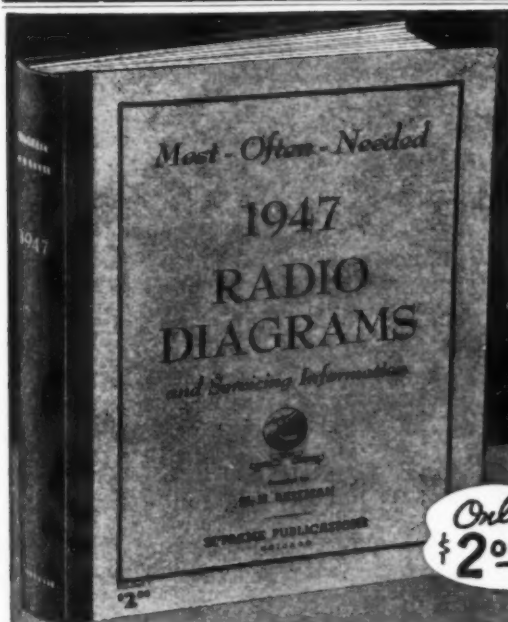

Only \$2⁰⁰



GET ALL 7 VOLUMES NOW

Be prepared to repair quickly all new 1947 sets. In this big single volume you have clearly-printed, large schematics, needed alignment data, replacement parts lists, voltage values, and information on stage gain, location of trimmers, and dial stringing, for almost all new sets. A worthy companion to the six previous volumes used by over 100,000 shrewd radio servicemen. The new 1947 manual covers 327 models of 52 different manufacturers. Large size: 8½x11 in., 192 pages + index. Manual style binding. Earlier volumes, covering previous years, similar in appearance and content. See next column and send coupon to examine manuals without risk.

Get ahead and save money by using SUPREME PUBLICATIONS Diagram Manuals. Every popular radio of every make from old-timers to new 1947 sets, is included. Clearly printed circuits, parts lists, alignment data, and helpful service hints are the facts you need to improve your servicing ability. Save hours each day, every day, let these seven volumes furnish diagrams for 80% of all sets. See pictures of these attractive manuals above. Each volume has between 192 and 240 pages, large size 8½x11 inches. Manual style binding. Complete satisfaction guaranteed. Send coupon today. →

NO RISK TRIAL COUPON

SUPREME PUBLICATIONS

9 S. KEDZIE AVE.

CHICAGO 12, ILL.

SHIP THE FOLLOWING MANUALS: (Complete satisfaction guaranteed, or your money refunded.)

☐ 1947 ☐ 1946 ☐ 1942 } \$2.00 ☐ 1926-1938
☐ 1941 ☐ 1940 ☐ 1939 } Each || Price: \$2.50

☐ I am enclosing \$.....; send postpaid.

☐ Send C.O.D. I am enclosing \$..... deposit.

Name.....

Address.....

SELENIUM RECTIFIERS

FOR ALL APPLICATIONS

FULL WAVE BRIDGE TYPES

Input	Output	Current	Price
From 0-18 V.A.C.	From 0-14 V.D.C.	1 AMP.	\$2.49
0-18 V.A.C.	0-14 V.D.C.	5 AMP.	4.95
0-18 V.A.C.	0-14 V.D.C.	10 AMP.	7.95
0-18 V.A.C.	0-14 V.D.C.	15 AMP.	10.95
0-18 V.A.C.	0-14 V.D.C.	20 AMP.	13.95
0-18 V.A.C.	0-14 V.D.C.	25 AMP.	16.95
0-18 V.A.C.	0-14 V.D.C.	30 AMP.	19.95

Input	Output	Current	Price
From 0-36 V.A.C.	From 0-28 V.D.C.	3 AMP.	\$5.95
0-36 V.A.C.	0-28 V.D.C.	5 AMP.	7.95
0-36 V.A.C.	0-28 V.D.C.	10 AMP.	13.95
0-36 V.A.C.	0-28 V.D.C.	15 AMP.	19.95
0-36 V.A.C.	0-28 V.D.C.	20 AMP.	25.95
From 0-120 V.A.C.	From 0-100 V.D.C.	2 AMP.	14.95
0-120 V.A.C.	0-100 V.D.C.	5 AMP.	19.95

FULL WAVE CENTER TAP

Input	Output	Current	Price
0-400 V.A.C.	0-350 V.D.C.	600 Mils	\$5.95

It would be impossible to give a complete listing of all our rectifier types. Our engineering staff is at your service to help you work out the application of selenium rectifiers to your specific problems. Write us for quotations or further information on capacitors and transformers to be used in conjunction with selenium rectifiers.

All Merchandise shipped via Railway Express, unless otherwise specified.

OPAD GREEN COMPANY • 191 GREENWICH ST. Dept. 2

NEW YORK 7, N. Y.

Phone: BEEKMAN 3-7385

HALF WAVE TYPES*

Input	Output	Current	Price
From 0-18 V.A.C.	From 0-7 V.D.C.	3 AMP.	\$2.25
0-18 V.A.C.	0-7 V.D.C.	5 AMP.	2.95
0-18 V.A.C.	0-7 V.D.C.	10 AMP.	4.95
0-18 V.A.C.	0-7 V.D.C.	15 AMP.	6.95
0-18 V.A.C.	0-7 V.D.C.	20 AMP.	8.95
0-18 V.A.C.	0-7 V.D.C.	25 AMP.	10.95

Input	Output	Current	Price
From 0-36 V.A.C.	From 0-14 V.D.C.	3 AMP.	\$2.95
0-36 V.A.C.	0-14 V.D.C.	5 AMP.	4.95
0-36 V.A.C.	0-14 V.D.C.	10 AMP.	7.95
0-36 V.A.C.	0-14 V.D.C.	15 AMP.	10.95
0-36 V.A.C.	0-14 V.D.C.	20 AMP.	13.95
0-36 V.A.C.	0-14 V.D.C.	25 AMP.	16.95

*Use with capacitor to obtain any voltage up to twice rated output.

CAPACITORS

1000 MFD., 15 V.D.C.	98c
Dual 3500 MFD., 25 V.D.C.	2.95

Technical BOOKS

"TELEVISION RECEIVER CONSTRUCTION" by Arthur Liebscher. Published by the author. 47 pages. Price \$1.50.

In this "how-to-do-it" book, the author has broken down the constructional process into 243 well-defined steps, beginning with the sorting and labelling of components to the installation of the last tube and turning on the television receiver.

Each series of steps is pictured so that non-technically trained persons who might have difficulty reading a schematic diagram can construct this television set without assistance.

The first chapter is devoted to a brief resumé of how television works. The discussion is non-technical and should prove of interest to the layman. A second chapter is devoted to the precautions which must be taken by the constructor in handling the high voltages present in a television receiver. The necessary tools and instruments are listed and explained in a separate chapter while a complete parts list including quantity, type, suppliers, and descriptions of the components is given in Chapter 4.

Details on inspection test and alignment, operation of the receiver, troubleshooting, antenna construction, and a glossary of television terms completes the text.

The receiver described in this book is the same unit described in Mr. Liebscher's article "Learn as You Build—Television" appearing on page 39 of the September issue of RADIO NEWS.

The material is clearly presented and no difficulties should be encountered by the constructor who follows instructions "to the letter." The lavish use of photographs and sketches further clarifies the presentation.

"PRINCIPLES OF ELECTRICAL ENGINEERING" by T. F. Wall. Published by Chemical Publishing Co., Inc., Brooklyn, New York. 554 pages. Price \$8.50.

This text is a comprehensive study of the basic principles of electrical engineering. The author has presented the subject in an orderly and well-thought out progression which starts with a thorough discussion of the basic technical units used in electrical engineering. A complete discussion of absolute units, the M.K.S. system, and the rationalized system is included.

Latest data on synthetic insulation materials, as applied to high-frequency applications, should be of particular interest to the radio engineer. One chapter is devoted to the principles of propagation, through space, of electromagnetic waves, with particular reference to the method of calculating energy relationships of receiving and transmitting antennas.

One valuable addition to the book

RADIO NEWS



RADIO COURSES

Preparatory, Broadcast, Marine Operating, Servicing, Aeronautical, Television, Frequency Modulation, Radar.

Classes forming for mid-year term
February 1st. Entrance Exam. Jan. 12th.

Veteran Training. Literature.

Commercial Radio Institute
(Founded 1920)
38 W. Middle St. Baltimore 1, Md.

EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready-to-go GRM.



ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY

4711 SHERIDAN ROAD, CHICAGO 40 ILLINOIS

Model TS-10K Sound Powered Phone (never used).....\$28.50 Pr.

AMAZING BLACK LIGHT

Complete with resistance line cord & ultra violet ray filter. Ready to operate from your 110 v. AC line.

Rigid Mount.....\$2.95
Goose-neck Mount.....3.49
Replacement Bulbs......35 ea.

FILTER CHOKES

30 Henry 50 MA. 2500 volt RMS 500 ohm DC resistance. Open frame.....\$0.75
10 Henry 100 MA. 455 ohm DC resistance. Mfd. by Westinghouse, hermetically sealed......85

WIRE WOUND RHEOSTATS

50 Watts, 8 ohms and 35 ohms.....\$0.85 ea.
25 Watts, 100 ohm, 25 ohm, 35 ohm, 2500 ohm......75 ea.

MALLORY CAPACITORS

1100 MFD. 50 Volt.....\$0.90
1500 MFD. 50 Volt.....1.10
2000 MFD. 50 Volt.....1.25

SWITCHES

Slide switch: Stackpole DPDT.....\$0.15
SPDT momentary, center off position, long bat handle......29

CONDENSERS

3 Gang Variable Condenser 50 MMFD per section. Ceramic insulation.....\$0.65
4 Gang Variable Condenser 50 MMFD per section. Ceramic insulation......85
Oil filled condensers:
103 mfd. 7500 v.....\$1.15
4 mfd. 2000 v. DC.....2.75
1 mfd. 2500v. D.C.....1.25
1 mfd. 1200 v. DC......65

A.M. RADIO SALES COMPANY

345 CANAL ST.

NEW YORK 13, N. Y.

No Sale Less than \$2.00
All Prices F.O.B. New York City
20% Deposit Required with All Orders

DECEMBER SPECIALS!

SURPLUS SPECIAL

Small 110 v. AC open frame motors, 1/2" shaft, 2700 R.P.M., 1/70 H.P., mfd. by BARBER COLMAN CO.\$2.00 ea.

KNOBBS

Large skirt knobs 2" diam.—1/4" shaft.....\$0.25
Finger grip knobs 1 1/2"—1/4" shaft......12
Red bar knob 2 1/4" long—1/4" shaft......10

MISCELLANEOUS

PL259A Coax Connector and Socket. *Silver Plated for RG8U and RG11U.....\$0.50 pr.
3AG fuse holder. Mfd. by Littelfuse......20
Flexible shafts, 4 1/2 inches long.....3 for
Grounding straps, heavy flexible wire, lugs both ends—4 inches long......05
Mica trimmers: Variable 3-30 Mmfd 4 gang......20
Variable ceramicon 4-30 mmf. 7-45 mmf. 4 Gang dial assembly 1 : 1 ratio. Ideal for centralizing controls using flexible shafts.....1.25
Filament Transformer: 5 volts @ 4 amp. 110 volt pri. open frame, porcelain standoffs. Mfd. by G.E.....1.00
0 to 15 DC Milliammeter. Simpson 3 1/2" Bakelite case.....2.95

SYNCHRONOUS MOTOR

1/2" shaft 110 v. AC 60 cy. 1 RPM, 2.2 watts. Mfg. by Hayden Mfg. Co.\$1.25

is a Bessel functions table in a simplified, easy-to-use form.

Ordinarily we would not recommend this book as a home-study text, but because of the clarity of presentation there is no reason why a student with a *thorough* background in mathematics shouldn't derive much benefit from a serious and careful study of this material.

A series of test examples covering each chapter are included in the book and those using the text can easily check their grasp of the subject by solving the problems related to the subject matter.

A rather comprehensive appendix has been provided and covers certain mathematical relationships, hyperbolic function tables, skin effect, and physical constants.

"ELECTRICAL ENGINEERING—PROBLEMS AND THEIR SOLUTIONS" by T. F. Wall. Published by Chemical Publishing Co., Inc., Brooklyn, New York. 307 pages. Price \$5.00.

In this companion volume to "*Principles of Electrical Engineering*" the author has extended the subject by a practical discussion of actual engineering problems and how they may best be solved.

A detailed, step-by-step description of problems covering the whole field of applied electricity and magnetism has been presented and then the author has carefully laid the foundation for the correct solution of the individual problem.

Each chapter contains a series of problems which might be encountered by the electrical engineer. Directly following each of these problems is a complete technical solution to the problem including the necessary formulas, mathematics and test procedures to be followed.

The structure of the book follows closely the companion volume and the two texts should be used together to provide maximum coverage and comprehension of the subject under discussion.

Like the book, "*Principles of Electrical Engineering*," the student studying independently will require a good working background of mathematics before tackling this text.

-30-

SERVICE GROUPS

LAST month we published a fairly comprehensive list of radio servicemen's associations in the United States, Canada, and Scotland.

The names and officers of three additional organizations have been furnished this office. Please add these names to your listings.

Radio Servicemen's Assn. of Luzerne County; E. L. Manual, Sec'y., 183 Bradford Street, Wilkes-Barre, Pa.

Radio Servicemen's Assn. of Salisbury; Harry Cohen, 219 Highland Avenue, Salisbury, Md.

Detroit Radio Servicemen's Assn.; Mr. Buchart, 12019 Hamilton, Detroit, Mich.

We will welcome additions and corrections for these listings at any time.

December, 1947

"The Kit for
the Millions"

NO TECHNICAL KNOWLEDGE
REQUIRED FOR ASSEMBLY!



... Tops in *quality* ... Tops in *value*!

TELE-
VISION
KITS

BUILD YOUR OWN TELEVISION AND FM SETS

12" TELEVISION KITS—

Standard and DeLuxe Models

Picture size $1\frac{1}{2}$ times larger than with 10" tube . . . A big 75 square inch picture!

Sharp, steady picture achieved with advanced Transvision television circuit. Picture has remarkable brightness even in lighted room (no darkening of room is required). **IDEAL FOR HOME or COMMERCIAL INSTALLATIONS.**

12" TRANSVISION TELEVISION KIT . . . Standard Model . . . FEATURES: 12" picture tube . . . Picture size $1\frac{1}{2}$ times larger than with 10" tube . . . RF Unit designed for 13 channels: factory wired and pre-tuned for 7 channels (no areas have been assigned more than 7 channels; however if desired, up to 6 more channels may be added at very nominal cost) . . . 4 mc bandwidth for full picture definition . . . High fidelity F.M. sound reproduction . . . picture size 75 square inches . . . 9000 volts second anode potential for brightness and contrast . . . maximum picture sensitivity (better than 50 microvolts) . . . 22 tubes and 12" picture tube, antenna, lead-in wire, etc. Cabinet extra, if desired). **LIST \$289.00**

12" TRANSVISION TELEVISION KIT . . . DeLuxe Model with Superb Built-in F.M. RADIO. Same characteristics as the Standard Model, plus the following **ADDITIONAL FEATURES:**—50-216 mc continuous tuning . . . Covers the entire F.M. band and all 13 television channels . . . Cut-off switch eliminates unused tubes when set is used only as F.M. receiver . . . **LIST \$359.00**



12" KIT (Table Model)

ALL TRANSVISION KITS ARE COMPLETE—Nothing more to buy! . . . All Transvision Television Kits are **COMPLETE** with all tubes, including picture tube, wired and pre-tuned RF units and IF's, high gain folded di-pole antenna with 60 ft. lead-in cable, wire and solder.

TRANSVISION TELEVISION CABINETS . . .

Beautiful, sturdily built cabinets with handsome rubbed wood finish. Fully drilled.

12" Table Model Cabinet. **LIST \$44.50**

12" Console Cabinet with compartment for record changer **LIST 74.50**


7" Table Model Cabinet. **32.50**

Other TRANSVISION Television and F.M. Radio values described in our advertisement this issue.

TRANSVISION ALL-CHANNEL R. F. UNIT

FACTORY PRE-WIRED and TUNED . . . For use in Building your own custom-made television receiver . . . for any 7", 10", 12", 15", or 20" Kit.

Transvision all-channel R.F. unit is factory pre-wired and tuned for 7 channels* (covers all channels in lower and higher bands in any single area operating presently or in the future). Average sensitivity 20 microvolts; has R.F. stage before oscillator; complete with 3 tubes; 1-6AK5, 1-6AK6, 1-6C4; input impedance—300 ohms, balanced to ground. Size— $9\frac{1}{2}$ " deep, $4\frac{1}{2}$ " high, 6" wide. *NOTE: No single area is scheduled for more than 7 channels. However, 6 more channels can be added to this unit, if desired, at nominal factory cost. It is not expected that these additional 6 channels will be required for several years. . . . **LIST \$37.95**

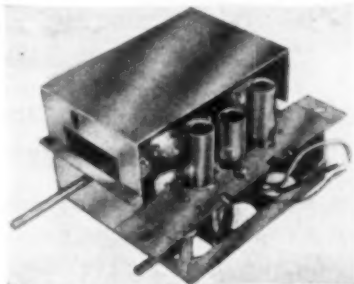

ALL-CHANNEL R-F UNIT

TRANSVISION FEATHERWEIGHT SOLDERING IRON

NOTE THESE NEW, REMARKABLE FEATURES: Weighs only 3 ounces (without the cord) . . . Delivers working output of 200 watt iron at fraction of current normally consumed by heavier irons . . . Heats up in 20 seconds . . . Finger-tip button control . . . Cool grip . . . Retains heat (with switch off) up to one minute . . . Featherweight permits long periods of soldering without fatigue . . . Economical—Intermittent control feature prevents tip corrosion and necessity of frequent cleaning . . . Long, thin tip permits soldering in tight corners . . . Tips are interchangeable to suit work at hand . . . For operation on 110V, AC, 60 cycles. Complete with 6 volt transformer. . . . **LIST \$13.95**



Featherweight Soldering Iron

All prices listed above are 5% additional west of the Mississippi. All prices are fair traded.

See your local distributor or for further information write to Dept. R.N.—



TRANSVISION, INC.

385 NORTH AVE., NEW ROCHELLE, N. Y.

IT'S HERE!

TRANSVISION

12" TELEVISION KIT



This 12" television kit is tops in television. Set, less cabinet.....

\$289.00

For this low cost you get a kit complete with 22 tubes, 12" picture tube, specially designed dipole antenna with 60 ft. of lead-in wire. Nothing more to buy. Easy-to-follow instructions come with each set. No tools or skills necessary.

De luxe with continuous tuning including FM Broadcasting reception.. **\$359.00**


Table model cabinet in walnut finish for 12" model **\$44.95**

Console model in walnut finish for 12" model **\$74.50**

Same kit with approximately 50% larger picture. Uses 15" C.R. tube, additional **\$75.00**

25% with order, balance C.O.D.

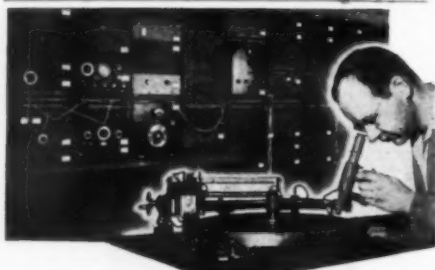TELETRONICS SERVICE AND SUPPLY CORP.
264 WEST 40TH STREET NEW YORK 18, N. Y.
Phone PE nnsylvania 6-8730



School of SOUND RECORDING and TRANSMISSION ENGINEERING

Learn sound recording and transmission engineering techniques of the professionals, as used in Motion Picture, Broadcast, F-M, Television, and Commercial Recording Studios.

A nine months practical engineering course, devoted exclusively to the technique of sound recording and transmission measurements. Well equipped studios, professional recorders and circuit laboratory containing latest model test equipment installed for student training. A portion of our laboratory is pictured above.

● New classes admitted the first School day of Jan., Apr., July, Oct.
Affiliated with the Don Martin School of Radio Arts
Approved for Veterans



H.M. Tremaine
Director

Write for Literature • Sound Department
Don Martin SCHOOL of RADIO ARTS
1655 Cherokee • Hollywood 28, California

166

Manufacturers' Literature

Readers are asked to write directly to the manufacturer for the literature. By mentioning RADIO NEWS, the issue and page, and enclosing the proper amount, when indicated, delay will be prevented.

MARINE RADAR BOOKLET

Installation views of radar equipment and actual radar scope photographs taken at strategic points in Chesapeake Bay, the Great Lakes, and the Neches River near Port Arthur, Texas are included in a new booklet on marine radar just issued by *Westinghouse Electric Corporation*.

The booklet explains how radar enables the navigator to see through "blind" weather, at distances from 100 yards to 32 miles. Sketches show how two developments, the two degree beam and the .3 microsecond pulse of the transmitted radar signal, improve bearings and range resolution.

Copies of booklet B-3845-A may be secured from the *Westinghouse Electric Corporation*, P.O. Box 868, Pittsburgh 30, Pennsylvania.

CATALOGUE SHEET

Telegraph Apparatus Co. of Chicago is now offering a new catalogue sheet describing the company's line of plugs, jacks, connectors, prods, and clips.

Complete specification and prices for these units is given.

A copy of the catalogue sheet, along with the newly revised price list, will be forwarded upon request to *Telegraph Apparatus Co.*, 412 South Green Street, Chicago 7, Illinois.

SHEET MICA PRODUCTS

A new price list and discount sheet covering compressed sheet mica products has just been released by *The Macallen Company* of Boston.

Included in the listing are India plate, amber plate, flexible plate, mica paper, mica cloth, mica and fish paper, mica and rope paper, mica and cellophane, India heater plate, amber heater plate, mica and fiberglass combinations, mica tape, mica fiberglass tape, mica tubing, mica V rings, and mica commutator rings.

A copy of this new listing is available from *The Macallen Company*, 16 Macallen Street, Boston, Massachusetts.

SPEAKER CATALOGUE

The company's complete line of loudspeakers is illustrated and described in the new catalogue, No. 1010, recently issued by *Jensen Manufacturing Company* of Chicago.

The 24-page catalogue, which contains useful information and data, is arranged by groups to facilitate reference. Included in the listing are the company's Standard Series, Concert Series, Extended Range Single-Radiator Series, Coaxial Series, Bass Reflex

Reproducers and Cabinets, and the Professional Series.

Three pages of the catalogue are devoted to a listing of impedance matching transformers in both fixed and adjustable impedance designs. A comparison chart has been included showing all *Jensen* models in their relative gap energy levels. Each band of gap energy is separated from the next by 1.5 db.

Copies of *Jensen* catalogue No. 1010 are obtainable from any company distributor or from *Jensen Manufacturing Company*, 6601 S. Laramie Avenue, Chicago 38, Illinois.

REFERENCE CHART

A handy, vest pocket reference chart containing special sales features for the complete *Stromberg-Carlson* radio line is now available to authorized dealers for use by their floor salesmen.

Features of each set in the line are listed, along with selling points for freshman salesmen.

Copies of this chart may be secured from *Stromberg-Carlson* distributors.

RADIO KITS

Eagle Electronics, Inc. of Irvington, New York, have published a new bulletin covering their line of "Pict-O-Graph" radio kits.

Included in the bulletin is information about the company's 1, 2, 3, and 4-tube a.c.-d.c. regenerative receivers, two 5-tube superheterodynes, a 4-tube t.r.f. receiver, a code practice audio oscillator, 3-tube and 4-tube amplifiers, wireless phono oscillator, crystal radio, and v.t.v.m.

A special constructional technique has been incorporated in the instruction manuals which accompany each kit.

A copy of this bulletin may be secured by writing *Eagle Electronics, Inc.*, Irvington, New York.

A.S.A. PRICE LIST

American Standards Association has issued a new price list covering available standards on civil engineering and construction, mechanical engineering, electrical engineering, automotive, transportation, ferrous materials and metallurgy, non-ferrous materials and metallurgy, rubber, etc.

This new listing is available free of charge from *American Standards Association*, 70 East 45th Street, New York 17, New York.

IRC DISPLAY

International Resistance Company of Philadelphia has developed a novel

RADIO NEWS

and colorful display piece for the merchandising of their volume control cabinets and resistor assortment kits.

The display is specially designed for adaptability to most space requirements on the counter or in the window. It is constructed in three sections which are easily erected and can be used individually or as a unit.

Displays are available to *International Resistance Company's* distributors who should contact the company at 401 North Broad Street, Philadelphia 8, Pa.

SALES AID FOLDER

A new sales aid folder, illustrating and describing the complete line of promotional pieces and displays prepared for the radio dealer and serviceman, has just been issued by the *RCA Tube Department*.

This handy catalogue, from which the radio dealer and serviceman can select store display material or mailing pieces, or otherwise plan a complete business getting program, describes 32 separate items ranging from counter to window displays to mats for newspaper advertising.

The folder is available free of charge from *RCA* distributors.

CRYSTAL DATA

Technical data covering twelve widely used crystal types is given in the new Bulletin No. 201 just issued by *Premier Crystal Laboratories, Inc.*

This four-page bulletin is profusely illustrated with photographs and drawings and includes specifications of crystal characteristics, frequency ranges, construction features, and physical dimensions. Information on supersonic crystal blanks and hints on ordering are also given.

Bulletin No. 201 may be secured by writing *Premier Crystal Laboratories, Inc.*, 57-67 Park Row, New York 7, New York.

SPECIALIZED EQUIPMENT

Of particular interest to manufacturers, testing and research laboratories is the new 43-page booklet "Specialized Testing and Measuring Equipment Catalogue" just issued by the *Apparatus Department of General Electric Company*.

The contents of the catalogue have been broken down into eleven sections with each individual section being devoted to a particular type of equipment. Covered are magnetic equipment; time, speed, and torque measuring equipment; force, strain, and thickness gauges; color, light, and spectro equipment; chemical analysis equipment; resistance and insulation testing equipment; materials testing equipment; vibration, sound, and balancing equipment; vacuum and pressure measuring units; electric circuit testing devices; and miscellaneous test units.

Applications for copies of this catalogue should be made to the *Apparatus Department, General Electric Company*, Schenectady, N. Y. -30-

December, 1947


make **henry**

your **hallicrafters**

headquarters

COMPLETE STOCKS

Henry has everything in the ham field

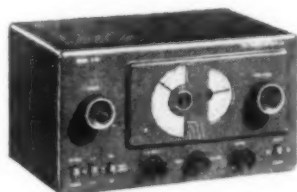

S-38 Biggest little buy on the market. Frequency range: 540 kc to 32 Mc in 4 bands. Separate electrical bandspread dial. CW pitch control adjustable from front panel, automatic noise limiter. Self-contained PM dynamic speaker . . . **\$47.50**



SX-43 Hottest ham performance ever at this price. All essential ham frequencies from 540 kc to 108 Mc. In the band of 44 to 55 Mc, wide band FM or narrow band AM, just right for narrow band FM reception is provided . . . **\$169.50**



SX-42 Greatest continuous frequency coverage of any communications receiver—from 540 kc to 110 Mc. Six bands; AM, FM, CW. Combines in one superb unit a top-flight standard and VHF communications receiver; standard short wave and FM broadcast receiver. Finest Halli-crafters equipment **\$275.00**

TRADE-INS

You can't beat Bob Henry for trade-ins. Write, wire or phone today about your equipment and Bob Henry will make you a better offer than you can get anywhere else.

TIME PAYMENTS


Because Bob Henry finances the terms himself you get a better break. Save time and money, deal with Bob Henry on his personal, profitable time payment plan.

BUTLER
MISSOURI

HENRY RADIO STORES

11240 Olympic Blvd
LOS ANGELES 25
CALIF.

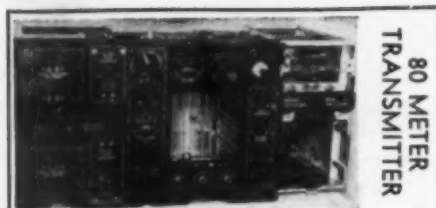"World's Largest Distributor of Short Wave Receivers"



80 METER
TRANSMITTER


Type BC-653-A, 2 to 4.5 Mc, 100 watts cw, 22 1/2 watts phone. Tubes include 1613 MO, 807 buffer, two 814's in parallel for PA, 1613 modulator. Gov't cost \$1227. Your last chance to get this fine set at such a ridiculous price. BRAND NEW w/tubes & diagram, less dynamotor...\$29.00; w/o tubes...\$15.00

PORTABLE FIELD TELEPHONE EE-8

With handset, generator, ringer, etc., in leather or heavy web case (please do not specify). Requires 2 flashlight cells. Fine for garage extension, farm phones, warehouses, etc. For local or common battery lines.

NEW, ea...\$15.95
two for \$31.00
GOOD USED...\$9.95
ea., two for \$19.00
USED, FAIR...\$6.95
ea., two for \$13.00

HIGH QUALITY SPEED KEY...\$5.85

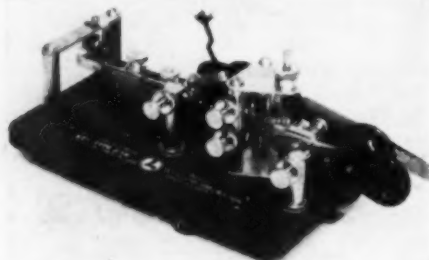

MONEY-BACK GUARANTEE If you are not well pleased with this fine key made by Licon on the pattern made famous by a well-known speed key mfr. Army J-36. BRAND NEW IN ORIGINAL BOXES, four for \$23; each...\$5.85
Very slightly used, perfect...4.45

SPECIALS THIS MONTH (Dec. only)

TUBES: 6DS-40c; 6HG-35c; 884-55c. NEW, in orig. cartons.
ATTENUATOR. Daven T-800; "T" network; 10 steps 0.5 db per step, 50,000 ohms Z plus or minus 5%; Linear; shaft 1/4"x15/16"...\$2.95

FM TRANSMITTER-RECEIVER



Altimeter type RT-7/APN-1, freq 418-462 Mc FM; with 14 tubes; 3-12SH7, 4-12SH7, 2-12H6, 1-VR150, 2-955, 2-9004, 27V dyn., diag.; easily converted to communications; as shown, still a few left. BRAND NEW, \$8.88; or GOOD, USED...\$6.88

REMOTE CONTROL UNITS

RM-12 (left): good for commercial or amateur stations. Has handset, ringer, generator, Weston 301 (or equiv) db meter. Contains KE-8 'phone. Used...\$14.95
RM-13: same as above but includes 115 V 60 cps power supply, one tube amplifier w/2 tubes. Used...\$12.95
RM-20 (right): like KE-8 telephone but in metal case 9 1/2"x6"x5" Includes generator, ringer, coil; no handset. Used...\$4.95



HORN - SQUAWKER. 115 V A.C. 5 1/2"x3 1/2"x4 1/2", weather-proof case, Navy type...\$4.85
LOADING COIL. w/3 sliding taps, 35 turns #14 wire on 20c form 8 1/4"x4"d...\$2.95

ATTENUATOR. Daven T-800; "T" Network; 10 steps 0.5 db per step, 50,000 ohms Z plus or minus 5%; Linear; shaft 1/4"x15/16"...\$2.95
INVERTER. PP-68/U; Input 6 or 12 VDC, output 115 V 60 cps, 15-50 watts; 884"x884"x934"; UN. USED, GOOD...\$12.95
TRANSFORMERS. Filament: 4 v @ 10 a, 2.5 v @ 1.75 a, 300, 115V shielded...\$1.88
SCOPE. 4000 vrms @ 10 ma using 2X2, 300, 115V shielded...\$3.88

Postage extra. Minimum order \$2.00. FREE LIST.
TERMS: Net cash, 25% deposit on C.O.D.'s.

ELECTRONIC SUPPLIES

317-R East 2nd St. Tulsa 3, Okla.

NEW MINIATURE, SUPER POWERED FILAMENT POWER SUPPLY

BY BOB GUNDERSON, W2JJO

ONE of the outstanding battery developments is the new line of "Vitamite" miniature lightweight storage batteries. These batteries are secondary, or rechargeable, (lead acid) type cells. They are durable, leakproof, and non-spill as there is no free-flowing electrolyte within the batteries.

A photograph of the "Vitamite" Flyweight Battery, Model 2A0.45 is shown in Fig. 1. This battery weighs one ounce, measures 9/16"x7/8"x1 13/16" and delivers an open circuit voltage of 2.2 volts, with short circuit current of better than 10 amperes. When fully charged, the battery can deliver in excess of 250 ma. for approximately 1.5 hours. At a discharge rate of 200 ma., the battery will run in excess of two hours to an end voltage of 1.7 volts, with corresponding increases in life at 100, 60, and 50 ma.

For the amateur, this 2 volt cell lends itself nicely to small battery-powered transmitters and receivers using miniature and subminiature tubes, to field strength meters, to heterodyne monitors, etc. Tubes having two volt filaments, such as the 19, 30, 31, 32, 33, 34, 1B5, 1F5, 1J5, 1J6, etc. are quite satisfactory types for use in numerous kinds of equipment. Tubes in the 1.4 volt classification such as types 1A7, 1N5, 1H5, 1C5, 1Q5, 1A5, 1T5 3Q4, 3Q5, 3S4, 1S4, 1S5, 1T4, 1R5, and many others may be used, with appropriate values of dropping resistance. Incidentally, the writer has used this dropping resistor as a means of providing "C" bias voltage for equipment. The 1.4 volt filament type acorn tubes, such as the 957, 958 and 959 are also applicable for amateur and experimental applications.

In addition, the new subminiature line of tubes introduced a short time ago, will meet many of these applications. A list of the most popular of these tubes is given below, and operating data can be obtained from tube manuals. The design of circuits with which such tubes can be used may be left to the amateur himself.

CK502AX, CK503AX, CK505AX, CK506AX, CK507AX, CK510AX, CK512AX, CK518AX, CK520AX, CK521AX, CK522AX, CK556AX, CK568AX, CK569AX, 2E31, 2E32, 2E35, 2E36, 2E41, 2E42, 2G21, 2G22.

The "Vitamite" Bantamweight Battery, Model 4A0.90, delivers 4.4 volts, open circuit, and has two lead acid cells, each twice the size of the Flyweight series. The battery measures 1 3/16"x3 3/16"x1 7/16", and weighs 4 1/2 ounces. A pair of floats built within the battery provide a means for visually checking the condition of the battery at all times. At a discharge current of 250 ma., the battery will supply this current for 3.5 hours, to an end voltage of 1.7 volts per cell (3.4 volts). This unit can well serve in the above mentioned circuits and in test equipment such as the common multimeter.

Owners of the Flyweight or Bantamweight Batteries may purchase ready-made charging equipment. However, a




Fig. 1.

variety of methods for charging these batteries is possible. The simplest method is to charge these batteries from the standard automobile battery, as shown in Fig. 2A. The series resistor R₁ may be a fixed or variable resistor, or may be made up with one or more pilot lamps, depending upon the type of bulb available in the amateur's "junk box." The charging rate for the Flyweight should not exceed 140 ma., and at this current rate, the charging time is from eight to ten hours. The charging current for the Bantamweight should not exceed 250 ma., with the same charging time. Lower charging currents result in less gassing and, therefore, distilled water need not be added as often. Also a lower charging rate results in a more uniform chemical action, which gives longer battery life.

The most satisfactory method for charging these batteries, however, is illustrated in Fig. 2B. The transformer is a common six-volt filament transformer which can deliver at least .5 amperes. The rectifier can be either copper oxide or selenium oxide. In this particular charger the rectifier is a single selenium plate. The value of the series resistor will depend upon the type of battery, together with the particular type of rectifier, and the value of the line voltage.


-30-

Fig. 2.

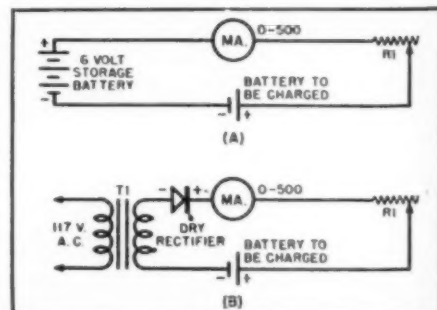

**NAVY-CRV-46151
AIRCRAFT
RADIO
RECEIVER**


INCLUDING
CASE
\$16.50

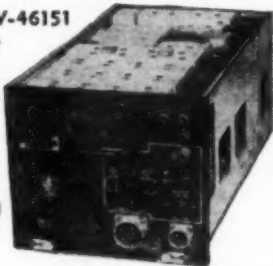

Four bands, including broadcast (195-9,050 KC). Circuit is six-tube superheterodyne with mechanical band change or remote operated electrical band change. Remote band change and tuning controls included, making this set readily adaptable to mobile ham use. Powered from self-contained 24 V. DC dynamotor.


The sets are complete with tubes, mounting rack and remote controls. No cables.

**ARC-4 TRANSMITTER
AND RECEIVER**

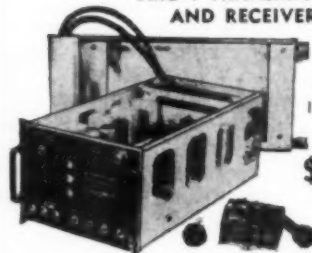

INCLUDING
CASE
\$19.75

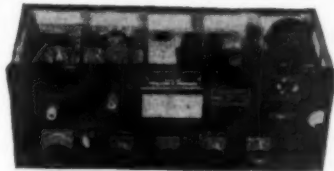
Operates on any of its 4 predetermined crystal controlled frequencies in the range of 140 MC. Complete with tubes, remote control, junction box, shock mounting base and connecting plugs. This unit is ideal for amateur UHF or mobile telephone. Operates from self-contained 24 V. DC dynamotor. 12 V. available upon request.



RADIO ALTIMETER APN/1

A complete 460 mc. radio receiver and transmitter which can be converted for ham or commercial use. Tubes used and included: 4-125H7, 3-125J7, 2-6H6 1-VR150, 2-955, 2-9004. Other components such as relays, 24 V. dynamotor, transformers, pots, condensers, etc., make this a buy on which you can not go wrong. Complete as shown in aluminum case 18" x 7" x 7 1/4".

\$8.95

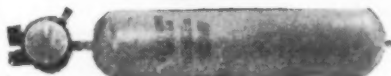

OXYGEN TANKS

These oxygen tanks, removed from surplus aircraft, have a capacity of 500 lbs. pressure. Type D2, with complete regulator assembly. Size of tank 22" x 5".

\$8.95

TERMS: CASH WITH ORDER
F.O.B. Indianapolis, Ind.

**AMERICAN SURPLUS
PRODUCTS CO.**

537 N. CAPITOL AVE.
INDIANAPOLIS, IND.

**NEW WILLARD RECHARGEABLE
STORAGE BATTERY**



New 6 Volt battery in spill-proof clear plastic case, housed in metal case for easy mounting. Applicable for a wide range of uses where battery power is needed. Shipped dry. Uses standard battery electrolyte, available everywhere.

Price, each.....\$4.00
In lots of ten, each.....\$3.35
Without metal case, each.....\$3.00
In lots of ten, each.....\$2.85

**Brand New SCR-625
MINE DETECTOR**

**ATTENTION, PROSPECTORS, MINERS,
OIL COMPANIES, PLUMBERS, ETC.**

Metallic Objects Only

Used by the Army to detect buried metallic mines its private use suggests the location of underground or underwater pipes, cables and ore-bearing rock, the location of metallic fragments in scrap materials, logs, etc., and the screening of personnel in plants for carrying of metallic objects.

New, complete in original overseas packing container. Originally sold by War Assets for \$165.00. The U. S. Forestry Service has recommended procedure for using the SCR-625 Mine Detector to find concealed metal in tree logs and other timber products.]

\$55.00

MELVILLE

RADIO INSTITUTE
Outstanding PRE-WAR Technical
Training Center for

TELEVISION & RADIO

Under the personal direction of Frank Melville, former Airlines, Merchant Marine, and Broadcast technician, you may soon qualify as:

- RADIO TECHNICIAN
- AIRLINES RADIO OFFICER
- PT. TO PT. TELEGRAPHER
- RADIO AMATEUR
- MERCHANT-MARINE RADIO OFFICER
- TELEVISION TECHNICIAN
- HOME RECEIVER REPAIRMAN
- VISUAL TELEGRAPH OPR. (SLIP TAPE)

MELVILLE RADIO INSTITUTE believes vocational training means vocational training. Thus we, like many radio schools, teach ample theory. But, unlike most schools, two-thirds of our technical students' time is spent in laboratories and shops, where, with superior equipment, they learn by doing — not memorizing.

FREE employment service is available to all MELVILLE graduates.

Visit the 10-story MELVILLE Building today as our guest and observe the school in operation.

Day and evening classes approved for veterans. Licensed by the State of New York.

MELVILLE RADIO INSTITUTE

Melville Building
15 West 46th St., N. Y. 19 • BRyant 9-5080

MAIL THIS COUPON NOW!

MELVILLE RADIO INSTITUTE R.N.
Melville Building
15 West 46th St., New York 19, N. Y.

Gentlemen: Send me Free Information about your school.

Name _____

Address _____

SENSATIONAL OFFERING

**Never Before
Never Again...
SUCH VALUE
at this price!**

We cannot replace this instrument at this price. Therefore, it's first come, first served. Please send check or money order. C.O.D.'s filled only if deposit of \$5.00 accompanies order.

\$29⁹⁵

REG.
PRICE

~~\$59.50~~



**ELECTRONIC VOLTMETER
OHMMETER**

A special "buy" makes this offer possible. This famous meter gives constant accuracy and guaranteed performance. Stable bridge circuit type. Hand calibration. Acid etched panel. 500 micro-amp Simpson meter. Reversal switch for positive or negative indication. Resistor in DC probe permits read-

ings in signal carrying circuits. Meter Ranges DC 0-3; 0-30; 0-150; 0-300; 0-600. AC 0-3; 0-30; 0-150; 0-300. Ohms 0-1000; 0-10M; 0-100M; 0-1 Meg.; 0-100 Meg. In original cartons. 1 pair test leads and 1 DC probe included. Complete instructions and diagram.

RADIO DISTRIBUTING COMPANY

140 SOUTH SECOND STREET • HARRISBURG • PENNA.


★ USE
A

KILOVOLT

HIGH
VOLTAGE

POWER
SUPPLY

for
TELEVISION

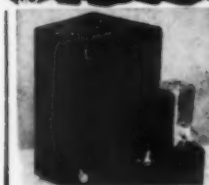

Model 6
4000-6000 VOLTS D.C.
FILTERED & SHIELDED
* IT'S SAFE. No 60 cycle a.c.
means no dangerous high ca-
pacity condensers.

* Does a PERFECT JOB with
the 7GP4; the new, brighter
7JP4; the just out 10" electro-
static tubes.
* GUARANTEED 3 months.

* ECONOMICAL. Compare
cost of transformer, filter con-
densers, recti-
fier and insula-
tion.

\$17⁹⁵


C-B MFG. CO., 412 W. 37 St., N. Y. 18, N. Y.

Experimental Work? Development and Design?

Eliminate Your Resistance Guesswork with LECTROHM ADJUSTABLE RESISTORS

They're ideal for unknown or variable resistances... as potentiometers and voltage dividers. Durable vitreous enamel coating... accurately spaced winding of low temperature coefficient resistance wire... low loss ceramic cores... silver soldered connections—these are quality features built into every Lectrohm Adjustable Resistor.

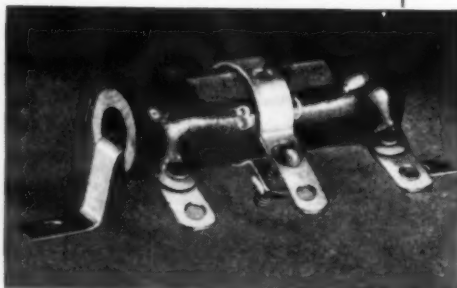Complete range of carefully rated styles from 1 to 100,000 ohms and from 10 to 200 watts. One adjusting lug supplied with each resistor. All standard sizes and ratings available for immediate delivery.



LECTROHM
INCORPORATED

5131 West 25th Street, Cicero 50, Illinois
Division of National Lock Washer Co.
Newark, N. J.

Write for
Lectrohm
Catalog
—It's Yours.



Television Tubes

(Continued from page 42)

revealed in 1932 by Bernard Schmidt, a research assistant in a German laboratory. At that time astronomical photography was unsatisfactory, due to spherical aberrations caused by the mirror used to reflect light from the stars and planets to the camera. By placing a "correcting lens" (corrector plate) between the mirror and the camera, Schmidt discovered that he obtained much clearer pictures. These plates, however, had to be ground by hand, and prior to the war there were only a few in existence because of the extreme difficulty of their manufacture. During the war, American scientists developed a new method for mass producing these "corrector plates" which were used in infrared viewing devices. Now, tens of thousands of these plates, embodying the same technique are being used for television reception. They are made by heating a flat piece of glass until it flows into the specially curved surface of a refractory on which the glass is placed. This mold is made of special composition that does not adhere to the glass and yet permits it to assume the desired curvature. One side of the glass is then ground and polished to a plane surface.

The mirror is aluminized in such a way that the reflectivity will be as high as possible. The problem of aluminizing large surfaces and producing an aluminum surface of the required durability was not simple, but it was solved.

Another contribution to the development of television receiving sets was the result of a war-time invention for producing glareless glass. This process makes possible the reception of clearer, sharper television pictures. The successful removal of light-consuming reflections from a television tube's glass face, which serves as the screen of a direct-viewing home television receiver, has been obtained through a new glare-removal technique which also produces images of greater clarity when applied to the optical system of the projection type. The technique was developed during the war to increase the efficiency of such military optical instruments as binoculars which gained over 60 per-cent in light transmission when reflections were reduced. Reflections are removed by directly coating the face of the television tube with a secret chemical composition. It is not necessary to disassemble the tube for the coating process or to apply the coating in the vacuum chambers used in earlier glare-removing techniques.

The coating improves the reception of television pictures by: (1) Reducing reflections in the glass face of the tube caused by light sources in the room housing the receiver. (2) Reducing the intensity of false images

RADIO NEWS

caused by reflections from the outer surface of the image-producing fluorescent screen in the tube, thus increasing the sharpness of the images. (3) *Reducing light losses* from reflections, thus increasing the amount of light transmitted.

It is a tribute to glass craftsmen, machine designers, optical technicians, skilled operators, and electronic engineers that these relatively high temperatures, automatic operations, accurate optical amplification, and extreme electronic sensitivity can be used effectively in such narrow confines as the interior of television tubes—the iconoscope and the kinescope—an accomplishment which has been due to the efforts of these men of vision and skill working in close cooperation.

-30-

Traffic Transmitter


(Continued from page 47)

nearly as great as the output obtained when operating "straight through" on 80.

The tuning of the amplifier tank will be somewhat different from the usual, and the following procedure is recommended:

1. Disable the 807 by removing the plate cap and, with the key closed, resonate the oscillator plate tank by using a neon bulb or a pickup loop and a pilot lamp.
2. Set the output condenser C_{11} to maximum capacity, and replace the plate cap on the 807.
3. Apply all voltages by pressing the key, and rapidly rotate the condenser C_{11} until resonance is reached. This will be indicated by a sharp dip in the reading of the plate milliammeter.
4. If the meter reading attained in step 3 is less than 80 mils, which will probably be the case, slowly decrease the capacity of the condenser C_{11} , all the while maintaining the plate current at a minimum by rotating the condenser C_{12} in the opposite direction. It will be noted during this procedure that the "minimum" plate current will steadily increase. Continue this procedure until the indicated current is about 80 milliamperes.
5. Retouch the tuning of the condenser C_8 for maximum reading of the meter.

Fig. 2. Calibration curve.

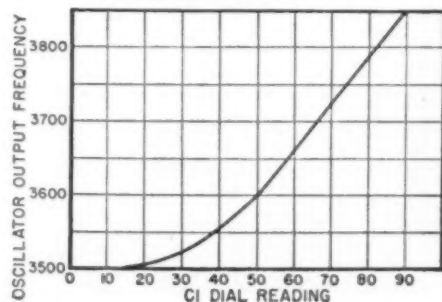

December, 1947



Maybe the Next Generation Will Just Love to Practice

It's only a wild dream now, of course, but perhaps science will be able to do something about Youth's greatest burden—learning to play the piano.

Marvels are being accomplished by electronics. And wherever you find applied electronics—or electric circuits of any kind—there is a place for Cannon Plugs.

For Cannon Plugs make circuits flexible—easy to install, change, repair. Cannon Plugs make electric contacts positive and firm—disconnects quick and simple. See what Cannon Plugs can do for your equipment. Write for Cannon Condensed Catalog.

Here's a clever number, picked at random from the Cannon Catalog—a cord plug with socket insert and cable clamp, (Type AP-CG-15), to be had in 2 to 8 contacts. A removable cap makes it easy to install. Interesting? Why not learn the whole story? Send for the Type AP Bulletin showing the various standard fittings in this series.



CANNON ELECTRIC DEVELOPMENT COMPANY

3209 Humboldt Street, Los Angeles 31, California

Canada & British Empire—Cannon Electric Co., Ltd., Toronto, Ontario • World Export Agents (excepting British Empire) Frazor & Hansen, 301 Clay St., San Francisco 11, Calif.

RADIO, TELEVISION PHONOGRAPH, ELECTRICAL SERVICING? EXPERIMENTING? BUILDING A SET?

Then this big, value-packed
**GOVERNMENT SURPLUS
RADIO PARTS KIT**

... is your once-in-a-lifetime bargain!

A "natural" for the "ham"!



IMAGINE ...

158 valuable radio parts you need every day! Every kit contains two coaxial switch units complete with 24 volt motors—worth much more than our price for the entire kit! It's the spare parts gold-mine you always wished you had—now available at a sensational bargain price.

HERE'S WHAT YOU GET:

- 2 COAXIAL SWITCH UNITS WITH 24 V. MOTORS
- 2 AEROVOX .01 MFD—5000 V. Oil Condensers
- 2 AEROVOX .02 MFD—8000 V. Oil Condensers
- 1 AEROVOX .1 MFD—3000 V. Oil Condenser
- 2 1-1 MFD—600 V. Oil Condensers
- 1 Dual 8-5 MFD Oil Condenser
- 1 80 MA. Filter Choke
- 1 .1—500 V. Oil Condenser
- 1 .02—600 V. Oil Filled Tubular
- 1 .01—600 V. Oil Filled Tubular
- 1 .05—600 V. Oil Filled Tubular
- 1 .1—600 V. Oil Filled Tubular
- 2 .1—1000 V. Oil Filled Tubular
- 4 20,000 ohm Volume Control W.W.
- 1 2000 ohm Volume Control W.W.
- 1 5000 ohm Volume Control W.W.
- 2 100,000 ohm Volume Controls
- 2 250,000 ohm Volume Controls
- 1 2-deck Wave Band Switch
- 1 Noise Filter Choke
- 2 IRC Candohm Resistors
- 1 Fast .01—600 V. Oil Condenser
- 1 1MH R.F. Choke
- 4 Insulated Grid Slips
- 1 IRC 25w. Adj. Resist.

—PLUS wire wound resistors, carbon resistors, acorn grid clips, screws, lock washers, nuts, mica condensers, pilot lamps, ceramicons, motor brushes and many other useful items.

Entire kit
sensationally
priced at **\$12.95** f.o.b. New York City
shipping wgt. 24 lbs.

Order yours **TODAY**—stocks are
extremely limited

Check our ad every month for unusual values in radio, television, phonograph and electrical parts and supplies bearing America's most famous trade-marks. Don't miss our monthly AUDIVIEW Super Value. Write for our big, value-packed 1948 catalogue, available soon.

**AUDIVIEW
RADIO PARTS CO.**
325 Canal St., New York 13, N. Y.

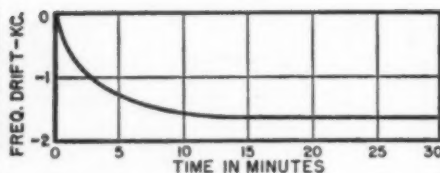


Fig. 3. Frequency drift vs. time. Curve shows that drift is negligible after the first five minutes of operation.

In tuning the condenser C_1 over the range of the 80 meter band it will be found that it will be necessary, in the average installation, to retouch only the condenser C_{12} for minimum plate current at each desired output frequency. The tuning of the oscillator plate tank condenser C_2 is broad enough to permit the oscillator to "put out" over the entire band.

For forty meter operation it will be found that closing the switch S_2 and repeating the steps 2 to 5 will provide output at the desired frequency. In each case the use of an absorption wavemeter coupled to the output inductor is recommended in order to ensure that the output circuit is tuned to the desired band.

Upon completion, it was decided to make qualitative measurements of the amount of drift of the oscillator as it was allowed to run continuously. The resultant graph of drift vs. time is illustrated in Fig. 3, and it will be obvious that the drift is negligible after the first five minutes of operation.

The operator will find that the transmitter described herein really is "what the doctor ordered" for traffic work, and will also find that this really flexible rig is hard to beat in contests and the like when the ability to QSY rapidly to the frequency of a calling station, and the snappy break-in permitted by the keyed oscillator really pays off.


The author wishes to express his thanks to W2TYU who offered many helpful criticisms of the output signal at various times during the development of preliminary models. —50—

TAPE GLASS DIAL COVERS

CERTAIN radios use a glass cover over the dial as in the case illustrated.

The glass often becomes chipped under the holding clamps so that it is free to vibrate at some frequencies and make an annoying sound.

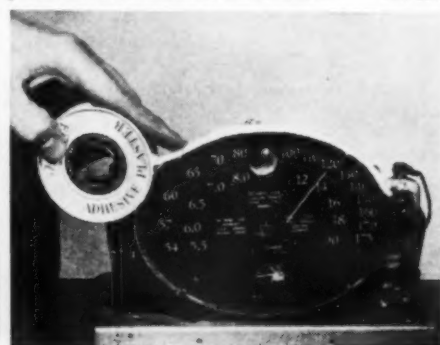Adhesive tape applied around the edge of the dial will keep the glass in place and eliminate the noise. H. L.



A CAREER WITH A FUTURE! TELEVISION

Shop Work . Shop Techniques . Theory
FULLY EQUIPPED LABORATORIES

- RADIO SERVICE & REPAIR
- F. M. & TELEVISION
- TRANSMITTER COURSES
Preparing for F.C.C. LICENSES
- RADIO TECHNOLOGY
A Junior College Level Course preparing for positions in Radio-Electronic Engineering Field.

Morning • Afternoon • Evening Classes
MODERATE RATES • INSTALLMENTS

Available Under G. I. Bill

Come In and See Our Students at Work

DELEHANTY SCHOOL OF
RADIO • ELECTRONICS • TELEVISION
105 East 13 St., N. Y. 3, N. Y. • Dept. S.
LICENSED BY STATE OF NEW YORK



RECEIVING
TUBES

TRANSMITTING
TUBES

TEST EQUIPMENT—AERIALS—
ELECTRONIC SPECIALTIES

**STANDARD ELECTRONICS
DISTRIBUTING CO., INC.**
1457 Main Street Buffalo 8, N. Y.



SPECIAL VALUE

SELENIUM RECTIFIER

Save time, space and money.

1x1x7/8
Max. A. C. Input 130 volts.
Max. Inverse Volts 380.
Max. D. C. Output 100 milliamperes.

and many others.

JCP RECTIFIER

65 West 181st St.
New York 53, N. Y.

ONLY
85¢ ea.
Any Quantity

Are You Getting Our Flyers???

If not, PRINT your name and address on a penny postcard. It will mean dollars in the bank for you! Ask for our latest catalog and flyer.

RADIO EQUIPMENT CO.
377 E. Main St. Dept. RN Lexington, Kentucky
"YOUR FRIENDLY PARTS HOUSE"

RADIO ENGINEERING IN 27 MONTHS

Intensive, specialized course, including strong basis in mathematics and electrical engineering, advanced Radio Theory and Design. Modern laboratory. Low tuition. Self-help opportunities. Also 27-month courses in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. Gov't approved for G.I.'s. Enter Dec., March, June, Sept. Catalogue.

INDIANA TECHNICAL COLLEGE
9127 E. Washington Blvd., Fort Wayne 2, Ind.

RADIO NEWS

Practical Radio Course

(Continued from page 74)

tween the primary and secondary windings of the r.f. tuning transformer, the typical double-humped tuning characteristic illustrated at Fig. 4B results. This may be flattened and broadened somewhat (with attendant reduction in gain) as shown in Fig. 4C by shunting the windings with resistors of appropriate value.

Frequency Conversion

It is common practice to use a single local oscillator to beat the incoming frequency-modulated video signal and amplitude-modulated sound signal (which is 4.5 mc. higher in frequency) into a video r.f. signal and a sound i.f. signal respectively.

Frequency conversion of both the video and audio signals to the proper respective intermediate frequencies is accomplished in the frequency converter. The conventional pentagrid converter tubes that are successfully used in ordinary sound broadcast receivers are not satisfactory for television receivers because they are troubled by undesirable interaction between the signal and oscillator circuits at frequencies above about 60 mc. This results in considerable variation in the oscillator frequency and output voltage. The conventional triode-hexode converter is not completely satisfactory. Consequently, at this writing, television receivers employ a separate oscillator (usually a triode) and a pentode mixer as shown in Fig. 3. Use of a pentode mixer has the added advantage of generating only about $\frac{1}{4}$ as much noise as does a conventional pentagrid converter.

Since two separate signals (video and sound) having carrier frequencies which differ by the amount 4.5 mc. (see Fig. 2) are applied to the mixer, the signal of the local oscillator, beating with each, will produce in the plate circuit of the mixer tube two i.f. signals (video and sound) whose carrier frequencies also differ by 4.5 mc.

It is now standard practice to purposely have the oscillator frequency higher than both the video and sound r.f. carrier frequencies, with the result that, since the video r.f. carrier frequency is always 4.5 mc. lower than that of sound r.f. carrier (see Figs. 2 and 5A) the difference between the oscillator and sound r.f. carrier frequency is less than the difference between the oscillator and video r.f. carrier frequency. This is illustrated in Fig. 5B. Consequently, the frequency of the sound i.f. carrier will always be 4.5 mc. less (lower) than that of the video i.f. carrier. This is illustrated in Fig. 5B. Observe that the result of employing an oscillator frequency higher than that of either the video or sound r.f. carrier frequencies is to "invert" the frequency relation of the video and sound carriers when they are both translated to intermediate frequencies

December, 1947


STAHL "SEZ"!!

If It's Radio—Electrical—
Electronic Equipment—Parts—
Supplies—Sets—these
BARGAINS must interest you

Gaze at these Items & Values

ULTRA HIGH FREQUENCY TRANSMITTER AN/APTS


BRAND NEW

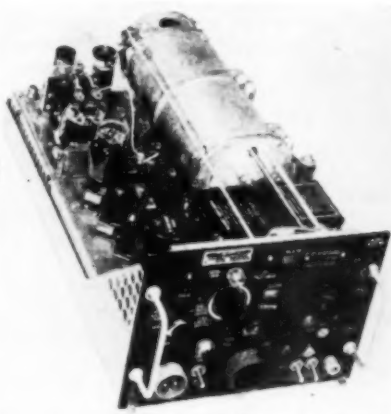

1500 Megacycle Transmitter, made for the U.S. Government, complete with the following tubes: 2—6AC7, 1—6L6, 2—829, 1—931A, 1—6AG7, 1—522 Ultra high frequency tube, complete with the Ultra High Frequency Cavity, 1—Blower to cool the 522, 1—time delay Relay, 2—Filament transformer condensers and many other component parts for Ultra High Frequency work. It has a frequency checker, complete Lecher Wires, with slider and a sensitive bulb for checking the wave length. The Lecher wires are so calibrated, that the setting of the slider may be read directly in Centimeters. Operates on 115 volt AC for filaments only. Does not include any plate supply. The tubes alone are worth many times more than what we are selling the complete Transmitter for. Each one is packed in original wooden case and contains instruction book. At this price, you cannot afford to miss this exceptional buy; Only..... \$11.95
Shipping weight 118 lbs.

INTERPHONE AMPLIFIER

BRAND NEW

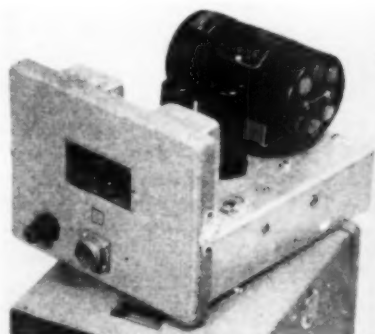


Beautifully constructed, in grey finish sturdy metal cabinet. Operates on 24 volt input, complete with dynamotor. Has 1—6V6 and 1—6SJ7 tube, volume control, carbon or magnetic microphone input. Fastened to sturdy resilient mounting on rubber. The case is worth the price. Only..... \$3.45

METERS

Westinghouse 2" bakelite case 0-150v AC \$3.25
Westinghouse 3" square 0-3 amp R.F. 3.00
Weston model 801—4" sq. 0-20 MH DC 4.75
Weston model 476—3" sq. voltmeter, 130v AC 4.95

ARMY AIR FORCE TRANSMITTER — RECEIVER

SCR-522—IDEAL 2 METER RIG

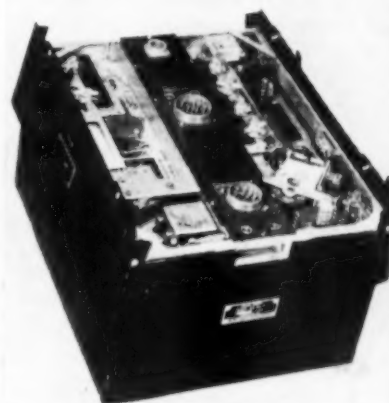


It's the best all around 100-156 Mc job. Crystal controlled, extremely sensitive superheterodyne; easily worked by anyone. 4 crystal controlled channels, push-pull operation. Receiver has 10 tubes—transmitter 7 tubes with 15 watt output. Can be easily converted to 110 volt, 60 cycle AC operation. Described in July C.Q. This wonderful buy comes complete with all tubes. Like new. \$14.50
All for only.....

6 TUBE Brand New Receiver with tubes, Only \$5.95

Receivers of the SCR-274-N (AN/ARC-5) Series. All-aluminum aircraft receivers 5" wide, 8" high, 12 1/2" long; weight 6 1/2 lbs. Typical tube line-up is: 12SK7 RF, 12K8 Converter, two 12SK7 IF's, 12SR7 Detector and BFO, 12A6 Output, gas-filled antenna-signal voltage limiter, and gas-filled output signal voltage limiter. Each set comes complete with all tubes in sockets. Item 1: 3 to 6 Meg. less dynamotor. Item 2: 6 to 9 Meg. less dynamotor. The dynamotor.... \$1.95

MICROPHONE AMPLIFIER BC216A

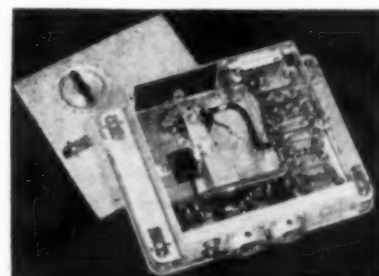

Never been removed from their original packing carton. This 2-tube Amplifier is in a magnificent heavy aluminum case, on resilient rubber mounts. Two single button carbon mike input requires 12 volt filament, 150 volt plate. Uses a 39/44 and 6F7 tube. The complete job case and all, less tubes \$1.95

Prompt Delivery—Write Dept. RND
25% deposit required on C.O.D. order
Shipped F.O.B. New York. Min. Order \$2.00

MICHAEL STAHL, INC.

39 VESEY ST.
Tel. CORTland 7-5980 New York 7, N. Y.

RADIO SURPLUS

Here are a few specials:

RADIO COMPASS RECEIVERS

100 to 1750 kc in four bands, 15 standard 6 v. tubes, makes an extremely sensitive and selective broadcast receiver by changing 110 v. 400 cycle power supply to 60 cycle supply, takes about two hours for a mediocre radioman, and adding controls. Conversion instructions included. New, \$19.50

ANTENNA CHANGE OVER RELAYS

BC 442 A—include 10 amp. rf meter, 50 mmf, 5000 volt vacuum condenser, thermocouple heating element and Tr.-Rev. relay. New, \$1.95

MODULATORS

BC 456B, excellent for salvage or conversion. Contains many readily useable mica condensers and high wattage condensers—tubes 12J5, 1625 and VR 150. Four sfe 20 fuses. Slightly used but guaranteed to be in good condition. \$1.70

CONDENSERS

Mica, .01, 5000 v. test, 2500 w.v.d.c., well known manufacturer, with mountings, New, 85c

TRANSMITTERS

BC 459A, used but in good condition, without dynamotors. \$2.75

Many other very desirable items are in stock but not in sufficient quantity to advertise nationally such as Scopes, Meters, Coils, Crystals, Dynamotors, Transmitters, Receivers, and others. Substantial discount for quantity orders. Write, wire or call. (Write for complete catalog.)

**SOUTHEASTERN
RADIO SURPLUS**
Rochelle, Georgia

Phones 4 and 51

RADIO ENGINEERING TELEVISION ELECTRONICS

Courses in every phase of radio and electronics open to high school graduates. Thorough training, modern courses. Enrollments limited. Approved Veteran Training.

VALPARAISO TECHNICAL INSTITUTE
Dept. RS Valparaiso, Indiana

TELEVISION RECEIVER—\$1.00

Complete instructions for building your own television receiver. 16 pages—11"x17" of pictures, pictorial diagrams, clarified schematics, 17"x22" complete schematic diagram and chassis layout. Also booklet of alignment instructions, voltage and resistance tables and trouble-shooting hints.—All for \$1.00.

CERTIFIED TELEVISION LABORATORIES
5507-13th Ave., Brooklyn 19, N. Y.

at the plate of the mixer tube. The reason for wanting this inversion to occur will be pointed out further along in this discussion.

The frequency of the sound i.f. carrier has now been standardized by the RMA at between 21.25 and 21.9 mc., thus providing a necessary tolerance for manufacture of the tuning units required in sound i.f. amplifiers. The frequency of the video i.f. carrier will be 4.5 mc. higher than this, that is, between 25.75 and 26.4 mc.⁵ Use of these standard video and sound i.f. values throws all possible image frequencies outside of the TV band.

Fig. 6 illustrates this and also summarizes pictorially what has been said about "inversion" of the video and audio carrier frequencies as a result of the frequency conversion process. The position in the frequency spectrum of the video and sound signals (marked V and S respectively) transmitted by a television transmitter assigned in each of the six television channels between 44 and 88 mc. is illustrated at the center. Observe that for each transmitter, the sound carrier frequency (S) is 4.5 mc. higher than the video carrier frequency (V). Also observe that the shape of the video transmission characteristic is similar to that illustrated in Figs. 1 and 2. The local oscillator frequency required for reception of the signals of each of the transmitters is indicated in its proper frequency position to the right, and labeled *Osc.* (Use of a sound i.f. of 21.9 mc. has been assumed.) The video and sound image frequencies (V_i and S_i respectively) corresponding to the signal of each of these transmitters are drawn dotted in their proper frequency positions at the far right. Observe that since all such frequencies fall outside of the television broadcast band, no signal from a television transmitter can qualify as being the image frequency signal for that from another television transmitter. Hence no television signal can cause image-frequency interference with reception of another. The sound and video i.f. carries (S_{i.f.} and V_{i.f.}) that

result in receivers tuned to these television signals are shown in their proper frequency positions at the far left. Observe that the video i.f. carrier is 26.4 mc., which is 4.5 mc. higher than the 21.9 mc. sound i.f. settled on. Observe also that this frequency relation is "inverted" from that which exists between the corresponding video and sound r.f. carrier frequencies V and S.


Separation of the Video and Audio I.F. Signals

Since the mixer plate circuit contains both the video i.f. and accompanying sound i.f. signals, these signals must be separated before they are fed to the separate i.f. amplifiers employed to amplify them (see Fig. 3). It is especially important that none of the sound signal voltages enter the video i.f. amplifier and reach the cathode-ray picture tube, since they will produce alternate dark bands across the picture. The intensity of these bands will change with the variations in the sound program. The possibility of video signal entering the sound i.f. amplifier is not important because the video signal is amplitude-modulated and would be automatically suppressed by the pulse-clipping action of the limiter stage of the FM sound i.f. amplifier. In addition, since the FM sound i.f. transformers have a comparatively narrow passband acceptance characteristic that is only about 80 kc. in total width (approximately 40 kc. each side of the intermediate carrier frequency), and the nearest video signal is .5 mc. (or 500 kc.) away from the audio carrier (see Fig. 2), the likelihood of interference from

⁵ Pre-1941 television receivers generally used a sound-channel i.f. of 8.25 mc. and a video i.f. of 12.75 mc.

⁶ The acceptance band of the sound i.f. amplifier is purposely broadened somewhat beyond that required for reception of the ± 25 kc. deviation FM sound signal transmitted by television broadcast transmitters because of the difficulty of keeping the local oscillator frequency from drifting. (Oscillator frequency drift results in a change in the video and sound intermediate frequencies produced). By purposely broadening the acceptance band of the sound i.f. channel, slight variations in oscillator frequency will have no appreciable effect on the quality of the reproduced sound.

Fig. 7. Ideal over-all bandpass acceptance characteristic for video i.f. amplifier in a television receiver employing a 21.9 mc. sound i.f. (postwar television standards). Note the variations in this diagram as compared with those shown in Figs. 1 and 2.

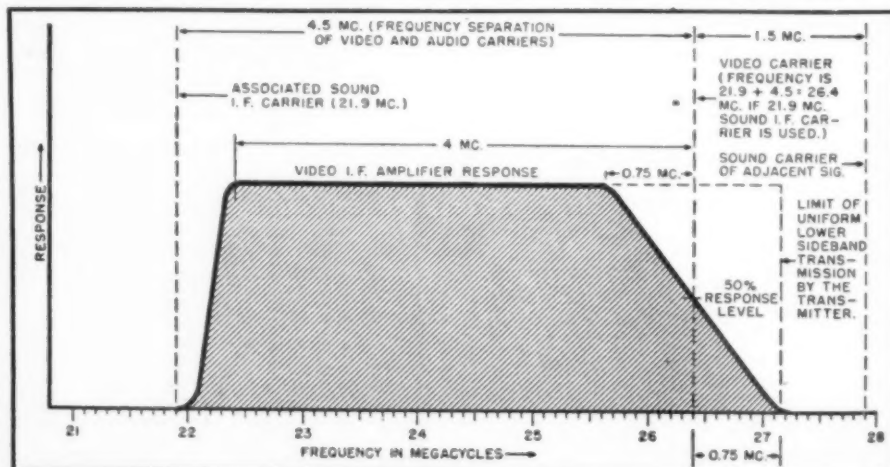

When Your Electronic Problem Hinges on a TRANSFORMER



Transformers
Impedance Matching
Bridging • Filament
Input • Output
Filters • Plate Supply
Smoothing Chokes
Swinging Chokes

Components
Jacks • Jack Panels
Plugs • Patch Cords
Sound Effects Filter
(Frequency cut-off adjust-
able from either end.)


When your circuit calls for a transformer response of $\pm 1/2$ db from 30 to 15000 c.p.s.—with low transmission loss and low harmonic distortion—for such applications as AM and FM broadcasting and high quality music reproduction... investigate ADC Quality Plus Series.

When you need top transformer performance for other audio circuits, you will find ADC provides you complete satisfaction. *Because ADC has specialized in designing and building high quality audio transformers for the most exacting electronics equipment makers and users for 12 years.*

From this experience you may feel confident that an ADC transformer can give the quality performance you need regardless of the specification. *Note the catalog line of transformers and other components listed on the left.*

Write today for your copy of ADC's catalog 46-T.

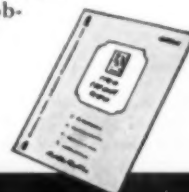For difficult or unusual transformer problems, send us your requirements. Our engineers will work with you to develop the most practical solution.



Audio Development Co.
2833-13th Avenue So., Minneapolis, Minn.

Audio Develops the Finest

Red Hot


At low cost

An extremely sensitive 6 tube receiver for the broadcast band with calibrated dial. Has one RF and two IF stages all with iron core coils and air trimmers. Compactly built. Makes an exceptionally "hot" car radio, portable, P.A. tuner, or home radio. Brand new, complete with tubes and modification data, less power supply. Stock No. B-422. Shipping wt. 9 lb.

We have sold hundreds of these receivers at \$14.95. **\$12.95**
Now a new shipment at a new lower price of only --

BROADCAST RECEIVER

BC-946-B

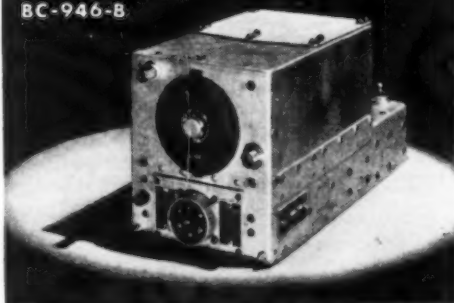


SPARE PARTS KIT

- 3 - BK-35 SPDT Relays Stock No. B-712
- 6 - AF Chokes 23 by, 3 ma. Shipping
- 6 - RF Chokes 15.8 microhenry weight 5 lb.
- 2 - 17 mmd Var. Condensers
- 2 - Bakelite Octal Sockets
- 2 - Ceramic Octal Sockets
- 30 - Mica Capacitors (4 values)
- 10 - .01 mfd 400V Molded Paper Capacitors
- 5 - .5 mfd 400V metal cased paper capacitors
- 10 - 50 mmd ceramic capacitors
- 30 - 1/2 watt carbon resistors (5 values)
- 6 - small ceramic feed-thru insulators

And other miscellaneous parts.
The relays alone are worth more than the cost of the kit. Originally used in Marker Beacon Receivers, they have SPDT contacts and are very sensitive. Closing current .5 ma, opening when current drops to .2 ma, 10500 ohms DC resistance. Ideal for keying monitors and all types of plate current control circuits.

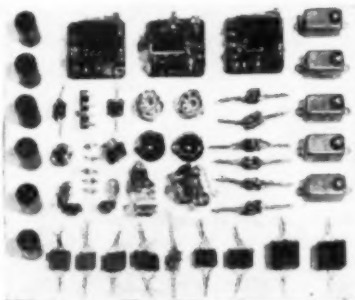Over \$40.00 worth of brand new **\$5.95**
useable radio parts - all for only PER KIT



Special - Brand-new HK24G Transmitting Tubes - - - Only .69¢ Each
On orders of from 1 to 4, add 20¢ to cover packing and postage.

SREPCO


STANDARD RADIO & ELECTRONIC PRODUCTS CO.
135 E. SECOND ST. DAYTON 7, OHIO.

*All prices are net,
f.o.b. Dayton, O.*

BC-645-A TRANSMITTER - RECEIVER

- Makes an excellent transceiver for hams, citizens radio and other services in the 420 to 500 MC range.
- See Feb. 1947 QST for conversion to 420-450 MC amateur band.
- Brand new complete with 15 tubes less power supply.

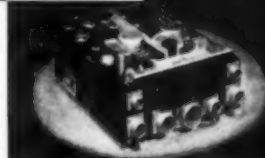
Stock No. B-828 **\$9.95**
Shipping Weight 25 lb.



BC-1023-A MARKER BEACON RECEIVER

- Designed for reception of modulated Marker Beacon signals on the 75 mc. band.
- Variable tuning permits 62 to 80 mc coverage.
- Sensitive relay circuit can be used to control indicator lamp, or external circuits for opening doors, etc.
- Plates and filaments operate directly from any 12 to 14 volt DC supply.
- Brand new complete with tubes, shock mount and instruction book. Dimensions 3 1/2" x 5-3/8" x 5-3/8".

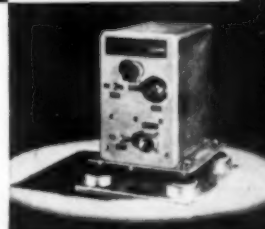
Stock No. B-567 **\$4.95**
Shipping weight 4 lb.



RCA AVT-112 A AIRCRAFT TRANSMITTER

- Operates on 6 to 12 volts, easily converted to 24 volt operation.
- Frequency coverage 2500 to 6500 kc.
- 6V6 Xtal Osc., 6V6 Pwr. Amp., 2-6V6 modulators.
- Electron-eye Tuning Indicator.
- Intercom Circuit Incorporated.
- Compactly built (5-3/8" x 6-1/4" x 4-7/8") for aircraft use. Makes an ideal portable xmitr for hams and other services.
- Brand new complete with 6 tubes and instruction book, less power supply and crystals.

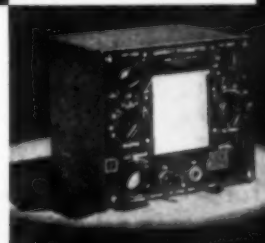Stock No. B-652 **\$12.95**
Shipping weight 8 lb.



AMATEUR VHF MOBILE XMTR-RCVR



One each Transmitter-Receiver,
Dynamotor and Hand Set

\$14.50

Package of six each Transmitter-
Receiver, six Dynamotors and
six Hand Sets

\$75.00

Sold as is, F.O.B. Pasadena,
cash with order.

FLETCHER RADIO, 194 West Colorado Blvd., Pasadena 1, Calif.

WESTERN ELECTRIC #233A 12 volts
VHF Transmitter-Receiver without
tubes. Used equipment.

BALLENTYNE DYNAMOTOR. Six or
twelve volt input, 500 volts, .16 amps.
output. New.

T-13 HANDSET. New.

DRY BATTERIES

Signal Corps Surplus—unused—new. Guar-
anteed, perfect condition. Made by leading
U. S. M'f's. in 1945. Packed in Vapor-proof
Export Cases.

Suitable and used for
"MINE** DETECTORS." Handie-Talkies —
Walkie-Talkies. Radio Receivers and Trans-
mitters. Hallicrafter Radios No. S-29, No. S-39.
Double Lantern Batteries. Amplifiers—Test
Equipment. Heavy Duty Large 45V. "B."

Countless others
Contact us for your special needs. Inquiries
—Tests—Inspection—Invited. Samples avail-
able on request. Immediate Delivery.

Write or phone
SIMWAR DISTRIBUTING CORP.
452 Rodney Street, Brooklyn, N. Y.
Evergreen 8-2129

ENLARGE YOUR Cathode Ray Tube IMAGES

Here's A War Surplus Bargain


SCHMIDT OPTICAL SYSTEM—These were used in the
Navy's Infra-Red Sniperscope and Signalling Units. Black
plastic body, size 3 1/2"x5 1/2". F.L. 2.4" . . . with amazing
speed of F 0.9. Gov't cost \$134.00. Can be placed in front of
C.R. Tubes for enlarging images of wave forms. Also used to
project images of miniature Television Receivers employing
1" tubes. Useful, too, with Oscilloscopes, Pan-Analyzers.

Stock No. 720-V \$6.00 Postpaid

We have literally millions of war surplus
Lenses and Prisms for sale at bargain prices.
Also numerous Optical Instruments, includ-
ing Telescopes, Sextants, Binoculars, etc
Write for Catalog "V"—sent free!

Order by Stock Number Satisfaction Guaranteed

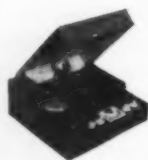EDMUND SALVAGE CO.
P. O. AUDUBON NEW JERSEY



THE NEW SYMPHONY RECORDER

MODEL—RE 80

\$129.50 LIST

FEATURING:

1. 6 tube super-heterodyne radio receiver including
rectifier.
2. High gain symphony loop using 300 ohm line.
3. Miniature P.A. system.
4. High Fidelity Record Player and Home Recorder.
5. A precision built radio transcriber.
6. Streamlined portable cabinet that is easy to carry
around; size 19x16 1/2 x 6 1/4.
7. Plexiglas dial. Variable tone control.
8. Beautiful Multi Color Etched Dial & Panel.
9. Crystal Cutter & Crystal Pick up.
10. A good unit for schools, stadium, etc.

This set is manufactured for top quality, appearance and performance. Set comes complete with microphone.
40% discount off list to Approved Dealers. Write for our latest Catalogue.

SYMPHONY RADIO & TELEVISION CORP.
230 S. Spring St. Los Angeles 12, Calif.

this source is remote. The usual trou-
ble of this kind that is encountered is
the presence of sound signal interfer-
ence in the picture, and not vice versa.

Separation of the video and accom-
panying sound i.f. signals is accom-
plished by circuit arrangements that
differ somewhat with each manufac-
turer. However, they all consist
basically of the use of a suitable filter
network (since the frequencies of
these two signals differ by 4.5 mc.)
that diverts these signals to their re-
spective i.f. amplifier systems, as illus-
trated in Fig. 3.

A suitable filter is also employed to
prevent the sound signal from the
television transmitter operating in the
next lower channel (see Fig. 6) from
entering the video i.f. amplifier, for
this too could cause interference in the
picture.

The Sound I.F. Amplifier

Since the 21.25 (to 21.9 mc.) FM
sound i.f. signal has fundamental char-
acteristics similar to those of the i.f.
signals dealt with in ordinary high-
fidelity FM sound broadcast receivers,
it is amplified, passed through a lim-
iter to remove any amplitude modu-
lations that have been picked up, then
applied to a discriminator for suitable
demodulation, conventional audio gain
stages and on to a loudspeaker (see
Fig. 3) in accordance with normal
high-fidelity FM sound broadcast re-
ception practice.⁷ Most television re-
ceivers employ two sound i.f. stages
with the second stage designed to pro-
vide the limiter action. In the more
elaborate receivers, two limiter stages
are employed to provide more thor-
ough limiter action.

The Video I.F. Amplifier

Returning now to the output side of
the filter network that separates the
video and sound signals (see Fig. 3),
we have the video i.f. signal which
has a bandsread 4 mc. wide. This
signal is applied to a specially designed
video i.f. amplifier whose passband
acceptance characteristic (at least in
television receivers employing the
larger picture screen size) is usually
made somewhat greater than 4 mc.

Fig. 7 illustrates what might be con-
sidered an ideal over-all bandpass ac-
ceptance characteristic for a video i.f.
amplifier designed for a video signal
having the standard transmission
characteristics illustrated in Fig. 1. It
should be carefully studied, and the

⁷ At the time when most of the prewar tele-
vision receivers were built, television trans-
mission standards called for an amplitude-modu-
lated sound channel. In these receivers, the i.f.
passband was quite wide (of the order of 250
kc.). When the standards were later changed to
specify frequency-modulation for the sound chan-
nel, most of these receivers were modified to
include a suitable discriminator in the sound
channel, but in some cases the expedient of sim-
ply moving the i.f. passband slightly so that the
center frequency of the sound i.f. carrier fell in
the middle of the slope of one side of the pass-
band characteristic. Although this is admittedly
sound signal is accomplished as the frequency
varies up and down along the slope of the pass-
band characteristic. Although this is admittedly
not the ideal method of accomplishing FM re-
ception, it has proven fairly satisfactory in these
receivers since the fidelity capabilities of the
sound channel are rather limited anyway due
to the limitations imposed by the use of AM
transmission.

following important things about it observed:

(1). An unusually wide passband is required.⁸


(2). The response at the carrier frequency of the sound i.f. signal 21.25 mc. (to 21.9 mc.) is purposely made very poor (see Fig. 7) in fact the response at this frequency is usually made at least 40 db. below that at the midfrequency level. The purpose of this is to drastically attenuate associated sound i.f. signal voltage that may get through the preceding separation filter network, and so keep it out of the video channel of the receiver. To further insure complete rejection of the associated sound i.f. signal from this channel, a 21.25 mc. (to 21.9 mc.) tuned rejection circuit will be found in an early video i.f. amplifier stage of some receivers. To prevent the sound signal from the adjacent lower-frequency television channel (see Fig. 2) from getting into a 25.75 mc. video i.f. amplifier of a receiver (crosstalk), a $25.75 + 1.25 + 0.25 = 27.25$ mc. tuned rejection circuit (see Fig. 7) is also inserted in an early video i.f. amplifier stage of some television receivers.

(3). Because the modified single-sideband (vestigial) method employed for the transmission of the composite video signal (see Fig. 1) would result in over-emphasis of the lower-frequency video modulations, the passband response characteristic in the video i.f. amplifier must be designed to compensate for this so that all modulation frequencies will be restored to their proper relative amplitudes in order to achieve, for the complete transmitter-receiver system, essentially flat response over the entire video modulation frequency band. This is accomplished by designing the video i.f. amplifier response characteristic with the unusual shape illustrated at the right of Fig. 7. It will be observed that the energy at the video carrier frequency is attenuated to one-half intensity; the transmitted upper sideband components from .75 mc. above the carrier to 4 mc. above the carrier (these invert to from .75 mc. below the carrier to 4 mc. below the carrier in the "inverted" diagram of Fig. 7), are allowed through at full intensity; the transmitted lower sideband components beyond .75 mc. below the carrier frequency (above the carrier frequency here) are attenuated completely (cut off).

It is obvious that the video i.f. amplifier bandwidth and response-curve

⁸ The reason for employing a higher intermediate frequency in the video i.f. amplifier than in the sound i.f. amplifier may now be discussed. It arises from the wider passband requirements of the video i.f. signal. The higher the video i.f. used, the smaller becomes the ratio of the 4 mc. video bandwidth to the intermediate frequency and the easier it becomes to design band-pass networks possessing the required sharp end attenuation and higher resistor loading. Consequently, a higher amplifier gain per stage may be realized.

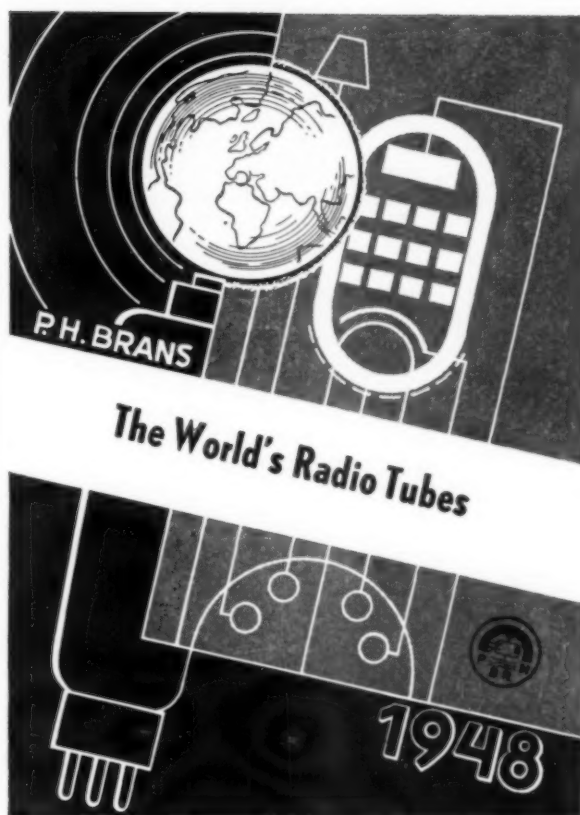The oscillator frequency is made higher than either the incoming video or sound r.f. carrier frequencies so that due to the "inversion" which takes place, the video i.f. carrier resulting from the frequency conversion process will be higher in frequency than the sound i.f. carrier (see Fig. 5B).



The WORLD'S RADIO TUBES

("Radio Tube
Vade Mecum")

More than 10,000 tubes
of 143 manufacturers
listed!

New "1948" Seventh
Edition Now Ready

The Only Book of Its
Kind in the World—
and one of the world's
largest-selling radio
books.

COMPLETE—IN TWELVE LANGUAGES! CHARACTERISTIC TUBE DATA OF

- U. S.
- BRITISH
- FRENCH
- CZECH
- GERMAN
- ITALIAN
- RUSSIAN

also Australian, Hungarian, Swedish, Japanese, Danish, Spanish, Dutch,
Belgian, Finnish, and all other available types!

More listings than ever before. • New, larger page size; 427 pages.
Better paper and appearance.

Of the previous, smaller edition, ELECTRONICS said, "Here at last is the radio tube handbook radio engineers have dreamed of . . . in many carefully prepared tables and charts." "Probably the most complete and authoritative set of tube data in existence," said RADIO CRAFT.

GET YOUR COPY NOW AT YOUR FAVORITE DEALERS, for \$3.00 (in U.S.A.), or by mail from us, \$3.10 postpaid; foreign, \$3.20.

DEALERS: "Technical" discounts allowed on this book when purchased by the radio, book, and news trades in quantities for resale.

CUSTOMERS OUTSIDE THE AMERICAS should send orders on inquiries on this book to P. H. Brans, Ltd., 28 Prins Leopold St., Borgerhout, Antwerp, Belgium. Price, 135 Belgian francs per copy.

Editors and Engineers 1302 KENWOOD ROAD Santa Barbara CALIFORNIA

Condensers, .01-400 volt, midget moulded, \$3.00 per 100.
Electrolytics, 20-350, 10-300, 20-25, single can, common negative, 20c ea.
Wire, # 22 stranded tinned, "Rockbestos" insulation \$3.50 (1000 ft. spool).
Rubber grommets, fit 1/2" hole, inside dia. 3/8" 50c per 100, \$3.00 per 1000.
Tubes: 925, 945 40c ea.; 12SK7, 12SK7GT (RCA, Hytron) 45c ea.

Postage extra. 25% deposit on C.O.D.

FRONTIER SUPPLY COMPANY

36 Kamper Street

Buffalo 10, N. Y.

REPAIR PARTS

Wholesale
Distributors

TRAFFIC APPLIANCES (Irons, toasters, mixers, fans, etc.)

VACUUM CLEANERS (All makes)

MISCELLANEOUS ELECTRICAL ITEMS

ARMATURES REBUILT (Vac. & small appliances)

ONE SOURCE SERVICE

Write for Catalogs

ELECTRIC SWEEPER SERVICE CO.

Dept. 5

2034 Euclid

Cleveland 15, Ohio

ELECTRONIC VOLT-OHMMETER

\$11.85

110 VOLTS AC 20 RANGES

0 / 5 / 10 / 50 / 100 / 500 / 1000 / 5000
volts DC and AC 0-1,000,000,000
ohms in six overlapping ranges. Sensitivity: over MILLION OHMS per Volt on 5 volt range.

POSTPAID

Complete kit includes all component parts, tubes, punched and drilled chassis and beautifully enameled panel. Easily assembled and wired.

Special slideback circuit developed during war by scientist at the California Institute of Technology gives amazing sensitivity and flexibility while completely eliminating necessity of batteries and expensive meter. Each instrument is individually calibrated. Dial scale over nine inches long!

In addition to performing the usual volt-ohm functions, this instrument easily measures these voltages: SUPERBET OSCILLATOR, AVC, AFC, TRUE GRID BIAS AT THE GRID. BIAS CELLS without affecting the circuit. Measures the exact leakage resistance of INSULATION, TUBES, CONDENSERS. It can be used with a signal generator for SIGNAL TRACING.

STERLING ELECTRONIC COMPANY

BOWLING GREEN, KENTUCKY

OUTSTANDING VALUES


BC 348 P • BC 375 E
BRAND NEW • ORIGINAL BOXES



RECEIVER BC 348 P

Six Bands—200 to 500 and 1.5 to 18 mc. HI ratio vernier tuning, crystal filter, complete with 8 tubes, dynamotor, shock mounted base, and 2 technical manuals. Shipping weight: 62 lbs.

PRICE \$4950

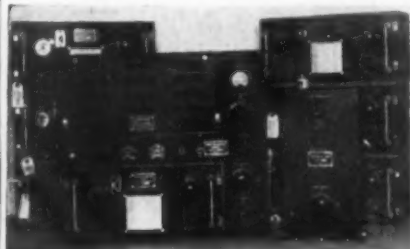

TRANSMITTER BC 375 E

Basic transmitter, complete with seven tuning units 200 to 500 and 1.5 to 12 mc. Antenna tuning unit and 2 technical manuals, less tubes and dynamotor. Shipping weight: 275 lbs.

PRICE \$2950

SPECIAL OFFER
BOTH UNITS—\$75.00

**NOTE: 25% DEPOSIT WILL HOLD
UNITS FOR 30 DAYS!**

Shipments made F.O.B. Lima, Ohio.
25% Deposit required on C.O.D. orders.

FAIR RADIO SALES
223 S. MAIN ST. • LIMA, OHIO



**GET HIGH SPEED WITHOUT
NERVOUS TENSION**

Amazing Book shows how "crack" operators rely on something besides practice to develop high speed and proficiency. You can learn code or improve your present efficiency in sending and receiving by the same system that has made code champions and radio telegraph experts. Send for 52-page book. It is free.

CANDLER SYSTEM CO.
P.O. Box 928 Dept. 2-O Denver, Colo.

shape requirements are far more difficult to satisfy than are those in sound i.f. channels. Not only is the 4-mc. bandwidth to be passed more than 26 times as great as that in a high-fidelity FM sound channel, but the over-all band acceptance characteristic required is of rather complicated and precise form. This makes accurate design and adjustment (alignment) of such video i.f. channels a very important "must."

In order to obtain the unusually wide 4 mc. over-all passband characteristic required in the video i.f. amplifier, double-tuned interstage coupling transformers are used. The primary and secondary are deliberately over-coupled sufficiently to produce a broad double-peaked response characteristic, then the secondary (and usually the primary) is sufficiently loaded with shunt resistance to flatten out the major portion of the peaks. Obviously, the gain per stage is much less under these loaded conditions than is the gain in the narrower-band i.f. amplifiers employed in the sound channels of superheterodynes. Consequently, even though high-gain r.f. pentode amplifier tubes of the latest type are used, it is not unusual to find four or five such stages of video i.f. amplification employed in a television receiver in order to provide sufficient gain.

The smaller table model television receivers which employ small diameter cathode-ray tubes having picture screen widths of the order of 5 or 7 inches do not require as sharp an image as is necessary when the larger C-R tubes are used. The sharpness of the reproduced image is a function of the bandwidth of the video signal applied to the picture tube. Consequently, since extremely fine picture detail is not required in such receivers it is not necessary to reproduce the higher modulating frequencies of the video signal. Therefore, the i.f. band-acceptance width is usually sacrificed for increased gain per stage so that fewer video i.f. amplifier stages are required and the receiver cost is correspondingly reduced. The selectivity of the video i.f. tuning circuits in these receivers will be found to be such that band-acceptance widths of only 2.5 or 3 mc., instead of the full 4 mc., are employed.

Rest of the Video Circuits

After passing through the successive video i.f. amplifier stages the composite video signal (which contains both the picture impulses and the synchronizing information) is applied to a diode video detector (see Fig. 3) which demodulates it. From there

Most cathode-ray picture tubes can be modulated over the useful brilliance range by a signal of the order of 50 volts. A well-designed video amplifier stage (see Fig. 3) roughly will provide a gain of 20 to 30—let us say a gain of 25. This makes necessary a detector output of approximately $50/25 = 2$ volts. Four video i.f. stages having a 4.5 mc. passband (see Fig. 7) usually will produce a gain of approximately 10 each or $10 \times 10 \times 10 \times 10 = 10,000$ total. This results in a mixer output signal strength requirement of $2 \div 10,000 = .0002$ volt, or 200 microvolts.

RADIO VALUES

ECOR DYNAMOTORS
Widely used in Police, amateur, broadcast and radio equipment.
Volts input 5.5 Amps. 5.5
Volts output 210 Amps. .070
Temp. rise 40° C. RPM 4400
Duty continuous. Size 5" L. x
4" H. x 3 3/4" Dia. Four colored lead wires.
No. 9645.....Each, \$3.50

WINCO DYNAMOTORS
Winco Double Shaft Dynamotor.
Input volts 18, output volts
450. 1-1/16" shaft length.
1 1/4" shaft length with small
gear. Size of motor 7 1/2" L. x 4 1/4" H. x 3 3/4" Dia.
No. 9645.....Each, \$9.50

Winco Dynamotor. Input volts 12 Amps. 9.0, output
volts 400 Amps. 180. Temp. rise 40° C.
R.P.M. 4200. Duty cont. Size 7" L. x 4" H. x
3 3/4" Dia. Four lead wires.
No. 9646.....Each, \$8.50

RADIO CONDENSERS
Sprague Auto Radio Condenser .5
MFD., 600 V.
D.C. Size 2" L.
x 1 1/16" Dia.
with lead wire.
No. 9644—lots of
10.....10c ea.

ROTARY SNAP SWITCH
Radio Snap Switch. Split
shaft 1 1/2" L. 2
lock nuts. Und.
Approved Rat.
use 15 Amps. 125
V. 1a Amp.
125 V. Single throw, 2
solder lugs.
No. 9643.....15c

PUSH BUTTON SWITCH
6 V. push button
switch. 2 screw
terminals. Size
1 1/2" L. x 3/8" Dia.
No. 9644
Each, 15c

BAKELITE HANDLE
Brown Marbled Bakelite Handle used for radios, luggage, etc. Size
5" L. x 2 1/2" W. with
holes on each end for
rings.
No. 9647.....8c

SHUNT MOTOR
Aluminum Body Shunt Motor.
Type B-9-1. 7 Amps. 27 1/2
volts. D.C. 5600 R.P.M. 1 1/2"
shaft length. Plunger Type. 3/16" shaft.
No. 9648.....Each, \$2.25

SEND FOR FREE CATALOG
G. & E. EQUIPMENT SUPPLY CO.
OGDEN AT FULTON, CHICAGO 7, ILL.
We ship C.O.D. All prices F.O.B. our warehouse.

RANGEMASTER

**MODEL 10
BY BRADSHAW**
A COMPLETE
SERVICE
INSTRUMENT

The model 10 RANGEMASTER covers 22 ranges.
Three direct reading capacity ranges.
Three A.C. current ranges for checking current drain of electric motors and appliances.
A.C. VOLTAGE:
1-10-100-500-1000 Volts
D.C. VOLTAGE: 10-100-500-1000 Volts
A.C. CURRENT: .15-1.5-15 Amperes
D.C. CURRENT: 1-10-100-1,000 Milliamps
OHMS 10,000-100,000—1 Meg.—20 Meg.
CAPACITANCE: .001-.1 .01-1 .1-10 Mfd.
RANGEMASTER MODEL 10.....\$23.50
COMPLETE KIT.....17.95
FOUNDATION METER WITH 3 COLOR
SCALE & INSTRUCTIONS.....7.85
TEST LEADS......85

COMPLETE SET OF PLANS, 25c
Stamps or Coin
AVAILABLE AT YOUR LOCAL DEALER
BRADSHAW INSTRUMENTS CO.
942 Kings Highway, Brooklyn 23, New York
SEND FOR DESCRIPTIVE LITERATURE

LOOK!

RESISTOR KIT
172 Assorted Carbon Resistors
From 1/3 to 2 WATTS
POPULAR VALUES—Less Than 1c Each
SPECIAL OFFER
Your Cost—\$1.69 per kit of 172
Subject to Prior Sale. Write for Latest Parts
Bulletin
INTERSTATE RADIO & PARTS CO.
6357 South Ashland Avenue, Chicago 36, Ill.

RADIOMEN SERVICEMEN BEGINNERS
MAKE MORE MONEY
EASILY—QUICKLY
\$250 WEEKLY POSSIBLE
WE SHOW YOU HOW—INFORMATION FREE
MERIT PRODUCTS,
216 32F 132 Ave., Springfield Gardens 13, New York, N. Y.

it proceeds through the video amplifier and on to the control grid of the cathode-ray picture tube. Also necessary are the pulse clipper, sync pulse separator, and horizontal and vertical sync sweep generators (all shown in Fig. 3) whose actions need not be discussed at this point.

I.F. Amplifier Design and Circuits

In this detailed discussion of the selectivity and passband acceptance characteristics required in the i.f. amplifiers of various types of receivers, no details of the i.f. amplifier components or circuits usually employed to achieve the desired performance have been given. The aim has been to first acquaint the reader with the requirements to be fulfilled in each type of receiver. In the next few articles of this series, the actual details of i.f. transformer construction, i.f. amplifier circuits, and methods of achieving wide-band response, variable bandwidth and freedom from interference will be explained.

(To be continued)

Hands That See

(Continued from page 67)

are soon heading for the FCC offices.

Keynoting the entire course is the practical application of the basic radio instruction absorbed by the student. The school's high fidelity audio system which serves the auditorium and playgrounds is an outstanding example of this application. With this system, programs are recorded for future presentation to assemblies, recordings by the student choral group are made for study and analysis, and general sound coverage is given the school for regular or extra-curricular activities.

Bob Gunderson's own call, W2JIO (Jump In the Ocean), is the basis for the "shack" in the school's administration building, where many of the boys are indoctrinated in the pounding of brass and talking one's self hoarse. The fellows are proud of their work at the school, especially Bob, for here, tomorrow's citizens are training today to become independent, self-sufficient members of an honorable profession and a happy fraternity.

-30-



December, 1947

NEWCOMB

MANUFACTURER OF AMERICA'S TOP QUALITY AMPLIFIER

ANNOUNCES the NEW E-SERIES

A LOW-PRICED LINE OF SUPERIOR UTILITY
AMPLIFIERS

THE maker of the incomparable K and H Series of quality amplifiers has designed and produced the new E-Series with the same high quality materials and workmanship, to produce the best low-priced 10-, 17- and 25-watt amplifiers ever offered. Included in the line are phono tops and portable assemblies. The E-Series fills the need of those who want a superior, dependable amplifier, but who must confine their purchases to the lower-price range. Here are amplifiers that fill all the requirements of standard utility applications, priced within reach of all.

MODEL E-10: An outstanding value in the public address market, the E-10 delivers a full 10 watts from push-pull 6V6 tubes in a multi-stage inverse feedback circuit . . . has inputs for microphone and phonograph and a full range tone control.

49⁵⁰
RETAIL

With tubes
less cover.

MODEL E-17: 17 watts of undistorted audio from push-pull 6L6 tubes. Inputs for a microphone and phonograph . . . Full range tone control . . . Multi-stage inverse feedback.

79⁵⁰
RETAIL



With tubes
and cover

MODEL E-25: A really fine utility amplifier for better performance, more dependable operation. Full range tone control, 25 watts of undistorted power and inputs for 2 mikes and a phonograph make the E-25 easily applicable to most sound jobs. Inverse feedback assures lowest distortion.

99⁵⁰
RETAIL

With tubes
and cover

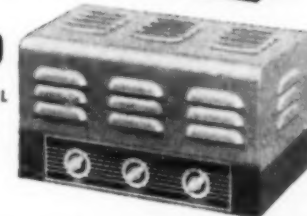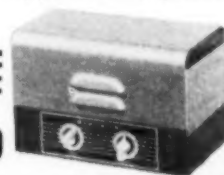(Prices slightly higher east of the Rockies.)





Send for Specifications

AUDIO PRODUCTS CO.

Dept. F, 6824 Lexington Avenue • Hollywood 38, California

SENSATIONAL NEWS! TWO WEEK DELIVERY!

SPEAKER REPAIR PRICE LIST

2"-3"-4"	\$1.20	10"	\$2.20
5"	1.30	12"	2.40
6"-4"x6"	1.40	15"	3.30
7"	1.70	5"x7"	1.90
8"-6"x9"	2.00		

Above prices do not include replacement of field coil.

Write for **FREE Parts Buying Guide**

SPEAKER REPAIR SERVICE

We repair and recondition any type or kind of speaker at the lowest price. All work done by factory trained experts—all work **GUARANTEED**.

-U.S.-R.-S.-


U. S. RADIO SUPPLY

5116 HARPER AVENUE

CHICAGO 15, ILLINOIS

DEPT. NE 9

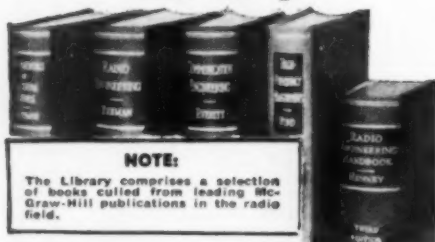NOW—A REALLY HIGH-POWERED— Radio Engineering Library



NOTE:

The Library comprises a selection of books culled from leading McGraw-Hill publications in the radio field.

- especially selected by radio specialists of McGraw-Hill publications.
- to give most complete, dependable coverage of facts needed by all whose fields are grounded on radio fundamentals.
- available at a special price and on easy terms.

THESE books cover circuit phenomena, tube theory, networks, measurements, and other subjects—give specialized treatments of all fields of practical design and application. They are books of recognized position in the literature—books you will refer to and be referred to often. If you are a practical designer, researcher or engineer in any field based on radio, you want these books for the help they give on hundreds of problems throughout the whole field of radio engineering.

5 VOLUMES, 3559 PAGES, 2558 ILLUSTRATIONS
1. Eastman's FUNDAMENTALS OF VACUUM TUBES

2. Terman's RADIO ENGINEERING
3. Everitt's COMMUNICATION ENGINEERING
4. Hund's HIGH FREQUENCY MEASUREMENTS
5. Henney's RADIO ENGINEERING HANDBOOK

10 days' examination. Easy terms. Special price under this offer less than books bought separately. Add these standard works to your library now; pay small monthly installments, while you use the books.

10 DAYS' FREE EXAMINATION—SEND COUPON

McGraw-Hill Book Co.
330 W. 42nd Street, New York 18, N. Y.

Send me Radio Engineering Library, 5 vols., for 10 days' examination on approval. In 10 days I will send \$22.50 plus few cents postage, and \$5.00 monthly till \$27.50 is paid, or return books postpaid. (We pay postage on orders accompanied by remittance of first installment.)

Name
Address
City and State
Company
Position RN-12-47



TRAIN FOR RADIO IN MIAMI

Prepare for a radio career in one of America's most beautiful cities—busy, romantic Miami—at the crossroads of two continents.

Embry-Riddle's internationally known Government-approved School of Aviation offers a full year Radio Course, designed to qualify you for important jobs in the Radio Industry. Approved training under G.I. Bill. Immediate enrollment.

FOR FREE INFORMATION
MAIL THIS COUPON—TODAY!

Dean of Enrollments—Dept. 88
EMBRY-RIDDLE SCHOOL OF AVIATION
Miami 30, Florida

Name Age

Address

City State

Check One: ☐ Veteran ☐ Non-Veteran


NEW RECEIVERS for Winter Market



TABLE MODEL RADIO

Symphony Radio & Television Corporation of Los Angeles has just introduced a new table model receiver in the low priced class.

Known as the S-90, this four-tube

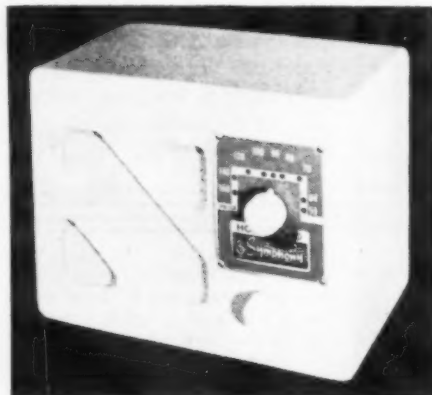

receiver has a 4" speaker. This model is available in either a natural wood finish or ivory.

Full details on the Symphony line will be furnished upon request to Symphony Radio & Television Corporation, Los Angeles, California.

FIVE-IN-ONE TV UNIT

Garod Radio Corporation of Brooklyn have announced a new five-in-one television receiver, their Model 42FMPT2, which combines television, AM-FM and short-wave, automatic record changer, and record storage space.

This model features a 10" picture tube, an automatic station finder, and image synchronizer. The receiver cir-



cuit employs 34 tubes, 4 rectifiers, and 1 ten inch picture tube.

The phonograph has a two-post automatic changer which accommodates 10 twelve inch or 12 ten inch records.

The unit stops automatically at the end of the last record.

Full details on this new model receiver, which is moderately priced, may be secured from Garod Radio Corporation, 70 Washington Street, Brooklyn 1, New York.

COMBINATION-RECORDER

Featuring a 6-tube a.c. receiver, the new "Ultratone" Model PR-7 radio-recorder-phonograph just announced by Audio Industries of Michigan City, Indiana, provides, within a single unit, complete home entertainment.

A dual speed recorder makes records at either 33½ or 78 r.p.m. The plywood case is covered with DuPont Fabricoid. The case is fully enclosed to protect the recording and reproducing unit. A companion extension speaker, available at an extra charge, converts the unit into a public address system. A specially designed midjet microphone facilitates recording.

Audio Industries, Michigan City,



Indiana, will furnish additional information on the "Ultratone" line of radio-recorders to those requesting it.

RADIO-CAMERA

Air King Products Co., Inc., of Brooklyn, New York, has recently introduced a novel radio-camera portable which is causing quite a stir in the industry.

This new Air King radio-camera weighs less than four pounds complete with batteries. It is 9½ inches high, 4¾ inches wide and 3¾ inches in depth. The radio is equipped with miniature tubes and operates on one 67½ volt "B" and two flashlight type "A" batteries. The camera is housed in an eveready case and contains a 50 mm. meniscus lens. It can take both black and white and color pictures, using number 828 standard film. The unit is equipped with an adjustable strap which permits either shoulder or hand carrying of the unit.

Further information on the radio-

camera may be obtained from Air King Products Co., Inc., 1523 Sixty-Third Street, Brooklyn 19, New York.

"THE MODERN"

Freed Radio Corp. of New York has just added a new AM-FM radio-phonograph console to the Freed-Eisemann line of home receivers.

Designated "The Modern," this unit is constructed of striped African mahogany veneers and is available in both blonde and brown mahogany finishes. The receiver incorporates a 20-



tube radio section with a separate power supply with an undistorted output of 20 watts and a coaxial speaker system with a high-fidelity tonal range of 30 to 15,000 cycles. The phonograph equipment consists of a Garrard Inter-

Mixer Record Changer that plays 10" and 12" records, in any sequence, automatically.

Prices and delivery information will be supplied by Freed Radio Corporation, 200 Hudson Street, New York 13, New York, upon request.

LOW-COST PORTABLE

Production on the new Model 300 portable radio has been announced by Philco Corporation of Philadelphia.

Designed to sell in the low-priced class, this new portable operates on a.c.-d.c. as well as batteries. The unit weighs only 12½ pounds with batteries. Among its features are a beam power pentode audio system, and oval speaker. A built-in high impedance antenna has been included to facilitate pick up of distant stations.

The Philco Model 300 is housed in a hardwood cabinet with novel decorative spatter lacquer finish and contrasting ivory grille with brown plastic controls.

The unit is now in production at the Philco Corporation plant in Philadelphia.

CHILD'S PHONOGRAPH

A new line of electrically amplified phonographs for children is now available from Universal Mart Associates Corp. of New York under the trade-name "Fon-O-Pal."

One of these units, the "Disc-Jockey," is a console model equipped

with a two-tube amplifier, high gain crystal pickup, 5" Alnico V speaker, and a.c. motor and turntable for playing both 10" and 12" records.



Sides and top of this unit are made of pressed masonite and comes either in red or blue. The front grille and sound board is made of kiln dried white pine and finished in buff. Provision is made for housing both 10" and 12" record albums. The finish on the unit is washable. Rubber feet on the bottom of each cabinet help prevent scraping.

Universal Mart Associates Corp., 15

The New Model 247 TUBE TESTER



Features:

The Model 247 incorporates a newly designed element selector switch which reduces the possibility of obsolescence to an absolute minimum. Any pin may be used as a filament pin and the voltage applied between that pin and any other pin, or even the "top-cap."

The new free-point system described above permits the Model 247 to overcome the difficulties encountered with other emission type tube testers when checking, Diode, Triode and Pentode sections of multi-purpose tubes, because sections can be tested individually when using the new model 247. The special isolating circuit allows each section to be tested as if it were in a separate envelope.

The Model 247 provides a super sensitive method of checking for shorts and leakages up to 5 Megohms between any and all the terminals. Continuity between various sections is individually indicated.

One of the most important improvements, we believe, is the fact that the 4 position fast-action snap switches are all numbered in exact accordance with the standard R.M.A. numbering system. Thus, if the element terminating in pin No. 7 of a tube is under test, button No. 7 is used for that test.

Model 247 comes complete with new speed-read chart. Comes housed in handsome, hand-rubbed oak cabinet sloped for bench use. A slip-on portable hinged cover is included for outside use. Size: 16¼" x 8¼" x 5¼".


20% deposit required on all C.O.D. orders.

ONLY
\$29.90

MOSS ELECTRONIC DISTRIBUTING CO.

DEPT. RN-12, 229 FULTON ST.
NEW YORK 7, N. Y.

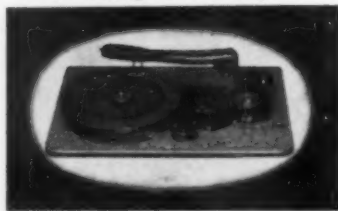THIS WIRE RECORDER HAS EVERYTHING (Including Record Player)



—and you can build it easily!

Model B-1 Magnetic Wire Recorder. (Foundation Unit) records up to 1 hour continuously. Full range fidelity 30-8000 CPS records from standard phono records, radio or microphone. This model uses two motors—one for play-recording, second motor for rewind. Connect to amplifier or radio. Model B-1 (as illustrated above) with crystal mike, 1 hour spool of wire, phono pickup, 40 K.C. oscillator wired and tested, and schematic diagrams.

1 Model B-1.....\$65.00
2 Model B-1's.....60.00 each
3 Model B-1's.....55.00 each

Quantity prices prevail while present stock of Recorders lasts. Prices will go up again after these have been disposed of. See your friends and act now. A diagram of a simple 4 tube amplifier for portable usage to connect to this Recorder can be had by requesting same.

Quantity sales ordered in name of one customer shipment will be made to same. Remit payment in full for Recorders with order. All Recorder sales are final.



M-110 Western Electric Microphones. These can be used with P.A. and Recording systems. Good frequency response. Complete with chest plate and 20 feet of high grade low impedance microphone cable \$5.00 each; with 50 feet length of cable \$6.50. The microphone cable alone is worth more than the purchase price.

NATIONAL UNION RADIO TUBES

Standard individually cartoned tubes. Discount 50% plus 10% from current list prices. Minimum order 50 tubes. Mail your order promptly with remittance. On hand large stock of standard and hermetically sealed wire wound resistors, mica condensers and other parts. Surplus assemblies too numerous to mention. Write us your needs.

30% Deposit with C.O.D. Minimum Order \$3.00
Recorder orders remit in full

Electronics of Staten Island, N. Y.
(Formerly Clarion Sound Eng. Co.)
P. O. Box 169

Gibraltar 7-8975 Staten Island 1, N. Y.

TRANSMITTER KIT

\$12.95



APPROX. 6 to 10 WATTS INPUT

COMPLETE with built in power supply for 115V AC and DC

Key (as illustrated) with plug.....\$1.25 additional
Extra coil......75
Crystal mounted, within 10 KC of freq. 80 or 40 meters.....1.50 additional
20 meter crystal.....3.50 additional

All condensers, choke, resistors and Resonance indicator lamp mounted and soldered. Only six wires to connect. Ready to operate within 15 minutes. Wire, coil for one band, 80-40 or 20 meters, and tube supplied. Excellent as a standby rig, or for local contacts. Ideal for apartment house use. No BCL-QRM. Size 7x7x2. Complete instructions included. We will wire and test this kit for \$2.00 additional.

Terms: 20% deposit, balance C.O.D.

TEK-KIT LABS

P. O. BOX 6,
Kew Gardens 15, N. Y.

Moore Street, New York 4, New York, will supply additional information on the "Disc-Jockey" or other units in their line on request.

MAGNAVOX "BERKELEY"

The beauty of 18th Century cabinetry has been faithfully reproduced in the Magnavox "Berkeley," a new



radio-phonograph which has been designed to fit into the modern home.

Available in mahogany finish, this new receiver features 18 watts undistorted power output, two 12" "Duosonic" speakers and a precision automatic record changer with noiseless feather-touch pickup.

The cabinet is 35" high, 30½" wide and 18" deep. This same model is also available with Armstrong FM carrying a tube complement of 14 amplifier tubes, 2 rectifiers, and 2 tuning tubes.

The Magnavox Company is located in Fort Wayne, Indiana. Requests for additional information on the "Berkeley" should be addressed to the company.

TAVERN TV SET

Colonial Television Corporation of New York has announced production on a new multi-color illuminated cabinet, the first of its kind to house a television receiver.

The new club model, No. 1530 "Vision Master," has been designed especially for taverns and other public viewing places.

The new cabinet was designed by Henry Anchester, who was instrumental in designing the present-day illuminated juke-box cabinets.

Colonial Television Corporation, 2139 Harrison Avenue, New York, New York, will merchandise the new unit.

AM-FM-PHONO CONSOLE

The popular "split lift-up" top has been incorporated in the new Model H-168 AM-FM-phonograph combination just announced by Westinghouse Electric Corporation.

Available in either mahogany or blond avodire finish, this new receiver provides full-width record storage space for 52 albums or 350 single records.

Featuring the new arc vernier dial, illuminated by edge and indirect lighting to provide a rainbow of color along

DECEMBER SPECIAL

Two Gang super-het tuning condensers.....\$0.75
3 for.....2.00

OPERATES FROM A BEAM OF LIGHT

Photo-electric relay kit complete with all parts including tubes, relay, sensitivity control and simple assembly instructions. Build your own magic eye alarm system—use light beam control. Only \$4.95.

LABS — SCHOOLS — INDUSTRIALS — GET ON OUR MAILING LIST—SEND US YOUR REQUIREMENTS.

Allied relay-24v. d.c., d.p.d.t. 10 amp. contacts, 75c; 10 for.....\$3.00

G. E. Solenoid operated contactor
#CR2820—controls 6 circuits—operates on 115V. 60CY. 30Amps. 15 amps contacts double break each circuit. G.E. Catalog price \$25.00. YOUR PRICE.....\$5.95

4 mfd. @ 600V oil filled with mtg. clamp, 59c; 10 for.....\$ 5.00

Dual 14mfd @ 200V electrolytic-KS8677; made by W.E., 59c; 10 for.....3.00

Leach 6V dc relay, 3 pole n.o., \$1.25; 10 for 10.00

UTC "S-6" input Xmtr.—line or mike to grid; dealer's price, \$3.10. Your cost, \$1.25; 10 for.....10.00

Weston #476—11½" Bakelite; 0-8V AC \$3.95


Weston #507 R.F., amps. 0-1.3 2% accuracy to 65mc; bakelite case.....3.95

Westinghouse Filter chokes—4 by 90 mills, 300 ohms res. hermetically sealed 2" can 69c; 5 for.....3.00

25% deposit with order; balance C.O.D. save C.O.D. charges; send full amount.

RADIO DEVELOPMENT & SALES CO.
382 State Street Brooklyn 2, N. Y.

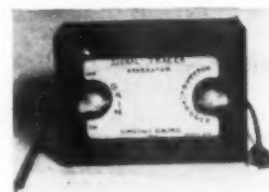2-IN-1 CHANNEL ANALYZER NEW PENCIL THIN PROBE



Extremely sensitive tracer permitting signal to be heard at any stage of radio under test. Uses new Pencil Thin Probe with loud speaker operation. Plus a signal generator that delivers a strong A.F., I.F., and R.F. signal, permitting the serviceman to trace and align any portion of receiver under test. Uses a multi-vibrator network.

A.C., D.C. operated.
Only two controls for complete operation.
SERVICEMAN'S NET PRICE.....\$14.95

If he can't supply you write us direct.
CONSTANT ELECTRIC
112 Cornelia St. Brooklyn 21, N. Y.

LEARN RADIO!

IN ONLY 10 MONTHS
PREPARE FOR A GOOD JOB!
COMMERCIAL OPERATOR (CODE)
BROADCAST ENGINEER
RADIO SERVICEMAN

Television Servicing—15 Months

(Approved for Veterans)

SEND FOR FREE LITERATURE
BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALT. 17, MD.

ROTA-BASE

NEW HANDY LAB. DIAL actually gives a "prong" picture of radio tube connections. INSTANTLY, ACCURATELY. No more valuable time lost thumbing pages or on lengthy readings. Filament, grid, plate, cathode, etc., to more than 300 tube types are shown. NOW ONLY \$1.00 post-paid, or sent C.O.D. plus postage. Order TODAY. Money refunded if you are not delightfully pleased.

REED MFG. CO.

11350-P, Burbank Blvd., N. Hollywood, Calif.

LOWEST PRICES ANYWHERE

TUBES: Standard Brands — sealed cartons — All Types 60% to 80% off.
HAND MIKE: "SHURE" Sig. Corps Type T17B. 5 ft. cord and PL 68. New. \$1.79.
MIDGET CHOKES—"UTC"—Universal replacements 69c each.

Send 20% Deposit—Bal. C.O.D.—Fast Service.
—Perfect Mdse.—Write for Catalog—
COMMERCIAL RADIO
36 BRATTLE ST.—BOSTON 8

RADIO NEWS

the full arc of the tuning band, this combination console has a tuning range of 540 to 1600 kc. on AM and 88 to 108 mc. on FM with a tuning ratio of 16 to 1.

Using a low-pressure crystal pickup and permanent needle, the H-168 has the new Westinghouse Speed Record Changer that plays 12 ten inch or 10 twelve inch records.

The receiver uses seven tubes plus rectifier and has a 10" electrodynamic speaker. Two built-in antennas are included in this model with provision for outside antennas if desired.

The Home Radio Division of Westinghouse Electric Corporation, Sunbury, Pa. will supply additional information on the Model H-168 upon request.

FRSMAP CONVENTION

THE Federation of Radio Servicemen's Associations of Pennsylvania has announced plans to hold its first annual convention in Philadelphia, January 11, 12, and 13 at the Bellevue-Stratford Hotel, Broad and Chestnut Streets.

The PRSMA is acting as host to the statewide group with Dave Krantz, president of the Philadelphia group serving as chairman in charge of arrangements.

Mr. Krantz points out that this meeting will convene for the purpose of exchanging mutually profitable ideas on operating a successful service business.

Persons interested in attending this convention may secure full details from Dave Krantz, 2109 South Seventh Street, Philadelphia, Pa.

COMMUNITY RADIO-PHONE SERVICE

A GROUP of prominent Freeport, Long Island citizens have recently banded together to form a new non-profit organization known as the Freeport Community Radio Association.


The purpose of this organization is to provide a new community radio-phone service which will be available to any resident of Freeport, Long Island and vicinity.

Designed to fill a need for radio-telephone services in small communities, continuous 24-hour operation of the central station will be provided. Central station equipment will be installed on the roof of the First National Bank and Trust Company. The signals are carried by telephone line to the switchboard of a local telephone answering exchange where the operator will acknowledge the radio call, take any message for delivery, and then relay it to its destination by ordinary telephone connection with any telephone subscriber of the Bell System. In a similar manner, messages may be transmitted from any telephone to the central station operator and then by radio to mobile units. No actual line connections are made with telephone circuits of the Bell System under this arrangement.

The new system will operate on the 152.03 and 157.29 mc. bands. Frequency modulation equipment is being used. Selective calling is used throughout the system.

RESCO HAS IT-FOR LESS!

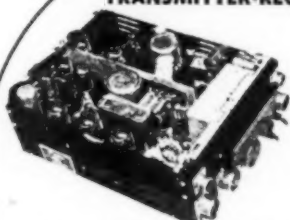BC 645 ULTRA HI-FREQUENCY TRANSMITTER-RECEIVER



You Read About It in Feb. QST!

Originally operated in the frequency band from 450 to 500 M.C. Can be converted to 420 MC amateur band. Consists of complete transmitter and modulator system, and receiver. Instructions for conversion to AC supply. Complete with 15 tubes, **14.95**



Burgess De Luxe VIBRO TOOL

Complete with 22 attachments and case. Engraves on metal, glass, stone, plastics. Cuts patterns on cloth, rubber; tools leather, etc.

With Needle 110 V AC, 60 Cycle—**9.90**
Alone 4.50 No. V 150, Complete

For Beginners and Experimenters ELECTRIC MOTOR KIT




Consists of complete set of 33 precision parts for building an electric motor that really runs, plus profusely illustrated 32-page book "The Drama of electricity" **2.64**

U. S. Army Signal Corps HS-18 HEADSET



Standard type double phones, 2000 ohms D.C. resistance; 8000 ohms impedance, similar to Trimm featherweights. Brand new, in original packing. Complete with cord, plug, leather-trimmed headband. Adjustable **1.49**

Meissner's BREWSTER MODEL FM RECEPTOR

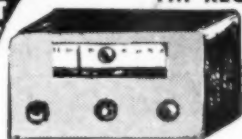

Adds frequency modulation to any regular AM set. Complete with 8 tubes **38.33**

AUDIO FIDELITY — Flat within 2 DB from 50 to 15000 C.P.S.
ANTENNA INPUT Impedance—300 ohms
SENSITIVITY—40 microvolts
CONTROLS—Tuning and combination volume control—line switch
POWER SUPPLY—105 to 125 volts, 50 or 60 cycle AC

NEW SHURE T-17 MICROPHONE




Single button mike used by armed forces. Perfect speech qualities. For portable rigs or simplified home transmitter, or where carbon mike is specified. In original cartons. With rubber covered 5-ft. cord and plug, cover, and switch. **14.95**

"RADIOGRAPH" for fun



Includes a complete kit of parts with earphone to build crystal receiver. Also 3-way telegraph outfit (blinker, buzzer, sounder). 2 persons can practice code, one sending, one receiving, through earphone. Complete with instructions and radio dictionary **1.95**

Listen to FM Stations with PILOTUNER

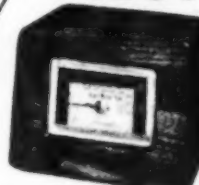

A complete tuner less audio system. **29.95**

PILOTUNER features:
3 gang copper condenser — Heavy duty transformer — Own power supply
— Tuned R.F. stage — Walnut cabinet — 8 1/4" wide; 6 3/4" high; 3 1/4" deep.

4-Prong 6-Volt VIBRATOR



Similar to Mallory 294 or Radiant 5300

1.29 ea. 1.15 ea. 1.05 ea.
Lots of 12 Lots of 25

Include Postage With Cash Orders

WRITE FOR FREE VALUE-PACKED BULLETIN

Radio Electric SERVICE CO. OF PENNA., INC.

7TH AND ARCH STREETS, PHILA. 6, PENNA.
Branches: 5930 Market St. & 3145 N. Broad St., Phila.
Also in Wilmington, Del., Easton, Pa., Allentown, Pa., Camden, N.J.

NEW VINYLITE FREQUENCY RECORD

33 1/3 & 78 RPM; 50 to 10,000 CPS; voice announcements; unmodulated grooves for checking rumble content. Available your local jobber or

UNIVERSAL RECORDING CORP.
20 North Wacker Drive
Chicago 6, Illinois

RADIO ENGINEERING!

COMPLETE Radio Engineering Course. Bachelor of Science Degree. Courses also in Civil, Electrical, Mechanical, Chemical, Aeronautical Engineering, Business Administration, Accounting, Secretarial, Science. Graduates successful 64th year. Enter Jan., March, June, Sept. Write for catalog.

TRI-STATE COLLEGE 15127 College Ave. ANGOLA, INDIANA

VERIFIED SPEAKERS

"Let The Guarantee Protect You Too"

WRIGHT Inc.

2232 University Avenue

St. Paul 4, Minnesota

ATTENTION: PROSPECTORS-EXPLORERS FIND HIDDEN TREASURES!

Do you seek hidden treasures or rare metallic ores? If so, construct a U.S. Army Type of Metallic Mine Detector from these U.S. Army Mine Detector Amplifiers that we are offering at a ridiculously low price. Complete Amplifier (as illustrated) (less tubes and batteries) with Battery case and cables. Cables, headphone cord and jack (no phones). Complete Army wiring diagram. U.S. Army DETECTOR SET Amplifier Type AN/FRS-1, as described. Only **\$2.95**



No C.O.D.'s. Eveready 45 volt batteries #482, \$1.65 ea., 6 volt A. 73c. 2-1N5 tubes, 95c ea. U.S. SIGNAL CORPS 5 METER SHORT WAVE XMTRS.

(72.2Mc) XMTRS and TUBE only, less mlke, batteries and antenna. One 1½ volt dry cell and 67½ volts of B operates it. Just attach di-pole, key or mike, connect the batteries and it's ready to use. Signal Corps spec. wired with silvered wire, mica condensers, and precision resistors. Highly stable circuit with Low Loss silvered inductance. (Adjustable paddler) Schematic supplied. Converts easily to walkie-talkie and Ham bands. Only **\$2.95**

No C.O.D.'s
FEDERAL SELENIUM RECTIFIERS
Lots of 12 65c
Single Lots 75c

BRAND NEW WESTON SENSITIVE RELAYS
MICRO-AMMETERS MODEL 705
(2½-0-2½ 2-0-2 range)
Cost Uncle Sam \$45.00. Our price **\$10.00** with A.C. Rectifier.

GENUINE SIGNAL CORPS FEATHER-WEIGHT HEADPHONES WITH CORD AND PLUG 2000 OHMS—8000 OHMS IMPEDANCE \$1.00

SPRAGUE—CORNELL—DUBILIER OIL FILLED FILTER CONDENSERS
1.—MFD—1000 working volts. **\$1.00**
4 for

WEBSTER RECORD CUTTING HEAD
Here is your opportunity to buy a genuine WEBSTER HOME RECORDING CUTTING HEAD. These units are all Brand new and were made for a nationally advertised manufacturer to be in their quality Home Recording Radios. Size 1½x2½ ready to fit your cutting arm or bracket. **\$2.95**

SPECIAL
NEWARK SURPLUS MATERIALS CO.
324 Plane Street Dept. N. Newark 1, N. J.

WAREHOUSE CLEARANCE

25 Lbs. **\$250** 25 Lbs.

Miscellaneous Radio Parts and Sub-Assemblies

- SWITCHES
- CONDENSERS
- RESISTORS
- INSULATORS
- DEFROSTERS
- MOTORS, 110 VAC
- THROAT MIKES
- ANTENNA BASES
- FUSE HOLDERS
- PILOT LIGHTS
- CABLES
- TRANSFORMERS
- SOLENOIDS
- HARDWARE ASS'T.
- TERM. BOARDS

Lots of other items . . . Hundreds of Pieces.

Remit with order only \$2.50 for each unit wanted. No shipments outside of U.S.A. Sorry, no C.O.D.

SPECIAL VALUES!

- NEON LAMPS, ¼ W., G.E. type NE 16, per 100 \$15.00
- SOCKETS, for the above (4 on a strip), per 100 10.00
- CAPACITORS, G.E. Pyranol, 1 MFD 500 V.D.C., per 100 30.00
- CAPACITORS, G.E. Pyranol, .25x.25 MFD 1000 VDC, per 100 30.00
- CAPACITORS, Indus. cond., 4 MFD 600 V.D.C., per 10 4.00
- RELAYS, Guardian Elec., 25 V.A.C. SPST, per 100 25.00
- RELAYS, G.E., 1 amp DPDT, 8000 ohms, 10 MA, per 8 2.50
- BATTERY CLIPS, Mueller, 25 amps, per 100 4.00
- MOTORS, Emerson, 24 V.D.C., series wound back geared, 100 RPM-Torque, 130 oz. ft. 3 x 6". Each 3.50
- TOGGLE SWITCHES, SPST, ¼" shank, screw term., per 100 15.00
- PILOT LITE, Dial Lite Co., 1" mounting, cand. base (red only), 125 V, per 100 35.00

GEORGE BROOKS & ASSOCIATES
777 West Adams Street Chicago 6, Illinois

LETTERS

from our readers

A COMPLAINT

"I think your mag is tops, except for the 'hire-purchase' system of your articles—'continued on page so and so.'

"The mag is full of time saving instruments, but to read about it is a hopeless case. Why not complete first one story and then start on the next one."

W. Niemann

Johannesburgh, South Africa

Yours is not the only complaint on this score, Mr. Niemann, but take it from us, it is not as easy to correct as you might think. We are doing everything we can to alleviate this situation.

ENGLISH RADIO

"WITH reference to your 'Letters from Our Readers' page in the September issue of RADIO NEWS and with particular reference to the letter from Robert Barlow, I would point out that International Reply Coupons are available at any main post office in this country, at a price of 6 pence (10 cents) each. These can be exchanged in almost any country in the world for local postage stamps, of a value to pay the ordinary letter post to the United Kingdom.

"I have sent these to two or three American manufacturers and all have replied to me. I would also mention that it is possible to obtain dollar currency, in the United Kingdom, to purchase technical publications.

"The great snag, of course, is when one decides to construct a device from an American circuit. Most U. S. receiving and low-power transmitting tubes are available at present here, being government surplus equipment, but of course this source will dry up soon. It is in the other components that the snag crops up.

"As an example, I was very kindly sent the specs on the 'R-9'er' by General Electric, and I decided to construct it. However, the construction notes state that the 'Q' of the coils must be high, and that the dimensions were critical. The notes specify certain Millen coil formers, without giving dimensions and of course unless one is prepared to spend a considerable amount of time and money on trying various coil formers which are made in this country, of which there is a very poor selection available at present, one has to give up the idea of being the proud owner of an 'R-9'er.'

"However, we're better off here than some countries in Europe, as we do have an industry which turns out high-class components, although only a limited range.

"As regards prices, ours are very

much higher than yours. The retail price of a new 807, manufactured in this country, is approximately \$6.50, although a government surplus 807 costs \$3.50. A 6L6 costs \$3.75, and standard r.f. pentodes, such as the 6SK7 and 6K7, cost \$2.50. (These prices are government controlled prices). A 1000 v. d.c. 100 µfd. variable condenser for a transmitter cannot be obtained much under \$4.00.

"As you can see from the foregoing, to build one's own receiver, or a 150 watt transmitter (which is the legal maximum here) costs one a very considerable sum, even if most of the components are purchased on the surplus market. For this reason, most people here try and make their gear as efficient as possible with the minimum of components.

"Finally, I would like to say how much I appreciate your magazine, and I hope to be a subscriber, the Chancellor of the Exchequer permitting, for many years to come."

N. H. Pettifor

Member, R.S.G.M. & A.R.R.L.
Sutton, Surrey

Thanks for the interesting sidelights on the radio game in England.

CYPRUS REPORTING

"LOOKING through my July issue of your excellent magazine RADIO NEWS, page 140, I came across 'We Get Around.' Yes, I guess you do at that!

"My wife wishes to thank you sincerely for the information sent along. "Our chief entertainment here is our SX-28A. I enclose a list of the few hams we get and thought you might like to pass them along in the issue. They might be interested to know that they can reach out to this little island."

S. C. Hanford

Skouriotissa, Cyprus Island

Thanks, Mr. Hanford, for your letter and your listing. He indicates that the following U. S. amateur stations can be heard in Cyprus; W1SI, W1GP, W2FG, W2AFQ, and W2QWS.

SOME FILE

"THE other night I was looking over some of my old back issues of RADIO NEWS and came across the enclosed ad from the August, 1935 issue. "Would it be possible to secure the booklet mentioned or a reasonable facsimile?"

G. V. Tatham
177 Grenadier Road
Toronto, Ontario

That certainly must be some file of back issues you have there Mr. Tatham.

—30—

RADIO NEWS

SERVICEMEN-AMATEURS

Why GUESS About Capacitors

For Only \$24.95 You Can Own a
SOLAR CB-160 ANALYZER



- Measures capacitance of electrolytic, paper, mica and air trimmers. Range from .00001 to 70 Mfd. in 3 ranges (48 in. of scale).
- Detects defective capacitors—directly indicates leaky, shorted, or wrong capacity units, and intermittents.
- Direct reading of all measurements eliminates extra charts.

• Measures power factor of any electrolytic directly on a scale in percentage.

• Cathode Ray Tube balancing—the "magic eye" 6E5 tube gives sensitive visual balance "Quick as a Wink."

• Measures resistance directly in ohms—50 ohms to 2 megs. in two ranges.

• Measures insulation resistance of capacitors and insulation at voltages up to 450—Self contained power supply.

(This instrument being offered at this low price due to slight damage on bottom of cabinets. Instruments otherwise guaranteed perfect.)

Solar CBB160—Same features as above except extended capacity range to 800 Mfd. **Special Net—\$34.95** (Reg. Price \$39.80). (Cabinets slightly damaged as mentioned above.)

Solar CF-160 Exam-meter—\$59.70—Combination condenser tester and vacuum tube voltmeter. This unit allows for checking condensers under actual load.

Also in stock for immediate delivery

Triplet 625N—10M/20M ohm per volt AC-DC multimeter	\$44.10
Triplet 2405—Square line—25M ohm per volt AC-DC V.O.M.	\$5.61
Triplet 666H—Pocket type—AC-DC Multimeter	19.60
Triplet 2413—Square Line—Tube Tester	48.51
Triplet 2432—Square Line—Signal Generator 75 KC to 50 MC	86.73
Radio City 802N—Combination Tube Tester and Multimeter	59.50
Radio City 461—20M per volt. AC-DC Multimeter	39.50
Radio City 447—1,000 ohm per volt. AC-DC Multimeter	17.95
Radio City 805—DeLuxe Tube and Multimeter	89.50
Radio City 705—Signal Generator	49.50
Radio City 710—Portable Generator. AC-DC	17.95
Radio City 776—Dynatracor—complete with tubes	29.95

ORDER NOW From this ad—immediate attention guaranteed. Write us about your requirements as we are glad to be of any assistance. All standard lines in stock.

ADSON RADIO CO.

221 Fulton St.

New York 7, N. Y.

Fixing Radios the Old Hard Way?



The Feiler Stethoscope does everything but make the actual repair. And the Stethoscope does it faster, better and much easier. Thousands of radio men, many with little experience, are already fixing radios and other electronic equipment this new way.

You will find that just this one low priced unit and a few basic hand tools are all you need to fix practically any radio.

Here is the new Model TS-5 "Pocket Stethoscope" built to take out on the job. It's light, compact and rugged yet performs like the bench models. Stethoscopes are available in 4 types ranging from \$9.85 to \$34.95.

The "Inside Story" of the STETHOSCOPE—how it works—how it instantly locates trouble in any circuit—is yours for the asking. The "Inside Story," a 24 page illustrated booklet, is full of practical tips and hints on radio servicing. To get your free copy, send your name and address on a penny post card today.

"MAKES RADIO REPAIRS AUTOMATIC"

Available for Export—Choice Territories Still Open



FEILER ENGINEERING COMPANY

945 George St. Dept. 12H7 Chicago 14, Illinois

December, 1947

TRIPLE BONUS---TRIPLE BONUS

the **GREATEST--**

yes, the **GREATEST--**

TEST EQUIPMENT story ever told

1000 pieces of **LATEST MODEL**, Standard Brand Test Equipment to be sold this month. **TUBE CHECKERS, SIGNAL GENERATORS, OSCILLOSCOPES, VTVM's, MULTITESTERS**, etc.

LABORATORIES, SCHOOLS, RADIO DEALERS, SERVICE MEN, HAMS, EXPERIMENTERS, STUDENTS:

Get a **TRIPLE BONUS** on **EACH** piece of equipment valued at \$40.00 or more. Just fill out the coupon below. Act now!

Buy for cash, on time-payment plan, or Radiomart lay-away plan

Radiomart

INC.

**Dept. RNA
149 Riverdale Ave.
Yonkers, New York**

I am interested in learning more about the greatest test equipment story ever told. Please send details of your great triple-bonus plan. I am particularly interested in buying the following equipment:

Name

Address

☐ Laboratory

☐ School

☐ Radio Dealer


☐ Service Man

☐ Ham

☐ Experimenter

WAR SURPLUS

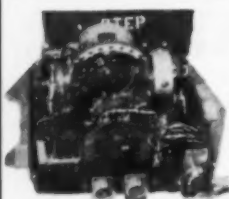
**BRAND NEW
COMPONENTS FROM FORMERLY SECRET
SPERRY "AUTO PILOT"**



**VERTICAL
GYRO UNIT**
Designed for
B-29 Superfort
ARMY PAID
\$2855.00
**YOU PAY ONLY
\$1495**

Less than 1/2 on the dollar!
Aluminum casing, housing one 400-cyc.,
115-v., 3-ph. motor propelled Gyroscope •
two 24-v. DC shunt-wound Motors • 2 Elec-
tronic Relays • Auto-Transformer • and
hundreds of other parts. A masterpiece of
precision. 15x14x9"; 36 lbs.

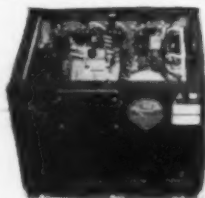**AMPLIFIER
RACK
WITH RELAYS
AND METERS**
GOVERNMENT PAID
\$100.00



**YOU PAY ONLY
\$695**


Consists of magnesium cabinet that mounts

- 7 DPDT Allied Relays • 1 SPST Relay
- 1 Weston 0-125 AC Volt Meter
- 1 350 to 450-cycle Frequency Meter
- 1 115-volt, 400-cyc. Transformer
- And many other parts

This unit is of special interest to "hams"! The cabinet would be excellent for small transmitters or receivers. 12 1/2 x 14 x 10"; 23 lbs.

You pay shipping costs. Send check or money order to

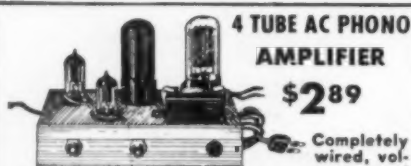SURPLEX RETAIL SALES INC.
2409 S. LaSalle St., Chicago 16, Ill.
Dept. RN-12, Phone CALumet 9130



**4 TUBE AC PHONO
AMPLIFIER**
\$289

tone controls. Complete with tubes; 2-9002;
1-6V6 or 6K6; 1-6X5.
6V6 output Trans. for above unit.....44c

Seaburg 2 post changer.....	\$19.95
Oak 2 post changer.....	\$7.00
G.I. or Alliance Motors.....	2.50
Astatic L-70 crystal pickup.....	1.89
Voi. Control & Sw. 1/2 meg. L. shaft.....	.45
Voi. Control 20,000 ohm.....	.20
Astatic Dynamic Mike & DN-HZ.....	12.10
Gen. Cement, dial cable & 73, 100 ft., heavy lines.....	1.95
AC-DC choke 250 ohm.....	.45
6 ft. rubber cord.....	.17
4" Speakers P.M.....	\$1.15
5" Speakers P.M.....	1.15
6" Speakers P.M.....	1.55
5" Speakers P.M. with 50L6 output.....	1.60
6 1/2" Speakers P.M. with 50L6 output.....	2.25
Wire, cotton on rubber covered, all colors.....	
20 Ga. stranded, per 1,000 ft. spool.....	\$5.00
22 Ga. stranded, per 1,000 ft. spool.....	7.00
Tubular electrolytic cond. Ea. per 10	
40x40 150v.....	\$0.45 \$4.10
50 150v.....	.20 2.75
30 150v.....	.25 2.25
10 50v.....	.15 1.25
.01, .05, .005, 600v.....	.05 .50
1-400v.....	.07 .50
.25-200v.....	.10 .80
.0004-2500v. transmitting cond.....	es. .20

"BABY GUARDIAN"
Speed phone-intercommunication system—2 way system
105 to 125 volts—AC DC—50 60
cycles—easy to install—economical to operate—efficient and dependable. Complete with 50 feet of cable.
\$1850
complete

ALL PRICES F.O.B. N. Y. C.
25% DEPOSIT, BALANCE C.O.D.

THE ROSE COMPANY
88 West Broadway, New York 7, N. Y.

Spot Radio News (Continued from page 20)

color, and language, but united in a common objective of furthering the technical means for world-wide understanding."

CONFIRMING THIS attitude was Charles R. Denny, recently-resigned chairman of the Federal Communications Commission and one of the ring-leaders at Atlantic City. He said: "To me, the cooperation, goodwill, patience, and perseverance of the delegates to the Atlantic City conferences were inspiring. They arrived with varying interests and with widely differing initial positions." (NOTE: For instance, U.S. gave up one major point—having permanent headquarters for international radio here. Switzerland was favored by many delegates, and U.S. voted with the majority.) "They made friends with each other. They worked hard. They worked with great skill. They solved numerous technical problems of immense difficulty. They submerged their individual differences for the common welfare. The success of their efforts insures the orderly use and the maximum growth of communications throughout the world." And P.S.—as we said before—will the United Nations please copy?

ONE THING that Mr. Denny found and frowned upon at Atlantic City and now points to with alarm is that, while other nations, almost without exception, are expanding their international broadcasting facilities, we are cutting ours down. When the war began, we had 13 short-wave transmitters sending programs to South America and Western Europe. During the war, this increased to 40, and by 1944 we were broadcasting over 1000 hours of programs in 40 languages and dialects each week. But today our operations are down to 232 program hours per week, leaving us a poor third in international broadcasting. Russia and England place first and second. "The Voice of America," in Mr. Denny's words, "has become a whisper." He adds: "Broadcasters have a duty even above and beyond their duty as citizens to take steps to insure that the United States plays its proper role in this important field. The voice that reaches out from our shores must be firm and clear. It must be heard throughout the world."

THAT FM IS STILL ROLLING along became dramatically clear following their first annual convention early in the fall, during which a number of new plans were revealed. One was the proposal that sets be built with, say, ten buttons, all but four of which would be tuned to variety-program stations. The other four would hook up with networks specializing in one type of feature only. There would be a net catching only classical music,



Rugged WCA outdoor speaker. Magnet 7 lbs. 30 watts. Complete with multiple use output transformer and voicecoil. Only \$9.95 at Almo. Model No. MI-2017-S.

10% Cash with Orders

ALMO
Covers the Globe

ALMO RADIO COMPANY
509 ARCH STREET PHILADELPHIA 6, PENNA.

BARGAINS

ARC 5 TRNSMTR 4 to 5.3 or 5.3 to 7mc with tubes & crystal.....	\$5.25
SENSITIVE RELAYS	
SIGMA SPDT type 4AH, 2000 ohms, 4ma close 1.5 ma hold, 5 prong shield plug-in #R28.....	.95
SIGMA same as #R28 but 2500 ohms #R29.....	.95
CLARE SPDT 3500 ohms, 6ma, #R30.....	.79
EDISON Thermal time delay, SPST norm open, 110 v A.C. or D.C., 45 sec. delay, 10 amp contacts.....	1.30
CHOKES & TRANSFORMERS	
OUTPUT, PP1L6 Class AB2 or 2A3 Class A to 1.5, 3, 5, 8 & 10, UTC PA Series 25 watts #T37.....	2.95
Class B INSTRSTGE driver plate to top Grids ratio 1 to 0.9, upright full shield #T38.....	1.50
25 lb FLTR, 50 ma 400 ohm ctr tappd, shield 2 1/4 x 4 1/2 #T36.....	.95
7-25 lb SWINGING, 300 ma 150 ohms, full upright shield 3 1/4 x 3 1/2 x 4 1/2 #T42.....	2.95
HI-VOLTAGE CAPACITORS	
0.0006 mf 2500 vdc Sanyo mica #C05.....	.95
0.02 mf 2000 vdc Aerovox mica #C06.....	1.25
0.2 mf 5000 vdc popular makes #C02.....	2.35

Write for additional lists of bargains in Radio & Electronic parts. Also Kits designed by ROBERT G. HERZOG.

Universal/General Corp.

(Dept. N-12)
365 Canal St., New York 13, N.Y. WALKER 5-9642

**FREE! VALUABLE
TECHNICAL DATA
About
NEW VIBRATORS**

Write for it today!
Postal card will do.

THE BEVITOR CO.
Box 5802, Cleveland 1, Ohio



**Amazing! POCKET
OR PURSE SIZE
NEW RADIO**

WORLD'S SMALLEST RADIO KNOWN!

Wt. only 1/2 lb. Beautiful Silver Black plastic case. Has Inductive Slide Tuning—W4 Crystal Diode—NO TUBES, BATTERIES OR ELECTRIC "PLUG IN" NEEDED! Should last for years!

GUARANTEED TO PLAY

on local stations if complete instructions sent are followed. Use it at home, in hotel, in many offices, hotels, cabins—most anywhere! HUNDREDS OF SATISFIED CUSTOMERS ALL OVER THE WORLD!

SEND ONLY \$1.00 (Cash, M.O. Check) and pay postman \$2.99 plus delivery less on arrival or send \$3.99 for Post Paid delivery. Complete as shown—ready to play with self contained personal phone. WONDERFUL GIFTS FOR CHILDREN! Order now at this low bargain price—Prompt shipment on orders sent now—today! Be the first to get YOUR Pocket Radio! (All foreign orders \$5.00 U. S. cash with order).

Pe-Kette Radio Co., Inc. Dept. RN-12 Kearney, Neb.

RADIO NEWS

another exclusively devoted to dance tunes, a third to features, a fourth to news. Thus listeners would be able to get what they wanted when they wanted it without so much as looking at a program or turning a dial. . . . How fast this type of broadcasting will become a reality depends on the speed with which FM itself develops audiences, but experts in the field say that such networks are not too far in the future.

THIS WAS A TOUGH YEAR for sunspots, according to the world's greatest authorities, who hasten to assure you that they will be able to predict future radio sunspot troubles with far more accuracy than formerly. This prediction of solar activity, which as you may know greatly affects radio communication and is evidenced by spots on the sun, has been advanced through the application of a new statistical method by two Americans—A. G. McNish and Virginia Lincoln, of the National Bureau of Standards. The method should also prove helpful in determining long-term weather variations and climatic changes. Teamed with the American method is basic information on sunspot numbers obtained from the Zurich, Switzerland, Observatory, which has kept records on all types of solar activity since long before radio was developed. Indeed, 1949 will mark the hundredth anniversary of the Zurich records. Also helping the Bureau of Standards experts are amateurs belonging to the American Association of Variable Star Observers as well as professional sources such as the Naval Observatory.

SUNSPOT HARVEST this year will be among the biggest of all time, the researchers report. May ran the highest score. The May record was preceded by the three largest sunspot groups ever observed in February and July, 1946, and in March and April of this year. The February group of '46 covered an area on the sun's surface of over a hundred times the area of the earth's disc. On the other hand, at times in a sunspot cycle, they reach almost zero. This was true in April, 1944, when only one sunspot showed for the entire month. The importance of sunspot prediction is shown by comparison of radio transmission in 1944, a lean year, and this year, a record-breaker. During '44, transmission across the North Atlantic was rarely possible for frequencies above 20 megacycles. During '47, when the extremely high annual sunspot number of 126 is predicted, already transmissions using frequencies above 50 mc. have been logged over this path.

EVERYBODY USING radio in a big way follows the Bureau of Standards predictions closely. This includes airlines, steamship lines, television and radio schools, universities, radio and telegraph companies, manufacturers of communications equipment, con-



TELEX MONOSET— WHEREVER, WHENEVER HEADSETS ARE REQUIRED

MODERN • LIGHTWEIGHT • COMFORTABLE

Cleverly designed in tough durable Tenite, the TELEX Monoset is quickly replacing old-style, cumbersome headsets because it is made to wear under the chin instead of over the head. Precision-built magnetic receiver assures excellent fidelity.

The NEW Monosets incorporate a volume control feature that permits the wearer to control volume of sound at the point of reception. Write Department AU for information.

Specifications

IMPEDANCE

2000 ohms—Part No. 2568
500 ohms—Part No. 2569
128 ohms—Part No. 2570

SENSITIVITY

88 d.b. above .000204 dynes per square centimeter for 10 microwatt input.

HEARING AT ITS BEST



TELEX INC.

ELECTRO-ACOUSTIC DIVISION

TELEX PARK
Minneapolis, Minn.

Canadian Distributors:

Addison Industries, Ltd., Toronto

RADIO COURSES

- RADIO OPERATING • CODE
- RADIO SERVICING — ELECTRONICS
- REFRIGERATION SERVICING

Personal Counselling Services for Veterans
Write for Latest Trade & Technical Catalog
Y.M.C.A. TRADE & TECHNICAL SCHOOLS
7 W. 64th Street New York City

In
Indiana
IT'S

Stanton Radio Supply
521 State St.
HAMMOND, INDIANA


UTICA TOOLS



ALL TYPES
FOR MORE
TOOL MILEAGE
Ask Your Dealer

**UTICA DROP FORGE
AND TOOL CORPORATION**
UTICA 4, NEW YORK

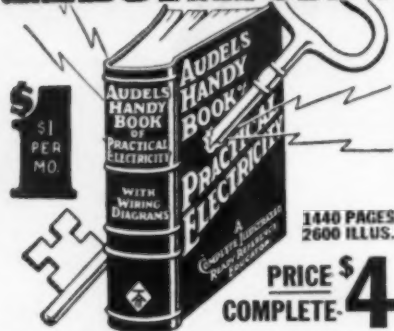KEY TO A PRACTICAL UNDERSTANDING OF ELECTRICITY



● **AUDELS HANDY BOOK OF ELECTRICITY** for Maintenance Engineers, Electricians and All Electrical Workers. A quick, simplified, ready reference handy book, giving complete instruction and practical

● **INSIDE TRADE INFORMATION ON** rules and laws of electricity—maintenance of electrical machinery—A.C. and D.C. motors—armature winding and repair—wiring diagrams—house wiring—power wiring—cable splicing—meters—batteries—transformers—elevators—electric cranes—railways—bells—sign flashers—telephone—ignition—radio principles—refrigeration—air conditioning—oil burners—air compressors—welding and many modern applications explained so you can understand. All indexed for ready reference.



To get this assistance for yourself, simply fill in and mail the **FREE EXAMINATION COUPON** below.

AUDEL, Publishers, 49 W. 23 St., NEW YORK 10, N.Y.
Please send me "Audels Handy Book of Practical Electricity" for free examination. If satisfactory, I will send you \$1 in 7 days, then \$1 monthly until \$4 is paid. Otherwise I will return it.

Name _____
Address _____
Occupation _____
Employed by _____ **RN**

FM—RADIO—TV TRAINING FREE BOOKLET NOW AVAILABLE

This new booklet gives you the facts you want to know before you enroll in any school. Profusely illustrated, interesting and factual. Enables you to check why WRCA SPECIALIZED TRAINING METHODS are outstanding in the West; why WRCA laboratory trained specialists are preferred for responsible high paying positions in the fields of Radio Communications and Radio-Television Servicing. Choose your school with care; read this 16 page booklet before you enroll anywhere. Our course is approved for veteran training. Get your free copy of this revealing booklet now. Send a penny postcard or letter today. Please mark it Dept. N for quick service, and address:

WESTERN RADIO COMMUNICATIONS INSTITUTE
431 West Ninth Los Angeles 15, Calif.
Member Los Angeles Chamber of Commerce

MILES "TELEMIKE"

A midget unit (1 1/4" x 1 1/4" x 1 1/4") requiring no physical contact to telephone. PICKS UP BOTH SIDES OF TELEPHONE CONVERSATIONS for group loud speaker listening or for recording when used with standard amplifier or recorder. PRICE \$25.00 postpaid. Write for details on our complete line of FILMGRAPH TELEPHONE—CONFERENCE—DICTATION—"TALKIE" RECORDERS & REPRODUCERS.

MILES REPRODUCER CO., Inc.
Dept. RN-12, 812 Broadway, New York 3, New York.

PEN-OSCIL-LITE

Extremely convenient test oscillator for all radio servicing; alignment ● Small as a pen ● Self powered ● Range from 700 cycles audio to over 600 megacycles u.f. ● Output from zero to 125 v. ● Low in cost ● Used by Signal Corps. ● Write for information.

GENERAL TEST EQUIPMENT
38 Argyle Buffalo 9, N. Y.

sulting radio engineers, newscasters, research labs, and electric power companies. Federal agencies, among them the Weather Bureau, State Department, FCC, CAA, the Forest Service and the Coast Guard, are also steady customers. Bureau of Standards issues predictions each month for the following three months.

COULD BE YOU ARE ALREADY FAMILIAR with the electronic analog, the radio brain that can calculate three million times faster than the human mind, but here are a few items on it that you may have missed. They were recently released by the men who developed the gadget. The fathers of the device are W. T. Stark and W. C. Schaffer of the Wright Engineering Department and C. A. Philbrick of Philbrick Researches. The analog can solve over a million mathematical operations in a single day, operated by a single engineer. Put it another way—in one two-hundred-and-fortieth of a second it can crack a problem that would take a highly-trained engineer or mathematician a full day to solve. Wright is using the machine to solve various problems covering a wide range of engine types. A typical one; investigating the attainment of temperature control under conditions of maximum power and efficiency in a jet engine. Expensive engine operation was minimized by designing control components from the analog data. Thus time-consuming tests were drastically cut without subjecting the engines to possible damage under actual test. . . . In operating the analog, a skilled expert presents the problem to the machine by setting a number of dials and reading the answers on either of two screens similar to those used in television sets. The answers are given in graphs intelligible to trained technicians, and are permanently retained by a camera which takes pictures of the screened solutions.

WITH ITS MOST successful National Radio Week (Oct. 26-Nov. 1) now a matter of history, the industry, this time under the leadership of the National Association of Broadcasters, is staging another nation-wide campaign, this time against juvenile delinquency. Justin Miller, president of NAB and spearhead of the campaign, has launched it by urging the public to "call on radio to help with increasing frequency." "Broadcasters," he added, are becoming increasingly conscious of their civic responsibility and are not only willing but anxious to cooperate with local government officials in all movements for community welfare."

BEFORE SOME NORTHERN COMMUNITY is snowed in and learns the value of ham radio in keeping them in touch with the outside world, mention should be made of amateur work done during the recent devastating Florida hurricane.

RISCO HAS IT

All Changers Brand New

V. M. MIXER CHANGER



\$15.50

Above Easily Attached to Any Radio or Can Be Used WITH AMPLIFIER BELOW

PHONO AMPLIFIER



3 TUBE AC-DC
Wired Vol. & Tone Control \$2.75

Uses 12SQ7, 50L6, 35Z5.
Wired & Tested—
Set of 3 Tubes . . . \$1.95
Output Trans.39
5" Alnico Spk. 1.19
DIAGRAMS for any radio sent prepaid 50c. as to cover cost of printing & mailing.

25% on C.O.D. orders. Orders Filled as Received, Free Catalog Just Out. We Sell Retail. We Specialize in Mail Orders.

RISCO ELECTRONICS WHOLESALE DISTRIBUTORS

22 Warren St., New York 7, N. Y.

S.S.S.

"Servicing by Signal Substitution"

Learn about this modern dynamic approach to radio servicing with ONLY BASIC TEST EQUIPMENT.

... Fully described in a 120 page book available from your Precision Distributor or factory at 35c.

... Schools are invited to inquire regarding quantity orders from our Educational Division.

PRECISION APPARATUS COMPANY INC.

ELMHURST 9, N. Y.
Manufacturers of Fine Test Equipment
RADIO • TELEVISION • ELECTRICAL • LABORATORY

GREYLOCK

A DEPENDABLE NAME IN RADIO TUBES

GT, Glass, and Miniature Types
12SA7—12SK7—12SQ7—50L6—12AT6—12BA6—
12BE6—35W4—50B5—each 39c
1A7—1R5—1R5—1T4—3S4—each 49c
32L7—70L7—117L7—each 59c
All Tubes Carry RMA 90-Day Guarantee.

PM SPEAKERS

4" Alnico No. 5 each \$1.19
5" Alnico No. 5 each 1.29
Special Crystal Pickup for 3-tube Amplifier 1.49

TERMS: Net C.O.D. No order accepted for less than \$5.00.

Write for Bargain Catalog
GREYLOCK ELECTRONIC SUPPLY CO.
30 Church Street New York 7, N. Y.

MULTI-METER

Save \$\$\$ by constructing your own test meter. OPERATES ENTIRELY FROM 110 v.a.c. or 45 volt "B" battery. Ranges: 0-10/100/500/5000 v.d.c., 0-10/100/200 v.a.c., 0-300/300,000/10,000,000 ohms 0-1/10/100/1000 m.a. Can be used as "B" BATTERY ELIMINATOR for portable radios. 30 min. to assemble. Meter, completed panel, and all parts included. PRICE \$14.65 postpaid. Special test leads —\$1.00.

METER MASTER

Box 51, Berkeley, Calif., Dept. 12.

PROJECTION TELEVISION

Adapt your present RCA, GE, Crosley, Philco television receiver for a 6x8 foot projected picture with the addition of a 30 KV-RF power supply and a 5TP4 projection lens assembly. Complete pictorial construction details of the 30 KV supply and projection system based on actual New York tavern installations described in booklet just published at \$2 each, postpaid.

PERFORMANCE RADIO CO.
2898 Jerome Avenue, New York 58, N. Y.


Authorized by the Federal Communications Commission, the ham network in Florida started operations almost before the big blow had died down to bridge the communications gap caused by downed wire circuits. FCC monitoring stations at Powder Springs and Miami were ordered to stand by, and P. H. Herndon, Jr., Atlanta FCC man, rushed to Miami to coordinate the work. Everything on the ham circuit was ready for activity before the first wire communications, telephone links between Atlanta-Miami and New York-Miami, went down. Aided by the American Radio Relay League, FCC cleared amateur frequencies between 3905 and 3915 kc., enabling hams within 1000 miles of West Palm Beach to get messages out. Coordinating the work up North was the FCC monitoring station at Laurel, Md., and more than 1000 hams in the greater Washington area got in on the job. Typical of their reaction to the work was the comment of Maj. Burke Edwards of Chevy Chase, Md., who spent most of his time during the night that the hurricane was at its height answering queries of relatives on the welfare of their loved ones in the stricken area. Asked if he had been bothered by the requests, Edwards said: "Bothered? No. We're always glad to be of help."

TELEVISION FOUND A NEW USE recently when the first public view of surgeons performing operations was televised for the benefit of doctors attending the eighteenth annual scientific assembly of the District of Columbia Medical Society in Washington, D. C. The operations were televised from Georgetown and Doctors Hospitals to the Statler Hotel, where the medics assembled. —30—

Constant and continuous radio contact by the AAF in Washington with aircraft flying anywhere in the world is made possible by the new Signal Corps-engineered rotary beam which depends on rotating, receiving and transmitting antennas which point in the direction of and "follow" aircraft in flight. The planes need no special radio equipment for this communications miracle. Here AAF officers explain the new beam to a visiting scientist as S/Sgt. Edwin B. Rosenberg of River Falls, Wisconsin climbs up an antenna tower to make an inspection.



December, 1947



Wishing you a
Merry Christmas
and a
Prosperous New Year

**MEISSNER
 RADIART
 THORDARSON**

MAGUIRE INDUSTRIES, INCORPORATED

ELECTRICAL TRAINING

Intensive 32 weeks' residence course in fundamentals of industrial electrical engineering, including radio, electronics. Prepares for technician, engineering aides. Approved for veteran training. 54th year. Catalog.

BLISS **ELECTRICAL SCHOOL**
 7698 Takoma Ave.
 Washington 12, D. C.

NOW "Sound"
FOR YOUR SILENT PROJECTOR
Economically

\$5995

Convert your 16mm silent projector to sound (regardless of make) with Apex sound head & radiofilm adapter. Guaranteed excellent performance. Write today for free information.

APEX VIDEO • 12209 J Branford St. • Roscoe, Calif.

Latest RCA Television Schematics

- RCA 7" Model 621TS
- RCA 10" Model 630TS, 630TCS
- RCA 10" Model 641TV
- RCA Projection Model 648PTK

ALSO PREWAR RCA MODELS

- TRK5, • TRK9, • TRK12

Large Clear Prints with All Component Values Marked

50c ea. Postpaid

Send Check or Money Order

BRITE-RAY TELEVISION CO.

7 Clinton St.

Brooklyn 2, N. Y.

"America's Best Buy"

TUBULAR ELECTROLYTICS

Fresh Stock. Fully Guaranteed

	Each	10	100
20 mfd..... 150V	\$0.21	\$1.79	\$18.9.
20-20 mfd..... 150V	.29	2.49	22.98
8 mfd..... 450V	.19	1.85	17.90

BY-PASS CONDENSERS


.01..... 600V	\$0.06	\$0.55	\$ 4.65
.02..... 600V	.06	.55	4.71
.05..... 600V	.06	.55	4.95
.1..... 600V	.07	.65	5.49
.25..... 600V	.11	.98	8.95
.005..... 1700V	.14	1.25	9.95
.01..... 1700V	.15	1.30	10.20
.02..... 1700V	.16	1.43	10.9.

RESISTOR ASSORTMENT

100 assorted $\frac{1}{4}$ - $\frac{1}{2}$ watt carbon resistors.
All RMA color coded. Special \$1.29.

CRYSTALS 74c each

Your frequency plus or minus 10 KC

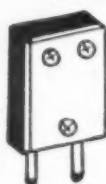

80	Meter, 3500-4000KC
40	Meter, 7000-7300KC for multiplying into
20	Meter, 7300-7425KC
10	Meter, 7300-7425KC
6	Meter, 6250-6750KC
2½	Meter, 8000-8222KC

Postage extra. 20% deposit on COD.
Write for latest bargain list featuring

"America's Best Buys."

POTTER RADIO CO.

1314 McGee St., Kansas City 6, Mo.

International Short-Wave

(Continued from page 154)

larly around 0400-0500 on 9.54, 11.78, beamed to Australia. (Radio Australia) QRA is P.O. Box 3045, Wellington, New Zealand. (Cushen)

Nicaragua—YNEW, 8.190, Managua, heard several times lately testing with records and with regular Spanish programs; good level evenings. (Nankervis) HTX1, 8.320, Managua, is heard evenings through heavy CWQRM; the "HT" prefix is assigned to Nicaragua in addition to "YN" prefix. (Legge via NNRC)

Northern Rhodesia—ZQP, Lusaka, is scheduled week days 1000-1200 on 7.220, 3.900, 9.710; Sundays to Europeans at 0400-0530 (news at 0400). The stations also transmit on Sundays at 1030-1130, although official schedules do not list this transmission. The 9.710 channel is heard on the West Coast, best on Sundays around 1030-1115, using English and native, period includes religious services. (Dilg)

Norway—Our Norwegian monitor, Bjorn Sundby, lists Norwegian schedules as LKJ, 9.54, Oslo; LLS, 15.17, Tromsø; LKQ, 11.735, and LLJ, 6.185, Fredrikstad, at 1100-1700. These stations relay the Home Service.

LKV, 15.170, Tromsø, was recently logged in Pennsylvania on a Sunday at 1500-1600, in clear. (Kary)

Palestine—Roland Peddle, Newfoundland, reports JCKW, 7.22, "The British Forces Station" in Jerusalem heard well on Sundays (may be Saturdays) around 1700-1815 closedown with a "Midnight Special" program; announces as beamed to Western Europe, North Africa, and East Asia; has program summary at 1645 Sundays and Wednesdays; gives QRA as British Forces Radio, 1st Unit, British Forces, Jerusalem, Palestine. Schedule is 1400-1600 except Sundays (may

be Saturdays) and Wednesdays when runs to 1815.

Jaffa appears to have added 9.653 to its frequencies. (Pearce) Has been heard in California on this "new" channel.

Philippines—KZRH, 9.64, Manila, is heard in Sweden signing off at 1100. (Nilsson) Full official schedule is 1700-1100.

KZRC, about 6.13, is heard on the West Coast announcing at 0850, nice level. (Balbi) This station, listed officially as 6.140, is affiliated with KZRH, Manila, and is located at Cebu. Operators of these stations project another SW outlet, to radiate in the 25-meter band. Cebu leaves the air at 1000.

"The Voice of America in Manila," 11.84, appears to be scheduled 0400-1005; has late news at 1000. (Balbi)

Radio Australia reports that KZRM has returned to the air on its prewar channel of 9.570, heard at 0500. The Philippine outlet widely reported on 9.515 is KZFM (Dilg).


KZPI, 9.500, is on the air 1700-1100 daily and on Saturdays (in America) runs full 1100-1100 (Sundays). KZOK, 9.690, is scheduled 24 hours a day except 1100-1630 Saturdays when its transmitters are off the air for maintenance. (KZPI is on during those hours.) Frequencies of KZPI and KZOK appear to vary.

Poland—Warsaw, 6.115, at last report had news yet at 1450; at 1515 on Saturdays has news in Yiddish. (Miers) The English news may be changed by this time to 1550-1610, this being the schedule last winter.

Portuguese China—CR8AA, 9.248, Macao, wants more reports. (Cushen) Present schedule is not known but probably is mornings to around 0915 or 0930. Not reported lately in U.S.

Rumania—Bucharest, 9.253, now has news at 1315; announces, "This is Rumanian Short Wave Station Dekka-Rumania on 25 meters and 32.4

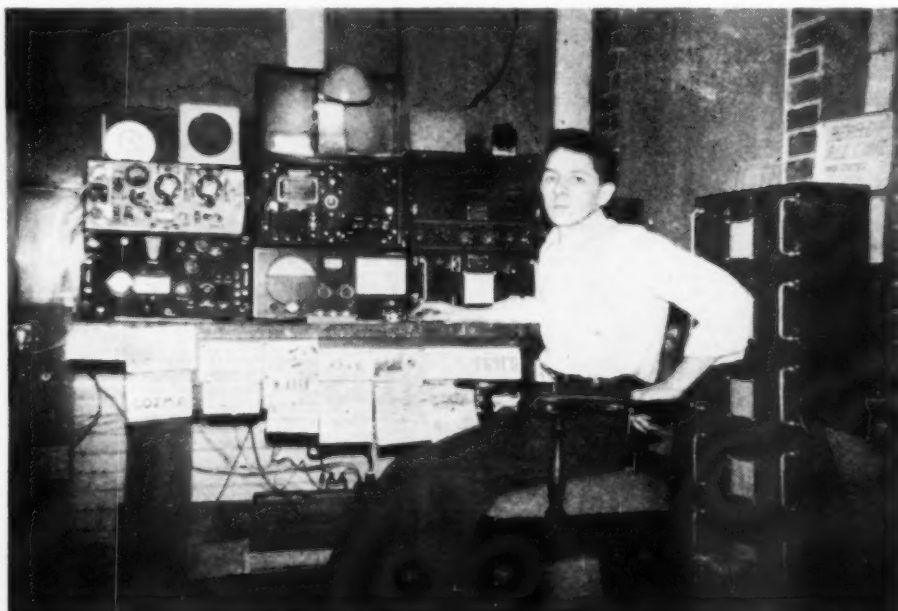This well-equipped listening post belongs to Wally Moore, Lawrenceburg, Tenn.




Serving the
RADIO TRADE
since 1929

Just **3** JFD
ADJUSTABLE
BALLASTS

Replace
Over **3000**

Exact Duplicate
AC-DC
Resistance Tubes!

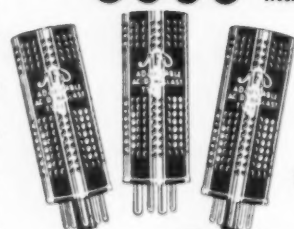

List
Price

\$1.50 each

New features!

- ✓ 1. Air-Cooled Perforated Shell
- ✓ 2. Larger Insulating Surface
- ✓ 3. Longer Life, Heavier Resistance Wire
- ✓ 4. Exact Adjustments made

Buy these essential JFD parts from your
Nearest Parts Jobber



Write for COMPLETE JFD CATALOG today!

MANUFACTURING CO. Inc.


4111 Fort Hamilton Parkway
Brooklyn 19, New York, U.S.A.

FIX ANY RADIO

Amazing New Invention



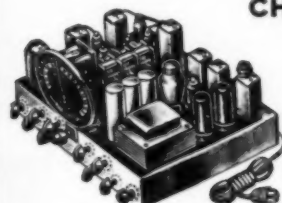Find radio faults with a new simplified method. Repair all radios in minutes instead of hours. Revolutionary, different Comparison technique permits you to do expert work almost immediately. Most repairs can be made without test equipment. Simplified point-to-point, cross-reference, circuit suggestions locate faults quickly and easily.



PRICE ONLY
\$1.50
COMPLETE

REPAIR RADIOS WITHOUT TESTERS NEW METHOD DEVELOPED BY BEITMAN

This newly developed method tells you how to locate the source of trouble in any radio set without equipment. Make needed tests, measure voltage, trace the signal, by using only a 5¢ resistor, small condenser, and a crystal detector. Inject signals without any signal generator. Test parts by the new Comparison method. Test tubes without equipment. Repair any radio expertly following simplified picture plans. Improve your radio servicing ability. Data on all sets, portables, AC-DC, FM, recorders, intercoms, P.A. Examine and apply the plan for 10 days without obligation or risk. Send trial coupon today

CHARTS, BLUE-PRINTS, TESTS, HINTS, JOB-SHEETS

Learn time-saving trouble-shooting short-cuts; find any radio fault with ease. Follow the tests shown on 24 large circuit blue-prints. Over 1,000 practical repair hints. For all types of radios. Hundreds of simplified tests using a 5¢ resistor and any filter condenser. Introductory material for beginners and to serve as review for experienced radio men. Several chapters on test equipment. Complete plan in manual form, 61 job-sheets, data on all tubes, 84 large pages, 8½x11 in. Schematics, pictures, charts. Sold on no-risk trial. Price, only \$1.50. Send coupon.

NO RISK TRIAL ORDER COUPON

SUPREME PUBLICATIONS

9 S. Kedzie Ave., Chicago 12, Illinois

Ship postpaid the new complete Simplified Radio Servicing by Comparison Method manual for 10 days' examination. I am enclosing \$1.50, full price. I must be entirely satisfied or you will refund my total remittance.

Name:

Address:

Manufacturers—Jobbers—Dealers—Radio Schools & Repairmen


HERE ARE NEW OFFERS—THE PRICES SPEAK FOR THEMSELVES!

RADIO TUBES—KNOWN BRANDS—BULK

	Each
80, 5U4G, 5Y3GT, 5Y4GT.....	\$0.42
35W4, 25Z5, 25Z6GT, 35Z5.....	.45
6F5G, 6F6GT, 6J5, 6SA7, 6SK7, 6SQ7.....	.47
12BE6, 12BA6, 12AT6, 12SK7, 12SA7, 12SQ7.....	.49
6H6, 6J7, 6K7, 6Q7, 6SF5GT, 6SN7GT.....	.55
5Z3, 35A5, 35L6, 50B5, 50L6.....	.55
43, 6A7, 6A8, 6V6GT, 25L6GT.....	.59
OZ4, 6X5GT, 7A8, 7B4, 7B5, 7B7.....	.65
1A5GT, 1A7GT, 1H5GT, 1N5GT, 1R5, 1S4, 1S5.....	.74
1T4, 3Q4, 3Q5GT, 50A5, 14A7, 14B6, 14Q7.....	.79
6AC7, 6L6G, 25A6G, 35Y4, 117Z6GT.....	.95
1LA6, 1LE3, 1LN5, 70L7, 117L7GT, 117N7GT.....	1.35

VOLUME CONTROLS, ¼ or 1 Meg. with switches.....	\$ 0.39
OUTPUT TRANSFORMERS, match 50L6.....	.39
VARIABLE CONDENSER, 2-Gang, 420/162.....	.68
VARIABLE CONDENSER, 3-Gang, 420/420/420.....	1.17
SOLDERING IRON, 60 Watts, list price \$2.95.....	1.77
SOLDERING IRON, 100 Watts, list price \$3.95.....	2.37
ELECTRIC MOTOR, with 9" Turntable.....	2.95
CRYSTAL PICK-UP ARM.....	1.75
CRYSTAL CARTRIDGE, fits most pick-ups.....	1.25
4" PM SPEAKER, Alnico No. 5, 1-oz. Magnet.....	.95
5" PM SPEAKER, Alnico No. 5, 1-oz. Magnet.....	1.22
DETROLA AUTOMATIC RECORD CHANGER.....	13.50
BROOKS INVERTER, 50 Watts, 110 V.....	8.95
LOOP ANTENNAE, assorted sizes, oval.....	.39
I.F. COILS, 456 Kc.....	.49
TOGGLE SWITCHES, SPST—15¢, DPST—25¢, DPDT—40¢.....	
LINE CORD, 6 feet.....	.14
RESISTANCE CORDS, 160, 180, 220, 290 ohms.....	.49
OSCILLATOR COIL, 456 Kc.....	.19
RESISTORS, ½ Watt, 100—assorted.....	1.50
SOCKETS, 100 assorted.....	4.50

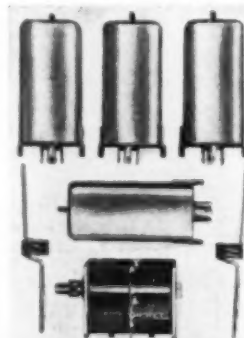BUILD YOUR OWN FM TUNER FM — CONDENSER & COIL KIT — (88 to 105 Mc)



Variable Condenser
Discriminator Coil
2—I.F. Coils
1—Limiter Coil
Antenna Coil
Oscillator Coil
Schematic Diagram
Instruction Chart

\$4.95

PAPER TUBULAR CONDENSERS

100—assorted, .001 to .02, 200 to 600V.....	\$3.95
.001—600 V, per hundred.....	3.95
.002—600 V, per hundred.....	3.95
.005—600 V, per hundred.....	4.40
.01—600 V, per hundred.....	4.40
.02—600 V, per hundred.....	4.40
.05—600 V, per hundred.....	4.95
.1—600 V, per hundred.....	7.20

ELECTROLYTIC CONDENSERS

	Each
10—150 V.....	\$0.22
20/20—150 V.....	.26
30—150 V.....	.28
40/40/20—150 V, 25 V.....	.44
8—450 V.....	.27
10—450 V.....	.32
16—450 V.....	.36
16/16—450 V.....	.59
20—450 V.....	.39
30—450 V.....	.47
40—450 V.....	.54

BROOKS RADIO DISTRIBUTING CORP.
80 VESEY STREET • DEPT. B NEW YORK 7, N. Y.

CO. 7-2312

**WE SHIP ANYWHERE
IN THE WORLD**
Internationally Famous

FLANAGAN RADIO CORP.

**RADIO TUBES
UP TO 80%
OFF
STANDARD
LIST PRICE**



FREE CATALOG

Send for free catalog and prices of hard-to-get Radios, Radio Tubes, Radio Parts, Pickups, Motors, Condensers, Tube Checkers, Volt and Ohm Meters, Signal Generators, Signal Tracers, etc.

**FLANAGAN
RADIO CORP.**

America's Largest Stock of Radio Tubes
MAIL ORDER DIVISION
5251 MARKET ST.
PHILA. 39, PA.

THE "Book" RADIO

The Lightweight Portable
that Plays Anywhere!



COMPLETE KIT

\$9.95

less batteries

FEATURES

- 4" PM Alnico Speaker
- Fingertip control of station and volume.
- Four miniature tubes.
- Size: 7 1/2" x 9 1/2" x 3"
- Weight: Only 4 lbs.
- Leatherette bound.

Here's the ideal gift for Xmas . . . the ideal radio for everybody.
Send \$3.50 with order. Balance C.O.D.

**GENERAL RESEARCH
LABORATORIES**

222 St. Marks Avenue
Brooklyn, New York
Dealer's Inquiries Invited

meters." (Pearce) *Has anyone heard this one on 25 meters?*

South Africa—ZBB is the callsign of the new South African Air Force station heard testing on 7.445, leaving the air at 0140; asked for reports to O/C, 64 Air School, Waterkloof, District Pretoria, South Africa. ZBB is to be used primarily for providing reports on weather, ionospheric conditions, and other data useful to pilots. The proposed program calls for hourly weather reports and other data every two hours; music will be used to fill in the gaps. Major N. Thomas of the station informs that the transmitter is an AVT RCA, 5 kw., feeding into a Kraus antenna (three half-wave dipoles folded back on themselves). Reports from overseas are welcome, the Major stated, and will be acknowledged. *No IRC required.* According to South African newspapers, the station is actually operated by the Telecommunications Branch of the Department of Defense at Pretoria, using S.A.A.F. transmitting facilities at Waterkloof (about two miles outside Pretoria). (Laubscher)

SABC, Johannesburg, lists current schedules as follows:

Johannesburg—No. 3, 5 kw., 3.450, not operating; 4.895, daily, 1050-1605; 6.007, week days at 2345-0130, Sundays at 0055-0110; 9.523, week days at 0315-0710 and 0900-1040, Sundays at 0315-1040; 11.710, not operating. No. 4, 1 kw., 6.095, week days at 2345-0130, 1120-1605, Sundays at 0055-0130, 1120-1605; 9.870, week days at 0315-0710, 0900-1110, Sundays at 0315-1110. No. 5, 4.373, week days at 2345-0130, 0315-0710, 0900-1605, Sundays at 0055-0115, 0400-1605.

Cape Town—No. 3, 5 kw., 5.887, week days at 2345-0130, 1100-1605, Sundays at 0055-0110; 9.61, week days at 0315-0710, 0900-1045, Sundays at 0315-1045.

Pietermaritzburg—No. 2, 0.5 kw., 4.878, week days at 2345-0130, 0315-0710, 0900-1605, Sundays at 0055-0115, 0400-1605.

International regulation has caused SABC to change the 9.912 Johannesburg frequency to 9.870, as the former was outside the allocation. (Laubscher)


Surinam—PZR, Paramaribo, appears to have moved from 11.332 to about 10.970; good signals evenings but has bad CWQRM. Uses many U.S. popular recordings, announcements are in Dutch, signs off with Dutch National Anthem around 2035. *No English noted.*

Switzerland—Berne appears to be using 9.535 now in the 1730-1815 beam to North America. (Worris) Watch for United Nations Radio, Geneva, on 9.515; heard irregularly with news bulletin, sometimes at 1430; wants reports to European Office of United Nations, Geneva, Switzerland.

Syria—According to *Radio Australia*, "Houna Damaash" is identification of the Damascus station operating on 6.000; schedule is 0000-0030, 0530-0630, 1100-1600. Uses mostly

PITCO LINE FILTERS

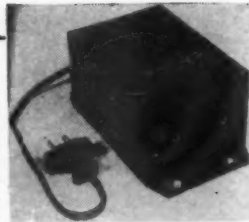- 5 Amp. 110-220 Volts, A.C. or D.C.
- 10 Amp. 110-220 Volts, A.C. or D.C.



Highest Quality . . . Dependable Performance

Exhaustive tests and actual operating performance have definitely proven the superiority of the Pitco Line Filter over other designs. This dependable unit presents a solution to the problem of serious radio interference from power lines, motors, and appliances . . . provides inductance as well as capacitance, thereby assuring thorough filtering action.

The Pitco Line Filter plugs into the electrical outlet and can be connected at the receptacle of the filter with either the radio set or interfering device. Wherever installed, you'll find this sturdy, compact filter is unsurpassed for high quality and outstanding performance.

See the Pitco Line Filter at your local distributor today. He has both the 5 Amp. and 10 Amp. sizes ready for immediate delivery.

FOR COMPLETE DETAILS, SEE YOUR DISTRIBUTOR OR WRITE DIRECT.

Pittsburgh Coil Co., Carnegie, Pa.

Coils • Test Leads • Line Filters • Indoor Aerials

RECORDS


LATEST & HARD-TO-GET BACK NUMBERS

Some slightly used and some brand new—Victor, Bluebird, Columbia, Okeh, Decca, Capitol, etc. Such artists as Glenn Miller, Benny Goodman, Harry James, Bing Crosby, Frank Sinatra, Gene Autry, Duke Ellington, Fats Waller, Guy Lombardo, Andrews Sisters, Kate Smith, Ink Spots, Mills Bros., etc.

BIG PROFITS Your opportunity to cash in on this new field that is sweeping the country. Specify the type of music that sells best in your territory such as Swing, Sweet Music, Cow-boy, Hill-billy, Polkas, Blues, etc. Your price \$13.90 per 100 records, f.o.b. Chicago, 2% off for cash with order. All shipments made within 48 hours.

CHAS. HOODWIN CO.

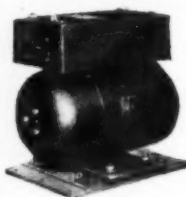4419 Broadway, D-13 Chicago 40, Illinois
World's Largest Dealers in Used Records



L. I. Specials

Dynamotor BD77L illustrated. 12 volt input, 1050 volt 350 ma. output, complete w/filter, starting relay, mounting and manual, NEW, ea. \$5.35
Dynamotor PE73, same as above except for 24 volt input. USED, less manual, ea. \$4.95

Extension Cord for HS33 headset, complete w/JK26 Jack on one end and PL55 Plug on other. Ea. \$0.27
MC211A, Right Angle Coupling for SCR274N. NEW, ea.75
MC203A, "T" Coupling for SCR269. NEW 3.90
Flexible Tuning Shaft for SCR274N, 79" length, complete w/ferrules, spline, etc. NEW, ea.1.45
BC375 Tuning Units (TU5 to TU26) complete w/black crackle finished case. USED, ea.1.95
M299 Microphone Adapter. Allows use of carbon microphone on SCR522. NEW, ea.1.35

All prices F.O.B. Flushing, N. Y.

See our list of Schematics in October Radio News

LONG ISLAND RADIO CO.

164-21 Northern Blvd. Flushing, New York

Radio Technician and Announcers

A practical 15-month course in First Class Radiotelephone Operation and Announcing is offered by Don Martin School of Radio Arts. Most stations these days require combination men. We specialize in this type of training and maintain a placement bureau for our graduates. Serving the industry for 10 years, the School of Radio Arts can train you. Write for our catalogue outlining the courses offered. Classes can be arranged so you can do part time work on the side.

APPROVED FOR VETERANS

DON MARTIN SCHOOL OF RADIO ARTS
1655 North Cherokee St. Hollywood 28, Calif.

RADIO NEWS

Arabic, but does play some French recordings.

U.S.S.R.—Tashkent (Usbek S.S.R.) is heard in Britain with news for India at 1200 on (announced) 6.825. (Pearce)

Moscow's 9.710 (announced) channel has excellent signal in beam to Britain mornings, including news at 1130. (Harrison) This is usually a good signal here in the East at 1500 with news.

Moscow's Home Service has been heard on West Coast lately on 8.100 at 0300-0425, poor quality. (Nankervis)

Vatican—HVJ, Vatican City, has moved from 5.968 to about 5.890, parallels 6.190 with German at 1445. (Nilsson)

The 15.095 outlet has been heard in Rhode Island at 0900 with news, good signal. (Pelland) If returned to winter schedule, this newscast may be at 1000 now.

Still has news at 1345 on 9.66 and 5.890. (Miers) Some list this for 1315.

Last Minute Tips

An Arabic-speaking station is heard well in Sweden at 1230-1500 on 12.000 and on approximately 7.500; some Swedish listeners believe this is Port Said; others give location as Medina; call sounds like "Hona Dimach." (Nilsson) Holmberg, Stockholm, gives call as "Hona Medina." Pearce, England, hears this one signing off at 1500 with military march; has news in Arabic at 1445; thinks call is "Huna Asmara." Very bad CWQRM at times.

Roster i Radio, Stockholm, reports a station called Radio Venezia, heard in Sweden at 1300 in the 49-m. band. (Nilsson)

YZZH is the call of a ship, Port of Beaumont, of the Ronne Expedition, heard in Germany giving location as 1500 km. south of Cape Horn; frequency appears to be 8.2/8.33, heard at 2300. Also on 10- and 11-meters as W3LYK/MM. (Miers)

Swiss schedules to North America are listed as 1730-1815, 11.865, 9.535; 2030-2200, 9.535, 11.865, 15.315; 2200-2230 (to Pacific Coast), 9.535, 11.865, 15.315. (Cain) However, Beck, New York, just flashed us revised Swiss schedules for the winter which are to South America, 1830-2000 on 9.539, 7.21, 9.655; to North America, 2030-2230, 9.539, 9.655, 6.165.

Radio Makassar, Celebes, reports it will shortly utilize full normal power of 10 kw. (Beck)

Jaffa's 9.645 outlet has terrific signals in New York around 2330. (Beck)

Officials of XGOA, Nanking, China, have notified me that the 15.35 frequency is being replaced with 11.835 for the transmission to North America beginning at 1930. Wants reports from North America on the 11.835 channel. It was not stated whether the 9.73 XGOA outlet would be parallel, but this is likely.

AIR's outlet on 6.190 is being heard again on West Coast after 0900. (Balbi)

December, 1947

**BIGGEST SAVINGS
IN HISTORY!**

RADIO PARTS & KITS

BUY THE PROGRESSIVE UNIT WAY!

NOW BUILD **\$14.75**
15 RADIOS
Complete Kit



**ABSOLUTELY NO KNOWLEDGE OF
RADIO NECESSARY
YOU NEED NO ADDITIONAL PARTS**

The Progressive Radio Kit is the **ONLY COMPLETE KIT**. Contains everything you need, Instruction Book, Metal Chassis, Tubes, Condensers, Resistors and all radio parts. The 36-page book written by expert radio instructors teaches you to build radios in a professional manner. You start with one-tube receivers, then build two-tube receivers, then three-tube receivers. (The three-tube receivers are equal to four-tube receivers because of the addition of a selenium rectifier.) You then construct a powerful public address system which will permit you to address large audiences. Then you make three different transmitters so you can get a real thrill out of being on the air. Before you are done with this kit, you will have built 11 receivers, 1 Public Address System and 3 transmitters.

PROGRESSIVE UNIT PRICES ON RADIO KIT

1 Kit.....	\$14.75
2 Kits.....	28.15
3 Kits.....	41.25

SPECIAL FREE OFFER

Electrical and Radio Tester sent absolutely **FREE** with each Progressive Radio Kit. **PLUS FREE** membership in Progressive Radio Club. Entitles you to free expert advice and consultation service with licensed radio technicians. Write for further information or **ORDER** your KIT NOW!

PROGRESSIVE AMPLIFIER KIT

This newest Progressive Kit—complete with all parts, tubes and a 12-inch speaker—will enable you to build a newly-designed, high fidelity, humless amplifier for phonograph, AM or FM tuner or microphone.

Regulated power supply maintains constant voltage supply. DC heater supply, whether amplifier is used on AC or DC, provides humless operation by eliminating cathode-heater leakage hum. Contains degenerative feedback for improved frequency response, balanced phase inverter and push-pull beam power output. Every stage thoroughly decoupled to improve low-frequency response and prevent motorboating. Tone control completely variable. Six-tube performance. Uses 1-VR 105, 1-2SL7, 2-50L6's and two selenium rectifiers.

Progressive Unit	1 kit.....	\$25.75
Prices on	2 kits.....	49.50
Amplifier Kit	3 kits.....	69.00

Radio Parts Scoop

NO SURPLUS - ALL PARTS GUARANTEED BRAND NEW!

PHONES
Single Headset.
1000 Ohms, D.C. Reg.
Price \$1.65

Buy 1 for **\$1.10** and save 55c
Buy 2 for **\$1.90** and save \$1.40
Buy 3 for **\$2.55** and save \$2.40

**ELECTROLYTIC
CONDENSERS**
20-20 mfd. 150 W.V. DC.
Reg. price 75c

Buy 1 for **30c** and save 45c
Buy 4 for **\$1.16** and save \$1.84
Buy 7 for **\$1.96** and save \$3.29
Buy 10 for **\$2.65** and save \$4.85

40-40 mfd. 150 W.V. DC. Reg.
Price \$1.05

Buy 1 for **45c** and save 60c
Buy 4 for **\$1.70** and save \$2.50
Buy 7 for **\$2.80** and save \$4.55
Buy 10 for **\$3.80** and save \$6.70

10-10 mfd. 450 W.V. DC. Reg.
Price \$1.25

Buy 1 for **65c** and save 60c
Buy 2 for **\$1.24** and save \$1.26
Buy 3 for **\$1.74** and save \$2.01

VARIABLE CONDENSER
(420-420 mfd.) Reg. price
\$1.80

Buy 1 for **\$1.45** and save 35c
Buy 2 for **\$2.60** and save \$1.00
Buy 3 for **\$3.60** and save \$1.80

CONDENSER KIT
50 paper tubular condensers. Values from .002 mfd. to .1 mfd., 400 v. dc. to 600 v. dc.
Regular Price \$5.00

Buy 1 kit for **\$1.95** and save \$3.05
Buy 2 kits for **\$3.80** and save \$6.20
Buy 3 kits for **\$5.55** and save \$9.45

RESISTOR KIT
100 carbon resistors, 1/4-watt, RMA color coded, values from 330 ohms to 2.2 megohms. Reg. price \$5.00

Buy 1 kit for **\$1.50** and save \$3.50
Buy 2 kits for **\$2.80** and save \$7.20
Buy 3 kits for **\$3.90** and save \$11.10

**ANTENNA AND RF
COIL SET**
(broadcast Band) Reg. Price \$1.00
Buy 1 set for **59c** and save 41c
Buy 2 sets for **\$1.10** and save 90c
Buy 4 sets for **\$2.08** and save \$1.92

**Famous Make
SOLDERING
IRON**

55 watts 110/120 volts. Reg. price \$2.50
Buy 1 for **\$1.90** and save 60c
Buy 2 for **\$3.60** and save \$1.40
Buy 3 for **\$5.10** and save \$2.40

SELENIUM RECTIFIERS
Regular price \$1.10
Buy 1 for **79c** and save 31c
Buy 2 for **\$1.54** and save 66c
Buy 3 for **\$2.25** and save \$1.05

**12" ALNICO SLUG
SPEAKER**
Regular price \$8.00
Buy 1 for **\$5.60** and save \$2.40

Buy 2 for **\$10.80** and save \$5.20
Buy 3 for **\$15.95** and save \$8.05
(No more than 3 to a customer)

**Radioman's Combination
LONG NOSE PLIERS
and CUTTERS**

6" exceptional quality. Hydrazed for extra toughness. Diamond-tested cutters. Reg. price \$1.95.
Buy 1 for **\$1.45** and save 50c
Buy 2 for **\$2.70** and save \$1.20
Buy 3 for **\$3.60** and save \$2.25

PROGRESSIVE RADIO TOOL KIT

A Progressive Electronics Special. Contains 55 watt 110/120 volt soldering iron, radioman's combination long-nose pliers and cutters, amber handle screw driver, Polystyrene alignment tool. Reg. price \$4.95.
Buy 1 kit for **\$3.25** and save \$1.70
Buy 2 kits for **\$6.10** and save \$3.40
Buy 3 kits for **\$8.70** and save \$6.15
(No more than 3 kits to a customer)

PROGRESSIVE ELECTRONICS CO. Dept. RN-4
22 HAVEMEYER ST. BROOKLYN 11, N. Y.

RADIO

Technician and Radio Service Courses
FM and TELEVISION

American Radio Institute
101 West 63rd St., New York 23, N. Y.
Approved Under GI Bill of Rights
Licensed by New York State

Serving Radio & Appliances
SERVICE DEALERS
FROM COAST TO COAST

With **4** **JOB CARDS**

ASK FOR SAMPLES **RADIO PRESS** MORGANTOWN WEST VIRGINIA

TOOL STEEL DRILL ROD

\$1.95
POSTPAID
in Continental U.S.
G.O.D.'S ACCEPTED

25 Rods 1001 USES FOR CRAFTSMEN, HOBBYISTS, MECHANICS, ETC.

SAMPLER KIT
Free machining, easily worked, yet can be made file hard. Hardening instructions included!

ORDER TODAY!

FLAT TOOL STEEL

The Precision ground flat tool steel with the satin-smooth finish. Simple to work, easy to harden, ready to use.

SHOP ASSORTMENT \$4.80; 5 dif. Pieces 1/32" to 1/8" thick; 1/2" wide; 18" long.

BOTH KITS FOR \$6.50

Include 25c postage on orders under \$5.00.

We can supply ALL your Tool Steel Needs.

BESSNER STEEL COMPANY OF AMERICA, Dept. LC-11
Small Shops Div., 1958 W. 59th St., Chicago 36, Ill.

CONVERSION TELEVISION CABINETS



Television
Cabinet
for 15"
Cathode
Ray Tubes

\$485⁰⁰

Build yourself in two hours your own 15" or 20" Television Set from a new RCA latest Model 7" Television Receiver. We supply you with Cabinet, new RCA 13 Channel Television set complete with tubes, 15" or 20" Picture tube, Focusing Coil, Focus Control and diagram of changes.

Cabinet for 20"
Cathode Ray Tubes..... **\$675⁰⁰**

World's First Specialized House in Television

TELETRONICS SERVICE AND SUPPLY CORP.
264 West 40th Street New York 18, N. Y.
Phone PENnsylvania 6-8730

MORE FOR YOUR MONEY

PORTABLE PHONOGRAPH

Has 3-Tube amplifier with Tone and Volume controls, 5" Alnico P.M. Speaker, Shure lightweight crystal pickup and Alliance Phono Motor for use on 110-120 Volts, 60 Cycle A.C. Luggage type simulated leather covered wood carrying case **\$19.95**.

Kit Form..... **\$16.95**

Above with Walnut Finish Table Model Cabinet **\$17.95**..... Kit Form **\$15.50**



INTERCOM UNITS



Up to ten stations may be used with each Master unit. The Master unit can call and talk with any remote unit. Has a volume control for quiet

conversation, a talk-listen switch and a station selector switch. Housed in walnut finish cabinets. Master and one Remote unit..... **\$24.95** for both units Remote Units..... each **\$ 5.25**

PHONO AMPLIFIER KITS

3 Tube Phono Amplifier Kit..... **\$2.35**
Completely wired and tested **2.85**
Kit of 3 tubes for above
128K7, 60L6, 35Z5..... **1.95**
5" Alnico Permanent
Magnetic Speaker and
Transformer..... **\$2.00**
Astatic Crystal Pick-
up Model L-70..... **\$1.95**
Shure Glider Crystal
Pickup..... **\$ 1.95**
Alliance Phono Motor..... **3.25**
V.M. Automatic Mixer-Changer..... **17.95**



WRITE FOR FREE CATALOGUE
ALL PRICES F.O.B. OUR WAREHOUSE N. Y.
25% Deposit. Balance C.O.D.

RAYTONE ELECTRONIC COMPANY

25A Frankfort St. New York 7, N. Y.

HHCN, 5.660, Port-au-Prince, Haiti, has good signal in Eastern U.S. to closedown around 2032; frequency sometimes as high as 5.675. (Kary) Bad aircraft QRM noted. (Hankins)

PCJ, Hilversum, Holland, is sending out questionnaires to find out likes and dislikes of its listeners. (Pearce) ZBW3, Hong Kong, has returned to 9.525 from 9.515; signs off at 0900. (Balbi) Sign-off seems to vary, 0845 to 0915. (Nankervis)

I recently picked up a station on 5.990 at 0545-0630 fade-out or close-down; had Chinese-like music at 0600-0615, then man reads news (seemed to be in *English*; probably is Bangkok, Siam. Usually, this spot has bad QRM.

Radio *Malaya*, Singapore, should be testing soon on 6.120 around 0230-0330, 0830-0930. (Radio Australia)

According to *Radio Australia*, the undercover station, "Radio Espana Independiente, Estacion Pyrenaica," purporting to be the Spanish Freedom Radio, transmitting from "somewhere in the Pyrenees," is heard at 1030-1100 on 15.390 and 11.640; at 1130-1200 on 17.690 and 15.400; at 1530-1545 on 15.400 and 10.280; at 1630-1645 on 11.640 and 10.300.

Radio *Saigon* has Listeners' Letter-box each Friday at 0855 on 11.78, 6.165; it is likely, however, that this may be changed soon to around 0515, as suggested by Arthur Cushen, New Zealand, to officials of the station, this being a more suitable reception time.

Radioelectrica Ushuaia, Tierra del Fuego, Argentina, sent a card with a view of the town, text in Spanish, signed by Vicente Rafael Guillem. (Holmberg, Sweden)

YHN, 11.001, Djokjakarta, Java, "Voice of Free Indonesia," is still heard in Britain signing on at 1200 with "Knightsbridge March"; news, commentary, music, more news and music from 1230 to sign-off of *English* program at 1800; afterwards often is heard in language that may be Arabic. (Pearce)

Rubens Villela, Brazil, reports call of Ushuaia, Tierra del Fuego, Argentina, is LPC on 5.250, 7.425, 10.330; lists schedule for commercial work as around 1915 to LQHE, 9.235, in Buenos Aires.

John Woodruff, California, has received this official list of Indonesian stations in Java, from "The Voice of Free Indonesia," Indonesian Broadcasting Centre, 10 Setjodiningratan, Jogjakarta, Java:

Jakarta I, 3.183; Jakarta II, 2.600; Jakarta III, 2.235; Bandung, 5.085; Garut, 4.000; Tjirebon, 1.525; Tegal, 4.120; Pekalongan, 3.532.5; Purwokerto I, 4.215; Purwokerto II, 2.888.6; Tjilatjap, 3.797.5; Kebumen, 2.335; Magelang, 3.630; Salatiga, 4.600; Djokja I, 5.620; Djokja II, 2.082; Solo I, 4.930; Solo II, 3.350; Madiun, 3.409.99; Pati, 3.986.25; Modjokerto, 4.724; Kediri, 3.750; Malang, 2.651; Djember, 4.630; Nusantara, 400 kcs.; and Indonesian Broadcasting Centre, 11 megacycles. Schedule of the main outlet, 11.001, Jogjawarta, is given as

LEARN TELEVISION ELECTRONICS RADIO

Modern Completely Equipped
Laboratories

DAY AND EVENING CLASSES
G.I. Approved—Veterans Receive
Subsistence

ENROLL NOW!

ELECTRONICS INSTITUTE, INC.
21 Henry, Detroit 1, Mich.

Mr. Radio Service Dealer

"Speed is our Motto"

One day service on all orders. None too small. Only Nationally Advertised Merchandise (No Surplus Handled). TUBES—Any quantity 50% off list.

Mail us your orders.

Illustrated list on request.

Bill Sutton's Wholesale
Electronics
Fifth at Commerce Fort Worth, Texas

AMPLIFIER

For Call System or
Phono. Amplifier



25%
Deposit
Required **\$1.95**

COMPACT-WIRED
READY TO OPERATE
USES 35Z5-50L6

SINGER RADIO & TELEVISION
553 Market St. Dept. A Newark 5, N. J.

Radio Shop Owners

Increase Your Profits Through
Our Speaker Reconing Service

Quick Service—Prices on Request

S & R CONING SERVICE
169 West Eldorado Decatur, Ill.

YEAR END SPECIALS

USED. CMX-40131-C SPEAKER AMPLIFIER UNIT. USES 35Z5 & 35L6, 105-125 AC or DC. Would make a talk back with a little work and some parts. Less tubes..... **\$5.95**
5" Speaker (New)..... **\$1.65**
SEND FOR OUR YEAR END SPECIAL BULLETIN OF UNBELIEVABLE BARGAINS
G. F. HEARD

242 W. Brookdale Fullerton, Calif.

RCA Institutes, Inc.

Offer thorough training courses in all technical phases of Radio and Television
WEEKLY RATES DAYS—EVENINGS
VETERANS! RCA Institutes is approved under G. I. Bill of Rights
For Free Catalog write Dept. RN-47
RCA INSTITUTES, Inc.
A Service of Radio Corporation of America
75 Varick St., New York 13, N. Y.

RADIO SERVICE MEN!

• RCA RADIODIOL
• TUNGSOL
• SYLVANIA
TUBES, PARTS AND EQUIPMENT
Serving Eastern New York State
Distributors of RADIO EQUIPMENT

CHIEF ELECTRONICS

104 MAIN STREET, POUGHKEEPSIE, N. Y.
The Square Deal Supply House

0400-0430 (in *English* to Australia); 0430-0530 (in Dutch to Australia, Indonesia, Malaya); 0530-0730 (in *English* to Australia, South East Asia); 0730-0800 (in Indonesian to Australia, South East Asia, Indonesia); 0800-0830 (in Chinese to China and Malaya); 0830-0900 (in French to Siam and French Indo-China); 0900-0930 (in *English* to India and Middle East); 0930-1000 (to same area but in Hindustani); 1000-1030 (in Arabic to India and Middle East); 1030-1130 (in Dutch to Holland); 1130-1230 (in *English* to Great Britain); and at 1730-1930 (in *English* to United States, news and commentary).

XGOA, Nanking, appears to be using 11.835 again in the transmission around 0300-0915; has very good signal in West Virginia at 0700-0745; is buried at 0800 due to interference from *Radio Australia's* VLC7, 11.84.

Java's 9.685 outlet has been replaced by 11.768; reported from Texas and California. It is presumed this is *Radio Batavia*.

Revised Moscow schedules to North America are announced for 0745-0815, 17.17, 15.17, 11.88, 11.75, 11.72, 9.56; 1820-1950, 15.17, 11.72, 9.78, 9.500, 5.95; 1820-1930 only, 15.23, 11.88. (Patterson)

YHN, 11.001, Djokjakarta, Java, recently announced that the present 2 kw. transmitter will soon increase power to 100 kw. (Anderson)

Graham Hutchins, DX editor of *Radio Australia*, flashes new schedules for the weekly DX sessions: To Western North America, Sundays, 0025, VLA5, 15.32, VLC7, 11.84; to South Africa, VLG6, 15.24. To Eastern North America, Sundays, 1800, VLA7, 17.800; to South America, VLC9, 17.84; to the Forces, VLB6, 15.200; to Europe, VLG7, 15.160. To the British Isles and Europe, Sundays, 1600, VLB9, 9.615, VLA8, 11.760, VLC11, 15.210. (Latter may change to Sundays, 0902.)

Engineer-in-Charge, Warrant-Officer Johnson of WLKS, the B.C.O.F. station in Kure, Japan, 6.065, has informed Graham Hutchins, *Radio Australia* DX editor, that he is interested in receiving reports from overseas listeners and that all correct reports will be confirmed by verification card. QRA is simply WLKS, B.C.O.F., Kure, Japan.

KZRC, Cebu, Philippines, is being heard on 6.130 (listed 6.140) to 1000, announcing as "The Voice of Cebu." KZFM, 9.515, Manila, runs to 0830. (Hutchins)

Rex G. Gillett, DX editor of "*Radio Call*," Adelaide, South Australia, sends these late tips: Tokyo is being heard in the Home Service on 15.235 at 1800, announcing as JOAK, which may be a medium-wave callsign since it is heard announced on various frequencies. Norway appears to be using the former frequency of 9.610, which had call of LLG, in relay with LKQ until both leave the air around 1705; has been heard as early as 1200; at sign-off has interference from ZYC-8 *Radio Romania Libera*, 6.120, Rumania, has been heard at 1430 using *English*; after a little recorded music, more *English* is heard; signs off at 1500 with vocal anthem; signal only fair in Australia. PCJ, Hilversum, Holland, has revised schedule to Pacific; the Tuesday beam is now heard at 0400-0630 on 15.22, 17.77. Schedules received from Brussels are listed 0600-0730 on 21.450; 1100-1200, 21.450; 1355-1500, 17.845. Officials of CR8AA, Macao Portuguese China, advise Mr. Gillett that the station is at present off the air awaiting the arrival of new equipment; former schedule was 0400-1930 on 9.248. KZRC, Cebu, Philippines, states power is 1 kw.; has news at 0730. KZFM, 9.515, uses the slogan, "The People's Station," and is heard in Australia from around 0500 with *English*.

VUD5, 15.19, Delhi, has improved signals evenings, news 213, 2230. VUD3, 11.85, heard at 0930 in native; AIR's 15.16, 9.59 heard in news at 0930, 1030. At 2200 Moscow uses 15.27, 15.40, 15.44, 11.74, 11.87, 11.89 in Home Service; after 2300, 15.17, 15.36 heard as late as 0430. The BBC's Pacific Service is now scheduled at 0100-0500. Paris is heard on 15.24 at 0200-0300; there is a separate program on 11.845. (Balbi)


Acknowledgment

Many thanks for the fine reports coming in. They should be mailed to reach your SW editor at 948 Stewartstown Road, Morgantown, West Virginia by the sixth of any month.....K. R. B.

December, 1947

CURRENT CONVERSION

WITH **ATR** QUALITY
PRODUCTS

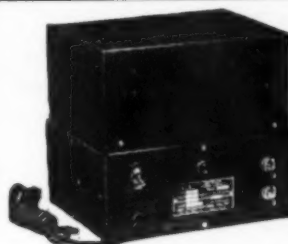

ATR "A" BATTERY ELIMINATORS

For DEMONSTRATING
and TESTING AUTO RADIOS

New Models . . . Designed for Testing D.C. Electrical Apparatus on Regular A.C. lines. Equipped with Full-Wave Dry Disc Type Rectifier, Assuring Noiseless, Interference-Free Operation and Extreme Long Life and Reliability.

- Eliminates Storage Batteries and Battery Chargers.
- Operates the Equipment at Maximum Efficiency.
- Fully Automatic and Fool-Proof.
- Type 60-ELIA . . . Rated Output 6.3 Volts at 6.5 Amperes.

Dealer Net Price \$22.80

- Type 120C-ELIO . . . Rated Output 6.3 Volts at 14 Amperes.

Dealer Net Price \$37.20



ATR AUTO RADIO VIBRATORS

Designed for Use in Standard Vibrator-Operated Auto Radio Receivers. Built with Precision Construction for Longer Lasting Life. Prices are approximately 15% lower.

ATR STANDARD AND HEAVY DUTY INVERTERS



For Inverting D.C. to A.C.
Specially Designed for Operating A.C. Radios, Television Sets, Amplifiers, Address Systems, and Radio Test Equipment from D.C. Voltages in Vehicles, Ships, Trains, Planes and in D.C. Districts.

Write for New ATR Catalog—Today!

AMERICAN TELEVISION AND RADIO CO.

Quality Products Since 1931

SAINT PAUL 1, MINNESOTA — U. S. A.

SURPLUS SAVERS IN STOCK

ZA localizer converter & audio adapter. Housed in beautiful black crackle shock mounted, NEW cabinet; 5 1/2" x 6" x 8". Complete with tubes, for less than you would pay for the chassis and cabinet. 7 lbs. \$2.50

ZA Control box & dummy plug; new. 1.00

COLLINS control box—contains 8P 10 pos. 7 deck rotary switch SPDT rotary switch. .75

Littelfuse 1 amp. 2 doz. \$1.00; 2x2 or 816 H.V. socket; 4 for. 1.00

White Head Pilot Lamp Bay base; GE Mazda tubular 6.3v; 20 for. 1.00

TOBE dual 8 mfd—600v DC—plug into 4 prong socket—oil condenser; some clean, some shelf worn, but guaranteed unused; each. .95

EXPERIMENTING? Brand new RCA 9" cathode ray tubes; each. 4.95

The Famous MAC telegraph key—black crackle w/switch; new. .75

A splendid selection of rotary switches, ceramics, silver contacts, etc. Single and Multi deck; new; 7 asstd. for. 1.95

40 meter—150 watt air wound coils; each. 1.00

Dual .5 mfd—400v upright oil condensers; 4 for. 1.00

BC 654 TRANSCVR—complete w/tubes & Crystal; L.N. 14.50

Less tubes and crystal. 7.95

HAMMARLUND 3 section 500 mmfd variable; large shielded case; terrific worm gear drive, with air padders; Brand new; exceptional value 2.00

New throat mike with 6 ft. extension cord; press to talk switch & terminating in PL-68 standard mike plug. 1.10

6 Conductor ext. shield cable; F.B. for Selsyn. etc.; per ft. .05

MICAS—.01, 2500v DC test SPRAGUE; 4 for \$1.00 New

.002, 5000v DC test C. D.; 3 for 1.00

25% deposit required on all C.O.D. orders. Prompt delivery assured. Write Dept. RND. Include postage with order.

GREENWICH SALES CO.

59 Cortland St. Digby 9-3813
NEW YORK CITY 7, N. Y.



HERE'S a new and highly profitable business that's a dead natural for the radioman who

wants to supplement his income with a minimum investment in both time and money. Today, individuals like yourself, all over the country, are realizing big dividends with TRADIO, the radio functionally-designed for coin operation in hotels, tourist camps, hospitals, etc. And they're doing it right in their own backyards, too.

● BIG EARNINGS, STEADY INCOME

TRADIO has pioneered in this new and flourishing post-war field. Get in on the ground floor and assure yourself of financial security for life.

TRADIO ★ TRIED ★ TESTED ★ PROVEN

TRADIO sells to operators only through franchised distributors. No routes are sold. We'll put you in touch with the distributor in your territory if you'll phone Asbury Park 2-7447 or Write Dept. P-12.



TRADIO, Inc. ASBURY PARK
NEW JERSEY

196

What's New (Continued from page 124)

of d.c. and a.c. voltages, d.c. and resistance analyses.

The new instrument features greater scale readability on the 3" "Red-



Dot" lifetime guaranteed instrument with black and red scale markings; simplified switching to provide greater ease in changing ranges; lower jack contact resistance and trouble-free

plug-in connections by means of banana type jacks; greater stability on a.c.-d.c. voltage ranges 0 to 5000, at 1000 ohms/volt by means of special resistors, and on current ranges to 500 ma. d.c., by means of a 250 ma. instrument.

The entire unit measures only 3 1/16" x 5 5/8" x 2 1/4" and weighs 1 1/2 pounds.

The Triplet Electrical Instrument Co., Bluffton, Ohio will provide complete details on request.

NEW OSCILLOSCOPE

Browning Laboratories, Inc. of Winchester, Massachusetts have developed a new all-purpose, 5" oscilloscope, their Model OL-15A.

Among the salient features of this new test unit is the response curve of the vertical amplifier which is linear and without positive slope from 10 cycles to 4 mc. Thus, the transient response is such that a 100 kc. square wave which rises or falls in the order of 500 v. per microsecond is faithfully reproduced, according to the company. The horizontal amplifier response extends linearly from 10 cycles to 1 mc. to accommodate any type of externally generated sweep voltage. The sawtooth sweep range is from 5 cycles to 500 kc. with synchronizing

REPORT ON LOS ANGELES TELEVISION SURVEY

THE results of the Los Angeles television survey made by "Television Research" reveal some interesting facts regarding the audience reaction to this new medium of entertainment.

In answer to the direct question "What do you think of television reception and programs at present?", 39% of the home audience voted "Very Good," 57% voted "Fair," and 4% voted "Poor." Those owning a set for more than six months were not more critical than those who purchased a set within the last six months.

Owning a television set seems to have two contrary effects on sports attendance. Sports fans in general go to events less frequently after purchasing a television receiver. Of all the set owners who frequented some sporting event at least once a month before owning a set, 55% attended less times after purchasing the set, 37% attended the same number of times, and 8% attended more times. On the other hand, owning a television set makes fans out of some persons who never attended. For that part of the audience who never went to a sporting event prior to owning a set, 20% have attended since purchasing a set and 80% still have not attended. The net effect for a specific sport can only be judged after an audience survey to determine the percentages applying to that sport and the number of fans among the set owners. For the Los Angeles area, and for all sports in general, the average attendance of set owners was reduced from 1.5 times per month to 1.3 times per month, or 13%.

Television will evidently give radio a run for its money because the survey showed that among 77% of the television audience, radio listening decreased after the installation of the TV receiver. Among the other 23%, radio listening remained the same.

Viewers were asked that if their

favorite radio program and favorite television program were on at the same time which would they tune in. 86% of the set owners replied that they would view their favorite television program while only 14% would pass up the TV show in favor of their favorite radio program.

Movie attendance will eventually be cut considerably by television, if the results of this survey are indicative. Movie attendance of the television audience surveyed averaged 3.6 times per month prior to owning a set, but now it only averages 2.3 times per month, or 36% less than before.

More than 90% of the audience would like to see first-run movies regularly on television. Newsreels are high on the audience "want" list. Most of the audience wants sports programs continued, with emphasis on football, wrestling, boxing, baseball, hockey, basketball, and horse races. Marked preference for musical comedies, and variety shows was indicated by the audiences.

This survey was taken in the Los Angeles area where there are approximately 3000 television receivers in use, about 1900 sets in homes and 1100 in places of business.

The average size of the families owning home television sets is 3.6 persons. Children under 10 years constitute 17% of the family audience and those between 10 and 19 years make up an additional 10%. The number of males and females in the families is approximately equal.

At home an average of 5 persons view a single TV program at the same time during an average evening. During the average morning there are 2.3 viewers and during an average afternoon there are 2.7 viewers for each set turned on. Approximately 36% of the home sets are never turned on in the mornings and 22% never turned on in the afternoons.

—50—
RADIO NEWS

sensitivity permitting synching and viewing 10 mc. r.f. sine waves.

Full details on the Model OL-15A



may be secured by writing *Browning Laboratories, Inc.*, Winchester, Massachusetts.

CHASSIS HOLDER

The *JFD Manufacturing Co., Inc.* of Brooklyn, New York has recently introduced a new service aid, the "Repairack," an all-purpose, cast aluminum radio chassis and phonograph turntable holder.

With this new stand, it is possible to rotate the chassis through 360 degrees in a horizontal plane, thus making it unnecessary to remove the set until the job is completed.

Special descriptive literature is available on this unit. Requests addressed to *JFD Manufacturing Co., Inc.*, 4117 Fort Hamilton Parkway, Brooklyn 19, New York should specify Bulletin No. 5479.

-30-

Amargit Singh, a native of Punjab Province, India (center), recently visited the research laboratories of Sylvania Electric Products, Inc., at Flushing, New York. At his right is R. K. McClintock, Field Engineer, International Division, and at his left, Dr. R. M. Bowie, Manager of the Research Laboratory. Mr. Singh plans to apply some of the techniques he saw at Sylvania in his own research laboratory on his return to India after completion of his studies at Harvard.



December, 1947

Now! HEAR FM FROM ALL DIRECTIONS

Ward Products scores again with a new high-gain non-directional FM dipole, the Model FMT-61.

This new "turnstile" dipole picks up FM signals efficiently from ALL directions, does not require orienting!

Engineered for quick assembly and easy mounting, it comes complete for only \$13.50 list.

See your Ward dealer or jobber, or write us direct.



LIST PRICE
\$13.50

NEW WARD NON-DIRECTIONAL TURNSTILE FM DIPOLE


THE WARD PRODUCTS CORP.,

Division of the Gabriel Company

EXPORT DEPT.: C. W. Brandes, Mgr., 4900 Euclid Ave., Cleveland 3

IN CANADA: Atlas Radio Corp., 560 King St., W., Toronto, Ontario

AUDIO OSCILLATOR Sine Wave—Square Wave

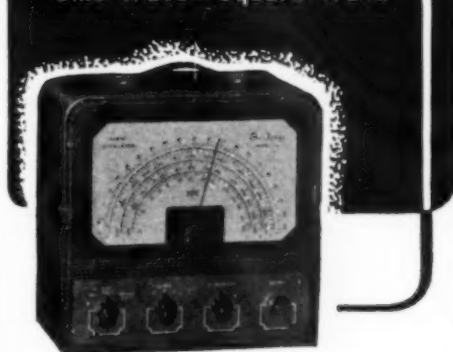

Model 710

Range: 20 to 24,000 Cycles.

Oscillator: RC type.

Sine or square wave throughout range by rotating panel switch.

High impedance output.

2% accuracy over all bands.

Three color, completely enclosed 9" dial for ease in reading.

Tubes: 6X4, 6AQ5, 6AU6, A4522, 6SL7.

\$89.95
Net



Write for catalog sheet

Dept 12-A

Coastwise Electronics Co., Inc.

130 North Beaudry Ave., Los Angeles 12, Calif.

New York Office & Warehouse

258 Broadway, New York 7, N. Y.

Announcing DONGENE Laboratories



New Better FM - AM TUNER

- 13 TUBES—including tuning indicator.
- CERAMIC CONDENSERS — temperature compensated!—used through FM section minimizing drift.
- IF TRANSFORMERS—all FM-IF Coils wound on ceramic coil forms. Iron core type used on AM and FM.
- HIGH FIDELITY—broad band AM-IF amplifier.
- SELF-CONTAINED POWER SUPPLY —117 volt, 50-60 cycles.
- SLIDE-RULE DIAL — 3-color, edge-lighted.
- ONLY HIGHEST QUALITY COMPONENTS used throughout!


If your dealer is out of stock, write us today.

DONGENE LABORATORIES, INC.

95 Van Dam Street

New York 13, N.Y. Watkins 4-9454

Perfect Christmas Item! ELECTRON-O KITS

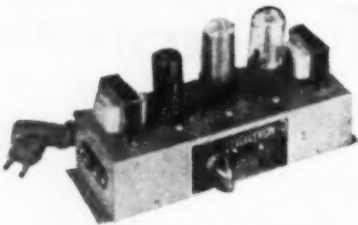

Today's newest, most exciting and instructive hobby. Immediate delivery.

- ELECTRON-O KIT No. 1**
LITTLE GIANT AMPLIFIER. Reg. \$16.95 **\$10²⁵**
- ELECTRON-O KIT No. 2**
RECORD PLAYER AND CONTROL UNIT. Reg. \$16.95 **\$10²⁵**
- ELECTRON-O KIT No. 3**
LOUD SPEAKER AND BAFFLE BOX. Reg. \$7.25 **\$4³⁵**
- ELECTRON-O KIT No. 200**
COMPLETE P.A. SYSTEM. Reg. \$22.50 **\$13⁵⁰**

Write for our Radio Parts Bulletins — issued monthly.

Henry O. BERMAN Co. Inc.

10 & 12 E. LOMBARD STREET

Dept. R-3 BALTIMORE 2, MD.
Electronic Equipment and Replacement Parts

RADIO TUBES

For immediate shipment

R.M.A. Guaranteed

Below Distributor Costs

Individually Sealed Cartons

Type	Price
6K6GT	.40
6K5GT	.46
6V6GT	.46
6SA7GT	.46
6SJ7GT	.46
6SK7GT	.46
6SQ7GT	.46
6X5GT	.40
12SA7GT	.46
12SQ7GT	.46
12SK7GT	.46
12SJ7GT	.46
35L6GT	.40
35Z5GT	.32
50L6GT	.46

RATED ACCOUNTS—2% 10 DAYS

ALL OTHERS 2% C.O.D.

10% DISCOUNT ON LOTS OF 50 OR MORE

RAVAC ELECTRONICS CORP.

432—4th Avenue
New York 16, N.Y.

Classified

Rate 20c per word. Minimum 10 words.

RADIO ENGINEERING

RADIO Engineering Broadcasting, Aviation and Police Radio, Servicing, Marine Operating and Electronics taught thoroughly. Expenses low. Write for catalog. Valparaiso Technical Institute, Dept. N, Valparaiso, Ind.

FOR SALE

BUILD a Portable Radio Tube Tester; improved design, checks all type radio receiving tubes; complete kit with easy to follow assembly blueprints; saves you \$20. Brand new factory parts. Standard Appliance Co., 1438 West Third Street, Dayton, Ohio.

ERECO Beam Rotator: 110VAC, Heavy Duty, Variable Speed, Selsyn Indicator, weather-proofed. Complete indicator and rotator ready to operate, \$49.95. Satisfied users all over the country. Write for free literature. Eresco, 2912 Hewitt, Everett 7, Washington.

KENTUCKY values! 826's, 50W HF triode, \$1.00; 829B's, \$4.95; Socket for either above, \$.59; New TU-5-B's, case, \$2.75. JAN 807's, 866's, many other items, tremendous bargains. 8mfd, 450V tubular, guaranteed equal of any made, \$.25. World's lowest prices service trade items. Write for circular and save money. Kentucky Radio Supply Co., Lexington, Ky.

FM TELEVISION antennas, ham parts, tubes. Bargain list. Wholesale Supply, 347 Lunenburg St., Fitchburg, Mass.

"FLASH-O-TEST." Probe light and continuity tester. Bulb, batteries, leads, complete \$1.00, postpaid. Special model also checks 2, 6, 110 volts, 50c additional. Stelco, Bowling Green, Kentucky.

NEW and used Hallcrafters, National, Hammarlund, Collins, Millen, RME, Sonar, Meissner, Pierson, other receivers, transmitters, amplifiers, test equipments, speakers, etc. Lowest prices. World's best terms. Reconditioned \$38, \$35.00; S20R, \$49.00; S40, \$59.00; RME84, \$69.00; RME45, \$99.00; DB20, \$29.00; NC240D, \$169.00; SPC400SX, \$199.00; SPC400X, \$249.00; KP81, \$249.00; S22R, SX25, SX16, SX28A, SX42, HQ129X, NC173, HRO, HT9, other receivers and transmitters. Shipped on approval. Write. Henry Radio, Butler, Mo.

CONVERSION plug for B. C. 645, \$5.00 set of three. Standing Wave Meter, \$12.00. John W. Collins, 758 Delaware Ave., Columbus 8, Ohio.

HALLCRAFTERS S20R for sale, \$55.00. One of last made. John Sherwood, Griswold House, Lawrenceville, N. J.

\$3.00. COMBINATION Directory. 600 Radio & Equip. Mfrs. 55 Radio Amplifiers Mfrs. 49 Radio Tube, tube parts mfrs. All \$3.00. House of Butte, 60 East 42nd Street, New York 17, N. Y.

TELEVISION components for assembly of a modern 52-square inch screen receiver using the newest circuits and tubes. The only kit on the market featuring an aluminized cathode ray tube, A.F.C. on horizontal sync and a wired, pre-aligned r.f. tuner covering any combination from 1 to 13 television channels. Sound and Picture IF's are on one sub-chassis using new 6AH6 miniature tubes having a gm of 9000! The IF Strip and the 9000 volt RF Power Supply are sold in kit form. The main chassis is sold with all holes punched, or blank with suggested chassis layout print. All components individually priced. Our catalog lists television components exclusively and shows parts and circuits of the "hard to find items" you have been looking for. Send for it today. It's free! Television Specialties Co., 315 Madison St., Oak Park, Ill.

NEW Cornell-Dubilier .5 mfd. 3000 volt working D.C. oil condensers with mounting clamps, \$.75 each, postpaid in U. S. Guaranteed. Production Control Units, 901 Shroyer Rd., Dayton 9, Ohio.

HALLCRAFTERS S27, 28.7, 144MC, FM-AM, \$210. Hammarlund Super Pro (Signal Corps 1004) 540KC. 20MC with power supply, \$175. Both used. Amie, 264 West 125th Street, New York, N. Y.

CONSTRUCTED seven inch Andrea Television Kit. Good condition. Reasonable. Irving Joseph, 548 Sheffield Ave., Brooklyn 7, N. Y.

6V DYNAMOTOR from 12V surplus. No rewinding. Full original output. Instructions, 50c. Paul Hawkins, 1306 E. 27th, Kansas City, Mo.

HOW to align Superheterodynes without a Signal Generator. Alignment jobs are better, and faster with this proven method. Money back if not entirely satisfied. Send \$1.00 to: C. J. Gates, 302 Ross Blvd., Pecos, Texas.

RADIO Tubes—Dealers, order your needs—be surprised at prices. Address Radio Tubes, Box 108, Elizabeth City, N. C.

SELENIUM Rectifiers, full wave, 1/2 ampere, \$1.85; 1 ampere, \$2.50. Half wave 5 amperes, \$4.50. 2.2 amperes, \$2.25; 1.5 ampere, \$1.85. Bulletin Bursma Radio, Route 5, Grand Rapids, Mich.

FREE wholesale bulletin. Tubes, parts. Bargain prices. Henshaw Radio Supply, 3313 Delavan, Kansas City, Kansas.

WRITE Dept. RN18 for our free wholesale list of Radio parts & accessories. R. C. Radio Parts & Distributing Co., 731 Central Ave., Kansas City 6, Kansas.

LOWEST Prices. Radio Tubes, parts. Bargain lists 3c. Potter, 1314 McGee, Kansas City 6, Mo.

CHOKES, swinging, rated 2-12 henries, 100-1000 MA. 5/8"x7"x10 1/2", heavy duty with porcelain insulators, \$7.50; Filament transformers, 2.5 volts, 11 amps, cased, porcelain insulators, \$2.50; with pair 866, \$4.00. SKL Laboratory, Box 188, Lexington 73, Mass.

TWO Meter Transmitter, BC-625 part of 522, including modulator and tubes, brand new in original carton, \$17.50; T-13 handsets, new, \$2.75; T-17 carbon mikes, \$.75; Filter condensers, 2 Mfd., 3000 Volts, \$2.95; Tubes (cartoned), 6AC7, 6AB7, 6SN7, 6H6, \$.25; 6SA7, 6SH7, 6J5, 6V6, 6V6GT, 6N7, 6E5, 6U5, 6A6, 5Y3GT, \$.35; 5U4G, 1624, 1625, 1641, 955, 956, 9002, 9006, 807, \$.50. SKL Laboratory, Box 188, Lexington 73, Mass.

TUBES, \$40.00 per 100 assorted. Brand new cartons, 100% meter tested, all numbers in stock. Best Radio Shop, 3349 Fulton, Cleveland 9, Ohio. 10% Deposit, Balance C.O.D.

IMPEDANCE calculator, new, plastic and duraluminum. Solves vector triangle or unit circle in five seconds. \$3.50. C.O.D. Triculator, 643 W. 109 Place, Los Angeles 44, Calif.

HOTTEST Item! Make your SCR-522 Receiver operate on 144 to 148 Mc with one dial control in less than 1 hour! Parts and instructions, \$3.00. Merit Radio Supply Co., 471 Merrick Rd., Lynbrook, N. Y.

TRANSFORMERS, Microphone, Audio and Output, highest quality, hermetically and glass sealed terminals, cylindrical, space-saving, size 1x1 1/2 in. Audio tfr. flat to 10,000 cycles, Output tfr. 600 ohms output can be used push-pull. \$1.50 each, three for \$4.00. Radioco, 1110 Marshall Bldg., Cleveland, Ohio.

SUPERHET two section variable .00036 condenser, \$1.00. 2mc permeability tuned I. F. transformers, \$1.00. Antenna Relay, silver contact switch, \$.75. Oil filled condenser .1 mfd 2000 volt, \$.50. Midget Plastic cabinet 4x6x6 in., \$1.00. Flexible Drive Shaft, bronze, 24 in., \$.75. Radioco, 1110 Marshall Bldg., Cleveland, Ohio.

RF, AF SIGNAL generator, \$5.00, diagram, 25c. 100 dials nameplates (silver paper), 25c. "Receiver Alignment without Instruments", 25c. Three, 50c. stamps. Nine foot circumference balloon, \$1.00. "Black light" (ultra-violet) bulb, \$1.00. Continuity tester, flashlight, \$1.00. Jackson, Box 853, Bowling Green, Kentucky.

B-29 SIGHTING stations, turret motors, connectors, etc. Get list. WTRK, Everett, Wash.

NEW bulk tubes 49c. 1R5, 1R5, 1T4, 384, 3Q4, 5Y3gt, 6AL5, 6C5, 6J5gt, 6SA7, 6SD7gt, 6SH7, 6SK7, 6SQ7, 6V6gt, 6X5gt, 12A6gt, 12AT6, 12BA6, 12BE6, 12J5gt, 12K8, 12SK7, 12SQ7, 12SN7gt, 31, 35W4, 35Z5, 38, 76, 80, 89. Sylvania bulk tubes 69c: 02A, 1H5gt, 1LD5, 5Z3, 6K7, 7A4, 7A6, 7A7, 7B4, 7B6, 7B7, 7C5, 7C6, 7E5, 7F7, 7H7, 7N7, 7Q7, 7Y4, 7Z4, 12SA7, 12SL7gt, 14A7, 14B6, 14J7, 14Q7, 35A5, 35Y4, 50A5, 50B5, 50L6gt. One hundred blank tube cartons \$1.39. Three tube phono oscillators complete with tubes for \$3.98. Write for bargain flyer. Henshaw Radio Supply, 3313 Delavan, Kansas City 2, Kansas.

3 "RADIO-BUILDERS," 25c. Unusual parts. Catalog, free. Laboratories, Eye-h, San Carlos, Calif.

REVERSIBLE Induction Motor or Selsyn, 1/20 hp 110 volt A.C. 60 cycle, size 3 1/2 x 5, weight 5 lbs., shaft 5/16 in. ball bearing precision made for rugged service. Simple conversion for use as motor or selsyn. Instructions included. Value \$22.50, our price \$5.50. Radioco, 1110 Marshall Bldg., Cleveland, Ohio.

WANTED

VOLUME One Rider's Manual. I. Goldwasser, Louisville, Georgia.

SITUATIONS WANTED

FIRST class radiotelephone, desires broadcast engineering. Edward Guertin, Oxford, Massachusetts.

HELP WANTED

RAILWAY Telegraphy needs men. Complete training. Instruments furnished. Positions waiting. Bell Telegraph Railway Institute, 10 Parker Ave., San Francisco 18, Calif.

INSTRUCTORS in Radio-Electronics and Television. Prefer former Navy Radio Technician Instructors with Teacher Training. Must be willing to locate in Detroit, Mich. Write to Box 452, % Radio News, 185 N. Wabash Ave., Chicago 1, Ill.

OIL Burner service and installation mechanic. Steady employment in semi-rural area in Central New Jersey. State experience, references and wages required in letter to Box 454, % Radio News, 185 N. Wabash Ave., Chicago 1, Illinois.

PATENT ATTORNEYS

PATENTS—U.S. and Foreign Patents Secured Trade-marks and Copyrights registered. Searches made to determine Patentability and Validity Patent, Trade-mark and Unfair Competition Causes. Lancaster, Allwine & Rommel, Registered Patent Attorneys, Suite 414, 815 15th St., N.W., Washington 5, D. C.

CORRESPONDENCE COURSES

USED correspondence courses and educational books bought, sold, rented. Catalog free. Educational Exchange, Henagar, Ala.

USED Correspondence Courses and Educational Books sold or rented. Inexpensive. Money-back guarantee. Write for Free Catalog listing 4000 bargains. — (Courses Bought.) — Lee Mountain, Pisgah, Ala.

AMATEUR radio licenses. Complete code and theory preparation for passing amateur radio examinations. Home study courses. American Radio Institute, 101 West 63rd Street, New York City 23.

BOOKS Astrological: Sold, rented. Write for catalog A-R. Library Astrolyte, 6531 West Blvd., Inglewood, Calif.

MISCELLANEOUS

ELECTRIC meter laboratory. Electrical instruments, tube checkers, and analysers repaired, checked and calibrated. Prompt and reliable service guaranteed. Hazelton Instrument Co., 140 Liberty St., New York 6, N. Y. Tel. Barclay 7-4239.

WHOLESALE Radio Service at reasonable rates, quick service, no job too big. Write for full information. Elkins Radio, Elkins, W. Va.

RADIOMEN, servicemen, beginners. Make more money, easily. \$250 weekly possible. We show you. Information free. Merit, 216-32R 132nd Ave., Springfield Gardens 13, New York, N. Y.

TESTING Equipment. All types and models. Expertly repaired and calibrated. Free estimates. Metropolitan Electronics, 42 Warren St., N. Y. 7, N. Y.

BUILD your own Radios, Phonographs, and Electronic Equipment. Send for our free gift offer and complete catalogue. McGee Radio, 1330 Broadway, Denver, Colo.

SQUARE-ROOT simplified. Easily remembered short cut. 10c. Prof. Lineback, Oklahoma A & M, Stillwater, Oklahoma.

LET us do your shopping for radio parts, ham gear, electrical appliances, etc. We can save you money. Arkay Buyers Service, 2575 Eighth Ave., New York, N. Y.

BC 929 RADAR Scope circuit schematic diagram, \$1.00. B. A. Carlisle, Box 336, Shawnee, Kansas.

PHONOGRAPH records cheap. Catalogue sent free. Paramount, NF-313 East Market, Wilkes-Barre, Penna.


\$1.00 RADIO Service. Write Wholesale Service, 780 E. 214 St., New York, N. Y.

EXPERIMENTERS, Technicians, Engineers! Build a laboratory tube tester. Emission, Transconductance, Power Output tests. More economical and flexible than best commercial models. Illustrated Pamphlet, \$2.00. Polytech Laboratories, Salina Star Route, Boulder, Colorado.

PHOTO CREDITS

Page	Credits
39, 40 (top) (bottom right), 41 (top), 42 (top)	American Gas Assoc.
40 (center) (bottom left), 41 (center, l. and r.), 42 (bottom), 122, 126 (top right), 128, 154	RCA
43	Joe Tillotson
44, 45	Cornell-Dubilier Elec. Corp.
48	Browning Labs., Inc.
52 (top)	Shur-Antenna Mount, Inc.
52 (bottom), 53 (bottom left), 68	Philco Corp.
53 (top) (bottom right)	Allen B. DuMont Lab.
58, 59, 116	McMurdo Silver
66, 67	Walter Steinhart
126 (top left)	Workshop Assoc.
126 (bottom left)	TACO
126 (bottom right)	Farnsworth T & R Corp.
168	The Vitamite Co.
189	Army Air Forces
197	Sylvania

SPECIAL SURPLUS SALE

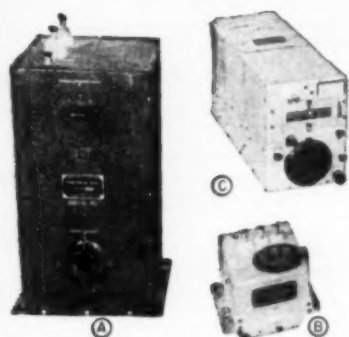

FL-8-C Radio Filter \$1.29

(A) ANTENNA TUNER

A. BC. 306-A National "Velvet Vernier" dial with 100-0 scale. 5 position heavy duty high voltage—3 section RF switch. Two high voltage standoff insulators with spring type binding posts. Low frequency variocoupler. Overall dimensions approx. 18½" high, 8" wide, 8" deep. **\$1.66**

(B) ANTENNA RELAY UNIT

B. 0-10 Meter Weston Thermo-couple unit with 50 MMF, 5000 V Vacuum cond. (illustrated as B-A). Complete. **\$2.45**

(C) RECEIVERS (274N Series)

B.C. 454A. 3-6MC. New.....\$3.95
B.C. 454A. 3-6MC. Used.....2.95
B.C. 455A. 6-9.1MC.....3.95
B.C. 453A. 190-550KC.....4.95

TRANSMITTERS

B.C. 696. 3-4MC (VFO).....\$5.95
B.C. 457A. 4-5.3MC.....3.95
B.C. 458A. 5-3.7MC.....3.95
B.C. 459. 7-9.1MC (VFO) New.....4.95

G.E.—SPRAGUE-AEROVOX oil filled condensers, 4000 Volts, 2MMF.....\$3.19
4000 Volts, 3MMF.....3.95
BEACON Receiver tunes to 75 Meg., has current relav. Operates on 2 Mils.....\$1.79

10-meter Receiver—New. 3-6 MC Receiver converts to 10. Diagram furnished. **SPECIAL 274N-SERIES.**

MODULATOR UNIT

B.C. 456A.....\$3.95
Conversion diagrams furnished.
DM-32 DYNAMOTOR.....1.50
B.C. 348. Receiver Mount and Plug...2.49
Fil. Trans. 1½-amp., 24 Volt.....1.79
Fil. Trans. 2½-amp. 12-24 Volt.....2.95
F. Band Pass Filter, 1000 cycle, close tolerance.....1.98
Dual Choke—12 HY-200 MA 550HM
D.C. resistance. Steel case with stand-off insulators. New.....2.95

TUBES

6AK5.....79c 6AJ5.....79c
Bendix Ant. Insulators, CAA approved—4-inch.....\$1.00 doz.

Also thousands of additional special items such as condensers, tubes, capacitors, transformers, insulators, radar equipment. Inquiries solicited. Get your name on our mailing list. Terms: Cash with order.

ESEGE SALES, Ltd.

1306 Bond Street
LOS ANGELES, CALIF.
TEL. RICHMOND 71162

LOWEST PRICES ANYWHERE

TUBES

Standard brands, in sealed cartons, 60% to 80% off. All types. No discount less than 60%.

5 tube kit—50L6, 35Z5, 12SA7, 12SK7, 12SQ7, **\$2.75**; 5 tube kit—50B5, 35W54, 12AT6, 12BA6, 12BE6, **\$2.75**; 70L7—**79c**; 12SA7, 717A, 6AK5, 12BD6, 9001, 9002, 6J6, **69c**; 12SK7, 12SQ7, 35L6, 50L6, **59c**; 35W4, 35Z5, **49c**.

Raytheon—Acorn Tubes—Nos. 954, 955, 956, 957, **49c** each; Hearing Aid Tubes—Nos. 501ax to 509ax, **49c** each.

CONDENSERS

All popular brands, fresh stock, guaranteed 1 full year. 20 @ 150, **25c**; 20/20 @ 150, **35c**; 8 @ 450, **29c**; 8/8 @ 450, **49c**; 16 @ 450, **49c**; 50/30 @ 150, **49c**; 30 @ 150, **29c**; 20 @ 100, **15c**; Can type—15/15 @ 450, **59c**; 30/30 @ 450, **89c**.

VOLUME CONTROLS

3" Shaft—¼, ½, 1 and 2 meg. with switch, **47c**; Alnico No. 5 P. M. Speakers, Heavy slugs, 5", **\$1.39**; 5" with output Transformer, **\$1.79**; 6", **\$2.49**; 12", **\$4.95**; 6" Dynamic, 450 Ohm field coil, **\$2.95**.

KIT of 100 IRC assorted carbon resistors, most popular types, at ½ and 1 watt, **\$1.79**. 4 Prong "OAK" Vibrator, fits any auto radio, **\$1.49**.

"Astatic" L-71 Pick-up. **\$1.69**; 50L6 Output Transformer, **39c**.

Money back guarantee
20% deposit with order—balance COD

COMMERCIAL RADIO
36 Brattle Street, Boston 8, Mass.

FREE

Up-to-the-Minute
Buying
Information



- Radio Repair Parts
- Sound Systems • Tools
- Kits • Phono Equipment
- Tubes • Test Instruments
- Experimenters' Supplies

REGULAR SUPPLEMENTS

KEEP YOU POSTED

Catalog sent immediately upon request. Price and Data Supplements, issued regularly, assure you of up-to-the-minute information—give exact and current data you need for profitable buying. Send the coupon today for this helpful buying service.

BIG VALUES, LARGE STOCKS, FAST, DEPENDABLE SERVICE.

FREE...SEND TODAY

RADOLEK CO., Dept. B-127
601 W. Randolph St., Chicago 6, Ill.
Please send your Free Profit Guide Catalog and regular Supplements.

Name
Address
City Zone State

SAVE AT RADOLEK

TELEVISION and OSCILLOSCOPE COMPONENTS

TUBES—ALL NEW—J.A.N. Inspected

5 BP1.....\$3.00	5 BP4.....\$3.25
3 AP1.....2.75	2x2/879.... .69

TRANSFORMERS

All Primaries—115V. 60 Cycle

ALL ARE METAL CASED WITH CERAMIC STANDOFFS

2100V. at 10 M.A.....\$2.50
735V. at 5 M.A. and 2.5V. at 3 AMP.. 2.95
6.4V. at 12 AMP. 6.4V. at 10 AMP.,
5V. at 3 AMP., 5V. at 3 AMP., and
2.5V. at 1.75 AMP..... 4.95

OIL FILLED CONDENSERS

.5 MFD. 750 V.A.C.....\$0.98
.2 MFD. 5,000 V.D.C..... 2.49
1 MFD. 3,600 V.D.C..... 2.95
2 MFD. 1,000 V.D.C..... .79

I.F. TRANSFORMERS

Set of 5, single slug tuned, staggered for
4 MC. band width from 9 to 13 MC..\$2.95 set

HEINEMAN MAGNETIC CIRCUIT BREAKER

10AMP. 115V.A.C. Protect Power Supply..\$1.95
10 MA. 2,360 V.D.C. Protect C.R.T. and
Trans..... 1.95

Write for free circular.

Sorry—No C.O.D.

All prices F.O.B. our Warehouse

ALL ITEMS SUBJECT TO PRIOR SALE.

QUAD ELECTRICAL SUPPLY

1650 N. Damen Avenue
Chicago 47, Illinois



THIS IS THE
BUSINESS
YOU DREAM ABOUT

QUICK, STEADY PROFITS

CORADIO

The Coin Operated Radio

Every day more and more men and women are going into the fabulous coin operated radio business. It's new, fast-growing depression proof. Coin operated radios are placed in hotels, tourist courts, clubs, hospitals, etc. on a commission basis... plays 1 or 2 hours for 25c and produces immediate profits. You continue to draw your profits every single month for years to come.

The best and most popular coin operated radio is the CORADIO.

ACT NOW

Here is a golden opportunity to start your own business, full or part time. Be your own boss at your own hours.

Send for Free Illustrated Catalogue and Complete Information

WRITE TODAY—Dept. R.N.

CORADIO

COIN OPERATED RADIO
108 W. 31st St. N.Y. 7, N.Y. WISCONSIN 7-5902

INDEX OF ADVERTISERS December, 1947

Advertiser	Page	Advertiser	Page
A. M. Radio Sales Co.	170	Federal Telephone & Radio Corp.	17
Abell Distributing Company.	140	Feller Engineering Co.	185
Acme Electronics	148	Flanagan Radio Corporation.	192
Adson Radio Co.	185	Fletcher Radio	176
Allied Radio Corp.	9, 74	Frontier Supply Co.	177
Almo Radio Company.	186		
Alvaradio Supply Co.	160	G & G Genuine Majestic Radio Parts Service.	137
American Merchandise Mart, Inc.	148	G & E Equipment Supply Co.	178
American Phenolic Corp.	155	General Cement Mfg. Co.	106
American Radio Institute	193	General Electric	114
American Sales Co.	144	General Electronics Distributing Co. 89, 111, 163	
American Surplus Products Co.	169	General Research Laboratories.	192
American Television, Inc.	36	General Test Equipment	188
American Television & Radio Co.	195	Greenlee Tool Co.	124
Amplifier Corp. of America.	114	Greenwich Sales Co.	196
Apex Video Co.	189	Greylock Electronic Supply Co.	188
Arrow Sales, Inc.	90, 91		
Ashe Radio Co., Walter.	121	Hallicrafters Radio	5
Audel Publisher	188	Hammarlund Mfg. Co., Inc., The.	38
Audio Development Co.	175	Harvey Radio Co., Inc.	18
Audivision Radio Parts Co.	172	Heath Company	112, 113
		Henry Radio Stores.	167
Baltimore Technical Institute.	182	Hershel Radio Company.	73
Bardwell & McAlister, Inc.	124	Hollywood Sound Institute.	170
Beard, George F.	194	Hoodwin Company, Charles.	192
Bell Telephone Laboratories.	26		
Belltone Radio & Television Corp.	77	Illinois Condenser Co.	144
Berman Company Inc., Henry O.	198	Indiana Technical College.	172
Bessemer Steel Co. of America.	193	Insuline Corp. of America.	134
Bevitor Co., The.	186	Interstate Radio & Parts Co.	178
Bliss Electrical School.	189	Instructograph Company	164
Boland & Boyce, Inc., Publisher.	71		
Bradshaw Instruments	178	J.F.D. Manufacturing Co., Inc.	190
Brite-Ray Television Co.	189	Jensen Industries, Inc.	152
Brooks & Associates, George.	184	Jensen Mfg. Co.	202
Brooks Radio Distributing Corp.	191	Johnson Company, E. F.	100, 138
Brush Development Co.	161	Joseph, Irving	87
Buffalo Radio Supply.	108, 109		
Burstein-Applebee Co.	72	Klein, Manuel	136
Buyers Syndicate	126		
		Lake Radio Sales Co.	152
C-B Mfg. Co.	76	Langsam, Harry	170
Candler System Co.	178	Lectrohm, Inc.	170
Cannon Electric Development Co.	171	Leeds Radio	130
Capitol Radio Engineering Institute.	32	Leotone Radio Co.	110
Centralab, Division of Globe-Union, Inc.	15	Long Island Radio Co.	192
Certified Television Lab.	174		
Chicago Industrial Instrument Co.	106	Maquire Industries, Inc.	189
Chicago Transformer Co., Division of Essex Wire.	6	Mallory & Co., Inc., P. R.	33, 3rd Cover
Chief Electronics	194	Maritime Switchboard	116
Cleveland Institute of Radio Electronics.	88, 105	Martin, Don, School of Radio Arts.	166, 192
Clippard Instrument	142	Melville Radio Institute.	169
Coastwise Electronics Co., Inc.	197	Merit Coil & Transformer Corp.	20
Collins Audio Products Co.	138	Merit Products	178
Columbia Wire & Supply Co.	124	Meter Master	188
Commercial Radio.	182, 199	Metropolitan Electronic & Instruments Co.	153
Commercial Radio Institute.	164	Mid-America Co., Inc.	118
Communications Equipment Co.	129	Midwest Radio Corp.	123
Concord Radio Corp.	147	Miles Reproducer Co., Inc.	188
Constant Electric Company.	182	Milwaukee School of Engineering.	150
Coradio	200	Morts Radio Shack.	94
Coyne Electrical School.	93	Moss Electronic Distributing Co.	181, 195
Coyne Electrical & Radio School.	154	Murray Hill Books, Inc.	34, 149
Crystal Devices Company.	114	McGee Radio Company.	78, 79, 80, 81
		McGraw-Hill Book Company.	180
D & H Distributing Co.	160	McMurdo Silver Company, Inc.	30
Davega Stores	10		
Deer & Taylor Co.	104	National Company, Inc.	29
DeForest's Training, Inc.	19	National Radio Institute	3
Delco Radio	35	National Schools	25
Delehanty School of Television.	172	Newark Surplus Materials Co.	184
Dongene Laboratories	197	Newcomb Audio Products Co.	179
Dow Radio	150	Niagara Radio Supply Corp.	132, 133
Eastern Electronics Sales.	156	Oelrich Publications	136
Editors & Engineers.	12, 177	Offenbach & Reimus Co.	157
Edwards F. M. Radio Corp.	134	Ohmite Manufacturing Company.	24
Electric Sweeper Service Co.	177	Olson Radio Warehouse, Inc.	82
Electro-Parts Company	160	Opad & Green.	164
Electro Products Laboratory.	144		
Electronic Distributors, Inc.	158	Pa-Kette Radio	186
Electronic Instrument Company	201	Peak Electronics Co.	156
Electronic Marketers	162	Performance Radio	188
Electronic Products	142	Permoflux Corporation.	94
Electronic Supplies	168	Philco Radio Corporation.	27
Electronic Technical Institute	100	Photocon Sales.	128
Electronics of Staten Island, N. Y.	182	Pilot Radio.	139
Electronics Institute, Inc.	194	Pittsburgh Coil Company.	192
Electronics Measurements	104	Potter Radio Company.	190
Embry-Riddle School of Aviation.	180	Precision Apparatus.	188
Esege Sales Co.	199	Presto Recording Corp.	31
Espey Mfg. Co.	76	Progressive Electronics Co.	193
Esse Radio Company.	96, 97, 98, 99		
Etude Electronics Lab.	150	Quad Electrical Supply.	200
		Quinn's Gadget Shop.	160
Fahnestock Electric Company, Inc.	120		
Fair Radio Sales.	178		

RADIO NEWS

Advertiser	Page
RCA Institutes, Inc.	194
R-L Electronic Corp.	152
R & M Radio Company	84, 85
Radio Center	155
Radio Corporation of America	21, 75
Radio Development & Sales Co.	182
Radio Distributing Co.	164
Radio Electric Service Co.	183
Radio Equipment Co.	172
Radio Ham Shack Inc.	101
Radio Kits	201
Radio Maintenance Magazine	23
Radiomart, Inc.	185
Radio Parts Company	151
Radio Parts Distributors	106
Radio Parts Outlet, Inc.	43
Radio Press	193
Radio Supply & Engineering Co., Inc.	127
Radio Wire Television, Inc.	83
Radionic Equipment Co.	117
Radolek Company	199
Ravac Electronics Corp.	198
Raylectron Company	104
Raytone Electronics	194
Rectifier, J.C.P.	172
Reed Mfg. Co.	182
Rider Publisher, Inc., John F.	16, 131
Risco Electronic Wholesale Distributors	188
Rose Company	186
SNC Manufacturing Co., Inc.	11
S & R Coning Service	194
Salvage, Edmund, Co.	176
Sams Company, Howard W.	22
Scenic Radio	134
Schuh's Radio Parts	156
Senco Radio, Inc.	102
Shure Brothers, Inc.	159
Simwar Distributing Corp.	176
Singer Radio & Television Corp.	194
Snap-On-Tools Corporation	2nd Cover
Southeastern Radio Surplus	174
Sprague Products Company	103
Sprayberry Academy of Radio	7
Stahl, Michael	173
Standard Electronics Distributing Co., Inc.	172
Standard Parts Corp.	92
Standard Radio & Electronic Products	175
Standard Transformer Corp.	107
Stanton Radio Supply	187
Star Measurements	140
Sterling Electronic Company	177
Stevens-Walden, Inc.	86
St. Louis Microphone Co.	156
Sun Radio of Washington D.C.	119
Supreme Instruments Corp.	150
Supreme Publications	163, 191
Surplex Sales	186
Sutton's Wholesale Electronics, Bill	194
Sylvania Electric Products, Inc.	4th Cover
Symphony Radio & Television Corp.	176
TAB	125
Technical Radio Parts	138
Tek-Kit	182
Teletronics Service & Supply Corp.	122, 166, 194
Television Assembly Co.	115
Telex, Inc.	187
Trading News	160
Tradio, Inc.	196
Transvision, Inc.	8, 165
Tri-State College	183
Tyler Commercial College	145
U.S. Radio Supply	179
Ungar Tools	150
United Surplus Materials	88
Universal General Co.	186
Universal Recording Corp.	183
University Loudspeakers, Inc.	140, 158
Utica Drop Forge & Tool Corporation	187
Valparaiso Technical Institute	174
Van Norman Radio Supply Co.	160
Variety Electric Co.	46
Vision Research	142
War Assets Administration	141
Ward Products Corp.	197
Warner Radio Co.	148
Warrent Distributors	14
Webster Electric	13
Weller Manufacturing Co.	28
Wells Sales, Inc.	135, 136, 201
Western Electrical Instrument Corp.	37
Western Radio Communications Institute	188
World Radio Laboratories, Inc.	148
Wright, Inc.	183
YMCA Trade & Technical Schools	187


December, 1947



Servicing
Simplified

FOR AM, FM
& TELEVISION

EICO FOR
BETTER SERVICING

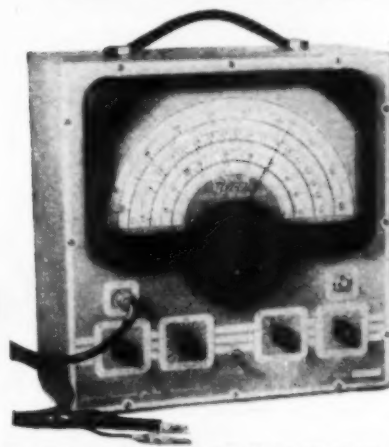

THE MULTI-ANALYST solves your radio problems quickly—The easiest, most effective method of diagnosis—Saves time—wide frequency response—No frequency controls—Both audible and visual indications—Perfect for checking distortion or fading—This handsome, compact unit contains a complete, stable Vacuum Tube Volt-Ohmmeter—electronic on all ranges—Reads video voltages—Big 4½" meter—Exceptional value..... **\$89.50**

THE MODEL 315 SIGNAL GENERATOR with microcycle band spread vernier tuning can be used to align AM, FM, and television receivers. Permits accurate adjustment of any bandwidth. Calibrated in seven ranges from 75 kc to 150 mc. Accuracy better than 1% on all ranges. Linear dial calibration. Praised by all who use it..... **\$64.50**

ELECTRONIC INSTRUMENT CO., Inc.



926 CLARKSON AVE.

BROOKLYN, N. Y.

Write for FREE illustrated brochure. Before you buy, see and hear EICO instruments at your jobber.

Complete instruction manual with each instrument.


TWO NEW HIGHS IN VALUE

Kit Model FM-7, a splendid, low-priced, self-contained table model Frequency Modulated Radio Receiver Kit



Complete with tubes, speaker and beautiful Bakelite cabinet. The FM-7 has a frequency response of 86-110MC, can also be used as a TUNER with a high quality amplifier. A phonojack is provided in the rear of the chassis with double pole, double throw switch for feeding signal to

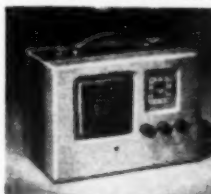either the radio speaker or to the phonojack. An additional jack for connecting extra loud speaker is included. The R.F. section of kit is pretuned at factory. This kit uses 2 I.F. stages, 1 limiter and 1 discriminator. Miniature tubes used throughout. Price of Model FM-7 complete as described..... **\$29.95**



Kit Model 210, a Three Way Portable Receiver

Operating on either AC or DC or self-contained batteries... power switch conveniently located on front of set so that "battery" or "AC-DC" may be selected without opening case. Five-inch Alnico 5 permanent magnet dynamic speaker, and case covered with weather tested aircraft material. Price of Model 210 complete with tubes..... **\$18.95**

All kits accompanied by a detailed illustrated instruction sheet. Many other kit models available. Write for catalog K.

Now ready! New educational pamphlet... complete and simplified diagrams and instructions on all our models..... **50c**

RADIO KITS COMPANY

120 Cedar Street, New York 6, N. Y.

CO-AX CONNECTORS



**AVAILABLE FOR
IMMEDIATE
DELIVERY**

We carry all popular standard and British type coaxial cable connectors in stock. These connectors are brand new and were produced for the Government by the leading manufacturers in this field. Our inventory contains sufficient quantities for the largest users at prices well below the market. Write or wire for special Coaxial Cable and Connector Listing 100A or send us your requirements.

**Manufacturers
and Distributors**

Wells maintains one of the world's largest inventories of highest quality radio-electronic components. Our new catalog, now ready, will be mailed upon request.



**WELLS
SALES, INC.**

320 N. LaSalle St., Dept. R
Chicago 10, Illinois

Listen!
...for **FM**
and **TELEVISION**
(finest in radio)

...it's a
Jensen
SPEAKER
(finest in sound)

FM and Television — latest refinements in the electronic art — are bringing to the radio listener new and undreamed-of realism and fidelity in program quality. Listening enjoyment has been increased a hundredfold for him whose receiver is capable of these lifelike programs.

For finest **FM** and Television reception, both receiver and loud speaker must offer smooth extended-range frequency response, low distortion, and startling "presence." Such a speaker, of course is a JENSEN!

World famous as fine acoustic equipment, JENSEN speakers are especially suitable for **FM** and Television. Before you purchase your **FM** or Television receiver, be sure it's JENSEN equipped. If the receiver you have does not include a JENSEN speaker, have your dealer replace it with one. The best **FM** or Television receiver made is made better with a JENSEN speaker.

JENSEN MANUFACTURING COMPANY
6617 South Laramie Ave., Chicago 38

In Canada: Copper Wire Products, Ltd., 11 King St., W. Toronto 1

*Designers and Manufacturers
of Fine Acoustic Equipment*


Jensen
SPEAKERS
with **ALNICO 5**



STOCK MODELS*
for **FM** and
Television Receivers



6-Inch
P6-TH

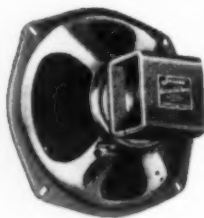

8-Inch
P8-SH



12-Inch
P12-SH
F12-NH

P12-QH
P12-NH
F12-SH



15-Inch
P15-NH
F15-NH

*See Catalog 1010 for complete listing of single-radiator and Coaxial extended range speakers, reproducers and systems, ranging in price from \$5.00 to \$1,500.

PRINTED IN U. S. A.

You Get PREMIUM QUALITY in Mallory Approved Precision Products



...and premium quality costs no more

FIFTEEN years of performance continue to justify the Mallory slogan, "Approved Precision Products." It's the kind of performance that's the natural result of Mallory insistence on premium quality—quality achieved through topnotch engineering, the finest raw materials and the most rigid standards of manufacture and inspection in the replacement parts industry.

Now, more than ever, Mallory performance

is available to you in *complete lines* of premium quality replacement parts *at no extra cost*. It's available through distributors who have been especially selected for their ability and willingness to serve you . . . who give you quick delivery on the items you need when you need them . . . and who offer special assistance on business problems, including those of management, sales and personnel.

The MALLORY "Good Service for Good Business" Plan
Includes Ideas that will help your business grow.
Ask Your Distributor about it.

P. R. MALLORY & CO. Inc.
MALLORY

VIBRATORS . . . VIBRAPACKS* . . . CAPACITORS . . . VOLUME
CONTROLS . . . SWITCHES . . . RESISTORS . . . FILTERS
. . . RECTIFIERS . . . POWER SUPPLIES.

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

The Lock-In Tube In Action

For Electric Department Public Service Electric and Gas Company



View of truck cab showing driver "on the road" in communication with headquarters station.



THROUGH an ingenious system of radio communication, the Electric Distribution Department of the Public Service Electric and Gas Company is able to service a given area swiftly and efficiently.

With 153 vehicles in operation (at the present time), equipped with two-way radio units, Public Service can direct any one of these mobile units to the scene of an electrical breakdown in a matter of minutes!


This elaborate repair system can't afford to risk communication failures. Sylvania Lock-In tubes are used in these Link Radio Corporation sets because no matter how rough the way, they'll *stay in* their sockets. Tubes have few welded joints and *no* soldered ones—the elements can't warp or weave. Short, direct connections . . . less loss; getter located on top . . . leakage reduced by separation of getter material from leads. See Sylvania Distributors or write Radio Division, Emporium, Pa.

SYLVANIA ELECTRIC

MAKERS OF RADIO TUBES; CATHODE RAY TUBES; ELECTRONIC DEVICES
FLUORESCENT LAMPS, FIXTURES, WIRING DEVICES; ELECTRIC LIGHT BULBS



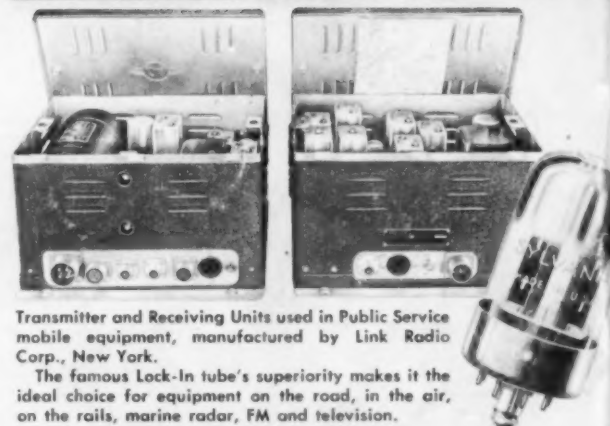Headquarters station in communication with any of the many Public Service units ready for prompt trouble-shooting.



Transmitter and Receiving Units used in Public Service mobile equipment, manufactured by Link Radio Corp., New York.

The famous Lock-In tube's superiority makes it the ideal choice for equipment on the road, in the air, on the rails, marine radar, FM and television.

n

any



Mac's Radio Service Shop (Part 1) (Frye)	63 Apr.
Mac's Radio Service Shop (Part 2) (Frye)	63 May
Mac's Radio Service Shop (Part 3) (Frye)	64 June
Mac's Radio Service Shop (Part 4) (Frye)	54 July
Mac's Radio Service Shop (Part 5) (Frye)	52 Aug.
Mac's Radio Service Shop (Part 6) (Frye)	66 Sept.
Mac's Radio Service Shop (Part 7) (Frye)	54 Oct.
Mac's Radio Service Shop (Part 8) (Frye)	58 Nov.
Mac's Radio Service Shop (Part 9) (Frye)	58 Dec.
New Trends in Receiver Design (Part 1) (Hensler)	46 June
New Trends in Receiver Design (Part 2) (Hensler)	38 July
New Trends in Receiver Design (Part 3) (Hensler)	44 Aug.
New Trends in Receiver Design (Part 4) (Hensler)	54 Nov.
Radio Servicing Hints (Orth)	60 Aug.
What? Where? and Why? (Cook)	118 Nov.

AUDIO

AMPLIFIERS

Additional Notes on Recording Amplifier	73 May
A Miniature Tube High Fidelity Amplifier (Boyer & Toops)	46 Sept.
A 2-Tube Phono Amplifier (Keroes)	45 May
Basic Amplifier for a Wire Recorder (Hicks)	44 Feb.
Build Your Own Communications Receiver (Part 1) (Goode)	46 Aug.
New Developments in D.C. Amplifiers (Wherry, WØDEX)	88 Aug.
Utility Amplifier Unit (Patterson)	42 Jan.
Wide Range Phonograph System (Southworth)	62 June

INTERCOMS

Intercom for Modern Home (Bramley)	63 Jan.
--	---------

MISCELLANEOUS

A Low Cost Extended Range Speaker (Drain & O'Neill)	136 Aug.
Adapting Webster Record Changers for Microgroove Recordings (Timmerman, W8YIF)	39 Nov.
Audio Oscillators (Elisberg)	92 Dec.
Dynamic Noise Suppression Circuits (Goodell)	46 Jan.
Equalizer and Preamplifier for Magnetic Phono Pickups (Carroll)	59 Dec.
Equalizing the G.E. Pickup (Gruber)	48 July
High Fidelity—Too Much Confusion Too Little Clarification (Becker)	43 Apr.
Negative Feedback Compression (Goode)	118 Jan.
Speech Blockade (Atkins)	60 Mar.
10 db. Volume Compression Without Splatter (Crottinger, WØGUY)	40 July
Wide Range Speaker Systems (Hoadley)	53 Sept.

RECORDING

Additional Notes on Recording Amplifier	73 May
A Quasi-Technical Discussion of Magnetic Recording (Clears)	52 Feb.
A Simple Device for Making Recording Easier (Lanza)	109 Aug.
Basic Amplifier for a Wire Recorder (Hicks)	44 Feb.
Build Your Own Magnetic Tape Recorder (Hust)	39 Feb.
Converting a Brush Tape Recorder for Broadcast Use (Fleming)	59 Feb.
Magnetic Tape Systems (Jackson)	46 Feb.
Reproduction of Microgroove Recordings (Pickering & Goodell)	40 Oct.
The Recording and Reproduction of Sound (Part 11) (Read)	54 Jan.
The Recording and Reproduction of Sound (Part 12) (Read)	56 Feb.

January, 1949

ALL NEW SURPLUS


MICROWAVE ANTENNA—

AS-217A/APG 15B. 12 Cm dipole and 13 inch Parabola housed in weatherproof Radome 16" diam. 24-v. DC spinner motor for conic scan. Stock #SD-95. Shipping wt. 70 lbs.

Price \$9.50 ea.



Remote Position Indicating System—

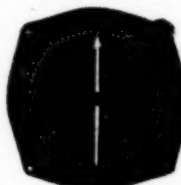

6-12 v. 60 cycles 5 inch indicator with 0 to 360° dial. Heavy duty transmitter. Stock #SD-115.

Price \$9.95 per system

110 RPM MOTOR

G.E. 5BA10J18D. 27 v. @ 0.7 amps. 1 oz./ft. torque. 1 3/4" diam. x 3 1/2" lg. Operates on AC or DC. Stock #SD-98.



Include 15c for P.P. and handling
Price \$2.95 ea. net

Phase Shift Capacitor—4 stators single rotor 0-360° phase shift. Stock #SD-114. Price \$4.75 ea.

Radio Compass Loop LP-21-LM. Stock #SD-99. Price \$9.50 each net.

Magnesyn—CL-3. Use as position indicator with 360 degree potentiometer on AC or DC. Stock #SD-6. Price \$1.95 each.



Blower Assembly MX-215/APG 28 v. DC. 1/100 h.p. motor. John Oster C-2P-1L. L-R #2 blower. 7000 rpm. 20 c.f.m. Stock #SD-202. Price \$4.00 ea.

SWEEP GENERATOR CAPACITOR



Hi-speed bearings. Split stat. or. Silver plated coaxial type. 5-10 mmf. Stock #SD-167.

Price \$2.75 each

TWX—PAT. 199

Write for complete listing, or call Armory 4-3366

INVERTERS

Three Phase 400 Cycle
Holtzer Cabot
MG-153



Input 28 volts DC at 52 amperes. Output three phase 115 v. 400 cycles at 750 V.A. 0.90 P.F. Also second output of 26 v. 400 cycles at 250 V.A. Stock #SD-134. Price \$99.50 each.

Also in stock—

Pioneer 12117-2, 12117-5, 12123-1A, General Electric 5D21NJ3A, PE-218, etc. Wincharger PU-7/AP, MG-750, etc. Holtzer Cabot MG-149F, MG-149H, etc. Leland 10285-1168.

Adcock Antenna—Two 8-ft. rotating beam half sections with tuner. 3-24 Mc. Ideal for DF work. Special Price \$49.50 each.



GYRO SERVO UNIT

Signal take-off — low inertia servo motor. Gear train and follow-up Autosyn. Stock #SD-160. Price \$9.50 each.




REMOTE Compass System

Kollsman transmitter and indicator. Operates from 26 volts 400 cycles. Use with Pioneer inverter. Stock #SD-22. Price less inverter \$6.95 per system.



DYNAMOTOR

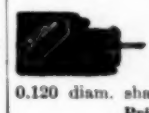D-101. 27 v. DC in @ 1.6 amps. DC output 285 v. @ .060 amps. Stock #SD-187. Price \$1.50 each.



Delco PM Motor—5068571

Alnico field. 27 v. DC. 10,000 rpm. 1" x 1" x 2" lg. 0.120 diam. shaft. 3/4" lg. Stock #SD-161. Price \$3.75 each.

SERVO-TEK

PRODUCTS CO.
Incorporated
Surplus Division

4 Godwin Ave.

Open account shipments to rated concerns.
All prices F.O.B. Paterson, N. J.

Paterson, N. J.

TUNING CONTROL KNOBS

69c ea., 3 for \$2

Postpaid in CONTINENTAL U. S. A. BC 453, 4, etc., series with locking sleeve. Brand new, not surplus. Makes tuning simple for fixed or mobile use.

"Satisfied users all over the world!"
ALVARADO, Dept. RN-16
903 S. Alvarado, Los Angeles 6, Cal.



PEN-OSCIL-LITE

Extremely convenient test oscillator for all radio servicing; alignment • Small as a pen • Self powered • Range from 700 cycles audio to over 600 megacycles u.h.f. • Output from zero to 125 v. • Low in cost • Used by Signal Corps • Write for information.

GENERAL TEST EQUIPMENT
38 Argyle Buffalo 9, N. Y.

RADIO COURSES

Preparatory, Broadcast, Marine Operating, Servicing, Aeronautical, Television, Frequency Modulation, Radar.

Classes forming for mid-term Feb. 1.
Entrance examination Jan. 17
Veteran Training. Literature.

COMMERCIAL RADIO INSTITUTE

(Founded 1920)
38 W. Biddle St. Baltimore 1, Md.



SAM'S SURPLUS

TRANSMITTERS

T20/ARC-5 4 to 5.3 mc.....	\$ 4.95
T22/ARC-5 7 to 9.1 mc.....	7.95
Special—Both for	11.95
BC375 with tubes.....	\$ 12.95
BC447E 500 watt CW.....	139.50
274 N Series 2.1 to 3 MC.....	4.95
BC 457 4. to 5.3 mc.....	4.95
BC 458 5.3 to 7 mc.....	4.95
BC 459 7 to 9.1 mc (new).....	12.95

RECEIVERS

MN-26C Radio Compass.....	\$19.95
BC 454 3 to 6 mc (new).....	5.95
BC 455 New.....	9.95
BC 603 27 to 39 mc FM.....	18.95

MODULATORS

MD-7/ARC-5 push-pull 1625's.....	\$ 7.95
BC 456.....	2.95

FILTER CONDENSERS (National Mfg.)

4 Mfd 600 volt.....	\$ 0.79
10 Mfd 600 volt.....	1.19
2 Mfd 2500 volt.....	3.95
2 Mfd 2500 volt.....	2.39
1 Mfd 4000 volt.....	2.95
2 Mfd 4000 volt.....	3.95
3 Mfd 4000 volt.....	4.95
2 Mfd 5000 volt.....	5.95

TRANSFORMERS 115 V. 60 CY. PRI.

250 vdc 150 ma, 6.3 v @ 5 a, 5 v @ 3 a.....	\$ 3.95
6.3 v ct @ 15 a.....	3.95
250 vdc @ 70 ma, 6.3 v @ 3 a, 6.3 v @ 3 a.....	2.95
33 v @ 150 ma, 6.3 v @ 6 a, 5 v @ 3 a.....	1.95
24 vct @ 2 a filament.....	2.95
3200 v 300 ma No C.T.....	8.95
Two for	15.95

DYNAMOTORS

PE-103 6/12 vdc to 500 v @ 160 ma with-out base.....	\$ 7.95
DM-34-D 12 vdc to 220 v @ 80 ma.....	4.95
274-N Receiver dynamotor.....	1.40

MISCELLANEOUS

FL-8 Audio Filters, see June CQ.....	\$ 1.39
BC 434 Compass Rec Control Head.....	2.39
500 kc crystals.....	1.95
EE-8 Field Telephone, Used, excel.....	9.95
EE-8 Field Telephone, New.....	13.95
12 v vibrator packs, 500 v @ 100 ma natl. adv.....	3.95
BC 375 Tuning Units.....	2.49
Modulation Xformers 807PP.....	4.49

TUBES

2x2.....	\$0.89	6SN7.....	\$0.89	8A1.....	\$12.95
3AP1.....	2.49	6J7.....	.79	888A.....	1.10
5Z3.....	.79	7STL.....	.59	9A5.....	.59
6AJ5.....	.89	VT127A.....	2.95	9A5.....	.59
6AK5.....	.89	807.....	.89	1616.....	.89
6SL6.....	1.35	810.....	.45	2894.....	2.95
6L6.....	.89	813.....	.79	872.....	.97
6SC7.....	.89	832A.....	1.05	954.....	.59
6SN7.....	.79	869.....	4.95		

FILTER

Mobile Generator, cuts out gen. noise. Special \$1.00

PRICES SUBJECT TO CHANGE

ESEGE SALES COMPANY, LTD.

Distributors Electronic Parts

1306 Bond Street at Pico
LOS ANGELES 15, CALIFORNIA
TERMS: CASH WITH ORDER

Radio & Television News

\$10,000 Contest

See next month's issue
for complete details

OUT THEY GO!

Just received a large shipment of rotator motors at a greatly reduced cost to us. We're passing our savings on to you with this low price.

3/4 RPM, HI-TORQUE ELECTRIC MOTOR

Brand New Surplus! Guaranteed



\$2.95
POSTPAID
U. S. A.

Gov't Cost \$40

- Operates on 110V AC, 60-cycles. (Requires only 12 MFD condenser)
- Reversible • Self-locking clutch • Quiet.
- With Full Instructions.
- FB for that new QUAD.
- For rotating ham, FM, television antennas and many other uses.

ALVARADIO, Dept. RN-15
903 S. Alvarado Los Angeles 6, Calif.

The Recording and Reproduction of Sound (Part 13) (Read).....	62 Mar.
The Recording and Reproduction of Sound (Part 14) (Read).....	72 Apr.
The Recording and Reproduction of Sound (Part 15) (Read).....	60 May
The Recording and Reproduction of Sound (Part 16) (Read).....	65 June
The Recording and Reproduction of Sound (Part 17) (Read).....	52 July
The Recording and Reproduction of Sound (Part 18) (Read).....	49 Aug.
The Recording and Reproduction of Sound (Part 19) (Read).....	48 Sept.
The Recording and Reproduction of Sound (Part 20) (Read).....	56 Oct.
The Recording and Reproduction of Sound (Part 21) (Read).....	50 Nov.
The Recording and Reproduction of Sound (Part 22-End) (Read & Endall).....	48 Dec.
Understanding the Wire Recorder (Frank).....	43 Feb.

FREQUENCY MODULATION

CIRCUITS	
FM Detectors (Kay).....	56 Aug.
MISCELLANEOUS	
The Inductuner.....	62 May
RECEIVERS	
An A.C.D.C. Receiver for AM and FM (Harris & Dunn).....	62 Nov.
TUNERS	
An Inexpensive FM Tuner (Peterson).....	46 May
A Low Cost FM Tuner (Goode).....	46 Mar.
More Pep for Your FM Pilotuner (Brown).....	58 May
The FreModyne FM Detector.....	48 Feb.

GENERAL

BOOK REVIEWS	
An Approach to Radio (Shrewsbury).....	173 Mar.
Antenna Manual (Smith).....	130 Aug.
Basic Mathematics for Radio (Maedel).....	118 Oct.
Broadcast Operators Handbook (Ennes).....	182 May
Dial Cord Stringing Guide (Sams Staff).....	173 Mar.
Electric Eye Circuits and Relays in Theory and Practice (Edelman).....	182 Nov.
Electron-Optics (Hatschek).....	182 Nov.
Elementary Industrial Electronics (Wellman).....	131 Aug.
FM Transmission and Reception (Rider & Usman).....	182 May
Frequency Modulation (Vol. 1) (RCA Staff).....	159 July
How to Use Diagrams in Radio Servicing (Beitman).....	88 Sept.
Industrial Electronics Maintenance (Roetger).....	154 Feb.
Listening (Williams).....	182 Nov.
Modern Radio Instruments and Testing Methods (Coyne Staff).....	155 Feb.
Most-Often-Needed FM and Television Servicing Information (Beitman).....	106 Apr.
Most-Often Needed 1948 Radio Diagrams (Beitman).....	173 Mar.
1947 Automatic Record Changer Service Manual (Sams Staff).....	154 Feb.
Plastics for Electrical and Radio Engineers (Tucker & Roberts).....	154 Feb.
Practical Amplifier Diagrams (Robin & Lipman).....	108 Apr.
Practical Disc Recording (Dorf).....	148 Dec.
Preparing for Federal Radio Operator Examinations (Shostak).....	182 May
Radio Aids to Navigation (Smith).....	118 Oct.
Radio Receiver Design (Sturley).....	148 Dec.
Radio Receiver Tube Placement Guide (Sams Staff).....	106 Apr.
Surplus Radio Conversion Manual (Evenson & Beach).....	96 June
Television and F-M Receiver Servicing (Kiver).....	88 Sept.

INVENTORY CLOSEOUTS WAR SURPLUS ELECTRONICS

25 FOOT ANTENNA SETS, complete with insulator base (8 steel mast sections). Ideal for hams, boats, mobile or field use. LIKE NEW, per set..... \$ 6.95

TELEPHONE SETS, complete with 2 control boxes with bells and ringers (RM-29's) and two hand telephones with cords and plugs (TS-12's). These telephone sets are BRAND NEW and ready to operate when dry cells are added. SPECIAL, per set..... 19.95

BD-77 DYNAMOTORS, for use with BC-375 or BC-191 transmitters for 12 v. operation. (12 v. input, 1000 v. at 350 ma. output.) BRAND NEW, EXPORT PACKED..... 4.45

BC-306A ANTENNA TUNING UNITS (for use with the BC-375 or BC-191 transmitters). A spare parts value. BRAND NEW..... 1.95

BC-375 TUNING UNITS, assorted numbers. In cases. BRAND NEW..... 2.45

T-17 MICROPHONES, with cords and plugs. BRAND NEW..... 1.95

We have large quantities of BRAND NEW FACTORY PACKED BC-375E TRANSMITTERS, BC-191 TRANSMITTERS, and RA-10 CA or RA-10 DA AIRCRAFT RECEIVERS. All sets are complete with all necessary components for operation. Inquiries invited. SCR-284A SPARE PARTS AVAILABLE.

SEE OUR CLASSIFIED AD THIS ISSUE—WRITE FOR LISTING OF MANY OTHER ELECTRONIC CLOSEOUT ITEMS

ALL ITEMS GUARANTEED AS ADVERTISED
TERMS: 25% with order, balance C.O.D. Shipments F.O.B. our Chicago warehouse, minimum order \$5.00

ACOUSTICRAFT CORPORATION
2144 S. Kedzie Ave. Chicago 23, Illinois
Phone: Blispho 7-5340

We have increased our production so we are now able to again make immediate delivery on Wright Verified Speakers with the



MOUNTING BRACKET

write for literature

WRIGHT, Inc.

2232 University Ave.

St. Paul W 4,

Minn.

Are
You a
Music
Lover?



Get live orchestra realism from your own records and radio with the new Langevin MUSIC IN FOCUS amplifier, Type 127-A. Ask your local jobber for a demonstration LISTEN...you can HEAR the difference!

Write for
bulletin
#1052

Langevin

37 west 65th Street, N.Y. 23, N.Y.

RADIO & TELEVISION NEWS

Television Encyclopedia (Kempner).....	96 June
Television Primer on Production and Direction (Sposar).....	182 May
The Radio Amateur's Beam Pointer Guide (Rider).....	159 July
The Self Advancement Guide for Applied Practical Electricity (Coyne Staff).....	108 Apr.
Understanding Television (Dunlop).....	148 Dec.
Understanding Vectors and Phase (Rider & Usan).....	108 Apr.

BUSINESS MANAGEMENT

Direct Mail for Dealers (Samkofsky).....	96 Mar.
Failures Don't Just Happen! (Bader).....	48 Apr.
How to Write an Ad (DeNike).....	114 Mar.
Money—What You Need and How to Get it (Pitman).....	42 Apr.
Portable Radios—For Rent! (Alth).....	42 May
Radio Service—A Business (Graf).....	56 Dec.
Sales Promotion Means More Business (Bader).....	45 Jan.
Selling Service (Vinson).....	98 Jan.
Sell Your Service (Ledbetter).....	49 Nov.
Television—Exclusively! (Alth).....	48 Mar.
Two-Way Mobile Radio—A New Field for Servicemen (Sands).....	39 May
Watch Your Labor Cost (Merish).....	72 Dec.

COMMUNICATIONS, BROADCASTING (See "Amateur")

Adding Single-Sideband Selectivity to the Communications Receiver (Silver).....	54 June
A Low Frequency Converter (Amundsen, W1HYF).....	49 July
Citizens Band Oscillator (Ritchey).....	44 Dec.
Dynamic Noise Suppression Circuits (Goodell).....	46 Jan.
High Speed Receiver Squelch (Kline, W2DKE).....	94 Apr.
Marine Radio Installation (Alth).....	35 July
New Mobile Field Strength Equipment for TV.....	61 Aug.
Radio Network For Rural Areas.....	64 Dec.
The Taylor "Super-Modulation" Principle (Part 1) (Taylor).....	42 Sept.
The Taylor "Super-Modulation" Principle (Part 2) (Taylor).....	49 Oct.
Two-Way Mobile Radio—A New Field for Servicemen (Sands).....	39 May

COMPONENTS

Parts—Then and Now.....	52 Oct.
hermistors—A New Electronic Component (Butler).....	49 Jan.

CRYSTAL DIODES

Crystal That Amplifies (Atkins).....	39 Oct.
--------------------------------------	---------

ELECTRONICS

amentals of Industrial Electronics (Endall).....	56 June
adio Seeks Black Gold (Patterson).....	55 July
ie Solovox (Miller).....	60 Dec.

ACSMILE

adio Facsimile May Print "News-papers of Tomorrow" (Lauden).....	39 Aug.
--	---------

ADGETS

Doorbell That Is Different (Houston).....	46 Apr.
Electronic Photo Timer (Pray).....	58 Aug.
Portable, Lightweight, 1-Tube Stroboscope (Turner, W1AY).....	38 Sept.
Simple Shutter Speed Meter (West-burg).....	58 July
Photo-Sensitive Devices and The Radioman (Gschwind).....	130 June
p That Pedestrian (Kaufman).....	66 Nov.

INDUSTRY REPORTS

n Open Letter to the Radio Manu-facturer (Saunders).....	43 June
ond Geddes' Report on Radio In-dustry.....	45 Mar.
The Audio Engineering Society (Goodfriend).....	82 Sept.

INSTRUCTION

Do You Know? (Scott).....	98 Dec.
Practical Radio Course (Part 58) (Ghirardi).....	88 Jan.
Practical Radio Course (Part 59) (Ghirardi).....	64 Feb.

January, 1949

SAVE \$ ON RADIO SURPLUS

**U. S. SIGNAL CORPS
5 METER SHORT WAVE XMTRS.**
(72.2Mc) XMTRS and TUBE only, less mike, bat-teries and antenna. One 1 1/2 volt dry cell and 67 1/2 volts of B operates it. Just attach di-pole, key or mike, connect the batteries and it's ready to use. Signal Corps spec. wired with silvered wire, mica condensers, and precision resistors. Highly stable circuit with Lo-Loss silvered inductance. (Adjustable paddler) Schematic supplied. Converts easily to walkie-talkie and Ham bands..... **\$3.25**



GENUINE SIGNAL CORPS FEATHER-WEIGHT HEADPHONES WITH CORD AND PLUG 2000 OHMS—8000 OHMS IMPEDANCE.....\$1.00

**NATIONALLY KNOWN
OIL FILLED FILTER CONDENSERS**
1.—MFD—2000 volts..... **95c ea.**
1.—MFD—1000 working volts. 4 for..... **\$1.00**

FAMOUS BRAND RECORD CUTTING HEAD
These units are all Brand new and were made for a nationally advertised manufacturer to be in their quality Home Recording Radios. Size 1 1/2 x 2 1/2 ready to fit your cutting arm or bracket. **SPECIAL \$2.95**
3 BAND ALL-WAVE DIAL 6" DIAMETER.....75c

TUBULAR ELECTROLYTICS
20-20 MFD, 150 V **27c** 30-30 MFD, 150 V **30c**
40-40 MFD, 150 V **35c** 40-40-20 MFD, 150 V **36c**
2 1/2 M.H. R.F. CHOKE COIL—27c ea. 4/\$1.00
3 BAND OVAL DIAL—7 1/4" L x 5 1/4" H, 2 Pilot Sockets.....79c

U.S. AIR FORCE RESISTOR ASST. 1/4-1/2-1 WATT—100 PIECES.....95c
U.S. AIR FORCE MICA COND. ASST. 25 PCS. 50M-1000MMFD.....49c

Low-Loss-Short Wave Variable Condensers 1/4" Shaft Type
5 Plate—20 MMFD..... **20c**
9 Plate—30-40 MMFD..... **25c**
14 Plate—35-60 MMFD..... **27c**
27 Plate—100-110 MMFD..... **45c**
37 Plate—150 MMFD..... **50c**
38 Plate—150-155 MMFD..... **55c**
53 Plate—210-21 MMFD..... **60c**
Lock Type Air Trimmer Variable Condensers
3 Plate—12-15 MMFD..... **10c**
5 Plate—20 MMFD..... **10c**
8 Plate—30-35 MMFD..... **13c**
10 Plate—40 MMFD..... **14c**
14 Plate—50 MMFD..... **20c**
20 Plate—80-100 MMFD..... **25c**
27 Plate—100-110 MMFD..... **35c**

SIGNAL CORPS TRANS. KEYS.....39c
4 PR. WAFER SOCKETS—\$1.49 per C. each 3c
PHILCO 4 MF—300 V—1% CAN CONDENSER—\$8.00 per C.....10c each
W-L—10 W. 1,000 ohm POWER RHEOST.....29c ea.

5-6 PRONG WAFER SOCKETS.....\$2.50 per C
100 ASST. SOCKETS 4-5-6-7.....\$3.50 per C
1,000 OHM WIRE WOUND POTENT.....15c
30 HY-FILTER CHOKE SHIELDED.....49c
UNSHIELDED.....39c
100 ERIE—1 WATT—2,000 OHM RESIS. \$1.15
10 WIRE WOUND RES. KIT—5-50 W. ASST. 49c
2 METER RF CHOKES.....7c
phone PICK-UP REST. RUBBER—1 Hole MTG. 6c
2,000 OHM WIRE WOUND RHEOSTATS.....\$1 per doz.

RCA-VICTOR NEEDLE CUPS—2 PIECE \$1.00 ea.
CARTER WIRE WOUND C.T. VARIABLE 20 OHM RESISTORS.....\$1.00 per doz.
G. E. TAPPED VOLTAGE DIVIDER—200 WATT—230 OHM—MOUNTED ON ASBESTOS BASE.....25c
RCA 6 OHM POWER RHEOSTATS.....39c
RCA RUNNING BOARD AUTO AERIAL.....49c
PHILCO AUTO SUPPRESSORS.....\$5.00 per C.....7c ea.

GEN. ELEC. WESTINGHOUSE, etc., 60 CYCLE WATT HOUR METERS, slightly used, perfect condition, same as used in your home, 110-125 volts, 5 Ampere.....\$3.50
10 Amp.....\$4.50

Philco rotary tap tone control, 3 position, including condensers. Only 1 wire to connect to grid of audio tube. 1/4" shaft. 25c

I. C. A. 30 MH RF choke.....23c
Grind your own crystals—Pure Brazilian Quartz, all sizes and thicknesses—1/2 lb. package.....\$1.00

National Velvet Vernier Dial Attachment—1/4" shaft—converts any dial to slow motion vernier.....75c
340 degree dial with 10 push button attachment—1/4" shaft—Ideal for Knitters—Nig Gen. or Ose.....49c

RCA Band Switches—3 gang 3 posit. 3 band.....30c
6 gang 5 posit. 4-5 band.....40c

Trimmer-Padder Asst.—all Isolantite—singles, dual, triples—100 asst. pieces.....\$2.25

Signal Corps V.T.2 receiving tubes—per doz.....\$1.00

MAGNAVOX—5"—450 ohm AC-DC dynamic.....\$1.49
5" 5M OHM RCA SPEAKER.....\$1.00

ATTENTION: Prospectors

Explorers for Hidden Treasures!

Do you seek hidden treasures of rare metallic ores? If so, construct a U.S. Army Type of Metallic Mine Detector from these U.S. Army Mine Detector Amplifiers that we are offering at a ridiculously low price. Amplifier unit only (less tubes and batteries) with cables, headphone cord and jack (no phones). Complete Army wiring diagram. U.S. Army DETECTOR SET Amplifier Type AN/PRS-1..... **Only \$1.95**

No C.O.D.'s. Eveready 45 volt batteries #482, \$1.65 ea., 6 volt A, 73c. 2-1N5 tubes, 95c ea.

TUBES—6SN7—45c; 53—39c; 2AT—39c; 55—39c; 117L7—59c; 27—25c; 215, same as #224—39c; 01A—25c; 31—20c; 85—25c.

DRY ELEC. FILTER COND. ASST. CONTAINS 10 PIECES ALL BRAND NEW 150-450V.....\$1.10
6 ASST. WET ELECTROLYTIC CONDENSERS.....39c

RADIO EXPERIMENTER'S SURPRISE PACKAGE—CONTAINS BYPASS & FILTER CONDENSERS, SHORT WAVE TUNING UNITS, POWER AND AUDIO TRANSFORMERS, SOCKETS, RESISTORS, CHASSIS HARDWARE, OVER 25 LBS. OF VALUABLE PARTS.....\$4.95

HEAVY DUTY SHIELDED GENERATOR CABLE. 3 1/2" Long. WILL CARRY 35 AMPS—3 WIRE.....19c

DRILLED CHASSIS FOR 5-6 tubes 7"x10"x1 1/2"—29c; 5"x10"x1 1/2".....29c

RCA ADJUSTABLE CODE INTERFERENCE WAVE TRAP 450-475 KC.....39c

PHONE JACKS—OPEN & CLOSED AUTOMATIC TYPE.....16c

RCA DOUBLE FILTER CHOKE.....80c

NATIONAL 5-15-450 VOLT CAN FILTER CONDENSER.....39c

EBY SPEAKER VOLUME CONTROL WIRE WOUND 60 OHMS FOR USE IN CONTROLLING VOLUME ON P. A. SPEAKERS. WITH SWITCH—SPECIAL 25c ea. LOTS OF 50.....20c ea.

SALE—PHONO RECORD ALBUMS—SALE 10"—3 comp.—15c; 4 comp.—20c; 12 comp. 49c 12"—3 comp.—15c; 4 comp.—20c; 12 comp. 49c

RECORD PLAYER CABINET & BASE—35c—Hk 14 1/2"x10 1/2" W.—MAHOGANY MADE FOR MOTOR & PICK & VOL. CONTROL—ROOM FOR SPEAKER & AMPLIFIER.....\$2.95 ea.

LIMITED QUANTITY ONLY
SERVICEMAN'S RADIO TUBE CARRIER—MADE OF BLACK FIBRE. SIZE 10"x5"x5" WITH LEATHER SHOULDER STRAP. LIMITED QUANTITY.....49c

MINIMUM ORDER \$2.00—NO C.O.D. SHIPMENTS—PLEASE INCLUDE POSTAGE
NEWARK SURPLUS MATERIALS CO. 324 Plane Street Dept. JA Newark 1, N. J.

The YAGI-BEAM

DODGES OUT GHOSTS

Super-sharp directivity of pin-pointing Yagi-Beam array is perfect for picking direct-path signal out of maze of reflection-path ghosts in "downtown" installations. Thin brass, silver-plated for 20 db gain. Hurricane-proof. All connections soldered. See your distributor or write:

Roger TELEVISION, INC., 366 MADISON AVE., N.Y. 17

SAVE \$\$\$



COMPACT PORTABLE ARMY FIELD TELEPHONES

Buy 2 phones
and SAVE \$1.50

**Special discount offered Limited
Time Only. Act Now!**

Amazingly simple to install and operate. Just hook up terminals of two or more phones to any two-strand wire and you are ready to talk up to 17 miles! Powered by standard flashlight batteries. Hundreds of uses for quick, low-cost, dependable 2-way communication around home, shop, farm, industry. Each phone complete with self-contained hand-operated ringer. Every phone checked for perfect operation and fully guaranteed.

	Buy 1 Phone Regular Price	Buy 2 Phones Save \$1.50
USED—good, serviceable condition	\$7.45	Special \$13.40
USED—excellent condition	8.95	Special 16.40
RECONDITIONED (By U. S. Signal Corps)	10.75	Special 20.00
LIKE NEW, Slightly used	12.95	Special 24.40

ARMY FIELD TELEPHONE WIRE

Weatherproof, Durable. 2-conductor, twisted, 3 copper and 4 steel strands, tinned, insulated. On Original Steel Reels.

W-110B. Unused, new, but stored in open. Half-mile reels (2500 to 2750 feet). Wt. 85 lbs. Each. \$14.25

500-foot coil (14 lbs.). 3.50

1000-foot coil (28 lbs.). 6.50

W-130 LIGHTWEIGHT ASSAULT WIRE. Weighs only 16 lbs. New, half-mile reels (2600 feet) Ea. \$15.00

Write for FREE Folder and Prices on Other Specials, Switchboards, Head & Chest Sets, etc. All Prices F.O.B. Sacramento. No C.O.D. Calif. residents add 2 1/2% for sales tax. Small orders sent postage collect plus small handling charge.

SEND CHECK OR MONEY ORDER **LORIS SALES**

P.O. Box 1896-M-1 Sacramento, California

BRILLIANT NEW AMPLIFIER!



- ★Wide-Range
- ★Scratch Suppressor
- ★Volume Expander

Supreme performance with any variable reluctance pickup.

EXCLUSIVE G.E. PICKUP CIRCUIT

New circuits enable you to attain full benefit from the new G-E Variable Reluctance Magnetic pickup. Employs an exclusive, humless pre-equalized pre-amplifier to produce the most satisfying musical amplifier the world has ever known. If you are a perfectionist, you are the one for whom the ACA-100GE was designed. Send for technical literature.

AMPLIFIER CORP. OF AMERICA

398-2 Broadway, New York 13, N. Y.

Practical Radio Course (Part 60—End) (Ghirardi)	72 Mar.
Students of Today—Technicians of Tomorrow (Chapel)	68 Oct.
MISCELLANEOUS	
A Crystal That Amplifies (Atkins)...	39 Oct.
Atom Smashers (Teevan).....	39 Mar.
Birth of a Service Note (Hooton)...	50 Mar.
Exploring the Infinitesimal (Gootee)...	39 June
Radio Quiz (Bukstein).....	148 Sept.
Television I.Q. (Bukstein).....	120 Oct.
POWER SUPPLIES	
A Compact Bias Supply (Clemens)...	180 Mar.
A Grid Bias Supply for Class "B" Modulators (Sherrod, W5ZG).....	94 Nov.
Another Method of Power Supply Control (Gallagher, W5HZR).....	88 June
A Regulated Power Supply (Rogers)...	68 May
Build Your Own Communications Receiver (Part 1) (Goode).....	46 Aug.
Methods of Producing Negative Potentials (Carter)	188 Mar.
Compact Power Supply Is Transformerless and Tubeless (Dexter).....	51 Mar.
New Television Power Supplies Use Selenium Rectifiers (Eannarino)...	54 Sept.
Novel Controlled Rectifier (Peschel)...	58 Nov.
Power Supply Output Voltage Control (Peschel)	66 Oct.
Regulated D.C. Supply Improvements (Kinsell)	68 June
RADAR, SONAR, ETC.	
The APS-42 Radar (Mallach).....	44 Apr.
RADIO CONTROL	
Guided Missiles (Chapel).....	39 Jan.
Radio Controlled Model Sailboat (Schmidt, W1VDY, & Williams)...	39 Apr.
TEST EQUIPMENT	
A Compact Distortion Meter (Turner, W1AY)	68 Nov.
A Compact Linear Diode V.T.V.M. (Turner, W1AY)	40 July
A Crystal Controlled Signal Generator (Bann)	51 May
A Crystal Diode Wave Shaper (Turner, W1AY)	44 May
A Low Cost Volt-Ohmmeter (Lawson)...	64 Sept.
A New AM-FM Signal Generator (Najork)	49 Feb.
A Television Oscilloscope (Part 1) (VanArsdale)	64 Apr.
A Television Oscilloscope (Part 2) (VanArsdale)	52 May
A Universal A.F.-R.F. Wattmeter (Dexter)	66 May
A Vacuum Tube Voltmeter (Krueger)...	60 June
A Versatile Service Test Instrument (Haist)	54 Apr.
A Versatile Signal Checker (Turner, W1AY)	42 Mar.
A Versatile Substitution Tester (Fleishman)	53 June
Audio Oscillators (Elisberg).....	92 Dec.
Gain Measuring Test Unit (Norman)...	61 Sept.
Home-Built Crystal Signal Generator (Chalfin)	47 Oct.
Low Cost All-Wave Signal Generator (Gould)	64 July
Low-Cost Multimeter (Siegel).....	100 Nov.
Make a Test Unit for Your Service Kit (Leeper)	41 July
New Test Equipment Speeds Video Servicing (Liebscher)	44 July
Sensitive A.F.-R.F. Signal Tracer (Turner, W1AY)	38 Aug.
Simplified RC Bridge (Parmenter, W1JXF)	126 Mar.
Simple Simon Signal Tracer (Gruber)	146 Oct.
Voltage, Current, Capacitance, and Resistance Measuring Devices.....	112 May
U.H.F.	
Microwave Plumbing Replaces Circuitry (Freedman)	35 Sept.
TELEVISION	
MISCELLANEOUS	
Microwaves for Relaying TV Programs (Freedman)	35 Nov.

NOW AVAILABLE! TO RETAIL BUYERS



R 110 F
\$9.50

**HORIZONTAL OUTPUT
& HV TRANSFORMER**
10 KV Output for 8 MH Yokes

R 2114
\$9.00

**DEFLECTION
YOKES**

50° Defl. 8 MH
Horiz. Induct.

Mail Orders Filled

VISION PRODUCTS CO.
Empire State Bldg. N. Y. 1, N. Y.

FREE

ILLUSTRATED 1949 CATALOG

Of Radio and Electronic
Tubes and Parts

Send For It Today

All Brand New Merchandise Selling Retail At Wholesale Prices—Catering To Hams, Experimenters, Servicemen and Students.

A New Radio Company Dealing Only In Mail Orders To Give You Quicker Service On All Orders Large Or Small.

RADIO MAIL ORDERS

75 Barclay St., Dept. RN, New York 7, N.Y.

LEARN RADIO!

IN ONLY 10 MONTHS
PREPARE FOR A GOOD JOB!
COMMERCIAL OPERATOR (CODE)
BROADCAST ENGINEER
RADIO SERVICEMAN

Television Servicing—15 Months

Veterans get \$130.00 Equipment
SEND FOR FREE LITERATURE
BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PL., DEPT. R, BALTO. 17, MD.

SOUND RECORDING SCHOOL

A practical engineering course in Sound Fundamentals, Recording, and Sound Transmission measurements; in laboratories containing transmission sets, oscillators, square wave generator and intermodulation analyzer, film, disc and magnetic recording equipment. Complete recording studio assimilating broadcast, motion picture and commercial sound recording. H. M. Tremaine, Pres. & Director.

HOLLYWOOD SOUND INSTITUTE, Inc.
1040-N Ne. Kenmore Hollywood 27, Calif.

WANTED

Teletypewriters complete, components or parts. Any quantity and condition.

Box 469, c/o Radio & Television News
185 N. Wabash Ave. Chicago 1, Illinois

RADIO & TELEVISION NEWS

New Mobile Field Strength Equipment for TV.....	61 Aug.
New Television Power Supplies Use Selenium Rectifiers (Eannarino)...	54 Sept.
Something New in Color Television (Crosman).....	40 Sept.
Television—Exclusively! (Alth)....	48 Mar.
Television Grows Up.....	47 Dec.
Television on Wheels (Wakeman & Goldsmith).....	46 July
The Inductuner.....	62 May
1948—Year of Television Progress (Gootée).....	35 Dec.

RECEIVERS

Custom-Build Telesets Provide New Video Market (Lescarboura).....	45 Nov.
The Television Kit (Flomenhof).....	42 Oct.

SERVICE NOTES (Theory)

ABC's of Home Television Servicing (Shore).....	35 Aug.
Automatic Frequency Control (Buchsbaum).....	68 Mar.
How to Use Sweep Generators with TV Receivers.....	46 Nov.
Individualized Television Installations (Taber).....	35 Oct.
Interference Traps for Television (Finley).....	70 Mar.
Modern Television Receivers (Part 1) (Kiver).....	59 Apr.
Modern Television Receivers (Part 2) (Kiver).....	74 May
Modern Television Receivers (Part 3) (Kiver).....	71 June
Modern Television Receivers (Part 4) (Kiver).....	66 July
Modern Television Receivers (Part 5) (Kiver).....	63 Aug.
Modern Television Receivers (Part 6) (Kiver).....	67 Sept.
Modern Television Receivers (Part 7) (Kiver).....	63 Oct.
Modern Television Receivers (Part 8) (Kiver).....	70 Nov.
Modern Television Receivers (Part 9) (Kiver).....	68 Dec.
New Test Equipment Speeds Video Servicing (Liebscher).....	44 July
Simplified Side Band Amplifiers (Burroughs).....	58 Oct.
Stagger Tuned Video I.F. Systems..	55 Oct.
Television Installation (Part 5) (Waye).....	57 Jan.
Television Installation (Part 6) (Waye).....	54 Feb.
Trap Circuits for Television Receivers.....	58 Sept.

-30-

"TOWN MEETINGS" SET

TWO additional meetings in the current series of Town Meetings of Radio Technicians have been scheduled for Atlanta, Georgia and Los Angeles.

The conference in Atlanta is being held January 31 and February 1 and 2 at the Municipal Auditorium in that city. The meeting in the Roger Young Auditorium, Los Angeles will take place February 28 and March 1 and 2.

The Town Meetings are part of a national program designed to help the radio repairman in major television centers equip himself for television. The meetings have a double purpose, i.e., to make available to the repairman information which will permit him to manage his business more expertly and second to give him the latest and most authoritative information on television.

The meetings are sponsored by the Radio Parts Industry Coordinating Committee made up of members from the RMA, EP & EM, the Sales Managers Club, and the WCMA.

-30-

January, 1949

EICO INSTRUMENTS IN KIT FORM

"The Same High Quality at New Low Prices!"



HIGH PRECISION VACUUM TUBE VOLTMETER Model 221K \$23.95 Complete Kit

THE MOST USEFUL TOOL ON YOUR RADIO BENCH! D.C. and A.C. ranges 0-5, 10, 100, 500, and 1000 volts. Ohmmeter ranges from .2 ohms to 1,000 megohms in steps of Rx1, Rx10, Rx100, Rx1,000 and Rx1 megohm. Db scale from -20 to +55 Db in 5 ranges. D.C. input resistance is 25 megohms. A.C. input impedance is over 1 1/2 megohms. Diode A.C. rectifier for greater accuracy range to 30 Kc. Large, rugged, 4 1/2" meter with all A.C. and D.C. readings on one simple scale. All multiplier resistors matched to 1% accuracy. Complete with 6H6, 6X5, 6SN7 tubes and test prods. All numbers etched into panel; can never rub off. Heavy gauge steel cabinet. Size: 9 1/4" x 6" x 5". Shipping Wt. 10 lbs. NOTHING ELSE TO BUY!

and wider frequency range to 30 Kc. Large, rugged, 4 1/2" meter with all A.C. and D.C. readings on one simple scale. All multiplier resistors matched to 1% accuracy. Complete with 6H6, 6X5, 6SN7 tubes and test prods. All numbers etched into panel; can never rub off. Heavy gauge steel cabinet. Size: 9 1/4" x 6" x 5". Shipping Wt. 10 lbs. NOTHING ELSE TO BUY!

ASSEMBLED VTVM

Model 221—Includes all advantages of above. Completely assembled, hand calibrated and tested, and ready to use, at the amazingly low price of..... \$49.95

SENSATIONAL PRICE REDUCTION! Model 113-A Multi-Analyst


Completely assembled Now for the First Time..... \$69.95

A Complete VTVM that follows signal from antenna to speaker! Extremely sensitive wide range AUDIBLE signal tracer. 6 tubes—gain over 90 in probe alone! Limited quantity—order NOW!



Pocket VOLT-OHM-MILLIAMMETER COMPLETE KIT

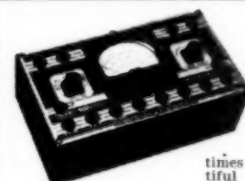Model 511-K A "MUST" FOR EVERY SERVICE-MAN! The small, handy instrument that every repairman uses a thousand times a day. Large, 3" meter, beautiful etched panel. Simple to assemble. A PERFECT KIT FOR



BEGINNERS. Ranges, DC-0/5/50/250/500/2500 volts, AC-0/10/100/500/1000 volts. Output-0/10/100/500/1000 volts. DC Ma.—0/1/10. DC Amps.—0/1/10. Ohmmeter—0/500/100,000 ohms/0/1 meg. Db meter -8 to +55 Db. \$14.95

ASSEMBLED—READY TO USE

Model 511—Completely wired, tested and assembled at the factory. Rugged, built for heavy duty. \$17.95

All prices shown above are FOB factory, Brooklyn, N. Y. If Your Jobber is Out of Stock, Order Directly from Us, Mentioning His Name

ELECTRONIC INSTRUMENT CO., Inc.

377 BLAKE AVENUE

We Welcome School Inquiries—Special Discounts to Quantity Users


BROOKLYN 12, N. Y.



EASY-TO-FOLLOW SCHEMATIC & PICTORIAL DIAGRAMS

Included with each kit. It's easy to assemble these precision instruments in one evening!

OSCILLOSCOPE

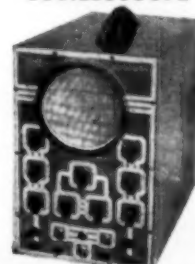

Model 400-K Indispensable for AM, FM, and TELEVISION. Horizontal sweep circuit 15 to 30,000 cycles. All controls on front panel. Linear sweep with 884 gas triode. Graph screen for measuring peak to peak voltage. Frequency response of horizontal and vertical amplifiers from 50 cycles to 50 Kc. Input impedance 1 megohm and 50 mmfd. Etched panel for long life. Tube complement: 2-6SJ7, 2-5Y3, 1-884, 1-5BP1. Provision for external synchronization, test voltage and intensity modulation. Deflection sensitivity: .50 volts per inch full gain. Detailed instructions and pictorial diagrams included. NOTHING ELSE TO BUY! \$39.95

Size: 8 1/2" W x 13" H x 17" D. Shpg. wt. 40 lbs. In Kit Form

COMPLETELY FACTORY WIRED OSCILLOSCOPE

Model 400—Same as above but wired, tested and assembled. A sturdy well-designed instrument, ready to use on your work bench. Don't wait, order NOW! \$69.95

RF PROBE

Model P-75K germanium crystal probe for visual RF signal tracing and measurements to over 200 megacycles. Can be used with models 221, 113A and 400 Eico instrument shown above (state which when ordering). \$3.75

IN KIT FORM..... Model P-75 RF probe same as above but factory wired, ready to operate...\$7.50

NEW PAINTED LEARN FUN CIRCUITS PROFIT

Conducting and Resistance Paints Now Available to the Experimenter

Be first to use this real aid in DESIGNING, TESTING, and REPAIRING modern electronic circuits. Paint working-circuits over your rough sketches and on any insulating base. Most new radios and hearing aids have partly printed circuits. High instruction value for colleges. Standard Kit, \$5, has Copper Conducting Paint, Low, Medium, and High Resistance Paints. Super Kit, \$5, has above plus Silver Conducting Paint, Insulating Lacquer, and Solvent and Brush Cleaner. Free Manual with each. Postpaid in U.S.A. Free Literature. Just jot down name, address, and desired kit; and send with cash or M.O. to MICROCIRCUITS COMPANY, Dept. 4D, New Buffalo, Michigan.

WANTED—Western Electric Carrier Telephone and Telegraph Equipment and Components. Filters, repeating coils, transformers, equalizers. Types CFI, CF2, H, C, and other carrier equipment. Telephone and telegraph repeaters.

Box 450, Radio & Television News, 185 N. Wabash, Chicago, Illinois